

Modeling and Control of Three-Phase PWM Converters

Dushan Boroyevich

Virginia Tech, Blacksburg, Virginia, USA

presented at:

PECon 2008

The 2nd IEEE International Power & Energy Conference
Johor Bahru, MALAYSIA
30 November 2008



Outline


**PECon
2008**

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**


- 6. More Complex Converters**

DB-2

First Three-Phase Converters

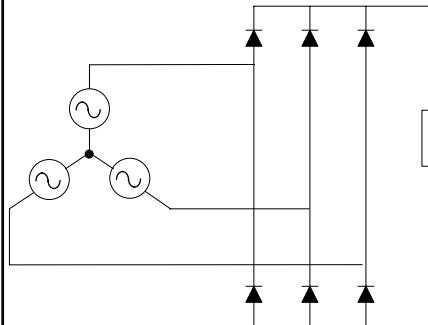


Diode Rectifier

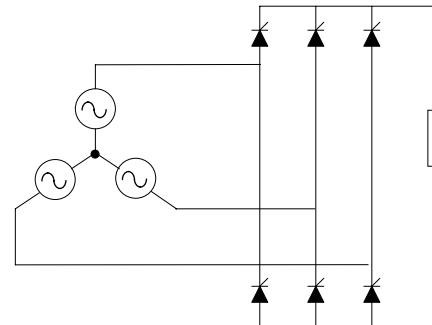

SCR Rectifier

DB-3


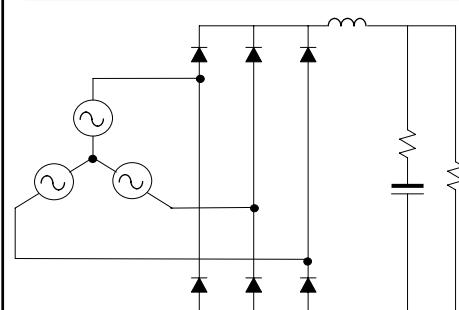
Three-Phase Diode Rectifier with Current Load



$$v_a = V_{am} \cos(\omega t)$$

$$v_b = V_{am} \cos(\omega t - \frac{2\pi}{3})$$

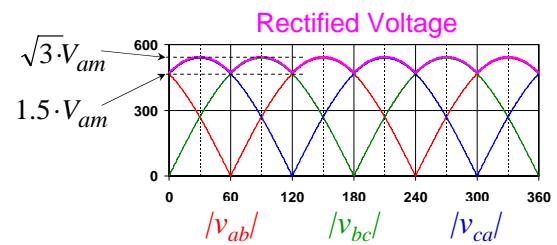
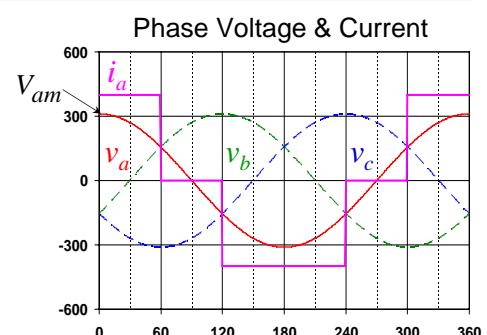
$$v_c = V_{am} \cos(\omega t + \frac{2\pi}{3})$$



DB-4


Three-Phase Diode Rectifier with Capacitive Load

Per phase load current

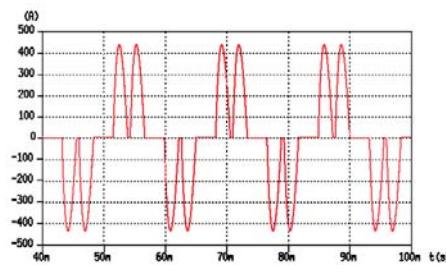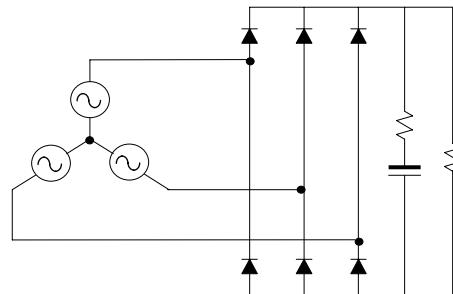


DB-5

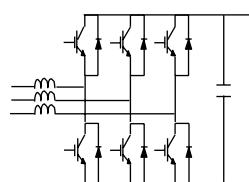
Three-Phase Pulse Width Modulated (PWM) Converters




Boost Rectifier

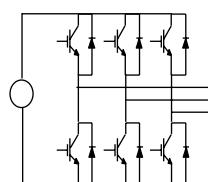

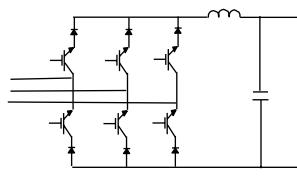Buck Inverter
Voltage Source Inverter (VSI)



Buck Rectifier

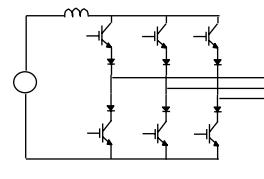

Boost Inverter
Current Source Inverter (CSI)

DB-6


Three-Phase Applications

- AC Motor Drives



- VSI with uncontrolled rectifier or CSI with SCR rectifier
- First and still the most common application
- Regulated output ac voltage or current (amplitude and frequency)
- Usually only unidirectional power flow

- Power Factor Correction

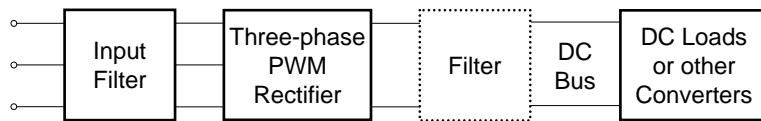


- Adjustable input displacement factor
- Regulated dc bus voltage

DB-7


Three-Phase Applications

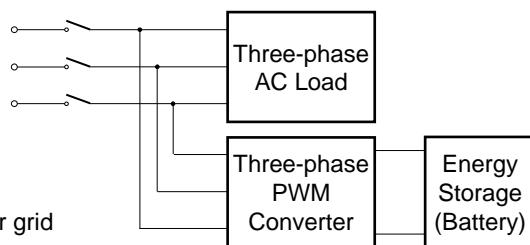- Uninterruptible Power Supply (UPS) – Parallel



- High efficiency
- Power interruption
- No power quality improvement to source or grid

- Uninterruptible Power Supply – Series

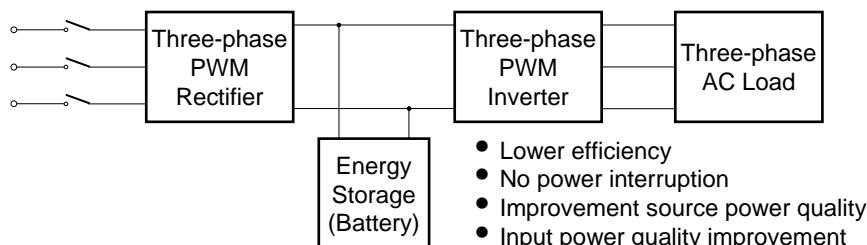


- Lower efficiency
- No power interruption
- Improvement source power quality
- Input power quality improvement

DB-8


Three-Phase Applications

- Active Filters

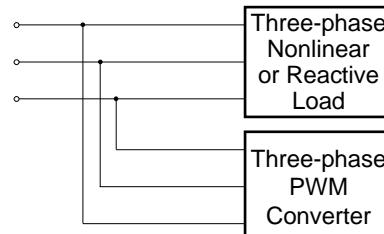- Power factor control
- Reduced current distortion
- Improved damping
- Utility applications (e.g. STATCOM)




- AC-AC Power Conversion

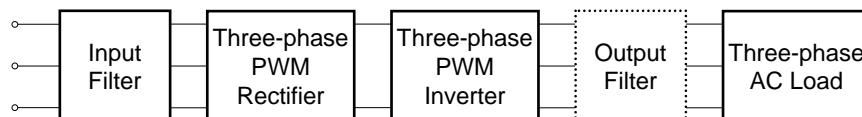

- Cascade connection of Boost rectifier and VSI or Buck rectifier and CSI
- Adjustable displacement factor at input and output
- Bidirectional power flow
- Utility applications (e.g. UPFC)

DB-9

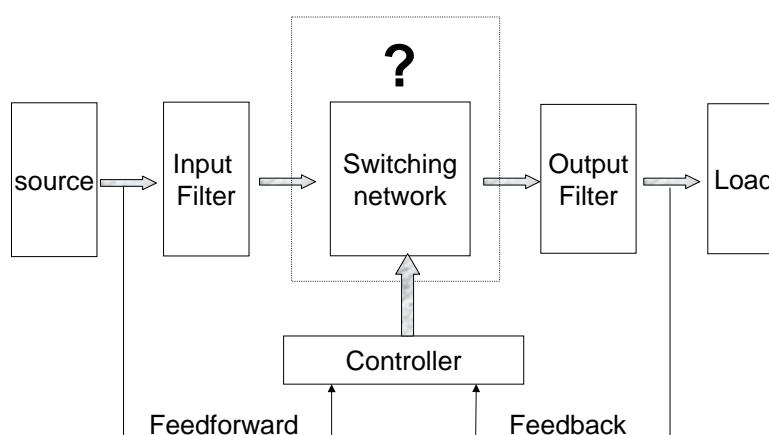Generalized Structure of A Power Converter



- Switching network is discontinuous and nonlinear

DB-10

Motivation

- Three-phase PWM converters below 100 kW operate with relatively high switching frequency (20 kHz - 100 kHz)
 - Elimination of audible noise
 - Reduction of the size of reactive components
 - **Significant improvement in waveform quality and closed-loop performance**




1. MODELING
2. CONTROL DESIGN

Only systems with switching frequency much higher than the line frequency will be studied!

DB-11


Modeling

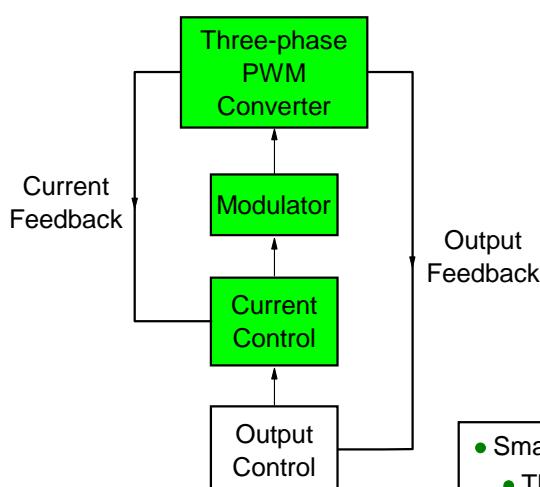

- Small-signal modeling of
 - Three-phase PWM converters
 - Three-phase modulator
 - Current controllers

DB-12

Control Design

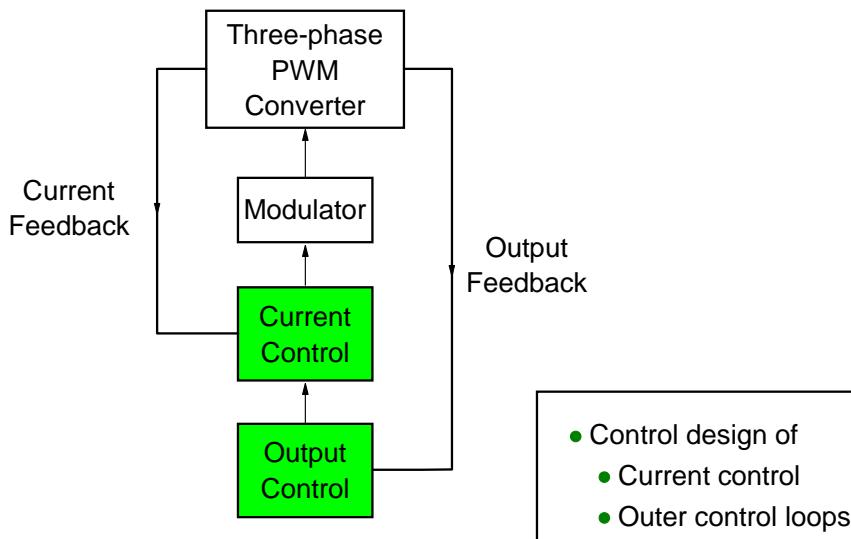

DB-13


Steps in Modeling of Three-Phase PWM Converters

1. Switching model
 - Time-discontinuous
 - Time-varying
 - Non-linear
2. Average model in stationary coordinates
 - Time-continuous
 - Time-varying
 - Non-linear
3. Average model in rotating (synchronous) coordinates
 - Time-continuous
 - Time-invariant
 - Non-linear
4. Small-signal model
 - Time-continuous
 - Time-invariant
 - Linear

DB-14

Focus

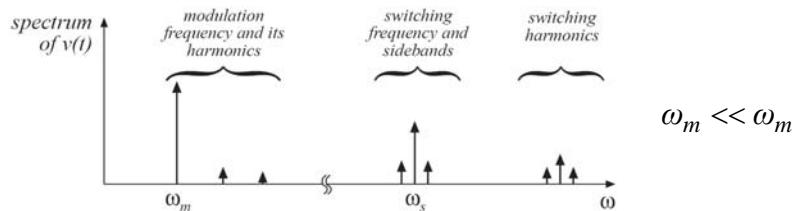- Power converter modeling for control design!
- Only converters utilizing high-frequency synthesis:



- Minor emphasis on modulation
- Only classical, small-signal control approach
- No power stage design and optimization
- No power device discussion
- No topology evaluation, only control implications
- No application considerations

DB-15


Outline

PECon
2008


1. Introduction
 - Vector representation of three-phase variables
2. Switching Modeling and PWM
3. Average Modeling
4. Small-Signal Modeling
5. Closed-Loop Control Design
6. More Complex Converters

DB-16


Three-Phase Circuits - Source

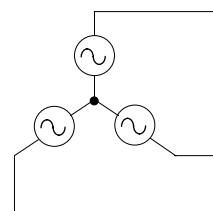

Y-connection

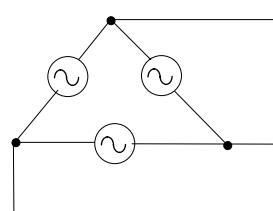


Δ -connection

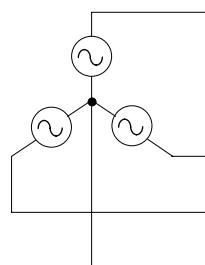


3-phase 4-wire

DB-17


Three-Phase Circuits - Load

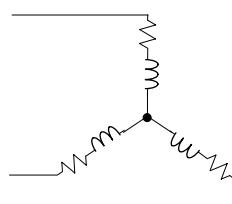

Y-connection

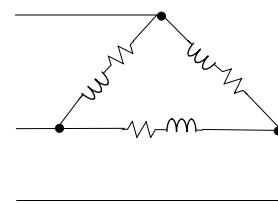

Δ -connection

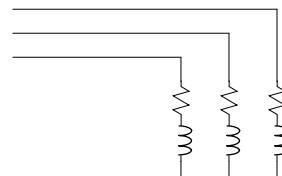


3-phase 4-wire

DB-18

Three-Phase Variables

Y-connection

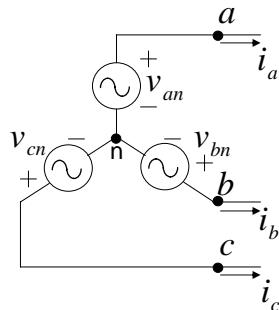

$$v_{ab} = v_a - v_b$$

$$v_{bc} = v_b - v_c$$

$$v_{ca} = v_c - v_a$$

$$i_a = i_{ca} - i_{ab}$$

$$i_b = i_{ab} - i_{bc}$$


$$i_c = i_{bc} - i_{ca}$$

$$i_a + i_b + i_c \equiv 0$$

$$v_{ab} + v_{bc} + v_{ca} \equiv 0$$

$$v_{an} + v_{bn} + v_{cn} \neq 0$$

Δ -connection

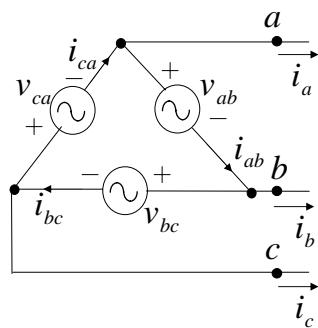


$$i_a + i_b + i_c \equiv 0$$

$$v_{ab} + v_{bc} + v_{ca} \equiv 0$$

$$i_{ab} + i_{bc} + i_{ca} \neq 0$$


DB-19

Sinusoidal, Balanced, Symmetrical

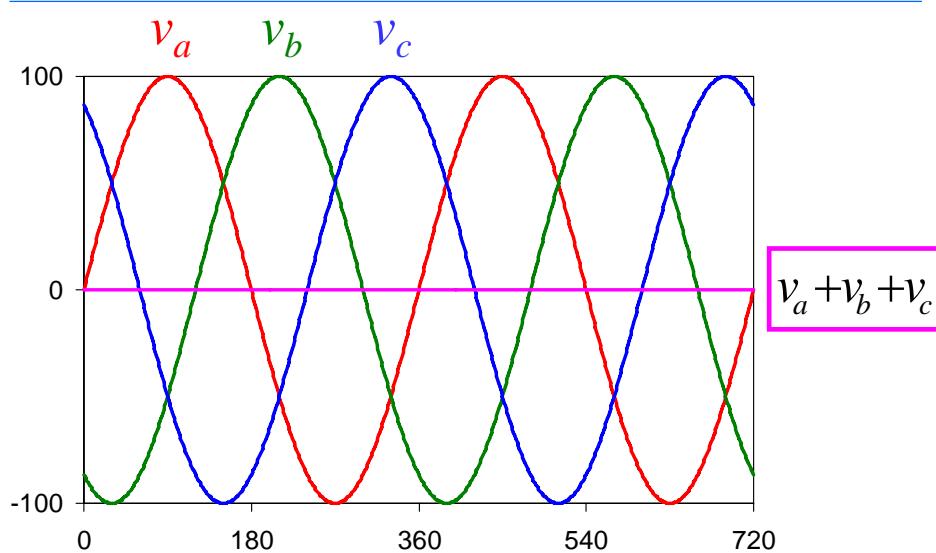


DB-20

Non-sinusoidal, Balanced, Symmetrical

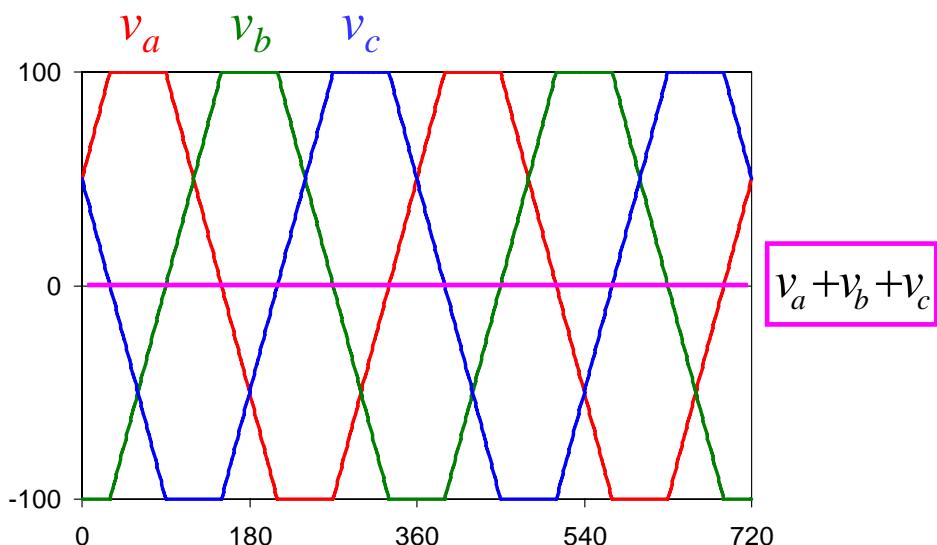


DB-21

Non-sinusoidal, Unbalanced, Symmetrical

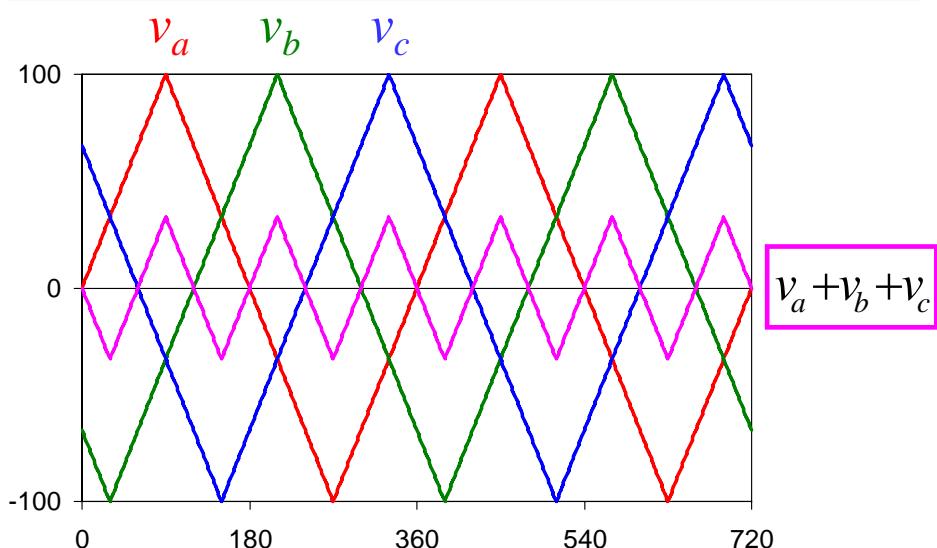


DB-22

Non-sinusoidal, Balanced, Asymmetrical

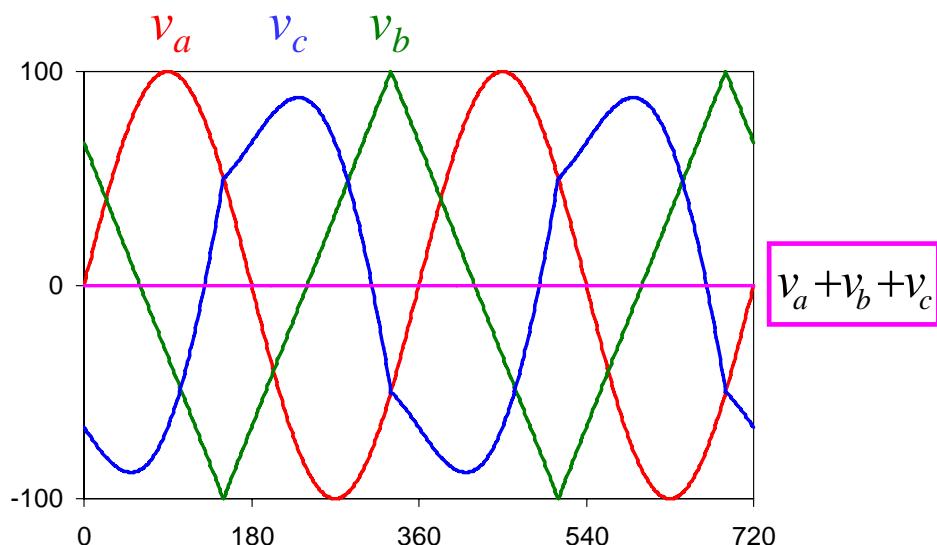

DB-23

Non-sinusoidal, Unbalanced, Asymmetrical

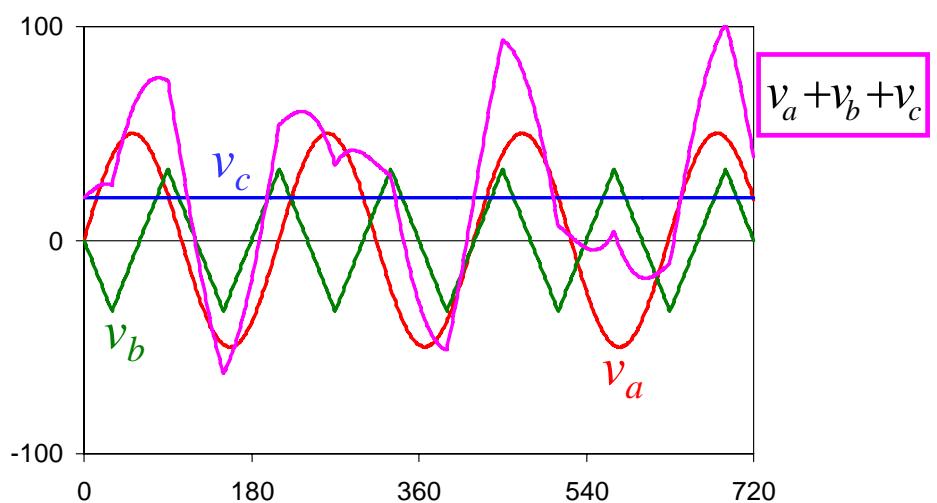

DB-24


Vector Representations of Three-Phase Variables

Euclid vector representations

$$\vec{v}(t) = \begin{bmatrix} v_a(t) \\ v_b(t) \\ v_c(t) \end{bmatrix} \quad \vec{i}(t) = \begin{bmatrix} i_a(t) \\ i_b(t) \\ i_c(t) \end{bmatrix}$$

Euclidean Space:

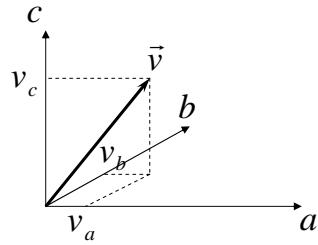
$$\vec{u}_a = \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} \quad \vec{u}_b = \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix} \quad \vec{u}_c = \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}$$



DB-25

Vector Multiplication and Norms in Euclidean Spaces

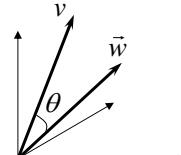- Inner product: $\langle \vec{v}, \vec{w} \rangle = \vec{v}^T \vec{w} = \vec{w}^T \vec{v} = \sum_{i=1}^n v_i w_i$



- “Dot” product: $\langle \vec{v}, \vec{w} \rangle = \|\vec{v}\| \cdot \|\vec{w}\| \cdot \cos \theta$

- “Cross” product: $\|\vec{v} \times \vec{w}\| = \|\vec{v}\| \cdot \|\vec{w}\| \cdot \sin \theta$

- Vector norm (length):

$$\|\vec{v}\| = \sqrt{\langle \vec{v}, \vec{v} \rangle^{\frac{1}{2}}} = \sqrt{\sum_{i=1}^n v_i^2} = \sqrt{v_1^2 + v_2^2 + \dots + v_n^2}$$

- Norm of a matrix: $\|\mathbf{A}\| = \max_{\forall \vec{x} \neq 0} \frac{\|\mathbf{A}\vec{x}\|}{\|\vec{x}\|}$

DB-26

Change of Coordinates

- Multiplication of a vector with any nonsingular matrix, \mathbf{T} , of the same order:


$$\vec{v}_{xyz} = \mathbf{T} \cdot \vec{v}_{abc}$$

is equivalent to the representation of the same vector in a different coordinate system (xyz), whose unit vectors have the following coordinates in the original coordinate system (abc):

$$\vec{u}_x \text{ in } abc = \mathbf{T}^{-1} \cdot \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} \quad \vec{u}_y \text{ in } abc = \mathbf{T}^{-1} \cdot \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix} \quad \vec{u}_z \text{ in } abc = \mathbf{T}^{-1} \cdot \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}$$

- If $\langle \vec{u}_x, \vec{u}_y \rangle = \langle \vec{u}_y, \vec{u}_z \rangle = \langle \vec{u}_z, \vec{u}_x \rangle = 0$, new coordinates are also orthogonal.

DB-27

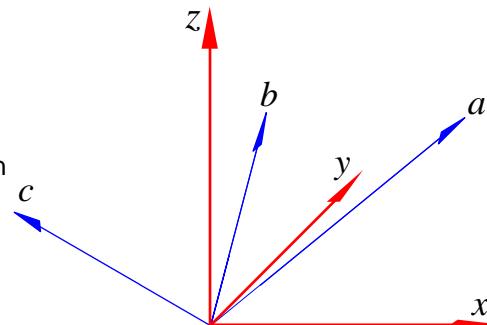


Example: Balanced Three-Phase Voltages in abc Space

$$v_a = \cos t$$

$$v_b = \cos(t - \frac{2\pi}{3})$$

$$v_c = \cos(t + \frac{2\pi}{3})$$
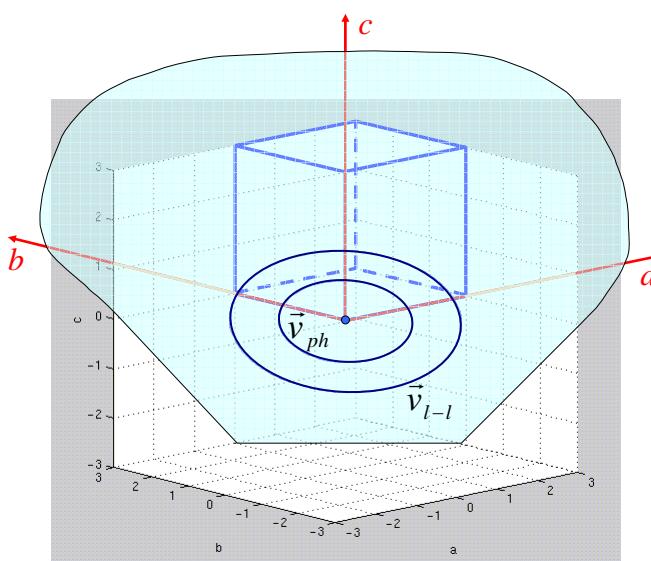
$$\vec{v}_{ph} = \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$$



DB-28


Change of Coordinates (abc to $\alpha\beta\gamma$)

$$i_a + i_b + i_c \equiv 0 \quad v_{ab} + v_{bc} + v_{ca} \equiv 0$$

This defines a 2-dimensional subspace χ , perpendicular to the vector $[1 \ 1 \ 1]^T$ in abc -space.

$\alpha\beta\gamma$ -space is traditionally defined by:

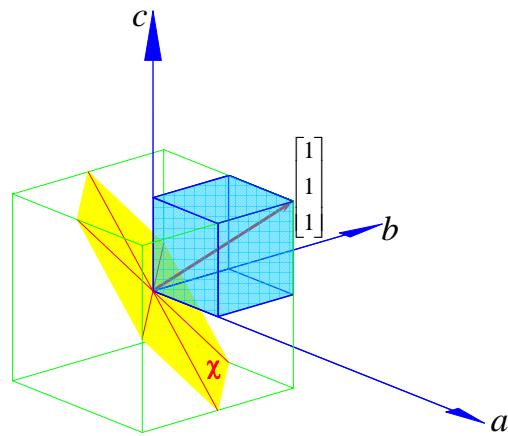- α -axis is chosen as projection of the a -axis onto χ ,
- γ -axis is co-linear with vector $[1 \ 1 \ 1]^T$
- β -axis is defined by right-hand rule.



DB-29

Transformation Matrix $T_{\alpha\beta\gamma / abc}$


The transformation matrix

$$\| T_{\alpha\beta\gamma / abc} \| = 1$$

$$T_{\alpha\beta\gamma / abc} = \sqrt{\frac{2}{3}} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \end{bmatrix}$$

$$\vec{v}_{\alpha\beta\gamma} = T_{\alpha\beta\gamma / abc} \cdot \vec{v}_{abc}$$
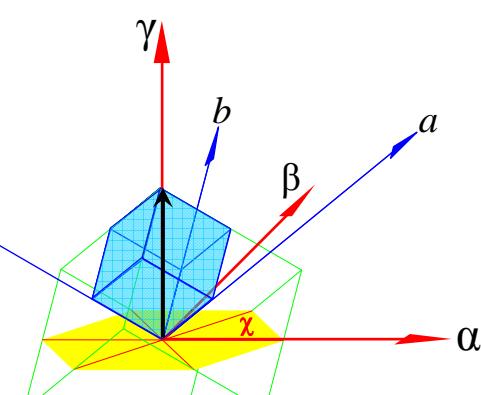
$$\vec{i}_{\alpha\beta\gamma} = T_{\alpha\beta\gamma / abc} \cdot \vec{i}_{abc}$$



Example:

$$\vec{x}_{abc} = \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} \Rightarrow \vec{x}_{\alpha\beta\gamma} = \begin{bmatrix} 0 \\ 0 \\ \sqrt{3} \end{bmatrix}$$

DB-30

Transformation Matrix $T_{abc/\alpha\beta\gamma}$

$$T_{abc/\alpha\beta\gamma} = T_{\alpha\beta\gamma/abc}^{-1} = T_{\alpha\beta\gamma/abc}^T = \sqrt{\frac{2}{3}} \begin{bmatrix} 1 & 0 & \frac{1}{\sqrt{2}} \\ -\frac{1}{2} & \frac{\sqrt{3}}{2} & \frac{1}{\sqrt{2}} \\ -\frac{1}{2} & -\frac{\sqrt{3}}{2} & \frac{1}{\sqrt{2}} \end{bmatrix}$$

$$\vec{v}_{abc} = T_{abc/\alpha\beta\gamma} \cdot \vec{v}_{\alpha\beta\gamma}$$

$$\vec{i}_{abc} = T_{abc/\alpha\beta\gamma} \cdot \vec{i}_{\alpha\beta\gamma}$$


DB-31

Example: Balanced Three-Phase Voltages in $\alpha\beta\gamma$ Space

$$v_a = \cos t \quad v_b = \cos(t - \frac{2\pi}{3}) \quad v_c = \cos(t + \frac{2\pi}{3})$$


$$\vec{v}_{abc} = \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$$
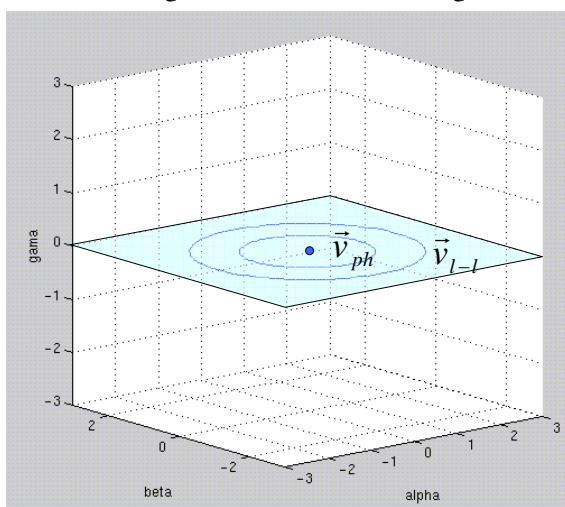
$$\vec{v}_{\alpha\beta\gamma} = T_{\alpha\beta\gamma/abc} \cdot \vec{v}_{abc}$$



DB-32

Example: State-Space Equations

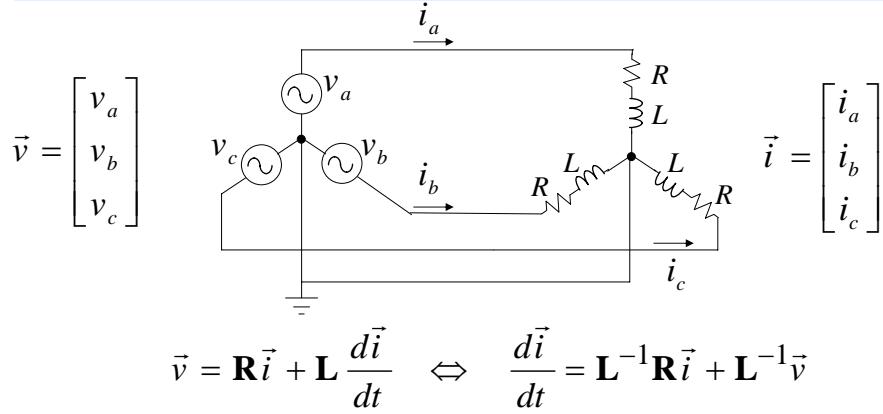


\vec{v} and \vec{i} are sinusoidal in steady-state! Find a coordinate transformation:

$\vec{v}_x = T_x \cdot \vec{v}$, $\vec{i}_x = T_x \cdot \vec{i}$, such that \vec{v}_x and \vec{i}_x are constant

in steady state, and T_x is differentiable and invertible.

DB-33

Example: State-Space Equations

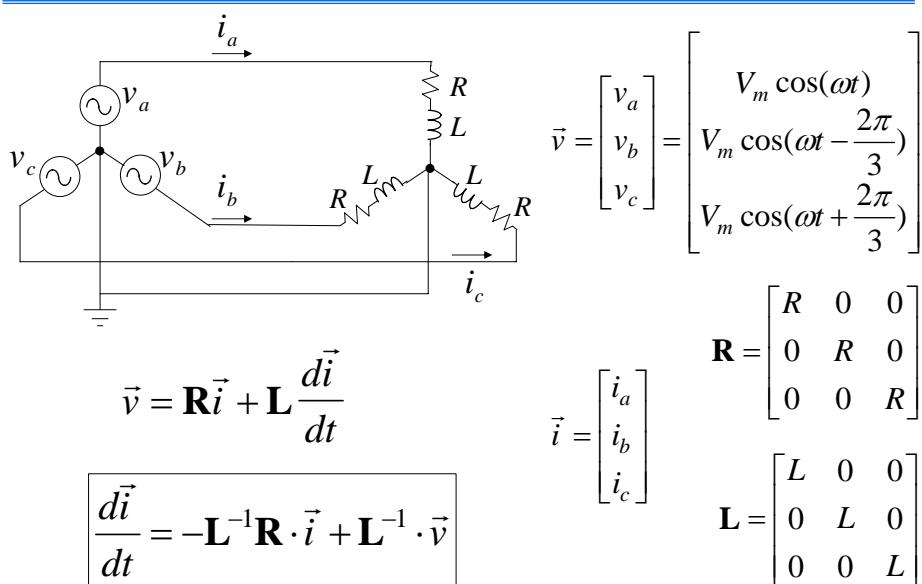

DB-34



Example: State-Space Equations – Solution

$$\vec{i}(t) = e^{-\mathbf{L}^{-1}\mathbf{R} \cdot t} \cdot \vec{i}(0) + \int_0^t e^{-\mathbf{L}^{-1}\mathbf{R} \cdot (t-\tau)} \cdot \mathbf{L}^{-1} \cdot \vec{v}(\tau) \cdot d\tau$$

Natural Response

Forced Response

$$\vec{i}(t) = \begin{bmatrix} i_a(0) \\ i_b(0) \\ i_c(0) \end{bmatrix} \cdot e^{-\frac{R}{L}t} + \frac{V_m}{Z} \cdot \begin{bmatrix} \cos(\omega t - \phi) - \frac{R}{Z} \cdot e^{-\frac{R}{L}t} \\ \cos(\omega t - \frac{2\pi}{3} - \phi) + \frac{R + \sqrt{3} \cdot \omega L}{2Z} \cdot e^{-\frac{R}{L}t} \\ \cos(\omega t + \frac{2\pi}{3} - \phi) + \frac{R - \sqrt{3} \cdot \omega L}{2Z} \cdot e^{-\frac{R}{L}t} \end{bmatrix}$$

where per-phase impedance, \mathbf{Z} , at the source frequency, ω , is defined as:

$$\mathbf{Z} = R + j\omega L = Z \cdot e^{j\phi} \quad Z = \sqrt{R^2 + \omega^2 L^2} \quad \phi = \arctan \frac{\omega L}{R}$$

DB-35



Example: State-Space Equations – Steady State Solution

$$\lim_{t \rightarrow \infty} [\vec{i}(t)] = I_m \cdot \begin{bmatrix} \cos(\omega t - \phi) \\ \cos(\omega t - \frac{2\pi}{3} - \phi) \\ \cos(\omega t + \frac{2\pi}{3} - \phi) \end{bmatrix} \quad I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \quad \phi = \arctan \frac{\omega L}{R}$$

$$\lim_{t \rightarrow \infty} \left[\frac{d\vec{i}}{dt} \right] \neq 0$$

Want to find change of variables:


$$\vec{v}_x = T_x \cdot \vec{v} \quad \text{where: } \vec{v}_x \text{ and } \vec{i}_x \text{ are constant in steady state}$$

$$\vec{i}_x = T_x \cdot \vec{i} \quad T_x : \text{differentiable and invertible}$$

DB-36

Transformation Matrix $T_{dq/\alpha\beta}$

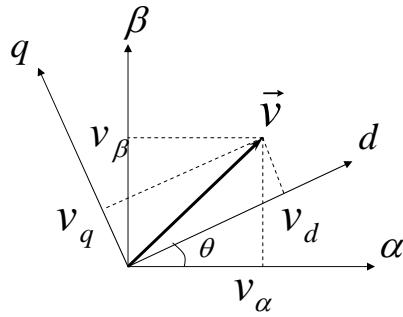A rotating vector in $\alpha\beta\gamma$ space can be a constant vector in a rotating space



$$\begin{bmatrix} v_d \\ v_q \end{bmatrix} = \begin{bmatrix} \cos \theta & \sin \theta \\ -\sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}$$

$$\theta = \int_0^t \omega(\tau) d\tau + \theta(0)$$

Where ω is the rotating speed

DB-37

Transformation Matrix $T_{dq0/\alpha\beta\gamma}$

Preserve the same third axis, that is 0-axis is the same as γ -axis

$$\begin{bmatrix} v_d \\ v_q \\ v_0 \end{bmatrix} = \begin{bmatrix} \cos \theta & \sin \theta & 0 \\ -\sin \theta & \cos \theta & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_\alpha \\ v_\beta \\ v_\gamma \end{bmatrix}$$

Therefore

$$T_{dq0/\alpha\beta\gamma} = \begin{bmatrix} \cos \theta & \sin \theta & 0 \\ -\sin \theta & \cos \theta & 0 \\ 0 & 0 & 1 \end{bmatrix} \quad \| T_{dq0/\alpha\beta\gamma} \| = 1$$

$$T_{\alpha\beta\gamma/dq0} = T_{dq0/\alpha\beta\gamma}^{-1} = T_{dq0/\alpha\beta\gamma}^T$$

DB-38

Transformation Matrix $T_{dq0/abc}$

$$\vec{v}_{dq0} = T_{dq0/\alpha\beta\gamma} \cdot \vec{v}_{\alpha\beta\gamma} = T_{dq0/\alpha\beta\gamma} \cdot T_{\alpha\beta\gamma/abc} \cdot \vec{v}_{abc}$$

Therefore

$$\vec{v}_{dq0} = T_{dq0/abc} \cdot \vec{v}_{abc}$$

where

$$T_{dq0/abc} = T_{dq0/\alpha\beta\gamma} \cdot T_{\alpha\beta\gamma/abc} \quad \text{Park's Transformation}$$

$$= \sqrt{\frac{2}{3}} \begin{bmatrix} \cos\theta & \sin\theta & 0 \\ -\sin\theta & \cos\theta & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \end{bmatrix} = \sqrt{\frac{2}{3}} \begin{bmatrix} \cos\theta & \cos(\theta - \frac{2\pi}{3}) & \cos(\theta + \frac{2\pi}{3}) \\ -\sin\theta & -\sin(\theta - \frac{2\pi}{3}) & -\sin(\theta + \frac{2\pi}{3}) \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \end{bmatrix}$$

$$\| T_{dq0/abc} \| = 1 \quad T_{abc/dq0} = T_{dq0/abc}^{-1} = T_{dq0/abc}^T$$


DB-39

Example: Balanced Three-Phase Voltages in $dq0$ Space

$$v_a = \cos t \quad v_b = \cos(t - \frac{2\pi}{3}) \quad v_c = \cos(t + \frac{2\pi}{3})$$

$$\vec{v}_{abc} = \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$$
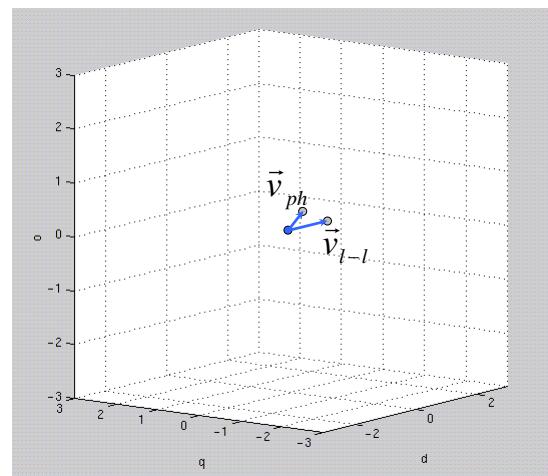
$$\vec{v}_{dq0} = T_{dq0/abc} \cdot \vec{v}_{abc}$$



DB-40

Power Definition in Three-Phase Circuits

$$\vec{p} = \vec{v} \cdot \vec{i} = \vec{v}^T \vec{i} = [v_a \quad v_b \quad v_c] \cdot \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = v_a i_a + v_b i_b + v_c i_c$$


where v & i are corresponding voltages and currents in a three-phase circuit.

It can be easily proved that:

$$v_a i_a + v_b i_b + v_c i_c = v_\alpha i_\alpha + v_\beta i_\beta + v_\gamma i_\gamma = v_d i_d + v_q i_q + v_o i_o$$

DB-41

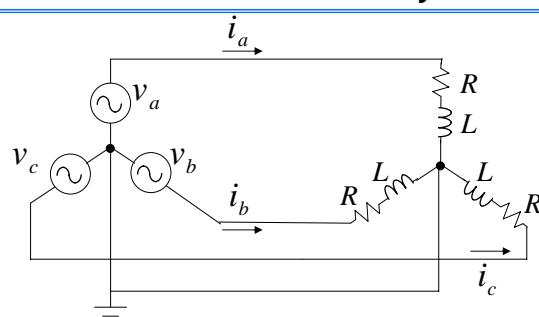Example: Power in Sinusoidal Steady State




$$\vec{v} = \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix} = \begin{bmatrix} V_{am} \cos(\omega t) \\ V_{am} \cos(\omega t - \frac{2\pi}{3}) \\ V_{am} \cos(\omega t + \frac{2\pi}{3}) \end{bmatrix} \quad \vec{i} = \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} I_{am} \cos(\omega t - \phi) \\ I_{am} \cos(\omega t - \frac{2\pi}{3} - \phi) \\ I_{am} \cos(\omega t + \frac{2\pi}{3} - \phi) \end{bmatrix}$$

where: $\phi = \arctan \frac{\omega L}{R}$

DB-42

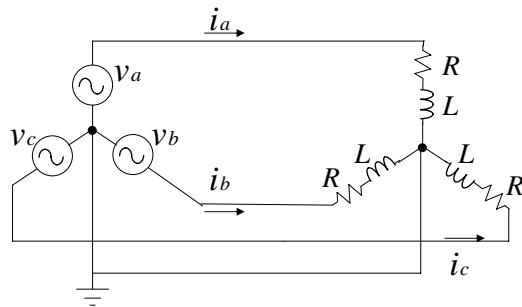Example:
Power in Sinusoidal Steady State



$$P = \|\vec{v} \cdot \vec{i}\| = \|\vec{v}\| \cdot \|\vec{i}\| \cos \phi = \frac{3}{2} V_{am} I_{am} \cos \phi$$


$$Q = \|\vec{v} \times \vec{i}\| = \|\vec{v}\| \cdot \|\vec{i}\| \sin \phi = \frac{3}{2} V_{am} I_{am} \sin \phi$$

DB-43

Phasor Representation

Phasors are defined **ONLY for sinusoidal steady state!**
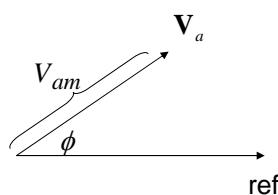
$$v_a = V_{am} \cos(\omega t + \phi) \quad \longleftrightarrow \quad \mathbf{V}_a = V_{am} \angle \phi = V_{am} \cdot e^{j\phi}$$



- Vector representation **is NOT** phasor representation!

DB-44


Phasor Representation

Phasors are defined **ONLY for sinusoidal steady state!**

Phasors are very useful for the analysis of linear systems without transients, which are excited by **constant single frequency (ω) sinusoidal generators.**

$$v_a = V_m \cos(\omega t + \phi) = \operatorname{Re}[V_m \cdot e^{j\phi}] = \operatorname{Re}[V_m \cos(\omega t + \phi) + jV_m \sin(\omega t + \phi)]$$

$$\mathbf{V}_a = \frac{V_m}{\sqrt{2}} \angle \phi = V_{rms} \cdot e^{j\phi}$$

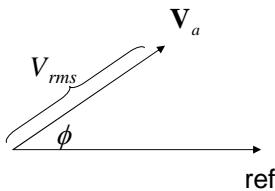
 $v_a = V_m \cos(\omega t + \phi) = \sqrt{2} \cdot \operatorname{Re}(\mathbf{V}_a \cdot e^{j\omega t})$

DB-45

Outline


PECon
2008

1. Introduction
2. Switching Modeling and PWM
 - Switching model of VSI & boost rectifier
 - Space vector modulation for VSI & boost rectifier
 - Other modulations for VSI & boost rectifier
 - Switching model and modulation for CSI & buck rectifier
3. Average Modeling
4. Small-Signal Modeling
5. Closed-Loop Control Design
6. More Complex Converters


DB-46

Boost Rectifier / Voltage Source Inverter

- Boost Rectifier

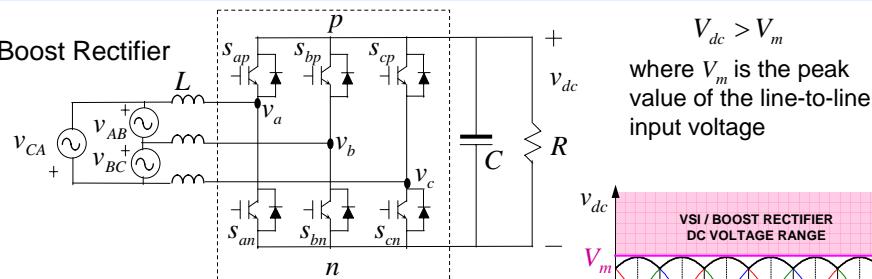



- Voltage Source Inverter (VSI)

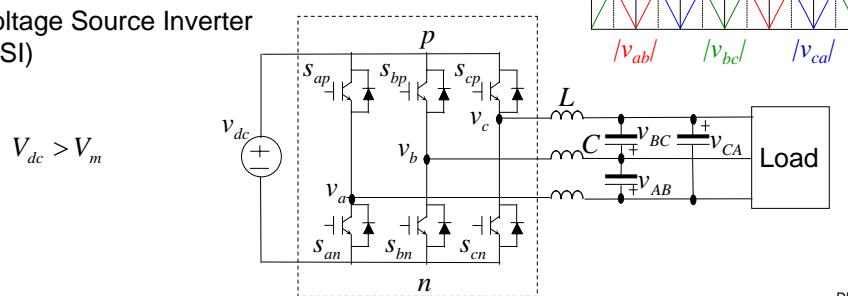


DB-47

Method of Modeling Switching Network

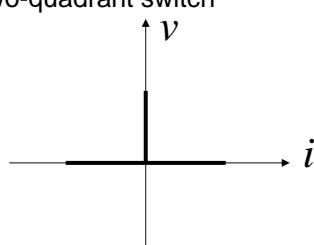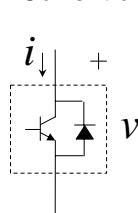Current bi-directional two-quadrant switch



Switching function:

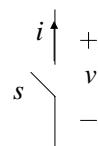

$$s = \begin{cases} 1, v = 0, \text{ if switch } s \text{ is closed} \\ 0, i = 0, \text{ if switch } s \text{ is open} \end{cases}$$

Switching constraints:


- Voltage source or capacitor cannot be shorted
- Current source or inductor cannot be open

DB-48

DC-Voltage-Unidirectional Three-Phase Switching Network

- Three-Switch (Single-Pole-Double-Throw)

Boost Rectifier
Voltage Source Inverter

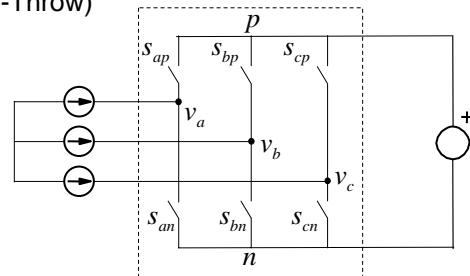


Allowed switching combinations:

$$s_{ip} + s_{in} = 1; \quad i \in \{a, b, c\}$$

- Define Voltage-Unidirectional Single-Pole-Double-Throw Switch and switching function
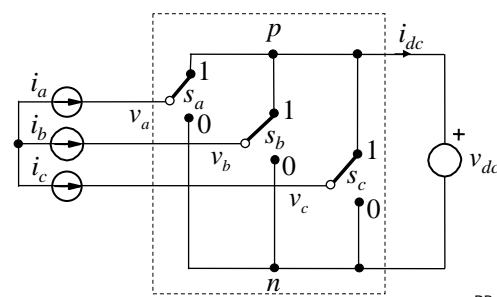
$$s_i = s_{ip} = 1 - s_{in}; \quad i \in \{a, b, c\}$$





DB-49

Development of Switching Model (Boost rectifier / Voltage source inverter)



Find the relationships:

$$v_{ab} = f_{ab}(s_{ab}, v_{dc}) \quad v_{bc} = f_{bc}(s_{bc}, v_{dc}) \quad v_{ca} = f_{ca}(s_{ca}, v_{dc})$$

$$i_{dc} = f_i(s_{ij}, i_a, i_b, i_c)$$

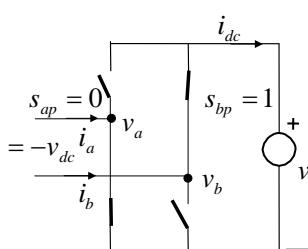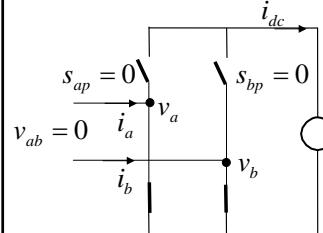
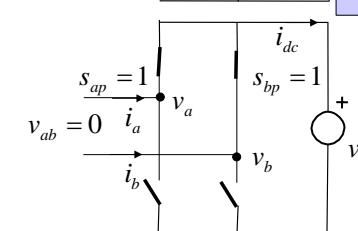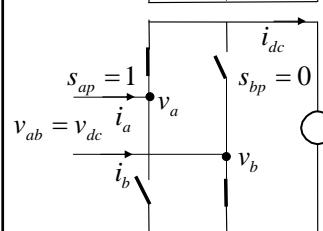
$$\begin{aligned} v_{ab} &= v_a - v_b \\ &= (s_{ap} - s_{bp})v_{dc} \\ &= s_{ab}v_{dc} \end{aligned}$$



$$i_{dc} = s_{ap}i_a + s_{bp}i_b$$


DB-50

Development of Switching Model

(Boost rectifier / Voltage source inverter)

Define phase-leg switching function
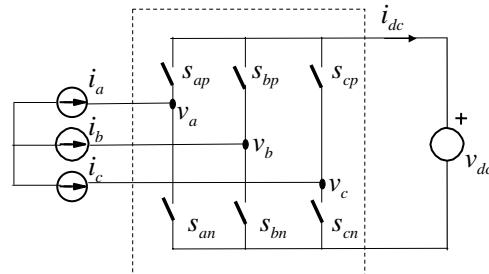
$$s_i = s_{ip} = 1 - s_{in}; \quad i \in \{a, b, c\}$$




s_a	s_b	s_c	s_a-s_b	s_b-s_c	s_c-s_a	i_{dc}	v_{ab}	v_{bc}	v_{ca}
0	0	0	0	0	0	0	0	0	0
0	0	1	0	-1	1	i_c	0	$-v_{dc}$	v_{dc}
0	1	0	-1	1	0	i_b	$-v_{dc}$	v_{dc}	0
0	1	1	-1	0	1	i_b+i_c	$-v_{dc}$	0	v_{dc}
1	0	0	1	0	-1	i_a	v_{dc}	0	$-v_{dc}$
1	0	1	1	-1	0	i_a+i_c	v_{dc}	$-v_{dc}$	0
1	1	0	0	1	-1	i_a+i_b	0	v_{dc}	$-v_{dc}$
1	1	1	0	0	0	$i_a+i_b+i_c$	0	0	0

DB-51

Development of Switching Model

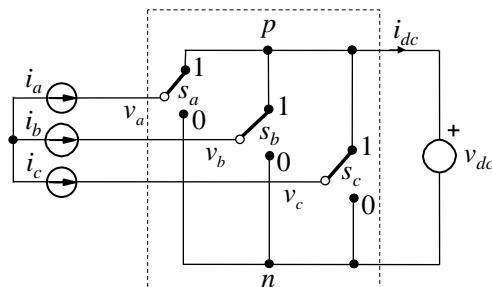(Boost rectifier / Voltage source inverter)



Instantaneous voltage equation

$$\begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix} = \begin{bmatrix} s_a - s_b \\ s_b - s_c \\ s_c - s_a \end{bmatrix} v_{dc} = \begin{bmatrix} s_{ab} \\ s_{bc} \\ s_{ca} \end{bmatrix} v_{dc}$$


Instantaneous current equation

$$i_{dc} = [s_a \quad s_b \quad s_c] \cdot \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix}$$

Note that: $s_{ab} = s_a - s_b \dots v_{ab} = v_a - v_b \dots$

DB-52

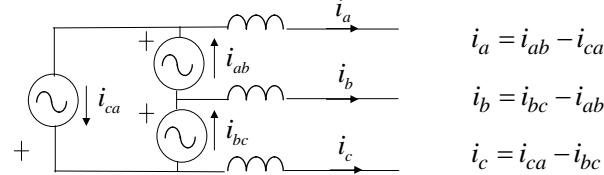Relationship Between Line-to-Line Current and Phase Current



$$\Rightarrow i_a - i_b = i_{ab} - i_{ca} - (i_{bc} - i_{ab}) = 2i_{ab} - (i_{ca} + i_{bc}) = \underset{\uparrow}{3i_{ab}}$$

Assume $i_{ab} + i_{bc} + i_{ca} = 0$


$$\Rightarrow i_{ab} = \frac{1}{3}(i_a - i_b) \quad \text{Similarly} \quad i_{bc} = \frac{1}{3}(i_b - i_c) \quad i_{ca} = \frac{1}{3}(i_c - i_a)$$

$$i_{dc} = s_a i_a + s_b i_b + s_c i_c = s_a(i_{ab} - i_{ca}) + s_b(i_{bc} - i_{ab}) + s_c(i_{ca} - i_{bc})$$

$$= i_{ab}(s_a - s_b) + i_{bc}(s_b - s_c) + i_{ca}(s_c - s_a) = [s_{ab} \quad s_{bc} \quad s_{ca}] \cdot \begin{bmatrix} i_{ab} \\ i_{bc} \\ i_{ca} \end{bmatrix}$$

DB-53

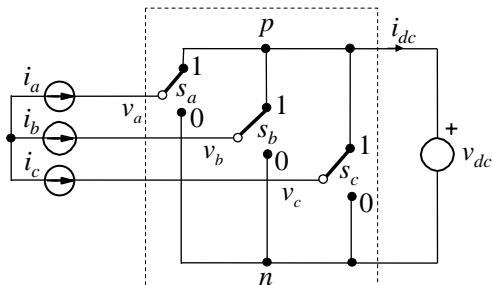Boost Rectifier / Voltage Source Inverter Switching Model



$$\vec{v}_{l-l} = \vec{s}_{l-l} \cdot \vec{v}_{dc}$$

$$\vec{i}_{dc} = \vec{s}_{l-l}^T \cdot \vec{i}_{l-l}$$

where:

$$\vec{v}_{l-l} = \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix} = \begin{bmatrix} v_a - v_b \\ v_b - v_c \\ v_c - v_a \end{bmatrix} \quad \vec{s}_{l-l} = \begin{bmatrix} s_{ab} \\ s_{bc} \\ s_{ca} \end{bmatrix} = \begin{bmatrix} s_a - s_b \\ s_b - s_c \\ s_c - s_a \end{bmatrix} \quad \vec{i}_{l-l} = \begin{bmatrix} i_{ab} \\ i_{bc} \\ i_{ca} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} i_a - i_b \\ i_b - i_c \\ i_c - i_a \end{bmatrix}$$


DB-54

1. Introduction
2. Switching Modeling and PWM

- Switching model of VSI & boost rectifier
- Space vector modulation for VSI & boost rectifier
- Other modulations for VSI & boost rectifier
- Switching model and modulation for CSI & buck rectifier

3. Average Modeling
4. Small-Signal Modeling
5. Closed-Loop Control Design
6. More Complex Converters

DB-55

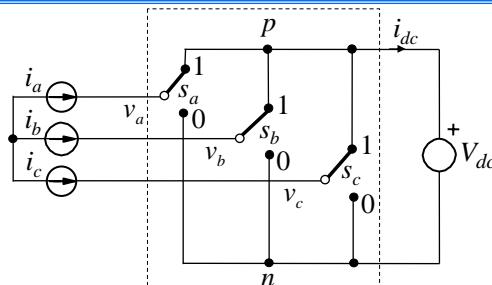
**Switching States for
Boost Rectifier / Voltage Source Inverter**


s_a	s_b	s_c	Switching state	i_{dc}	v_{ab}	v_{bc}	v_{ca}
0	0	0	<i>nnn</i>	0	0	0	0
0	0	1	<i>nnp</i>	i_c	0	$-V_{dc}$	V_{dc}
0	1	0	<i>npn</i>	i_b	$-V_{dc}$	V_{dc}	0
0	1	1	<i>npp</i>	$i_b + i_c$	$-V_{dc}$	0	V_{dc}
1	0	0	<i>pnn</i>	i_a	V_{dc}	0	$-V_{dc}$
1	0	1	<i>pnp</i>	$i_a + i_c$	V_{dc}	$-V_{dc}$	0
1	1	0	<i>ppn</i>	$i_a + i_b$	0	V_{dc}	$-V_{dc}$
1	1	1	<i>ppp</i>	$i_a + i_b + i_c$	0	0	0

DB-56

Vector Space of Line-to-Line Variables

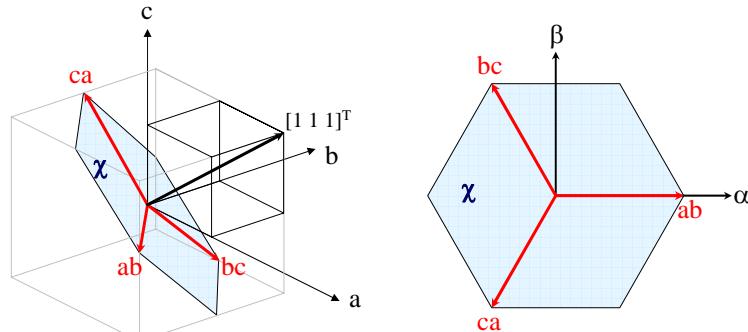- Phase variables (a, b and c) produce line-to-line variables (ab, bc and ca) in plane- χ
- Line-to-line variables (ab, bc and ca) do not have γ -component in $\alpha\beta\gamma$ -coordinate system



DB-57

Line-to-Line Voltage Space Vector

$$\begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix} \quad \text{where}$$


$$T_{\alpha\beta/abc} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix}$$

- Space vector

$$\vec{v} = \rho \cdot e^{j\theta}$$

$$\rho = \sqrt{v_\alpha^2 + v_\beta^2}$$
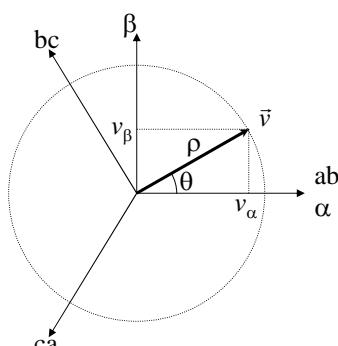
$$\theta = \tan^{-1}\left(\frac{v_\beta}{v_\alpha}\right)$$



☞ If V_m is the amplitude of balanced, symmetrical, three-phase line-to-line voltages, then $\rho = \sqrt{\frac{3}{2}} \cdot V_m$

DB-58


Switching State Vector [pnn]

$$\vec{V}_{pnn} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{pnn} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{pnn} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \cdot \begin{bmatrix} V_{dc} \\ 0 \\ -V_{dc} \end{bmatrix} = \begin{bmatrix} \sqrt{\frac{3}{2}} \cdot V_{dc} \\ \sqrt{\frac{1}{2}} \cdot V_{dc} \\ \sqrt{\frac{1}{2}} \cdot V_{dc} \end{bmatrix}$$

$$\vec{V}_{pnn} = \vec{V}_I = \rho \cdot e^{j\theta}$$

$$\rho = \sqrt{2} \cdot V_{dc}$$
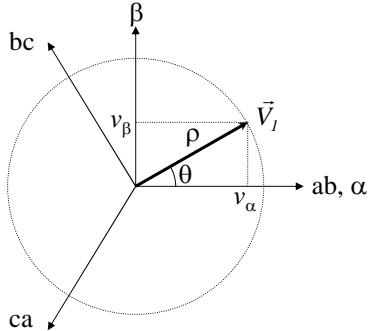
$$\theta = \tan^{-1} \left(\frac{v_\beta}{v_\alpha} \right) = 30^\circ$$



DB-59


Switching State Vector [ppn]

$$\vec{V}_{ppn} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{ppn} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{ppn} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \cdot \begin{bmatrix} 0 \\ V_{dc} \\ -V_{dc} \end{bmatrix} = \begin{bmatrix} 0 \\ \sqrt{2} \cdot V_{dc} \\ -\sqrt{2} \cdot V_{dc} \end{bmatrix}$$

$$\vec{V}_{ppn} = \vec{V}_2 = \rho \cdot e^{j\theta}$$

$$\rho = \sqrt{2} \cdot V_{dc}$$
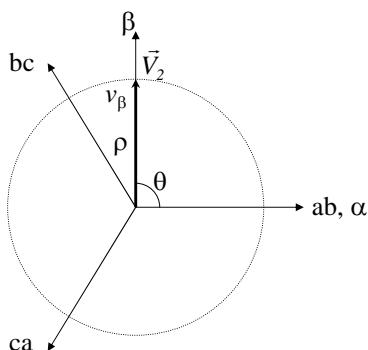
$$\theta = \tan^{-1} \left(\frac{v_\beta}{v_\alpha} \right) = 90^\circ$$




DB-60

Switching State Vector [ppp]

$$\vec{V}_{ppp} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{ppp} = T_{\alpha\beta/abc} \cdot \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{ppp} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \cdot \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$


$$\vec{V}_{ppp} = \vec{V}_o = 0$$

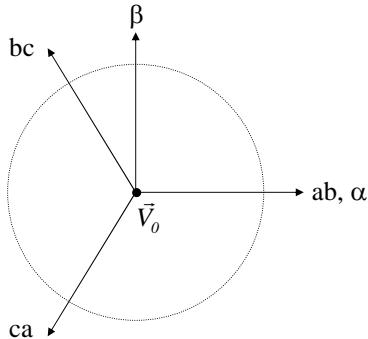

DB-61

Switching State Vectors

	ρ	$\theta (\circ)$
$\vec{V}_1[pnn]$		30
$\vec{V}_2[ppn]$		90
$\vec{V}_3[npn]$		150
$\vec{V}_4[npp]$		-150
$\vec{V}_5[nnp]$		-90
$\vec{V}_6[pnp]$		-30
$\vec{V}_o[ppp]$	0	0
$\vec{V}_o[nnn]$	0	0

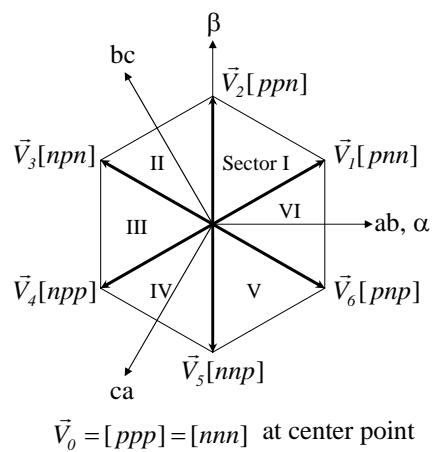

DB-62

Reference Voltage Vector, Vref

Assume $\begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}_{ref} = \begin{bmatrix} V_m \cdot \cos(\omega t) \\ V_m \cdot \cos(\omega t - 120^\circ) \\ V_m \cdot \cos(\omega t + 120^\circ) \end{bmatrix}$


$$\vec{V}_{ref} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix}_{ref} = \rho \cdot e^{j\theta}$$

where $\rho = \sqrt{v_\alpha^2 + v_\beta^2} = \sqrt{\frac{3}{2}} \cdot V_m$

$$\theta = \tan^{-1}\left(\frac{v_\beta}{v_\alpha}\right) = \omega t$$

☞ In general,
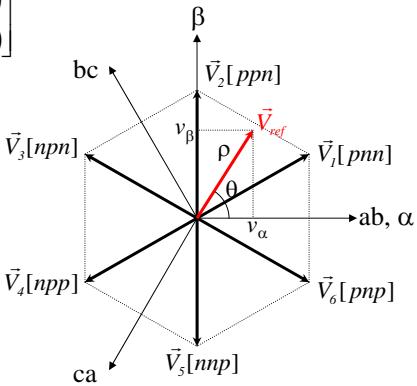
$$\vec{V}_{ref}(t) = \sqrt{\frac{3}{2}} \cdot V_m(t) \cdot e^{j\theta(t)}$$




$\vec{V}_0 = [ppp] = [nnn]$ at center point

DB-63

Definition of High Frequency Synthesis

$$\int_0^{T_S} \vec{V}_{ref} dt = \sum_i \left(\int_0^{T_i} \vec{V}_i dt \right), \quad \sum_i T_i = T_S$$

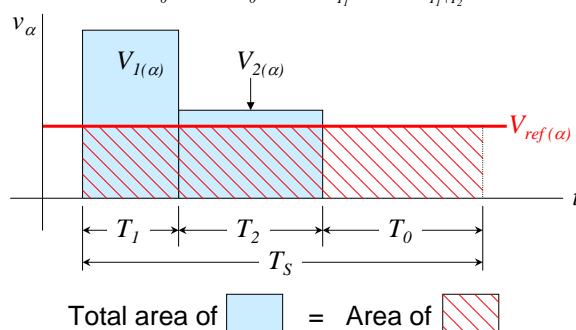☞ For example $\int_0^{T_S} \vec{V}_{ref} dt = \int_0^{T_I} \vec{V}_I dt + \int_{T_I}^{T_I+T_2} \vec{V}_2 dt + \int_{T_I+T_2}^{T_S} \vec{V}_0 dt$



DB-64

Space Vector Modulation

Step 1 : Choose desired switching state vectors to synthesize \vec{V}_{ref}







Step 2 : Calculate the duty ratios of chosen switching state vectors



Step 3 : Make the sequence of chosen switching state vectors

DB-65

Switching State Vectors

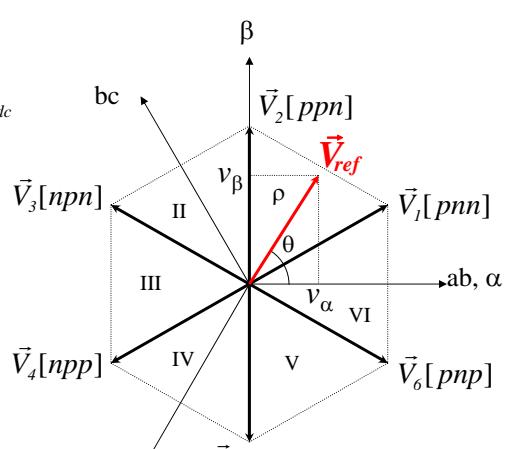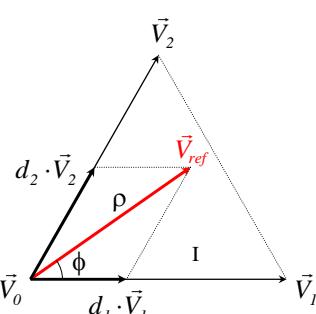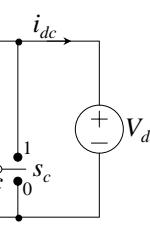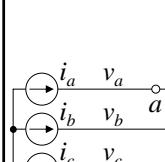

$$\vec{V}_0 = [ppp] = [nnn]$$


DB-66

Step 1 : Choice of Switching State Vectors

- Minimize the number of switching
- Minimize the harmonic distortion

Choose minimum number of switching state vectors adjacent to \vec{V}_{ref} .

\vec{V}_{ref} location	Chosen vectors
Sector I	\vec{V}_1 and \vec{V}_2
Sector II	\vec{V}_2 and \vec{V}_3
Sector III	\vec{V}_3 and \vec{V}_4
Sector IV	\vec{V}_4 and \vec{V}_5
Sector V	\vec{V}_5 and \vec{V}_6
Sector VI	\vec{V}_6 and \vec{V}_1 and \vec{V}_o

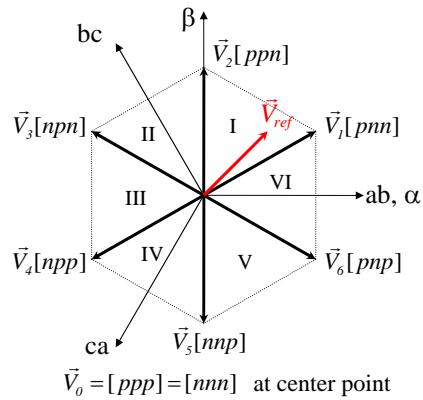

DB-67

Step 2 : Duty Ratio of Switching State Vectors at Sector I

From HF synthesis definition, $\int_0^{T_s} \vec{V}_{ref} dt = \int_0^{T_1} \vec{V}_1 dt + \int_{T_1}^{T_1+T_2} \vec{V}_2 dt + \int_{T_1+T_2}^{T_s} \vec{V}_o dt$

Assume \vec{V}_{ref} is constant in T_s , $\vec{V}_{ref} \cdot T_s = \vec{V}_1 \cdot T_1 + \vec{V}_2 \cdot T_2$


$$\rho \cdot \begin{bmatrix} \cos\phi \\ \sin\phi \end{bmatrix} \cdot T_s = \|V_1\| \cdot \begin{bmatrix} 1 \\ 0 \end{bmatrix} \cdot T_1 + \|V_2\| \cdot \begin{bmatrix} \cos 60^\circ \\ \sin 60^\circ \end{bmatrix} \cdot T_2$$

where $\phi = \theta - 30^\circ$

$$\frac{T_1}{T_s} = d_1 = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_1\|} \cdot \sin(60^\circ - \phi)$$

$$\frac{T_2}{T_s} = d_2 = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_2\|} \cdot \sin \phi$$

$$d_o = 1 - d_1 - d_2$$

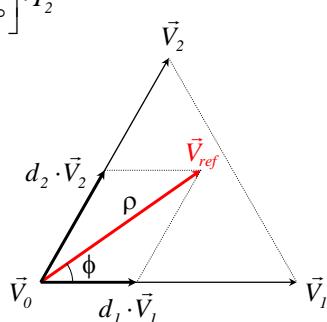

DB-68

Duty Ratio of Switching State Vectors


☞ Other sectors have the same results of duty ratio.

$$\frac{T_N}{T_S} = d_N = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_N\|} \cdot \sin(60^\circ - \phi)$$

$$\frac{T_{N+1}}{T_S} = d_{N+1} = \frac{2}{\sqrt{3}} \cdot \frac{\rho}{\|V_{N+1}\|} \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

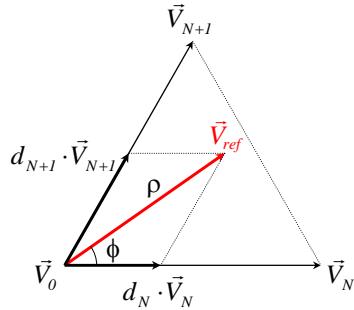where $\phi = \theta - (N-1) \cdot 60^\circ - 30^\circ$
 N : sector number (1 ~ 6)



DB-69

Modulation Index

For all the switching state vectors, $\|V_N\| = \sqrt{2} \cdot V_{dc}$ and $\rho = \sqrt{\frac{3}{2}} \cdot V_m$

$$d_N = \frac{V_m}{V_{dc}} \cdot \sin(60^\circ - \phi)$$

$$d_{N+1} = \frac{V_m}{V_{dc}} \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

☞ Define the modulation index $M = \frac{V_m}{V_{dc}}$

$$d_N = M \cdot \sin(60^\circ - \phi)$$

$$d_{N+1} = M \cdot \sin \phi$$

$$d_0 = 1 - d_N - d_{N+1}$$

DB-70


Maximum Amplitude of V_{ref}

Assume $d_0 = 0$, then $d_N + d_{N+1} = 1$

$$\begin{aligned} d_N + d_{N+1} &= M \cdot (\sin(60^\circ - \phi) + \sin \phi) \\ &= M \cdot \cos(30^\circ - \phi) \\ &= \frac{V_m}{V_{dc}} \cdot \cos(30^\circ - \phi) \\ &= 1 \end{aligned}$$

$$\therefore V_m = \frac{V_{dc}}{\cos(30^\circ - \phi)}$$

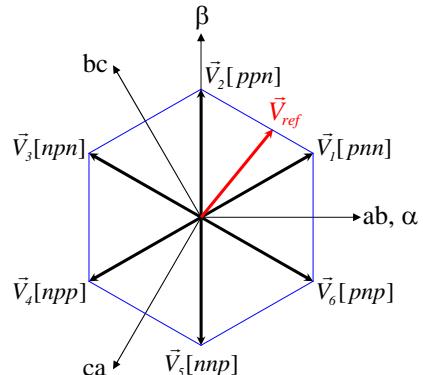☞ The trajectory of \vec{V}_{ref} makes a hexagon.



$\vec{V}_0 = [ppp] = [nnn]$ at center point

DB-71

Maximum Amplitude of V_{ref}


Assume $M = 1$, then $\frac{V_m}{V_{dc}} = 1$

$$\therefore V_m = V_{dc}$$

$$\vec{V}_{ref} = \sqrt{\frac{3}{2}} \cdot V_{dc} \cdot e^{j\theta}$$

☞ The trajectory of \vec{V}_{ref} makes a circle whose radius is $\sqrt{\frac{3}{2}} \cdot V_{dc}$

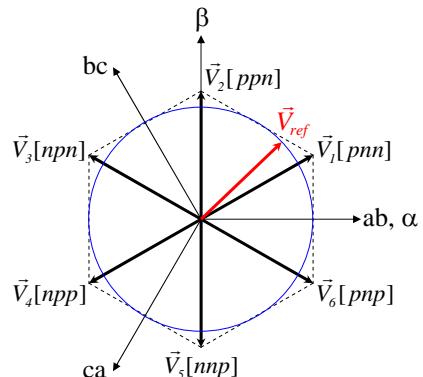☞ This trajectory of \vec{V}_{ref} represents the largest 3-phase sinusoidal voltage that can be synthesized.



$\vec{V}_0 = [ppp] = [nnn]$ at center point


DB-72

Step 3 : Sequence of Switching State Vectors

Asymmetrical
sequence
Symmetrical
sequence

2-phase
commutation
3-phase
commutation

Feed forward
Feedback

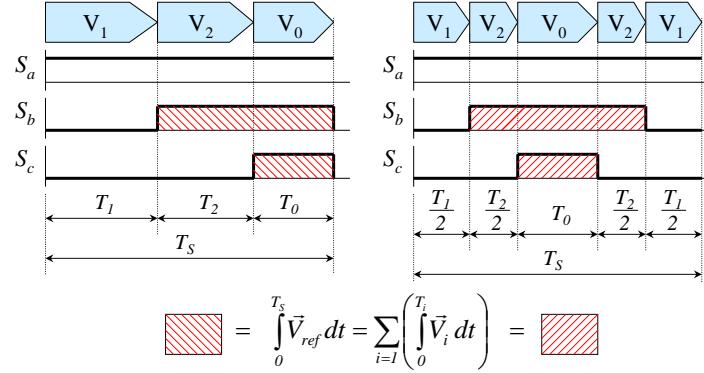


DB-73

Sequence of SSVs – SVM 1

(Three-Phase – Right Aligned: 3Φ-RA)

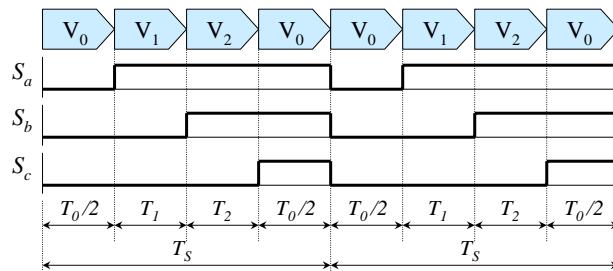- Use both zero switching state vectors
- Asymmetrical sequence
- Six commutations per switching cycle



< Example in sector I >

- 3Φ-LA has same characteristics




DB-74

Sequence of SSVs – SVM 2

(Three-Phase – Centered: 3Φ-C)

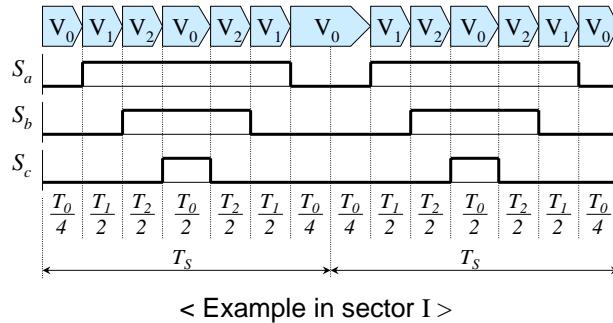- Use both zero switching state vectors
- Symmetrical sequence \rightarrow Low THD
- Six commutations per switching cycle




DB-75

Sequence of SSVs – SVM 3

(Three-Phase – Double-Period: 3Φ-2T)

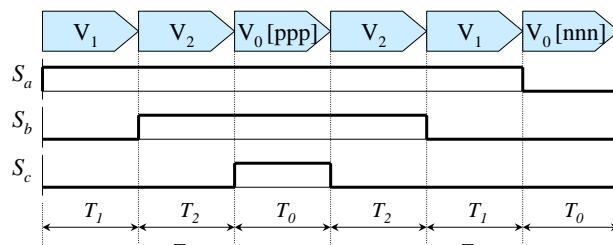- Use zero vectors alternatively in adjacent switching cycle
- Asymmetrical sequence in T_S , but symmetrical in $2 \cdot T_S$
- Three commutations \rightarrow 50 % switching loss reduction
- Introduction of harmonics around $\frac{1}{2 \cdot T_S}$




DB-76

Sequence of SSVs – SVM 4 (Two-Phase – Right Aligned: 2Φ-RA)

- Use a zero vector in one switching cycle

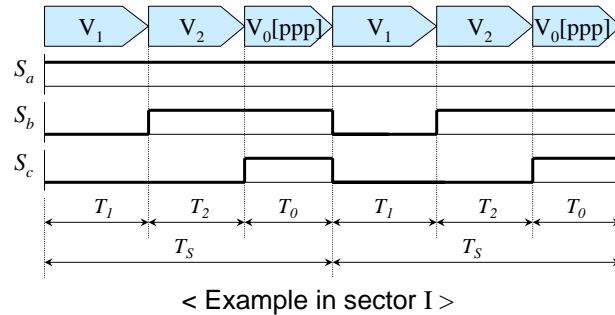$\left\{ \begin{array}{l} \text{Sector I, III, V : [ppp]} \\ \text{Sector II, IV, VI : [nnn]} \end{array} \right.$
- Asymmetrical sequence
- Four commutations \rightarrow Reduced switching losses




- 2Φ-LA has same characteristics

DB-77

Sequence of SSVs – SVM 5 (Two-Phase – Centered: 2Φ-C)

- Use a zero vector in one switching cycle

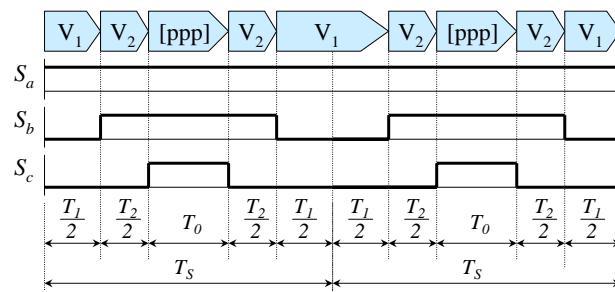$\left\{ \begin{array}{l} \text{Sector I, III, V : [ppp]} \\ \text{Sector II, IV, VI : [nnn]} \end{array} \right.$
- Symmetrical sequence \rightarrow Low THD
- Four commutations \rightarrow Reduced switching losses




DB-78

Sequence of SSVs – SVM 6 (Minimum-Loss SVM)

(Two-Phase – Right Aligned – minimum Loss: $2\Phi\text{-RA-mL}$)

- Choose a zero switching state vector to avoid switching the phase with the highest instantaneous current
- Reduce the switching losses up to 50% compared to 3Φ modulations, assuming that switching losses are proportional to the current

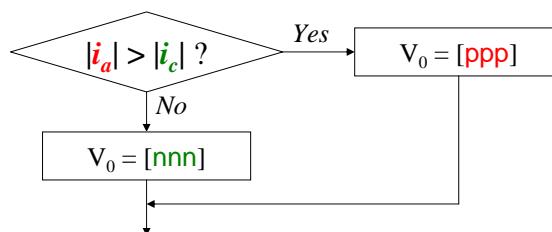
Choice of zero vector in sector I (pnn, ppn, and ppp or nnn)




- Possible sequences: $2\Phi\text{-RA-mL}$, $2\Phi\text{-LA-mL}$, or $2\Phi\text{-C-mL}$

DB-79

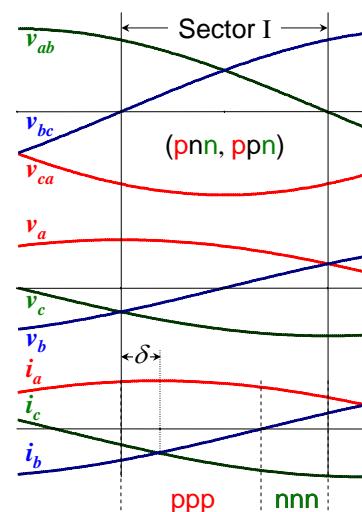Example of $2\Phi\text{-x -mL SVM in Sector I}$ for balanced, symmetrical, sinusoidal, steady-state case



- $|\delta| \leq 30^\circ$
- Switching loss reduction = 50%

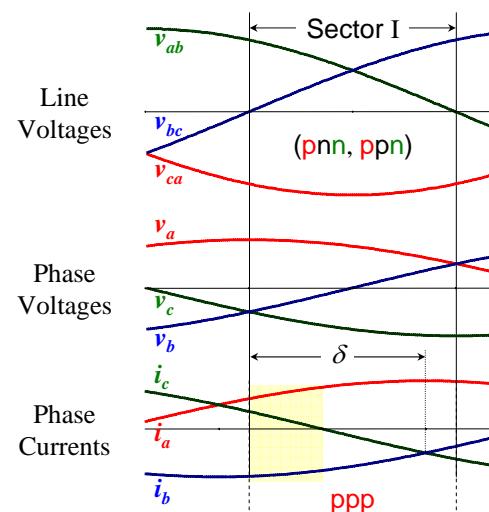


- $|\delta| > 30^\circ$
- Switching loss reduction < 50%

DB-80


Comparison: Total Harmonic Distortion (THD)

With the Fourier series $V = \sum_{n=1}^{\infty} V_n \cdot e^{j n \omega t}$, $THD = \sqrt{\sum_{n=2}^{\infty} V_n^2} / V_1$

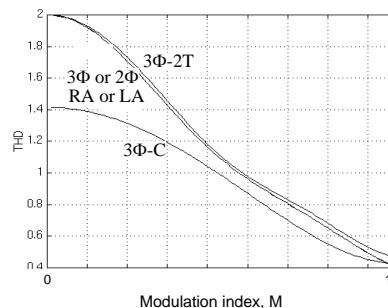Calculated and switching-model simulation results for $f_S > 100 \cdot f_{line}$.



THD of line-to-line voltage

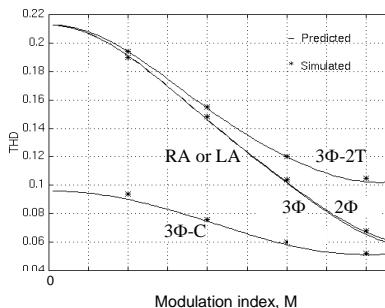

THD of phase current
with $L + V_{ABC}$ load/source

DB-81

Comparison: Peak-to-Peak Current Ripple

For RA or LA modulations:

$$I_{pp} = \frac{2 \cdot V_{dc}}{3 \cdot L} \cdot (1 - M) \cdot M \cdot T_S$$


For centered modulations:

$$I_{pp} = \frac{V_{dc}}{3 \cdot L} \cdot (1 - M) \cdot M \cdot T_P$$

where $T_P = T_S$, except
 $T_P = 2T_S$, for 3Φ-2T.

M : modulation index

L : load inductance

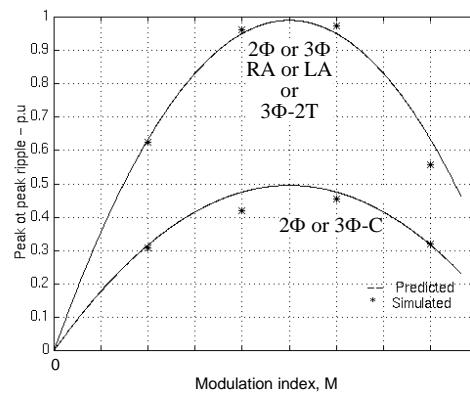

Relative peak-to-peak current ripple

DB-82


Comparison: Switching Losses

- Number of commutations per switching cycle:

$3\Phi-x$: 6

$3\Phi-2T$: 3

$2\Phi-x$: 4

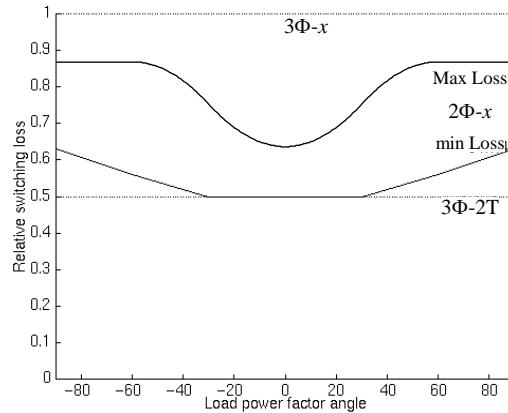

☞ $2\Phi-x$ -mL avoids switching the phase with highest current between -30° and 30° .

DB-83


Outline

PECon
2008

1. Introduction
2. Switching Modeling and PWM
 - Switching model of VSI & boost rectifier
 - Space vector modulation for VSI & boost rectifier
 - Other modulations for VSI & boost rectifier
 - Switching model and modulation for CSI & buck rectifier
3. Average Modeling
4. Small-Signal Modeling
5. Closed-Loop Control Design
6. More Complex Converters


DB-84

Modulation Methods

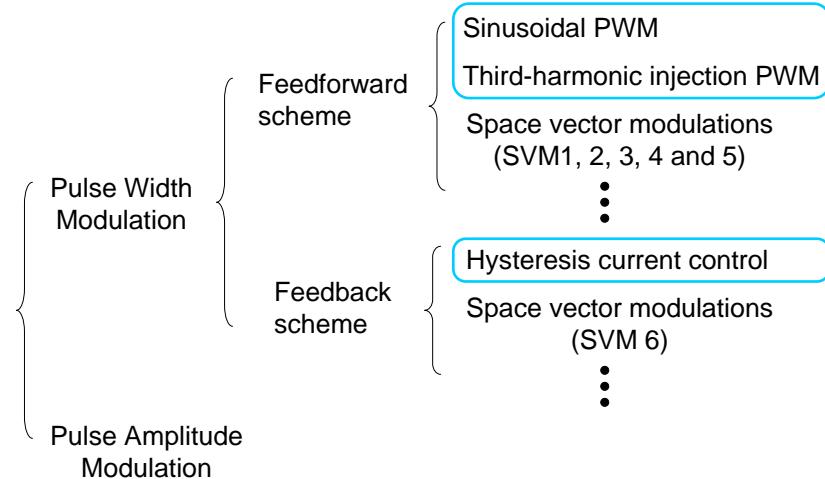

DB-85


Sinusoidal Pulse Width Modulation (SPWM)

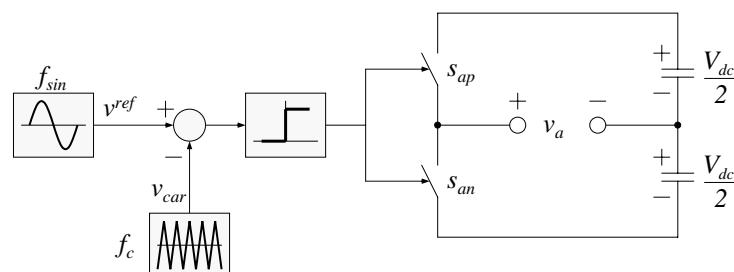

- Determine the switching state by magnitude of v^{ref} and v_{car}
 - If $|v^{ref}| > |v_{car}|$, then s_{ap} on,
 - If $|v^{ref}| < |v_{car}|$, then s_{an} on
- Switching frequency is the same as carrier wave frequency, f_c



DB-86

Waveforms of Single-Phase SPWM

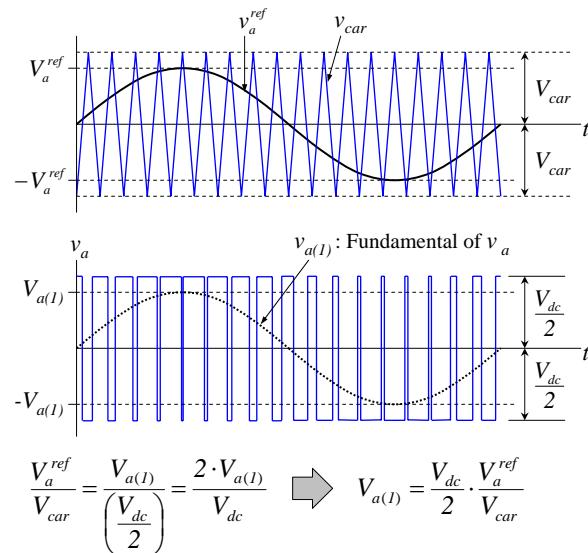

DB-87

Three-Phase SPWM

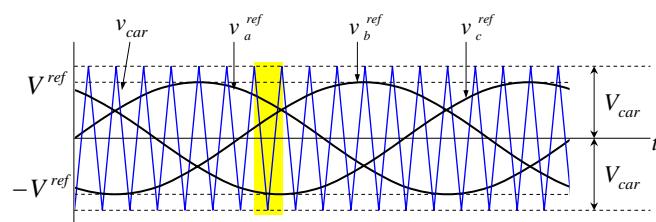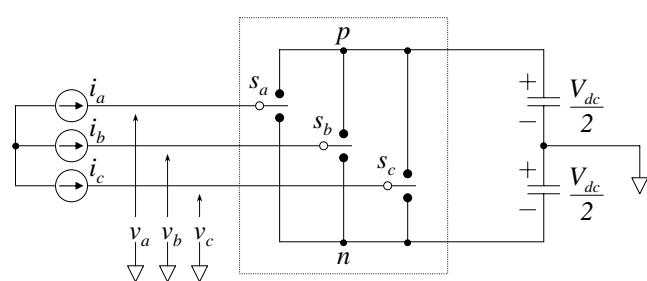

DB-88

Modulation Example of SPWM in Sector I


Assume v_a^{ref} , v_b^{ref} and v_c^{ref} are constant in a switching cycle.

☞ Symmetrical (Center-based) Three-phase commutation




$$\text{☞ } T_{ON} = -\frac{T_s}{4 \cdot V_{car}} \cdot (v_a^{ref} - V_{car})$$
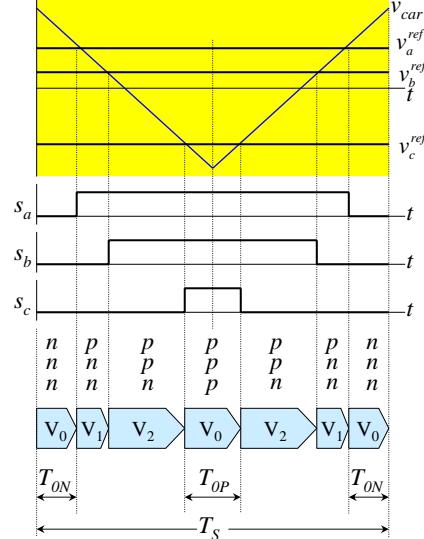
$$\begin{aligned} \frac{T_{OP}}{2} &= \frac{T_s}{2} + \frac{T_s}{4 \cdot V_{car}} \cdot (v_c^{ref} - V_{car}) \\ &= \frac{T_s}{4 \cdot V_{car}} \cdot (v_c^{ref} + V_{car}) \end{aligned}$$



DB-89


Modulation Example of SVM2 in Sector I

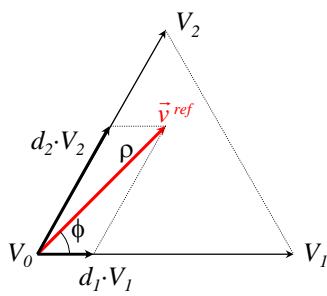

$$\frac{T_1}{T_s} = d_1 = \sqrt{2} \cdot \frac{V_m}{\|V_1\|} \cdot \sin(60^\circ - \phi)$$

$$\frac{T_2}{T_s} = d_2 = \sqrt{2} \cdot \frac{V_m}{\|V_2\|} \cdot \sin \phi$$

$$d_0 = 1 - d_1 - d_2$$

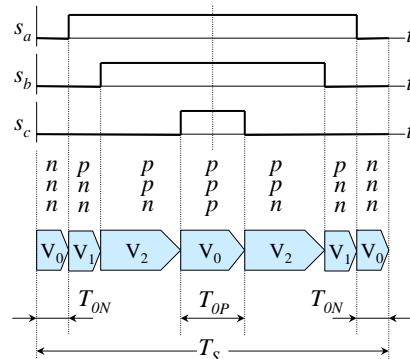

$$\begin{aligned} \frac{T_{OP}}{2} &= T_{ON} = \frac{T_o}{4} \\ &= \frac{T_s}{4} - \frac{V_m}{V_{dc}} \cdot \frac{T_s}{4} \cdot \cos(30^\circ - \phi) \end{aligned}$$

DB-90


Zero Vector Timings in Sector I

- In SPWM, assume $V^{ref} = V_{car}$

$$T_{0N} = -\frac{T_s}{4 \cdot V^{ref}} \cdot (v_a^{ref} - V^{ref})$$

$$\frac{T_{0P}}{2} = \frac{T_s}{4 \cdot V^{ref}} \cdot (v_c^{ref} + V^{ref})$$

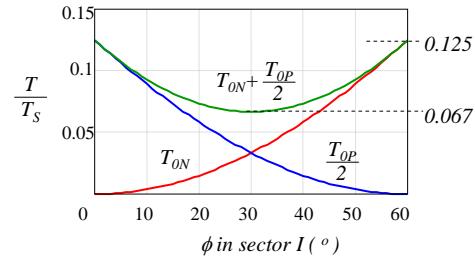
where $v_a^{ref} = V^{ref} \cdot \cos \phi$
 $v_c^{ref} = V^{ref} \cdot \cos(\phi + 120^\circ)$



- In SVM2, assume $V_m = V_{dc}$

$$\frac{T_{0P}}{2} = T_{0N} = \frac{T_s}{4}$$
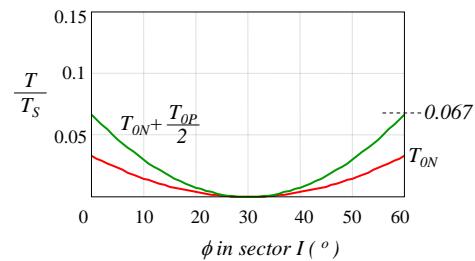
$$= \frac{T_s}{4} - \frac{T_s}{4} \cdot \cos(30^\circ - \phi)$$



DB-91


Maximum AC Voltage of SPWM

The \vec{v}^{ref} trajectory in SPWM: $\vec{v}^{ref} = \frac{3}{2\sqrt{2}} \cdot V_{dc} \cdot e^{j\theta}$

By definition: $\vec{v}^{ref} = \sqrt{\frac{3}{2}} \cdot V_m \cdot e^{j\theta}$

The maximum AC voltage: $V_m = \frac{\sqrt{3}}{2} \cdot V_{dc}$

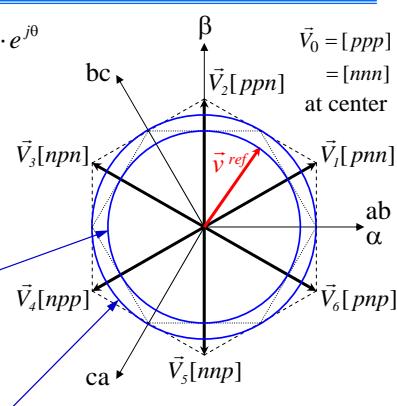
The maximum AC voltage of SVM: $V_m = V_{dc}$



☞ $\frac{V_m|_{SVM}}{V_m|_{SPWM}} = \frac{V_{dc}}{\left(\frac{\sqrt{3} \cdot V_{dc}}{2}\right)} = 1.155 \rightarrow \text{SVM produces 15.5% higher maximum output than SPWM !}$

DB-92


Over Modulation of SPWM

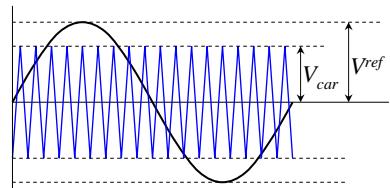

- $V_{ref} \leq V_{car}$: Linear modulation
- $V_{ref} > V_{car}$: Over modulation


☞ Over modulation region is non linear with more harmonics

$$\text{☞ } \frac{V_{(I)}^{\max}|_{SPWM}}{V_{(I)}^{\max}|_{Square}} = \frac{\left(\frac{V_{dc}}{2}\right)}{\left(\frac{4}{\pi} \cdot \frac{V_{dc}}{2}\right)} = \frac{\pi}{4} = 0.785$$

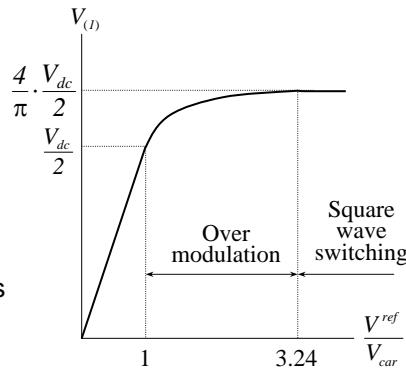

DB-93

Third-Harmonic Injection PWM

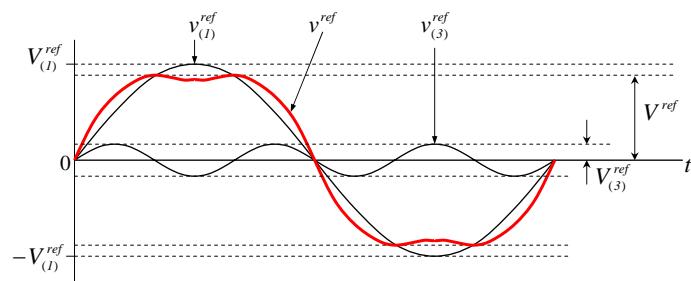

$$v^{ref} = V_{(I)}^{ref} \cdot \sin \omega t + V_{(3)}^{ref} \cdot \sin 3\omega t$$

$$V^{ref} = V_{(I)}^{ref} + V_{(3)}^{ref}$$


DB-94

Maximum AC Voltage of Third-Harmonic Injection PWM

In general, $v^{ref} = V_{(I)}^{ref} \cdot \left(\sin \theta + \frac{1}{6} \cdot \sin 3\theta \right)$


Assume $V^{ref} = I$,

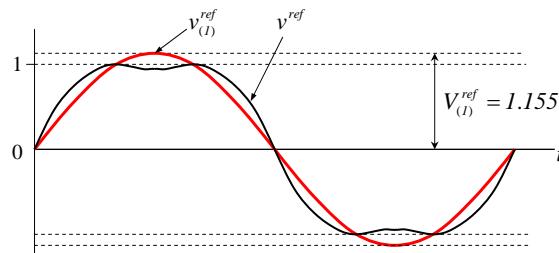then $V_{(I)}^{ref} = \frac{I}{\left(\frac{\sqrt{3}}{2}\right)} = 1.155$  The maximum AC voltage is 15.5 % more than SPWM



DB-95

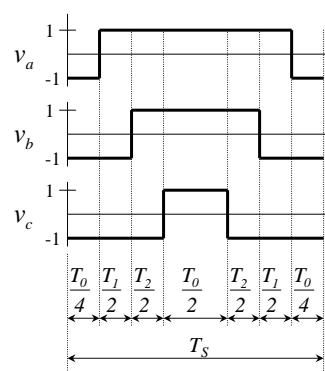Average Values of Phase-to Neutral Voltage for SVM 2 (3Φ-C) in Sector I



$$\begin{aligned} \frac{\bar{v}_a}{V_{dc}} &= -\frac{d_0}{2} + d_1 + d_2 + \frac{d_0}{2} \\ &= \sin(60^\circ - \phi) + \sin \phi \\ &= \sin(60^\circ + \phi) \end{aligned}$$

$$\begin{aligned} \frac{\bar{v}_b}{V_{dc}} &= -\frac{d_0}{2} - d_1 + d_2 + \frac{d_0}{2} \\ &= -\sin(60^\circ - \phi) + \sin \phi \\ &= \sqrt{3} \cdot \sin(\phi - 30^\circ) \end{aligned}$$

$$\begin{aligned} \frac{\bar{v}_c}{V_{dc}} &= -\frac{d_0}{2} - d_1 - d_2 + \frac{d_0}{2} \\ &= -\sin(60^\circ + \phi) \\ &= -\bar{v}_a \end{aligned}$$

DB-96


Average Values of Phase-to Neutral Voltage for SVM 2 (3Φ-C)

- In sector II,

$$\begin{aligned}\frac{\bar{v}_a}{V_{dc}} &= -\frac{d_0}{2} + d_1 - d_2 + \frac{d_0}{2} \\ &= \sin(60^\circ - \phi) - \sin \phi \\ &= \sqrt{3} \cdot \sin(30^\circ - \phi) \\ &= \sqrt{3} \cdot \sin(90^\circ - \theta)\end{aligned}$$


- In sector III,
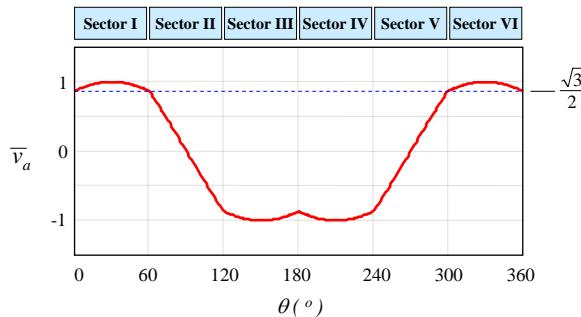
$$\begin{aligned}\frac{\bar{v}_a}{V_{dc}} &= -\frac{d_0}{2} - d_1 - d_2 + \frac{d_0}{2} \\ &= -\sin(60^\circ - \phi) - \sin \phi \\ &= -\sin(60^\circ + \phi) \\ &= -\sin(\phi - 60^\circ)\end{aligned}$$



DB-97

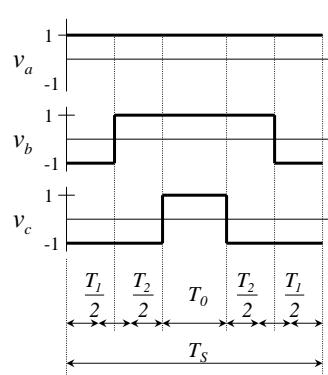Average Values of Phase-to Neutral Voltage for SVM 6 (2Φ-C-mL) in Sector I



- If i_a is the largest current,

$$\begin{aligned}\bar{v}_a &= I \\ \bar{v}_b &= -d_1 + d_2 + d_0 \\ &= I - 2 \cdot d_1 \\ &= I - 2 \cdot \sin(60^\circ - \phi) \\ \bar{v}_c &= -d_1 - d_2 + d_0 \\ &= I - 2 \cdot (d_1 + d_2) \\ &= I - 2 \cdot \sin(60^\circ + \phi)\end{aligned}$$


- If i_c is the largest current,

$$\begin{aligned}\bar{v}_a &= -d_0 + d_1 + d_2 \\ &= 2 \cdot \sin(60^\circ + \phi) - I \\ &= 2 \cdot \sin(60^\circ + \theta) - I\end{aligned}$$


DB-98

Average Values of Phase-to Neutral Voltage for SVM 6 (2Φ-C-mL)

- $M = 1$


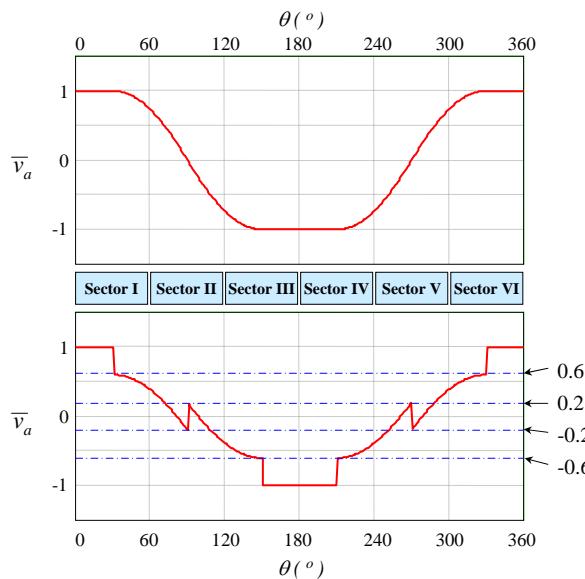


- $M = 0.8$

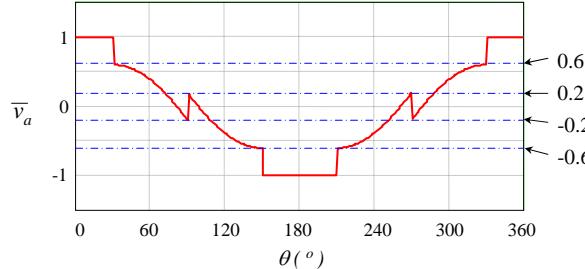


DB-99

Hysteresis Current Control

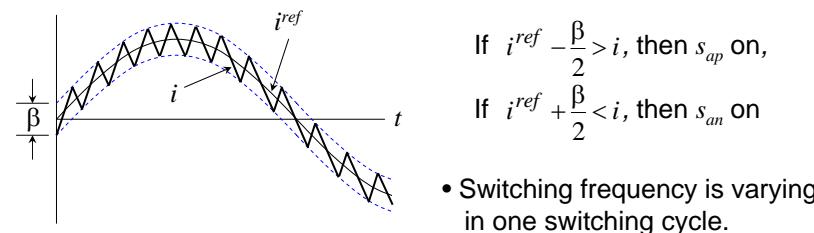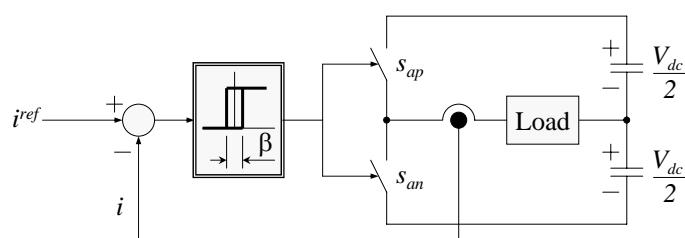

DB-100

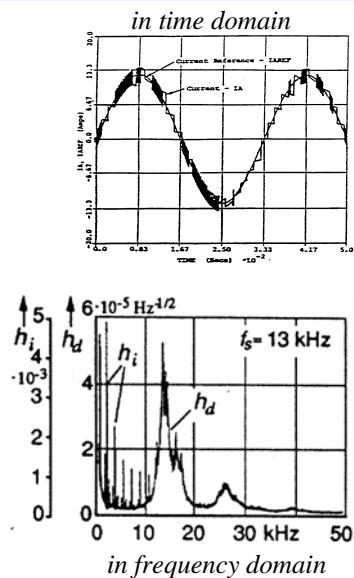Pros and Cons of Hysteresis Current Control



➤ **Pros:**

- Simple to implement
- Excellent dynamic performance

➤ **Cons:**

- Strong harmonics lower than the switching frequency (Subharmonics)
- No intercommunication between the individual hysteresis controllers
 - ➡ Increase the switching frequency at lower modulation index
- A tendency at lower speed to lock into limit cycle of high-frequency switching
- Not strictly limit the current error

DB-101

Outline

PECon
2008


- 1. Introduction**
- 2. Switching Modeling and PWM**
 - Switching model of VSI & boost rectifier
 - Space vector modulation for VSI & boost rectifier
 - Other modulations for VSI & boost rectifier
 - Switching model and modulation for CSI & buck rectifier
- 3. Average Modeling**
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**
- 6. More Complex Converters**

DB-102

Buck Rectifier / Current Source Inverter

– similar approach but different results –

- Buck Rectifier

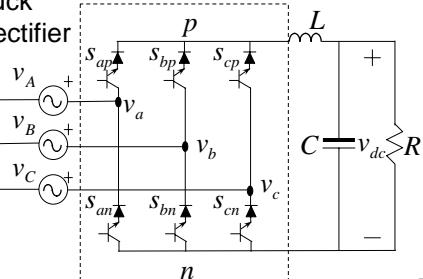


- Unidirectional DC current


- Bi-directional DC voltage

$$\bullet V_{dc} < V_x = \left(\frac{\sqrt{3}}{2} V_m \right)$$

- CSI

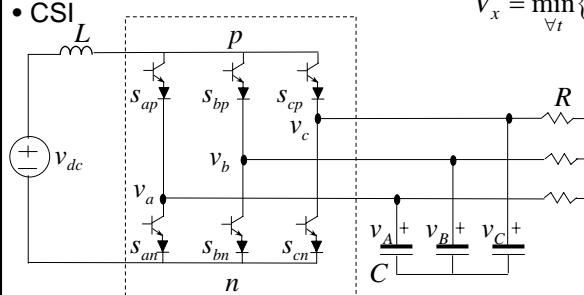

$$V_x = \min_{\forall t} \{ \max \{ |v_{ab}(t)|, |v_{bc}(t)|, |v_{ca}(t)| \} \}$$

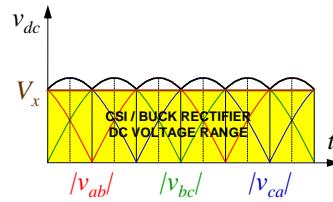


DB-103

DC-Current-Unidirectional Three-Phase Switching Network

- Topology:

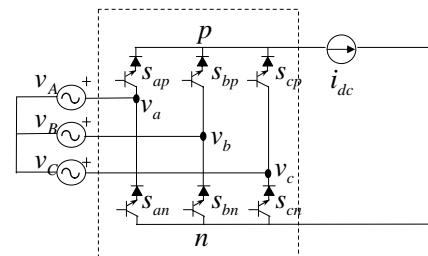
- Three-phase terminals are voltage controlled
- DC port is current controlled
- Six current-unidirectional, voltage-bi-directional, switches



- Allowed switching combinations:


$$s_{ak} + s_{bk} + s_{ck} = 1; \quad k \in \{p, n\}$$

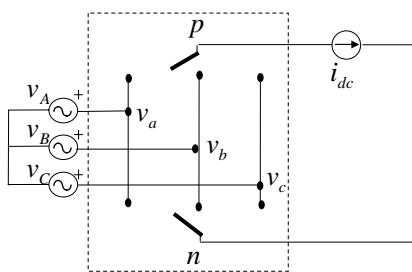- Two single-pole-triple-throw (SPTT) current-unidirectional switches



DB-104

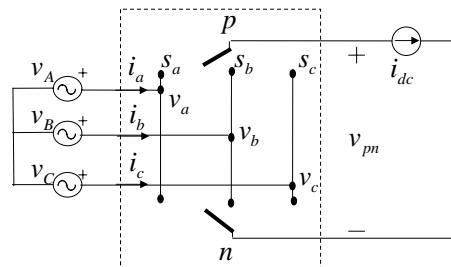Buck Rectifier / Current Source Inverter Switching Model



$$\vec{i}_{abc} = \vec{s}_{abc} \cdot \vec{i}_{dc}$$

$$v_{pn} = \vec{s}_{abc}^T \cdot \vec{v}_{abc}$$


where:

$$\vec{i}_{abc} = \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} \quad \vec{s}_{abc} = \begin{bmatrix} s_a \\ s_b \\ s_c \end{bmatrix} = \begin{bmatrix} s_{ap} - s_{an} \\ s_{bp} - s_{bn} \\ s_{cp} - s_{cn} \end{bmatrix} \quad \vec{v}_{abc} = \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$$

DB-105

Switching State Vectors

	ρ	$\theta (\circ)$
$\vec{I}_1[ab]$		-30
$\vec{I}_2[ac]$		30
$\vec{I}_3[bc]$		90
$\vec{I}_4[ba]$		150
$\vec{I}_5[ca]$		-150
$\vec{I}_6[cb]$		-90
$\vec{I}_0[aa]$		0
$\vec{I}_0[bb]$		0
$\vec{I}_0[cc]$		0

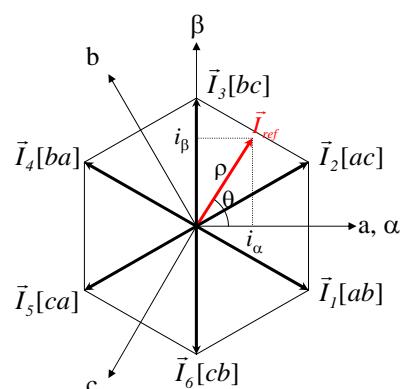

$$\vec{I}_0 = [aa] = [bb] = [cc] \text{ at center point}$$


DB-106

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
 - Average model of boost rectifier
 - Average model of VSI
 - Average models in rotating coordinates
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**
- 6. More Complex Converters**

DB-107

Boost Rectifier Switching Model State-Space Equations
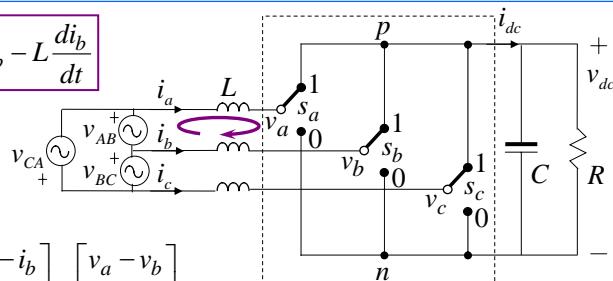
$$v_{AB} = L \frac{di_a}{dt} + v_{ab} - L \frac{di_b}{dt}$$



$$\begin{bmatrix} v_{AB} \\ v_{BC} \\ v_{CA} \end{bmatrix} = L \frac{d}{dt} \begin{bmatrix} i_a - i_b \\ i_b - i_c \\ i_c - i_a \end{bmatrix} + \begin{bmatrix} v_a - v_b \\ v_b - v_c \\ v_c - v_a \end{bmatrix}$$

$$= 3L \frac{d}{dt} \begin{bmatrix} i_{ab} \\ i_{bc} \\ i_{ca} \end{bmatrix} + \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix}$$

$$i_{dc} = C \frac{dv_{dc}}{dt} + \frac{v_{dc}}{R}$$

$$\left\{ \begin{array}{l} \frac{d}{dt} \begin{bmatrix} i_{ab} \\ i_{bc} \\ i_{ca} \end{bmatrix} = \frac{1}{3L} \begin{bmatrix} v_{AB} \\ v_{BC} \\ v_{CA} \end{bmatrix} - \frac{1}{3L} \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix} \\ \frac{dv_{dc}}{dt} = \frac{1}{C} i_{dc} - \frac{v_{dc}}{RC} \end{array} \right.$$

DB-108

Boost Rectifier Switching Model State-Space Equations

$$\vec{v}_{L-L} = \begin{bmatrix} v_{AB} \\ v_{BC} \\ v_{CA} \end{bmatrix} \quad \vec{v}_{l-l} = \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_{ca} \end{bmatrix} \quad \vec{i}_{l-l} = \begin{bmatrix} i_{ab} \\ i_{bc} \\ i_{ca} \end{bmatrix} \quad \vec{s}_{l-l} = \begin{bmatrix} s_{ab} \\ s_{bc} \\ s_{ca} \end{bmatrix}$$

$$\frac{d\vec{i}_{l-l}}{dt} = \frac{1}{3L} \vec{v}_{L-L} - \frac{1}{3L} \vec{v}_{l-l} \quad \vec{v}_{l-l} = \vec{s}_{l-l} \cdot v_{dc}$$

$$\frac{dv_{dc}}{dt} = \frac{1}{C} i_{dc} - \frac{v_{dc}}{RC} \quad i_{dc} = \vec{s}_{l-l}^T \cdot \vec{i}_{l-l}$$

➡

$$\frac{d\vec{i}_{l-l}}{dt} = \frac{1}{3L} \vec{v}_{L-L} - \frac{1}{3L} \vec{s}_{l-l} \cdot v_{dc}$$

$$\frac{dv_{dc}}{dt} = \frac{1}{C} \vec{s}_{l-l}^T \cdot \vec{i}_{l-l} - \frac{v_{dc}}{RC}$$

DB-109

Average Circuit Modeling

Applying an average operator to switching model $\bar{x}(t) = \frac{1}{T} \int_{t-T}^t x(\tau) d\tau$

- Switch duty cycle $d_{ap} = \bar{s}_{ap}(t) = \frac{1}{T} \int_{t-T}^t s_{ap}(\tau) d\tau$

- Phase-leg duty cycle $d_a = d_{ap} = 1 - d_{an}$

- Line-to-line duty cycle $d_{ab} = \bar{s}_{ab}(t) = \frac{1}{T} \int_{t-T}^t s_{ab}(\tau) d\tau = d_a - d_b$

- KVL and KCL $\sum \bar{v} = 0 \quad \sum \bar{i} = 0$

- Linear components $\bar{v}_R = R \bar{i}_R \quad \bar{v}_L = L \frac{d \bar{i}_L}{dt} \quad \bar{i}_C = C \frac{d \bar{v}_C}{dt}$

DB-110




Averaging of Quadratic Terms

$$v_{ab} = s_{ab} \cdot v_{dc}$$

$$\bar{v}_{ab} = \frac{1}{T} \int_{t-T}^t s_{ab}(\tau) \cdot v_{dc}(\tau) d\tau \approx \bar{s}_{ab} \cdot \bar{v}_{dc} = d_{ab} \cdot \bar{v}_{dc}$$

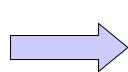if maximum-frequency components of $v_{dc}(t)$ are $\ll 1/2T$.



$$\overline{\vec{s}_{l-l} \cdot v_{dc}} \approx \bar{\vec{s}}_{l-l} \cdot \bar{v}_{dc} = \vec{d}_{l-l} \cdot \bar{v}_{dc}$$

$$\overline{\vec{s}_{l-l}^T \cdot \vec{i}_{l-l}} \approx \bar{\vec{s}}_{l-l}^T \cdot \bar{\vec{i}}_{l-l} = \vec{d}_{l-l}^T \cdot \bar{\vec{i}}_{l-l}$$

DB-111



Development of Boost Rectifier Average Model


$$\begin{cases} \frac{d\vec{i}_{l-l}}{dt} = \frac{1}{3L} \vec{v}_{L-L} - \frac{1}{3L} \vec{s}_{l-l} \cdot v_{dc} \\ \frac{dv_{dc}}{dt} = \frac{1}{C} \vec{s}_{l-l}^T \cdot \vec{i}_{l-l} - \frac{v_{dc}}{RC} \end{cases} \quad \text{Applying average operator} \quad \rightarrow$$

$$\begin{cases} \frac{1}{T} \int_{t-T}^t \frac{d\vec{i}_{l-l}(\tau)}{dt} d\tau = \frac{1}{T} \int_{t-T}^t (\frac{1}{3L} \vec{v}_{l-l}(\tau) - \frac{1}{3L} \vec{s}_{l-l}(\tau) \cdot v_{dc}(\tau)) d\tau \\ \frac{1}{T} \int_{t-T}^t \frac{dv_{dc}(\tau)}{dt} d\tau = \frac{1}{T} \int_{t-T}^t (\frac{1}{C} \vec{s}_{l-l}^T(\tau) \cdot \vec{i}_{l-l}(\tau) - \frac{v_{dc}(\tau)}{RC}) d\tau \end{cases}$$

$$\rightarrow \begin{cases} \frac{d\bar{\vec{i}}_{l-l}}{dt} = \frac{1}{3L} \bar{\vec{v}}_{L-L} - \frac{1}{3L} \vec{d}_{l-l} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \vec{d}_{l-l}^T \cdot \bar{\vec{i}}_{l-l} - \frac{\bar{v}_{dc}}{RC} \end{cases} \quad \vec{d}_{l-l} = \begin{bmatrix} d_{ab} \\ d_{bc} \\ d_{ca} \end{bmatrix}$$


DB-112

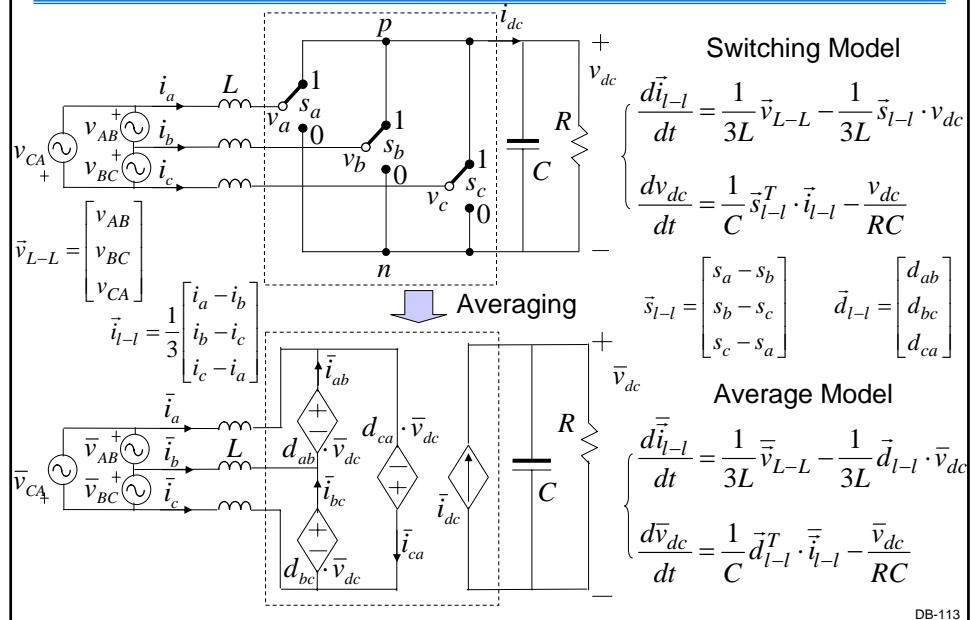Average Model of Three-Phase Boost Rectifier



DB-113

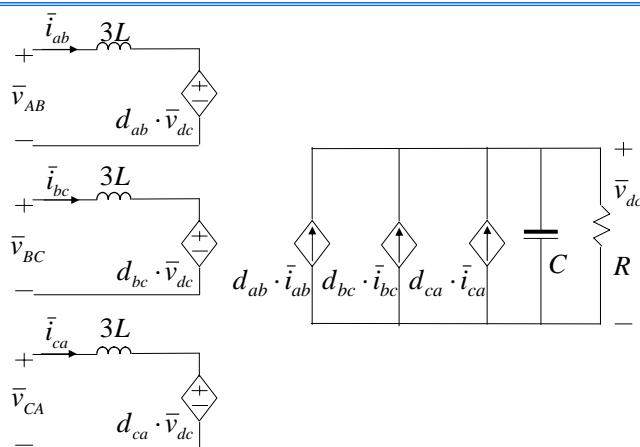Another Equivalent Circuit for Boost Rectifier Average Model





- Third order system due to degeneration

DB-114

Steady-State Operation under Balanced Sinusoidal Excitation


Given:
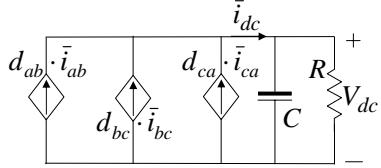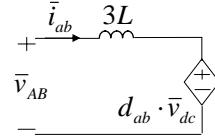
$$\begin{bmatrix} v_{AB} \\ v_{BC} \\ v_{CA} \end{bmatrix} = \begin{bmatrix} V_m \cos(\omega t) \\ V_m \cos(\omega t - 2\pi/3) \\ V_m \cos(\omega t + 2\pi/3) \end{bmatrix}$$



Goal:
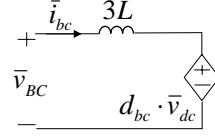
$$\begin{bmatrix} i_{ab} \\ i_{bc} \\ i_{ca} \end{bmatrix} = \begin{bmatrix} I_m \cos(\omega t) \\ I_m \cos(\omega t - 2\pi/3) \\ I_m \cos(\omega t + 2\pi/3) \end{bmatrix}$$



Assume:

$$\begin{bmatrix} d_{ab} \\ d_{bc} \\ d_{ca} \end{bmatrix} = \begin{bmatrix} D_m \cos(\omega t - \theta) \\ D_m \cos(\omega t - 2\pi/3 - \theta) \\ D_m \cos(\omega t + 2\pi/3 - \theta) \end{bmatrix}$$

$$\bar{i}_{dc} = D_m I_m \left[\cos \omega t \cos(\omega t - \theta) + \cos(\omega t - \frac{2\pi}{3}) \cos(\omega t - \frac{2\pi}{3} - \theta) + \cos(\omega t + \frac{2\pi}{3}) \cos(\omega t + \frac{2\pi}{3} - \theta) \right]$$

$$\bar{i}_{dc} = \frac{D_m I_m}{2} \left[\cos \theta + \cos(2\omega t - \theta) + \cos \theta + \cos(2\omega t - \frac{4\pi}{3} - \theta) + \cos \theta + \cos(2\omega t + \frac{4\pi}{3} - \theta) \right]$$

$$\bar{i}_{dc} = \frac{3}{2} D_m I_m \cos \theta = \text{const.} \Rightarrow V_{dc} = \frac{3}{2} R D_m I_m \cos \theta = \text{const.}$$

DB-115

Steady-State Operation under Balanced Sinusoidal Excitation

$$\bar{v}_{dc} = \text{const.} = V_{dc}, \Rightarrow d_{ab} \cdot \bar{v}_{dc} = D_m \cdot V_{dc} \cos(\omega t - \theta)$$

→ Can use positive sequence phasors for steady state:

$$\mathbf{V}_{AB} = \frac{V_m}{\sqrt{2}} \quad \mathbf{I}_{AB} = \frac{I_m}{\sqrt{2}}$$

$$\mathbf{D}_{ab} \cdot V_{dc} = \frac{D_m \cdot V_{dc}}{\sqrt{2}} \cos \theta - j \cdot \frac{D_m \cdot V_{dc}}{\sqrt{2}} \sin \theta$$

$$\mathbf{V}_{AB} = j3\omega L \cdot \mathbf{I}_{AB} + \mathbf{D}_{ab} \cdot V_{dc}$$

$$\rightarrow \theta = \frac{1}{2} \sin^{-1} \left(\frac{4\omega L}{RD_m^2} \right), \quad V_{dc} = \frac{V_m}{D_m \cos \theta}, \quad I_m = \frac{2}{3} \cdot \frac{V_m}{RD_m^2 \cos^2 \theta}$$

$$d_{ab} = d_a - d_b \equiv d_{ap} - d_{bp}, \quad d_{ap}, d_{bp} \in [0, 1] \Rightarrow -1 \leq d_{ab} \leq 1$$


$$\rightarrow D_m \leq 1 \Rightarrow V_{dc} \geq V_m$$

DB-116

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
 - Average model of boost rectifier
 - Average model of VSI
 - Average models in rotating coordinates
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**
- 6. More Complex Converters**

DB-117

Development of VSI Average Model

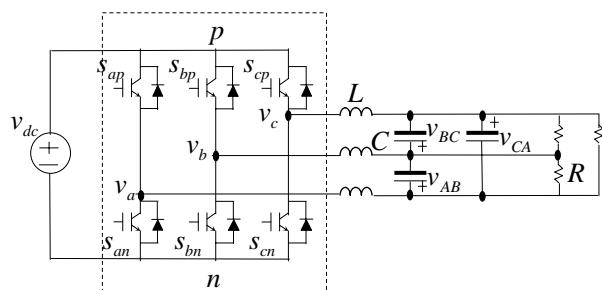


$$\left\{ \begin{array}{l} \frac{d\vec{i}_{l-l}}{dt} = \frac{1}{3L} \vec{s}_{l-l} \cdot \vec{v}_{dc} - \frac{1}{3L} \vec{v}_{L-L} \\ \frac{d\vec{v}_{L-L}}{dt} = \frac{1}{C} \vec{i}_{l-l} - \frac{1}{RC} \vec{v}_{L-L} \\ i_{dc} = \vec{s}_{l-l}^T \cdot \vec{i}_{l-l} \end{array} \right.$$

Averaging →

$$\left\{ \begin{array}{l} \frac{d\bar{\vec{i}}_{l-l}}{dt} = \frac{1}{3L} \vec{d}_{l-l} \cdot \vec{v}_{dc} - \frac{1}{3L} \bar{\vec{v}}_{L-L} \\ \frac{d\bar{\vec{v}}_{L-L}}{dt} = \frac{1}{C} \bar{\vec{i}}_{l-l} - \frac{1}{RC} \bar{\vec{v}}_{L-L} \\ i_{dc} = \vec{d}_{l-l}^T \cdot \bar{\vec{i}}_{l-l} \end{array} \right.$$

DB-118


Equivalent Circuit for VSI Average Model

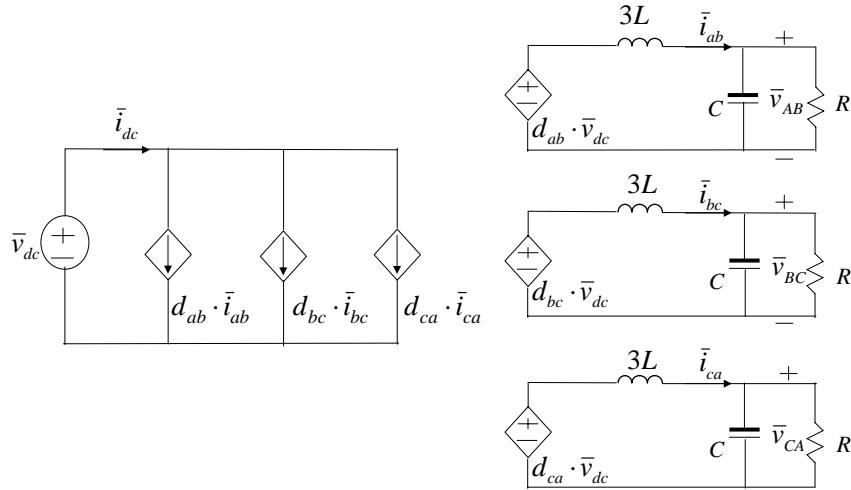

- Fourth order system due to degeneration

DB-119

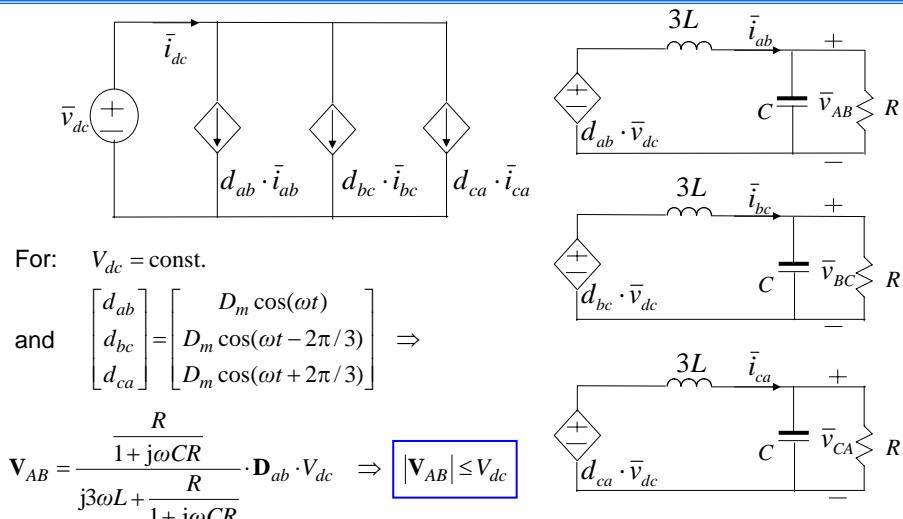Steady-State Operation under DC Input and Balanced Sinusoidal Duty-Cycles



- Steady-state ac voltages and currents are sinusoidal if
- Difficult to define small-signal model. Operating point ?

DB-120

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
 - Average model of boost rectifier
 - Average model of VSI
 - **Average models in rotating coordinates**
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**

- 6. More Complex Converters**

DB-121

Choose

$$T_{dq0/abc} = \sqrt{\frac{2}{3}} \begin{bmatrix} \cos \omega t & \cos(\omega t - \frac{2\pi}{3}) & \cos(\omega t + \frac{2\pi}{3}) \\ -\sin \omega t & -\sin(\omega t - \frac{2\pi}{3}) & -\sin(\omega t + \frac{2\pi}{3}) \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \end{bmatrix}$$

where: $\omega=2\pi f$, f is ac line frequency(source frequency for boost rectifier;
desired output frequency for VSI)

$$X_{dq0} = T \cdot X_{abc} \quad X_{abc} = T^{-1} \cdot X_{dq0}$$

$$(T = T_{dq0/abc})$$

DB-122

Coordinate Transformation – Boost Rectifier –

$$\begin{cases} \frac{d\bar{\vec{i}}_{l-l}}{dt} = \frac{1}{3L} \bar{\vec{v}}_{L-L} - \frac{1}{3L} \vec{d}_{l-l} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \vec{d}_{l-l}^T \cdot \bar{\vec{i}}_{l-l} - \frac{\bar{v}_{dc}}{RC} \end{cases}$$

$X_{abc} = T^{-1} \cdot X_{dq0}$

$\Rightarrow \begin{cases} \frac{d(T^{-1} \cdot \bar{\vec{i}}_{dq0})}{dt} = \frac{1}{3L} T^{-1} \cdot \bar{\vec{v}}_{dq0} - \frac{1}{3L} T^{-1} \cdot \vec{d}_{dq0} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \vec{d}_{l-l}^T \cdot T^{-1} T \cdot \bar{\vec{i}}_{l-l} - \frac{\bar{v}_{dc}}{RC} \end{cases}$

$\Rightarrow \begin{cases} \frac{dT^{-1}}{dt} \cdot \bar{\vec{i}}_{dq0} + T^{-1} \cdot \frac{d\bar{\vec{i}}_{dq0}}{dt} = T^{-1} \cdot \frac{1}{3L} \bar{\vec{v}}_{dq0} - T^{-1} \cdot \frac{1}{3L} \vec{d}_{dq0} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \cdot (T \cdot \vec{d}_{l-l})^T \cdot T \cdot \bar{\vec{i}}_{l-l} - \frac{\bar{v}_{dc}}{RC} \end{cases} \quad T \times$

DB-123

$\Rightarrow \begin{cases} T \frac{dT^{-1}}{dt} \cdot \bar{\vec{i}}_{dq0} + \frac{d\bar{\vec{i}}_{dq0}}{dt} = \frac{1}{3L} \bar{\vec{v}}_{dq0} - \frac{1}{3L} \vec{d}_{dq0} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \cdot (T \cdot \vec{d}_{l-l})^T \cdot T \cdot \bar{\vec{i}}_{l-l} - \frac{\bar{v}_{dc}}{RC} \end{cases}$

$$T \cdot \vec{d}_{l-l} = \vec{d}_{dq0} \quad T \cdot \bar{\vec{i}}_{l-l} = \bar{\vec{i}}_{dq0}$$

$\Rightarrow \begin{cases} T \frac{dT^{-1}}{dt} \cdot \bar{\vec{i}}_{dq0} + \frac{d\bar{\vec{i}}_{dq0}}{dt} = \frac{1}{3L} \bar{\vec{v}}_{dq0} - \frac{1}{3L} \vec{d}_{dq0} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \vec{d}_{dq0}^T \cdot \bar{\vec{i}}_{dq0} - \frac{\bar{v}_{dc}}{RC} \end{cases}$

DB-124

Coordinate Transformation

$$\begin{aligned}
 T \cdot \frac{dT^{-1}}{dt} &= T \cdot \frac{dT^T}{dt} = T \cdot \frac{d}{dt} \left(\sqrt{\frac{2}{3}} \begin{bmatrix} \cos \omega t & -\sin \omega t & \frac{1}{\sqrt{2}} \\ \cos(\omega t - \frac{2\pi}{3}) & -\sin(\omega t - \frac{2\pi}{3}) & \frac{1}{\sqrt{2}} \\ \cos(\omega t + \frac{2\pi}{3}) & -\sin(\omega t + \frac{2\pi}{3}) & \frac{1}{\sqrt{2}} \end{bmatrix} \right) \\
 &= T \cdot \sqrt{\frac{2}{3}} \begin{bmatrix} -\omega \sin \omega t & -\omega \cos \omega t & 0 \\ -\omega \sin(\omega t - \frac{2\pi}{3}) & -\omega \cos(\omega t - \frac{2\pi}{3}) & 0 \\ -\omega \sin(\omega t + \frac{2\pi}{3}) & -\omega \cos(\omega t + \frac{2\pi}{3}) & 0 \end{bmatrix} \\
 &= \sqrt{\frac{2}{3}} \begin{bmatrix} \cos \omega t & \cos(\omega t - \frac{2\pi}{3}) & \cos(\omega t + \frac{2\pi}{3}) \\ -\sin \omega t & -\sin(\omega t - \frac{2\pi}{3}) & -\sin(\omega t + \frac{2\pi}{3}) \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \end{bmatrix} \cdot \sqrt{\frac{2}{3}} \begin{bmatrix} -\omega \sin \omega t & -\omega \cos \omega t & 0 \\ -\omega \sin(\omega t - \frac{2\pi}{3}) & -\omega \cos(\omega t - \frac{2\pi}{3}) & 0 \\ -\omega \sin(\omega t + \frac{2\pi}{3}) & -\omega \cos(\omega t + \frac{2\pi}{3}) & 0 \end{bmatrix}
 \end{aligned}$$

DB-125

Coordinate Transformation

Using the following trigonometric relationships

$$\cos^2 x + \cos^2(x - \frac{2\pi}{3}) + \cos^2(x + \frac{2\pi}{3}) = \frac{3}{2}$$

$$\sin^2 x + \sin^2(x - \frac{2\pi}{3}) + \sin^2(x + \frac{2\pi}{3}) = \frac{3}{2}$$

$$\sin x \cdot \cos x + \sin(x - \frac{2\pi}{3}) \cdot \cos(x - \frac{2\pi}{3}) + \sin(x + \frac{2\pi}{3}) \cdot \cos(x + \frac{2\pi}{3}) = 0$$

$$\cos x + \cos(x - \frac{2\pi}{3}) + \cos(x + \frac{2\pi}{3}) = 0$$

$$\sin x + \sin(x - \frac{2\pi}{3}) + \sin(x + \frac{2\pi}{3}) = 0$$

DB-126

Coordinate Transformation – Boost Rectifier –

$$\xrightarrow{\hspace{1cm}} T \cdot \frac{dT^{-1}}{dt} = \begin{bmatrix} 0 & -\omega & 0 \\ \omega & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

Therefore:

$$\begin{cases} T \frac{dT^{-1}}{dt} \cdot \bar{i}_{dq0} + \frac{d\bar{i}_{dq0}}{dt} = \frac{1}{3L} \bar{v}_{dq0} - \frac{1}{3L} \vec{d}_{dq0} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \vec{d}_{dq0}^T \cdot \bar{i}_{dq0} - \frac{\bar{v}_{dc}}{RC} \end{cases}$$

$$\xrightarrow{\hspace{1cm}} \begin{cases} \frac{d\bar{i}_{dq0}}{dt} = \frac{1}{3L} \bar{v}_{dq0} - \begin{bmatrix} 0 & -\omega & 0 \\ \omega & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \cdot \bar{i}_{dq0} - \frac{1}{3L} \vec{d}_{dq0} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \vec{d}_{dq0}^T \cdot \bar{i}_{dq0} - \frac{\bar{v}_{dc}}{RC} \end{cases}$$

DB-127


State-Space Equations – Boost Rectifier –

$$\begin{cases} \frac{d}{dt} \begin{bmatrix} \bar{i}_{ab} \\ \bar{i}_{bc} \\ \bar{i}_{ca} \end{bmatrix} = \frac{1}{3L} \begin{bmatrix} \bar{v}_{AB} \\ \bar{v}_{BC} \\ \bar{v}_{CA} \end{bmatrix} - \frac{1}{3L} \begin{bmatrix} d_{ab} \\ d_{bc} \\ d_{ca} \end{bmatrix} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} [d_{ab} \quad d_{bc} \quad d_{ca}] \cdot \begin{bmatrix} \bar{i}_{ab} \\ \bar{i}_{bc} \\ \bar{i}_{ca} \end{bmatrix} - \frac{\bar{v}_{dc}}{RC} \end{cases} \quad (\text{abc coordinates})$$


$$\xrightarrow{\hspace{1cm}} \begin{cases} \frac{d}{dt} \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \\ \bar{i}_0 \end{bmatrix} = \frac{1}{3L} \begin{bmatrix} \bar{v}_d \\ \bar{v}_q \\ \bar{v}_0 \end{bmatrix} - \begin{bmatrix} 0 & -\omega & 0 \\ \omega & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \cdot \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \\ \bar{i}_0 \end{bmatrix} - \frac{1}{3L} \begin{bmatrix} d_d \\ d_q \\ d_0 \end{bmatrix} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} [d_d \quad d_q \quad d_0] \cdot \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \\ \bar{i}_0 \end{bmatrix} - \frac{\bar{v}_{dc}}{RC} \end{cases} \quad (\text{dq0 coordinates})$$

DB-128

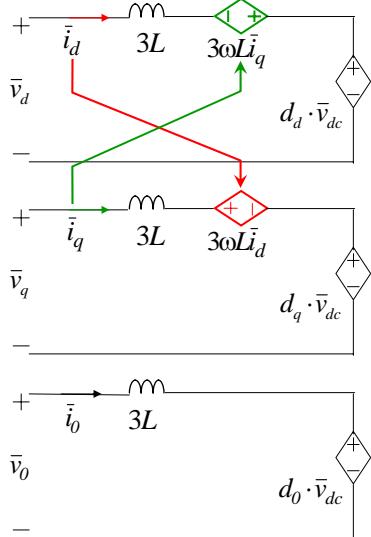Equivalent Circuit in dq0 Coordinates – Boost Rectifier –



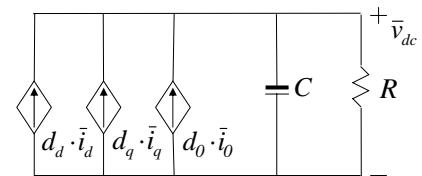The cross-coupling terms,
 $3\omega L\bar{i}_q$ and $3\omega L\bar{i}_d$,
in dc coordinates (dq0),
account for the voltage drops
across inductances at line
frequency in ac coordinates,
 $j \cdot 3\omega L\bar{i}_{ab}$, $j \cdot 3\omega L\bar{i}_{bc}$, $j \cdot 3\omega L\bar{i}_{ca}$.




DB-129

0-Channel

Since


$$\begin{cases} \bar{v}_{AB} + \bar{v}_{BC} + \bar{v}_{CA} \equiv 0 \\ \bar{i}_{ab} + \bar{i}_{bc} + \bar{i}_{ca} \equiv 0 \\ d_{ab} + d_{bc} + d_{ca} \equiv 0 \end{cases} \quad \Rightarrow \quad \begin{array}{l} \bar{v}_0 \equiv 0 \\ \bar{i}_0 \equiv 0 \\ d_0 \equiv 0 \end{array}$$

0-channel can be omitted

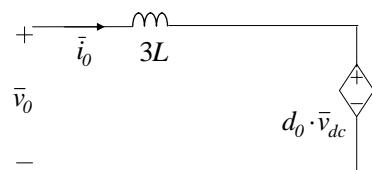

DB-130

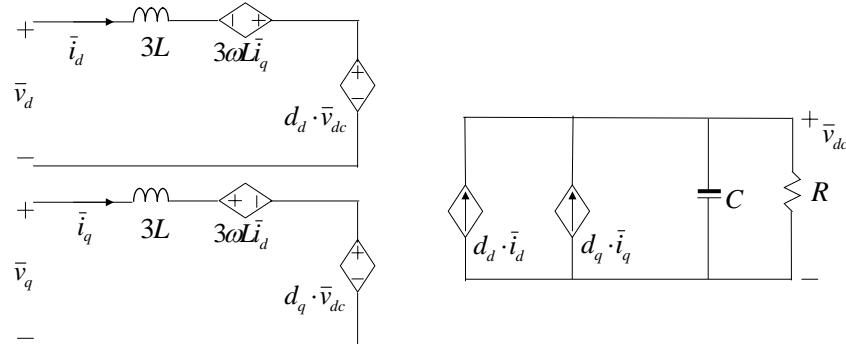Equivalent Circuit in dq0 Coordinates – Boost Rectifier –



$$\begin{cases} \frac{d}{dt} \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix} = \frac{1}{3L} \begin{bmatrix} \bar{v}_d \\ \bar{v}_q \end{bmatrix} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix} - \frac{1}{3L} \begin{bmatrix} d_d \\ d_q \end{bmatrix} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \begin{bmatrix} d_d & d_q \end{bmatrix} \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix} - \frac{\bar{v}_{dc}}{RC} \end{cases}$$

DB-131

State-Space Equations – Voltage Source Inverter –


$$\begin{cases} \frac{d\bar{i}_{l-l}}{dt} = \frac{1}{3L} \vec{d}_{l-l} \cdot \bar{v}_{dc} - \frac{1}{3L} \bar{v}_{l-L} \\ \frac{d\bar{v}_{l-L}}{dt} = \frac{1}{C} \bar{i}_{l-l} - \frac{1}{RC} \bar{v}_{l-L} \\ \bar{i}_{dc} = \vec{d}_{l-l}^T \cdot \bar{i}_{l-l} \end{cases} \quad (\text{abc coordinates})$$

Transformation 

$$\begin{cases} \frac{d\bar{i}_{dq0}}{dt} = \frac{1}{3L} \vec{d}_{dq0} \cdot \bar{v}_{dc} - \begin{bmatrix} 0 & -\omega & 0 \\ \omega & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \cdot \bar{i}_{dq0} - \frac{1}{3L} \bar{v}_{dq0} \\ \frac{d\bar{v}_{dq0}}{dt} = \frac{1}{C} \bar{i}_{dq0} - \begin{bmatrix} 0 & -\omega & 0 \\ \omega & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \cdot \bar{v}_{dq0} - \frac{1}{RC} \bar{v}_{dq0} \\ \bar{i}_{dc} = \vec{d}_{dq0}^T \cdot \bar{i}_{dq0} \end{cases} \quad (\text{dq0 coordinates})$$

DB-132


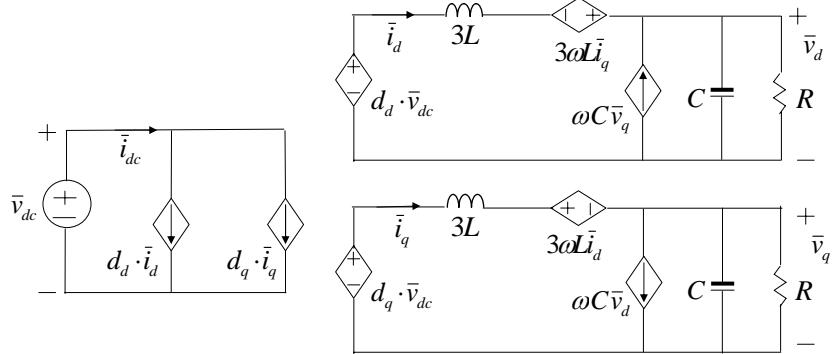
Equivalent Circuit in dq0 Coordinates – Voltage Source Inverter –



$$\left\{ \begin{array}{l} \frac{d\bar{i}_{dq}}{dt} = \frac{1}{3L} \bar{d}_{dq} \cdot \bar{v}_{dc} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \bar{i}_{dq} - \frac{1}{3L} \bar{v}_{dq} \\ \frac{d\bar{v}_{dq}}{dt} = \frac{1}{C} \bar{i}_{dq} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \bar{v}_{dq} - \frac{1}{RC} \bar{v}_{dq} \\ \bar{i}_{dc} = \bar{d}_{dq}^T \cdot \bar{i}_{dq} \end{array} \right.$$

DB-133

Buck Rectifier / CSI dq0 Model – similar approach but different results –

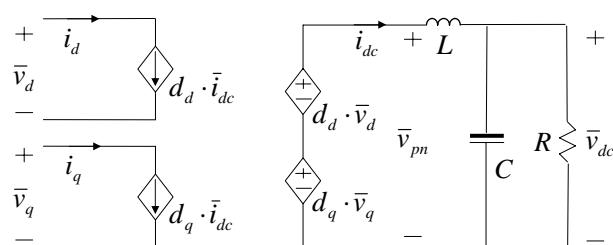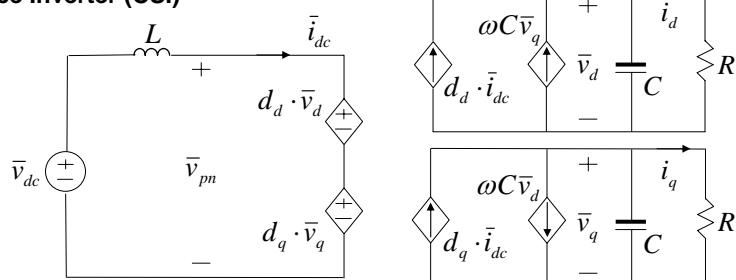Buck Rectifier**Current Source Inverter (CSI)**

DB-134

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
- 4. Small-Signal Modeling**
 - Small-signal model of boost rectifier
 - Small-signal model of VSI
 - Three-phase modulator modeling
- 5. Closed-Loop Control Design**
- 6. More Complex Converters**

DB-135

Autonomous dynamic system: $\frac{d\vec{x}}{dt} = \vec{f}(\vec{x}, \vec{u})$

If \vec{f} is analytic it can be expressed as Taylor series:

$$\begin{aligned}\vec{f}(\vec{x}, \vec{u}) &= \vec{f}(\vec{x}_0, \vec{u}_0) + \frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{x}} \cdot (\vec{x} - \vec{x}_0) + \frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{u}} \cdot (\vec{u} - \vec{u}_0) + \\ &+ \frac{1}{2!} \left[\frac{\partial^2 \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{x}^2} (\vec{x} - \vec{x}_0)^2 + \frac{\partial^2 \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{x} \partial \vec{u}} (\vec{x} - \vec{x}_0)(\vec{u} - \vec{u}_0) + \frac{\partial^2 \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{u}^2} (\vec{u} - \vec{u}_0)^2 \right] \\ &+ \dots\end{aligned}$$

Retaining the first 3 terms results in linear approximation of \vec{f} :

$$\vec{f}(\vec{x}, \vec{u}) \approx \vec{f}(\vec{x}_0, \vec{u}_0) + \frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{x}} \cdot (\vec{x} - \vec{x}_0) + \frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{u}} \cdot (\vec{u} - \vec{u}_0)$$

But the dynamic system is **NOT** linear because:

$$\frac{d\vec{x}}{dt} \cong \underbrace{\frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{x}} \cdot \vec{x}}_{\vec{x} = \mathbf{A} \vec{x}} + \underbrace{\frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{u}} \cdot \vec{u}}_{\vec{u} = \mathbf{B} \vec{u}} + \underbrace{\vec{f}(\vec{x}_0, \vec{u}_0) - \frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{x}} \cdot \vec{x}_0 - \frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{u}} \cdot \vec{u}_0}_{\vec{g} \neq 0}$$

DB-136

Linearization

$$\frac{d\vec{x}}{dt} = \vec{f}(\vec{x}, \vec{u}) \cong \vec{f}(\vec{x}_0, \vec{u}_0) + \frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{x}} \cdot (\vec{x} - \vec{x}_0) + \frac{\partial \vec{f}(\vec{x}_0, \vec{u}_0)}{\partial \vec{u}} \cdot (\vec{u} - \vec{u}_0)$$

If (\vec{x}_0, \vec{u}_0) is an equilibrium point (\vec{X}, \vec{U}) , and $(\tilde{\vec{x}}, \tilde{\vec{u}})$ is perturbation around it:

$$\Rightarrow \underline{\vec{f}(\vec{X}, \vec{U}) \equiv 0} \quad \vec{x} = \vec{X} + \tilde{\vec{x}} \quad \vec{u} = \vec{U} + \tilde{\vec{u}}$$

$$\Rightarrow \underline{\frac{d\vec{X}}{dt} = 0} \quad \Rightarrow \quad \frac{d\vec{x}}{dt} = \frac{d\vec{X}}{dt} + \frac{d\tilde{\vec{x}}}{dt} = \frac{d\tilde{\vec{x}}}{dt}$$


$$\Rightarrow \frac{d\tilde{\vec{x}}}{dt} \cong \left. \frac{\partial \vec{f}(\vec{x}, \vec{u})}{\partial \vec{x}} \right|_{(\vec{X}, \vec{U})} \cdot \tilde{\vec{x}} + \left. \frac{\partial \vec{f}(\vec{x}, \vec{u})}{\partial \vec{u}} \right|_{(\vec{X}, \vec{U})} \cdot \tilde{\vec{u}}$$

$$\tilde{\vec{x}} = \mathbf{A} \cdot \tilde{\vec{x}} + \mathbf{B} \cdot \tilde{\vec{u}}$$

$$\Rightarrow \mathbf{A} = \left. \frac{\partial \vec{f}(\vec{x}, \vec{u})}{\partial \vec{x}} \right|_{(\vec{X}, \vec{U})} \quad \mathbf{B} = \left. \frac{\partial \vec{f}(\vec{x}, \vec{u})}{\partial \vec{u}} \right|_{(\vec{X}, \vec{U})}$$

DB-137

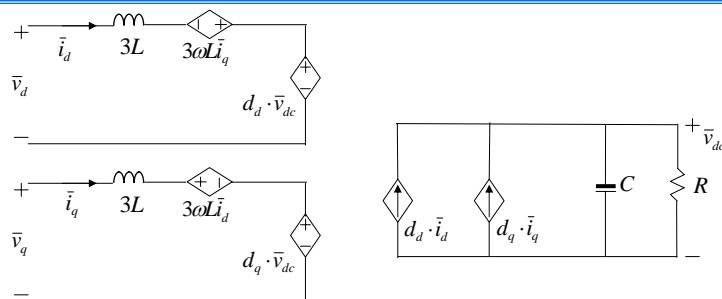Average Large-Signal Model Boost Rectifier



A steady-state operating point:

$$V_d = \sqrt{\frac{3}{2}} \cdot V_m \quad (V_m: \text{Max line-to-line voltage})$$

$$V_q = 0$$

$$D_d = \frac{V_d}{V_{dc}}$$

$$D_q = -\frac{3\omega L I_d}{V_{dc}}$$

$$I_d = \frac{V_{dc}}{R \cdot D_d}$$

$$I_q = 0$$

DB-138

Linearization – Boost Rectifier

$$\left\{ \begin{array}{l} \frac{d}{dt} \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix} = \frac{1}{3L} \begin{bmatrix} \bar{v}_d \\ \bar{v}_q \end{bmatrix} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix} - \frac{1}{3L} \begin{bmatrix} d_d \\ d_q \end{bmatrix} \cdot \bar{v}_{dc} \\ \frac{d\bar{v}_{dc}}{dt} = \frac{1}{C} \begin{bmatrix} d_d & d_q \end{bmatrix} \cdot \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix} - \frac{\bar{v}_{dc}}{RC} \end{array} \right. \quad \text{Linearization} \rightarrow$$

$$\left\{ \begin{array}{l} \frac{d}{dt} \begin{bmatrix} \tilde{i}_d \\ \tilde{i}_q \end{bmatrix} = \frac{1}{3L} \begin{bmatrix} \tilde{v}_d \\ \tilde{v}_q \end{bmatrix} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \begin{bmatrix} \tilde{i}_d \\ \tilde{i}_q \end{bmatrix} - \frac{1}{3L} \begin{bmatrix} \tilde{d}_d \\ \tilde{d}_q \end{bmatrix} \cdot V_{dc} - \frac{1}{3L} \begin{bmatrix} D_d \\ D_q \end{bmatrix} \cdot \tilde{v}_{dc} \\ \frac{d\tilde{v}_{dc}}{dt} = \frac{1}{C} \begin{bmatrix} \tilde{d}_d & \tilde{d}_q \end{bmatrix} \cdot \begin{bmatrix} I_d \\ I_q \end{bmatrix} + \frac{1}{C} \begin{bmatrix} D_d & D_q \end{bmatrix} \cdot \begin{bmatrix} \tilde{i}_d \\ \tilde{i}_q \end{bmatrix} - \frac{\tilde{v}_{dc}}{RC} \end{array} \right.$$

DB-139


Small-Signal Model – Boost Rectifier

$$\dot{\vec{x}} = \mathbf{A} \vec{x} + \mathbf{B} \vec{u} + \mathbf{D} \vec{v}$$

$\underbrace{\dot{\vec{x}}}_{\text{Intrinsic System Dynamics}}$ $\underbrace{\vec{x}}_{\text{Control Input}}$ $\underbrace{\vec{u}}_{\text{Disturbance Input}}$ $\underbrace{\vec{v}}_{\text{Disturbance Input}}$

DB-140



Small-Signal Model – Boost Rectifier

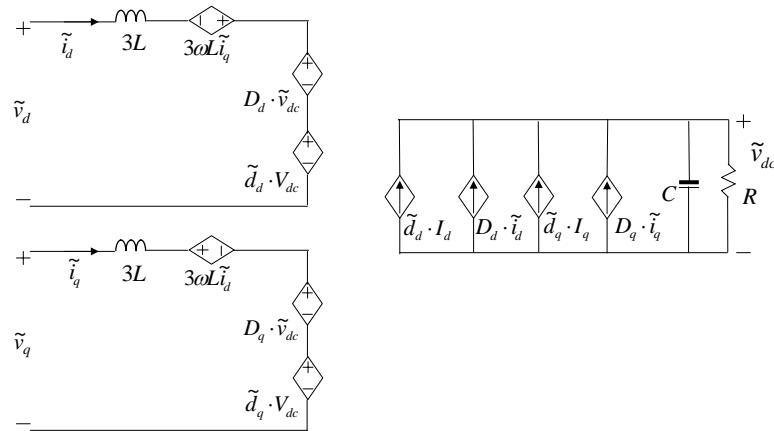

DB-141

Open-Loop Transfer Functions
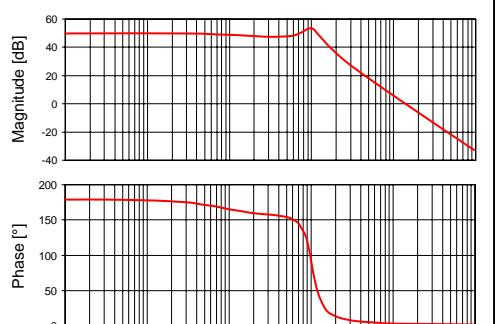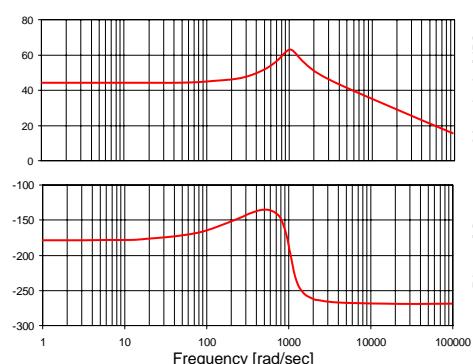
$$\frac{\tilde{i}_d}{\tilde{d}_d} = \frac{K_{iddd} \cdot (s + z_{iddd1}) \cdot (s + z_{iddd2})}{(s + p_1) \cdot (s + p_2) \cdot (s + p_2^*)}$$





$$\frac{\tilde{i}_q}{\tilde{d}_q} = \frac{K_{iddq} \cdot (s + z_{iddq})}{(s + p_1) \cdot (s + p_2) \cdot (s + p_2^*)}$$

DB-142

Open-Loop Transfer Functions
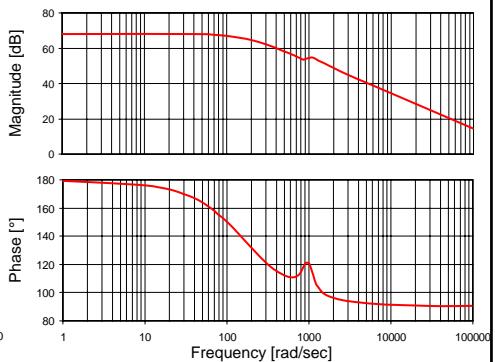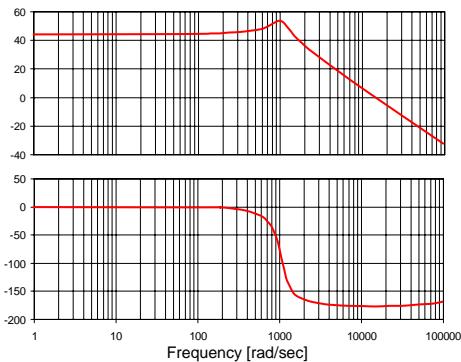
$$\frac{\tilde{i}_q}{\tilde{d}_d} = \frac{K_{iqdd} \cdot (s + z_{iqdd\ 1}) \cdot (s + z_{iqdd\ 2})}{(s + p_1) \cdot (s + p_2) \cdot (s + p_2^*)}$$





$$\frac{\tilde{i}_q}{\tilde{d}_q} = \frac{K_{iqdq} \cdot (s + z_{iqdq}) \cdot (s + z_{iqdq}^*)}{(s + p_1) \cdot (s + p_2) \cdot (s + p_2^*)}$$

DB-143

Open-Loop Transfer Functions
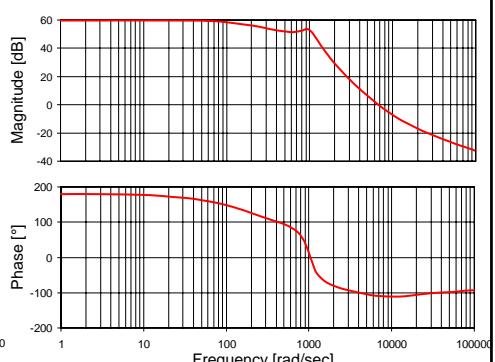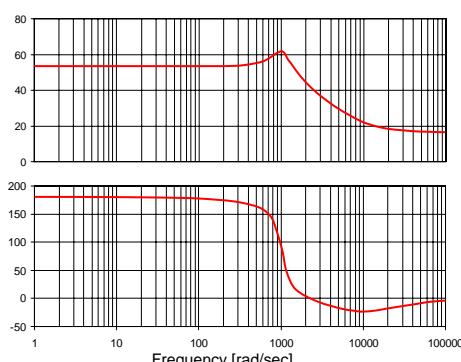
$$\frac{\tilde{v}_{dc}}{\tilde{d}_d} = \frac{K_{vdcd} \cdot (s + z_{vdcd\ 1}) \cdot (s + z_{vdcd\ 2}) \cdot (s - z_{RHP})}{(s + p_1) \cdot (s + p_2) \cdot (s + p_2^*)}$$




$$\frac{\tilde{v}_{dc}}{\tilde{d}_q} = \frac{K_{vdcdq} \cdot (s + z_{vdcdq\ 1}) \cdot (s - z_{RHP})}{(s + p_1) \cdot (s + p_2) \cdot (s + p_2^*)}$$

DB-144

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
- 4. Small-Signal Modeling**
 - Small-signal model of boost rectifier
 - Small-signal model of VSI
 - Three-phase modulator modeling
- 5. Closed-Loop Control Design**
- 6. More Complex Converters**

DB-145

Average Large-Signal Model – VSI

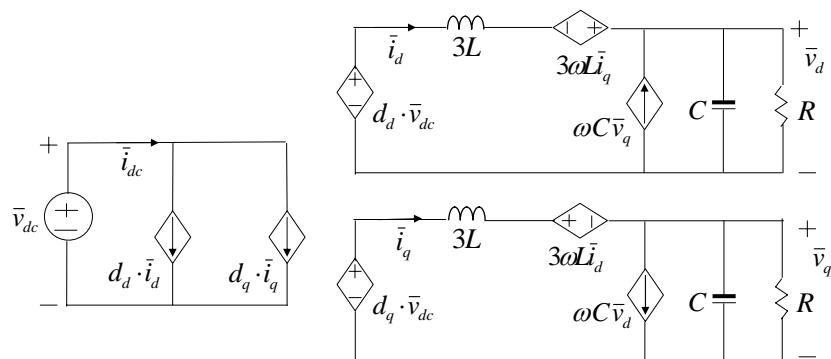

A steady-state operating point:

$$I_d = \frac{V_d}{R} - \omega C V_q$$

$$D_d = \frac{V_d - 3\omega L I_q}{V_{dc}}$$

$$I_q = \frac{V_q}{R} + \omega C V_d$$

$$D_q = \frac{V_q + 3\omega L I_d}{V_{dc}}$$

DB-146

Linearization – VSI


$$\begin{cases}
 \frac{d}{dt} \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix} = \frac{1}{3L} \begin{bmatrix} d_d \\ d_q \end{bmatrix} \cdot \bar{v}_{dc} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix} - \frac{1}{3L} \begin{bmatrix} \bar{v}_d \\ \bar{v}_q \end{bmatrix} \\
 \frac{d}{dt} \begin{bmatrix} \bar{v}_d \\ \bar{v}_q \end{bmatrix} = \frac{1}{C} \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \begin{bmatrix} \bar{v}_d \\ \bar{v}_q \end{bmatrix} - \frac{1}{RC} \begin{bmatrix} \bar{v}_d \\ \bar{v}_q \end{bmatrix} \\
 i_{dc} = [d_d \quad d_q] \cdot \begin{bmatrix} \bar{i}_d \\ \bar{i}_q \end{bmatrix}
 \end{cases}$$

Linearization \rightarrow

$$\begin{cases}
 \frac{d}{dt} \begin{bmatrix} \tilde{i}_d \\ \tilde{i}_q \end{bmatrix} = \frac{1}{3L} \begin{bmatrix} \tilde{d}_d \\ \tilde{d}_q \end{bmatrix} \cdot V_{dc} + \frac{1}{3L} \begin{bmatrix} D_d \\ D_q \end{bmatrix} \cdot \tilde{v}_{dc} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \begin{bmatrix} \tilde{i}_d \\ \tilde{i}_q \end{bmatrix} - \frac{1}{3L} \begin{bmatrix} \tilde{v}_d \\ \tilde{v}_q \end{bmatrix} \\
 \frac{d}{dt} \begin{bmatrix} \tilde{v}_d \\ \tilde{v}_q \end{bmatrix} = \frac{1}{C} \begin{bmatrix} \tilde{i}_d \\ \tilde{i}_q \end{bmatrix} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \begin{bmatrix} \tilde{v}_d \\ \tilde{v}_q \end{bmatrix} - \frac{1}{RC} \begin{bmatrix} \tilde{v}_d \\ \tilde{v}_q \end{bmatrix} \\
 \tilde{i}_{dc} = [D_d \quad D_q] \cdot \begin{bmatrix} \tilde{i}_d \\ \tilde{i}_q \end{bmatrix} + [\tilde{d}_d \quad \tilde{d}_q] \cdot \begin{bmatrix} I_d \\ I_q \end{bmatrix}
 \end{cases}$$

DB-147

Small-Signal Circuit Model – VSI

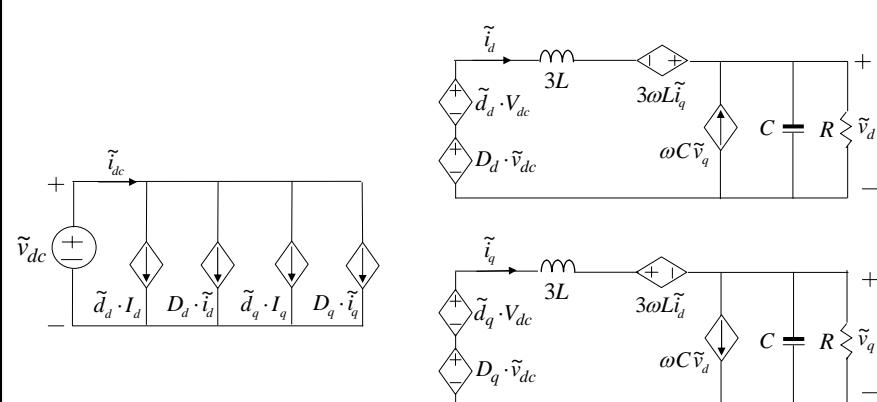

DB-148

Small-Signal State-Space Model – VSI

$$\underbrace{\frac{d}{dt} \begin{bmatrix} \tilde{i}_d \\ \tilde{i}_q \\ \tilde{v}_d \\ \tilde{v}_q \end{bmatrix}}_{\dot{\vec{x}}} = \underbrace{\begin{bmatrix} 0 & \omega & -\frac{1}{3L} & 0 \\ -\omega & 0 & 0 & -\frac{1}{3L} \\ \frac{1}{C} & 0 & -\frac{1}{RC} & \omega \\ 0 & \frac{1}{C} & -\omega & -\frac{1}{RC} \end{bmatrix}}_{\mathbf{A}} \cdot \underbrace{\begin{bmatrix} \tilde{i}_d \\ \tilde{i}_q \\ \tilde{v}_d \\ \tilde{v}_q \end{bmatrix}}_{\vec{x}} + \underbrace{\begin{bmatrix} \frac{V_{dc}}{3L} & 0 \\ 0 & \frac{V_{dc}}{3L} \\ 0 & 0 \\ 0 & 0 \end{bmatrix}}_{\mathbf{B}} \cdot \underbrace{\begin{bmatrix} \tilde{d}_d \\ \tilde{d}_q \end{bmatrix}}_{\vec{u}} + \underbrace{\begin{bmatrix} \frac{D_d}{3L} \\ \frac{D_q}{3L} \\ 0 \\ 0 \end{bmatrix}}_{\mathbf{D}} \cdot \underbrace{\tilde{v}_{dc}}_{\vec{v}}$$

DB-149

Outline



PECon
2008

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
- 4. Small-Signal Modeling**
 - Small-signal model of boost rectifier
 - Small-signal model of VSI
 - Three-phase modulator modeling
- 5. Closed-Loop Control Design**
- 6. More Complex Converters**



DB-150

Natural and Uniform Sampling

Natural Sampling

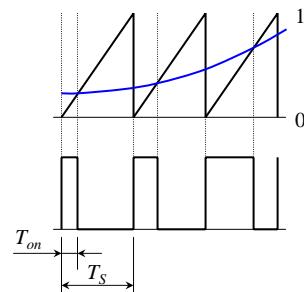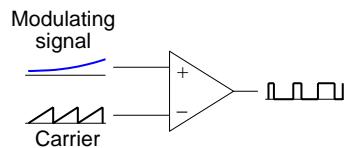



Uniform Sampling

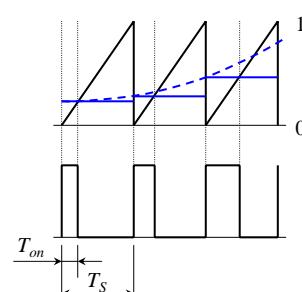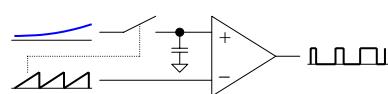



DB-151

Trailing- and Leading-Edge Modulation

Trailing-Edge Modulation

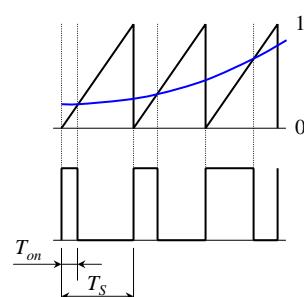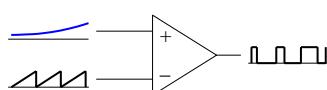

Leading-Edge Modulation

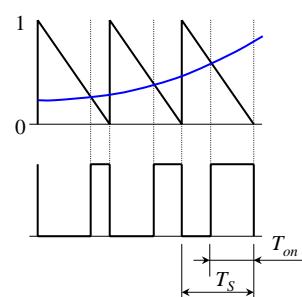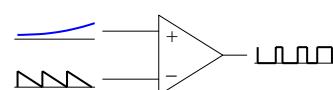

☞ Both are the natural sampling

DB-152


Review of Modulator Modeling for DC-DC Converters

- Natural sampling
 - Unity gain
 - No delay
- Uniform sampling
 1. Trailing-edge modulation
 - Unity gain
 - Phase delay at a modulation frequency
$$D \cdot T_s \cdot \omega_m$$
 2. Leading-edge modulation
 - Unity gain
 - Phase delay at a modulation frequency
$$(1 - D) \cdot T_s \cdot \omega_m$$

DB-153

Three-Phase Modulator Modeling

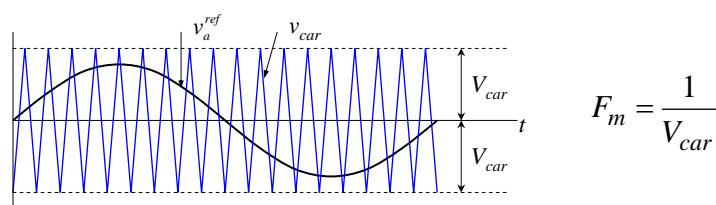
- All naturally sampled modulators can be modeled by the constant gain term
 - Modulators associated with analog controllers
- Small-signal models **have to be derived** for uniformly sampled three-phase modulators
 - Modulators associated with digital controllers



DB-154

Example – for Boost Rectifier and VSI


- Trailing-edge modulation (2Φ-RA)

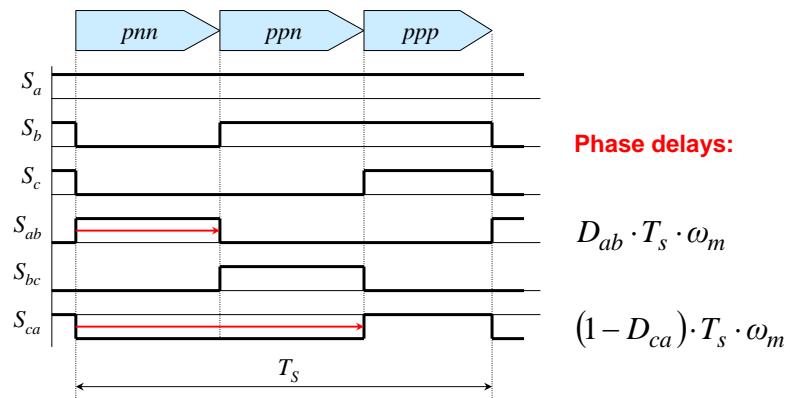

- Two out of three switching functions always have pulses synchronized to the beginning of the switching period

DB-155

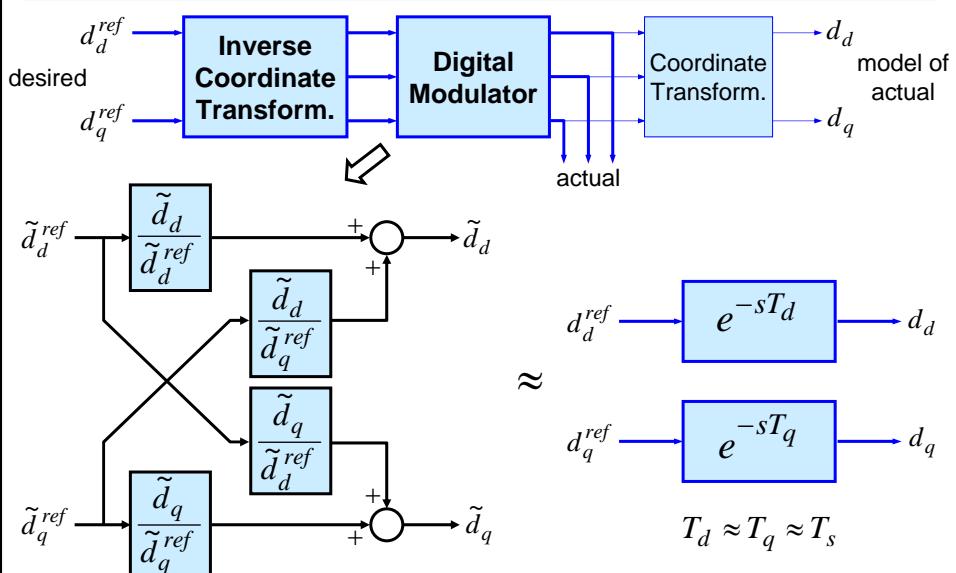Approximate Average Model of Digital Modulator




DB-156

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**
 - **Control approach**
 - **Current-loop design**
 - **Voltage-loop design**
 - **Limiting**
- 6. More Complex Converters**

DB-157

Classical Linear Control Design Approach

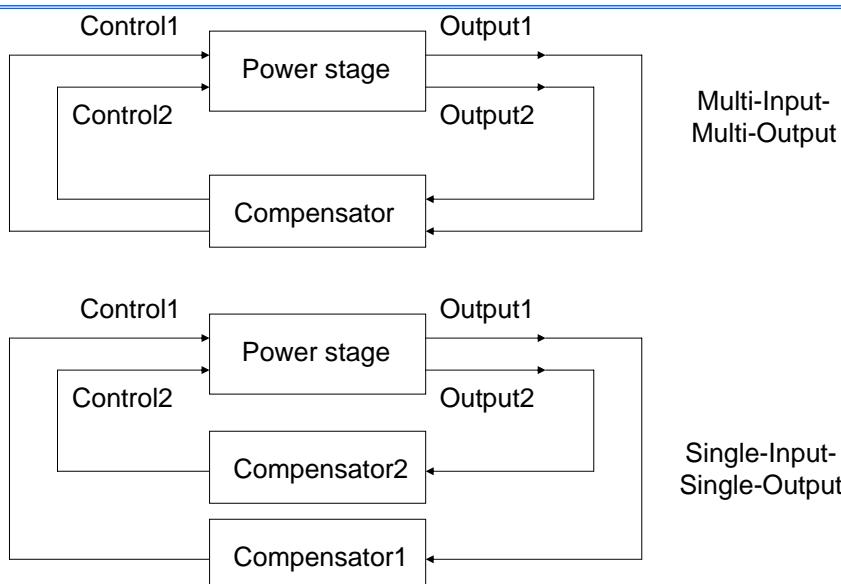

DB-158

Closed-Loop Control Design

- Based on small-signal models

Advantage

- Classical control design methods can be used
(Bode plots, root loci, etc.)


Disadvantages

- Design is valid only at a certain operating point
- The approach does not guarantee large-signal stability

DB-159

Control Structure: Cascade Control

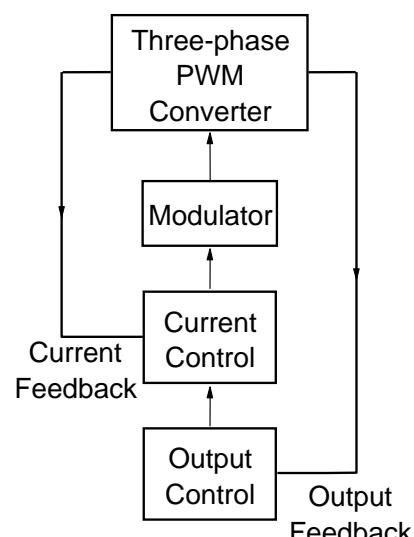1. Inner current control
 - a. Bang-bang current control (and PWM) in stationary coordinates
 - b. Current control in stationary coordinates with two independent or three dependent current controllers (P, PI, or resonant regulators)
 - c. Current control in rotating coordinates with two independent current controllers (P or PI regulators)
2. Outer output voltage or torque / flux / speed / position control (PI regulators)




DB-160

Control Realization

1. Completely analog control
Complete analog control is rarely used because of hardware complexity
2. Combination of analog and digital control
Analog current control in stationary and digital output voltage or speed and flux control
3. Completely digital control
Used in most new designs


DB-161

Open-loop Boost Rectifier Control

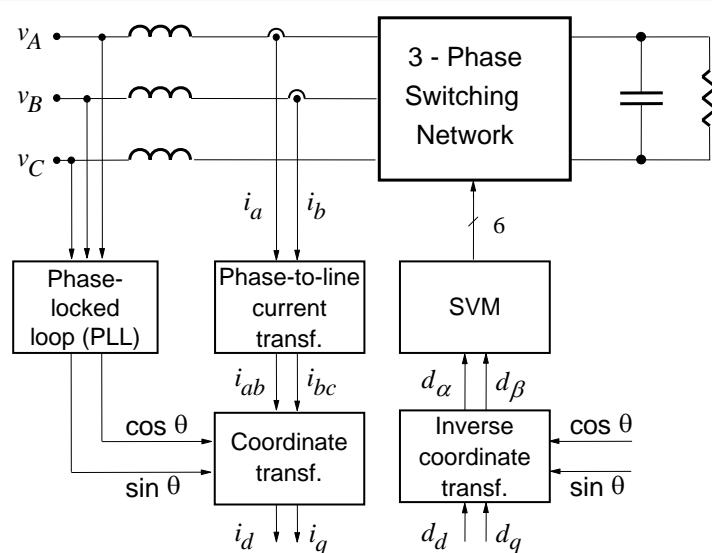


DB-162

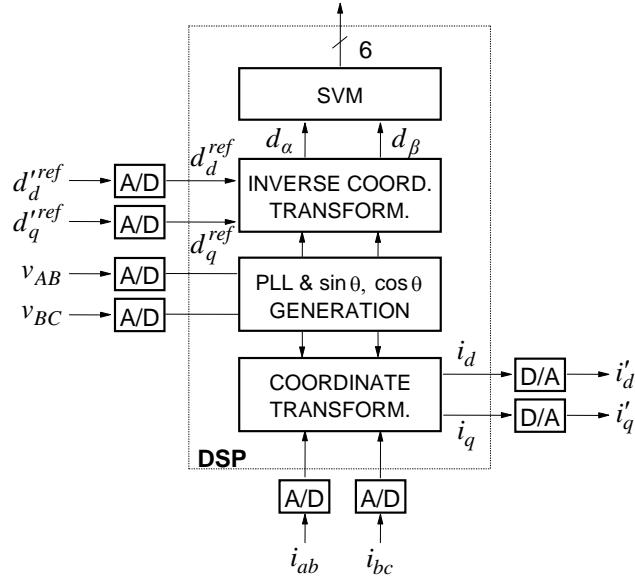Open-loop Boost Rectifier Control Digital Signal Processor (DSP) Implementation




DB-163

Transfer Function Measurement Set-up

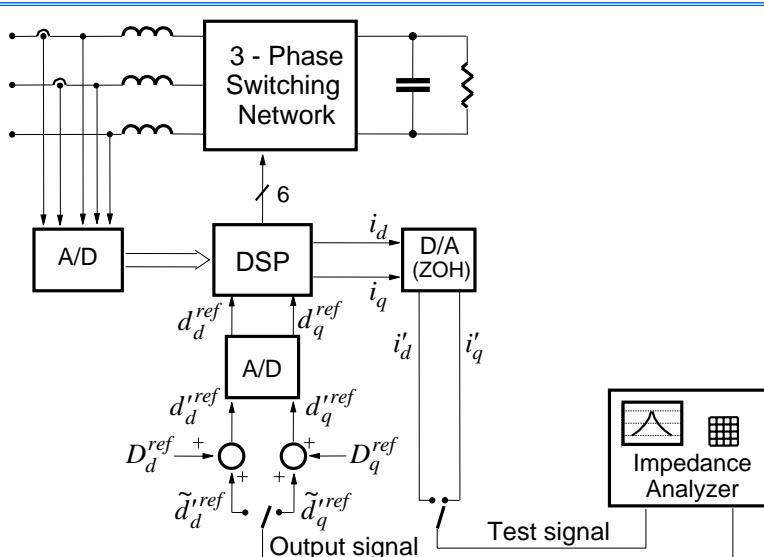


DB-164

Digital Delay

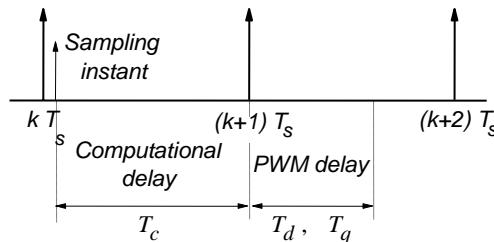


- Modified small-signal model

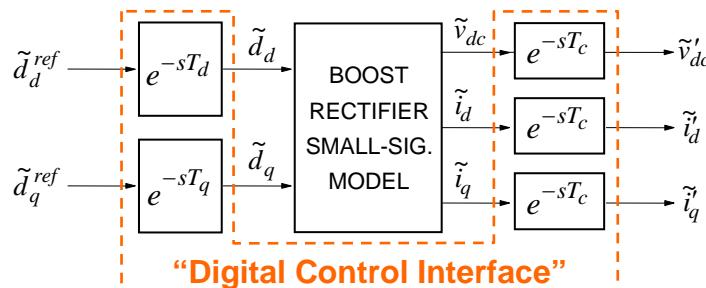

DB-165

Digital Delay

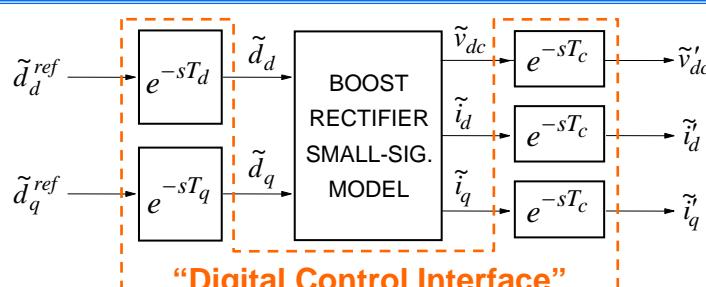

- Simplified approximations in continuous time domain:

$$e^{-sT_{del}} \approx \frac{1 - \frac{sT_{del}}{2} + \frac{(sT_{del})^2}{12}}{1 + \frac{sT_{del}}{2} + \frac{(sT_{del})^2}{12}}$$


- Often choose: $T_{del} \approx T_c \approx T_d \approx T_q \approx T_{sampling} = T_{switching}$

DB-166

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**
 - Control approach
 - Current-loop design
 - Voltage-loop design
 - Limiting
- 6. More Complex Converters**


DB-167

Current Loop Design

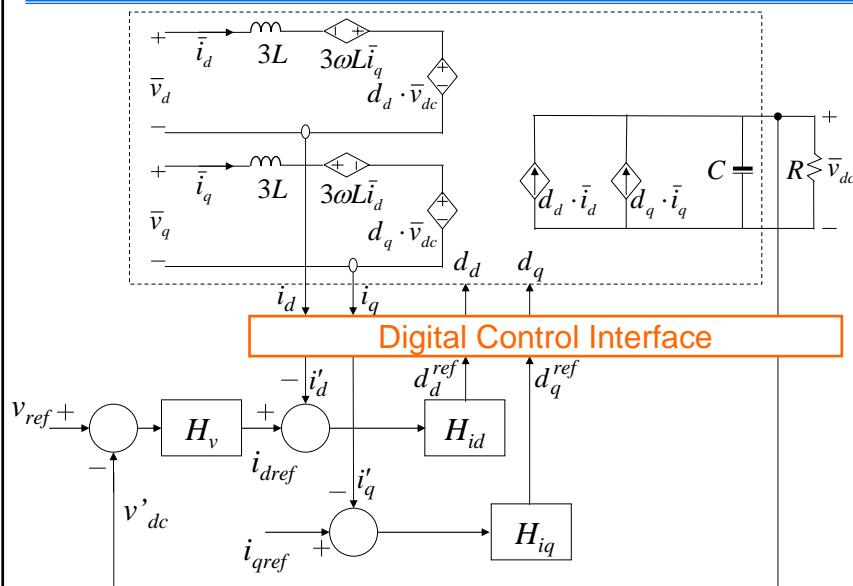

DB-168


Control-to-Current Transfer Function

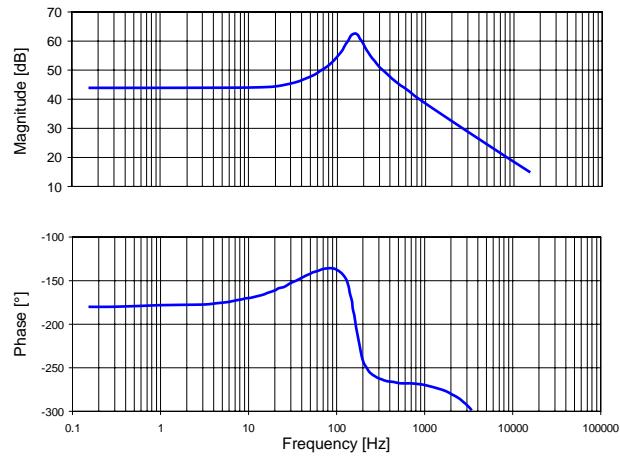

$$\frac{\tilde{i}_d}{\tilde{d}_d} = \frac{K_{iddd} \cdot (s + z_{iddd\ 1}) \cdot (s + z_{iddd\ 2})}{(s + p_1) \cdot (s + p_2) \cdot (s + p_2^*)} \quad H_{id} = K_p + \frac{K_i}{s}$$

DB-169



Control-to-Current Transfer Function

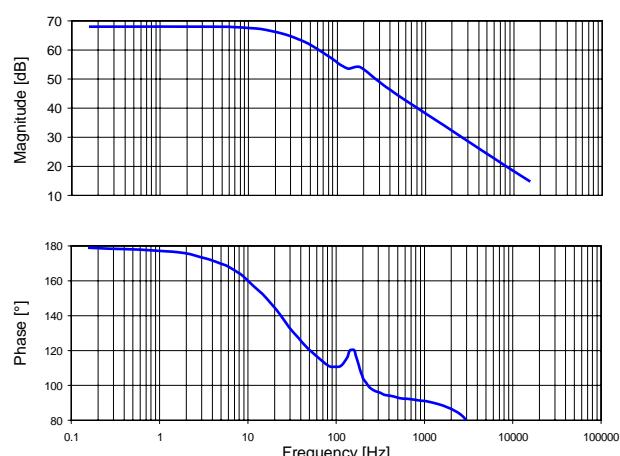

$$\frac{\tilde{i}_q}{\tilde{d}_q} = \frac{K_{iqdq} \cdot (s + z_{iqdq}) \cdot (s + z_{iqdq}^*)}{(s + p_1) \cdot (s + p_2) \cdot (s + p_2^*)} \quad H_{iq} = K_p + \frac{K_i}{s}$$

DB-170



Current Loop-Gain

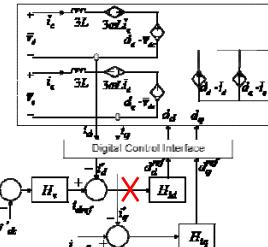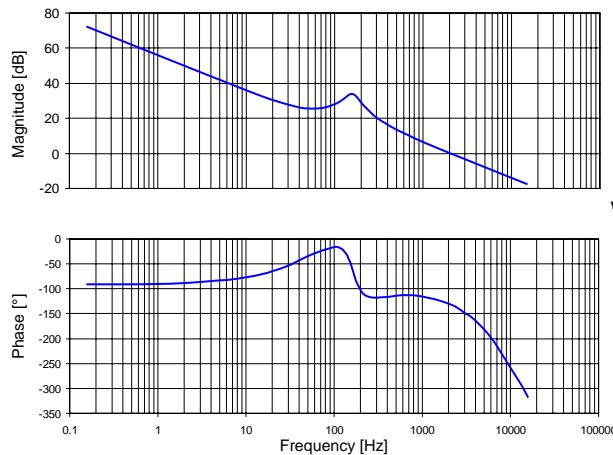

- D channel loop-gain T_d
- Bandwidth is limited by delay ($f_{sw}=20\text{kHz}$)

DB-171

Current Loop-Gain

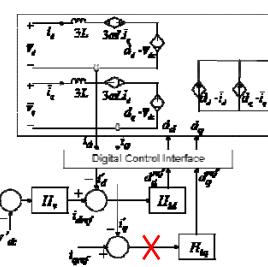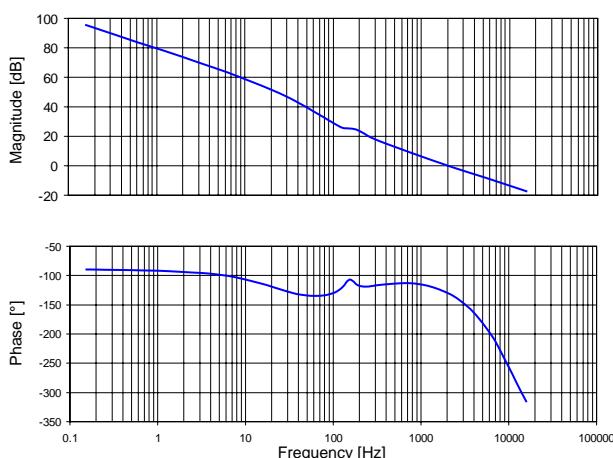


- Q channel loop-gain T_q
- Bandwidth is limited by delay ($f_{sw}=20\text{kHz}$)

DB-172


Current Regulation

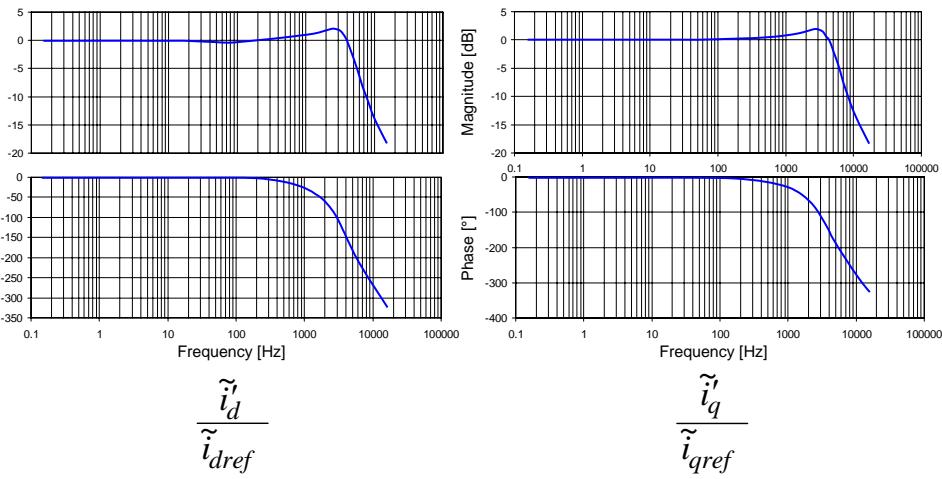- Peak is more pronounced when gain increases



DB-173

Current Loop with D and Q Decoupling

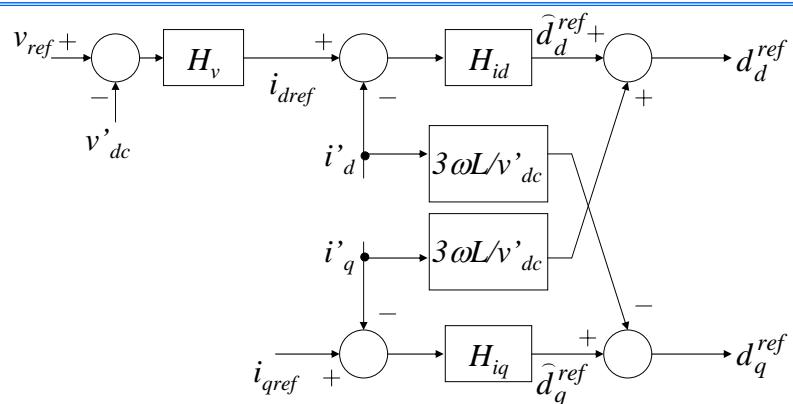


$$d_d = d_d^{ref} \cdot e^{-sT_d} = (\hat{d}_d^{ref} + 3\omega L i'_q / v'_{dc}) \cdot e^{-sT_d} = \hat{d}_d + 3\omega L \frac{1}{v'_{dc}} \cdot e^{-sT_d} \cdot i'_q$$

$$d_q = d_q^{ref} \cdot e^{-sT_q} = (\hat{d}_q^{ref} - 3\omega L i'_d / v'_{dc}) \cdot e^{-sT_q} = \hat{d}_q - 3\omega L \frac{1}{v'_{dc}} \cdot e^{-sT_q} \cdot i'_d$$

DB-174


Decoupled D and Q Channels

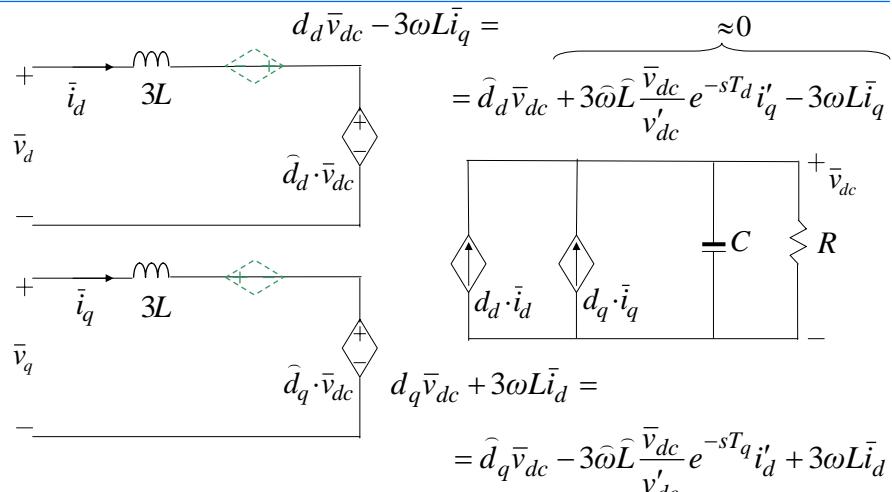

- Similar to two parallel dc-dc boost converters after d and q decoupled

DB-175

Cross-Coupling Effect After Decoupling

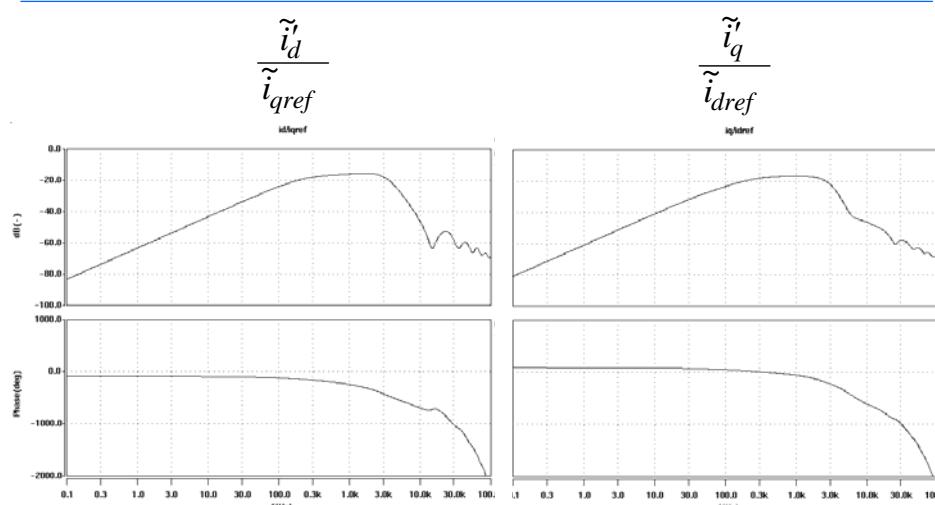


DB-176

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**
 - Control approach
 - Current-loop design
 - **Voltage-loop design**
 - Limiting
- 6. More Complex Converters**

DB-177


Output Voltage Loop Design

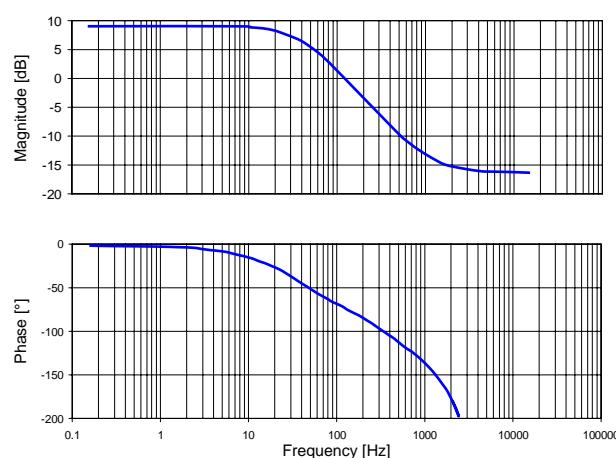

$$G_c = \frac{\tilde{v}_{dc}}{\tilde{i}_{dref}} = \frac{K \cdot (s - z_{RHP})}{(s + p_L) \cdot (s + p_H)}$$

DB-178

COMPENSATOR DESIGN

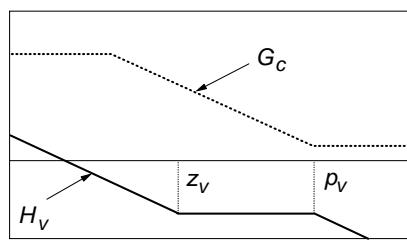


- Voltage compensator

$$H_V = \frac{K_V(1 + s/z_V)}{s(1 + s/p_V)}$$


- Place z_V as high as possible for required phase margin.
- Place p_V for loop-gain attenuation.
- Attainable voltage-loop bandwidth:

$$\omega_c < 1/4 z_{RHP}$$

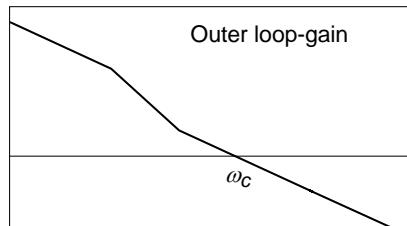

DB-179

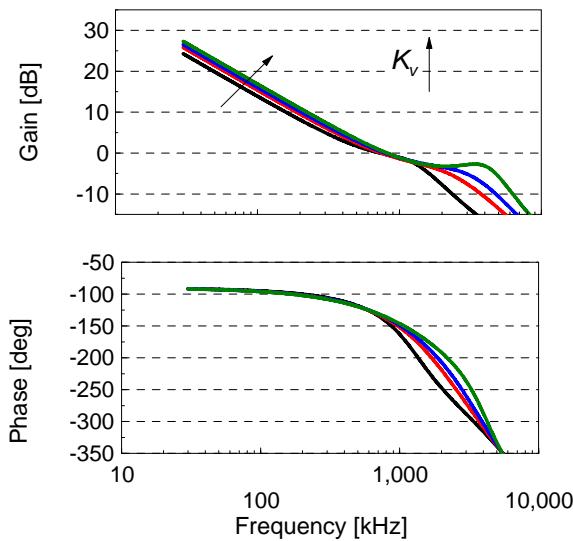Attainable Voltage Loop Bandwidth with Delay





- Voltage compensator


$$H_V = \frac{K_V(1 + s/z_V)}{s(1 + s/p_V)}$$

- Zero is placed close to the crossover to improve the phase margin

DB-180

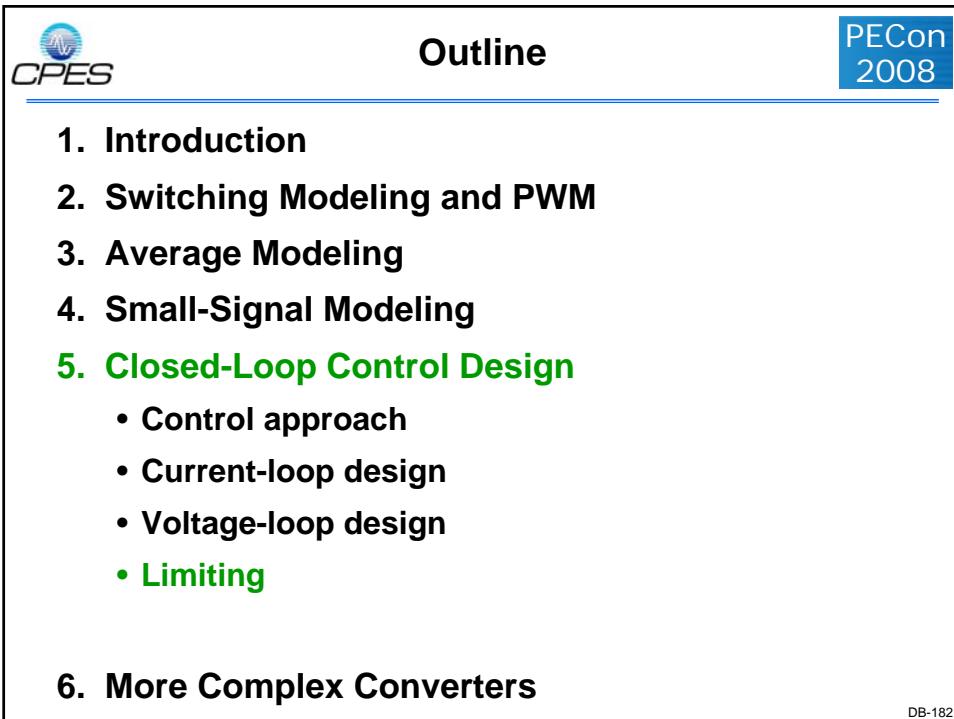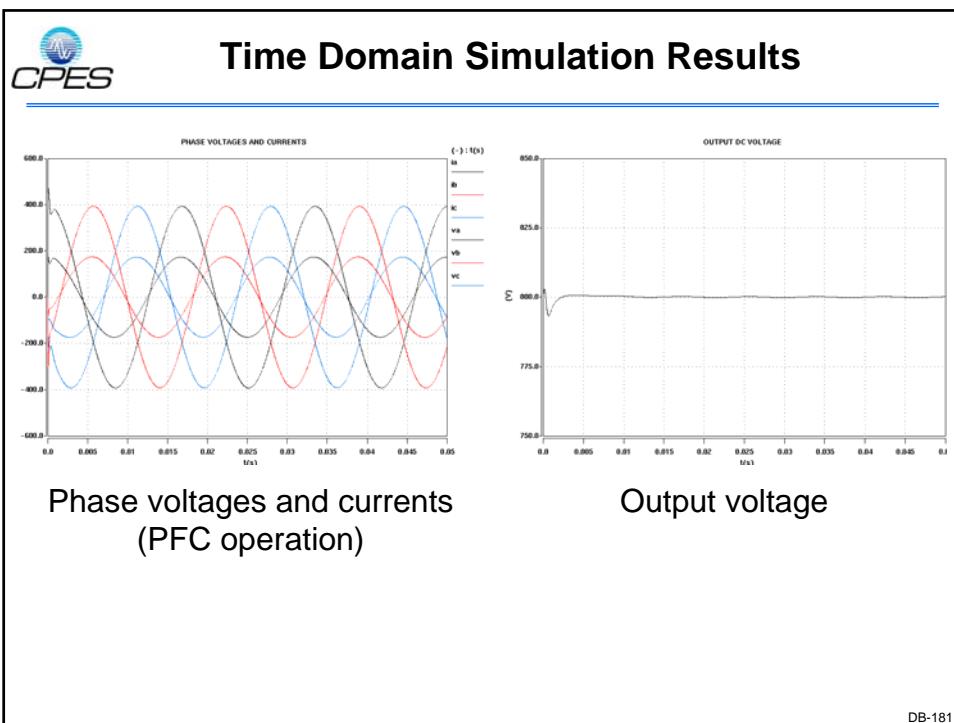


LIMITING IN THREE-PHASE CONVERTERS

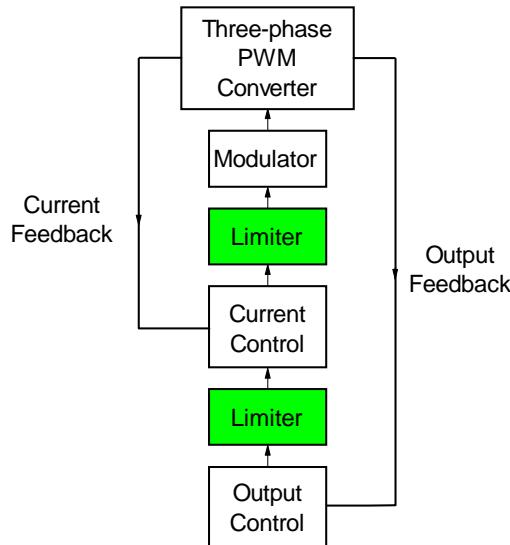

DB-183

Duty Cycle Limiting

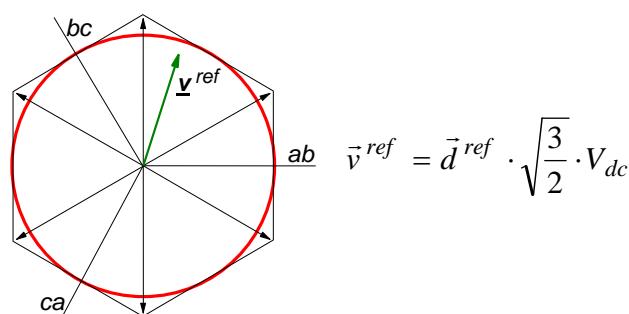- Boost Rectifier/VSI Switching State Hexagon




- Maximal attainable voltage vector lies on the hexagon
- For sinusoidal average output voltages the voltage vector must be inside the inscribed circle

$$|\vec{v}^{ref}| \leq \sqrt{\frac{3}{2}} \cdot V_{dc} \Rightarrow |\vec{d}^{ref}| \leq 1 \Rightarrow d_d^2 + d_q^2 \leq 1$$

DB-184

Duty Cycle Limiting

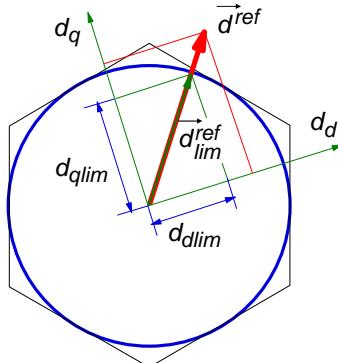

$$\text{If } d_d^2 + d_q^2 > 1$$


$$d_{d \text{ lim}} = \frac{d_d}{\sqrt{d_d^2 + d_q^2}}$$

$$d_{q \text{ lim}} = \frac{d_q}{\sqrt{d_d^2 + d_q^2}}$$

- Vector angle is kept constant
- $(d_d)_{lim}$ and $(d_q)_{lim}$ should be fed back to the anti-windup current controllers
- If output of each current controller is limited separately it can result in unattainable voltage vector

DB-185

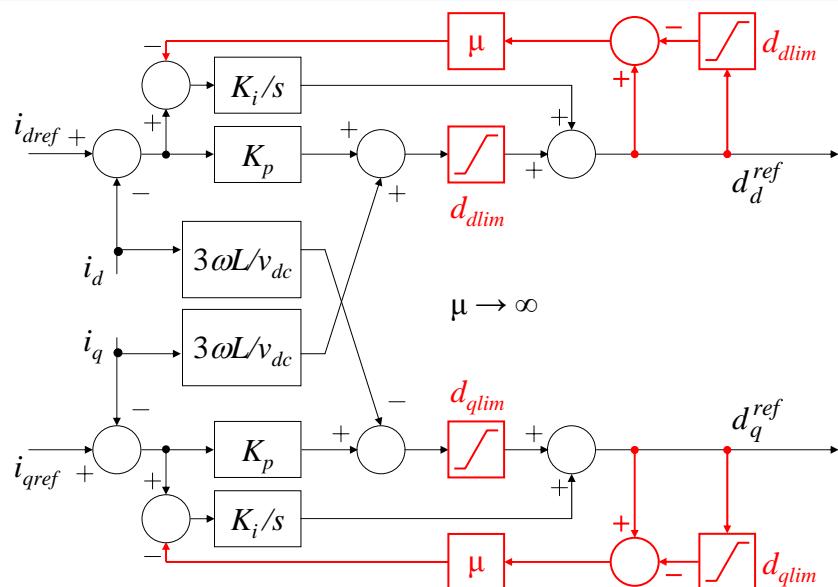Variable Limit PI (“Smart Anti-windup”) Current Controllers



DB-186

Current Limiting


- Maximal current magnitude is limited

$$\sqrt{(i_d^{ref})^2 + (i_q^{ref})^2} \leq I_{max}$$

- Limiting of each reference current component is determined by the control algorithm

EXAMPLE

- Boost rectifier control

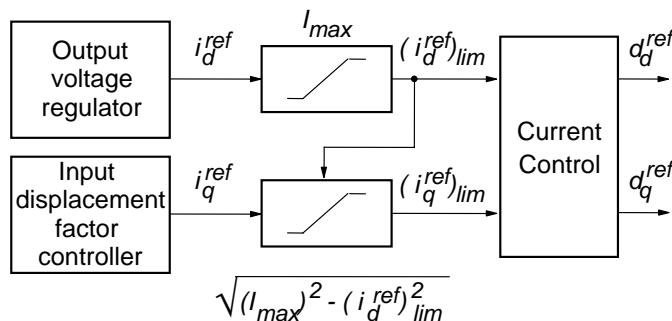



DB-187

Outline

1. Introduction
 2. Switching Modeling and PWM
 3. Average Modeling
 4. Small-Signal Modeling
 5. Closed-Loop Control Design
-
- 6. More Complex Converters**
- Three-phase four-wire (four-phase) converter
 - Multilevel converters
 - Parallel converters

DB-188

Limitations of Three-Leg Converters

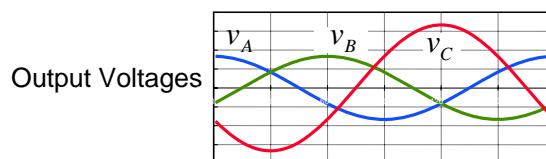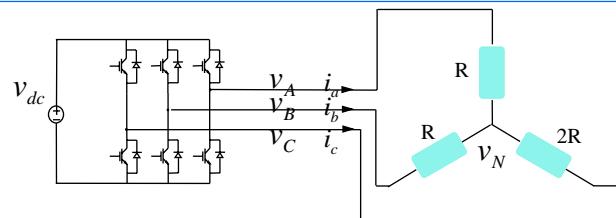


- There is no path for the neutral current.
- Output voltages are unbalanced.

Conventional inverter is not good for highly unbalanced load.

DB-189

Applications

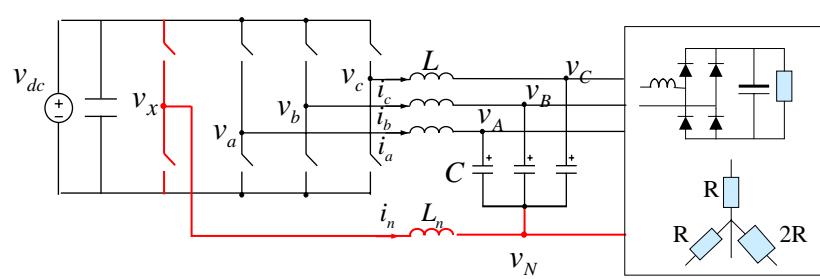- Provide three-phase four-wire
- Deal with unbalanced and nonlinear load




Load

Advantages

- The fourth leg provides a neutral current path
- Compared to generating v_n with capacitive divider:
 - Much smaller dc-link capacitance is needed
 - Full utilization of dc-link voltage (15% higher) with SVM

DB-190

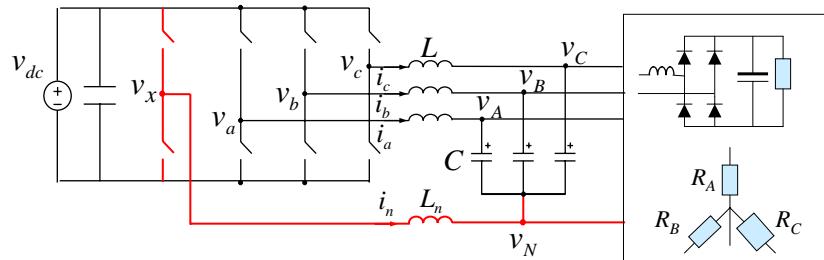
Three-Dimensional Space Vector for Four-Leg Converter



a-b-c coordinates $\Rightarrow \alpha-\beta-\gamma$ coordinates

$$V_\gamma = V_{an} + V_{bn} + V_{cn} \neq 0$$

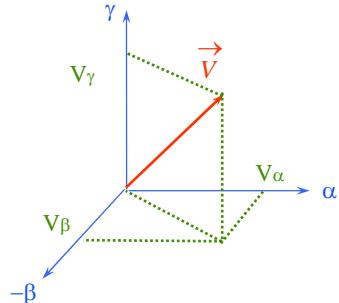
- V_γ is the zero-sequence component
- V_γ is related to the neutral current




DB-191

A Nonlinear Load

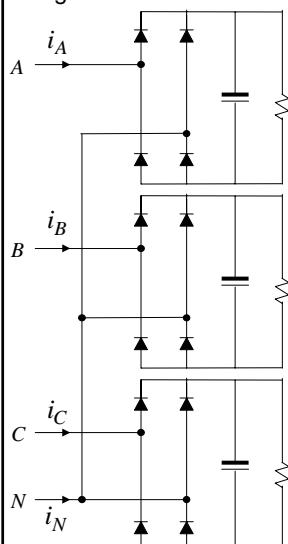Three Single-Phase Diode Bridge Rectifiers with C Filter




Load current
 $[i_A \ i_B \ i_C]^T$

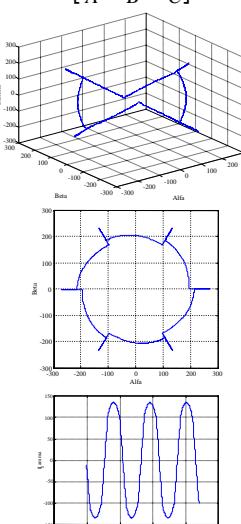


Desired voltage $[v_{ax} \ v_{bx} \ v_{cx}]^T$
 for sinusoidal $[v_{AN} \ v_{BN} \ v_{CN}]^T$

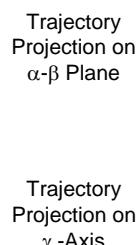Vector Trajectory
 in $\alpha-\beta-\gamma$
 Coordinates





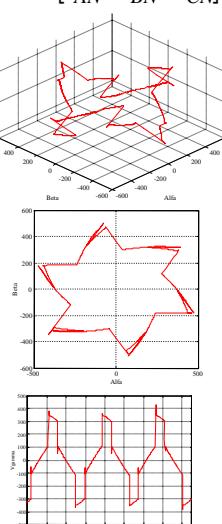Trajectory
 Projection on
 $\alpha-\beta$ Plane




Trajectory
 Projection on
 γ -Axis

92

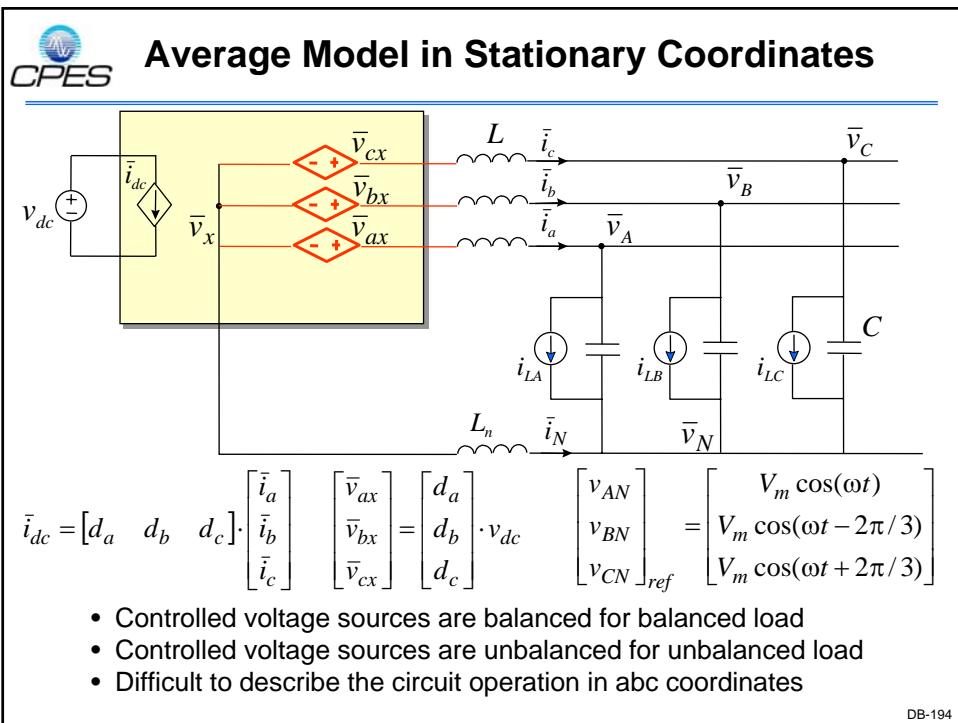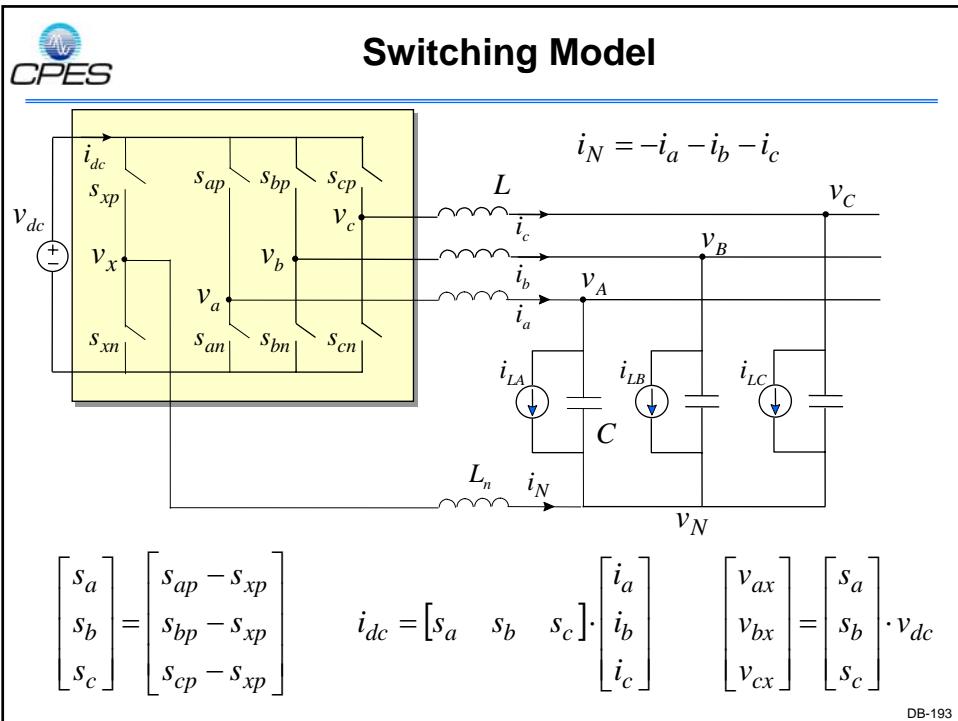


Average Model in Rotating Coordinates

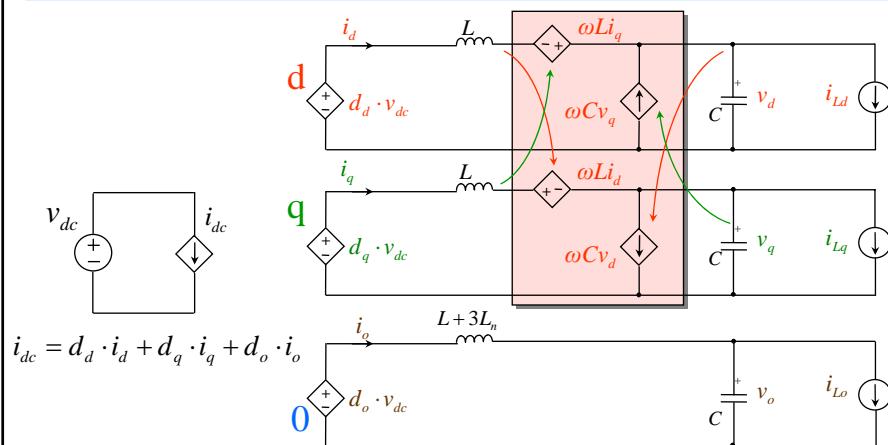

- 2 decoupled subsystems with reduced system orders
- Transfer functions can be derived based on the dc operating point

DB-195


Transfer Functions

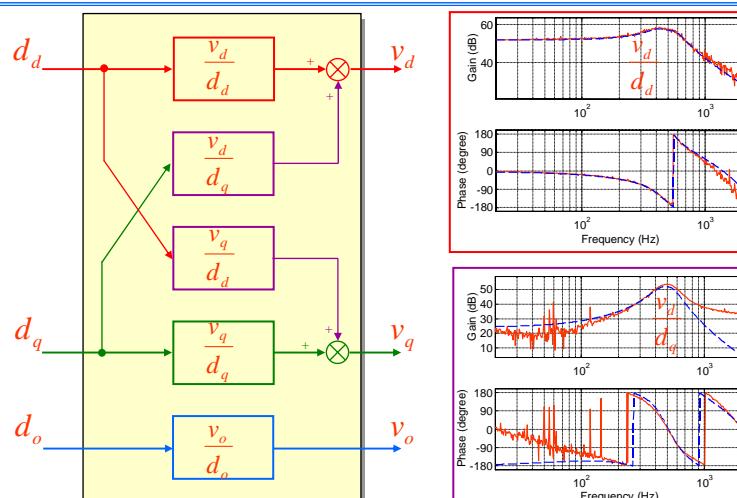

- Sampling delay and PWM delay are incorporated in the model
- The derived model agrees with the measurement very well

DB-196

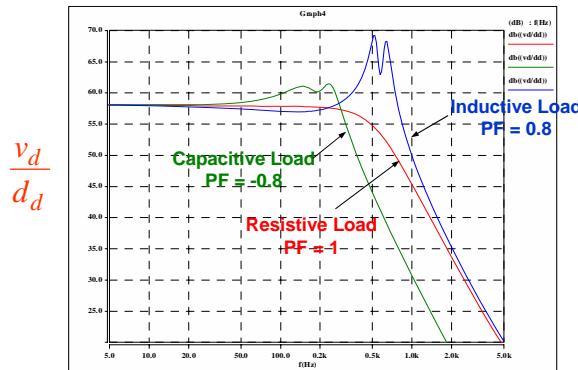Impact of Load Power Factor on Control-to-Output Voltage TFs




Resistive, capacitive (PF=-0.8), and inductive (PF=0.8) are all at 150 kW



- Capacitive load shift the resonant frequency to lower frequency
- Inductive load leads to a higher system order and higher resonant peaking
- Both capacitive and inductive loads are worse loads than resistive load

DB-197


Control Block Diagram

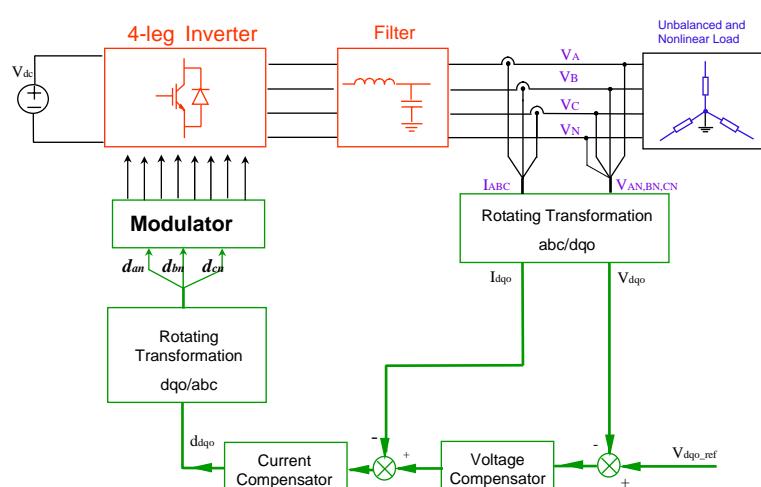


DB-198

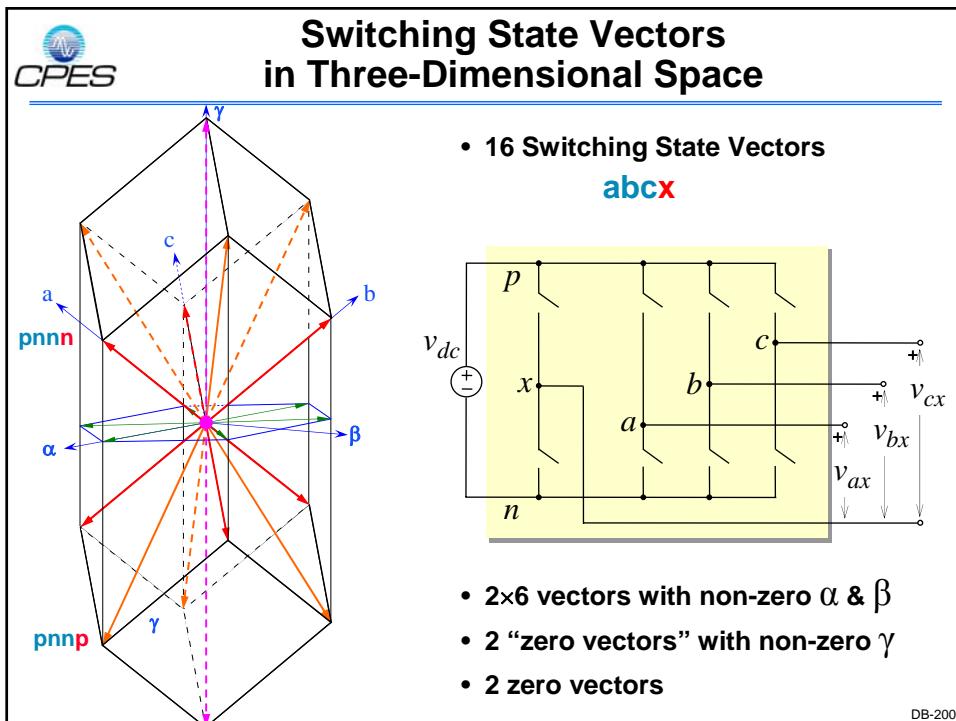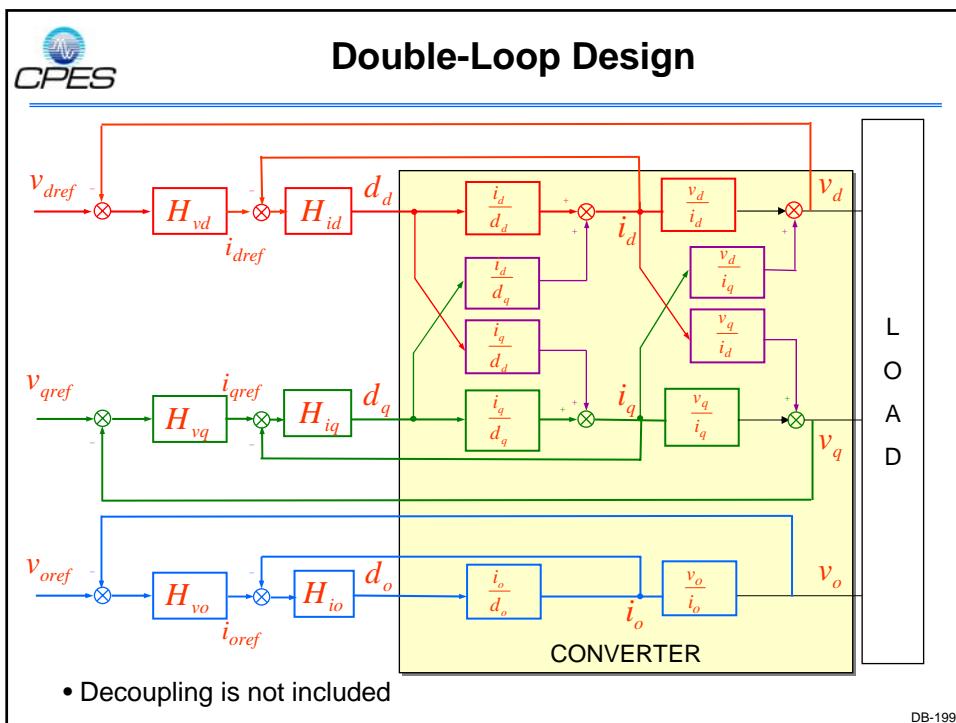





Three-Dimensional Switching Vectors

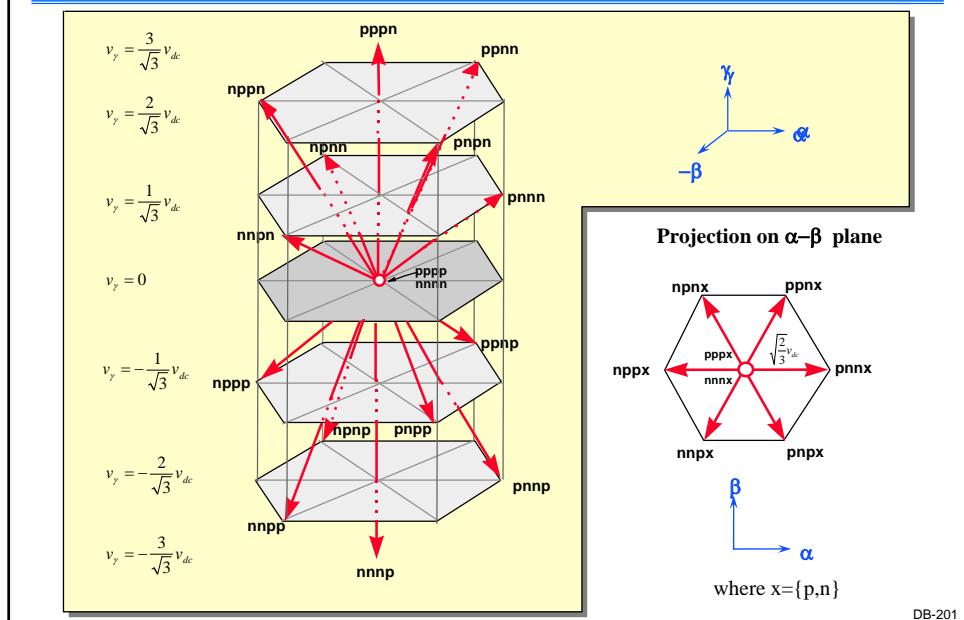

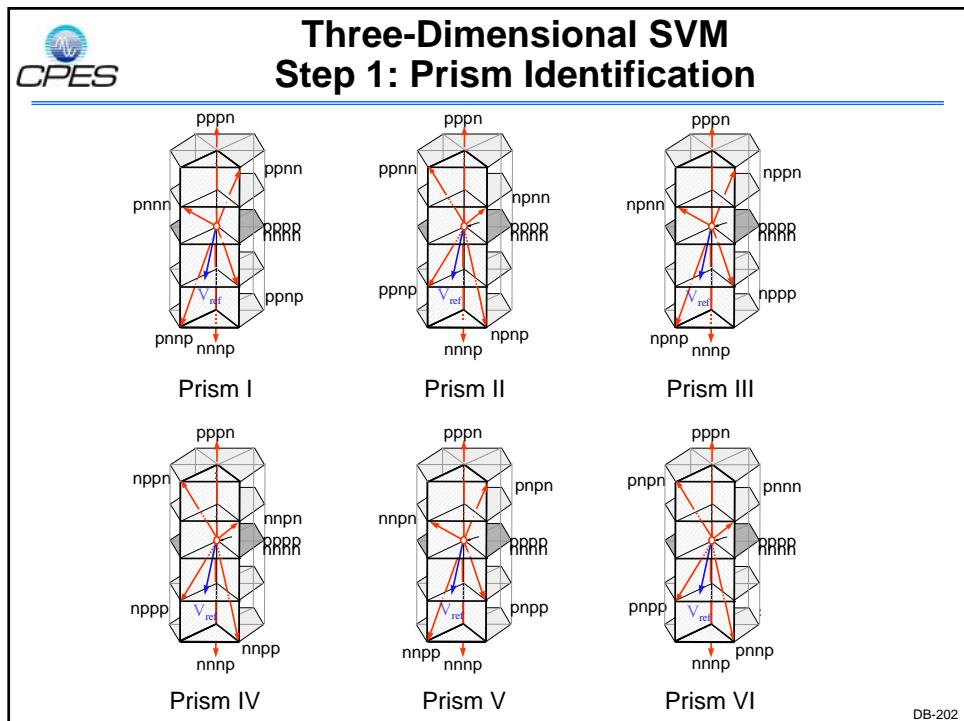Three-Dimensional SVM Step 1: Prism Identification




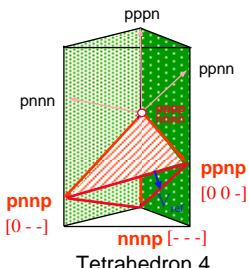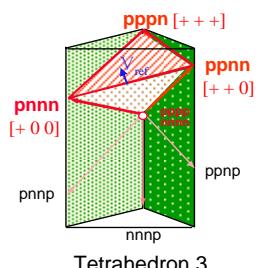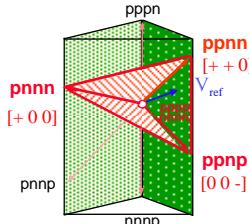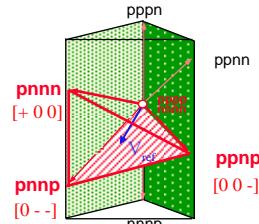Three-Dimensional SVM Step 2: Tetrahedron Identification



DB-203

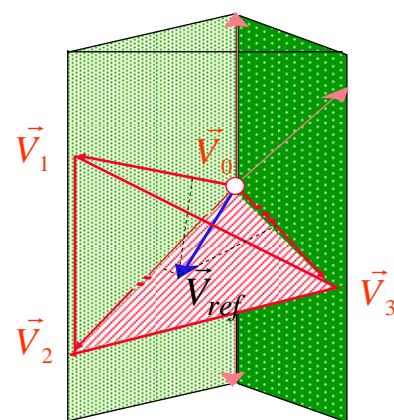Three-Dimensional SVM: Step 3: Duty-Cycle Calculation




$$\vec{V}_{ref} = d_1 \vec{V}_1 + d_2 \vec{V}_2 + d_3 \vec{V}_3$$

$$d_0 = 1 - d_1 - d_2 - d_3$$

DB-204

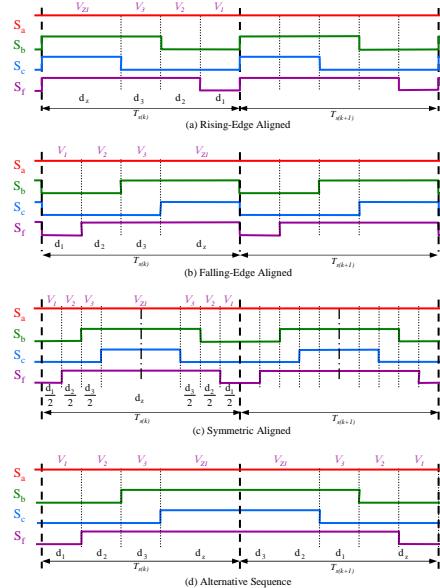**Three-Dimensional SVM:
CPES Step 4: Switching Sequencing (Minimum Loss)**




DB-205


**Experimental Results with Only
Voltage Loops Closed**

Unbalanced Load

Load current and neutral current

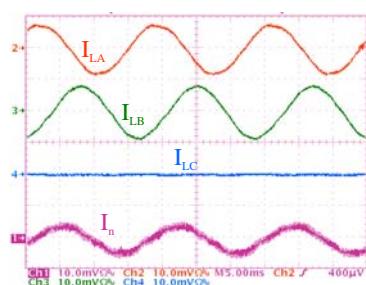

Output voltage and neutral current

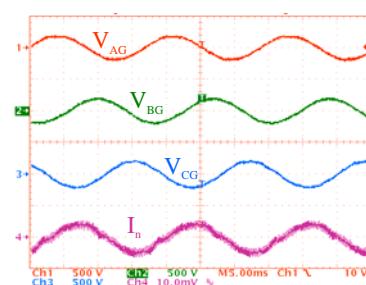

DB-206


A Four-Leg Inverter with Common-Mode Filter Function

- Common-Mode Noise
- A 4-Leg Inverter for Common-Mode Noise Elimination
- A New Modulation and Control Scheme for Inverter Power Supplies with Unbalanced/Nonlinear Load


DB-207

A Four-Leg Inverter with Common-Mode Filter Function

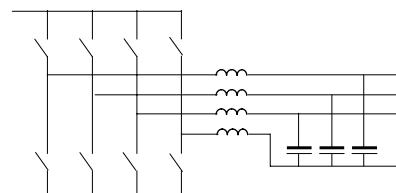4-leg inverter for unbalanced / nonlinear load



4-leg inverter for common-mode reduction

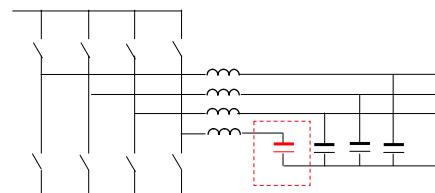


If $v_a + v_b + v_c + v_x \equiv 0$, there is NO common-mode noise!

In order to have both functions, we need

- A new switching modulation strategy
- A new control design because of the series capacitor in neutral leg

DB-208


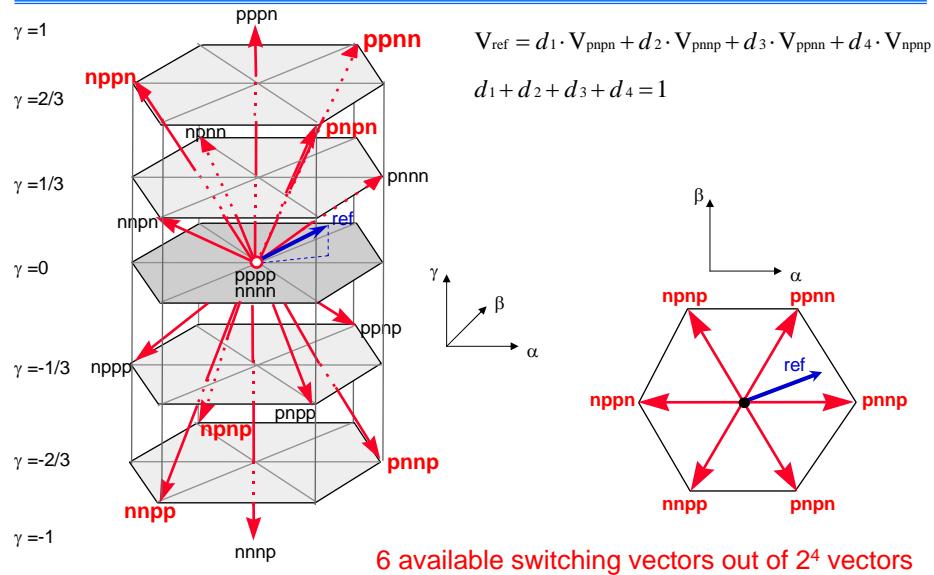
Use Only Switching Vectors with 2 p's and 2 n's





DB-209

Common-Mode Noise Reduction and Trade-Offs

Conventional 4-leg inverter

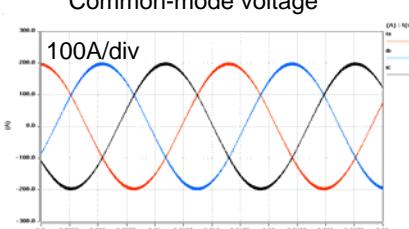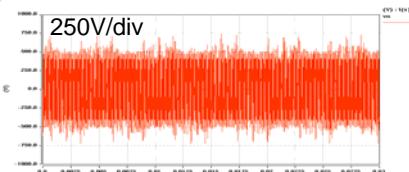

4-leg inverter with CM reduction

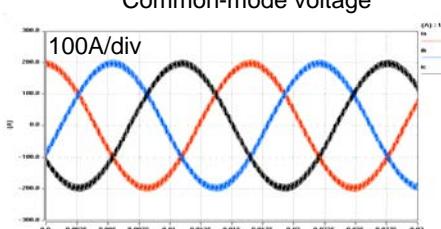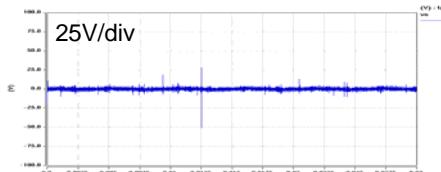

- DM ripple is increased because of reduced vector choice
- 15% smaller maximum modulation index

DB-210

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**


- 6. More Complex Converters**
 - Three-phase four-wire (four-phase) converter
 - Multilevel converters
 - Parallel converters

DB-211

Major Multilevel Three-Phase Topologies


Diode clamped

Nabae, 1980; Choe, 1991; Carpita, 1991

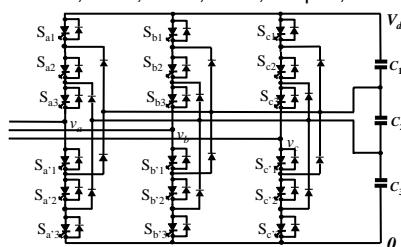


Flying capacitor

Meynard, 1992

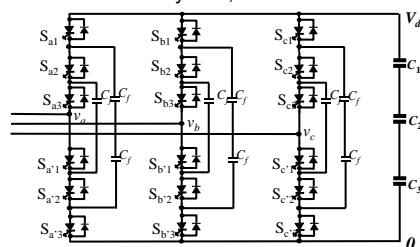

Cascaded H-bridge

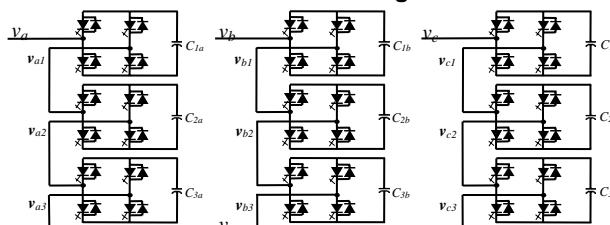


DB-212

Merits of Multilevel Converter Technologies

Advantages

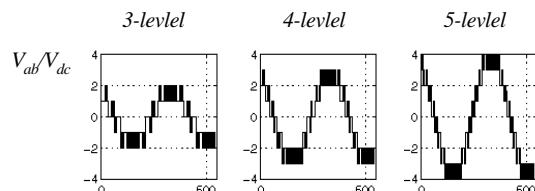- Easy voltage sharing among devices
- Improved spectral performance of output waveforms
- Reduced dv/dt resulting in reduced reflections and damage to insulation
- Reduced switching and conduction losses




Disadvantages

- Increased number of devices
- Increased control complexity
- Depending on topology:
 - Issues with capacitors balancing
 - Issues with bi-directional power flow

DB-213

Multilevel Converter Control

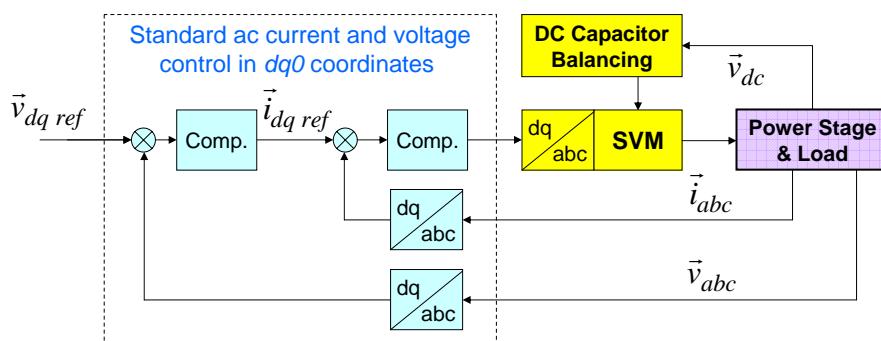


- Average and small-signal models are the same as for two-level VSI or boost rectifier, except for multiple dc voltages
- Closed-loop control of ac quantities in rotating dq coordinates is the same as for two-level VSI or boost rectifier
- **Additional controller for voltage balancing on dc-link capacitors**
- **Modulator is significantly more complex**


DB-214

Space-Vector Representation of Three-Level Converters

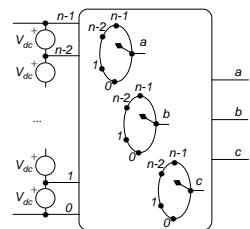- Switching model of n-level converter:
Three single-pole n-throw switches


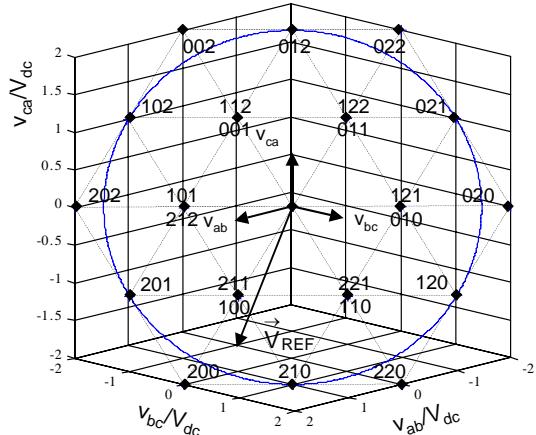
$$\vec{v}_{ijk} = V_{dc} \cdot \begin{bmatrix} i - j \\ j - k \\ k - i \end{bmatrix}$$




- Voltage space-vectors can be represented in a three dimensional line-to-line coordinate system


DB-215

Voltage Space-Vectors of Three-Level Converters

$$KVL : v_{ab} + v_{bc} + v_{ca} = 0$$

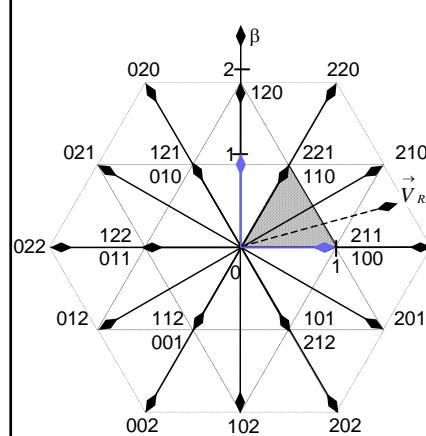

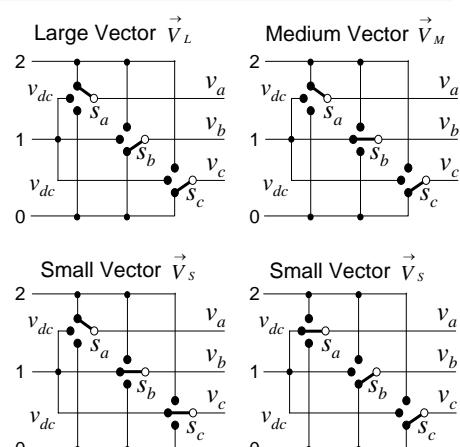- All the voltage space-vectors of a three-phase converter are located on a plane



- Voltage space-vectors have different length: small, medium and large.
- Every small vector has two corresponding switching states—redundancy.


DB-216



SVM for Multilevel Three-Phase Converters?

Five-level converter

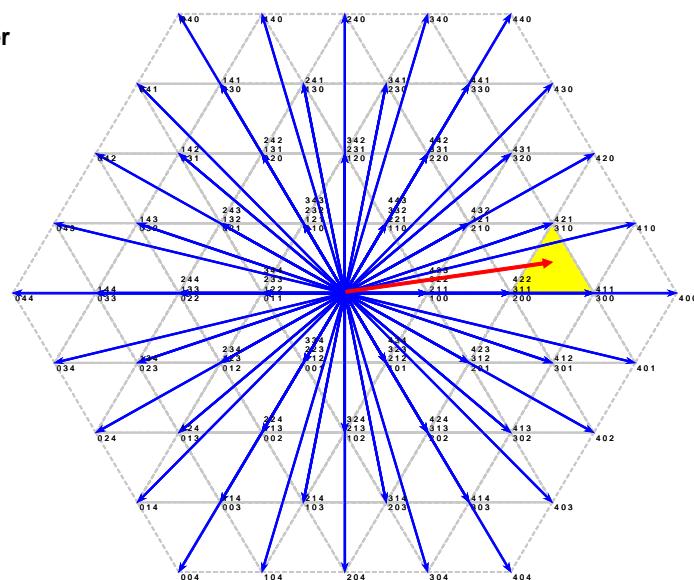- Switching states:
 $n^3 = 125$
- Switching vectors:
 $3n(n-1)+1 = 61$
- Triangular areas:
 $6(n-1)^2 = 96$



How to do SVM?




Complexity?
Speed?

DB-217

Coordinates and Transformation

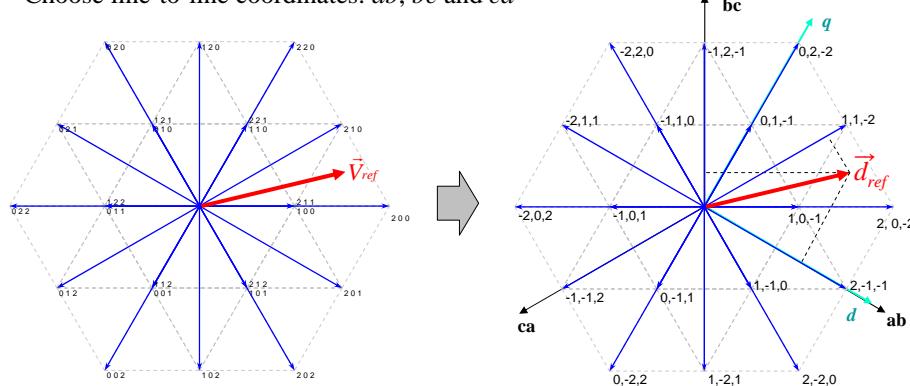- Choose line-to-line coordinates: ab , bc and ca




- Transform \vec{V}_{ref}/V_{dc}
from dq to abc :

$$\vec{d}_{ref} = \begin{bmatrix} d_{ab} \\ d_{bc} \\ d_{ca} \end{bmatrix} = \frac{1}{V_{dc}} \sqrt{\frac{2}{3}} \begin{bmatrix} \cos\theta & -\sin\theta \\ \cos(\theta - \frac{2\pi}{3}) & -\sin(\theta - \frac{2\pi}{3}) \\ \cos(\theta + \frac{2\pi}{3}) & -\sin(\theta + \frac{2\pi}{3}) \end{bmatrix} \begin{bmatrix} v_{d\ ref} \\ v_{q\ ref} \end{bmatrix}$$


DB-218

Identify the Vectors and Calculate their Duty Cycles

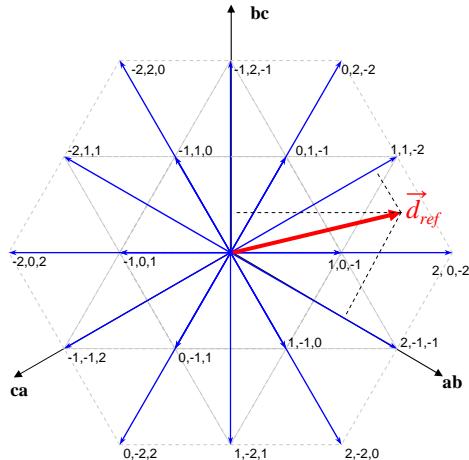
- Calculate the floor and ceiling of the projections:
- $$f_{ab} \leq d_{ab} \leq c_{ab},$$
- $$f_{bc} \leq d_{bc} \leq c_{bc},$$
- $$f_{ca} \leq d_{ca} \leq c_{ca}$$



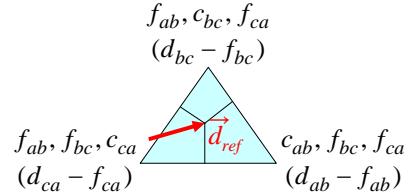- If $f_{ab} + f_{bc} + f_{ca} = -1$ then \vec{d}_{ref} falls in a triangle as follows:



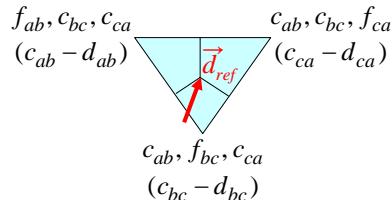
- If $f_{ab} + f_{bc} + f_{ca} = -2$ then \vec{d}_{ref} falls in a triangle as follows:



DB-219

An Example

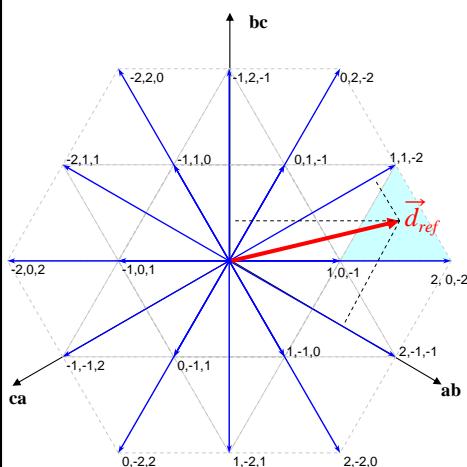\vec{d}_{ref} with a length of 1.7 and an angle of 45° from ab axis



- The projections are

$$d_{ab} = 1.202 \quad d_{bc} = 0.440 \quad d_{ca} = -1.642$$

- The floors and ceilings are


$f_{ab} = 1$	$f_{bc} = 0$	$f_{ca} = -2$
$c_{ab} = 2$	$c_{bc} = 1$	$c_{ca} = -1$

- Since $f_{ab} + f_{bc} + f_{ca} = -1$, the nearest three vectors and their duty cycles are:

$2,0,-2$	$d_{2,0,-2} = d_{ab} - f_{ab} = 0.202$
$1,1,-2$	$d_{1,1,-2} = d_{bc} - f_{bc} = 0.440$
$1,0,-1$	$d_{1,0,-1} = d_{ca} - f_{ca} = 0.358$

DB-220

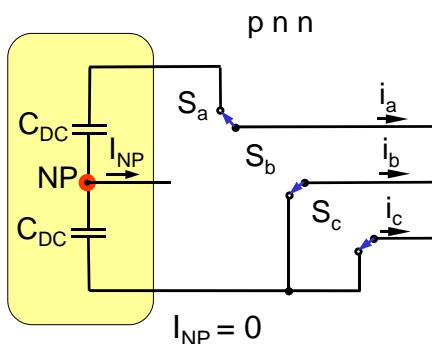Capacitor Balancing Problem in Three-Level Neutral-Point (NP) Clamped Converter




$$V_{ab} = V_{dc}$$

$$V_{bc} = 0$$


$$V_{ca} = -V_{dc}$$

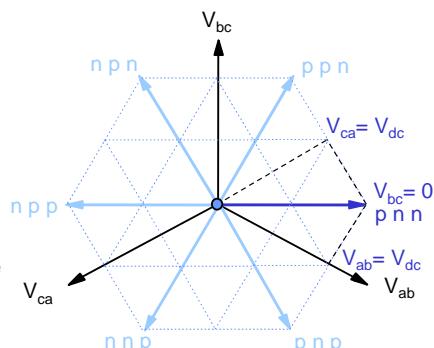Amplitude = $\frac{2}{\sqrt{3}} \cdot V_{dc}$
Phase = 0°



DB-221

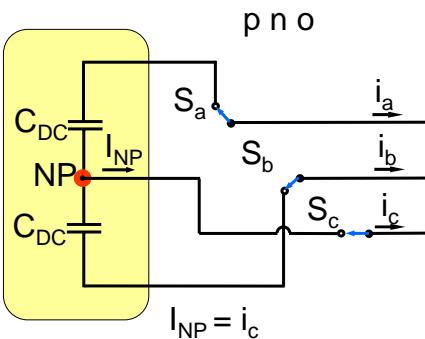Medium vectors affect the charge balance in the neutral point causing the low frequency ripple




$$V_{ab} = V_{dc}$$

$$V_{bc} = -V_{dc}/2$$


$$V_{ca} = -V_{dc}/2$$

Amplitude = V_{dc}
Phase = -30°

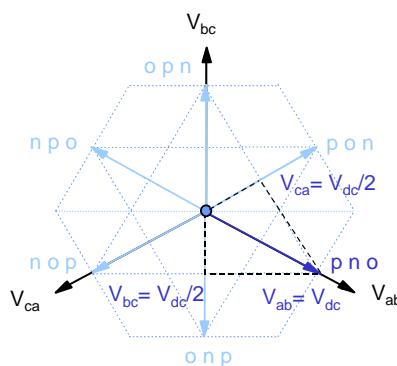

DB-222


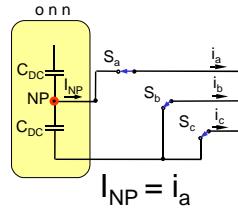
Small vectors also affect the capacitor charge balance and their effect can be controlled



$$V_{ab} = V_{dc}/2 \quad \text{Amplitude} = \frac{1}{\sqrt{3}} \cdot V_{dc}$$

$$V_{bc} = 0 \quad \text{Phase} = 0^\circ$$

$$V_{ca} = -V_{dc}/2$$

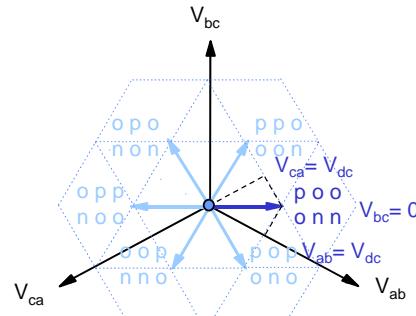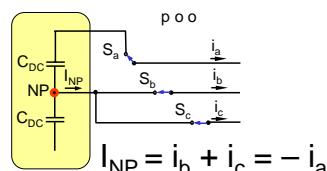

Small vectors come in pairs

Freedom to select either vector in a pair helps balance NP

DB-223

Modified SVM algorithm can effectively compensate the voltage ripple in the neutral point


- Compute the location of voltage space vectors in every switching cycle

$$\vec{V} = \frac{2}{3}(v_{ab} + v_{bc} \cdot e^{j\gamma} + v_{ca} e^{j2\gamma}) \quad \gamma = \frac{2\pi}{3}$$

- Based on the commanded balancing effort, virtual small vector
- can be computed (need to use both vectors every cycle)


$$\vec{V}_{vso} = c \cdot \vec{V}_{s0} + (1-c) \cdot \vec{V}'_{s0} \quad c \in [0, 1]$$

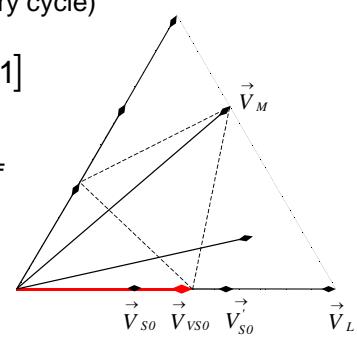- Determine the sector location of the current V_{REF}
- Compute the duty cycles




DB-224

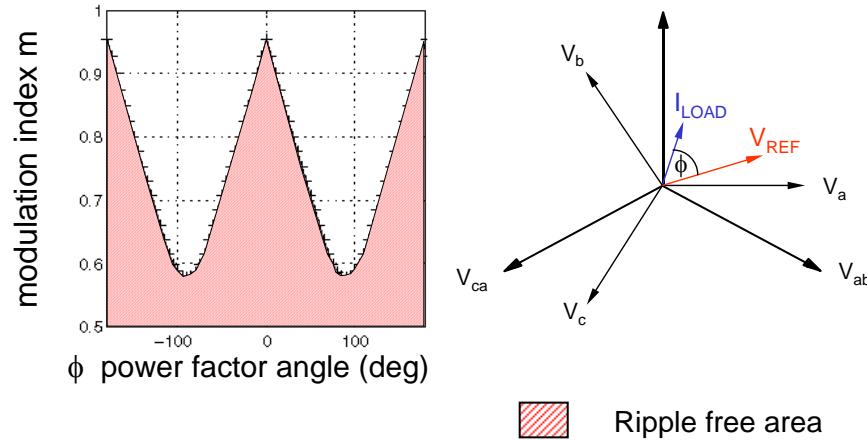Neutral point can be balanced in every switching cycle only in the part of the operating region



DB-225

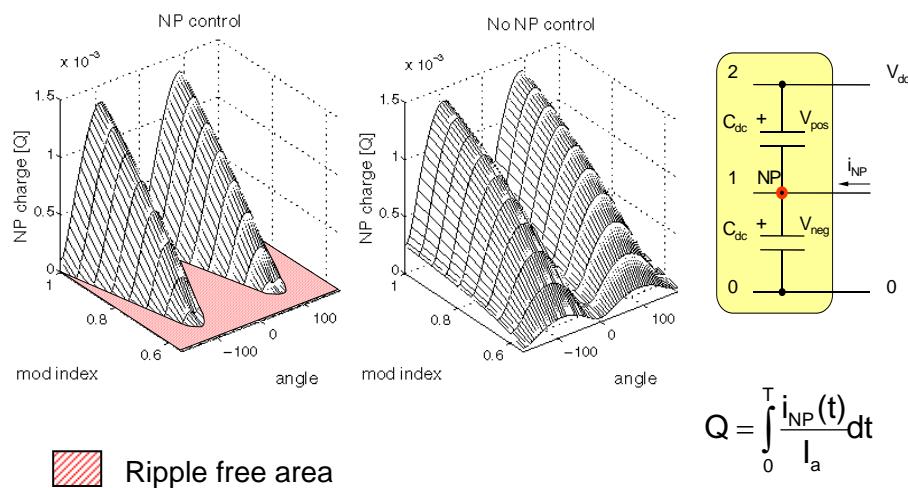Finding the normalized charge ripple for all operating conditions helps design dc-link capacitors




DB-226

As expected, the effect of NP charge control diminishes for the decreasing power factor angle

System Parameters

- 1800 V DC bus
- 1% NP ripple
- 200 A Peak current

With NP control
 Without NP control

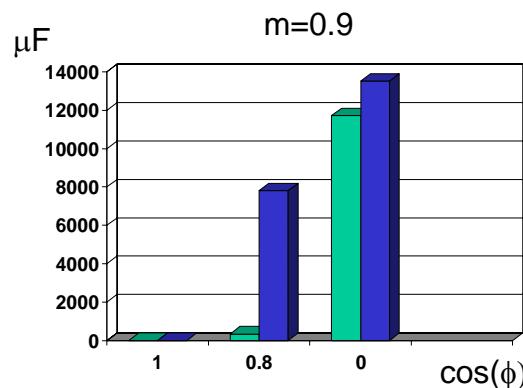



$$2 \cdot C_{DC} = \frac{K \cdot I_{max}}{\Delta U_{DC_max}}$$

K - normalized amplitude of NP charge

DB-227

Balancing of clamping capacitor for flying capacitor converter is load-independent

$$V_{an} = V_{pn}/2$$

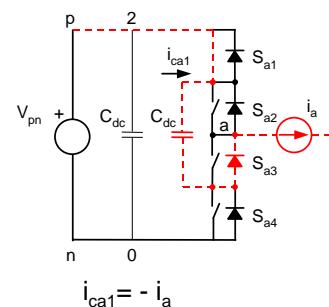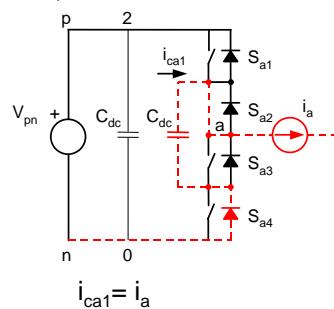


- The inner capacitor handles only switching frequency ripple current
- There is no clamping diode reverse recovery problem
- The modulation and higher level control remains the same
- Flying capacitor converters with any number of levels can be balanced.
- Diode-clamped converters with number of levels above three CANNOT!

DB-228

- 1. Introduction**
- 2. Switching Modeling and PWM**
- 3. Average Modeling**
- 4. Small-Signal Modeling**
- 5. Closed-Loop Control Design**

- 6. More Complex Converters**
 - Three-phase four-wire (four-phase) converter
 - Multilevel converters
 - Parallel converters


DB-229

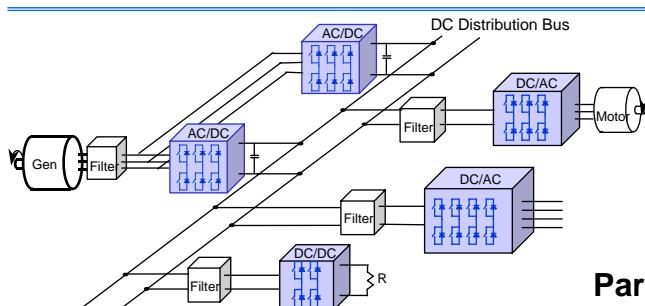
Parallelability

- Modular design
- N+1 redundancy (reliability)
- No limit for current level
- Maintainability
- Availability
- Reduced cost, size and weight
- Improved performance

DB-230

Possible Solutions

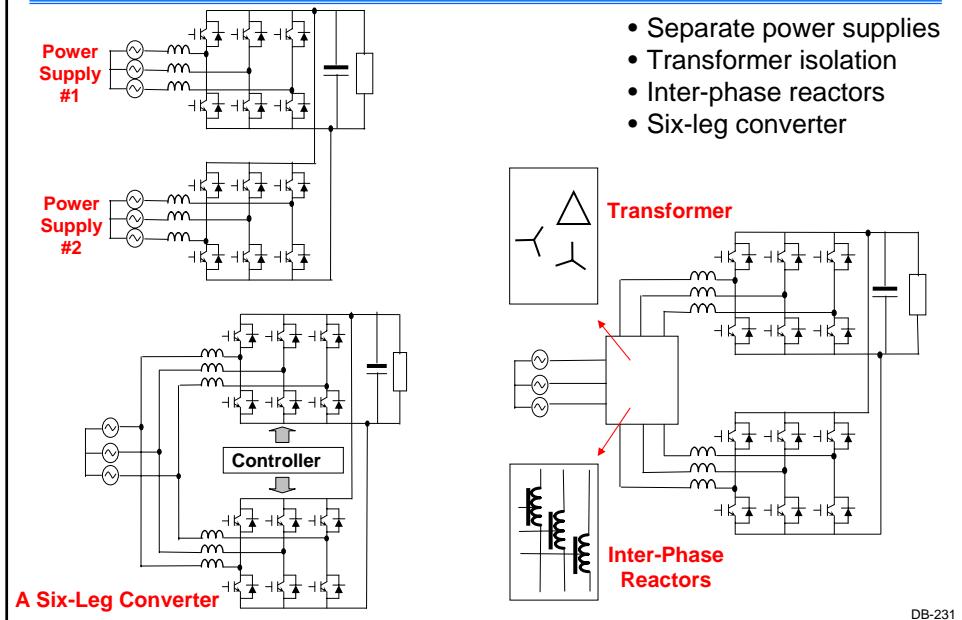

DB-231

Issues – Modeling

Challenges


- High-order system
- Coupling

Existing results

- High-order multi-input-multi-output modeling¹
- Reduced order modeling²

¹Matakas, 1993

²Mao, 1994

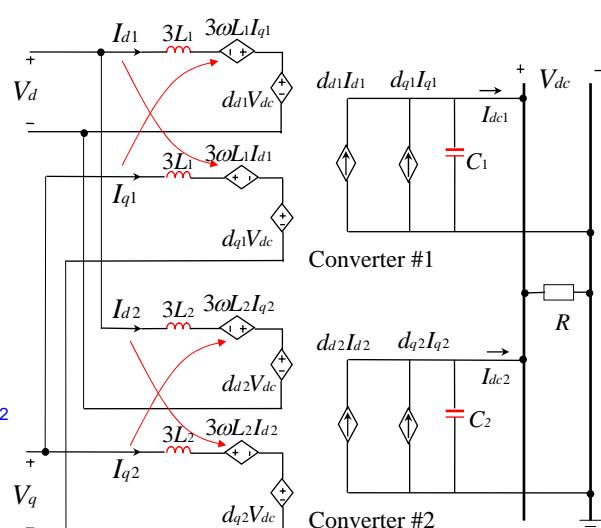


DB-232

Issues – Load Sharing

Challenge

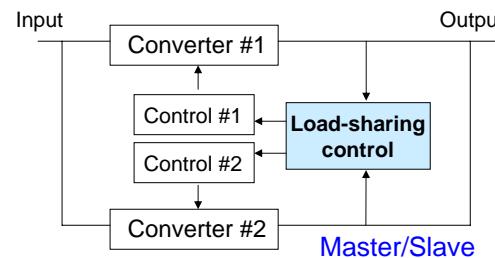- Load sharing
- Voltage regulation
- Modular design





Existing results

- Master/Slave¹
- Droop²


¹Siri, 1992

²Jamerson, 1994

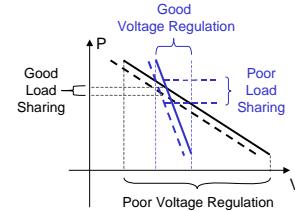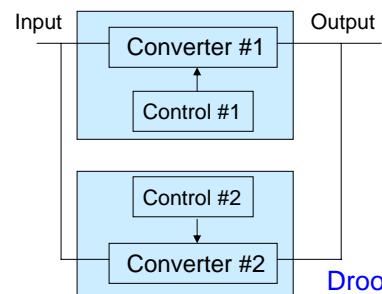




DB-233

Issues – Zero-Sequence Current

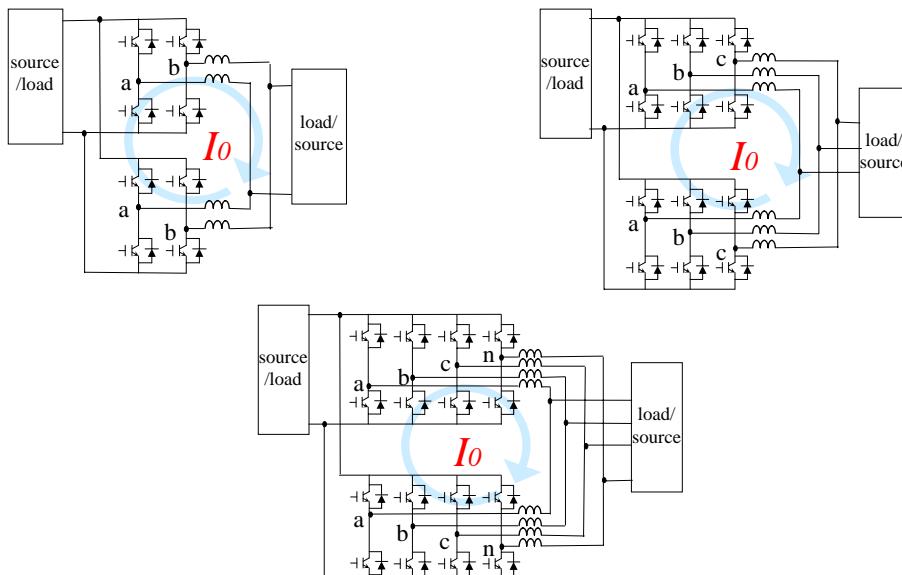


DB-234

Phase-Leg Averaging

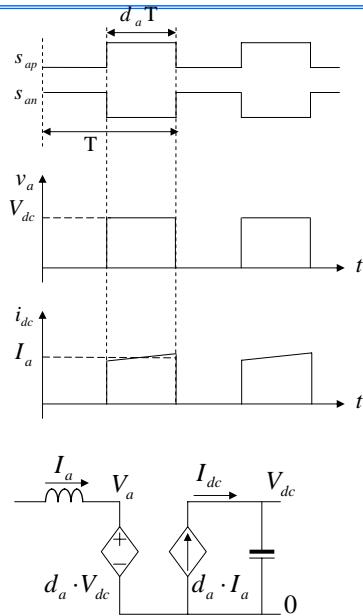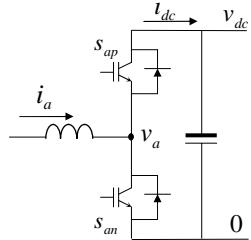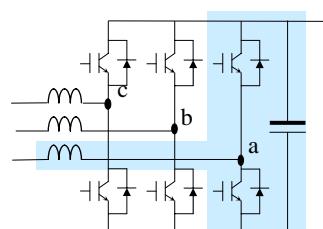


An Averaged Three-Phase Converter Model

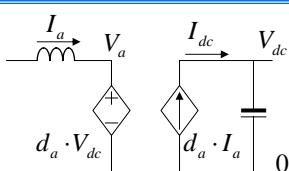

phase-leg model

converter model

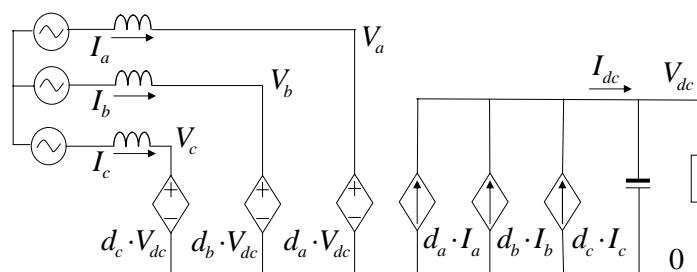

DB-236

Extraction of Zero-Sequence Components

A zero-sequence component \equiv the sum of all phases components

$$\text{e.g. } I_0 = I_a + I_b + I_c$$

$$\text{Define: } d_z = d_a + d_b + d_c$$

$$\Rightarrow (d_a - \frac{d_z}{3}) + (d_b - \frac{d_z}{3}) + (d_c - \frac{d_z}{3}) = 0$$


$$\Rightarrow d_a' + d_b' + d_c' = 0$$

$$\text{Where: } d_a' = d_a - \frac{d_z}{3} \quad d_b' = d_b - \frac{d_z}{3} \quad d_c' = d_c - \frac{d_z}{3}$$

$$\Rightarrow \boxed{d_a = d_a' + \frac{d_z}{3} \quad d_b = d_b' + \frac{d_z}{3} \quad d_c = d_c' + \frac{d_z}{3}}$$

DB-237


The Model with Zero-Sequence Components

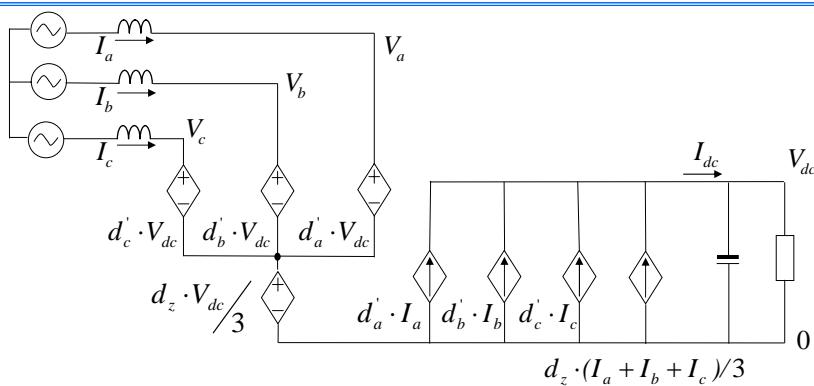

- For a single converter, there is a zero-sequence voltage but no zero-sequence current because $I_a + I_b + I_c \equiv 0$

DB-238

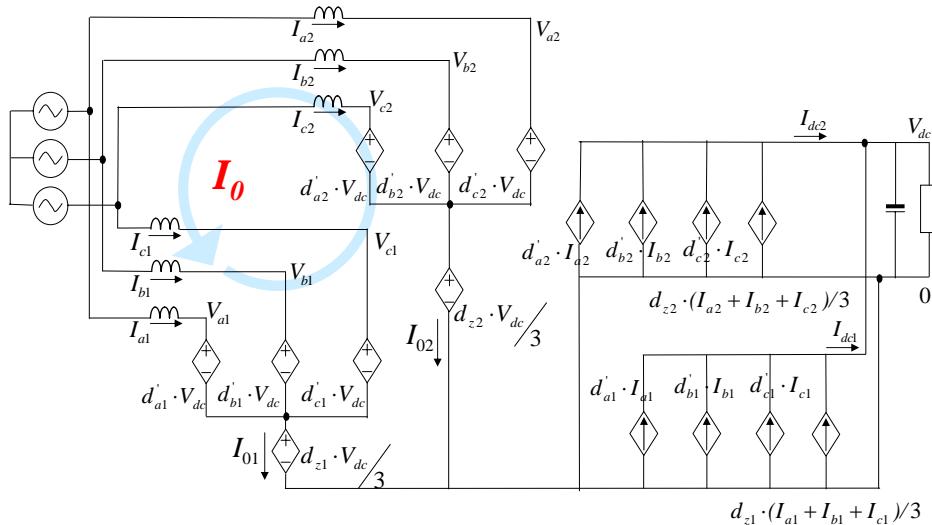Zero-Sequence Current in Parallel Converters



DB-239

An Averaged Model of Zero-Sequence Dynamic

In AC side, there are three-loops forming three equations:


$$d_{z1} \cdot V_{dc}/3 + d_{a1}' \cdot V_{dc} - L_1 \frac{dI_{a1}}{dt} - R_1 \cdot I_{a1} = d_{z2} \cdot V_{dc}/3 + d_{a2}' \cdot V_{dc} - L_2 \frac{dI_{a2}}{dt} - R_2 \cdot I_{a2}$$

$$d_{z1} \cdot V_{dc}/3 + d_{b1}' \cdot V_{dc} - L_1 \frac{dI_{b1}}{dt} - R_1 \cdot I_{b1} = d_{z2} \cdot V_{dc}/3 + d_{b2}' \cdot V_{dc} - L_2 \frac{dI_{b2}}{dt} - R_2 \cdot I_{b2}$$

$$d_{z1} \cdot V_{dc}/3 + d_{c1}' \cdot V_{dc} - L_1 \frac{dI_{c1}}{dt} - R_1 \cdot I_{c1} = d_{z2} \cdot V_{dc}/3 + d_{c2}' \cdot V_{dc} - L_2 \frac{dI_{c2}}{dt} - R_2 \cdot I_{c2}$$

$$\xrightarrow{\text{+}} V_{dc} \cdot (d_{z1} - d_{z2}) = (L_1 + L_2) \frac{dI_0}{dt} + (R_1 + R_2) \cdot I_0$$



Equivalent circuit

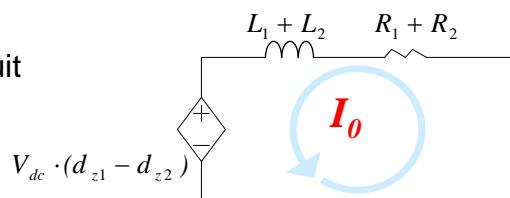

DB-240

Zero-Sequence Duty Cycle

For example:

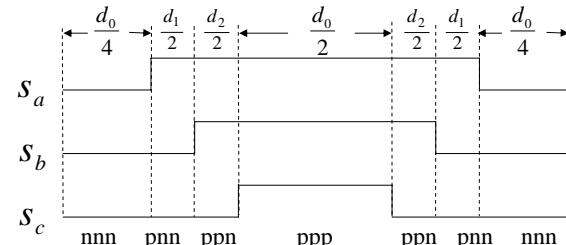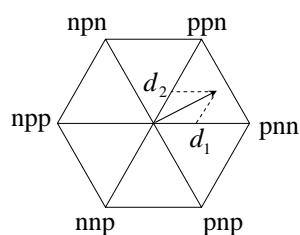


$$\begin{aligned}
 d_z &= d_a + d_b + d_c = (d_1 + d_2 + 0.5d_0) + (d_2 + 0.5d_0) + 0.5d_0 \\
 &= d_1 + 2d_2 + 1.5d_0
 \end{aligned}$$

DB-241

A New Zero-Sequence Control Variable k

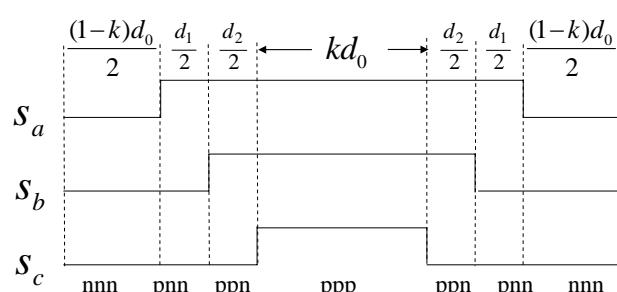$k \equiv d_{ppp}$ i.e. the duration of zero-vector ppp



Therefore:


$$\begin{aligned}
 d_z &= d_a + d_b + d_c = (d_1 + d_2 + kd_0) + (d_2 + kd_0) + kd_0 \\
 &= d_1 + 2d_2 + 3kd_0
 \end{aligned}$$

- k is not definable in minimum loss SVM schemes

DB-242

A New Zero-Sequence Model with the New Control Variable k

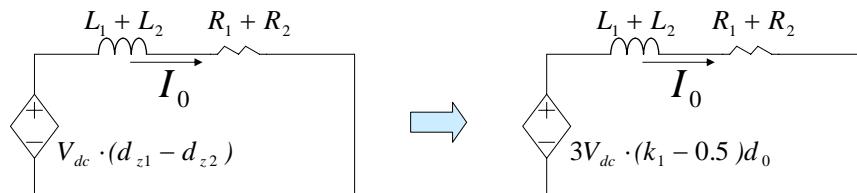
$$d_{z1} - d_{z2} = d_1 + 2d_2 + 3k_1 d_0 - (d_1 + 2d_2 + 3k_2 d_0) \\ = 3(k_1 - 0.5)d_0 \quad \text{where } k_2 \text{ is set to 0.5}$$



- I_0 can be controlled by controlling k_1 dynamically
- High control bandwidth can be achieved because it is a first-order system

DB-243





Implementation

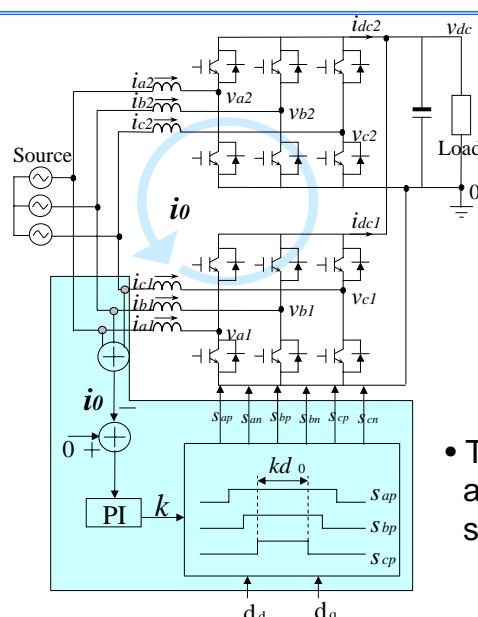

- This part is added onto a regular controller for a single converter.

DB-244


Simulation Results

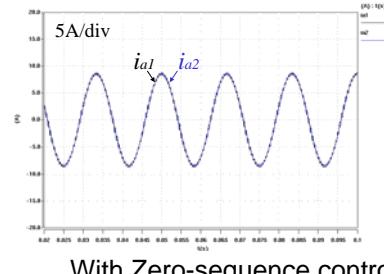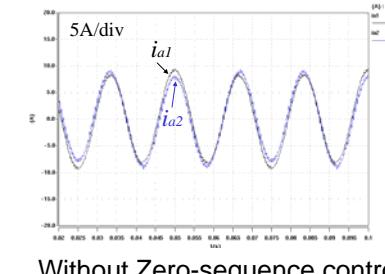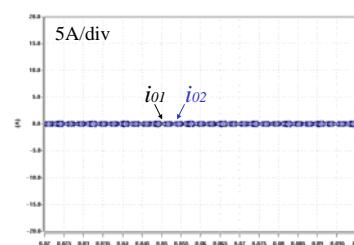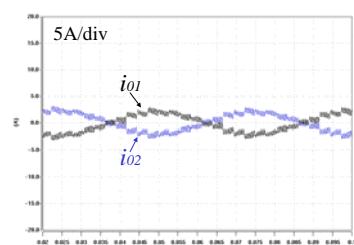

Without Zero-sequence control With Zero-sequence control
 (Two converters with different switching frequencies operate independently)

DB-245

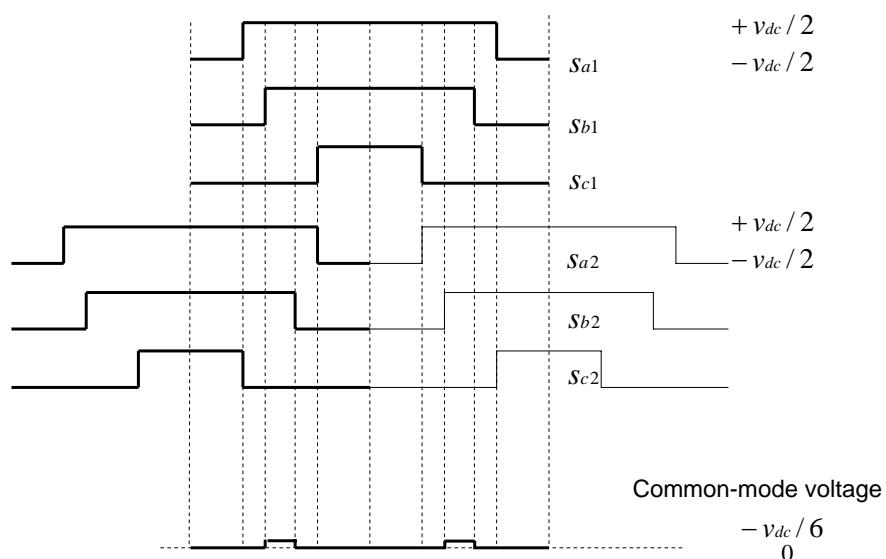
Clock Phase Shifting Common-Mode Voltage Reduction



DB-246



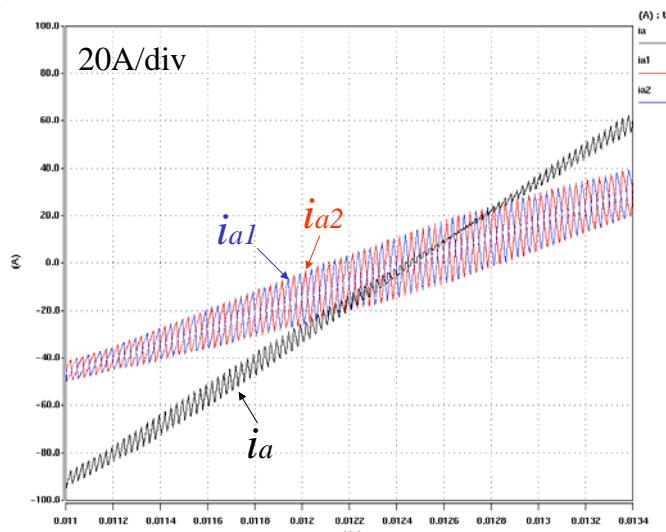Clock Phase Shifting Differential-Mode Ripple Reduction



DB-247



Thank You

**PECon
2008**

The work and contributions are by many CPES faculty, students, and staff.

Many global industrial and US government sponsors of CPES research
are gratefully acknowledged.

This work was supported in part by



ERC Program of the US National Science Foundation under Award Number ECC-9731677

This trip was partially sponsored by



IEEE Power Electronics Society
(PELS)



Joint PELS / IAS / IES Chapter of
IEEE Malaysia Section

DB-248

Some References

1. C. T. Chen, *Linear system theory and design*, 3rd ed., New York, NY: Oxford University Press, 1999.
2. W. J. Rugh, *Linear system theory*, 2nd ed., Englewood Cliffs, NJ.: Prentice Hall, 1996.
3. John S. Bay, *Fundamentals of linear state space systems*, New York, NY: McGraw-Hill, 1999.
Chapter 2, “Vectors and vector spaces”
Chapter 3, “Linear operation on vector spaces”
4. D. G. Holmes and T. A. Lipo, *Pulse Width Modulation for Power Converters: Principles and Practice*, New York, NY: IEEE Press and John Wiley & Sons, 2003.
5. R. Krishnan, *Electric motor drives: modeling, analysis, and control*, Upper Saddle River, NJ: Prentice Hall, 2001.
Chapter 5, “Polyphase induction machines”
Chapter 7, “Frequency controlled induction motor drives”
6. Paul C. Krause, *Analysis of electric machinery*,
Chapter 3, “Reference-frame theory”
7. Vincent Del Toro, *Electric power systems*,
Chapter 8, “Parameters of electric power systems: a description in terms of symmetrical components”
8. Silva Hiti, *Modeling and control of three-phase PWM converters*, Ph.D. Dissertation, Virginia Tech, 1995.
9. P. T. Krein, J. Bentsman, R. M. Bass, and B. Lesieture, “On the use of averaging for the analysis of power electronic systems,” *IEEE Trans. Power Electr.*, vol. 5, no. 5, 1990, pp. 182-190.
10. R. D. Middlebrook, and S. Cuk, “A general unified approach to modeling switching-converter power stages,” *IEEE PESC’76, Rec.*, 1976, pp. 18-34.
11. G. W. Wester, and R. D. Middlebrook, “Low-frequency characterization of switched dc-dc converters,” *IEEE PESC’72, Rec.*, 1972, pp. 9-20.
12. C. T. Rim, D. Y. Hu, and G. H. Cho, “Transformers as equivalent circuits for switches: General proofs and D-Q transformation-based analyses,” *IEEE Trans. Ind. Appl.*, vol. 26, no. 4, 1990, pp. 777-785.
13. J. M. Noworolski, and S. R. Sanders, “Generalized in-place circuit averaging,” *IEEE PESC’91, Rec.*, 1991, pp. 445-450.
14. S. R. Sanders, J. M. Noworolski, X. Z. Liu, and G. C. Verghese, “Generalized averaging method for power conversion circuits,” *IEEE Trans. Power Electr.*, vol. 6, no. 2, 1991, pp. 251-259.
15. K. D. T. Ngo, *Topology and analysis in PWM inversion, rectification, and cycloconversion*, Ph.D. Dissertation, California Institute of Technology, Pasadena, CA, 1984.
16. K. D. T. Ngo, “Low frequency characterization of PWM converters,” *IEEE Trans. Power Electron.*, vol. PE-1, 1986, pp. 223-230.
17. P. Bauer, and J. B. Klaassens, “Dynamic modelling of AC power converters,” *IEEE PCC 1993 Rec.*, pp. 502-507, 1993.
18. S. Hiti, and D. Borojevic, “Small-signal modeling and control of three-phase PWM converters,” *1994 IEEE IAS Annu. Meet. Conf. Rec.*, 1994.
19. R. H. Park, “Two-reaction theory of synchronous machines I and II,” *AIEE Trans.*, vol. 48, and vol. 52, 1929 and 1933.
20. H. Mao, D. Boroyevich, and F. C. Lee, “Novel reduced-order small-signal model of three-phase PWM rectifier,” *PESC’96*.
21. D. M. Brod, and D. W. Novotny, “Current control of VSI-PWM inverters,” *IEEE Trans. Industry Appl.*, vol. IA-21, 1985, pp. 562-570.
22. Wu, S. B Dewan, and G. R. Slemmon, “A PWM Ac-to-DC converter with fixed switching frequency,” *IEEE Trans. Industry Appl.*, vol. 26, 1990, pp. 880-885.

23. T. G. Habetler, "A space vector-based rectifier regulator for AC/DC/AC converters," *IEEE Trans. Power Electron.*, vol. 8, 1993, pp. 30-36.
24. R. Wu, S. B Dewan, and G. R. Slemon, "Analysis of an ac-to-dc voltage source converter using PWM with phase and amplitude control," *IEEE Trans. Industry Appl.*, vol. 27, 1991, pp. 355-363.
25. J. W. Dixon, and B T. Ooi, "Indirect current control of a unity power factor sinusoidal current boost type three-phase rectifier," *IEEE Trans. Industrial Electron.*, vol. 35, 1988, pp. 508-515.
26. Y. Jiang, F. C. Lee, and D. Borojevic, "Simple high performance three-phase boost rectifiers," *IEEE PESC'94, Rec.*, vol. 2, 1994, pp. 1158-1164.
27. H. Sugimoto, S. Morimoto, and M. Yano, "A high-performance control method of a voltage-type PWM converter," *IEEE PESC'88, Rec.*, 1988, pp. 360-368.
28. J. W. Kolar, H. Ertl, K. Edelmoser, F. C. Zach, "Analysis of the control behavior of a bidirectional three-phase PWM rectifier system," *EPE '91*, vol. 2, 1991, pp. 95-100.
29. T. Kawabata, T. Miyashita, and Y. Yamamoto, "Digital control of three-phase PWM inverter with L-C filter," *IEEE PESC'88, Rec.*, 1988, pp. 634-643.
30. S. Hiti, and D. Borojevic, "Control of front-end three-phase boost rectifier," *IEEE APEC'94, Conf. Proc.*, vol. 2, 1994, pp. 927-933.
31. K. Biswas, M. S. Mahesh, B S. R. Iyengar, "A three-phase GTO AC to DC converter with input displacement factor and output voltage control," *1987 IEEE IAS Annu. Meet. Conf. Rec.*, 1987, pp. 685-690.
32. Y. Sato, and T. Kataoka, "State feedback control of current type PWM ac-to-dc converter," *1991 IEEE IAS Annu. Meet. Conf. Rec.*, 1991, pp. 840-846.
33. Busse, and J. Holtz, "Multiloop control of a unity power factor fast switching ac to dc converter," *IEEE PESC'82, Rec.*, 1982, pp. 171-179.
34. S. Hiti, D. Borojevic, F. C. Lee, B. Choi, and S. Lee, "Small-signal modeling of three-phase PWM buck rectifier with input filter," *1991 VPEC Sem. Proc.*, 1991, pp. 229-237.
35. O. Ojo, and I. Bhat, "Analysis of three-phase PWM buck rectifier under modulation magnitude and angle control," *1993 IEEE IAS Annu. Meet. Conf. Rec.*, 1993, pp. 917-925.
36. S. Hiti, V. Vlatkovic, D. Borojevic, F. C Lee, "A new control algorithm for three-phase PWM buck rectifier with input displacement factor compensation," *IEEE Trans. Power Electron.*, vol. 9, 1994, pp.173-180.