

***Fast and Accurate System Level  
Simulation of Time-Based Circuits using  
CppSim and VppSim***

***IEEE Distinguished Lecture  
Lehigh Valley SSSS Chapter***


**Michael H. Perrott**

**October 2013**

**Copyright © 2013 by Michael H. Perrott**

**All rights reserved.**

# Modern Mixed Signal Circuit Design

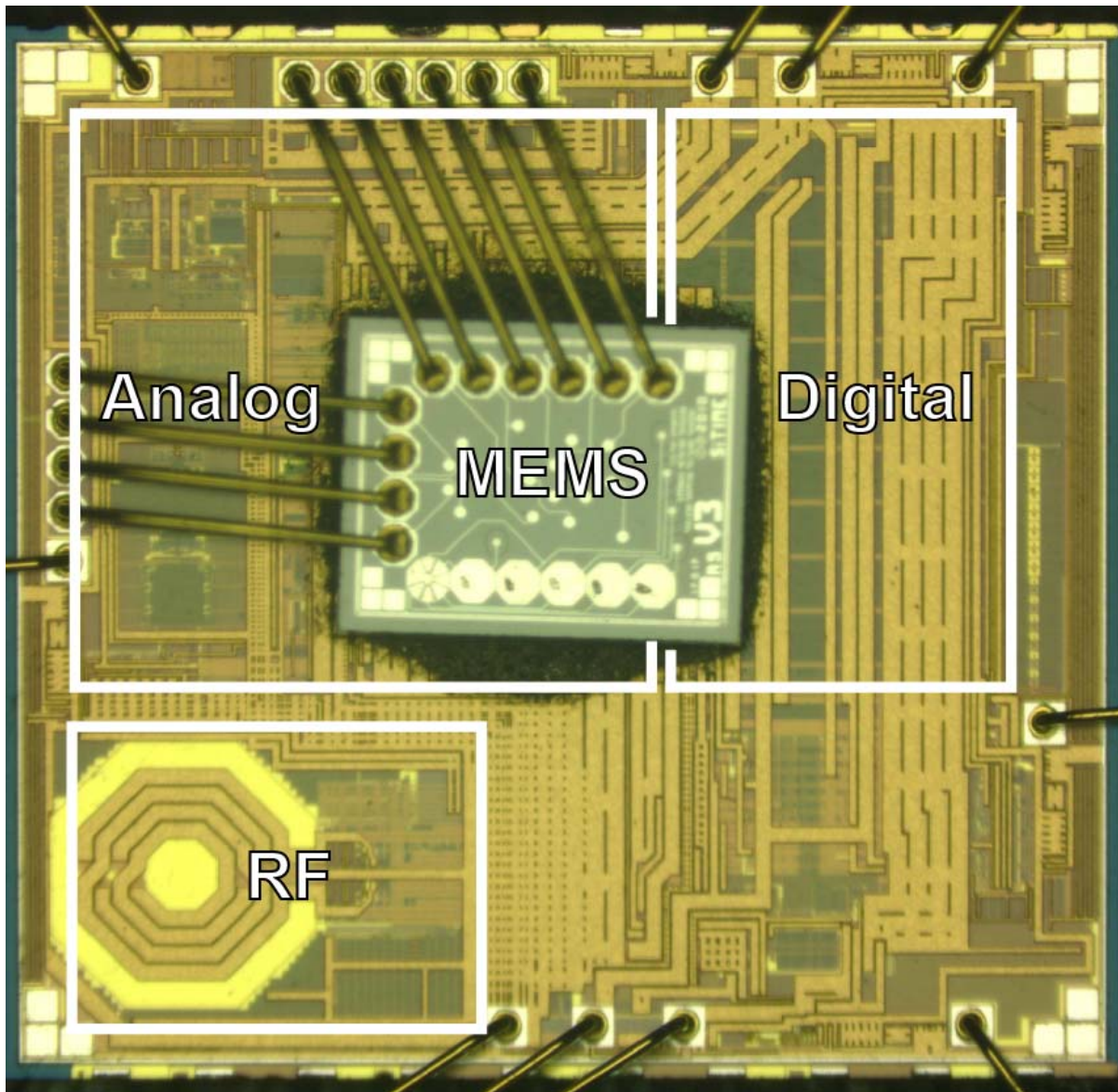


## A Programmable MEMS Oscillator

- *Analog*  
Temperature sensor, ADC, oscillator sustaining circuit
- *Digital*  
signal processing
- *RF*  
clocking (2.5 GHz)
- *MEMS*  
high Q resonator


**System level design is critical**

# System-Level Modeling: A Basic Example

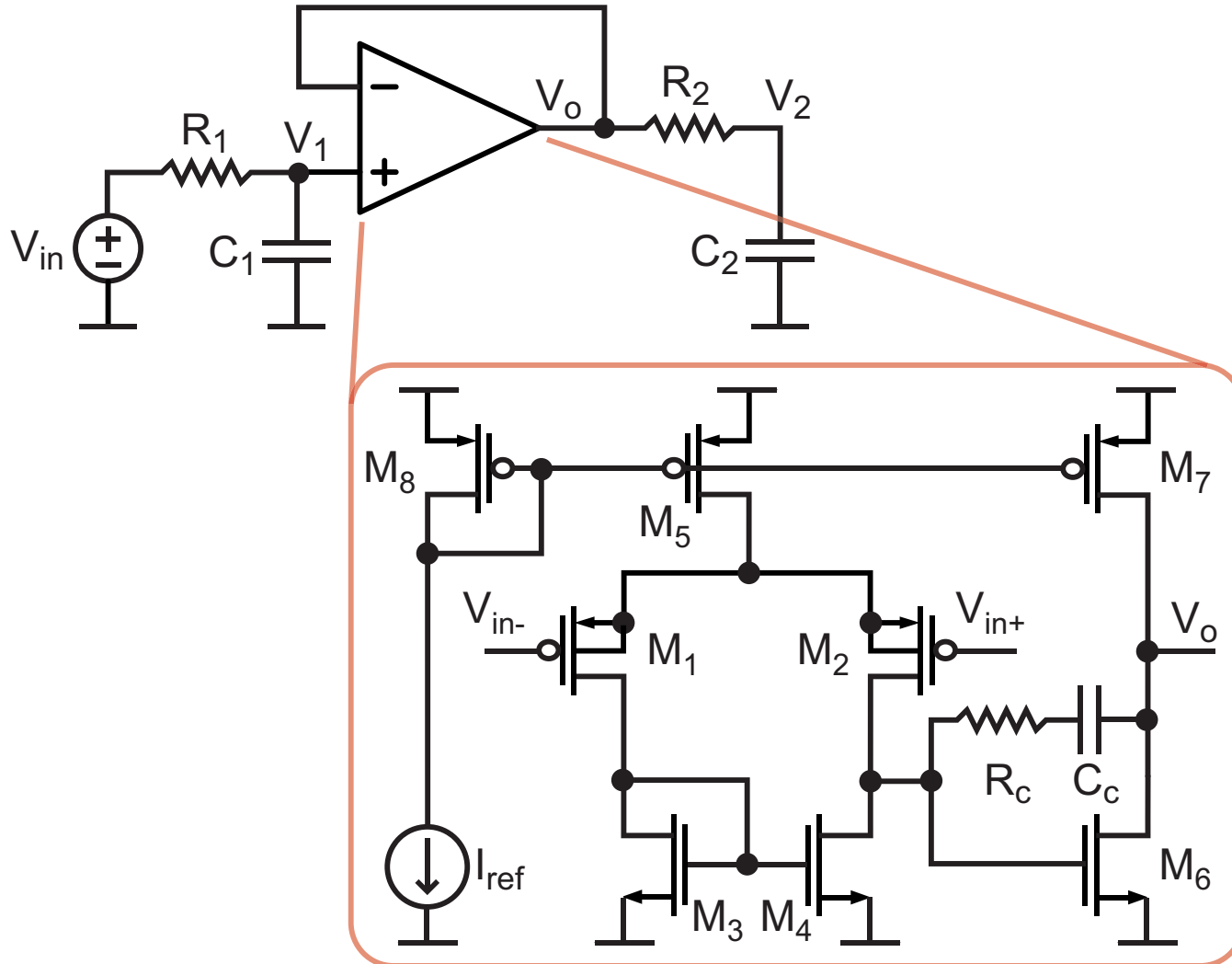


- **Opamp is a nonlinear, transistor-level circuit**
  - **Device level representation mandates SPICE-level simulation**
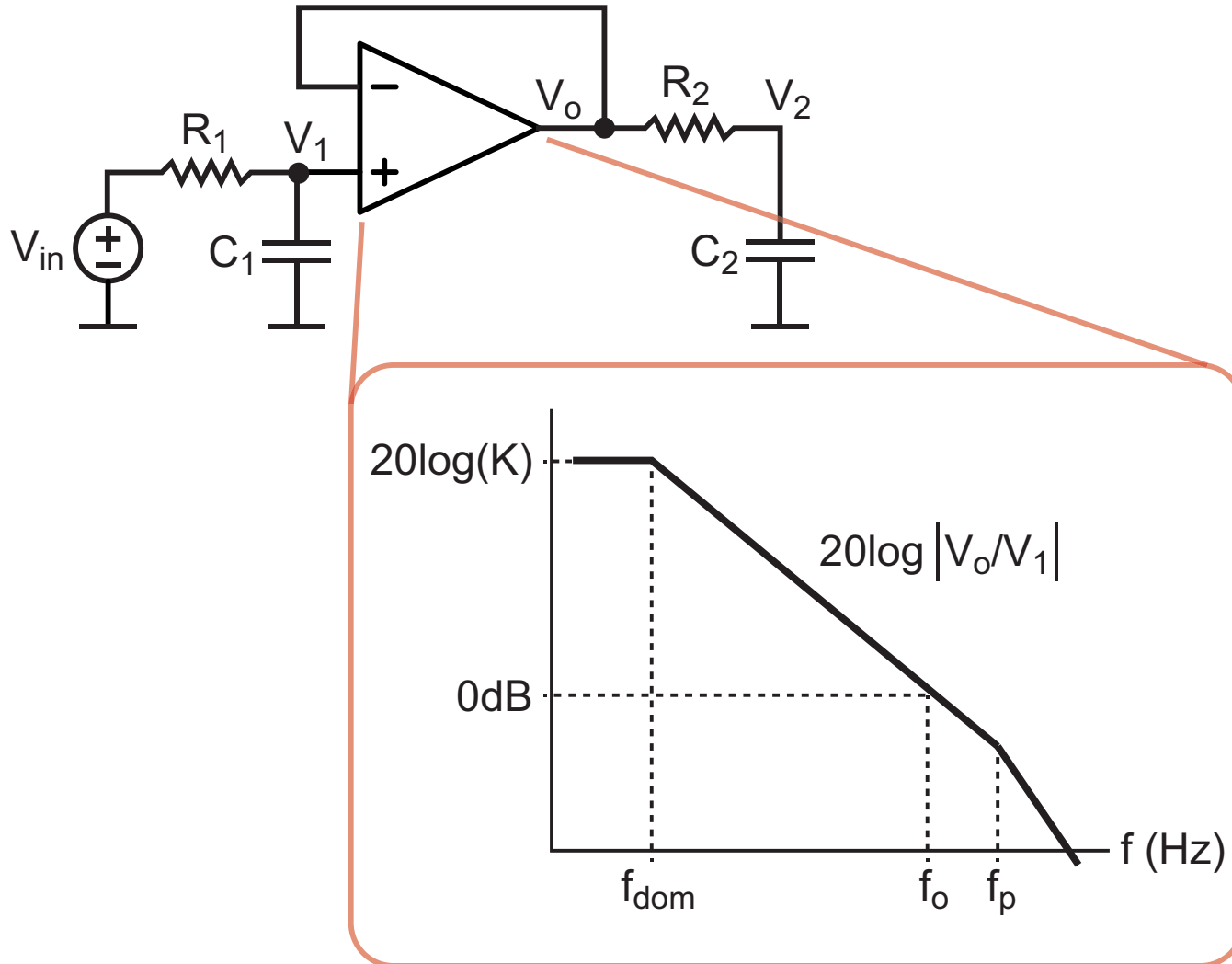
# Opamps Often Modeled at Transfer Function Level




- Works well for small perturbations about steady-state
  - Key parameters are gain and bandwidth

# A Simple Block Diagram Model of Opamp

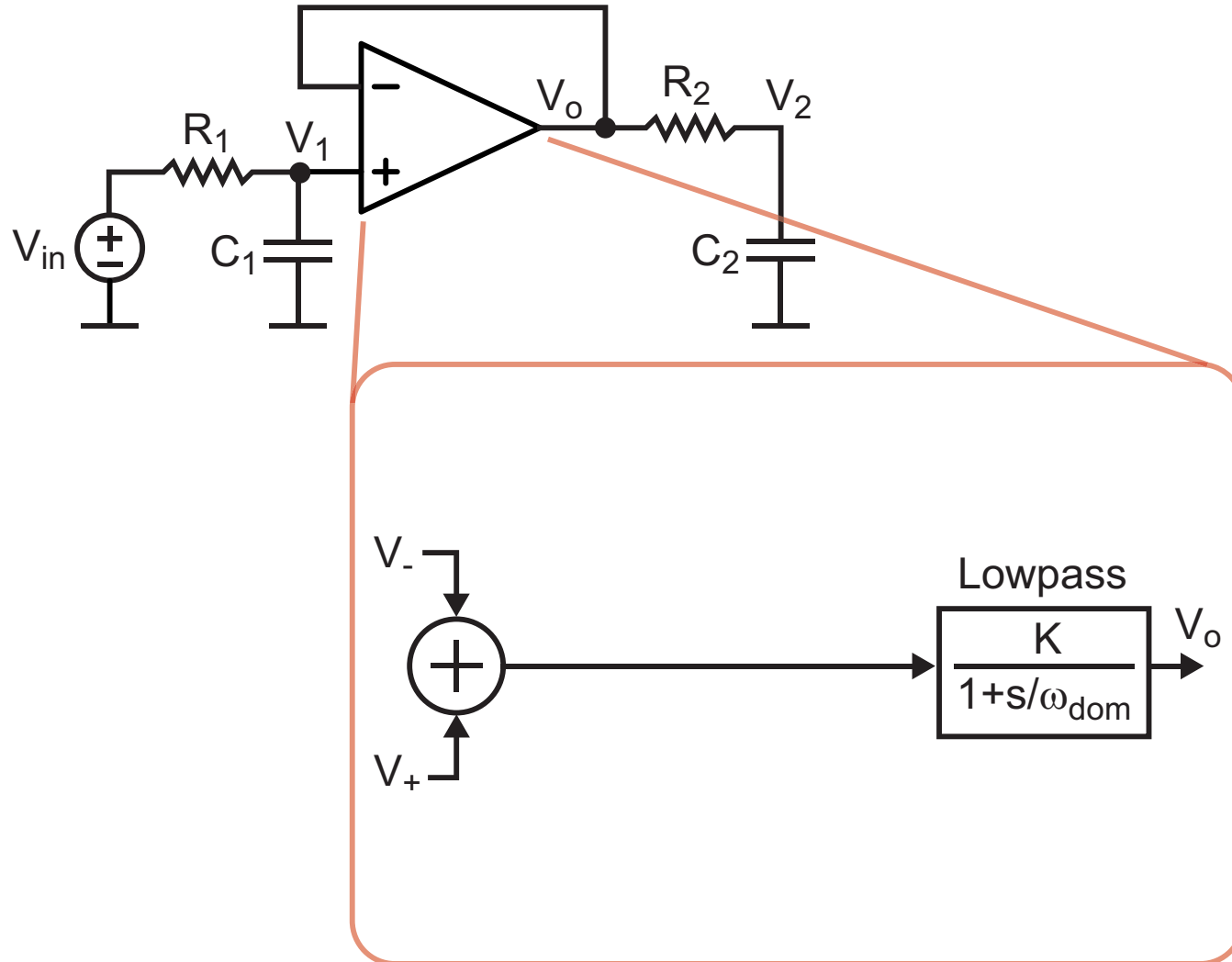


- Approximates first order behavior of opamp

## Inclusion of Second Order Effects

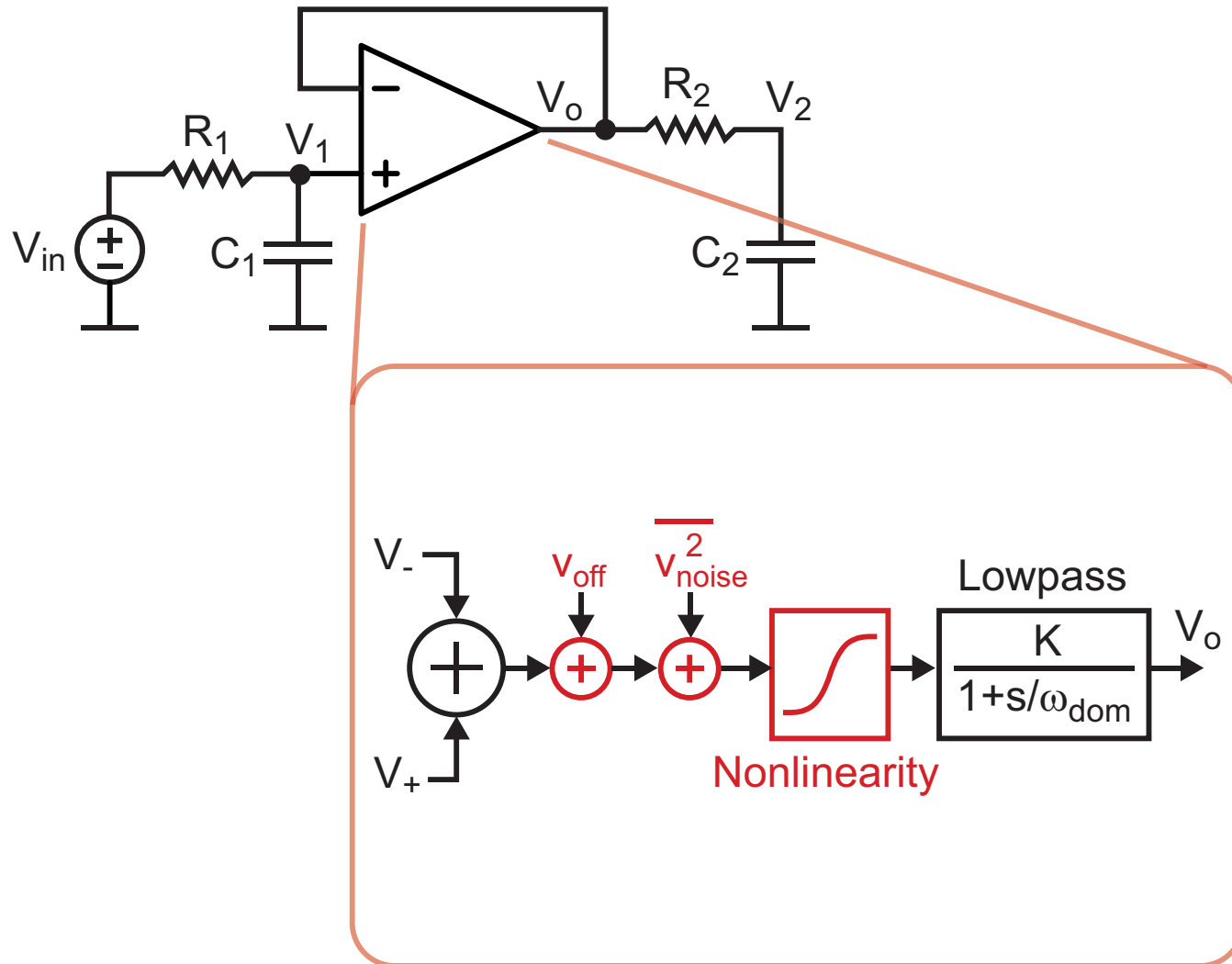

- **Offset, noise, and nonlinearity of front end-differential pair**
  - Parasitic poles are also easy to add as additional blocks


# Overall Block Diagram Model

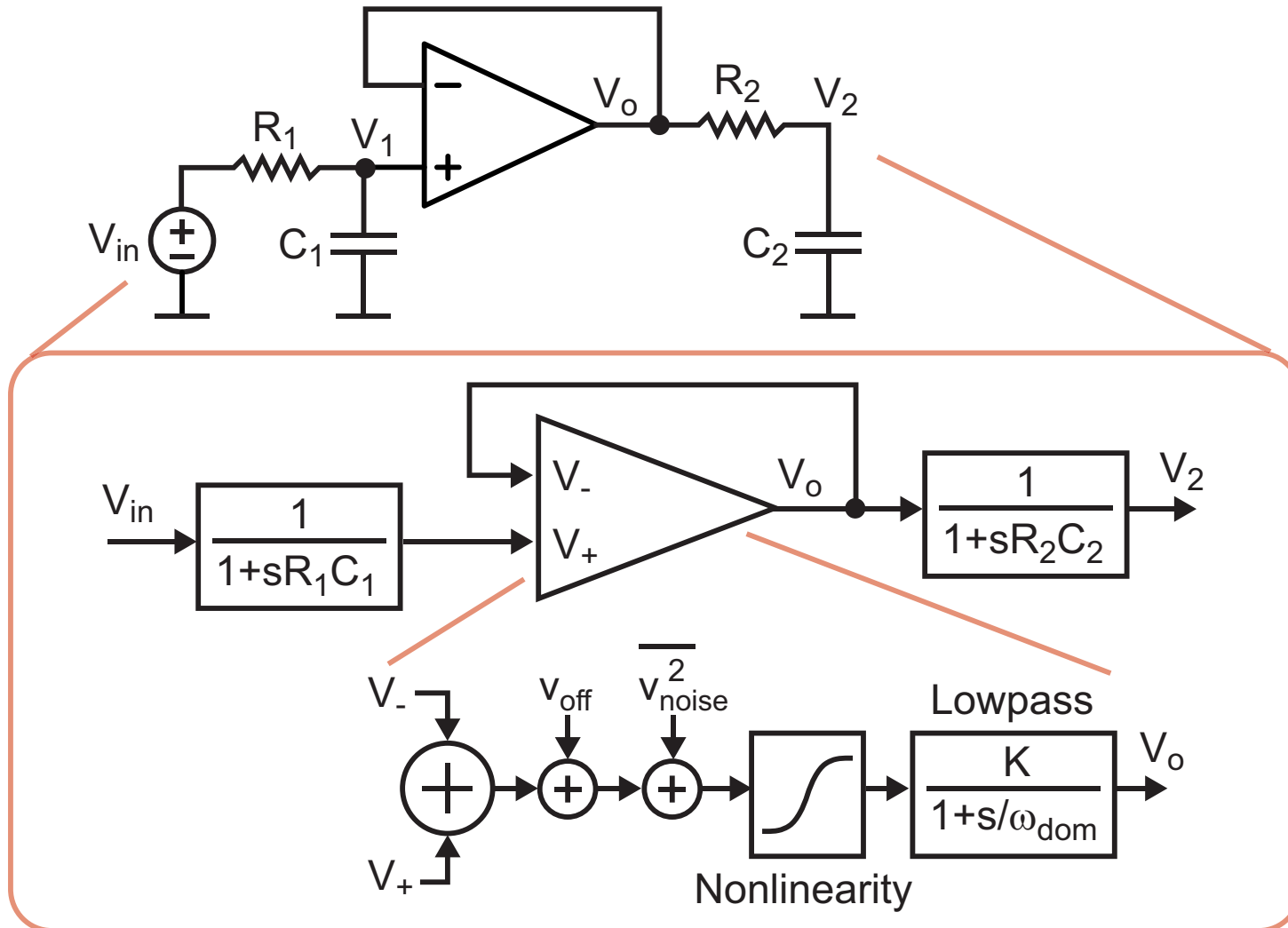

- Unilateral flow through blocks allows fast simulation
  - Compute block outputs one at a time for each time step

# Advantages of Block-by-Block Computation


---

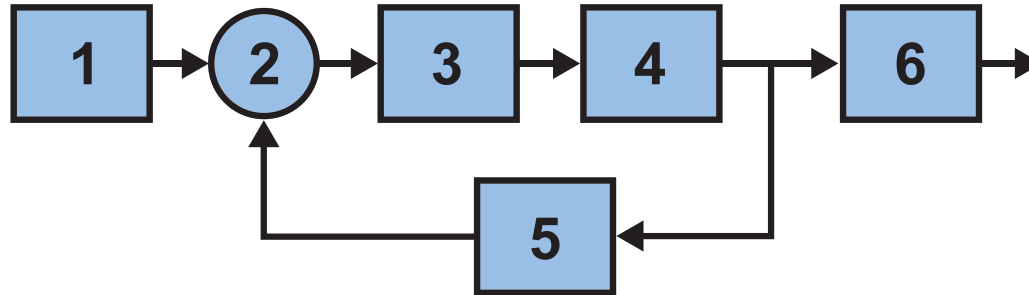

- **Simple, fast computational structure**
  - Simply perform computation for each block one at a time for each time step
    - Extends to hierarchical design quite easily
- **High level of system complexity can be handled**
  - Overall computational load is simply the sum of the computation required for each block
  - Contrast with SPICE whose computational load grows exponentially with the number of elements



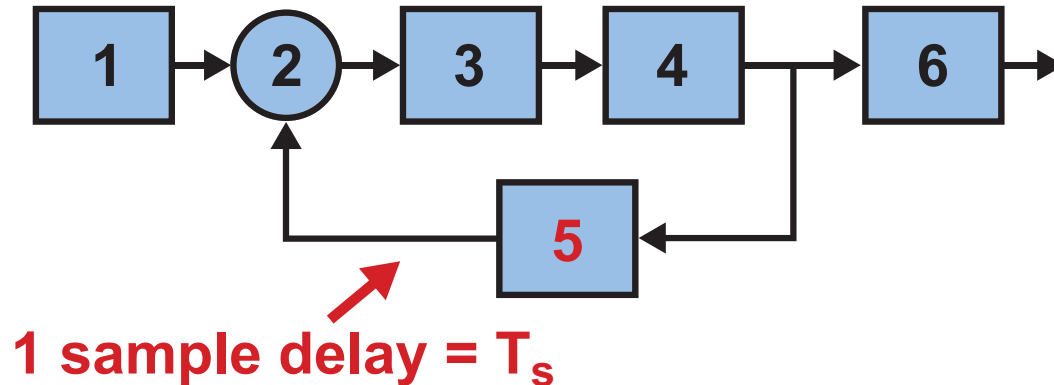
# The Issue of Delay with Block-by-Block Computation



- **Minimum possible delay within a feedback loop is one sample period**
  - Example: Block 2 will not receive updated value from Block 5 until next time sample
  - For unity gain crossover frequency  $f_o$  and delay  $T_s$ :
    - Phase margin reduced by  $f_o \cdot T_s \cdot 360^\circ$

**Time step of simulation must be small compared to bandwidth of feedback loops being simulated**

## The Issue of Block Order

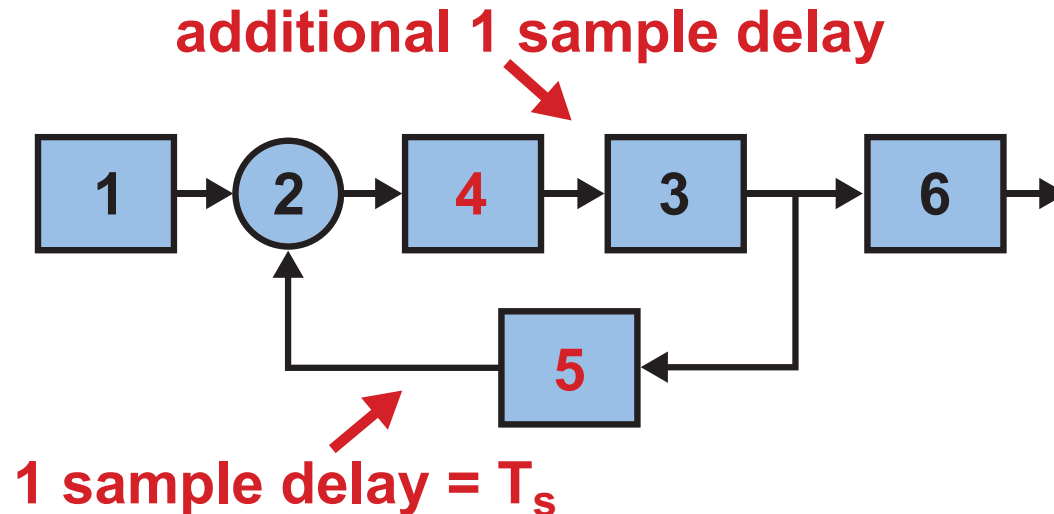


- Poor ordering of blocks leads to additional delay within feedback loops
  - Issue is made worse if blocks computed concurrently
    - Leads to one sample delay *per block*
- Block-by-block computation requires additional algorithm to achieve minimum delay ordering

**CppSim provides automatic minimum delay ordering and allows user specified ordering**

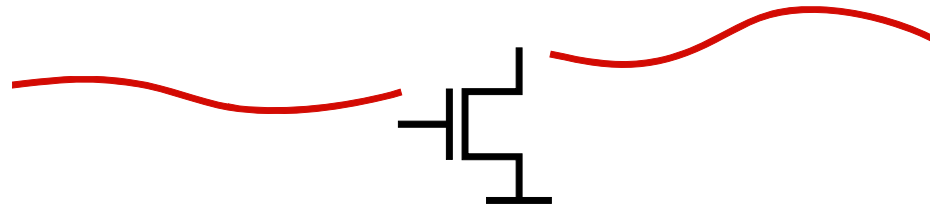
## *Time-Based Circuits*

---

- Traditional analog circuits utilize voltage and current with bandwidth constrained signaling



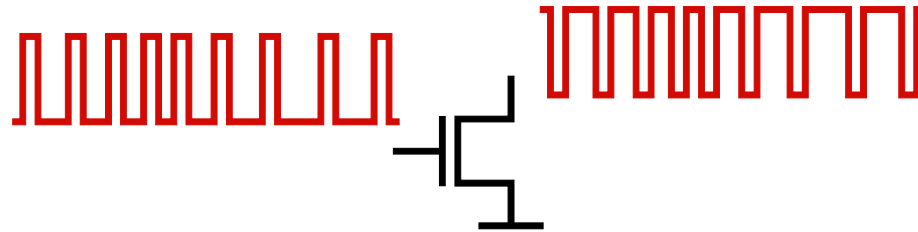
- Time-based circuits utilize the timing of edges produced by “digital” circuits



- Modern CMOS processes are offering faster edge rates and lower delay through digital circuits

**High bandwidth of time-based circuits  
creates challenges for high speed simulation**


# A Common Time-Based Circuit

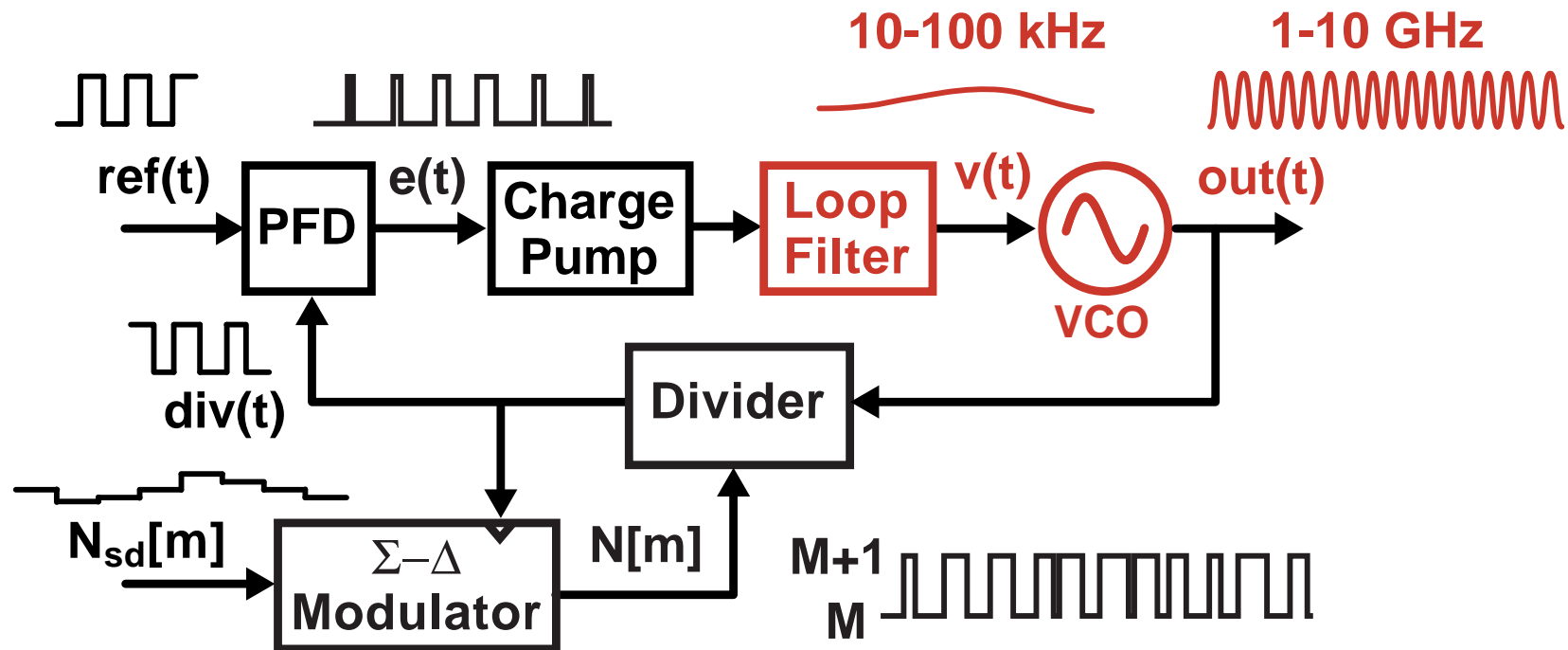

- Consider a fractional-N synthesizer as a prototypical time-based circuit
  - High output frequency → High sample rate
  - Long time constants → Long time span for transients


Large number of simulation time steps required
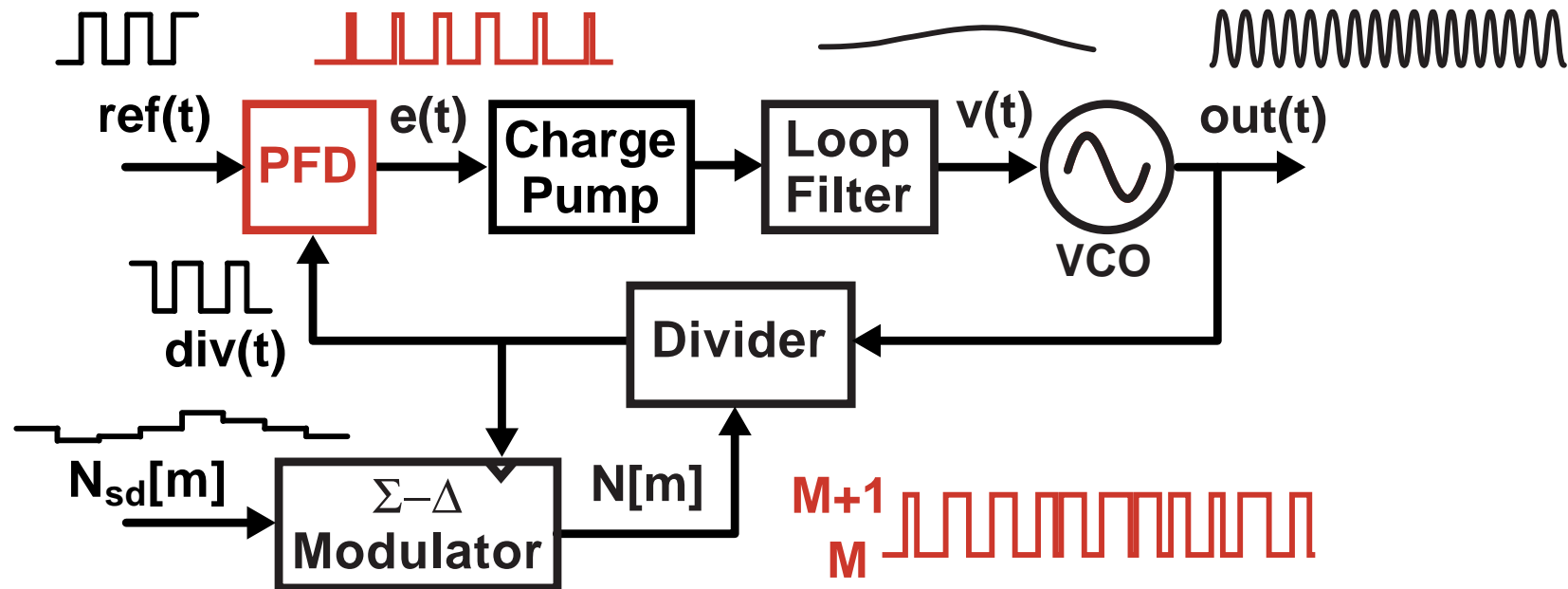
# Continuously Varying Edges Lead to Accuracy Issues



- PFD output has very high bandwidth
  - Difficult to achieve high accuracy within a conventional discrete-time or SPICE level simulator
- Non-periodic dithering of divider complicates matters
  - Periodic, steady-state methods do not apply

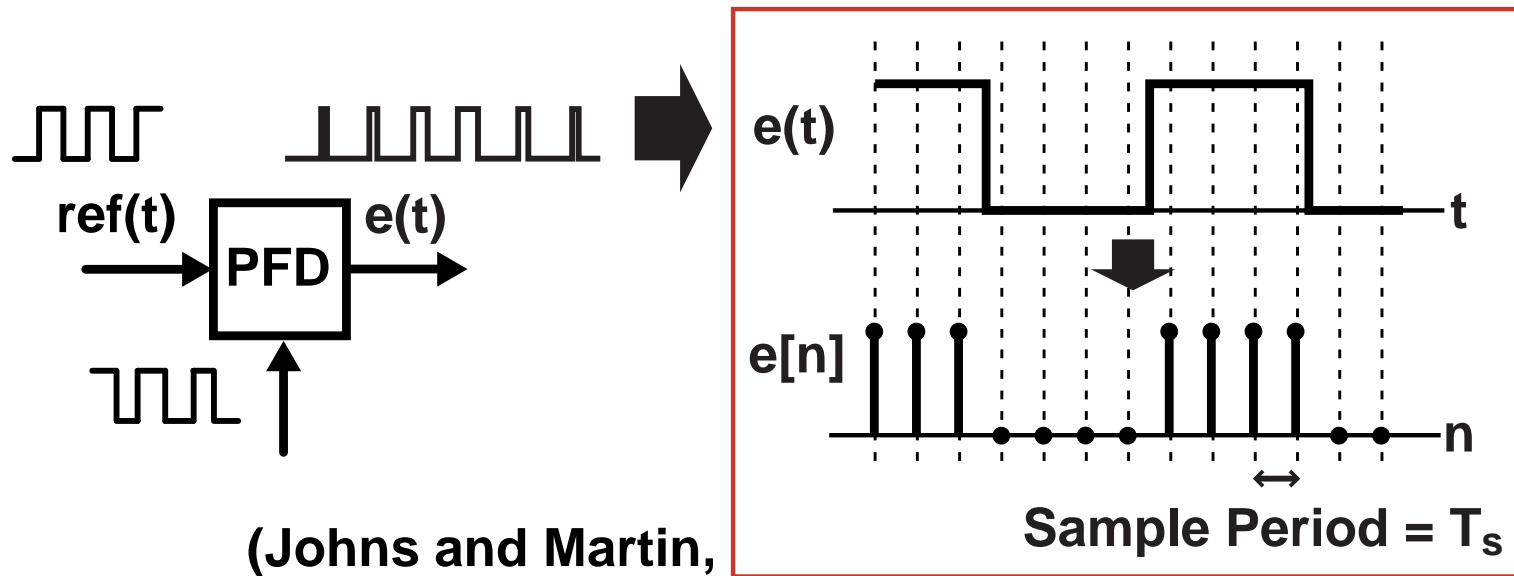
# Consider A Classical Constant-Time Step Method



(Johns and Martin,  
Analog Integrated Circuit Design)


- **Directly sample the PFD output according to the simulation sample period**
  - Simple, fast, readily implemented in Matlab, Verilog, C++
- **Issue – quantization noise is introduced**
  - This noise can overwhelm the PLL noise sources we are trying to simulate

## Alternative: Event Driven Simulation

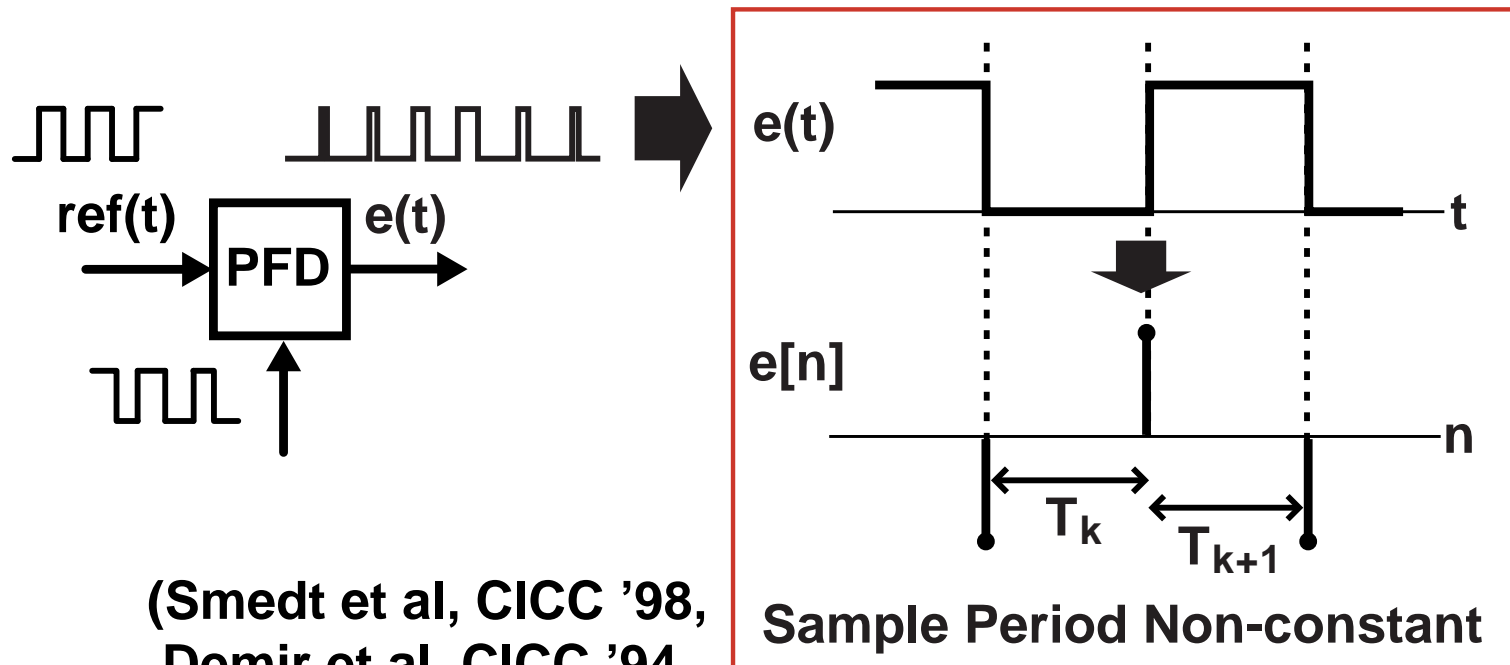

- Set simulation time samples at PFD edges
  - Sample rate can be lowered to edge rate!
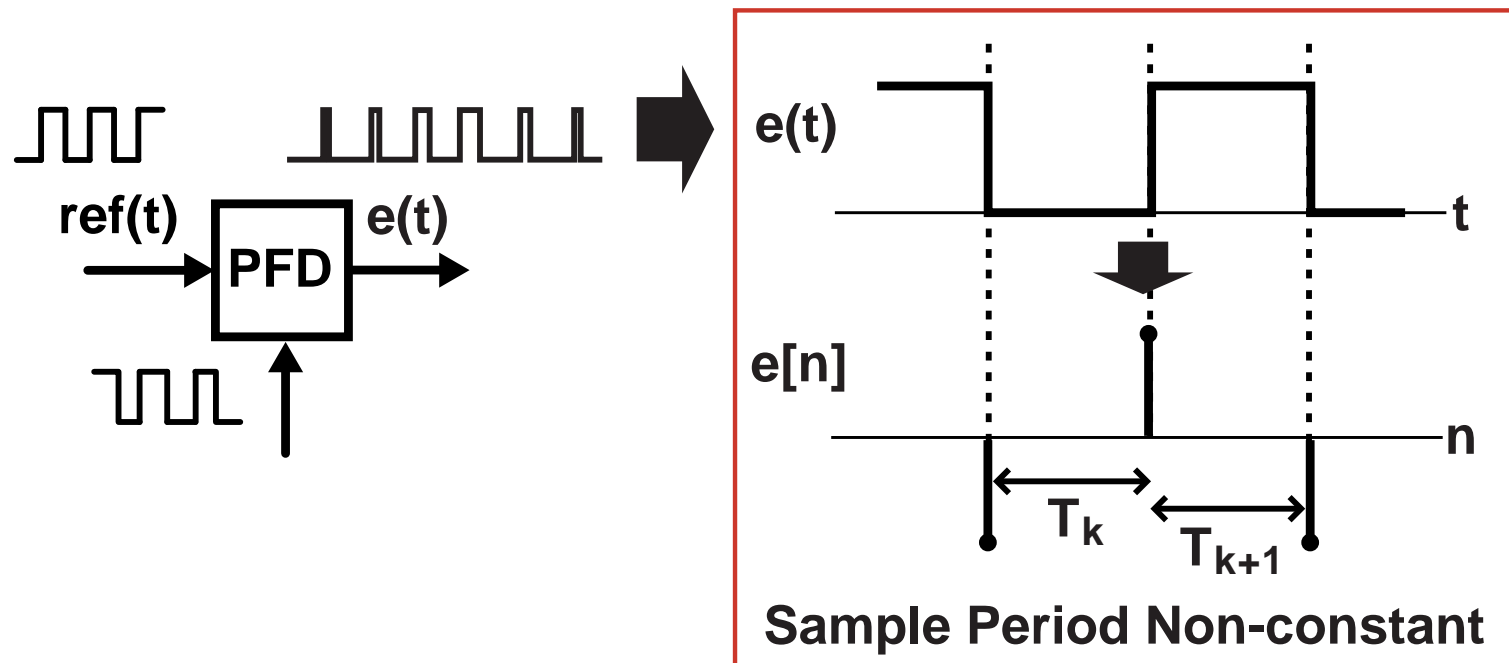
## Issue: Non-Constant Time Step Brings Complications




- Filters and noise sources must account for varying time step in their code implementations
- Spectra derived from mixing and other operations can display false simulation artifacts
- Setting of time step becomes progressively complicated if multiple time-based circuits simulated at once





***Is there a better way?***
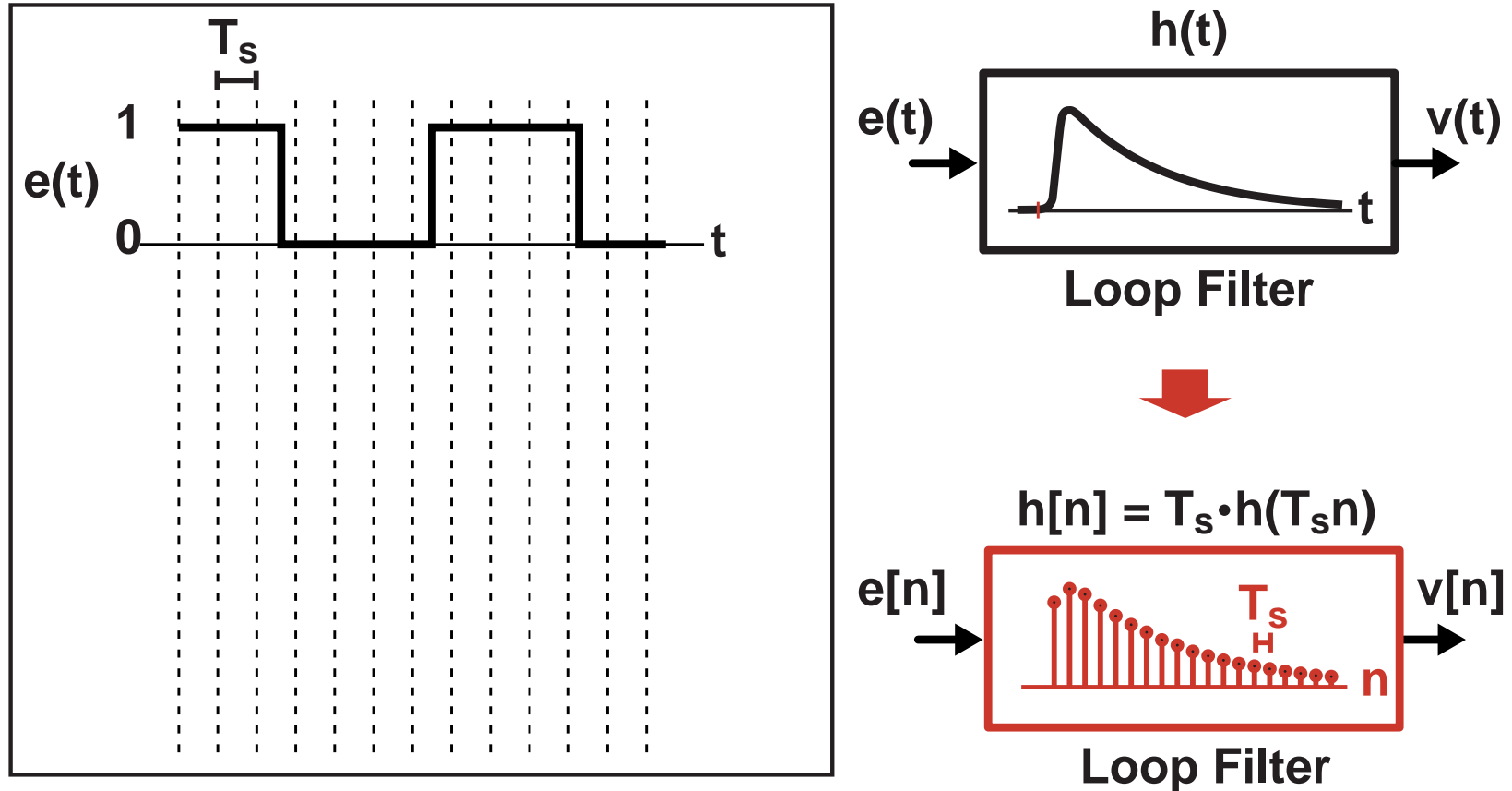
## Proposed Approach: Use Constant Time Step





- **Straightforward CT to DT transformation of filter blocks**
  - Use bilinear transform or impulse invariance methods
- **Overall computation framework is fast and simple**
  - Simulator can be based on Verilog, Matlab, C++
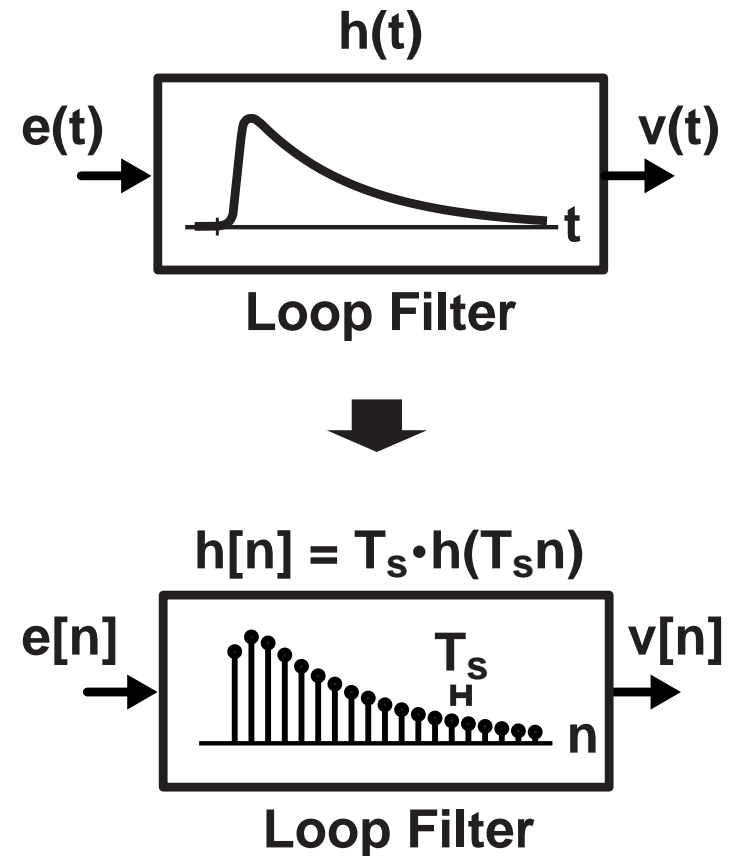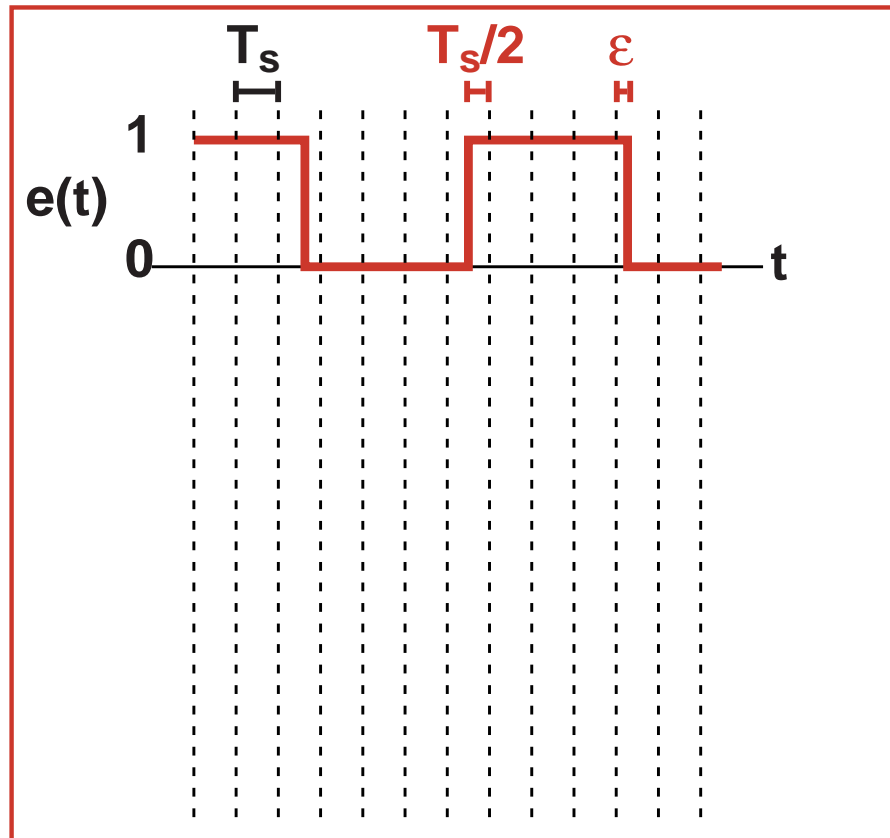
## Problem: Quantization Noise at PFD Output





- Edge locations of PFD output are quantized
  - Resolution set by time step:  $T_s$
- Reduction of  $T_s$  leads to long simulation times
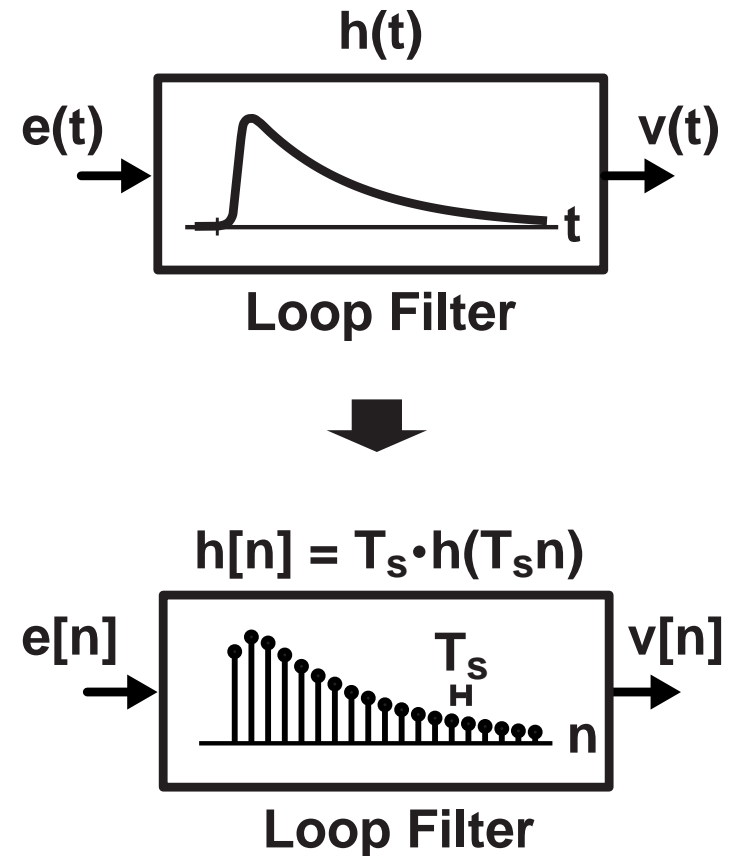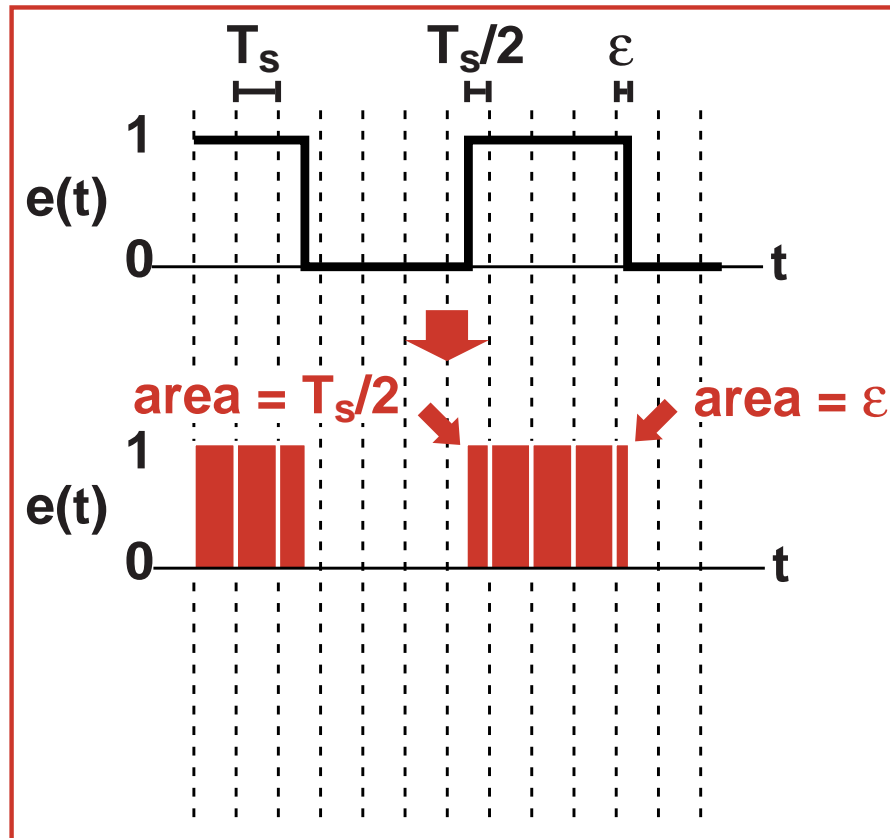
# Proposed Approach: View as Series of Pulses




- Area of each pulse set by edge locations
- Key observations:
  - Pulses look like impulses to loop filter
  - Impulses are parameterized by their area and time offset

# Proposed Area Conservation Method

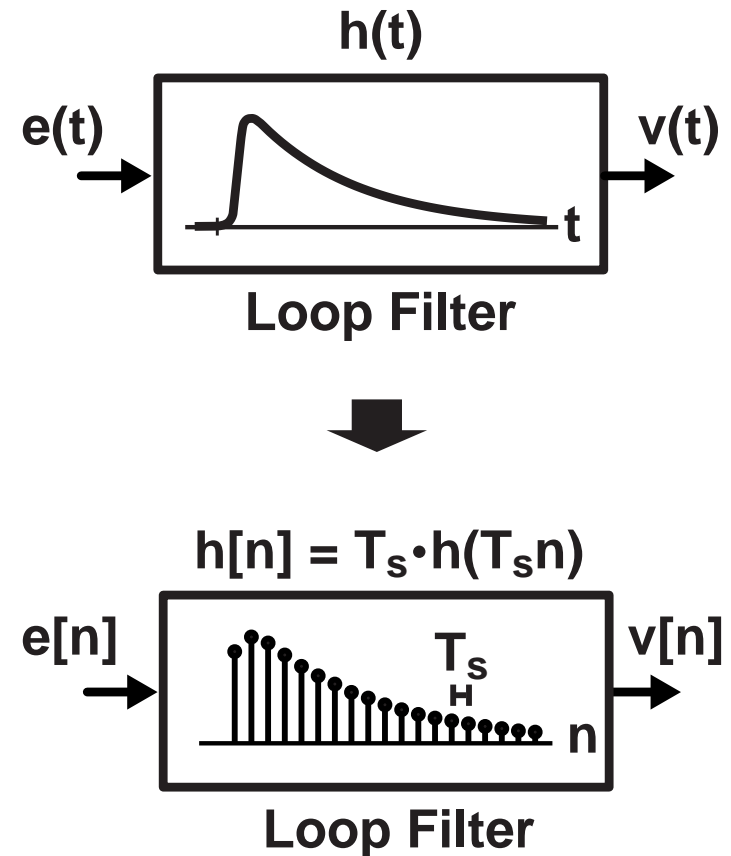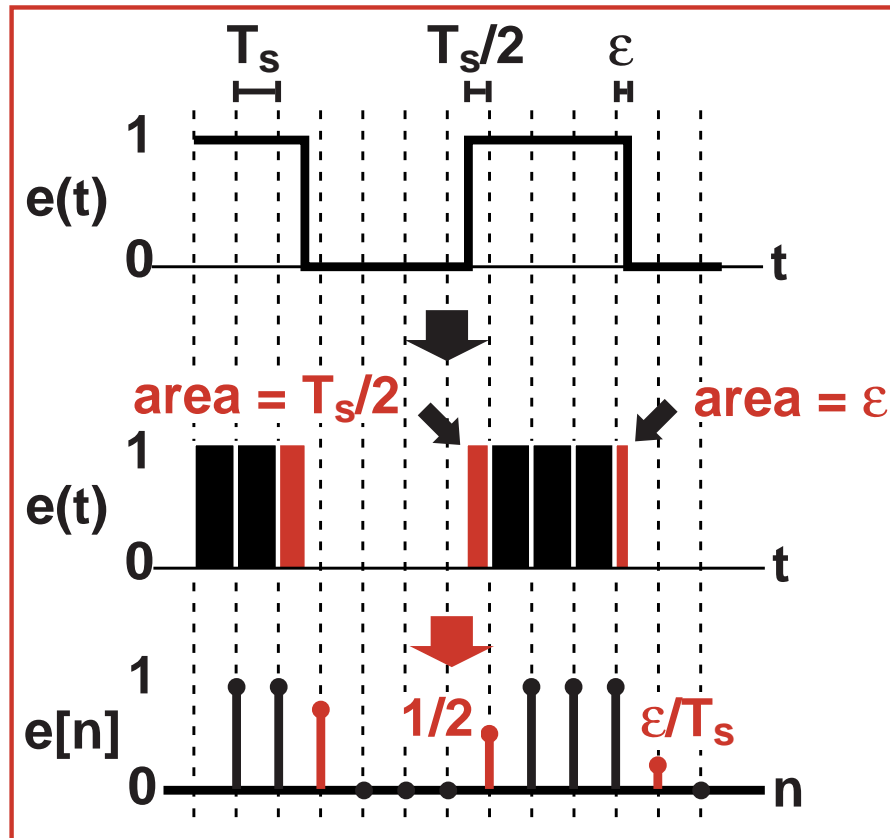


- **Set  $e[n]$  samples according to pulse areas**
  - Leads to very accurate results
  - Fast computation

# Double\_Interp Protocol

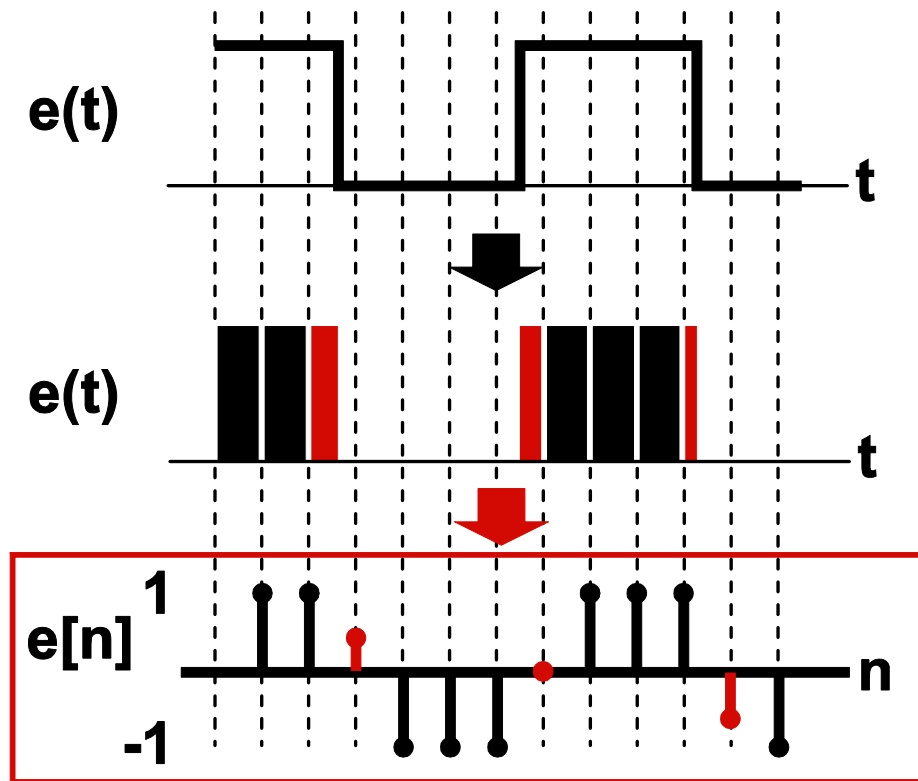



- Protocol sets signal samples to -1 or 1 except for transitions
  - Transition values between -1 and 1 are directly related to the edge time location
  - Can be implemented in C++, Verilog, and Matlab/Simulink
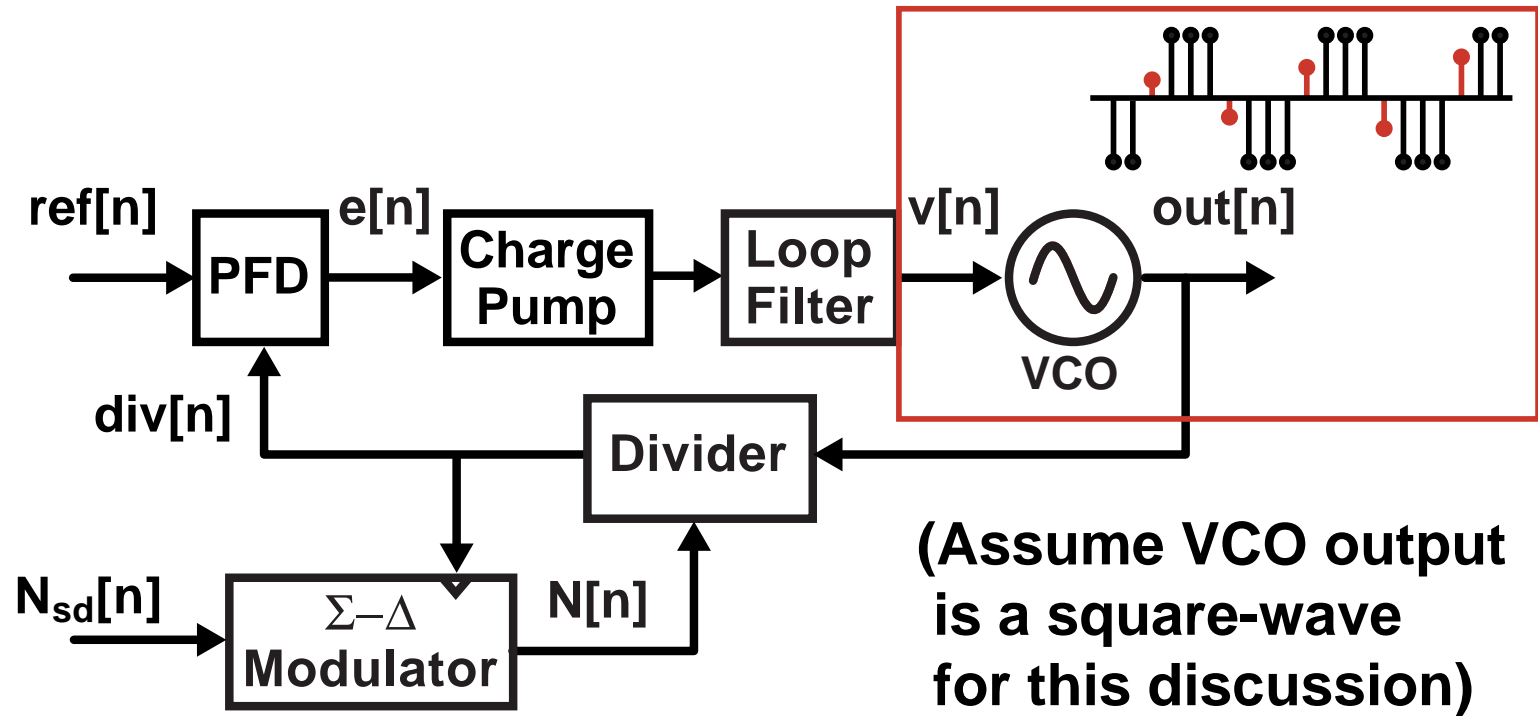
## VCO is a Key Block for Double\_Interp Encoding



- The VCO block is the key translator from a bandlimited analog input to an edge-based waveform
  - We can create routines in the VCO that calculate the edge times of the output and encode their values using the `double_interp` protocol


# Calculation of Transition Time Values

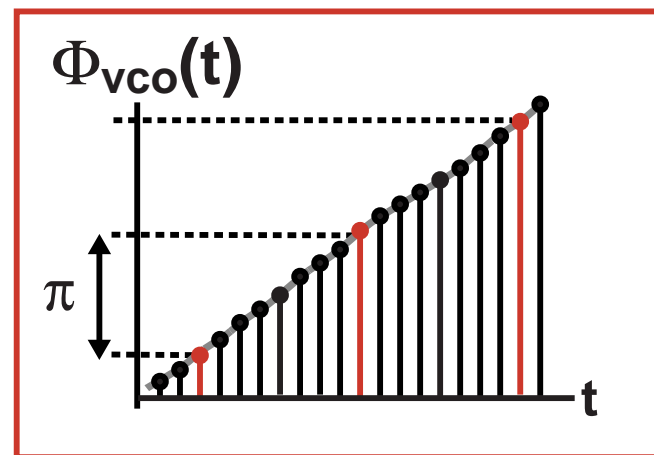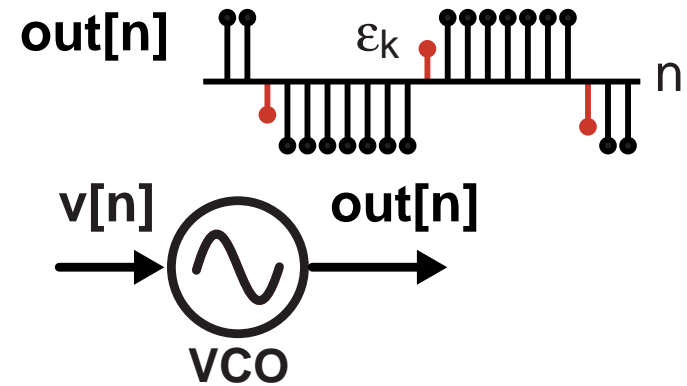

- Model VCO based on its phase



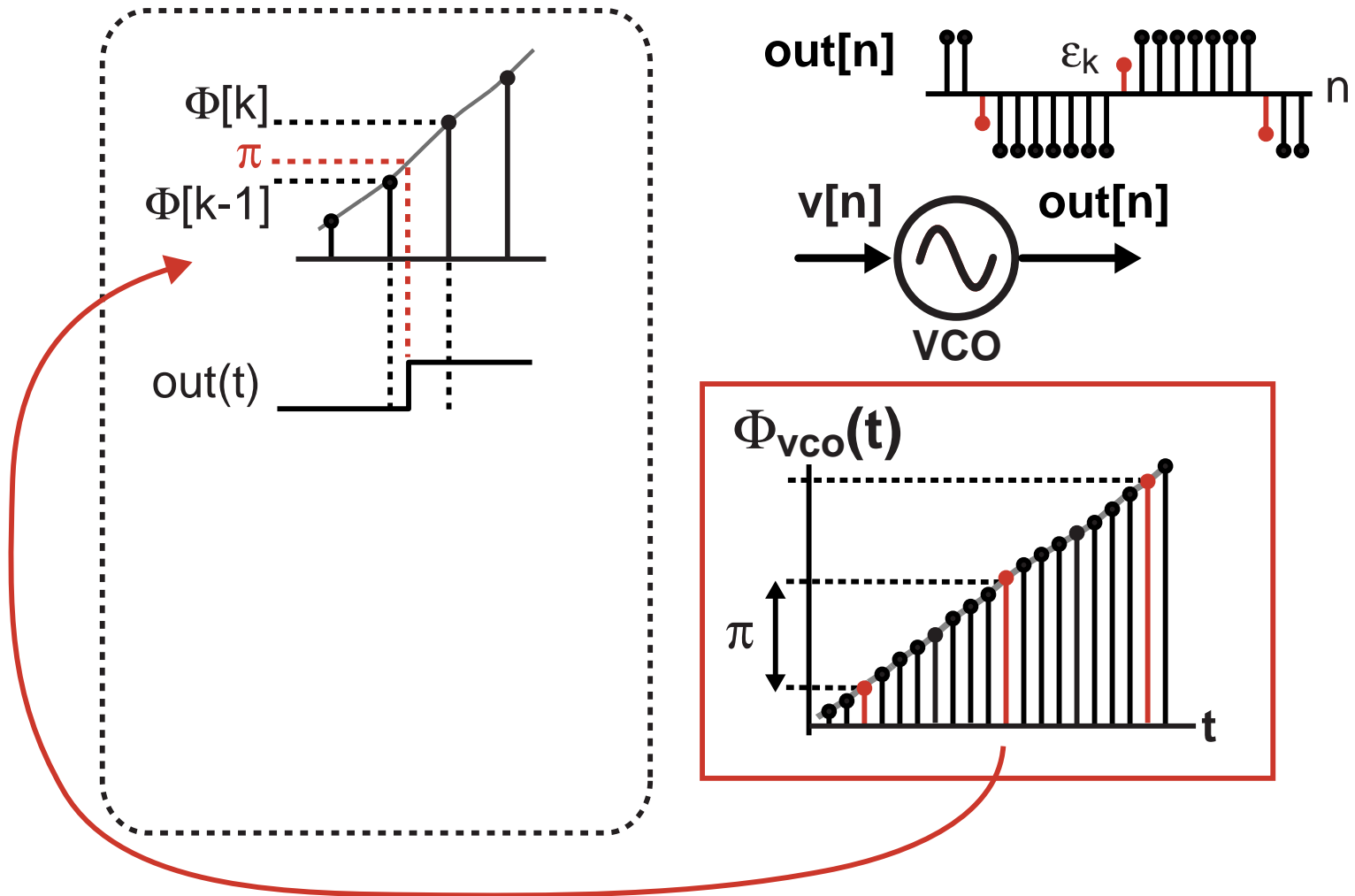
# Calculation of Transition Time Values (cont.)




- Determine output transition time according to phase
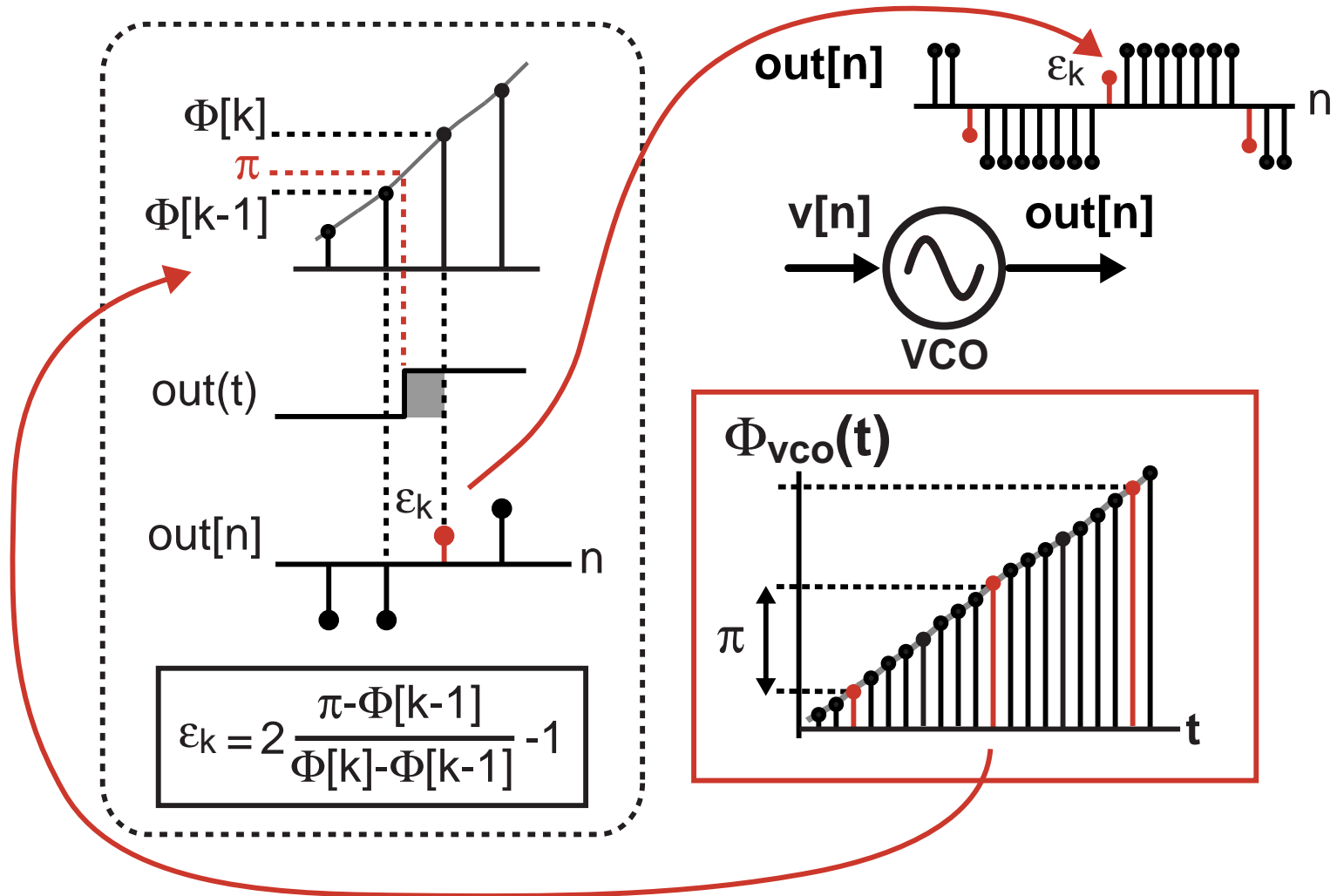
## Calculation of Transition Time Values (cont.)




- Use first order interpolation to determine transition value
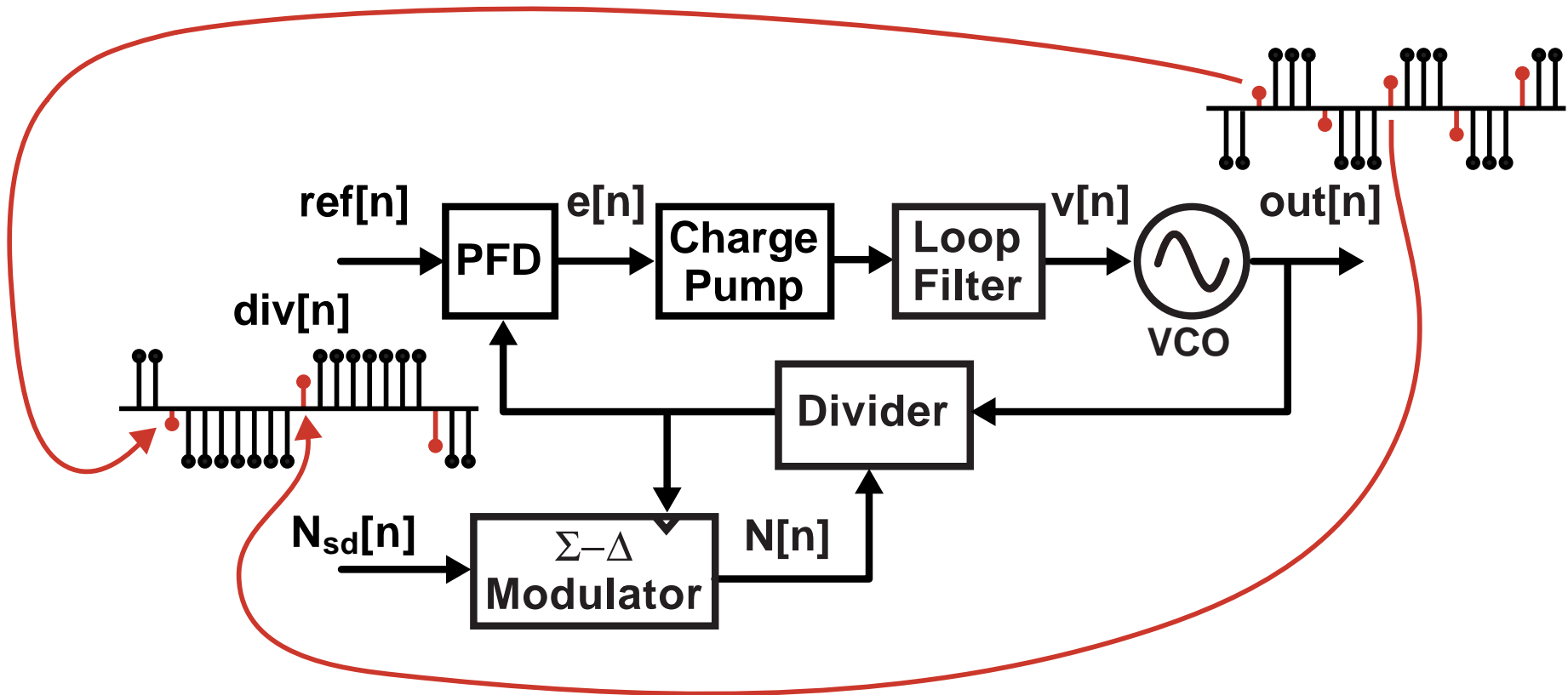
# Processing of Edges using Double\_Interp Protocol




- Frequency divider block simply passes a sub-sampling of edges based on the VCO output and divide value
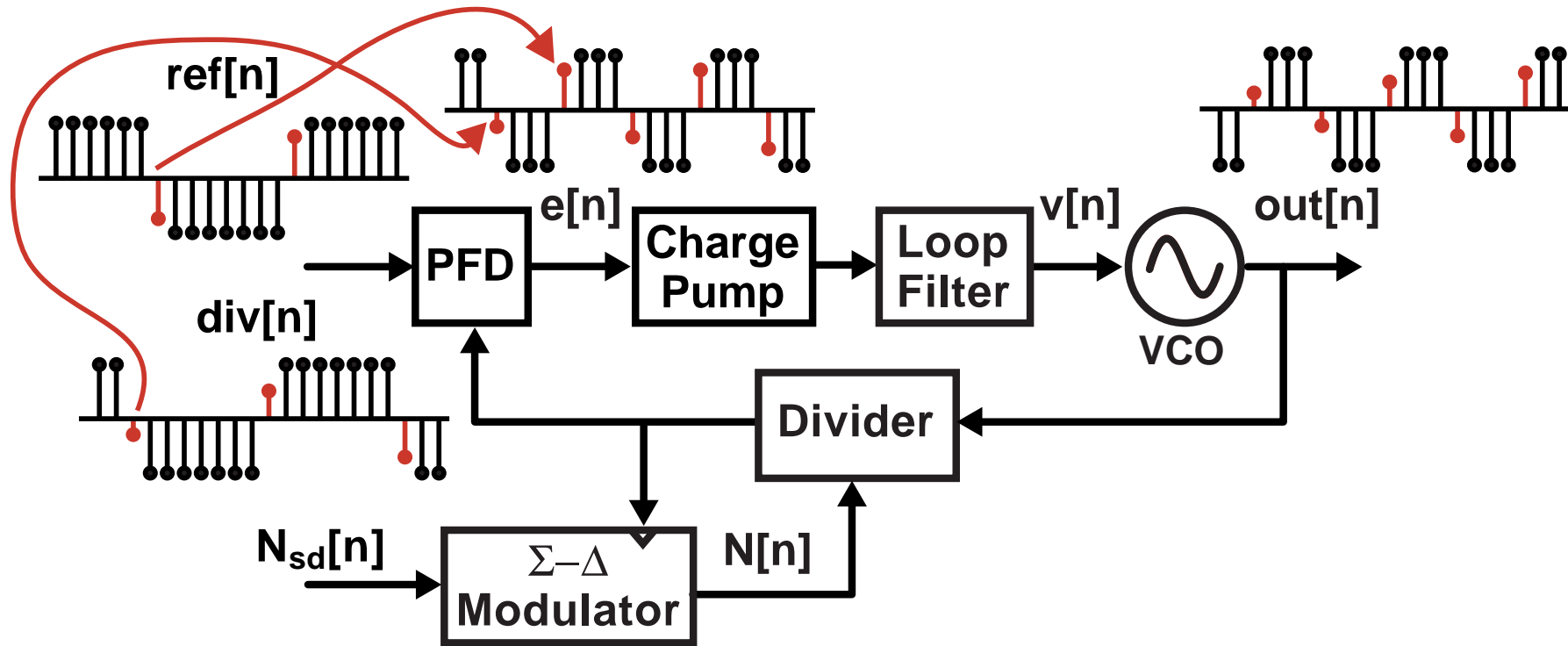
# Processing of Edges using Double\_Interp Protocol




- Phase Detector compares edges times between reference and divided output and then outputs pulses that preserve the time differences
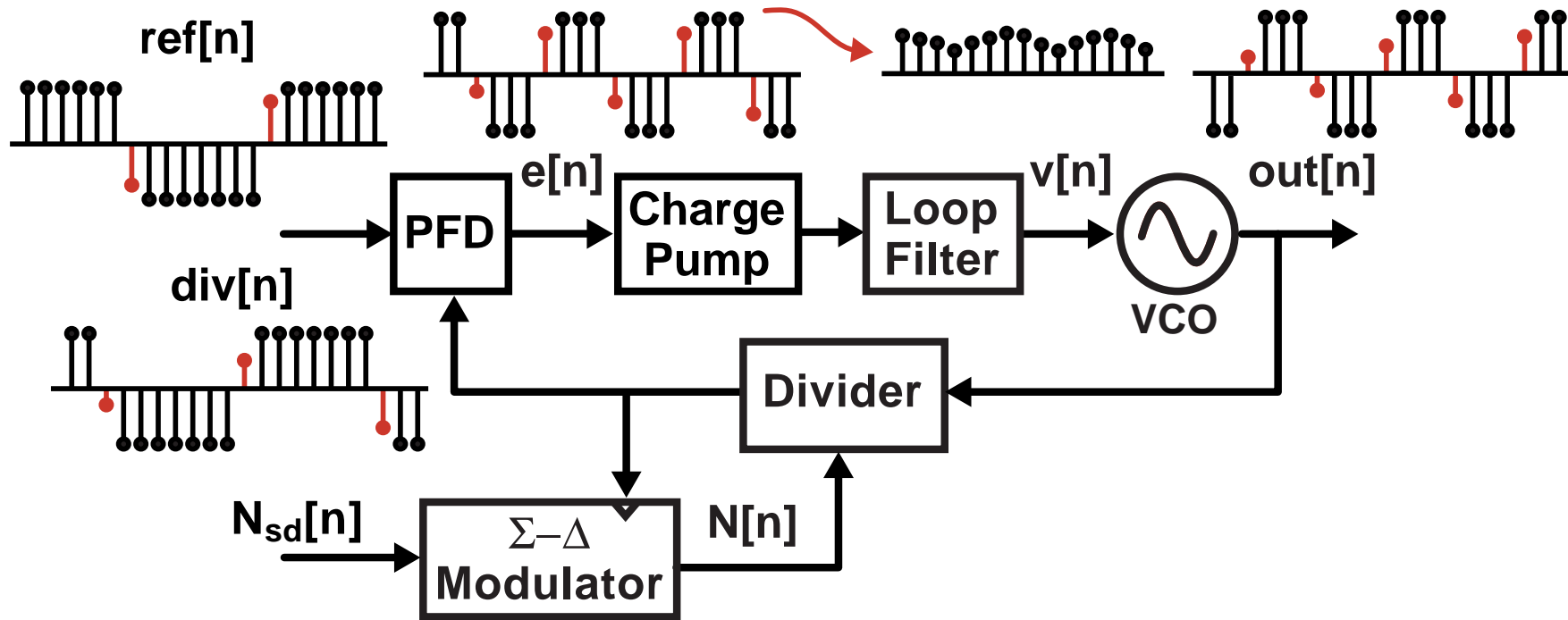
# Processing of Edges using Double\_Interp Protocol




- Charge Pump and Loop filter operation is straightforward to model
  - Simply filter pulses from phase detector as discussed earlier
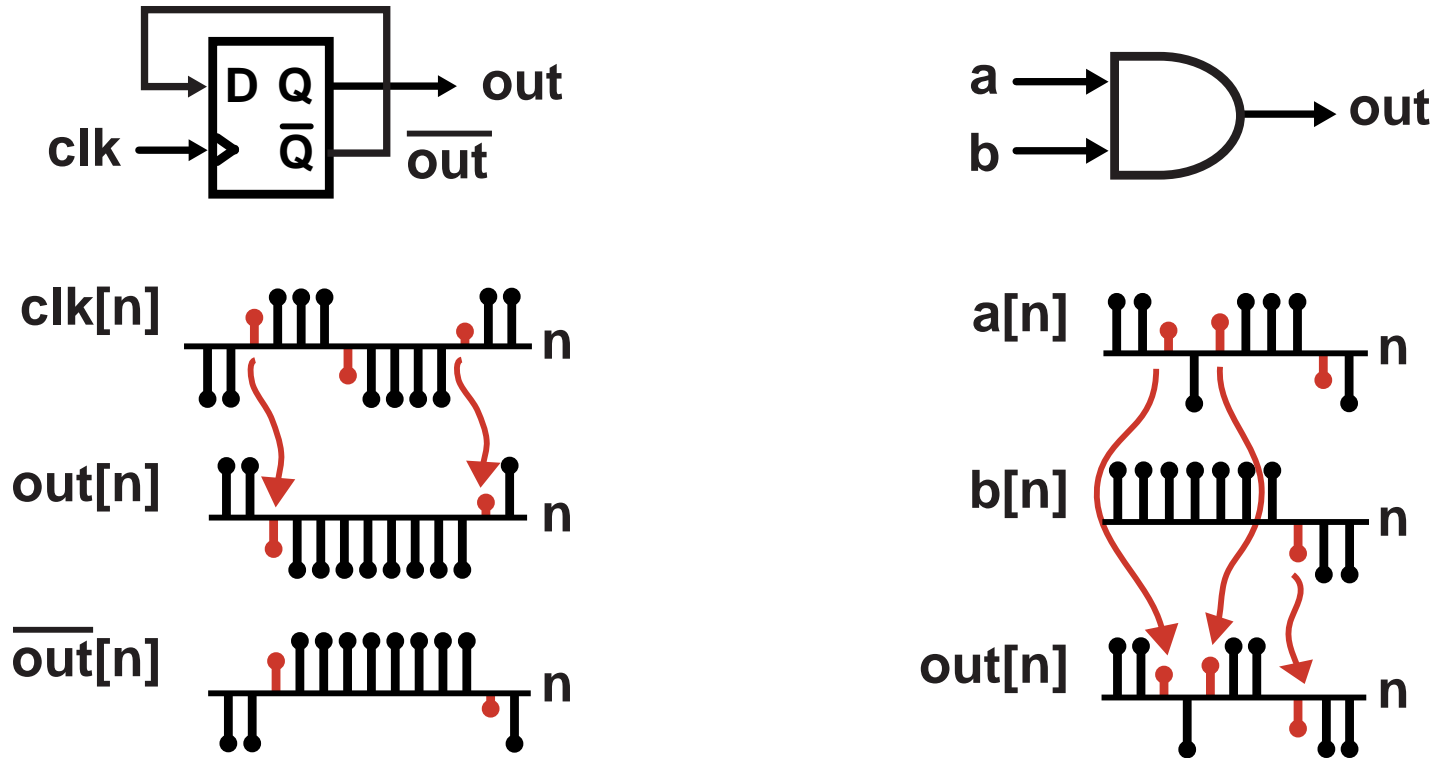
# Using the Double\_Interp Protocol with Digital Gates



- Relevant timing information contained in the input that causes the output to transition
  - Determine which input causes the transition, then pass its transition value to the output

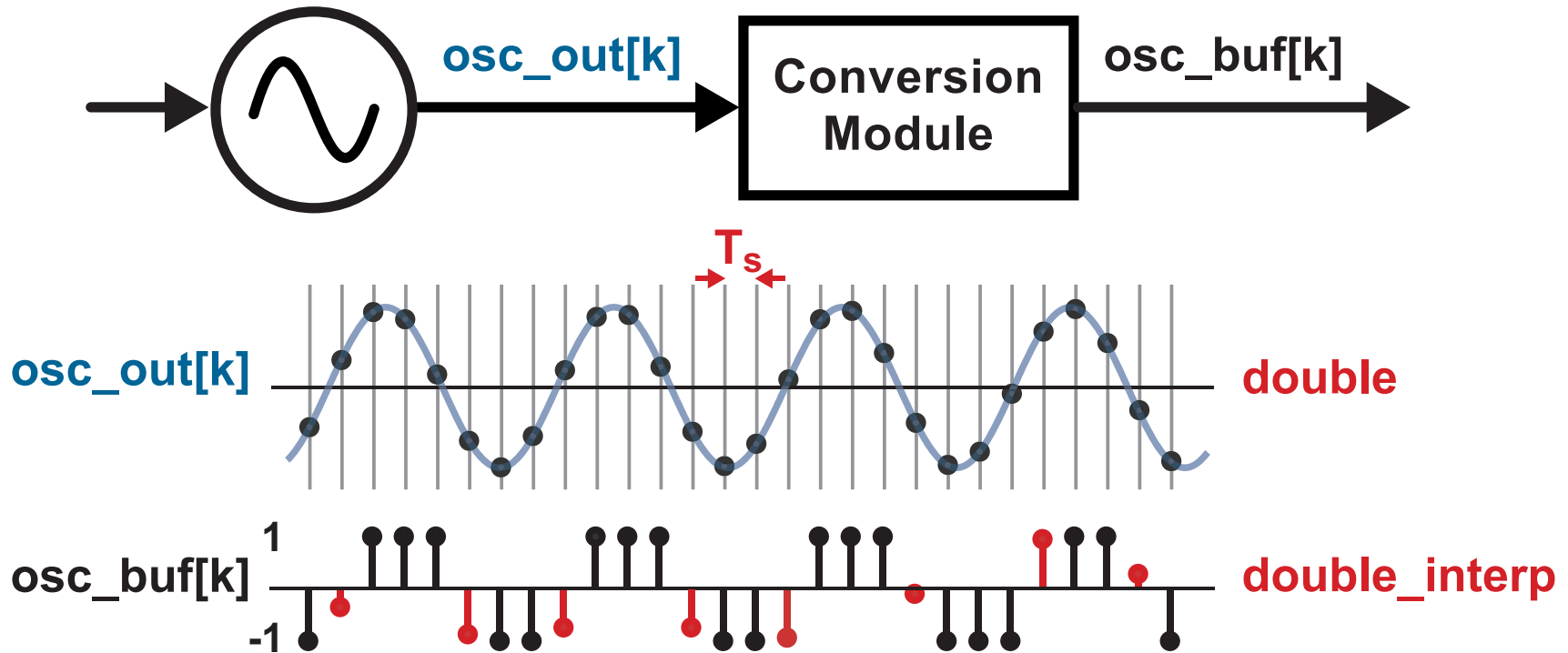
# Using the Double\_Interp Protocol with Sine Waves



- In some systems we must deal directly with sine waves
  - An explicit conversion module should be utilized
    - We can convert to `double_interp` protocol using a similar interpolation technique as described earlier
  - See **`gmsk_limitamp`** module within **GMSK\_Example** library
    - Used in module **`gmsk_pll_transmitter`** in the same library

# Summary of Block-by-Block Computation Method


---

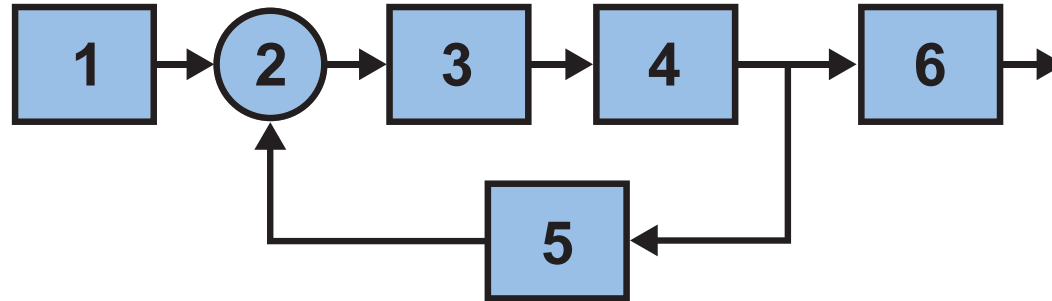

- Requires unilateral flow through blocks
- Impacts phase margin of feedback loops
  - Need  $1/T_s \gg$  bandwidth of feedback loop
  - Need proper ordering of blocks (automatic in CppSim)
- Constant time step simplifies simulation
  - Easier block descriptions
  - Frequency domain analysis become straightforward
  - Time-based signals handled with **double\_interp** protocol



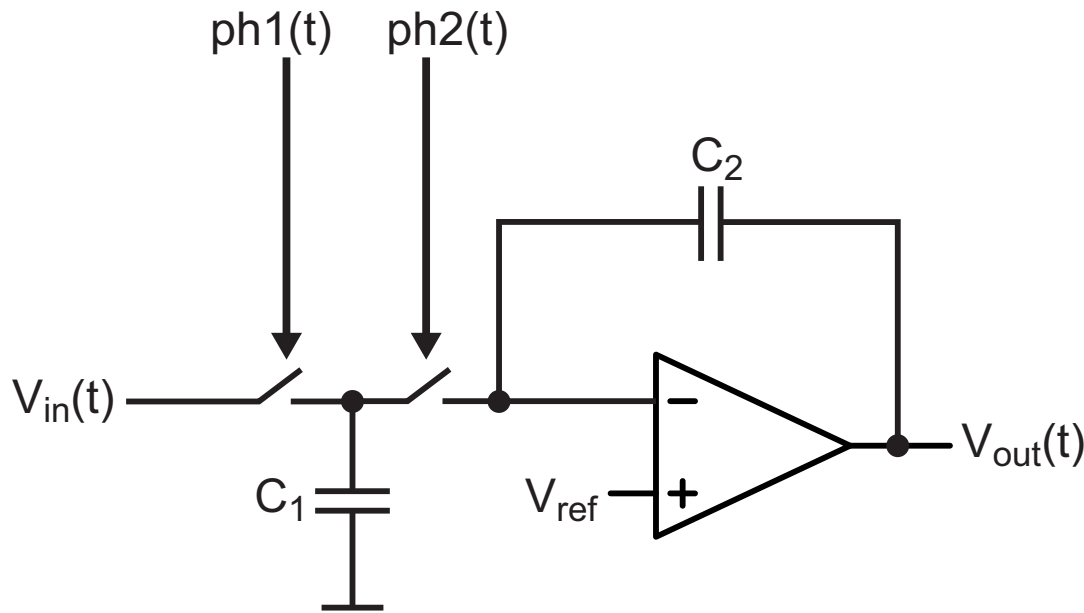
# Simulation of Switched Capacitor Circuits



- **Capacitor network with switches can be modeled with unilateral flow blocks, but many practical issues:**
  - Very challenging for beginners, tedious for experts
  - Difficult to check correctness of model
  - Difficult to investigate alternative architectures


**We need a way to automate the modeling process...**

# Automatic Unilateral Model Generation

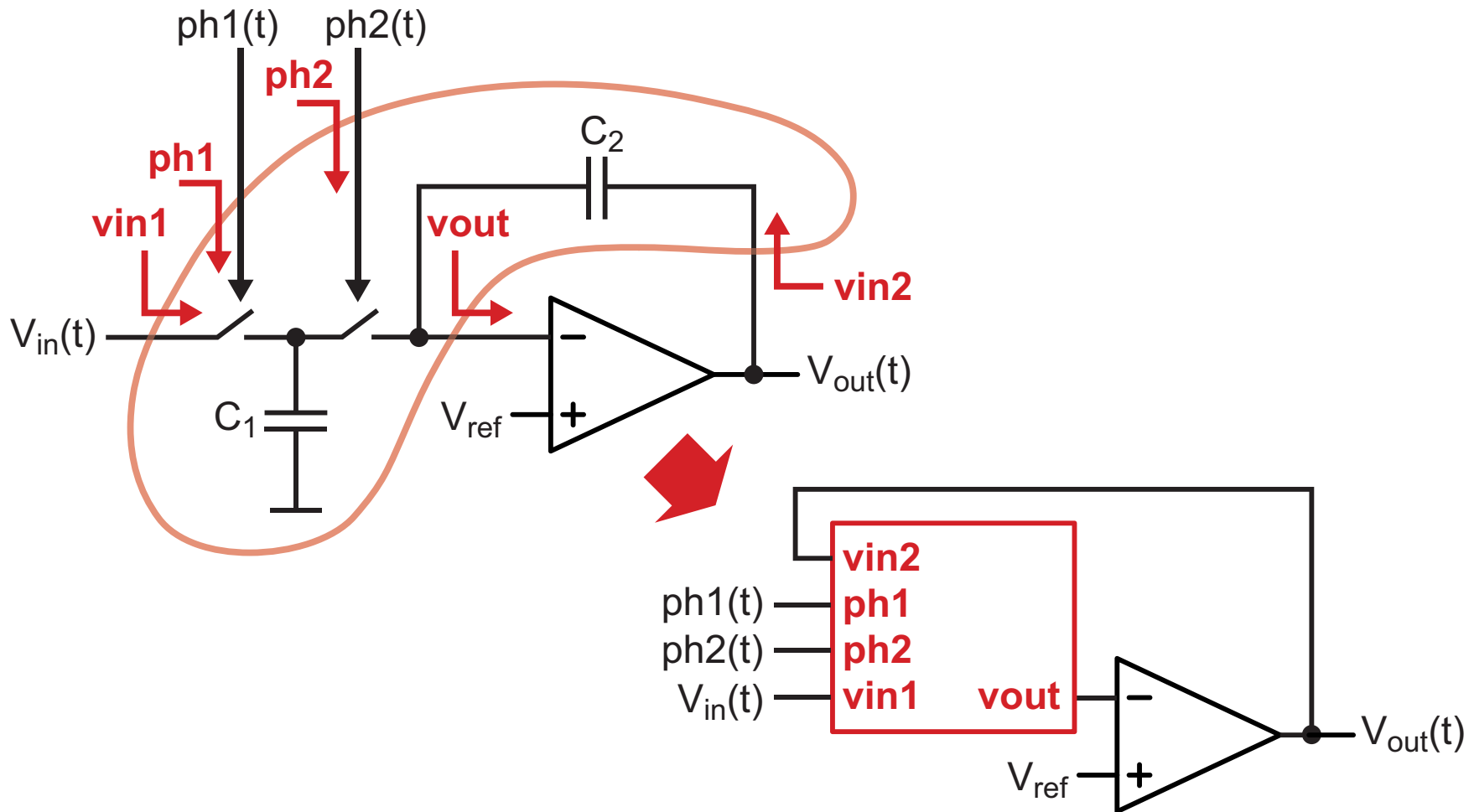


- A linear network with switches can be represented as a state-space model with switch dependent matrices
  - An equivalent unilateral flow block is created
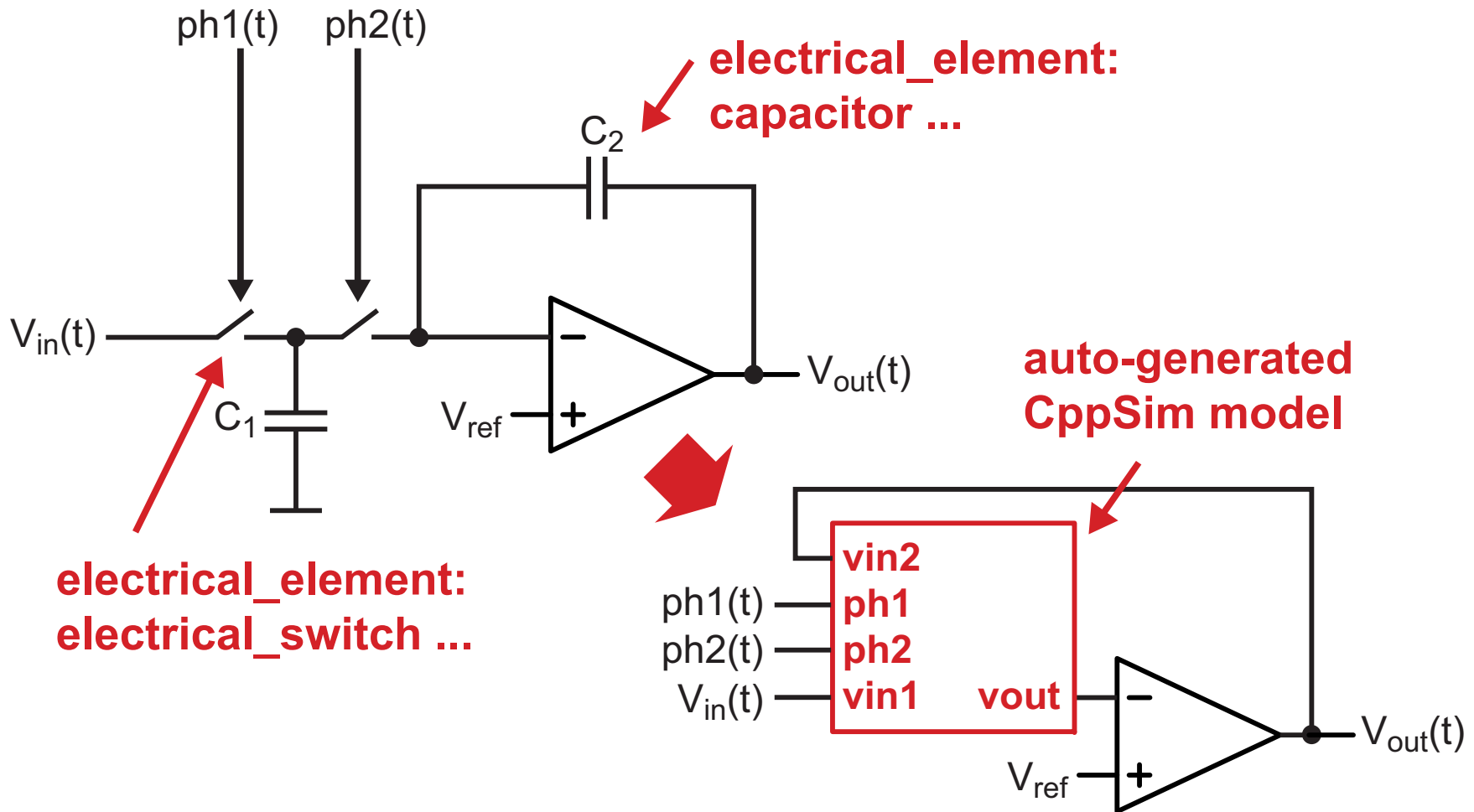
# CppSim Approach to Linear Networks with Switches




- User specifies the CppSim model for linear elements, switches, and diodes using **electrical\_element:** command
  - ▀ Draw the schematic and CppSim takes care of the rest!

# Transient Noise Analysis is Supported

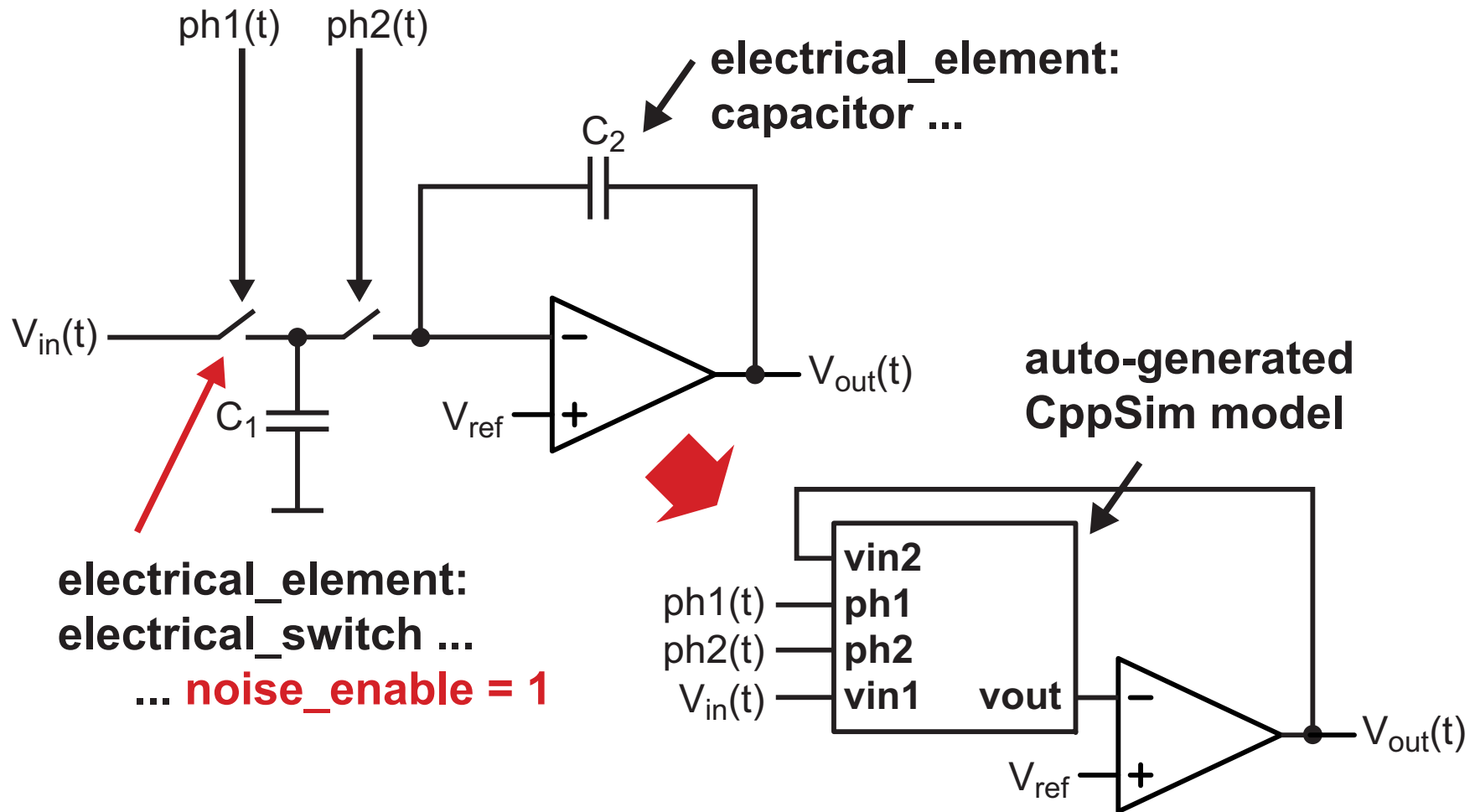


- Resistors, switches, voltage/current thermal + 1/f noise
- For  $kT/C$  noise, need adequately small time step,  $T_s$ 
  - Accuracy requires  $1/T_s > 20 \cdot \text{bandwidth of switch settling time}$
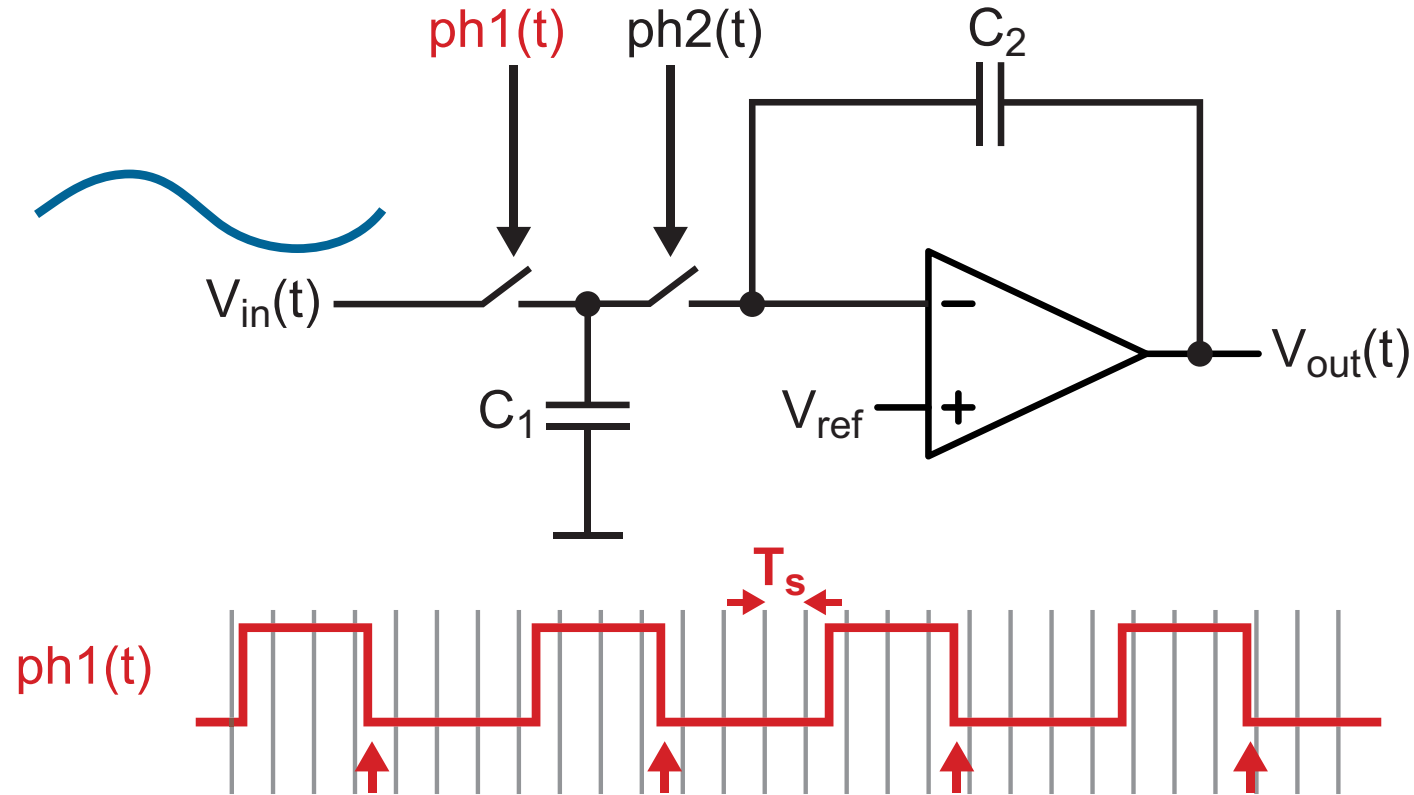
# Time Based Signals with Electrical Elements




- **Constant time step of CppSim could lead to quantization effects on sample times of clock edges**
  - **Would result in sampling errors of input waveform**

# Leverage Double\_Interp Protocol

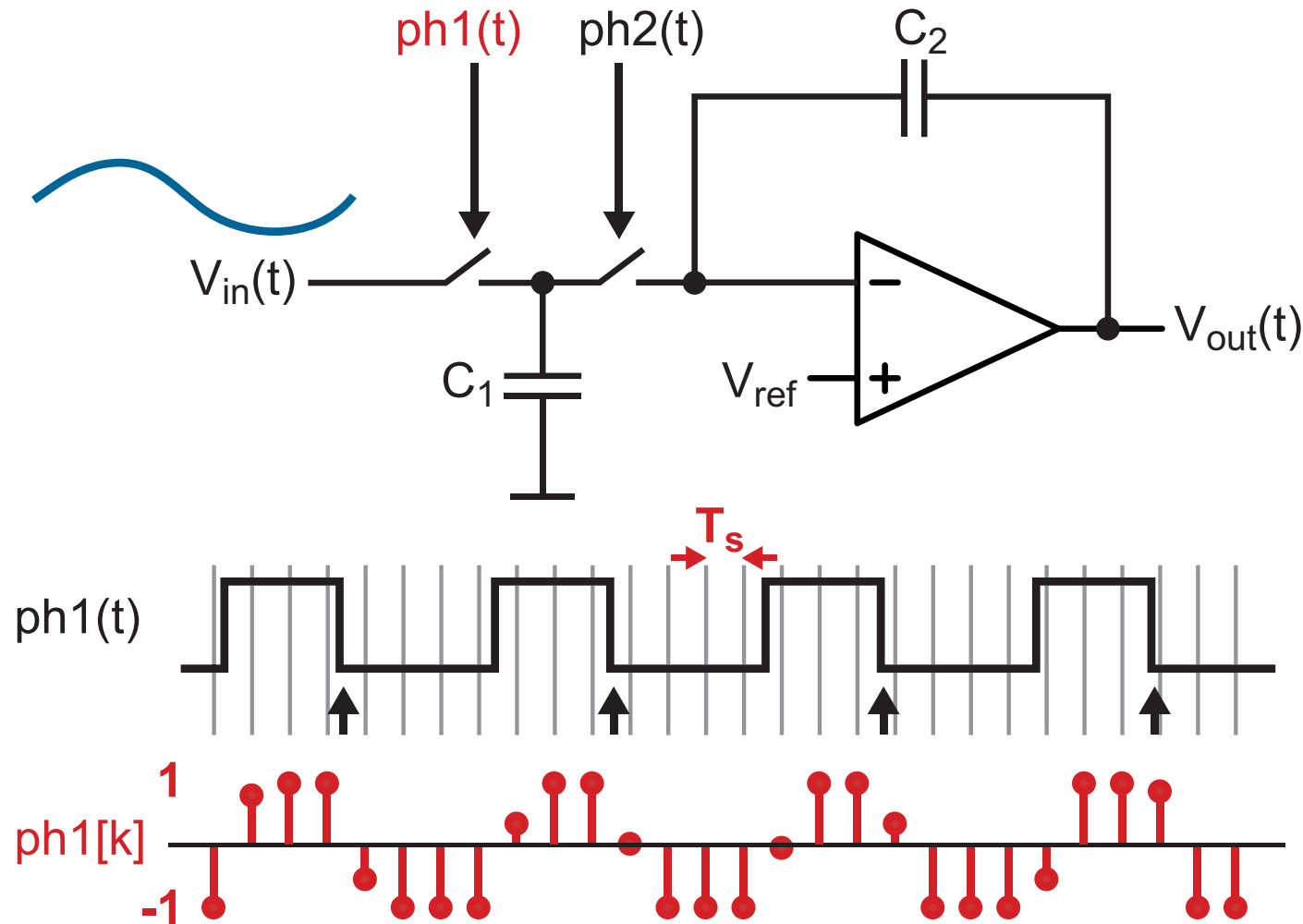


- Electrical switches within CppSim require **double\_interp** signals for the control nodes
  - Good timing accuracy achieved despite constant time step
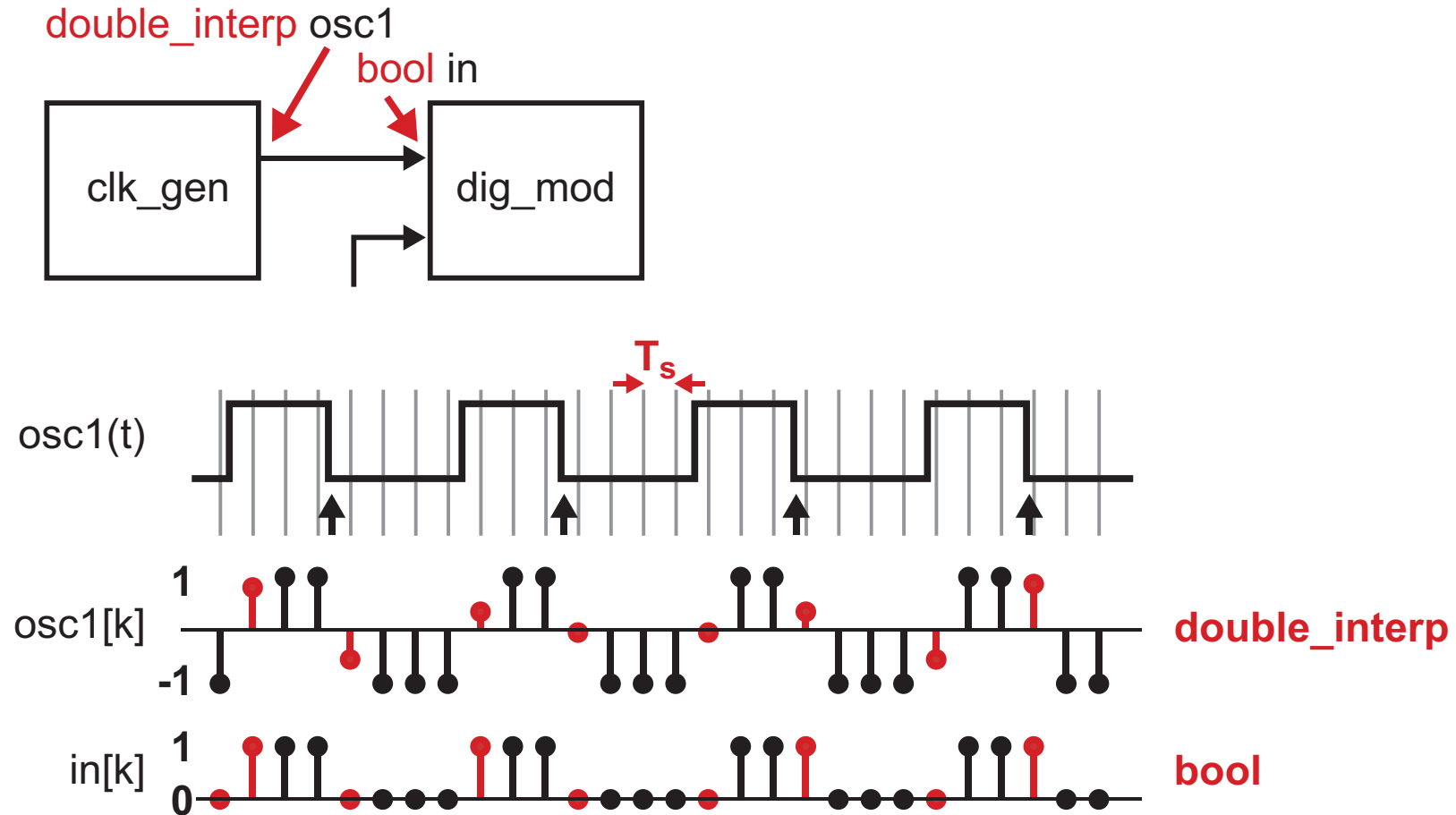
# Feeding Bool Input with Double\_Interp Signal



- **Conversion module automatically inserted**
  - **-1,1 signaling converted to 0,1 signaling**
  - **High resolution edge timing information is lost**
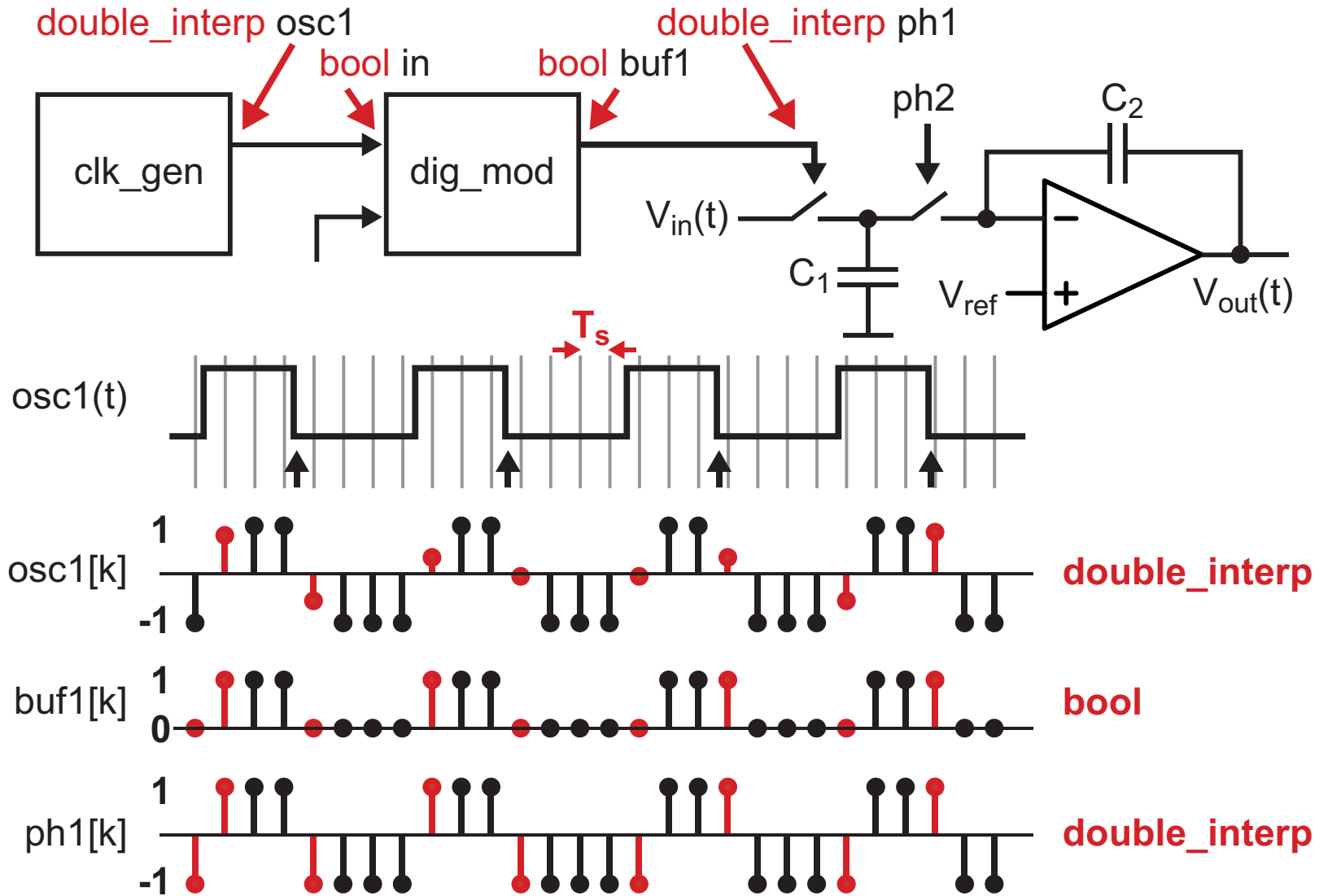
# Feeding Double\_Interp Input with Bool Signal



- **Automatic translation of 0,1 signaling to -1,1 signaling**
  - **Loss of timing information causes quantization noise!**



# Supported Electrical Elements in CppSim

resistor




capacitor




inductor




electrical\_transformer

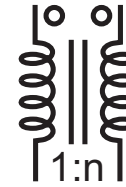


mutual\_inductors

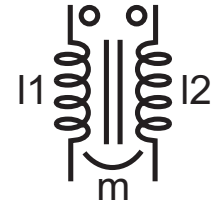


VCCS

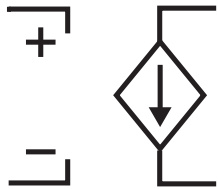


CCCS

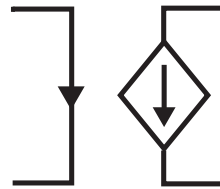


VCVS

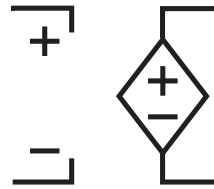

CCVS

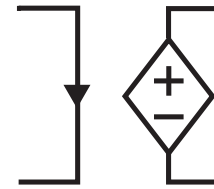

ccvs\_single\_out

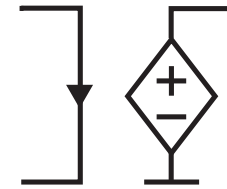

electrical\_diode



electrical\_switch



dc\_voltage




dc\_current




dc\_voltage\_with\_noise




dc\_voltage\_with\_noise\_sq

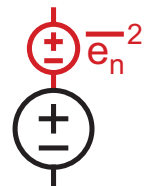


dc\_current\_with\_noise

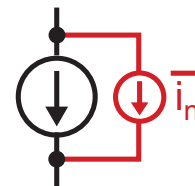

dc\_current\_with\_noise\_sq

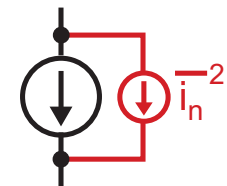

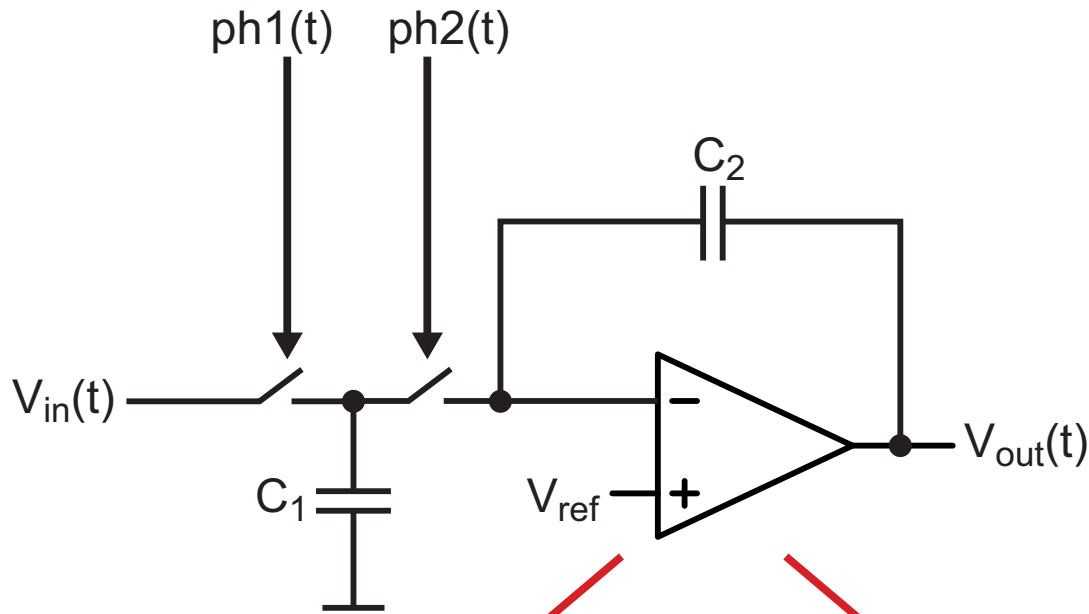
# CppSim Code Versus Electrical Element Modules



**code:**


```
Filter filt1("K", "1+1/wo*s", ...)
      ⋮
vout = filt1(vinp-vinm)
```

**electrical\_element:**

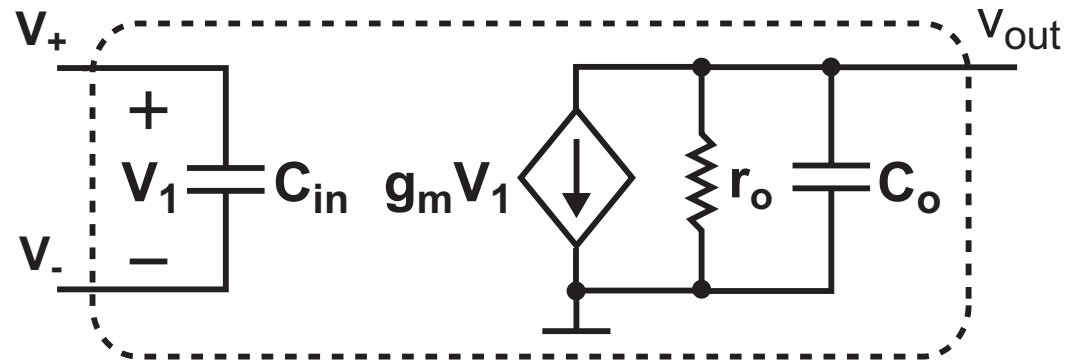


- Which approach is best for circuit blocks such as opamps?
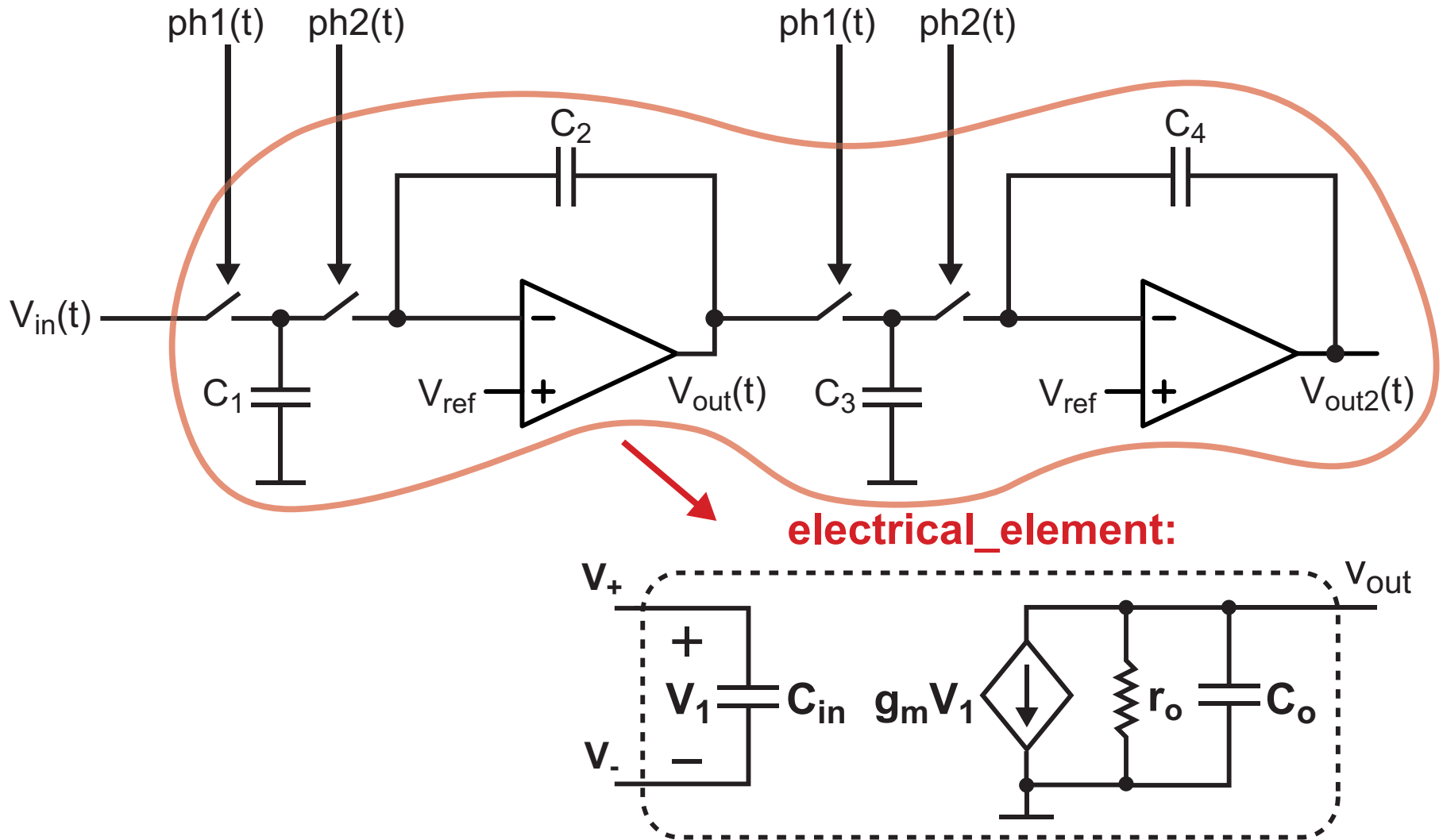
# Complexity Issue with Electrical Element Modules



- State-space calculations increase as (number of elements)<sup>2</sup>
  - Large networks dramatically slow down simulation speed
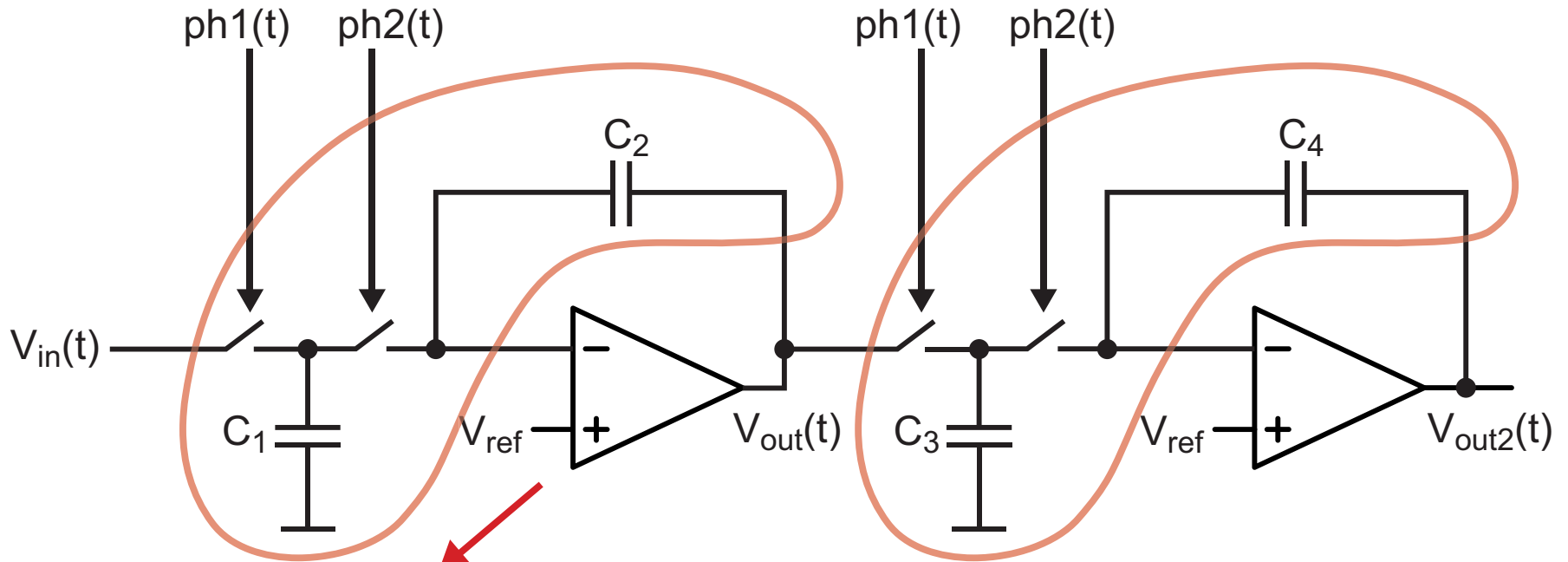
# Code Modules Allow De-Coupling Between Networks



code:

Filter filt1("K", "1+1/wo\*s", ...)


⋮

vout = filt1(vinp-vinm)

- Code modules are not sensitive to loading
  - Allows CppSim to automatically separate into sub-networks

**Code modules preferred to achieve fast simulation speed**

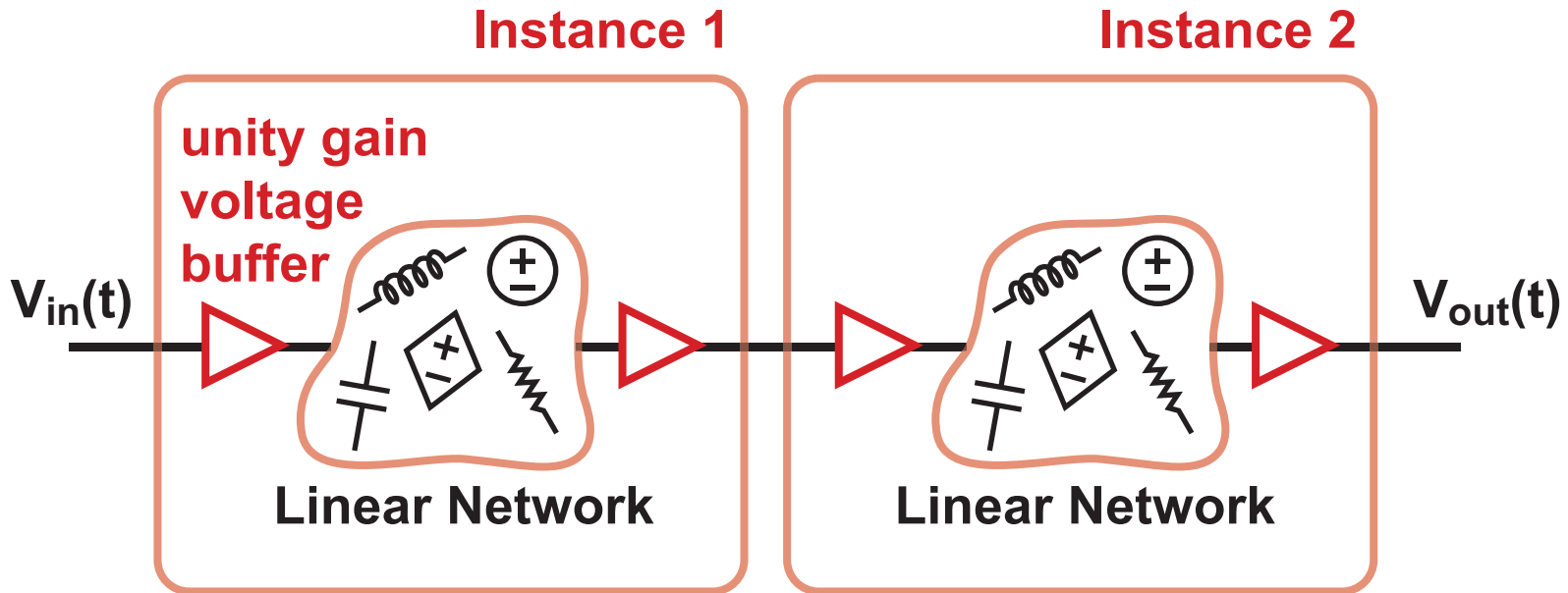
# Impact of Hierarchy on Electrical Element Networks



- CppSim implicitly inserts unity gain voltage buffers at all inputs and outputs of instances
  - Allows hierarchical simulation structure of overall system to be retained
  - De-couples networks at instance level to discourage creation of large state-space models

## Example: A Second Order RC Network


---

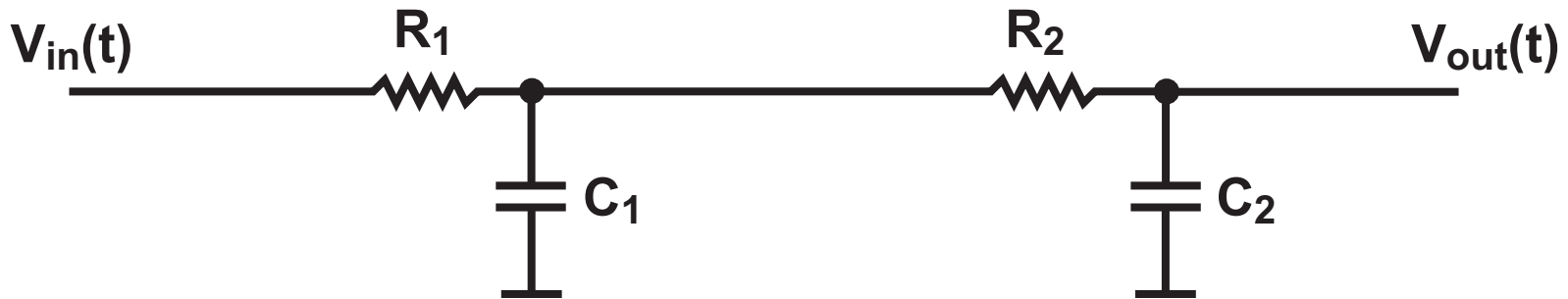

- Resulting transfer function is *NOT* simply the cascade of two identical RC filters
  - Actual pole locations are influenced by mutual coupling of the two first-order RC networks


# Cascade of First Order RC Networks as Instances

---

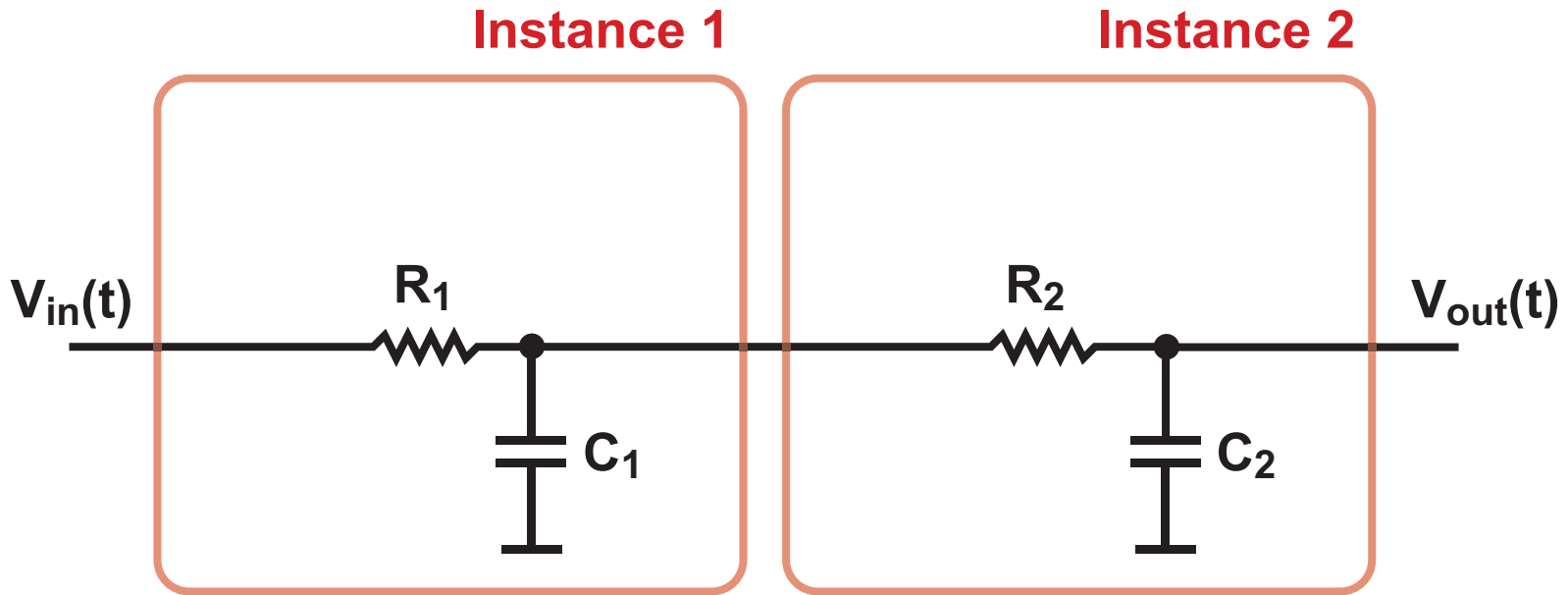

- This would appear to be the same as cascading the RC networks at the same level of hierarchy...
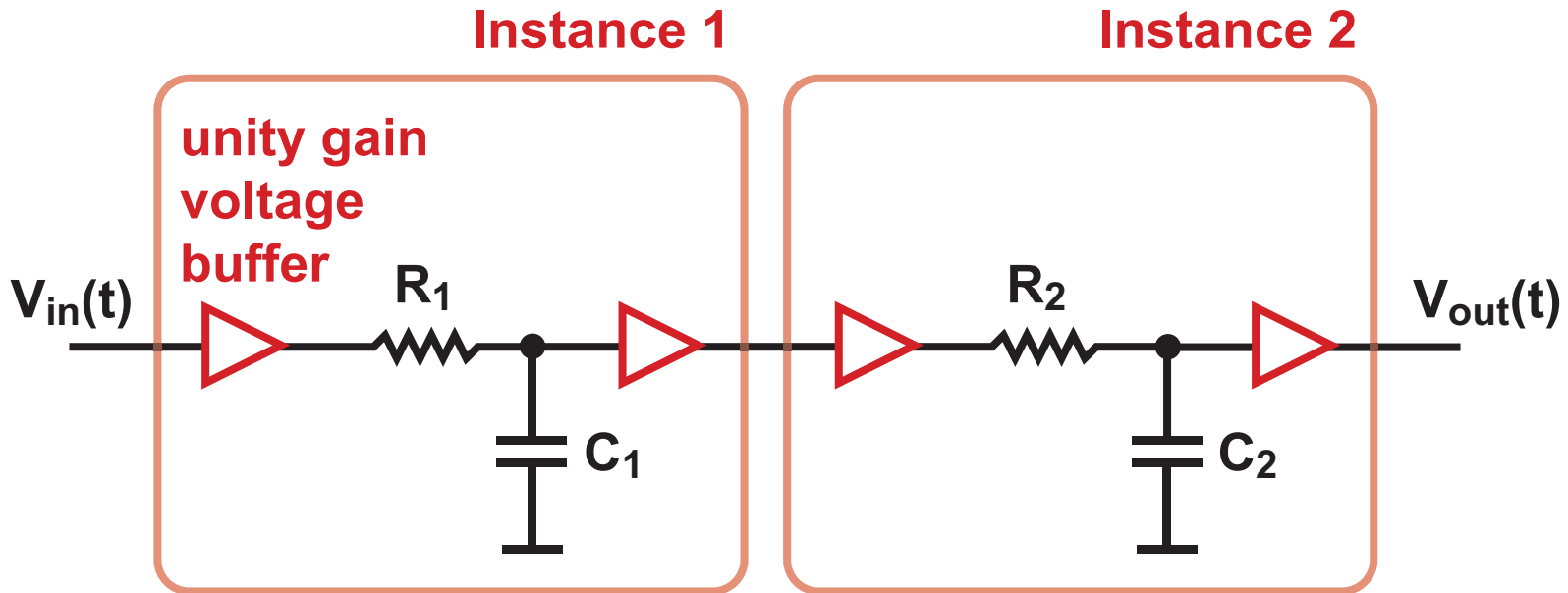
## Recall Unity Gain Voltage Buffer Insertion




- CppSim implicitly adds unity gain voltage buffers
  - Resulting transfer function is actually the cascade of two identical RC filters

How do you achieve network coupling with hierarchy?



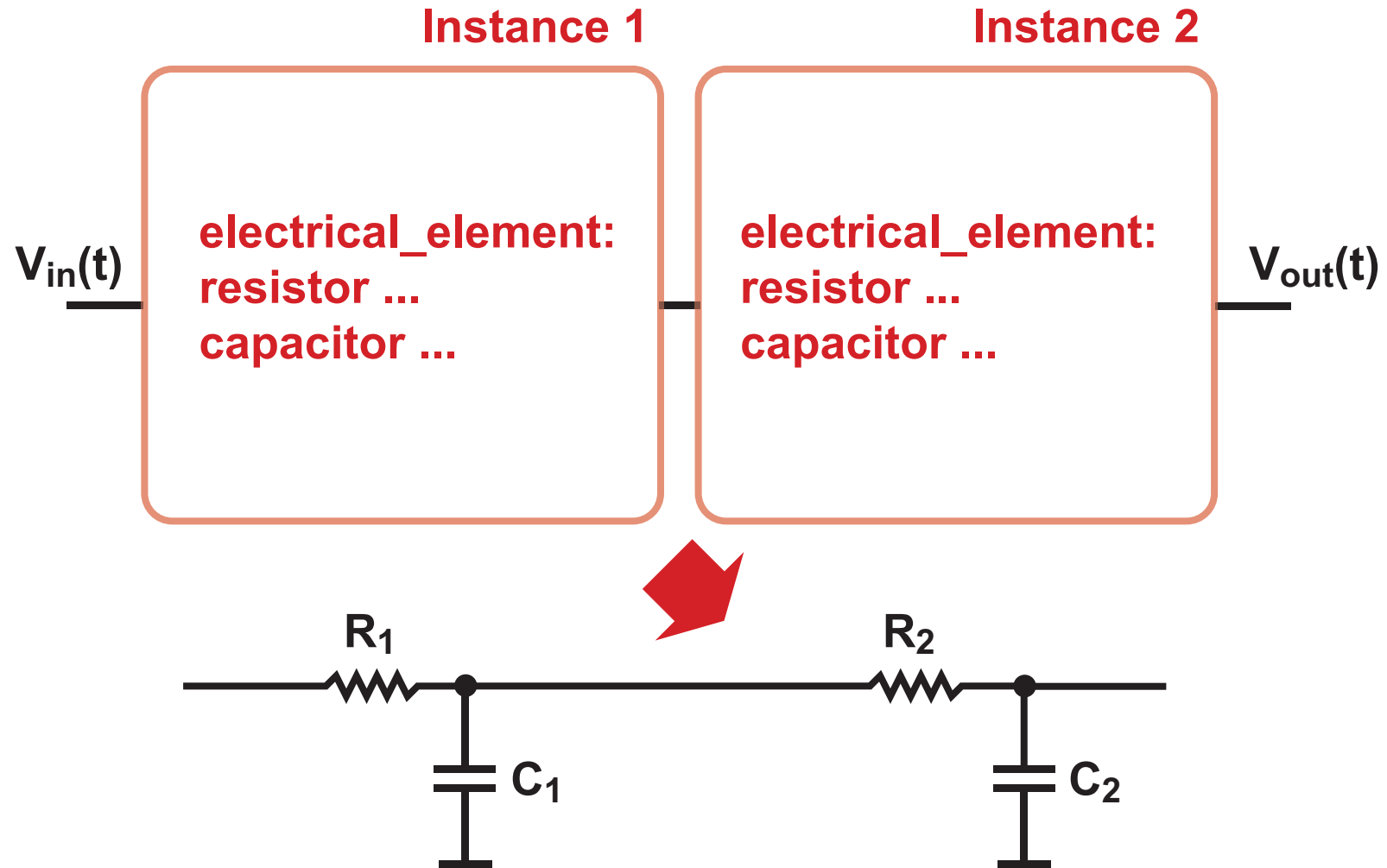
# Electrical Element Modules Form Coupled Networks



**CppSim allows one level of hierarchy for coupled networks**
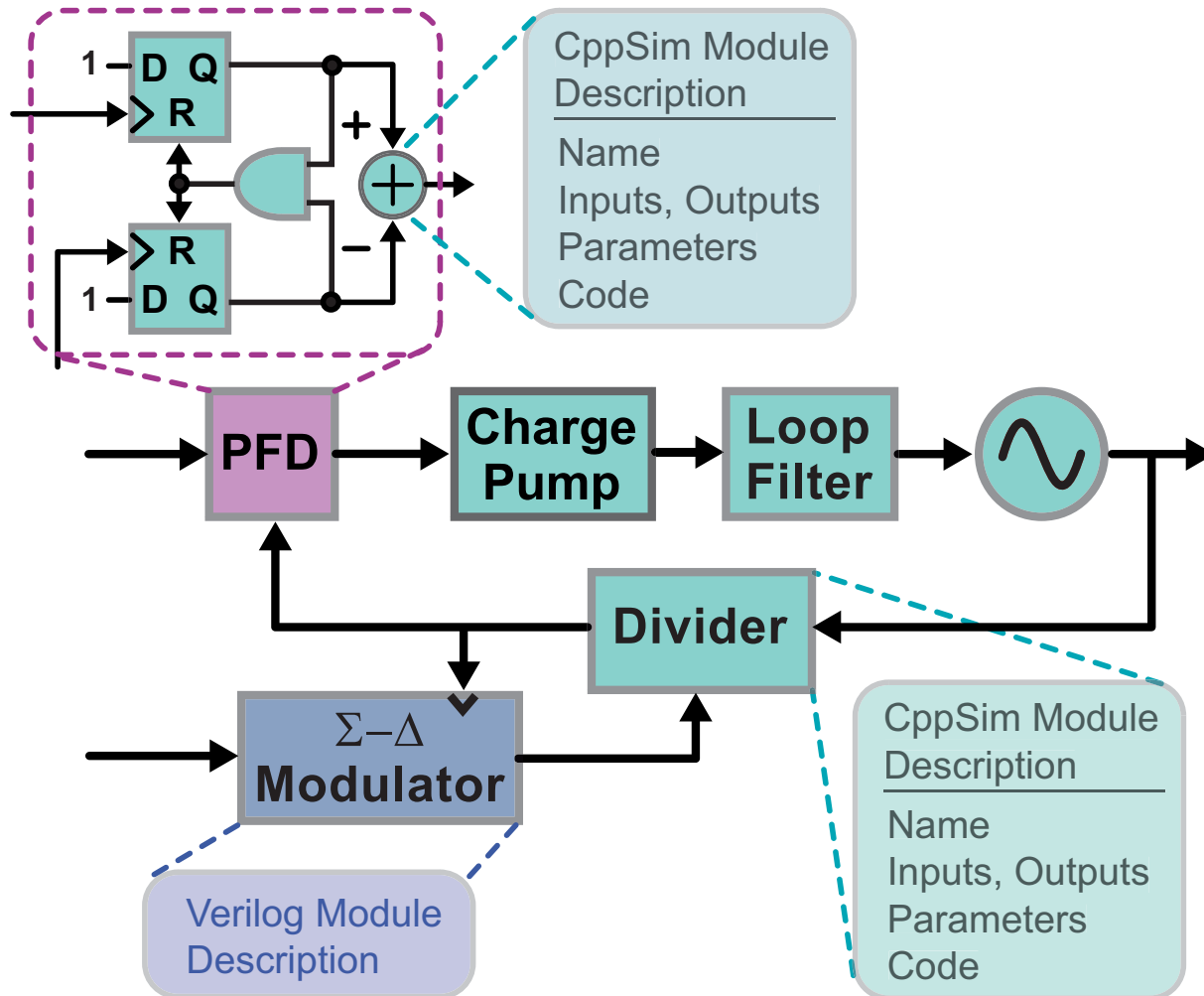
# Schematic Based Simulation using CppSim/VppSim



- **Schematic**
  - Provides hierarchical description of system topology
- **Code blocks**
  - Specify module behavior using templated C++ code or Verilog code

- **Designers graphically develop system based on a library of C++/Verilog symbols and code**
  - Easy to create new symbols with accompanying code

# *CppSim versus VppSim*

---

## ■ CppSim

- **C++ is the simulation engine**
  - Verilog code translated into C++ classes using Verilator
- **Best option when system simulation focuses on analog performance with digital support**

## ■ VppSim


- **Verilog is the simulation engine**
  - C++ blocks accessed through the Verilog PLI
- **Best option when system simulation focuses on digital verification with C++ stimulus**

**Constant time step approach allows seamless connection between C++ and Verilog models**

# VppSim Example: Embed CppSim Module in NCVerilog
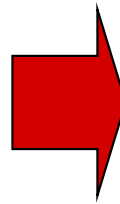
## CppSim module

```
module: leadlagfilter
parameters: double fz, double fp,
            double gain
inputs: double in
outputs: double out
static_variables:
classes: Filter filt("1+1/(2*pi*fz)s",
                    "C3*s + C3/(2*pi*fp)*s^2",
                    "C3,fz,fp,Ts",1/gain,fz,fp,Ts);
init:
code:
filt.inp(in);
out = filt.out;
```



## Resulting Verilog module

```
////// Auto-generated from CppSim module ////
module leadlagfilter(in, out);
    parameter fz = 0.00000000e+00;
    parameter fp = 0.00000000e+00;
    parameter gain = 0.00000000e+00;
    input in;
    output out;

    wreal in;
    real in_rv;
    wreal out;
    real out_rv;

    assign out = out_rv;

    initial begin
        assign in_rv = in;
    end

    always begin
        #1
        $leadlagfilter_cpp(in_rv,out_rv,fz,fp,gain);
    end
endmodule
```

# EdgeDetect() versus timing\_sensitivity: for VppSim

## EdgeDetect (simplified)

```
///// Auto-generated from CppSim module /////  
module dig_mod(a,b,clk,y,r);
```

```
    always begin  
        #1  
        $dig_mod_cpp(a,b,clk,y,r);  
    end  
endmodule
```

- **PLI routine is called every time step**
  - Dramatically slows down VppSim!

## timing\_sensitivity:


```
///// Auto-generated from CppSim module /////  
module dig_mod(a,b,clk,y,r);
```

```
    always@(posedge clk) begin  
        $dig_mod_cpp(a,b,clk,y,r);  
    end  
endmodule
```

- **PLI routine is only called on positive clk edges**
  - Much less impact on simulation speed


Use **timing\_sensitivity**: unless you need to perform computation during every time step  
(Note: no penalty for **EdgeDetect** method in CppSim)
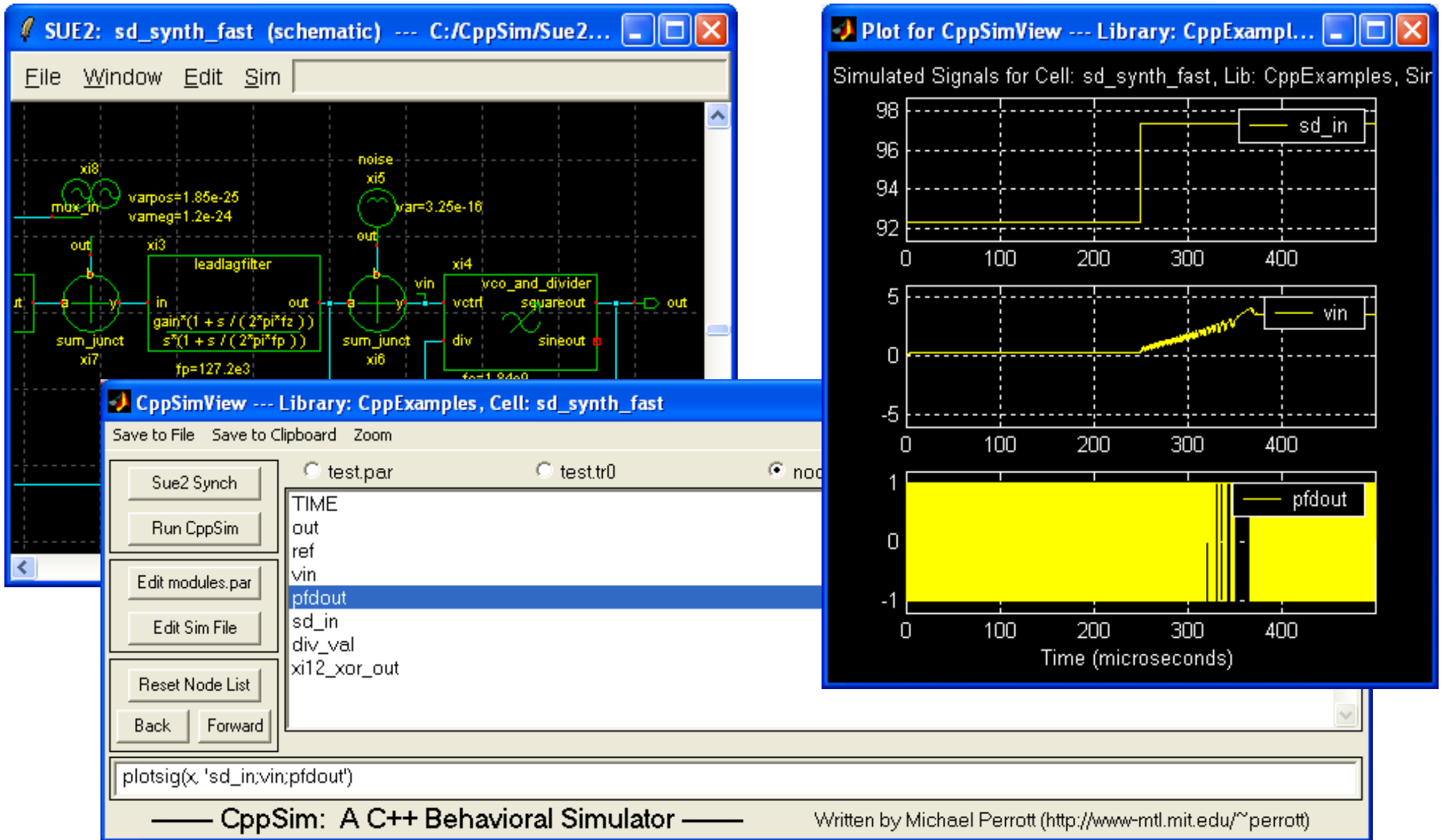
# Screenshot of CppSim/VppSim (Windows Version)



Readily Interfaces with Matlab and GTKWave
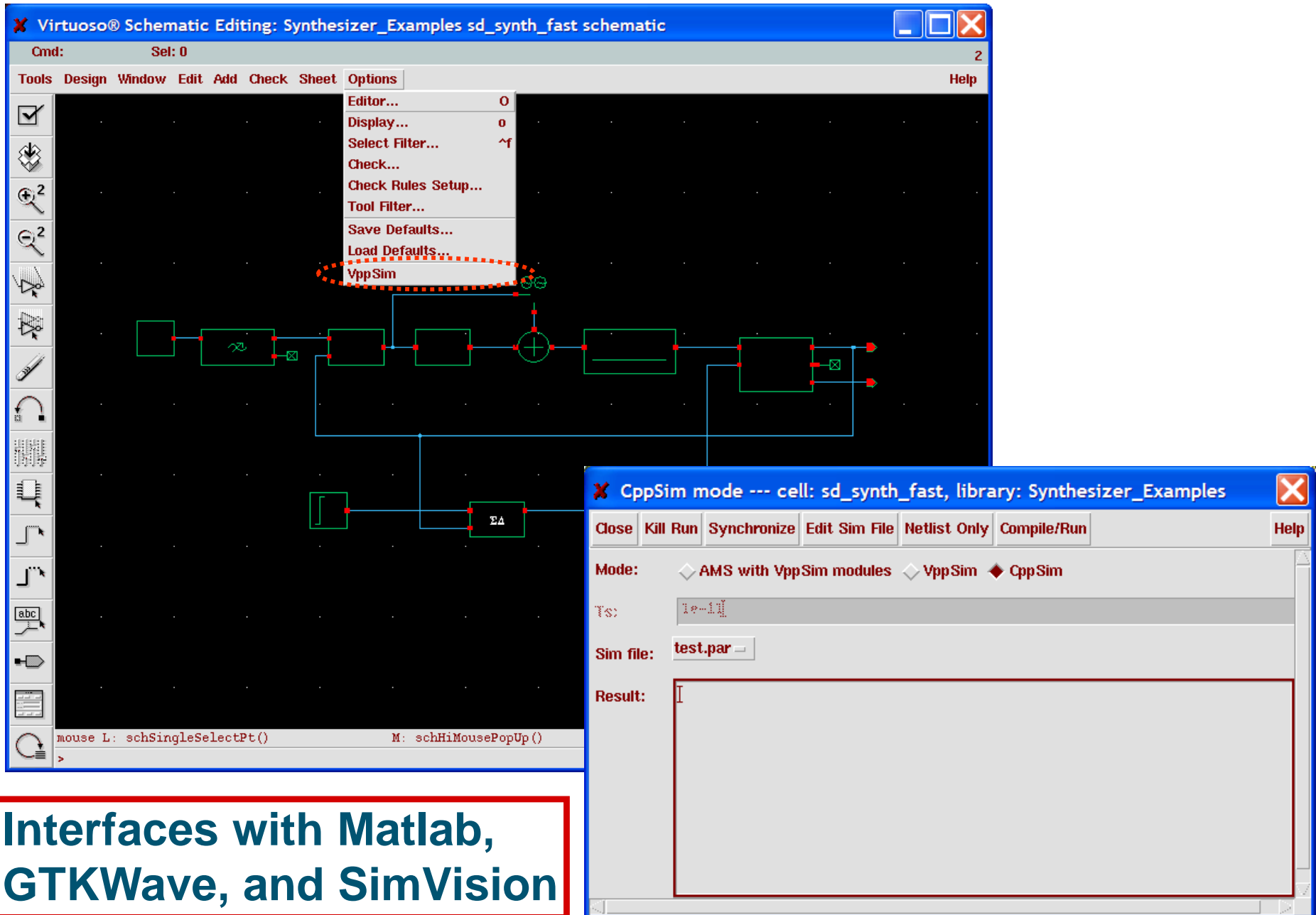
# Screenshot of CppSim/VppSim (Cadence Version)



# Free Download at [www.cppsim.com](http://www.cppsim.com)



The screenshot shows a web browser window displaying the homepage of the CppSim System Simulator. The browser's address bar shows the URL [www.cppsim.com](http://www.cppsim.com). The website features a navigation menu with links for Home, Download, About, Manuals, Tutorials, Publications, and Lectures. A central banner with a blue background and glowing circuit lines contains the text: "Discover a faster and easier way to perform system level simulation of complex mixed-signal circuits." Below the banner are six circular icons representing the website's main sections: Download, About, Manuals, Tutorials, Publications, and Lectures. A testimonial box on the left contains a quote about the challenges of designing precision timing circuits. The main content area highlights that CppSim automatically generates, compiles, and runs C++ code corresponding to the schematic design. Three key features are listed: Graphical Interface, Analog modules, and Digital modules, each with a brief description.

CppSim System Simulator

Home Download About Manuals Tutorials Publications Lectures

Discover a faster and easier way to perform system level simulation of complex mixed-signal circuits.

Download About Manuals Tutorials Publications Lectures

*"Designing precision timing circuits that exhibit grossly non-linear behavior requires performing accurate simulations in the time domain. Such simulations take prohibitively long, even in commercial behavioral simulators, which have often limited our ability to evaluate new PLL, CDR, and ADC architectures in the past. CppSim and its Cadence compatibility have filled this void and have been instrumental in the design of*

**CppSim automatically generates, compiles, and runs C++ code corresponding to the schematic design that you create.**

- Graphical Interface:** Systems are specified and simulated within a schematic editor, Sue2, and results are viewed using a waveform viewer (CppSimView or GTKWave).
- Analog modules:** A simple text template for each module is filled in by the user which can make use of a rich set of C++ classes to represent common functions such as filtering, noise, etc.
- Digital modules:** CppSim utilizes Verilator to automatically create C++ code corresponding to your Verilog modules, and seamlessly integrates this code into your system simulation.



## *Many Tutorials Available for CppSim/VppSim*

---


- **Wideband Digital fractional-N frequency synthesizer**
- **VCO-based Analog-to-Digital Convertor**
- **GMSK modulator**
- **Decision Feedback Equalization**
- **Optical-Electrical Downversion and Digitization**
- **OFDM Transceiver**
- **C++/Verilog Co-Simulation**

 **See <http://www.cppsim.com>**
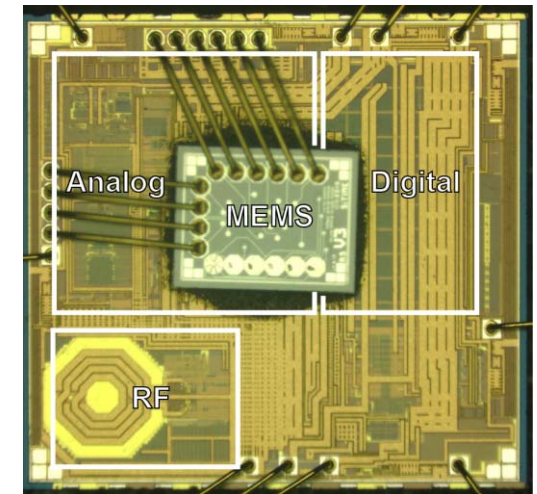
# Example Benchmarks for a Full Chip Simulation

Tabulated simulation times for a MEMS-based oscillator:

- **SPICE-level** model
  - Checking of floating gate, over-voltage, startup of bandgap and regulators, etc.
    - Spectre Turbo: 2 microseconds/day
    - BDA: **8 microseconds/day**
- **Architectural** model using CppSim
  - Examination of noise and analog dynamics
    - **2.8 milliseconds/hour**
- **Verification** model using VppSim
  - Validation of digital functionality in the context of analog control and hybrid digital/analog systems
    - **7 milliseconds/minute**



# Conclusion

---

- **CppSim is designed for high productivity and versatility**
  - **Easy to create your own code blocks**
    - Use existing modules to see examples, but don't limit yourself to what is available
  - **Allows very detailed modeling of complex circuits**
    - You are not confined to an overly simplified model
  - **Invites a scripted approach to running simulations**
    - Excellent integration with Matlab/Octave
  - **Runs in Windows, Mac OS X, or within Cadence**
    - Has been used to simulate entire ICs in Cadence
- **Extensive 10 year track record of enabling new circuit architectures with first chip success**