

***High Performance Digital
Fractional-N Frequency Synthesizers***

***IEEE Distinguished Lecture
Lehigh Valley SSSS Chapter***

Michael H. Perrott

October 2013

Copyright © 2013 by Michael H. Perrott

All rights reserved.


Why Are Digital Phase-Locked Loops Interesting?

- **PLLs are needed for a wide range of applications**
 - Communication systems, digital processors, ...
- **Performance is important**
 - Phase noise/jitter is often a limiting factor
- **Standard analog PLL implementations present issues**
 - Analog blocks pose design and verification challenges
 - The cost of implementation is becoming too high ...

Can digital phase-locked loops offer excellent performance with a lower cost of implementation?


Just Enough PLL Background ...

What is a Phase-Locked Loop (PLL)?

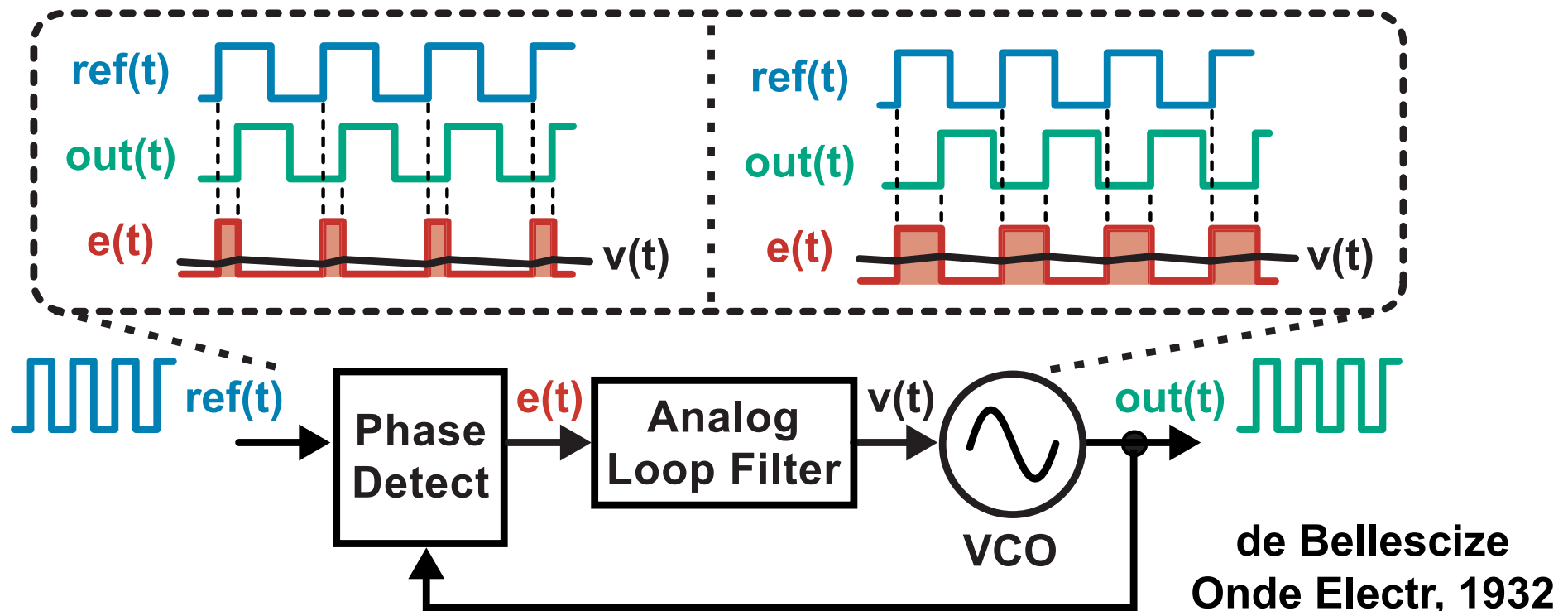

- Voltage Controlled Oscillator (VCO) efficiently provides oscillating waveform with variable frequency
- PLL synchronizes VCO frequency to input reference frequency through feedback
 - Key block is phase detector
 - Realized as *digital gates* that create pulsed signals


Integer-N Frequency Synthesizers

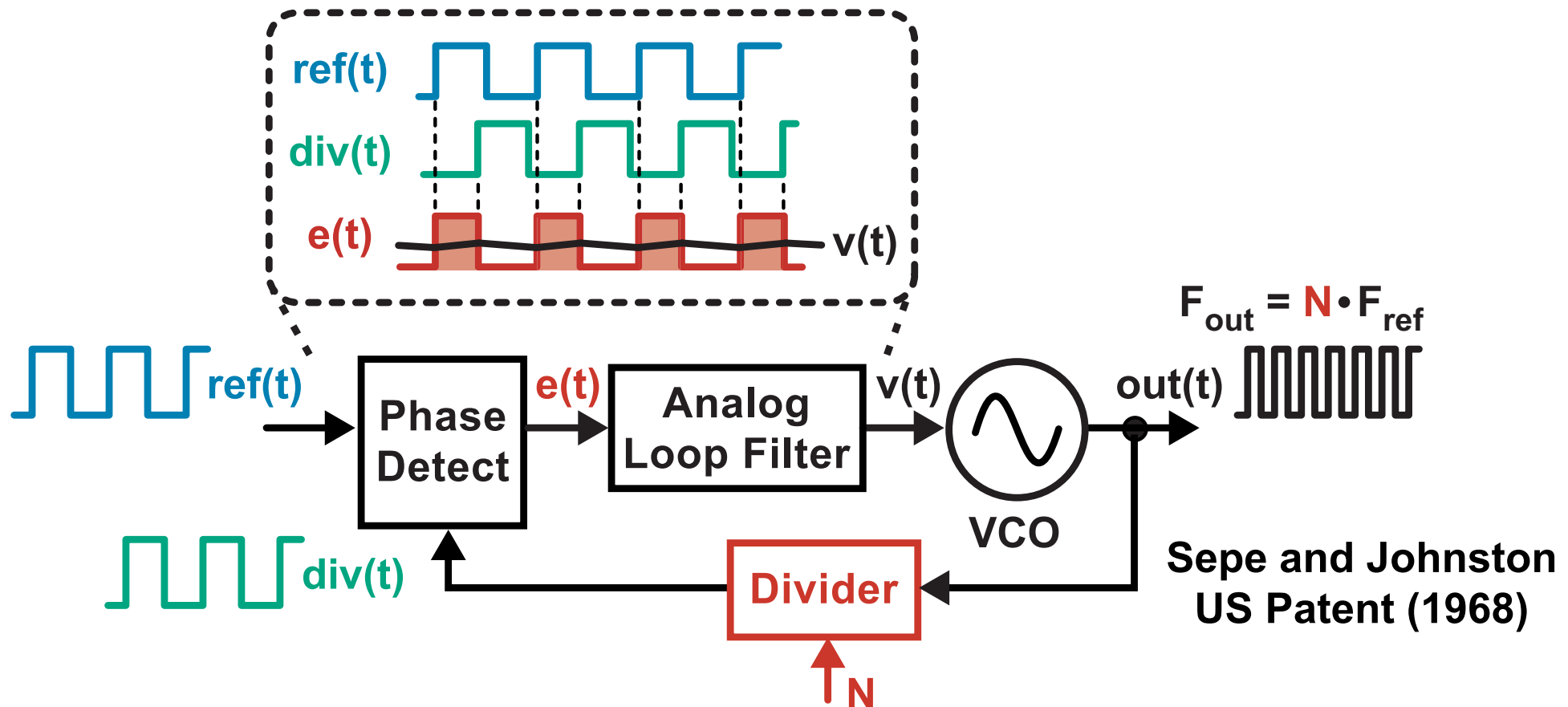

- Use digital counter structure to divide VCO frequency
 - Constraint: must divide by integer values
- Use PLL to synchronize reference and divider output

Output frequency is digitally controlled


Fractional-N Frequency Synthesizers

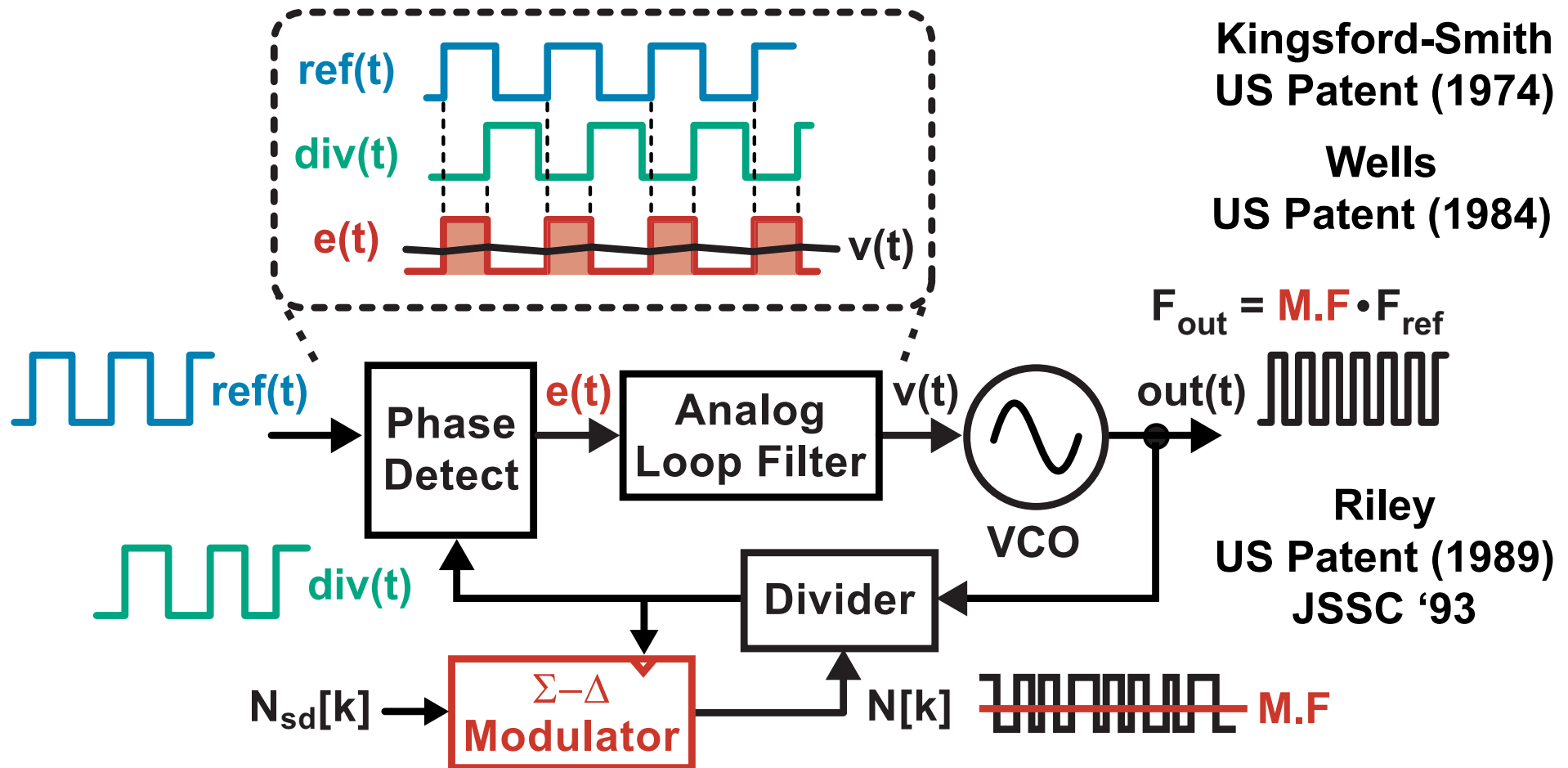


- Dither divide value to achieve fractional divide values
 - PLL loop filter smooths the resulting variations

Very high frequency resolution is achieved

The Issue of Quantization Noise

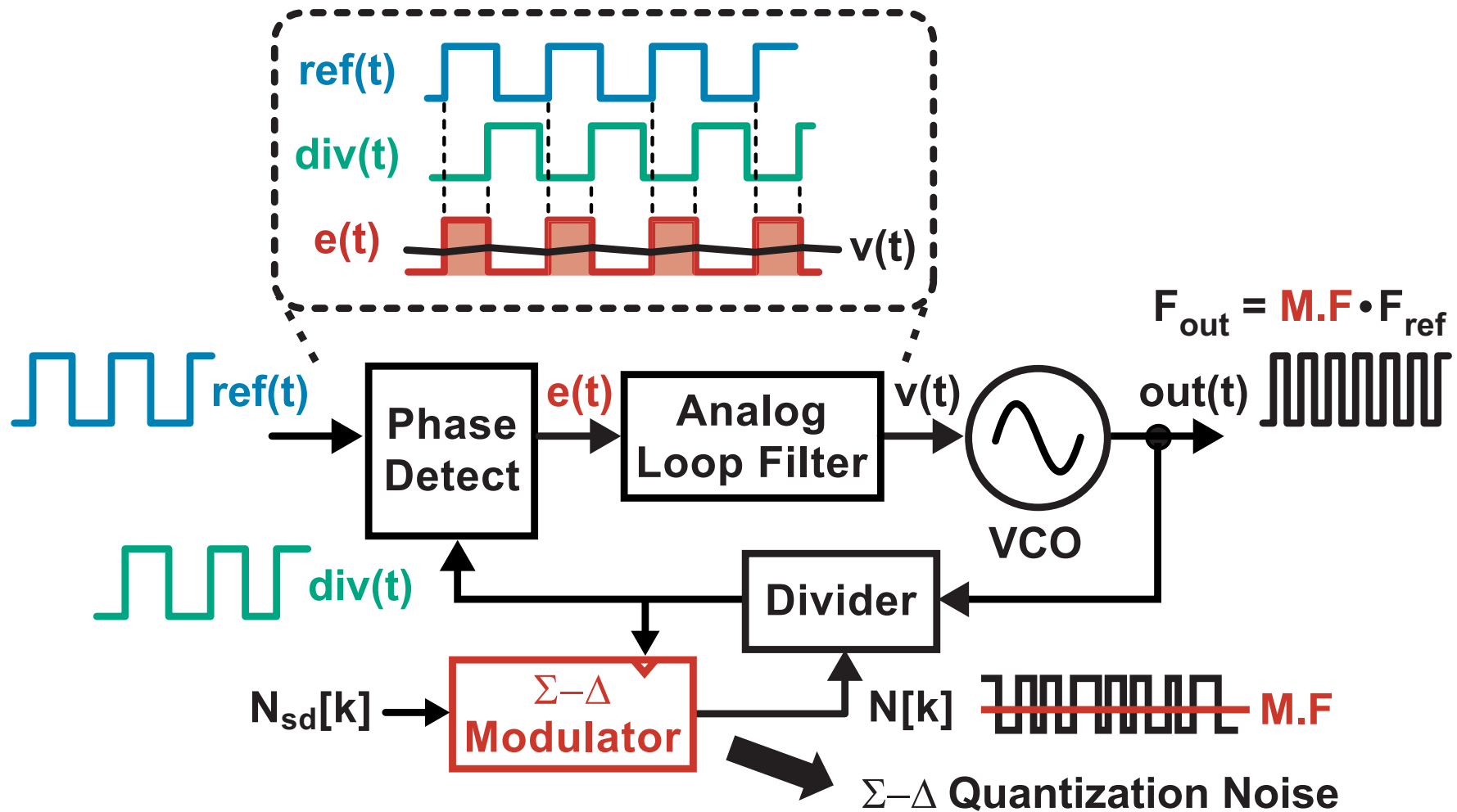


 - Limits PLL bandwidth
- Increases linearity requirements of phase detector





Striving for a Better PLL Implementation

Analog Phase Detection

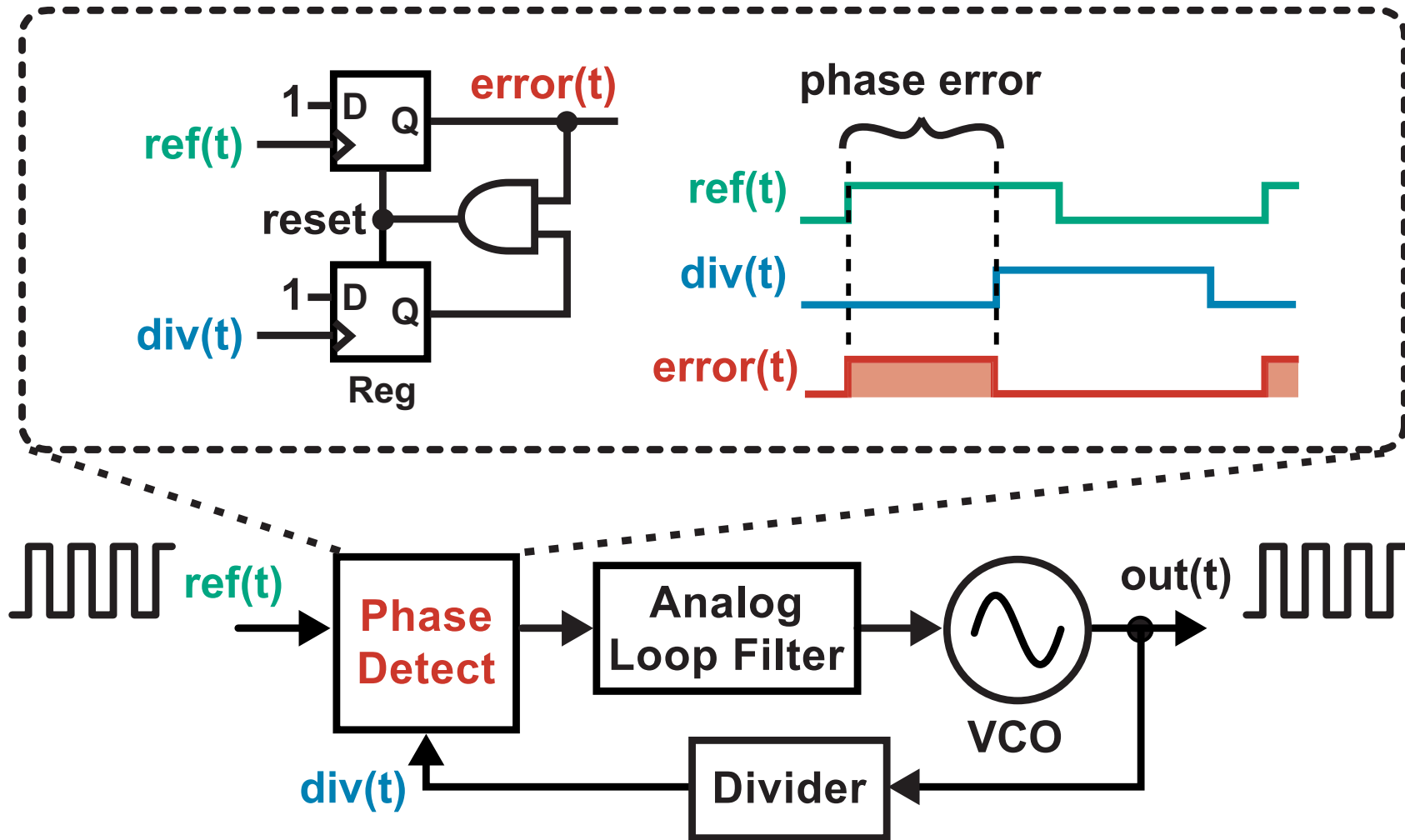


- Pulse width is formed according to phase difference between two signals
- Average of pulsed waveform is applied to VCO input

Tradeoffs of Analog Approach

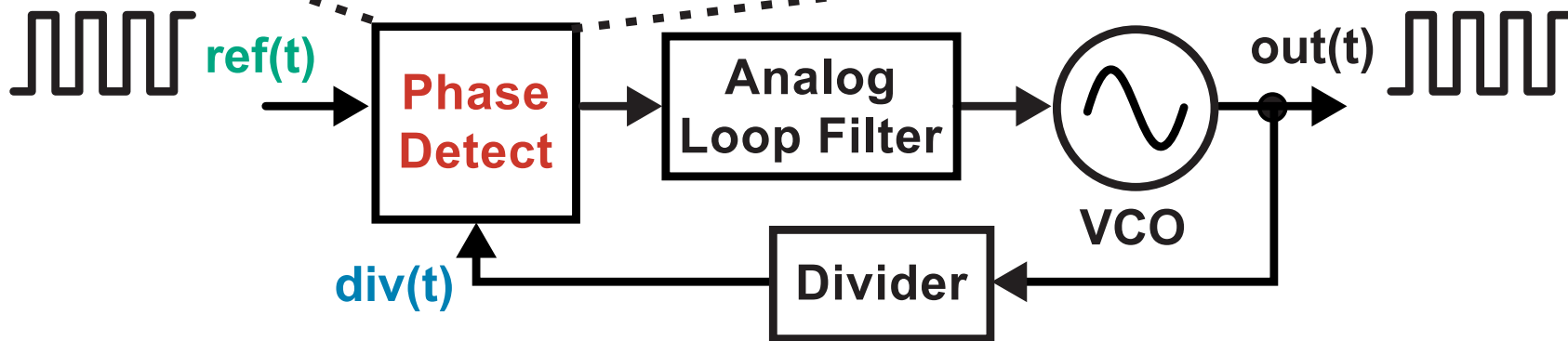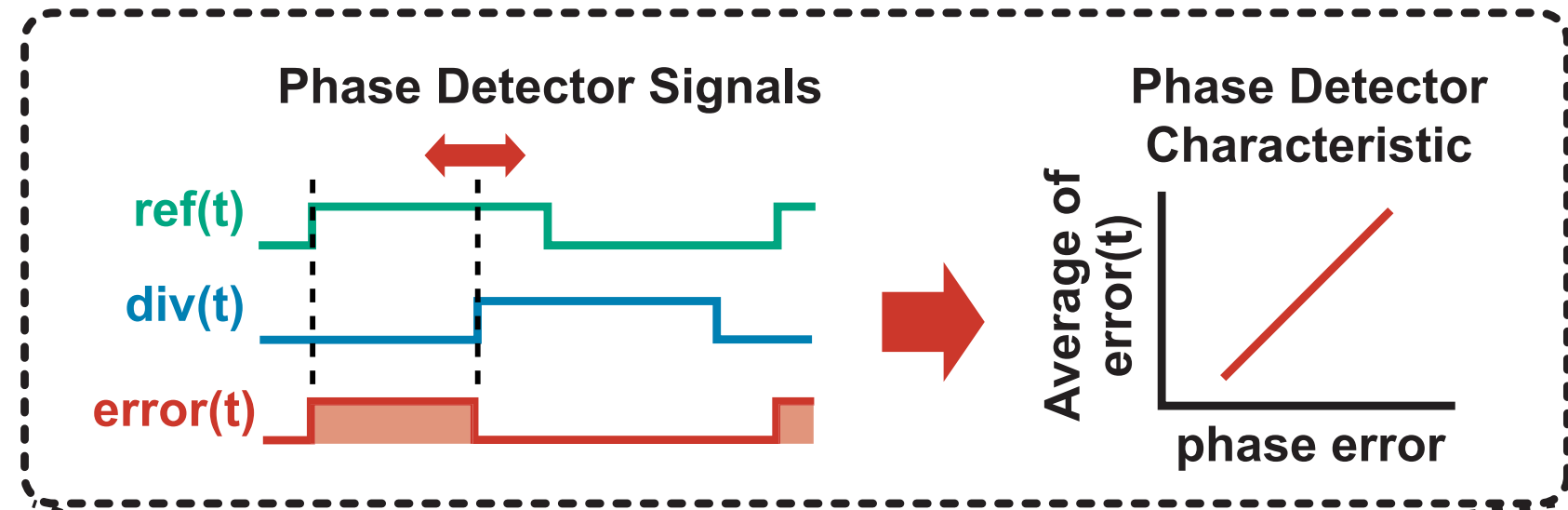



- **Benefit:** average of pulsed output is a continuous, linear function of phase error
- **Issue:** analog loop filter implementation is undesirable

Issues with Analog Loop Filter

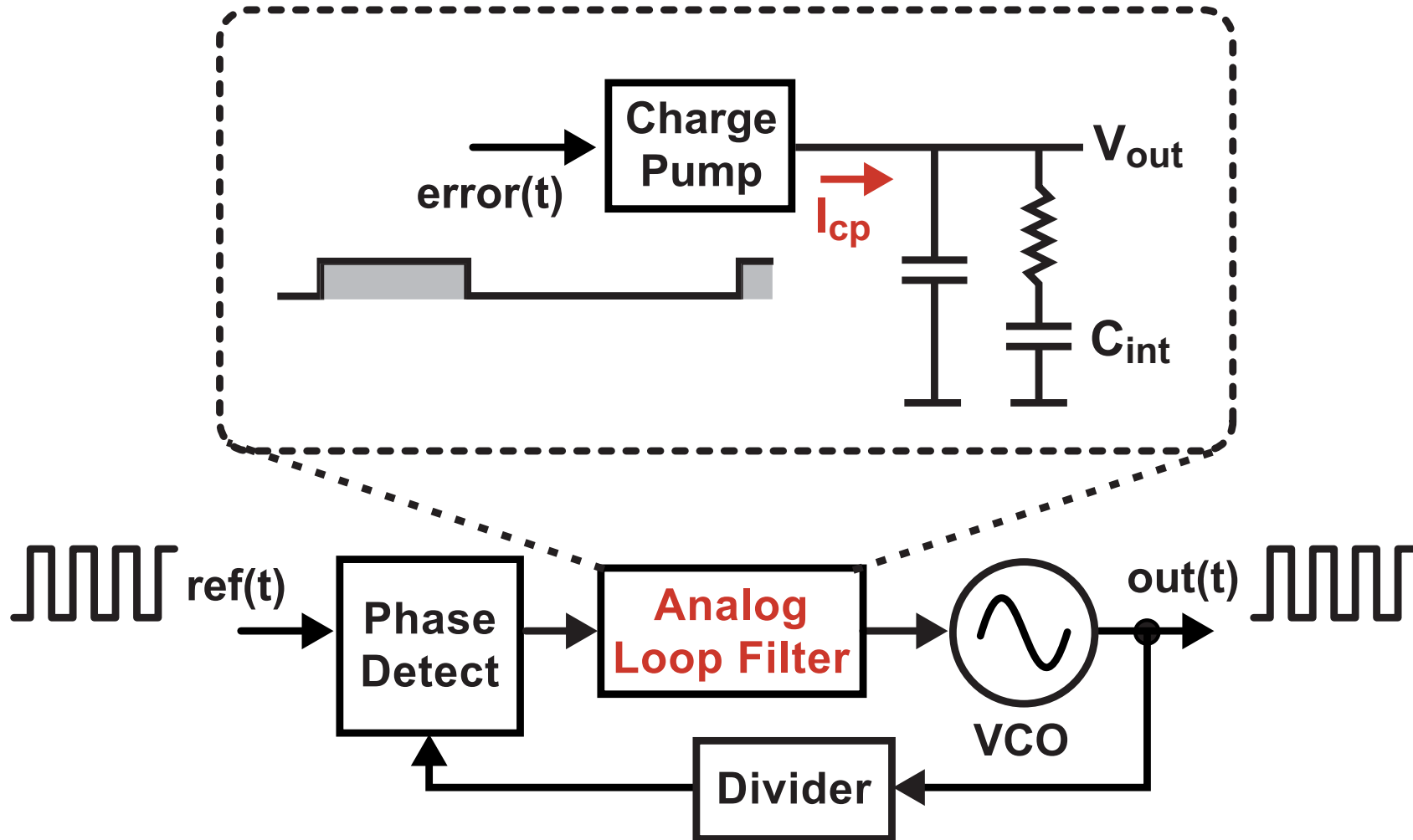

- Charge pump: output resistance, mismatch
- Filter caps: leakage current, *large area*

Going Digital ...

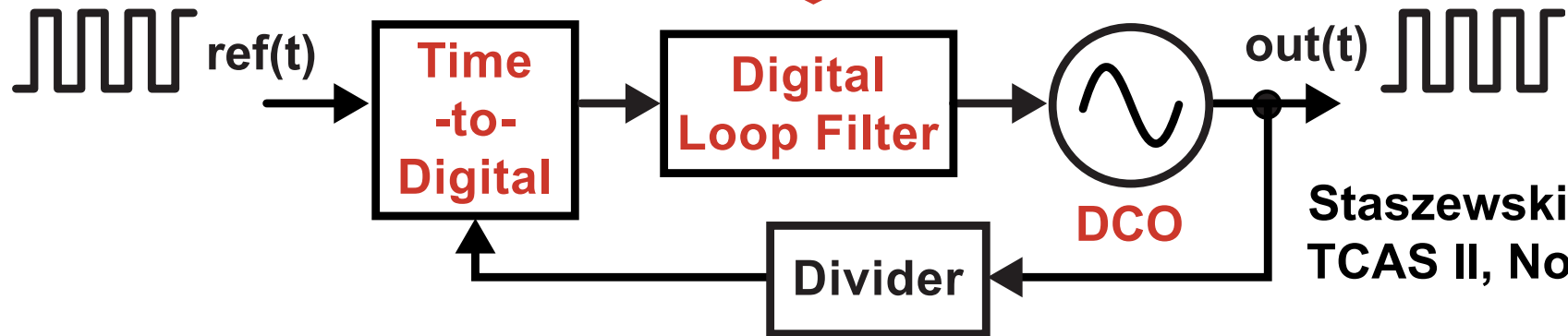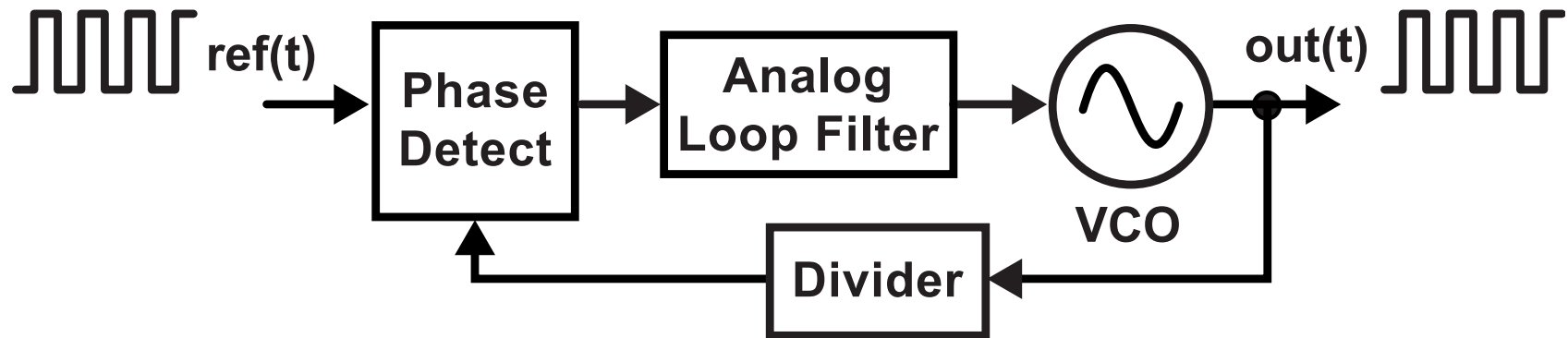


Staszewski et. al.,
TCAS II, Nov 2003

- Digital loop filter: compact area, insensitive to leakage
- Challenges:
 - Time-to-Digital Converter (TDC)
 - Digitally-Controlled Oscillator (DCO)

Outline of Talk


- **Basics**
 - Time-to-Digital Converters (TDCs)
 - Digitally-Controlled Oscillators (DCOs)
- **Modeling**
 - Transfer function modeling
 - Noise analysis
- **Improving the TDC**
 - Background
 - Gated-Ring Oscillator (GRO) structure
- **A high performance digital PLL example**
 - GRO TDC for low noise
 - Quantization noise cancellation
 - Low jitter divider design

Classical Time-to-Digital Converter

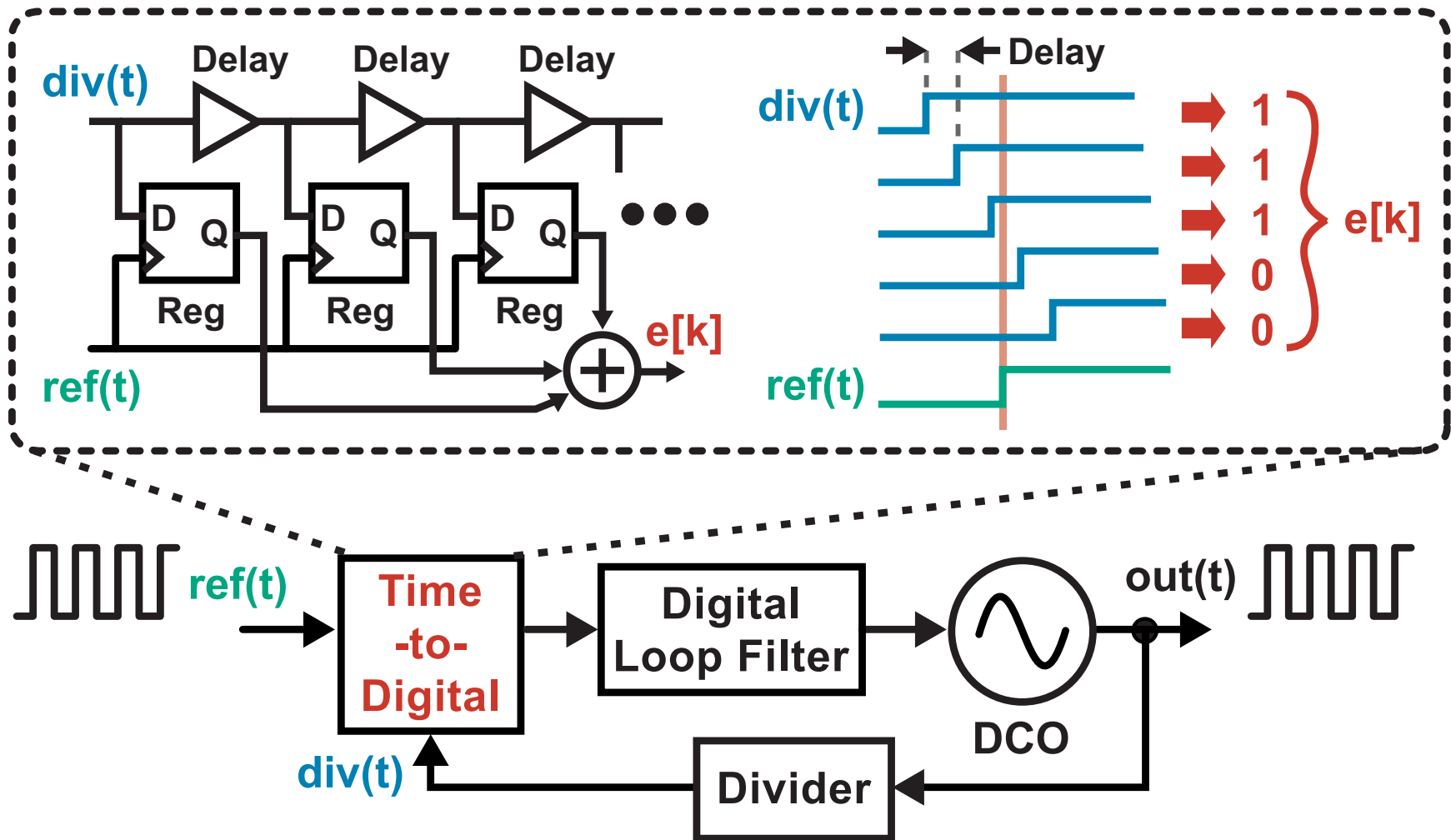



- Resolution set by a “Single Delay Chain” structure
 - Phase error is measured with delays and registers
- Corresponds to a flash architecture

Modeling of TDC

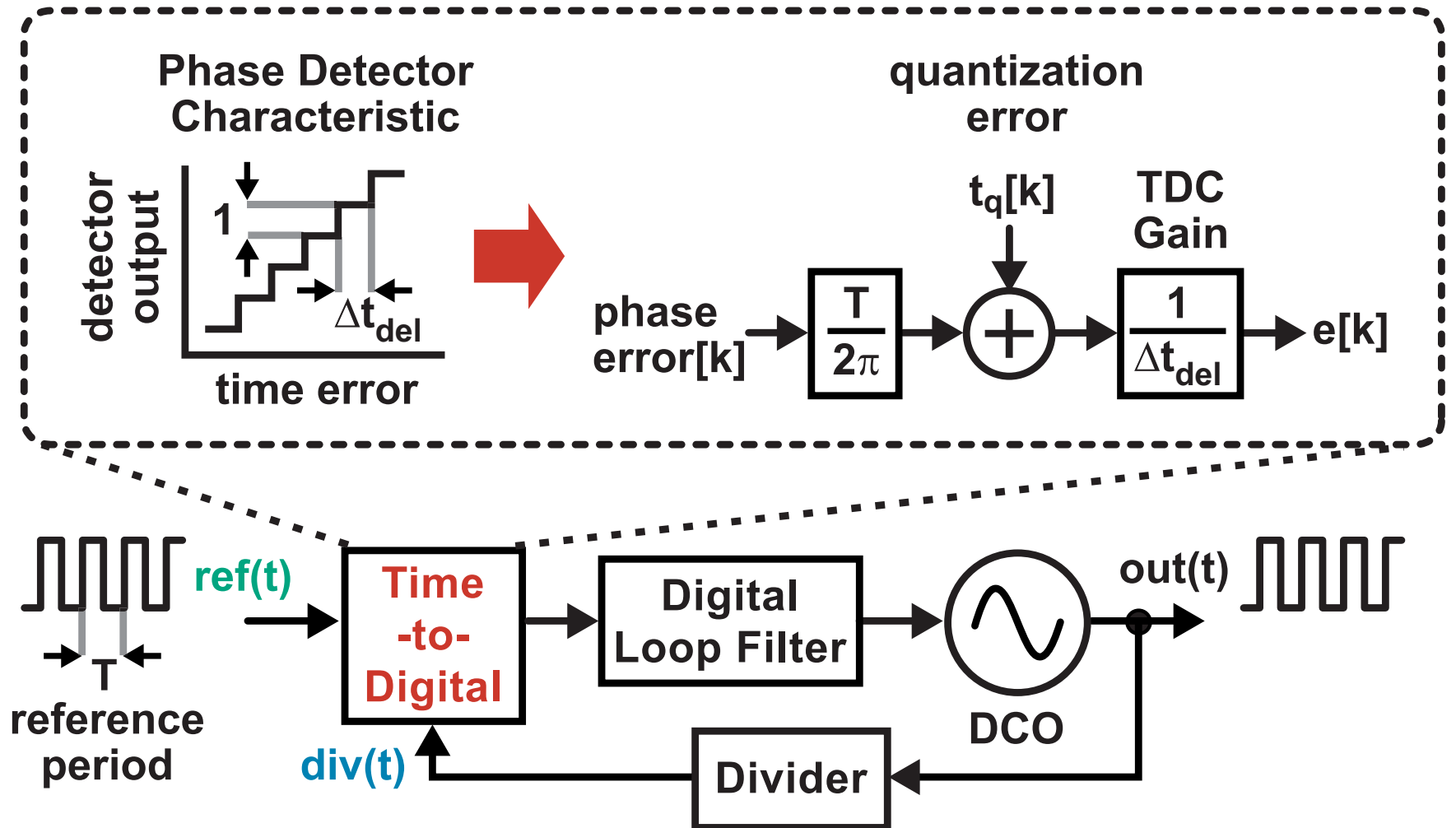



- Phase error converted to time error by scale factor: $T/2\pi$
- TDC introduces quantization error: $t_q[k]$
- TDC gain set by average delay per step: Δt_{del}

 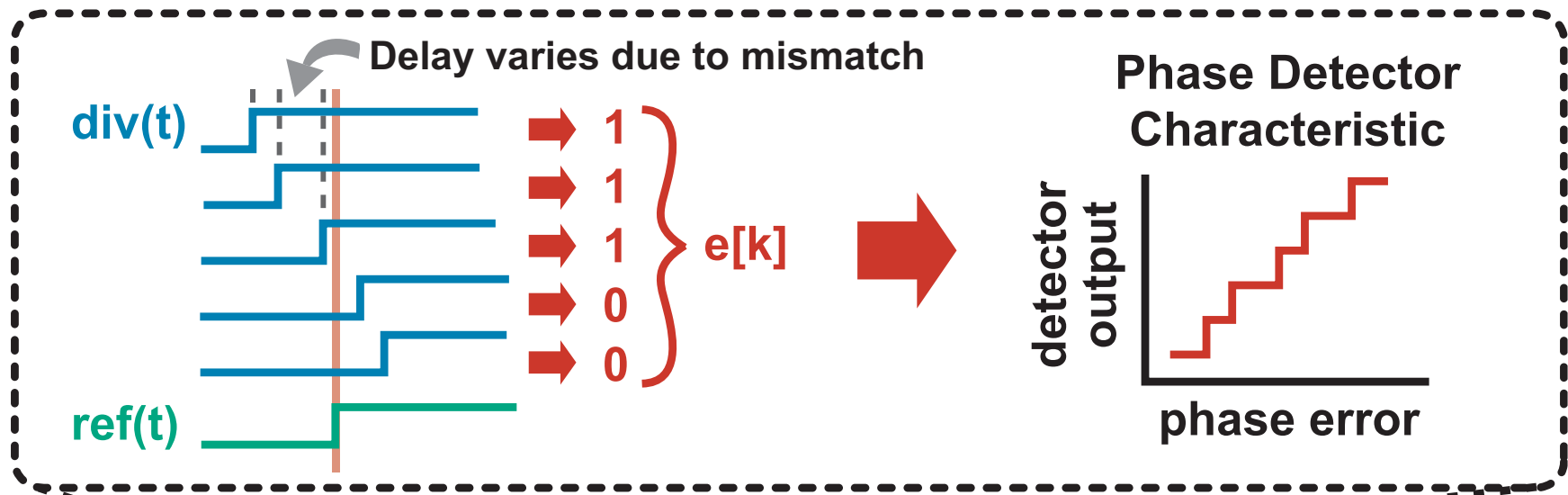Impact of Limited Resolution and Delay Mismatch





- Integer-N PLL
 - Limit cycles due to limited resolution (unless high ref noise)
- Fractional-N PLL
 - Fractional spurs due to non-linearity from delay mismatch

  A Straightforward Approach for Achieving a DCO



- Use a DAC to control a conventional LC oscillator
 - Allows the use of an existing VCO within a digital PLL
 - Can be applied across a broad range of IC processes


A Much More Digital Implementation

  

Staszewski et. al.,
TCAS II, Nov 2003


- Adjust frequency in an LC oscillator by switching in a variable number of small capacitors
 - Most effective for CMOS processes of 0.13u and below

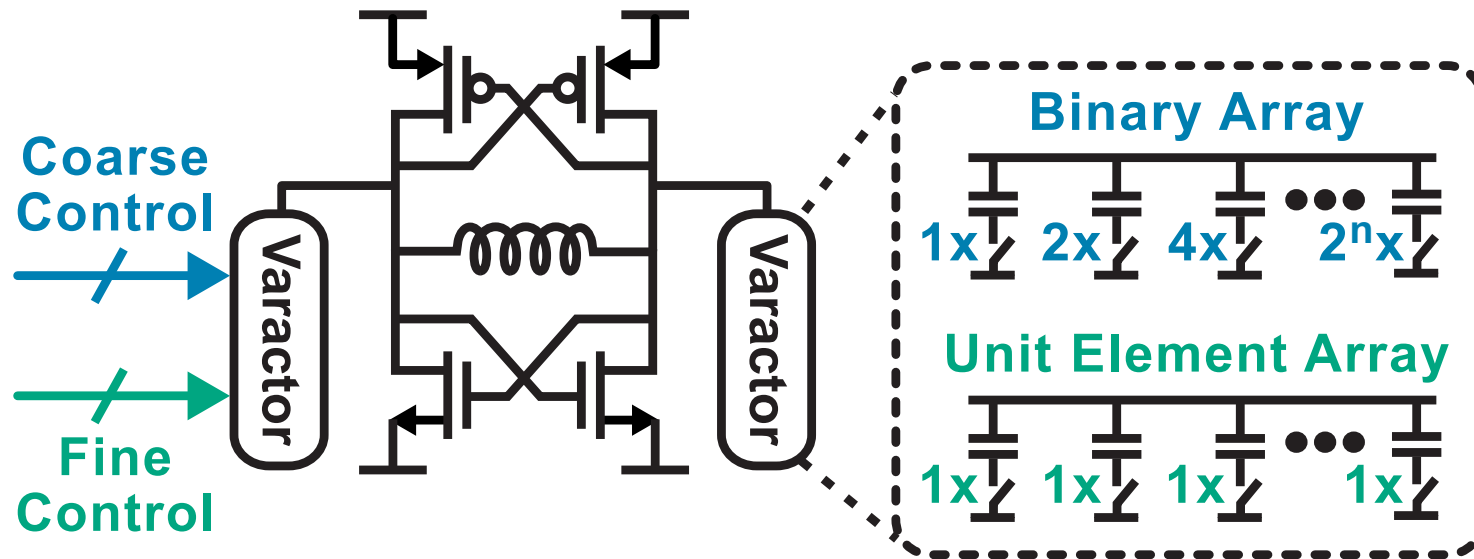Leveraging Segmentation in Switched Capacitor DCO



- **Similar tradeoffs as *segmented* capacitor DAC structures**
 - Binary array: efficient control, but may lack monotonicity
 - Unit element array: monotonic, but complex control
- **Coarse and fine control segmentation of DCO**
 - **Coarse control: active only during initial frequency tuning**
 - Binary array provides efficient control implementation
 - **Fine control: controlled by PLL feedback**
 - Unit element array minimizes dynamic charge transfer

Noise Spectrum of a Switched Cap DCO

 


- **Phase noise**

- Same as for conventional VCO (tank Q, etc.)


- **Quantization noise from dithering**

- Designed to be lower than phase noise

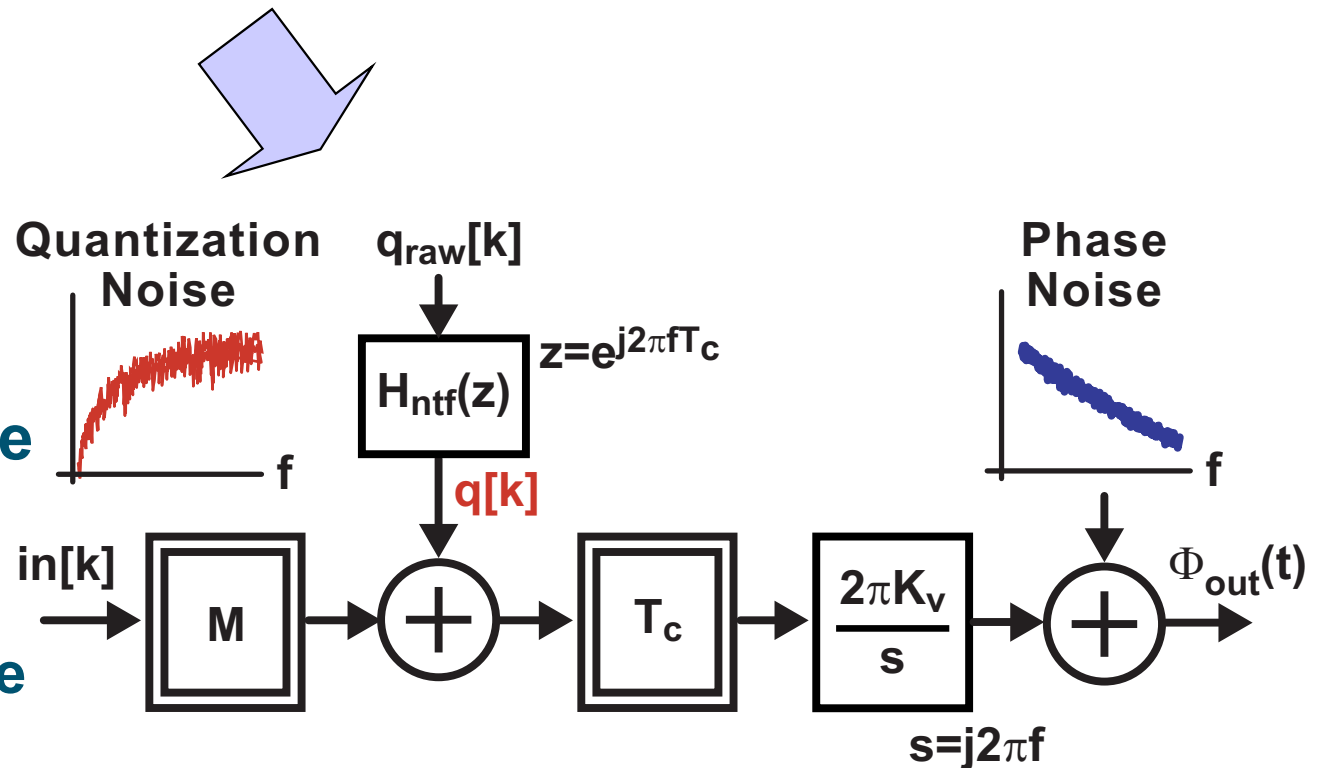


Modeling

Overall Digital PLL Model

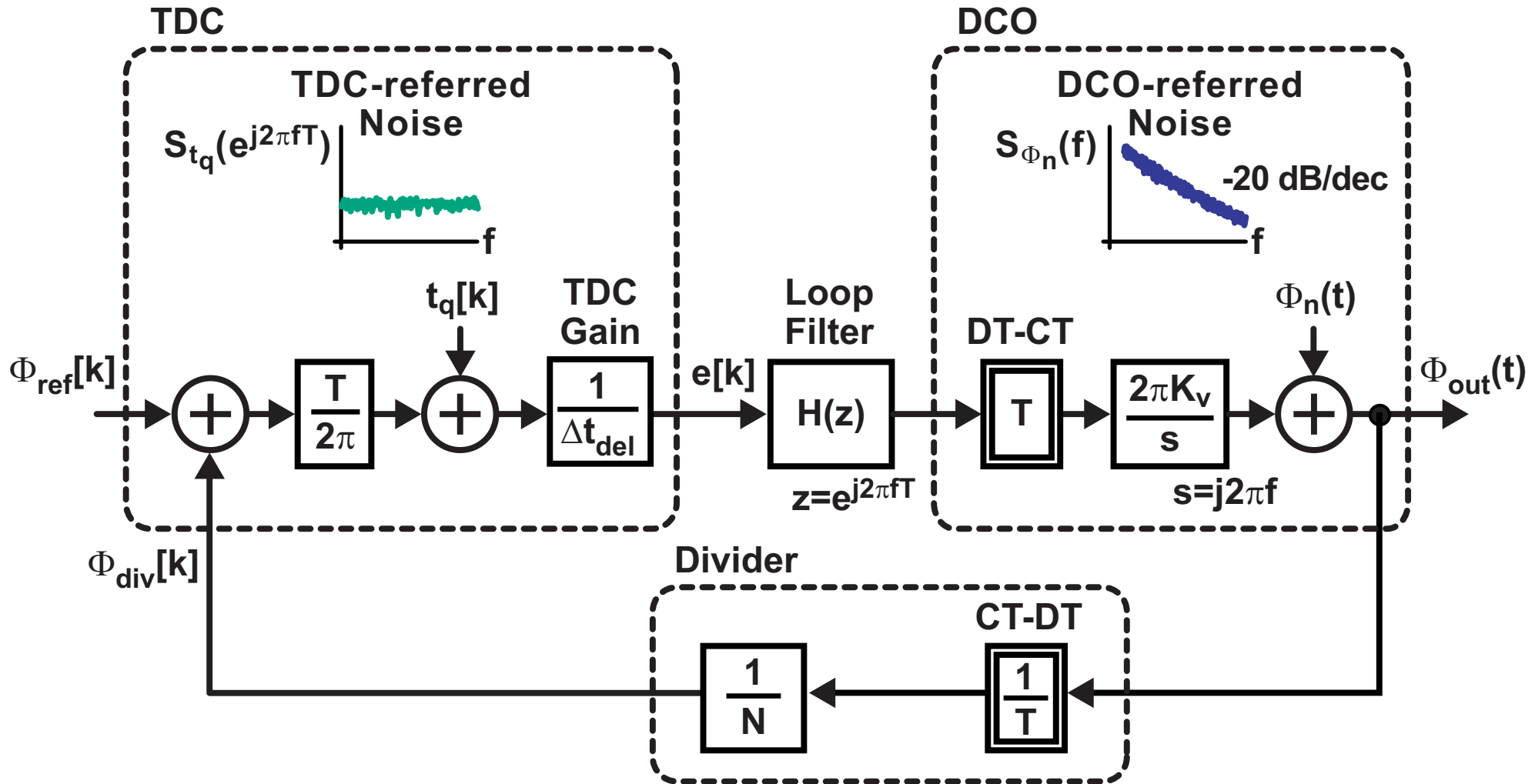

- TDC and DCO-referred noise influence overall phase noise according to associated transfer functions to output
- Calculations involve both discrete *and* continuous time

Key Transfer Functions

 


- **TDC-referred noise**

$$\frac{\Phi_{out}}{t_q} = \frac{(1/\Delta t_{del})H(e^{j2\pi fT})T2\pi K_v/(2\pi jf)}{1 + (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)}$$

- **DCO-referred noise**

$$\frac{\Phi_{out}}{\Phi_n} = \frac{1}{1 + (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)}$$

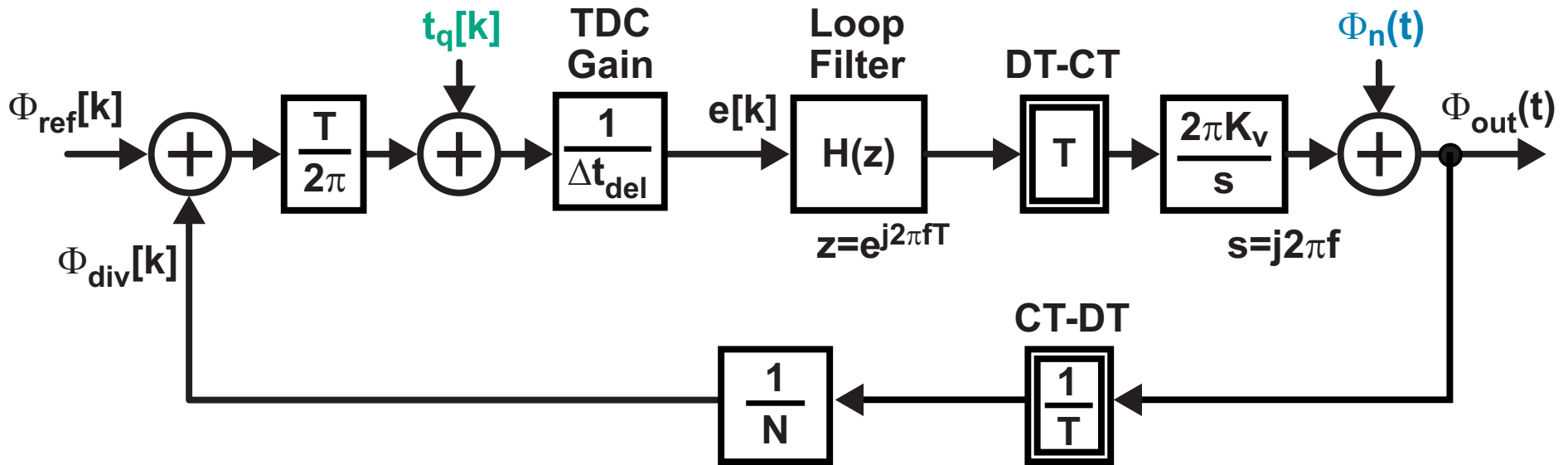Utilize $G(f)$ as a Parameterizing Function



- Define open loop transfer function $A(f)$ as:

$$A(f) = (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)$$

- Define closed loop parameterizing function $G(f)$ as:

$$G(f) = \frac{A(f)}{1 + A(f)}$$

- Note: $G(f)$ is a lowpass filter with DC gain = 1

Transfer Function Parameterization Calculations


- **TDC-referred noise**

$$\begin{aligned}\frac{\Phi_{out}}{t_q} &= \frac{(1/\Delta t_{del})H(e^{j2\pi fT})T2\pi K_v/(2\pi jf)}{1 + (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)} \\ &= \frac{2\pi NA(f)}{1 + A(f)} = \boxed{2\pi NG(f)}\end{aligned}$$

- **DCO-referred noise**

$$\begin{aligned}\frac{\Phi_{out}}{\Phi_n} &= \frac{1}{1 + (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)} \\ &= \frac{1}{1 + A(f)} = \frac{1 + A(f) - A(f)}{1 + A(f)} = \boxed{1 - G(f)}\end{aligned}$$

Key Observations

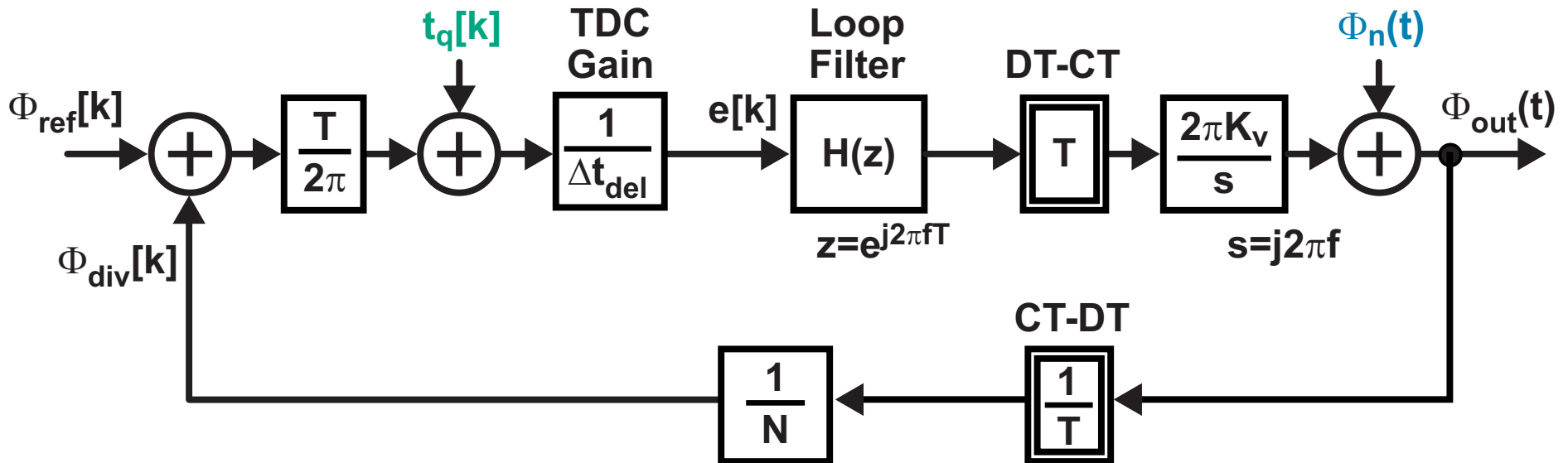

- **TDC-referred noise**

$$\frac{\Phi_{out}}{t_q} = 2\pi N G(f)$$

Lowpass with a DC gain of $2\pi N$


- **DCO-referred noise**

$$\frac{\Phi_{out}}{\Phi_n} = 1 - G(f)$$

Highpass with a high frequency gain of 1

How do we calculate the output phase noise?

Phase Noise Calculation

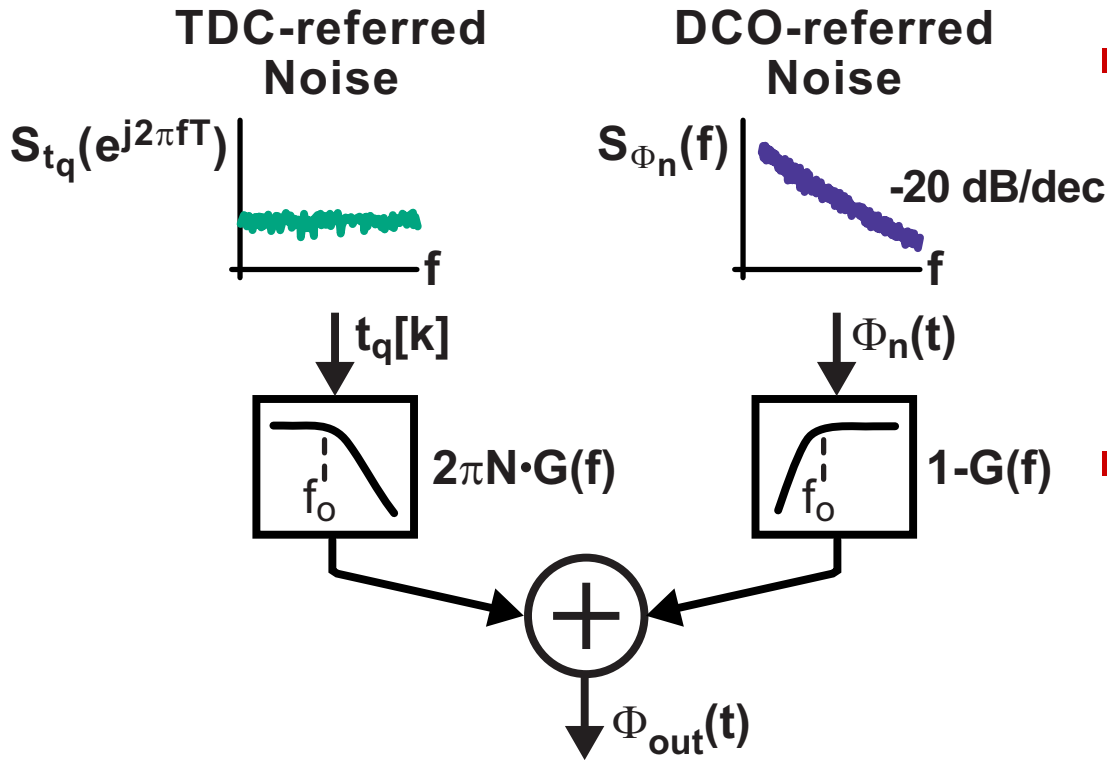


■ TDC noise


- Dominates PLL phase noise at low frequency offsets

■ DCO noise

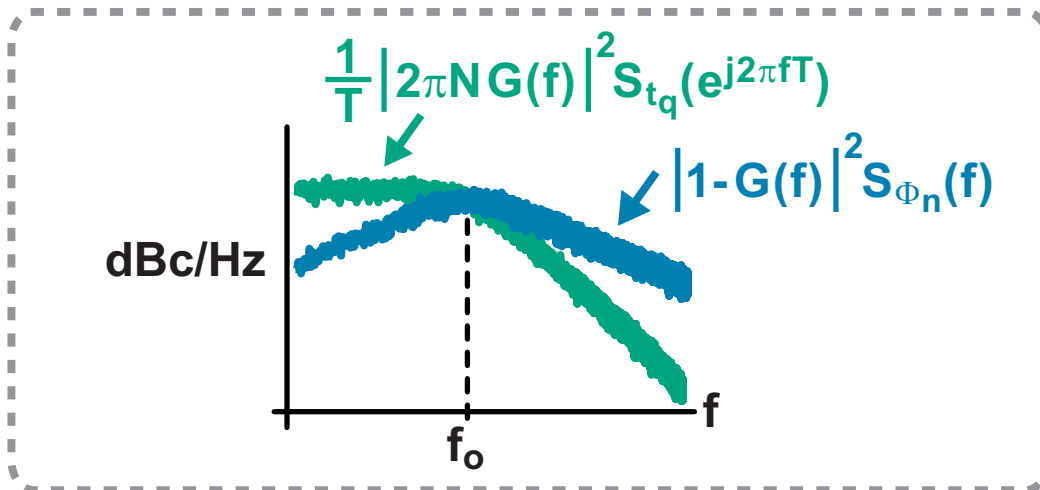- Dominates PLL phase noise at high frequency offsets



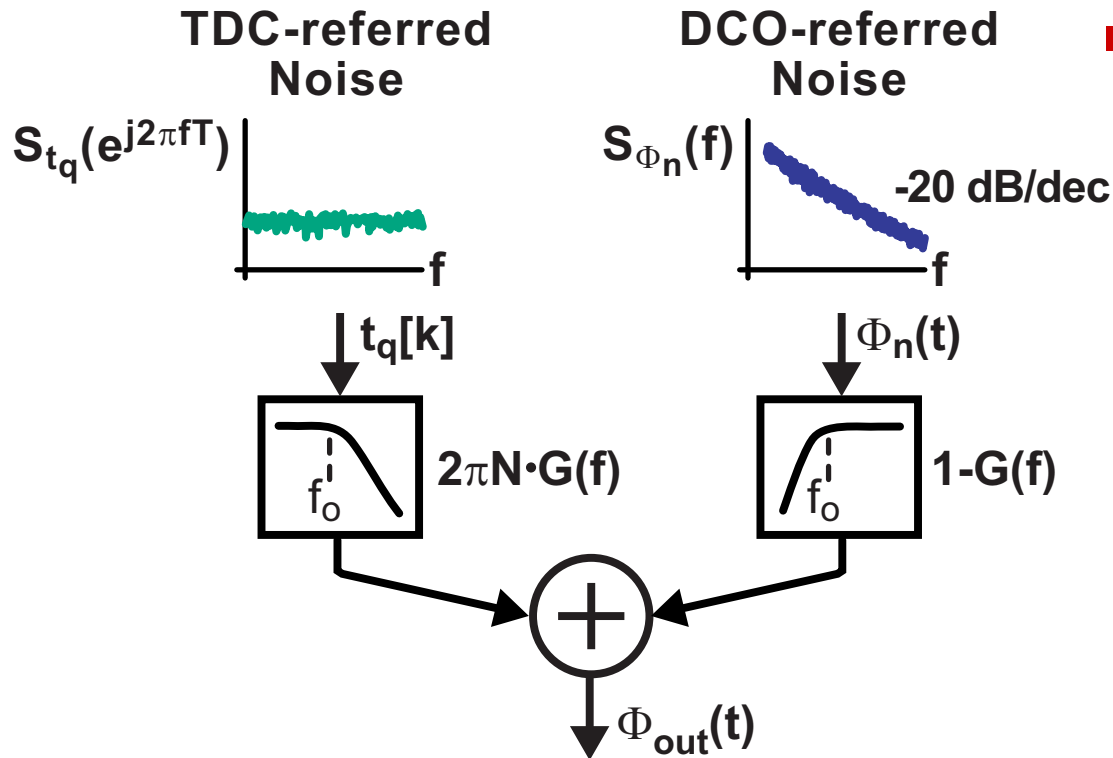
A Closer Look at the Influence of TDC Noise



- PLL bandwidth dramatically influences relative impact of TDC and VCO noise

Want high PLL bandwidth?

➔ Need low TDC Noise




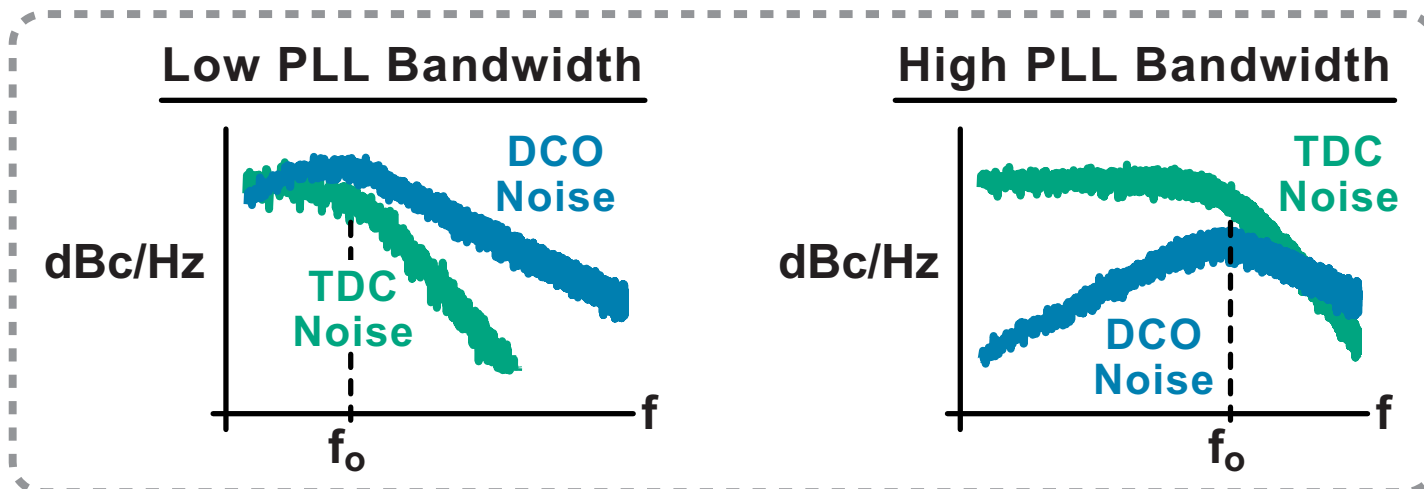


How Do We Improve TDC Performance?

Two Key Issues:

- **TDC resolution**
- **Mismatch**

 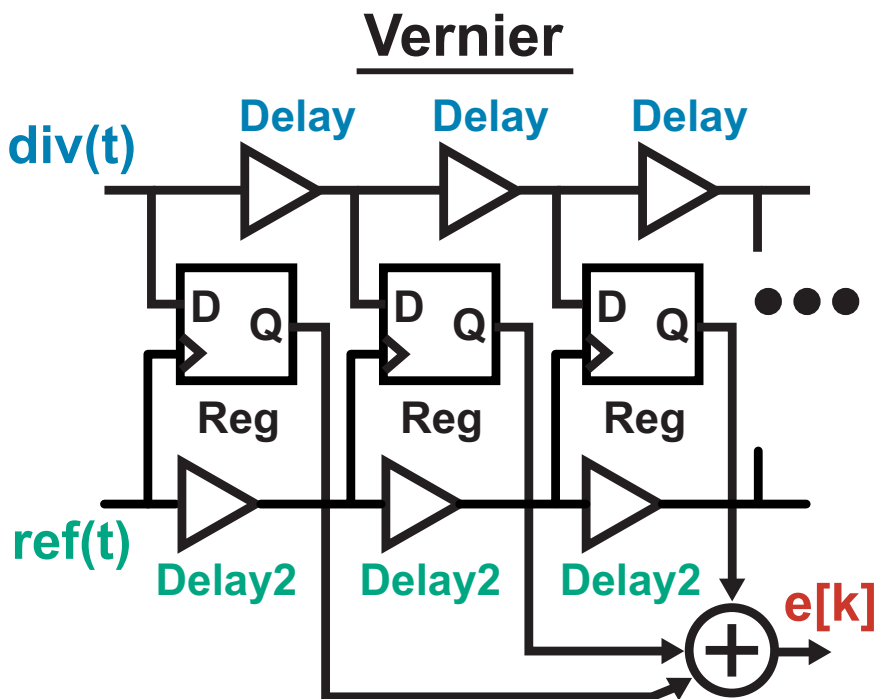  
Improve Resolution with Vernier Delay Technique




Effective resolution:
Delay-Delay2

Issues with Vernier Approach

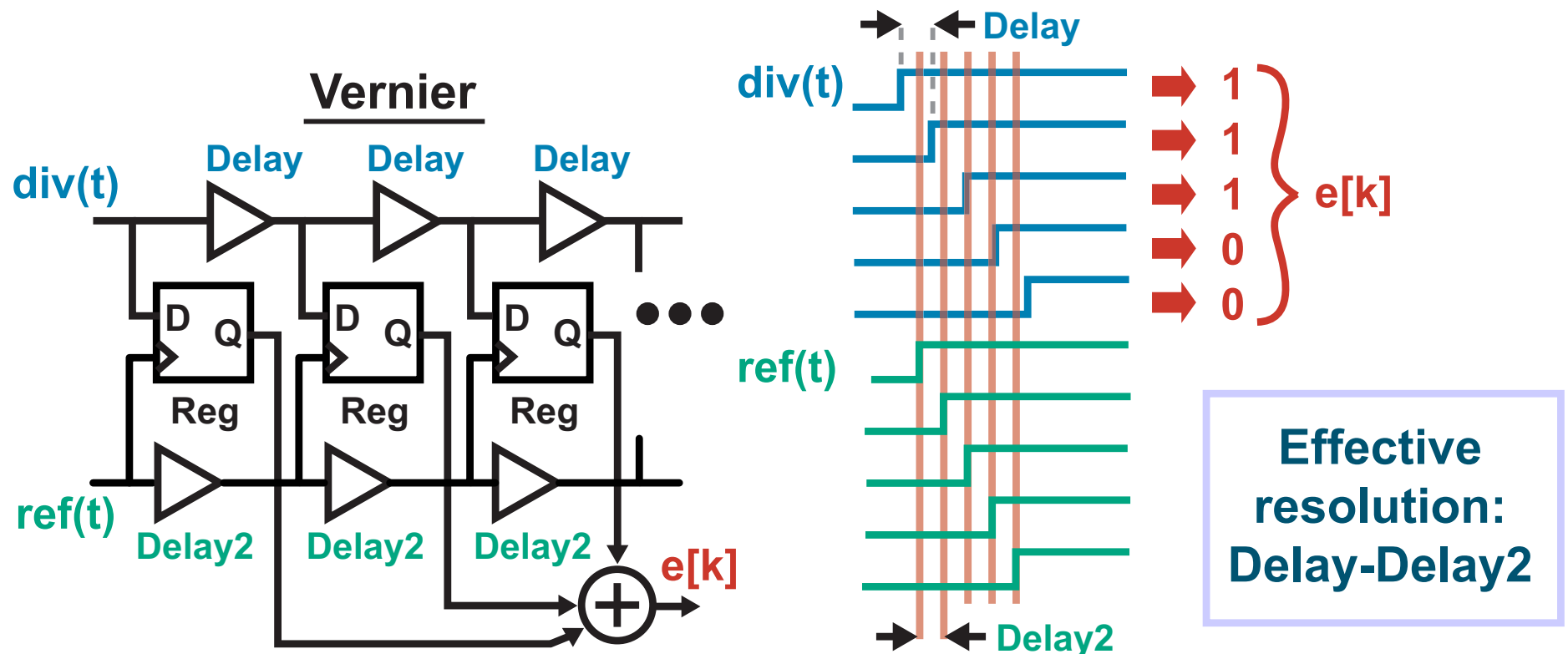- Mismatch issues are more severe than the single delay chain TDC
 - Reduced delay is formed as *difference* of two delays
- Large measurement range requires large area
 - Initial PLL frequency acquisition may require a large range




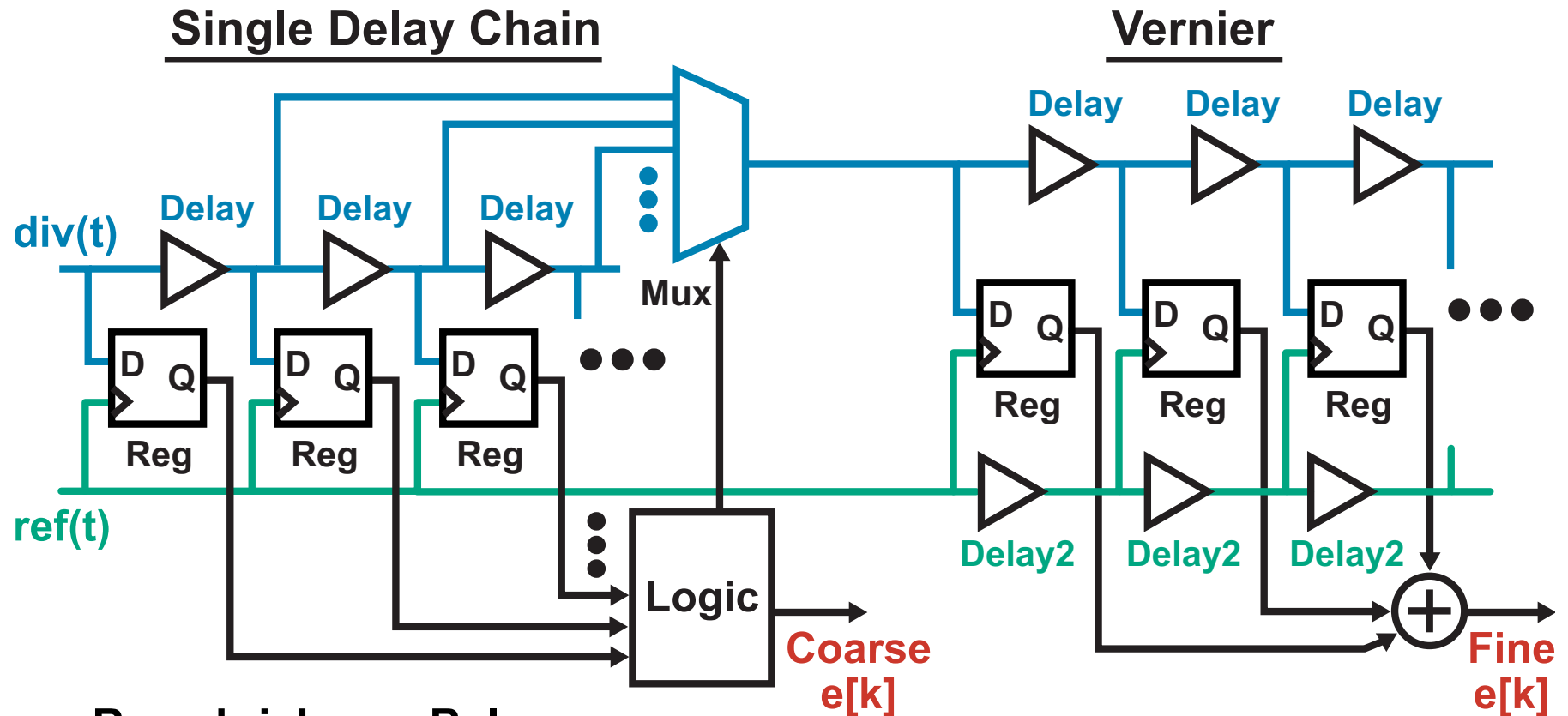Two-Step TDC Architecture Allows Area Reduction




Ramakrishnan, Balsara
VLSID '06

 - Single delay chain provides coarse resolution
- (Folded) Vernier provides fine resolution




Two-Step TDC Using Time Amplification

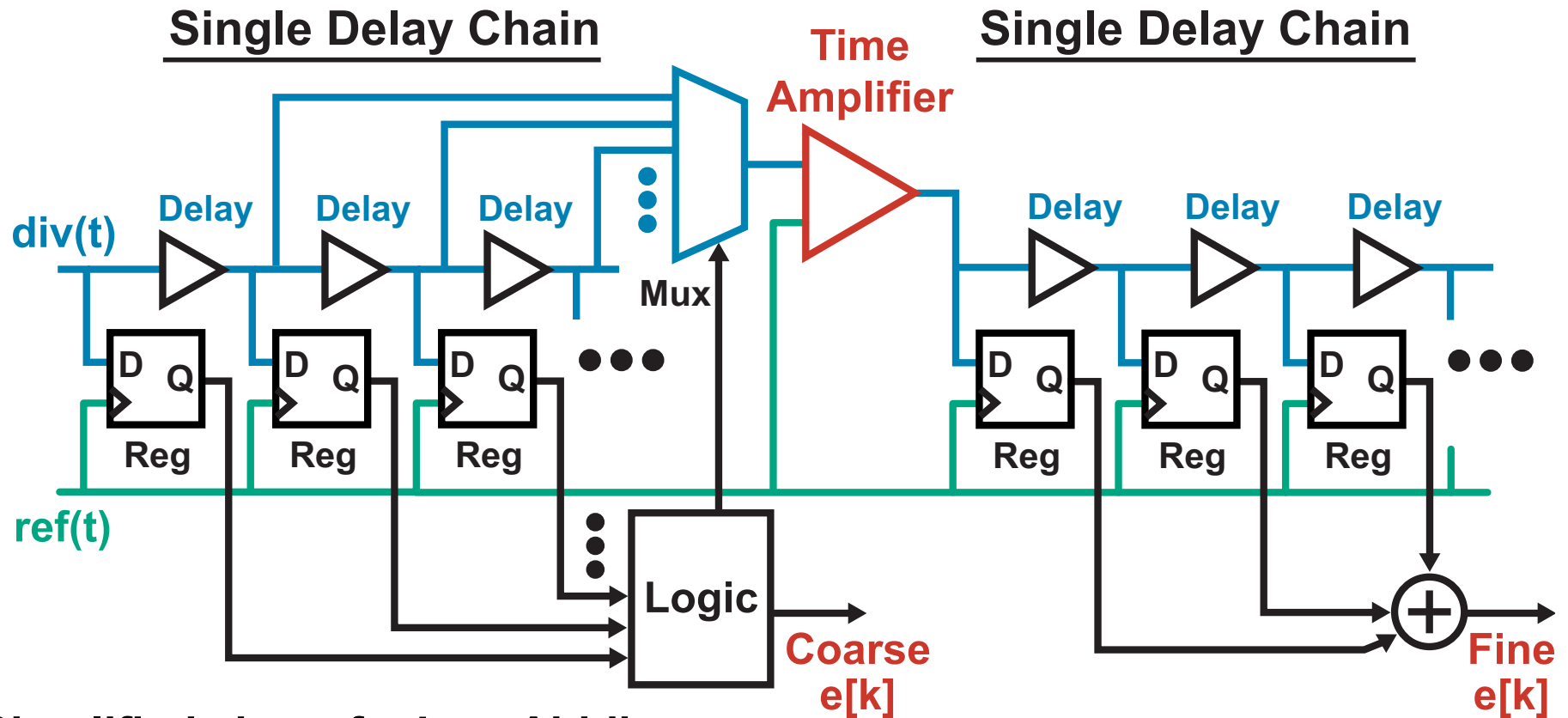


Simplified view of: Lee, Abidi
VLSI 2007

 - Single delay chain provides coarse and fine resolution
- Time amplification is used to improve resolution



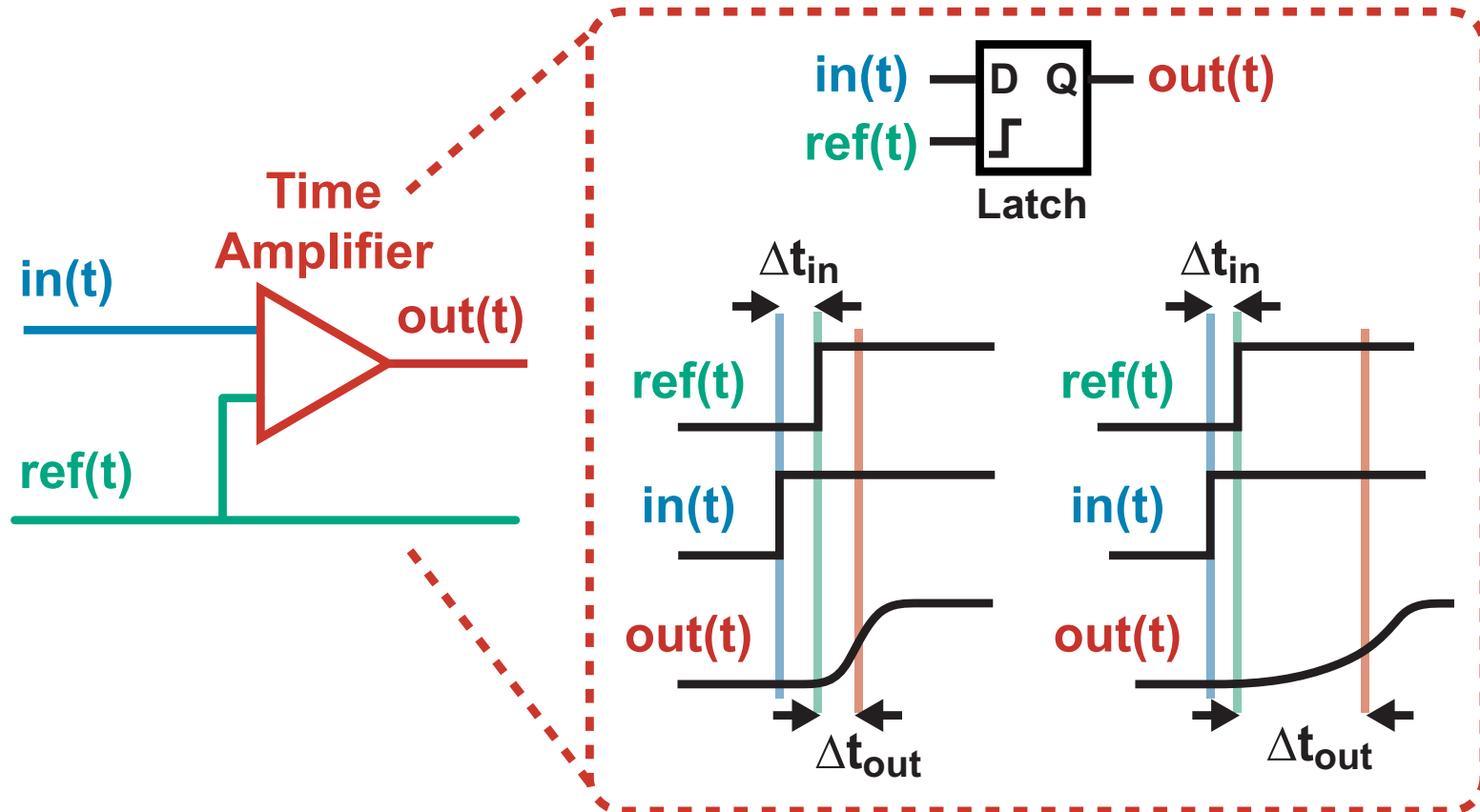
Leveraging Metastability to Create a Time Amplifier



Simplified view of: Abas, et al., Electronic Letters, Nov 2002
(note that actual implementation uses SR latch)

- **Metastability leads to progressively slower output transitions as setup time on latch is encroached upon**
 - Time difference at input is amplified at output



Interpolating time-to-digital converter

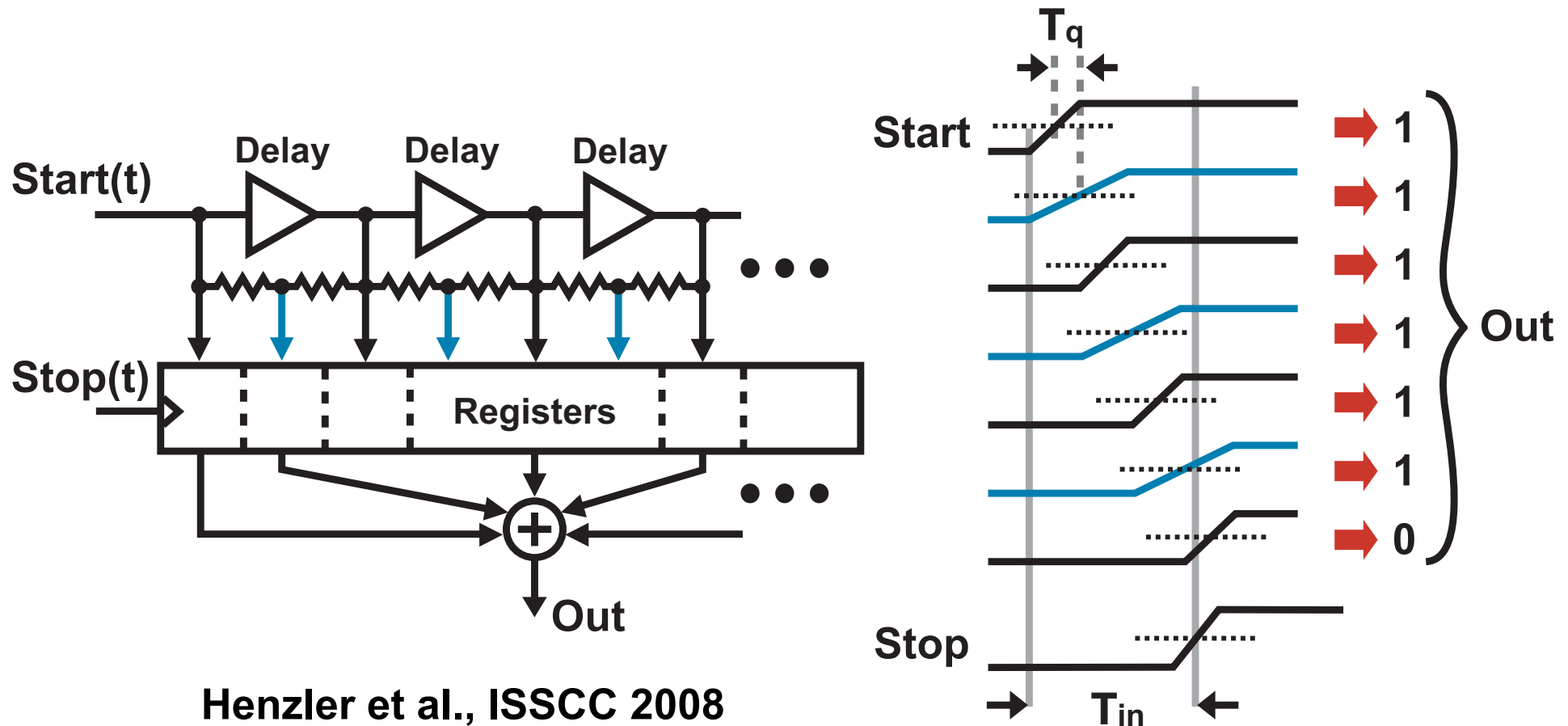

Henzler et al., ISSCC 2008


- Interpolate between edges to achieve fine resolution
- Cyclic approach can also be used for large range

An Oscillator-Based TDC

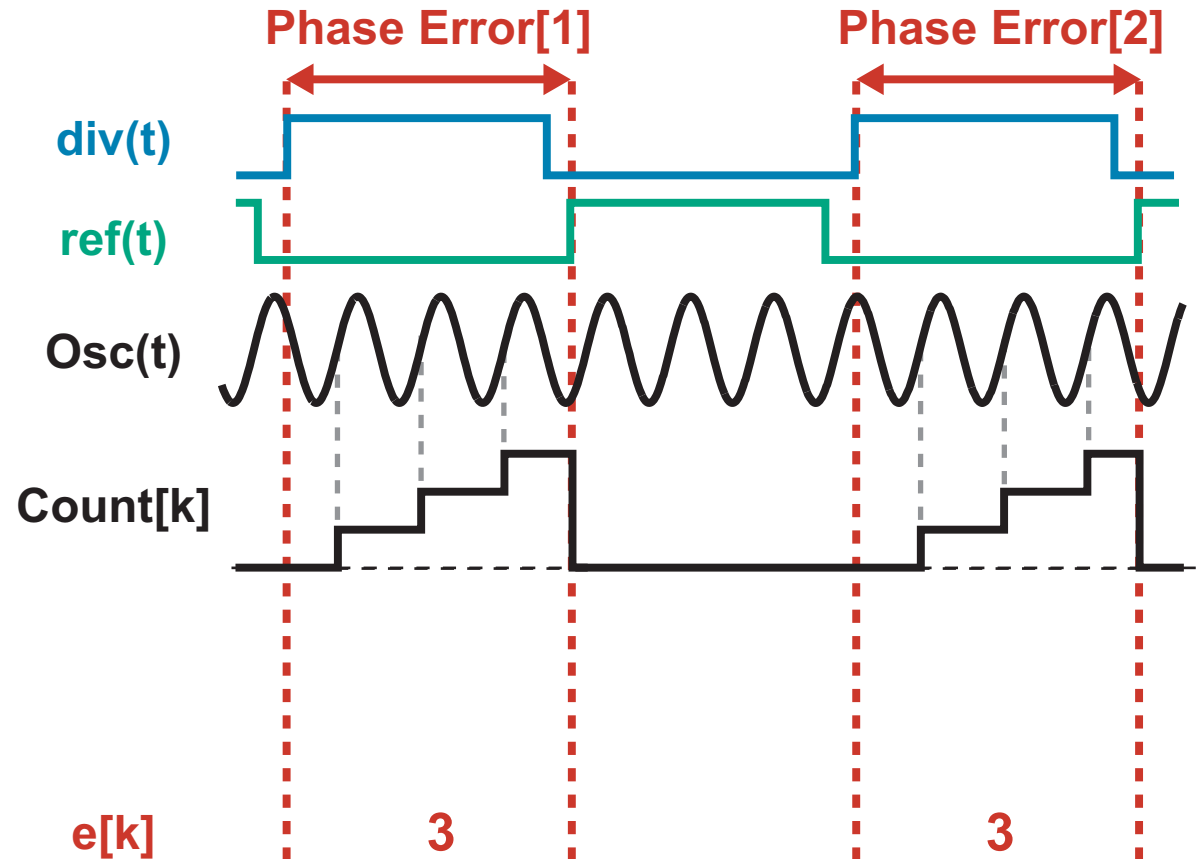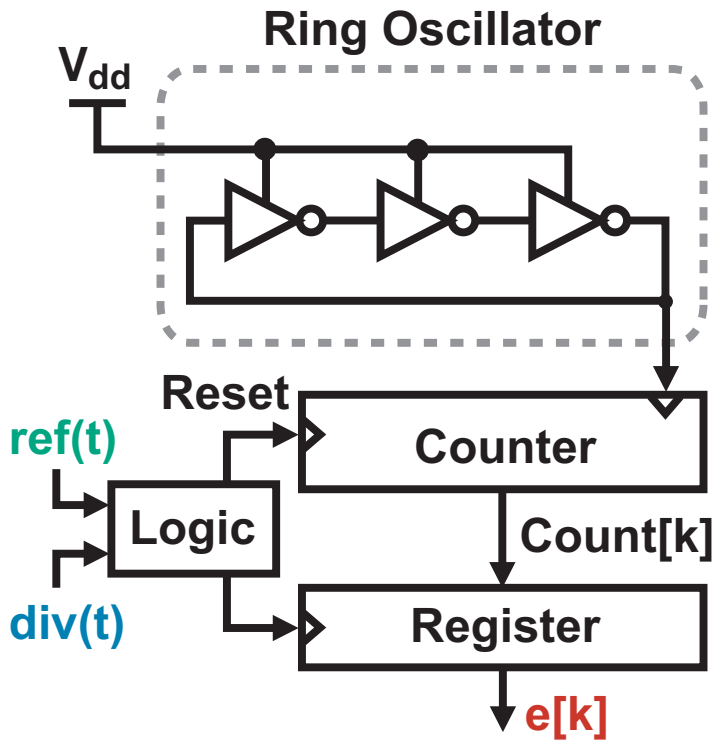


- Output $e[k]$ corresponds to the number of oscillator edges that occur during the measurement time window
- Advantages
 - Extremely large range can be achieved with compact area
 - Quantization noise is scrambled across measurements

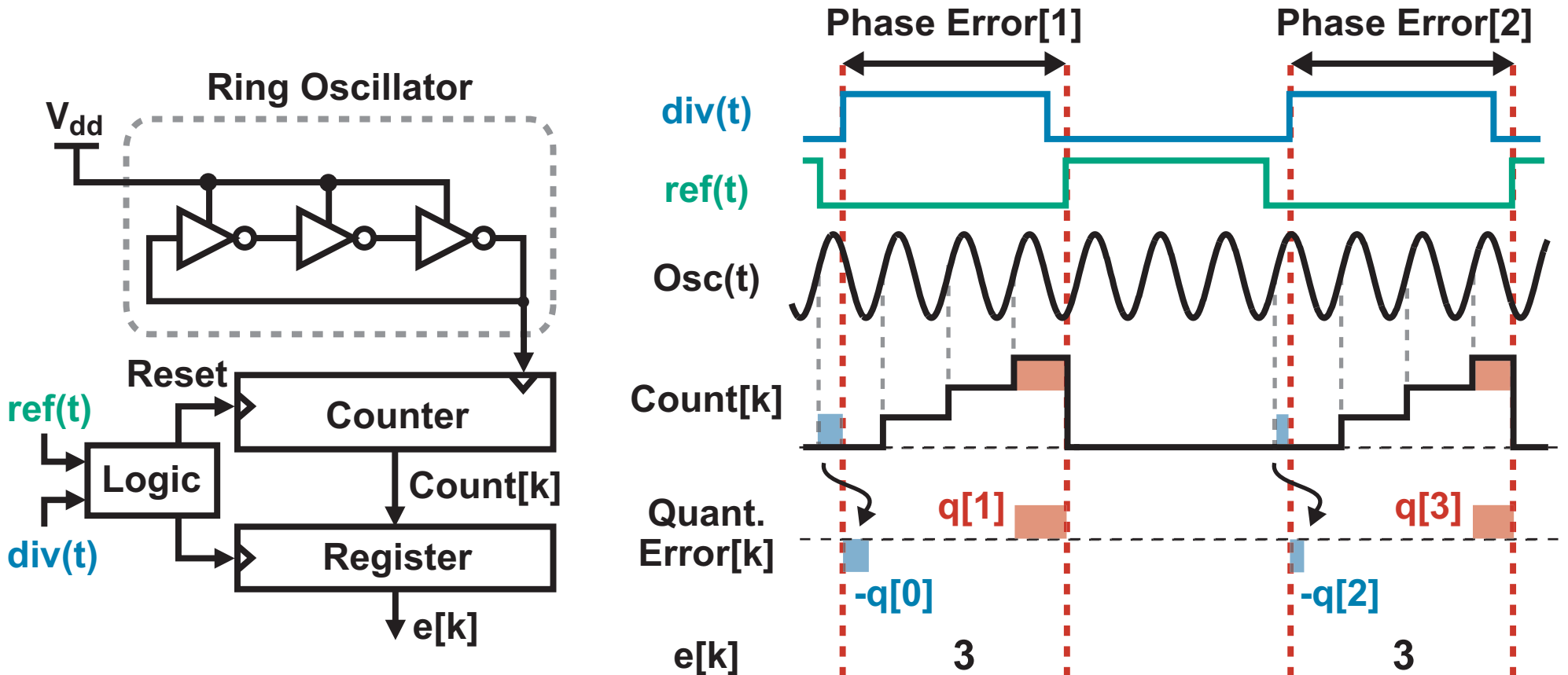A Closer Look at Quantization Noise Scrambling



- Quantization error occurs at beginning and end of each measurement interval
- As a rough approximation, assume error is uncorrelated between measurements
 - Averaging of measurements improves effective resolution

 
Deterministic quantizer error vs. scrambled error



- **Deterministic TDC do not provide inherent scrambling**
- **For oversampling benefit, TDC error must be scrambled!**
- **Some systems provide input scrambling ($\Delta\Sigma$ fractional-N PLL), while some others do not (integer-N PLL)**


Proposed GRO TDC Structure

A Gated Ring Oscillator (GRO) TDC

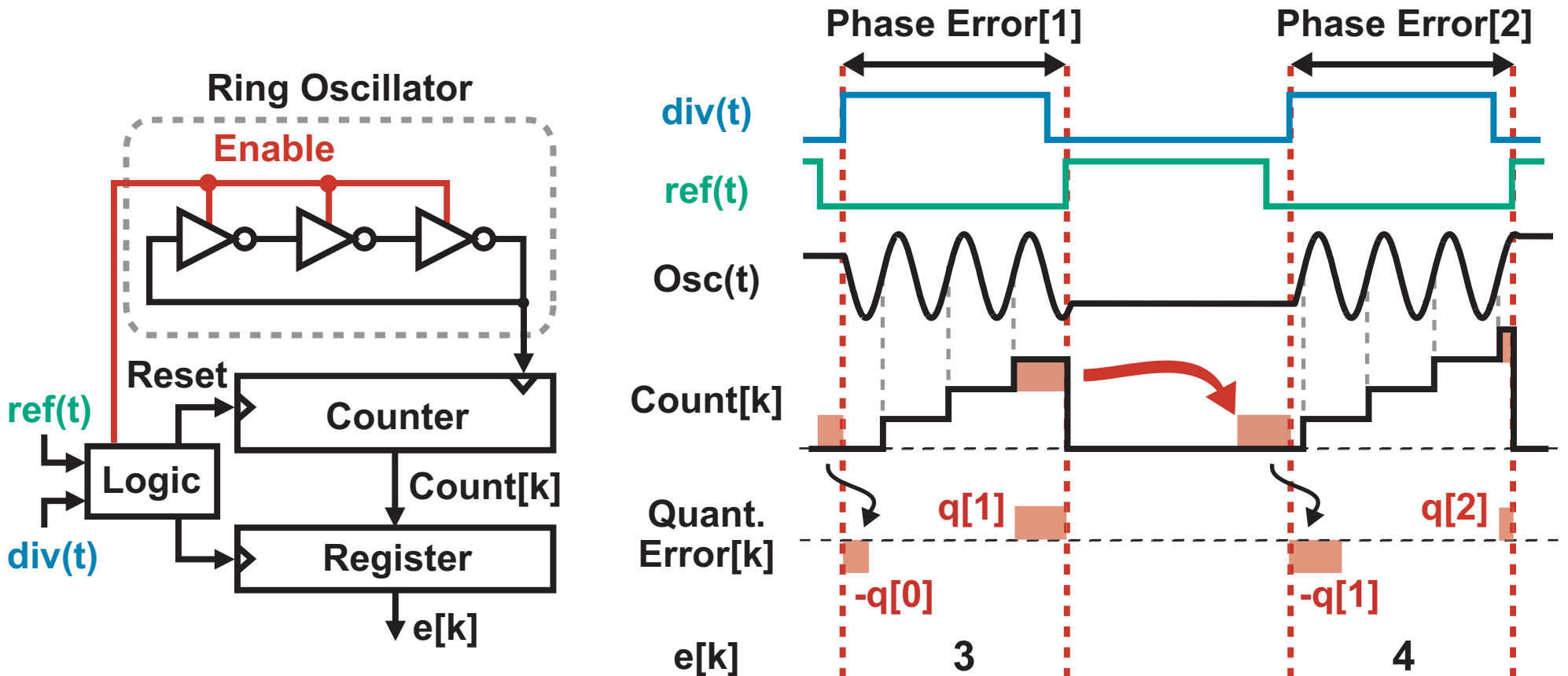


- Enable ring oscillator only during measurement intervals
 - Hold the state of the oscillator between measurements
- Quantization error becomes first order noise shaped!
 - $e[k] = Phase Error[k] + q[k] - q[k-1]$
 - Averaging dramatically improves resolution!

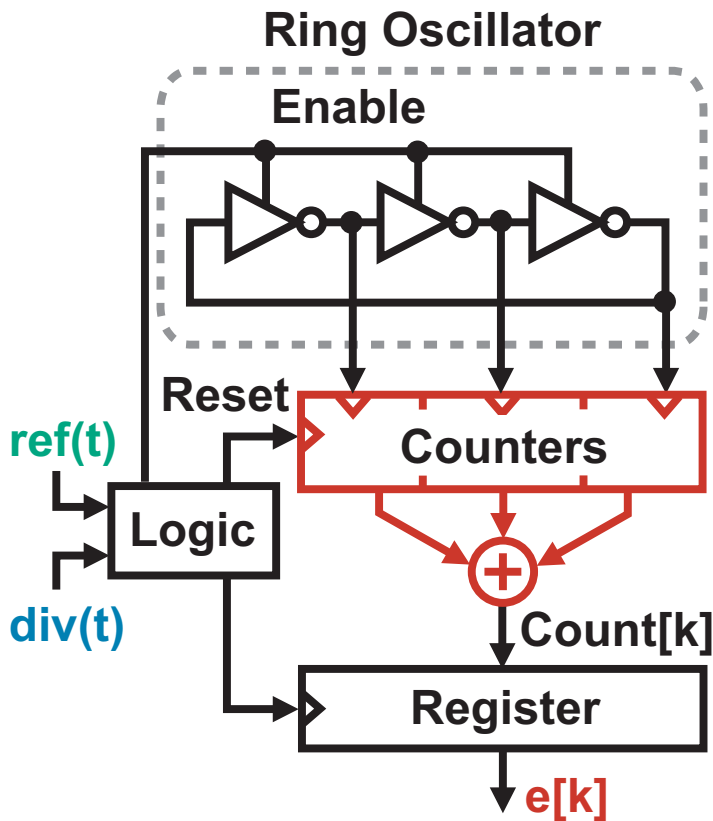Improve Resolution By Using All Oscillator Phases




Helal, Straayer, Wei,
Perrott VLSI 2007

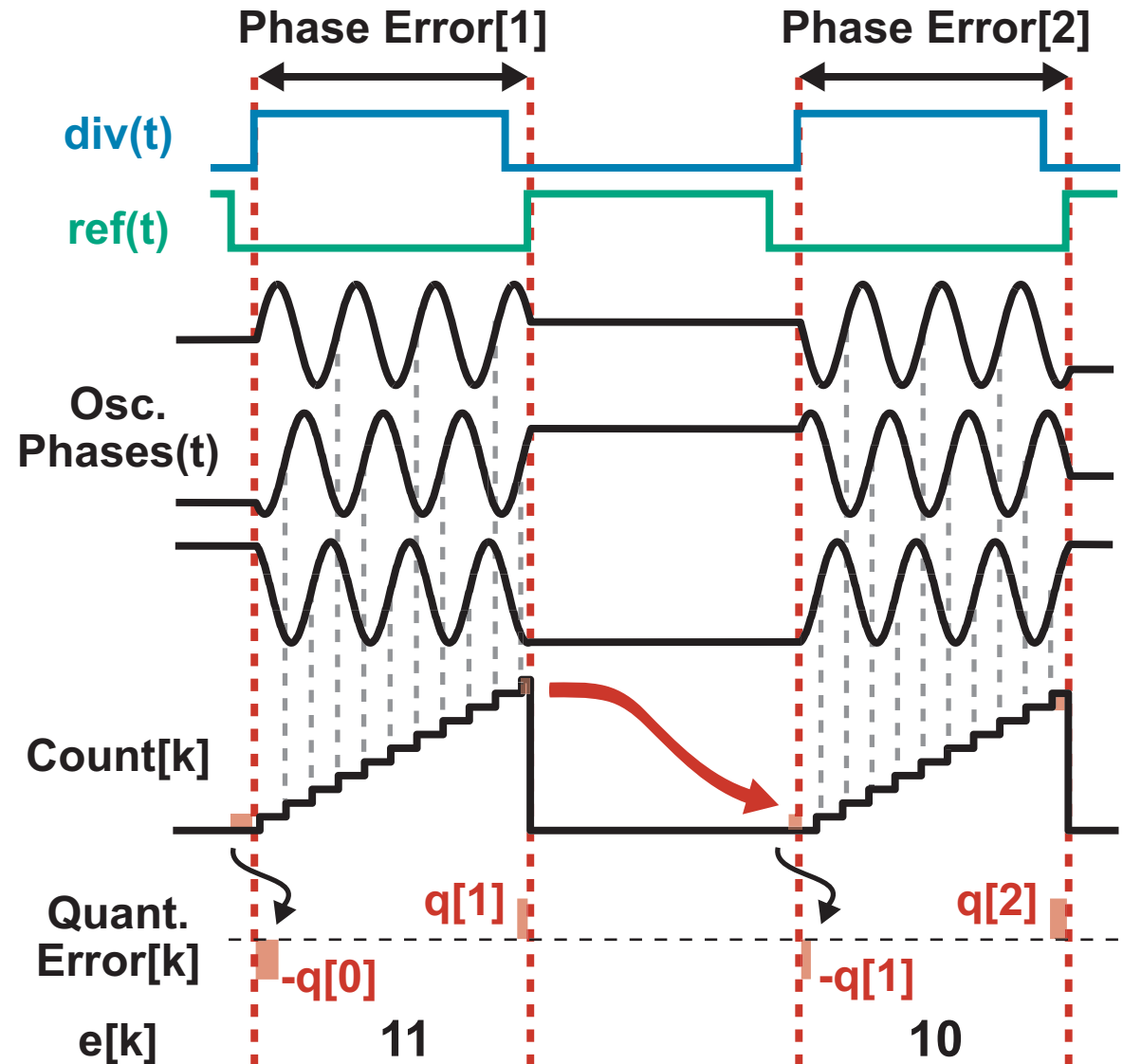



- Raw resolution is set by inverter delay
- Effective resolution is dramatically improved by averaging

GRO TDC Also Shapes Delay Mismatch

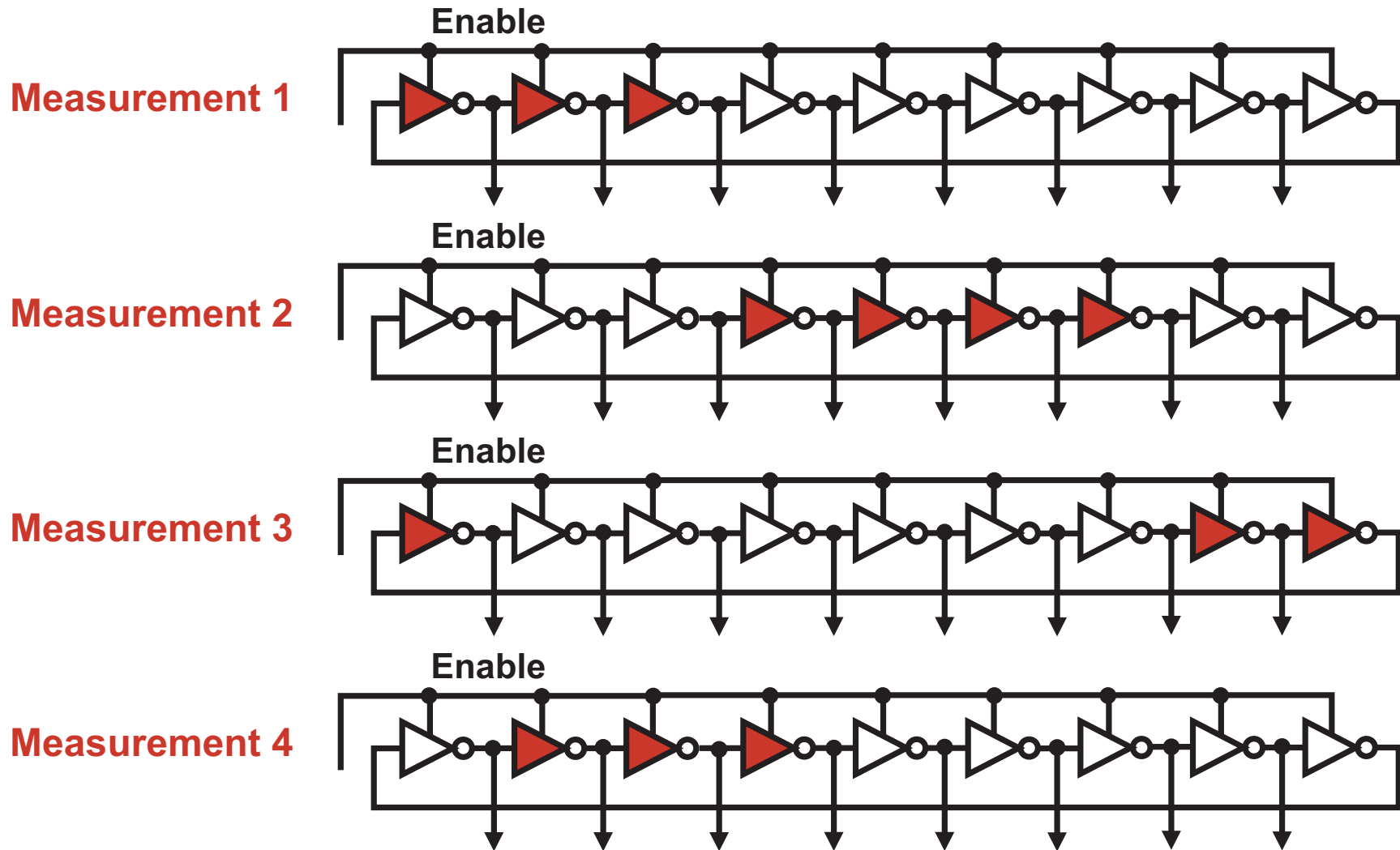


- Barrel shifting occurs through delay elements across different measurements
 - Mismatch between delay elements is first order shaped!

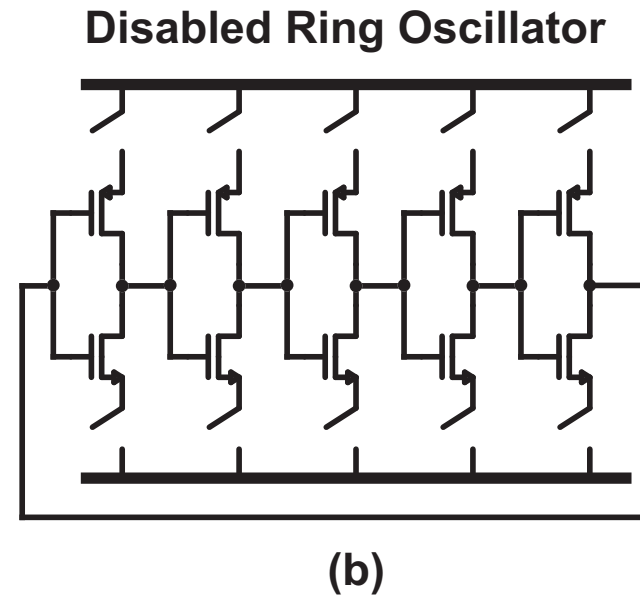 
Simple gated ring oscillator inverter-based core



 
Gate the oscillator by switching the inverter cores to the power supply




GRO Prototype

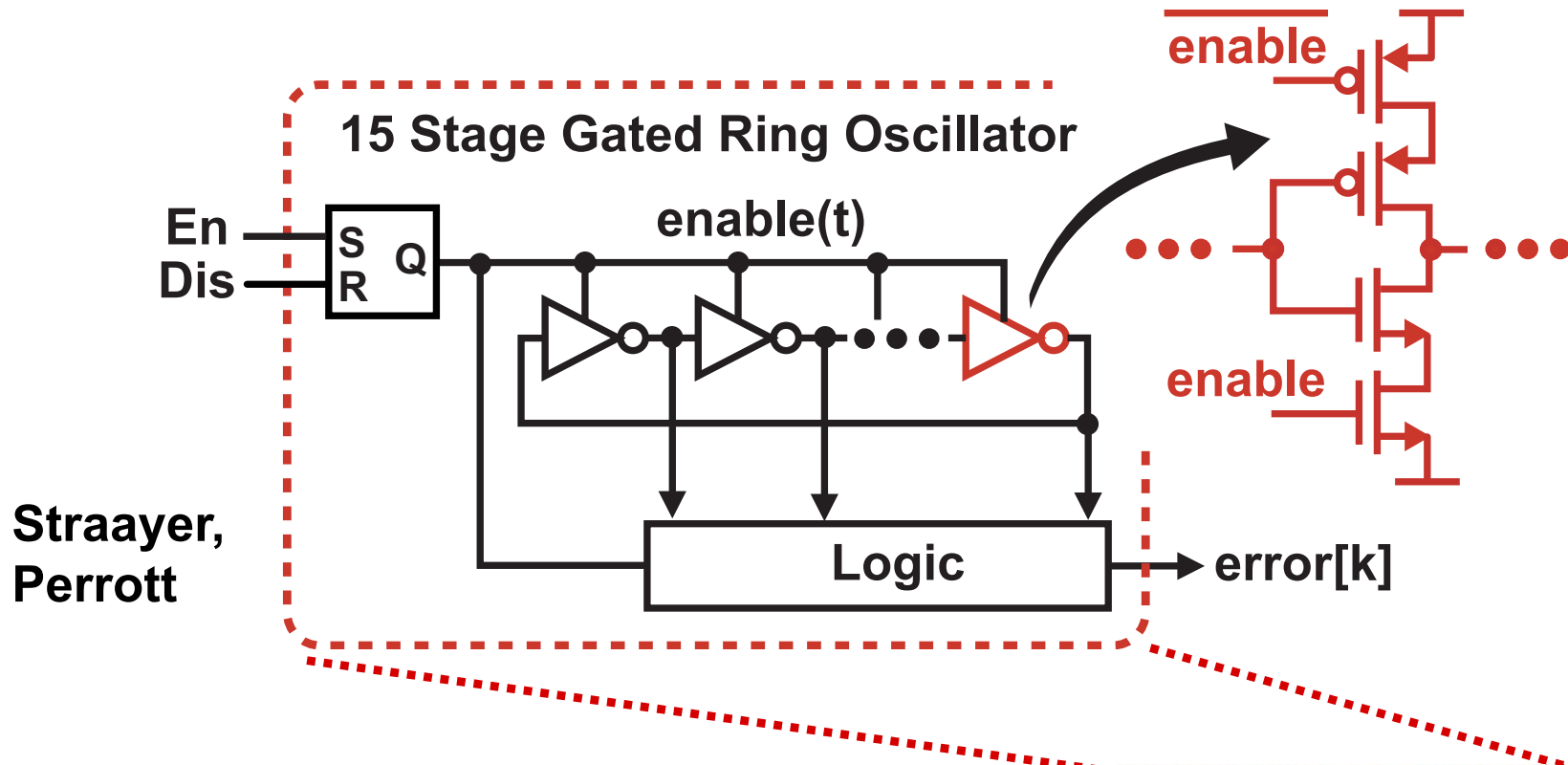

 
- GRO implemented as a custom 0.13 μm CMOS IC



 
Measured GRO Results Confirm Noise Shaping



 Measured deadzone behavior of inverter-based GRO



(a)

 


(b)


- Deadzones were caused by errors in gating the oscillator
- GRO “injection locked” to an integer ratio of F_s
- Behavior occurred for almost all integer boundaries, and some fractional values as well
- Noise shaping benefit was limited by this gating error

Next Generation GRO: Multi-path oscillator concept

Single Input
Single Output

 


Multiple Inputs
Single Output

 


- Use multiple inputs for each delay element instead of one
- Allow each stage to optimally begin its transition based on information from the entire GRO phase state
- Key design issue is to ensure primary mode of oscillation

Multi-path inverter core

 


(a) Asymmetrically skewed inverter

Lee, Kim, Lee
JSSC 1997


 


(b) Multiple skewed inverters


Mohan, et. al.,
CICC 2005

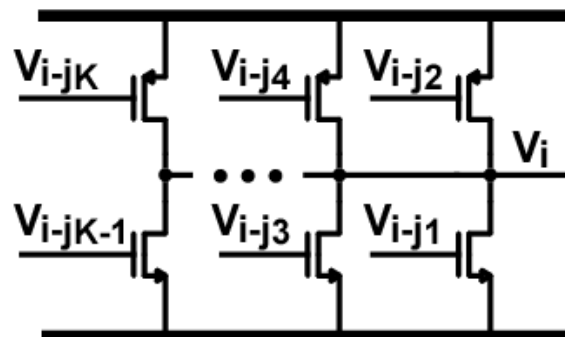

(c) Unrestricted connections

 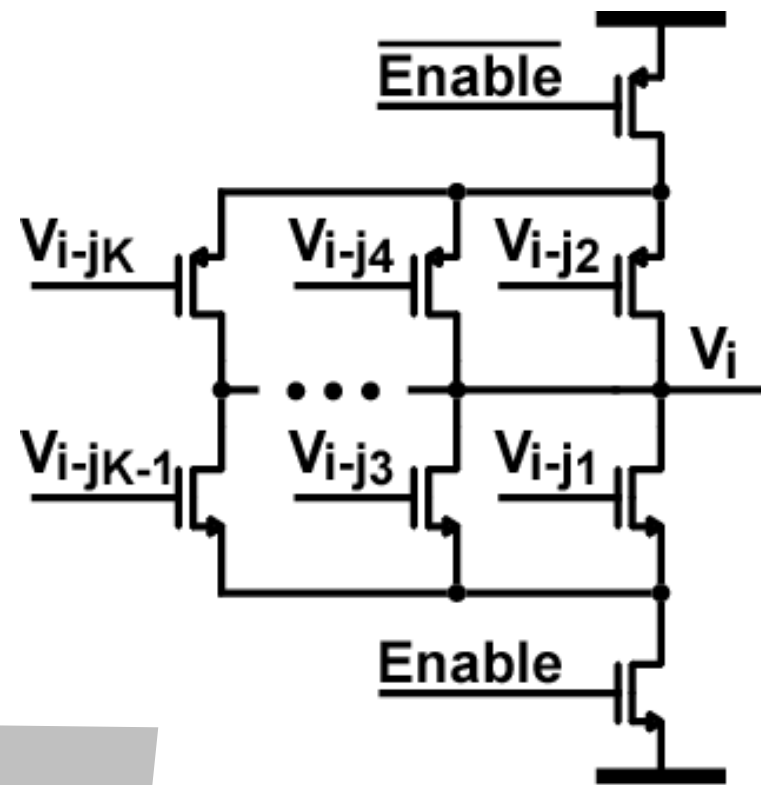

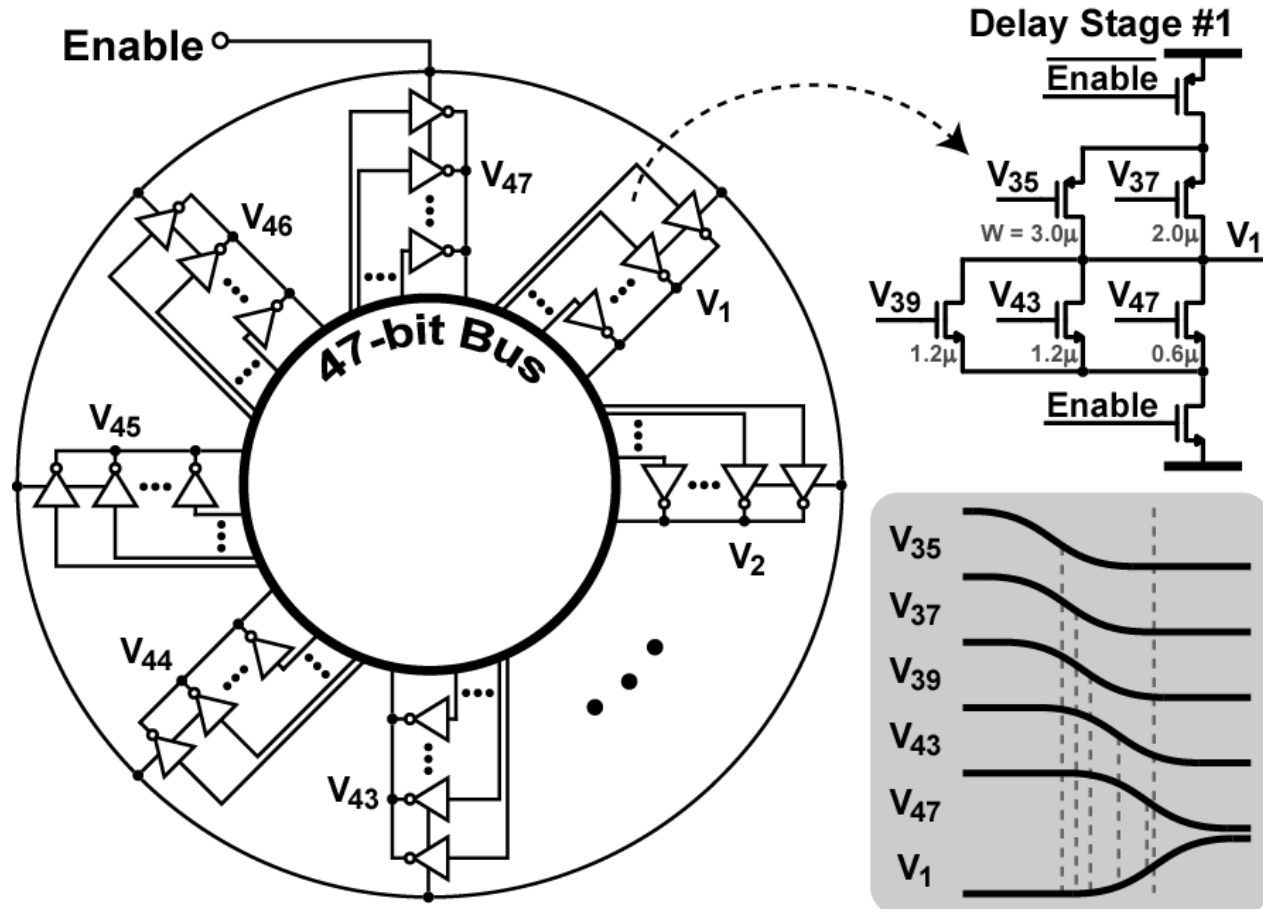
Proposed multi-path gated ring oscillator



Hsu, Straayer, Perrott
ISSCC 2008

- Oscillation frequency near 2GHz with 47 stages...
- Reduces effective delay per stage by a factor of 5-6!
- Represents a factor of 2-3 improvement compared to previous multi-path oscillators



A simple measurement approach...

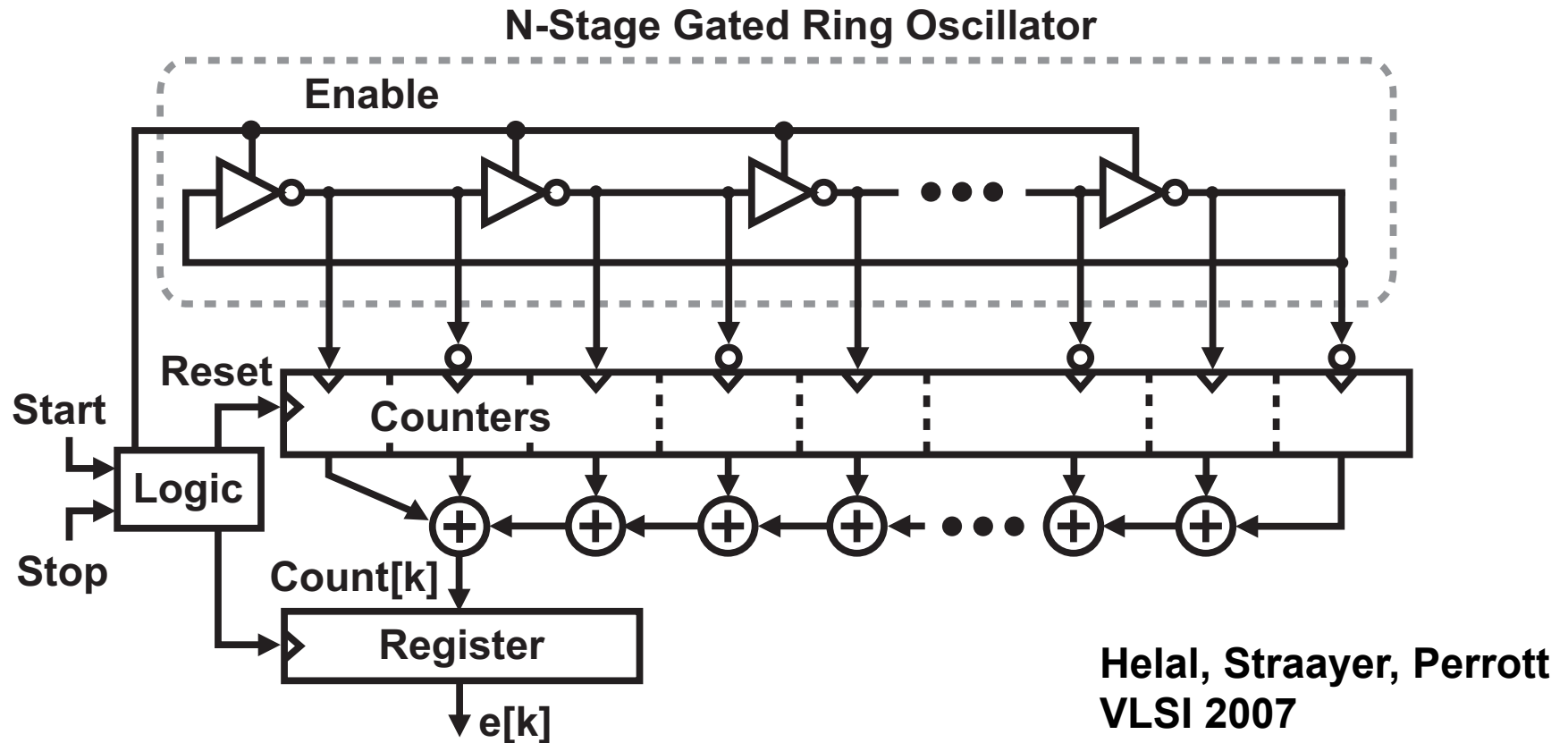

- 2 counters per stage * 47 stages = 94 counters each at 2GHz
- Power consumption for these counters is unreasonable


Need a more efficient way to measure the multi-path GRO

Count Edges by Sampling Phase

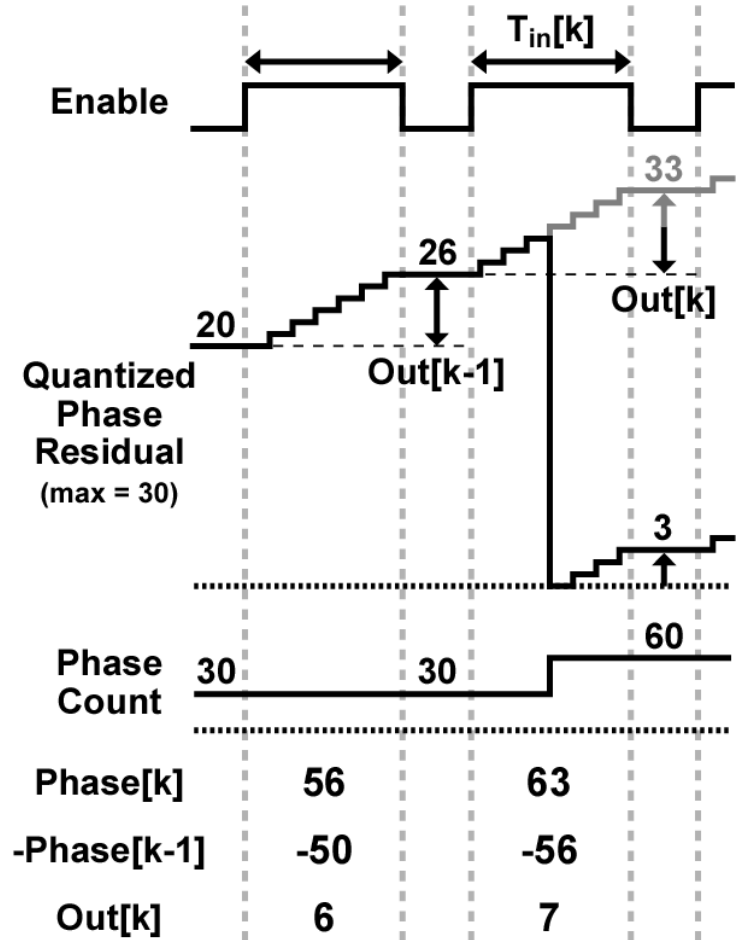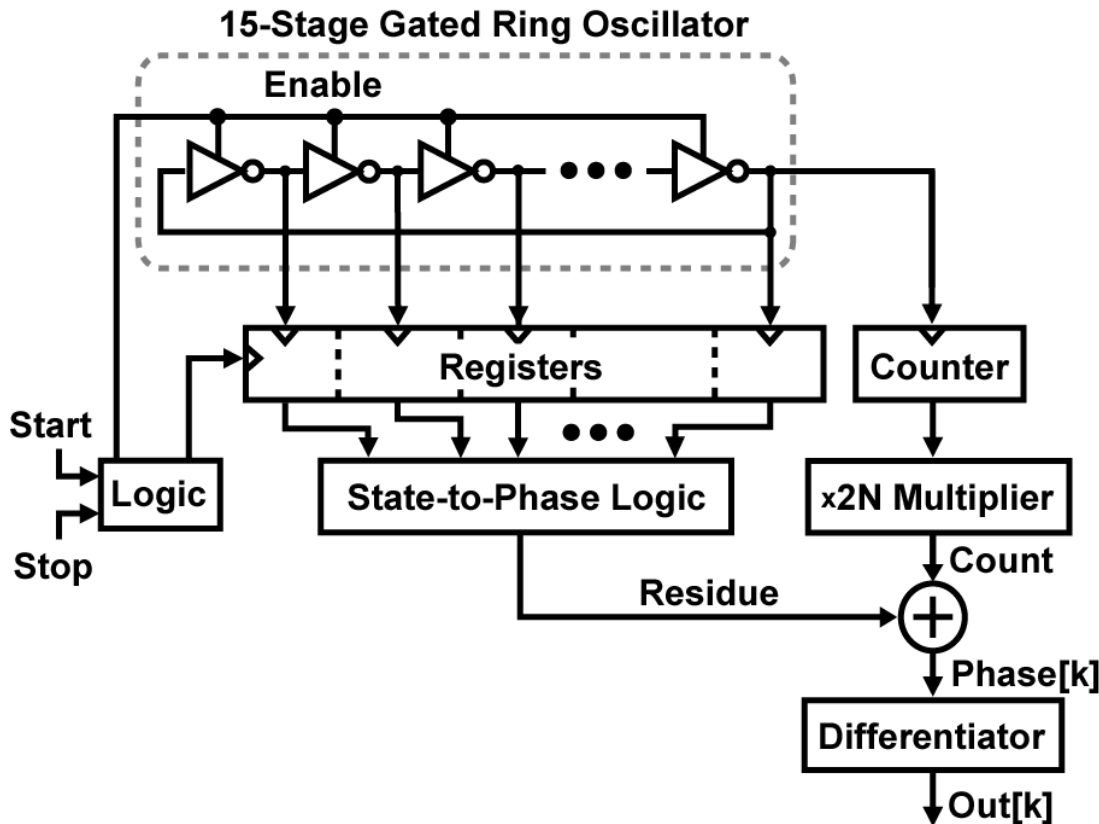



- Calculate phase from:
 - A single counter for coarse phase information (keeps track of phase wrapping)
 - GRO phase state for fine count information
- 1 counter and N registers → much more efficient

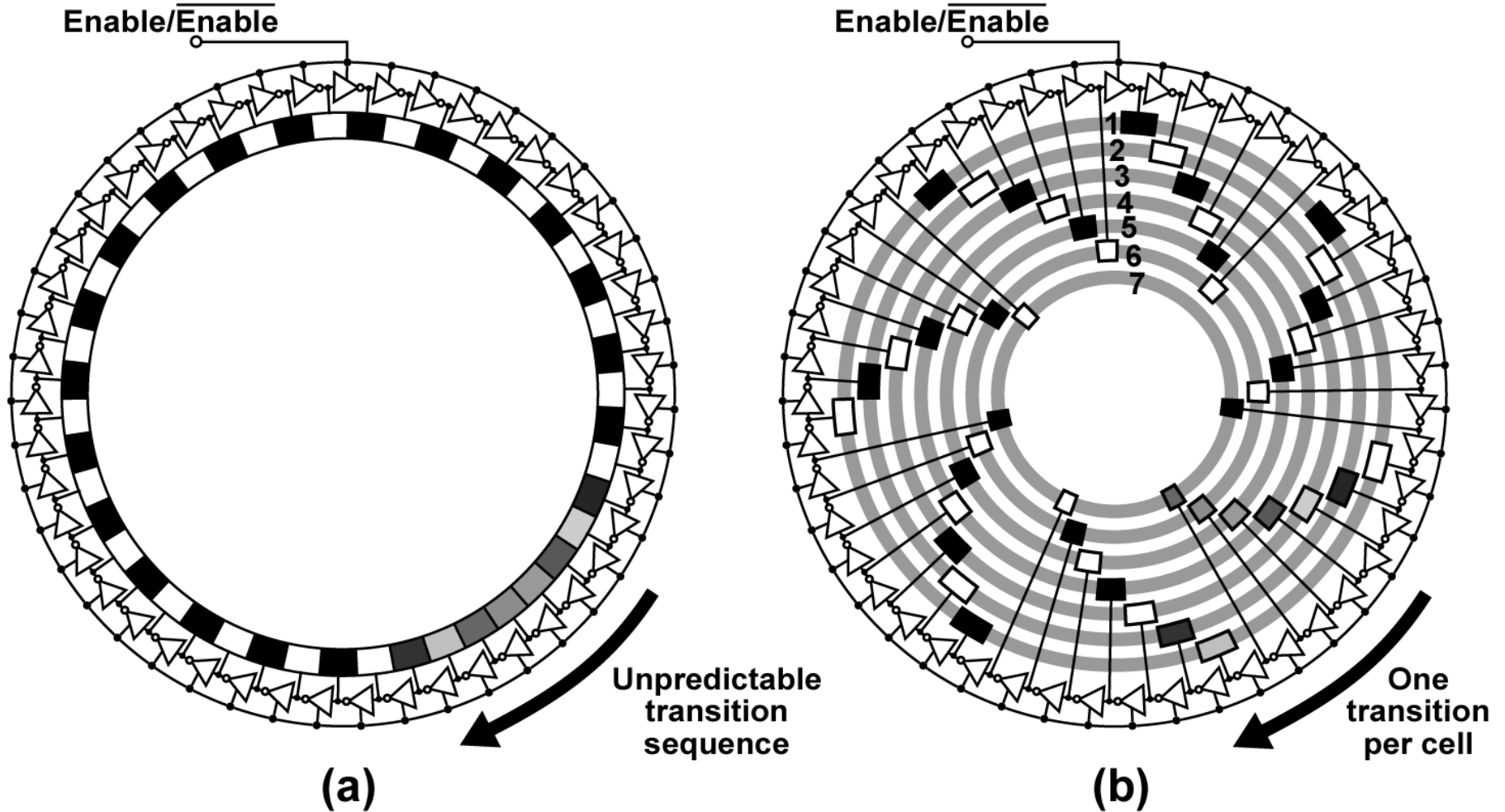Proposed Multi-Path Measurement Structure



- Multi-path structure leads to ambiguity in edge position
- Partition into 7 cells to avoid such ambiguity
 - Requires 7 counters rather than 1, but power still OK

 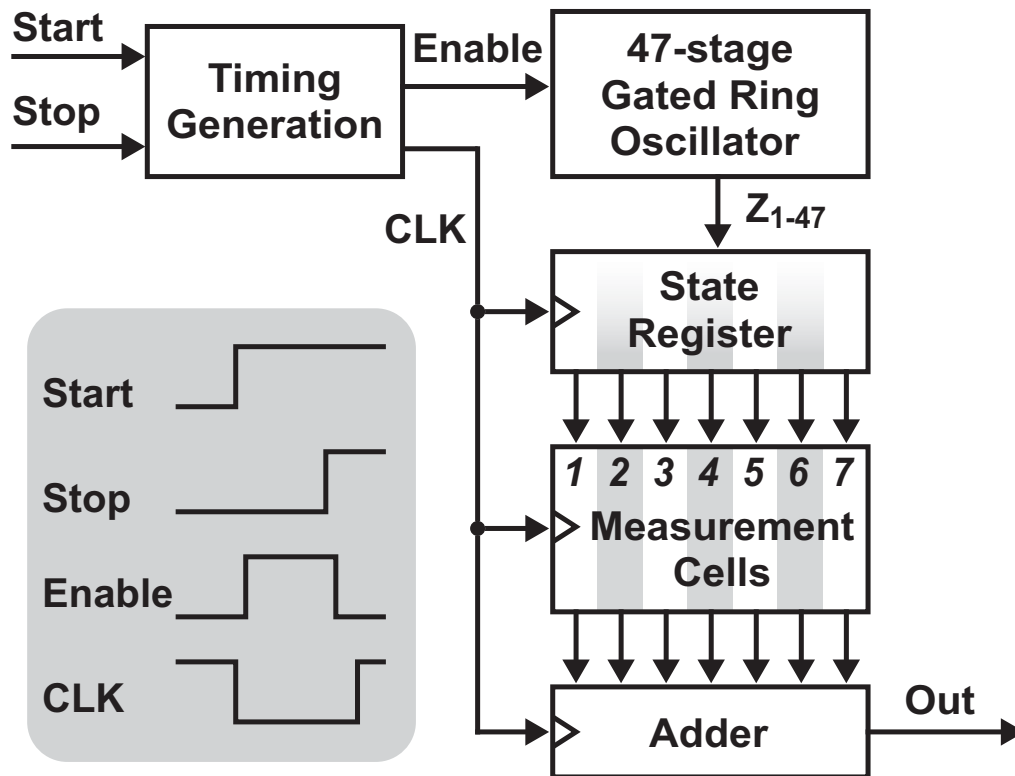
Prototype 0.13 μm CMOS multi-path GRO-TDC




Straayer et al., VLSI 2008

- **Two implemented versions:**
 - 8-bit, 500Msps
 - 11-bit, 100Msps version
- **2-21mW power consumption depending on input duty cycle**

Measured noise-shaping of multi-path GRO

 


(a)

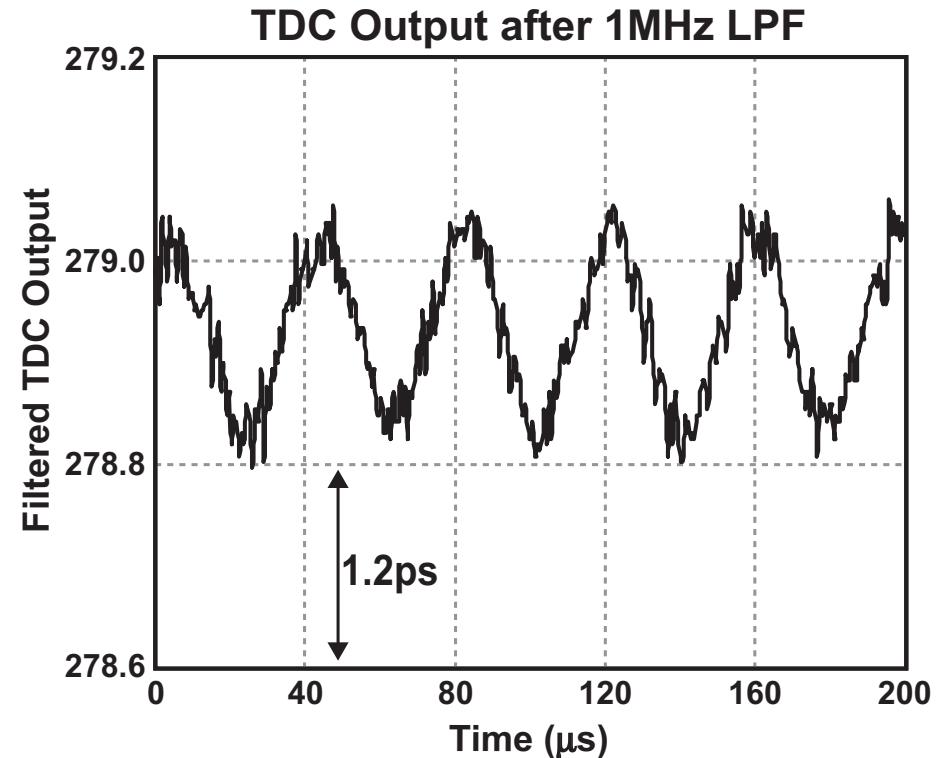


(b)

- Data collected at 50Msps
- More than 20dB of noise-shaping benefit
- 80fs_{rms} integrated error from 2kHz-1MHz
- Floor primarily limited by 1/f noise (up to 0.5-1MHz)

 Measured deadzone behavior for multi-path GRO



(a)

 


(b)

- Only deadzones for outputs that are multiples of $2N$
 - 94, 188, 282, etc.
 - No deadzones for other even or odd integers, fractional output
- Size of deadzone is reduced by 10x


***The Issue of Quantization Noise Due to
Divider Dithering***

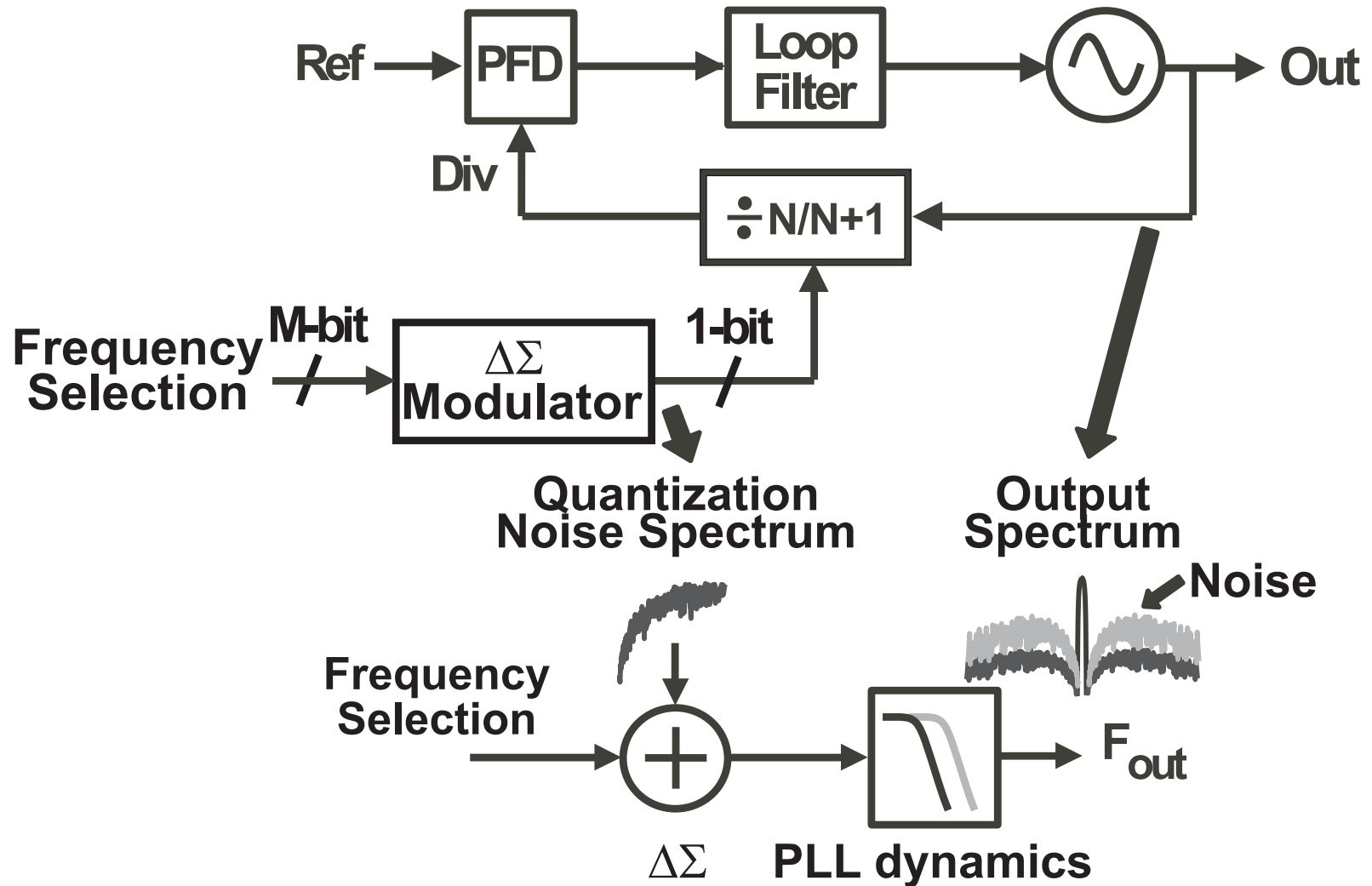The Nature of the Quantization Noise Problem



- Increasing PLL bandwidth increases impact of $\Delta\Sigma$ fractional-N noise
 - Cancellation offers a way out!

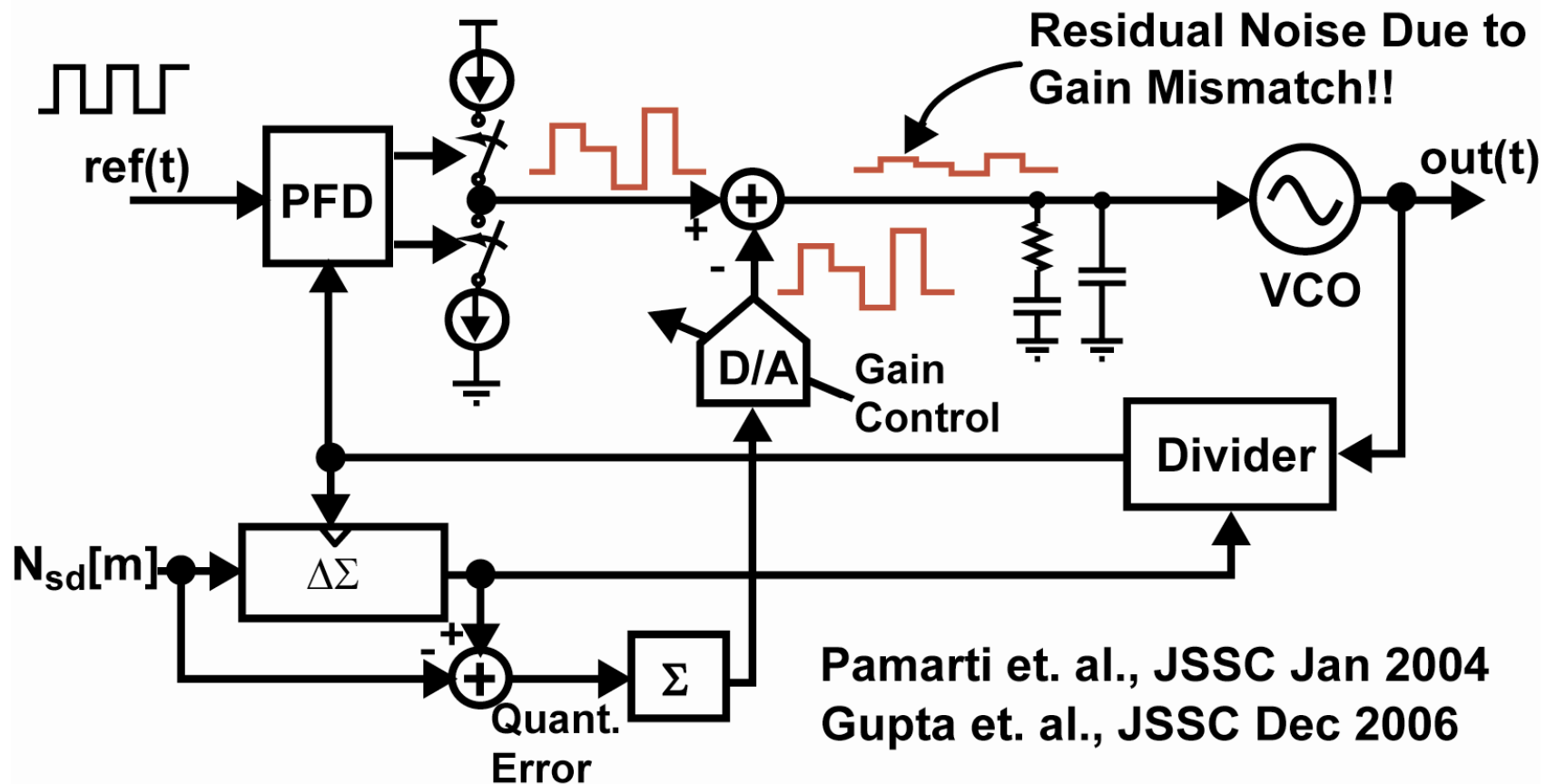
Previous Analog Quantization Noise Cancellation



- Phase error due to $\Delta\Sigma$ is predicted by accumulating $\Delta\Sigma$ quantization error
- Gain matching between PFD and D/A must be precise


Matching in analog domain limits performance

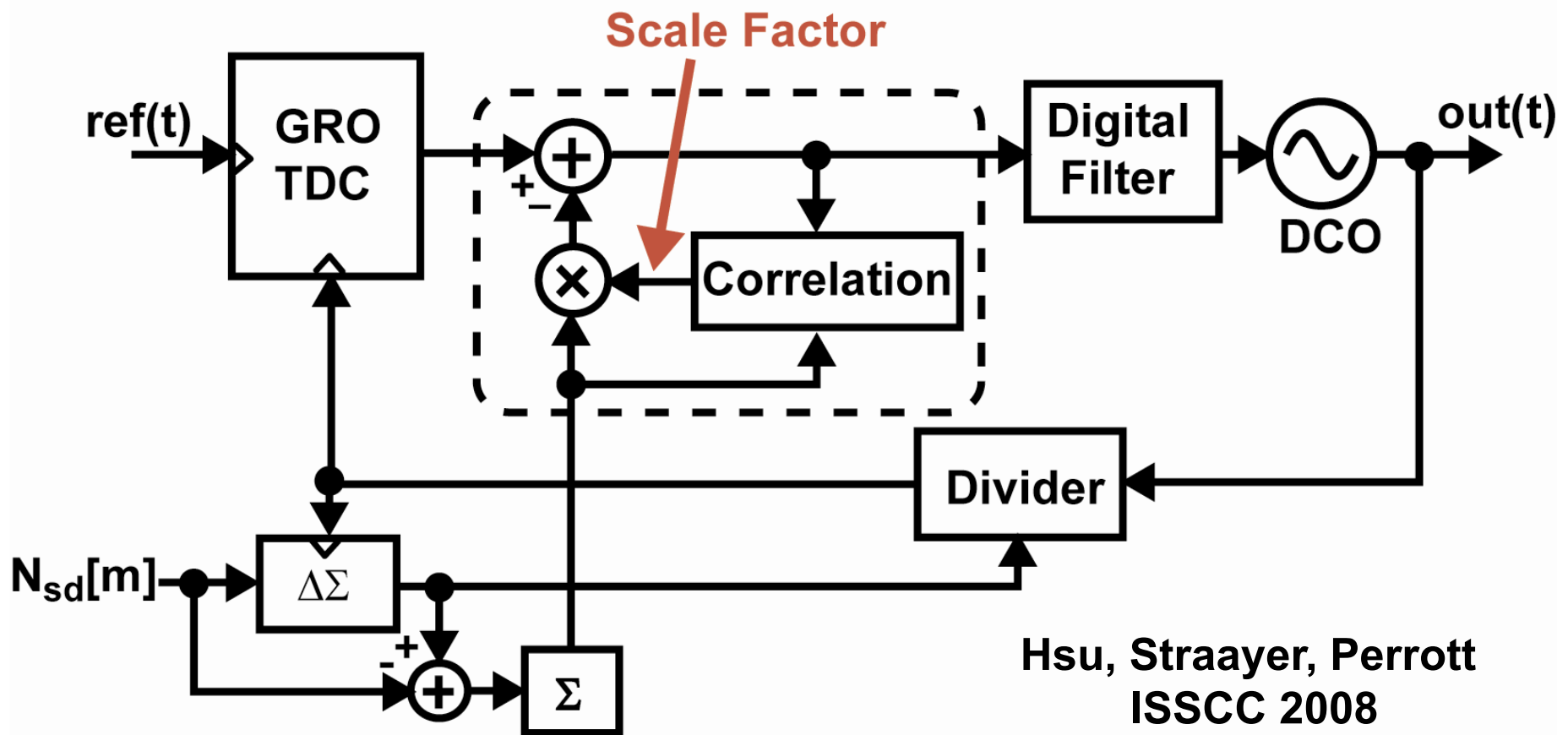Proposed All-digital Quantization Noise Cancellation




- Scale factor determined by simple digital correlation
- Analog non-idealities such as DC offset are completely eliminated

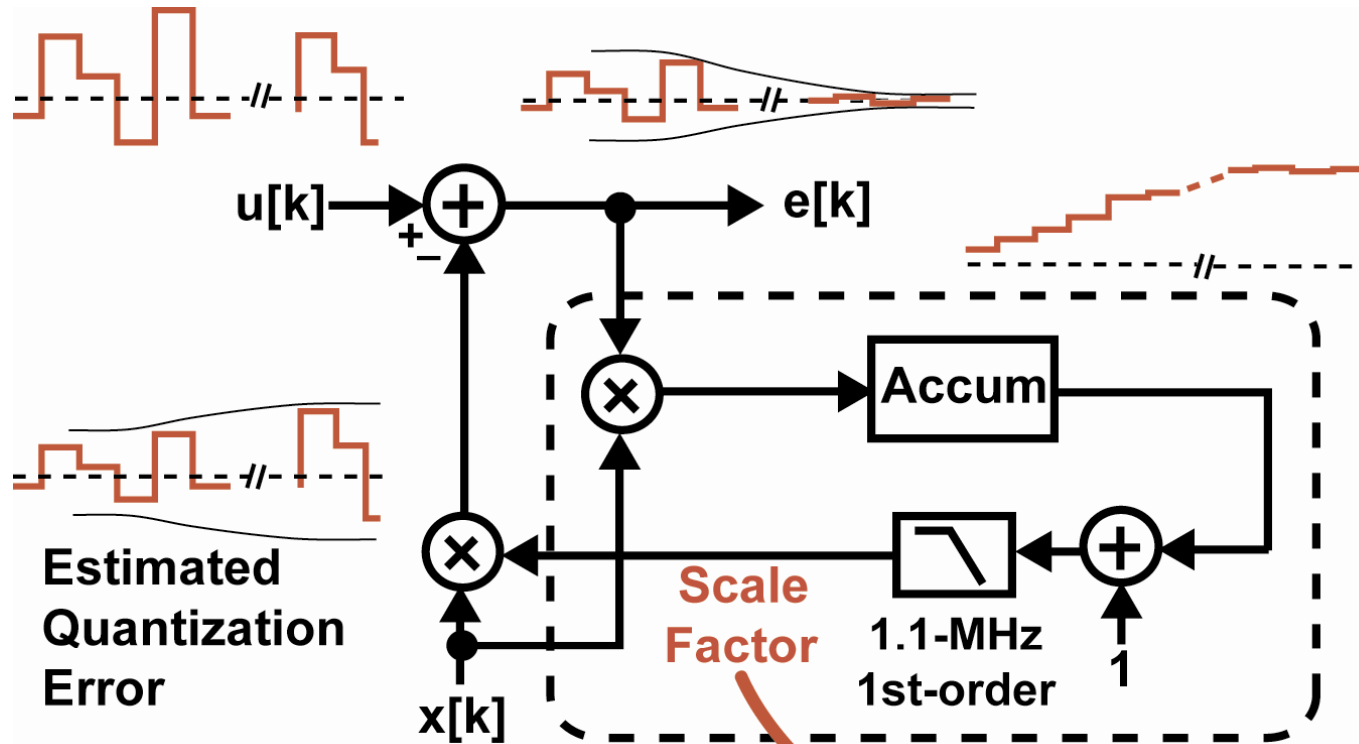
Details of Proposed Quantization Noise Cancellation



 - **Correlator out is accumulated and filtered to achieve scale factor**
 - Settling time chosen to be around 10 us
- See *analog* version of this technique in *Swaminathan et.al., ISSCC 2007*




Proposed Digital Wide BW Synthesizer

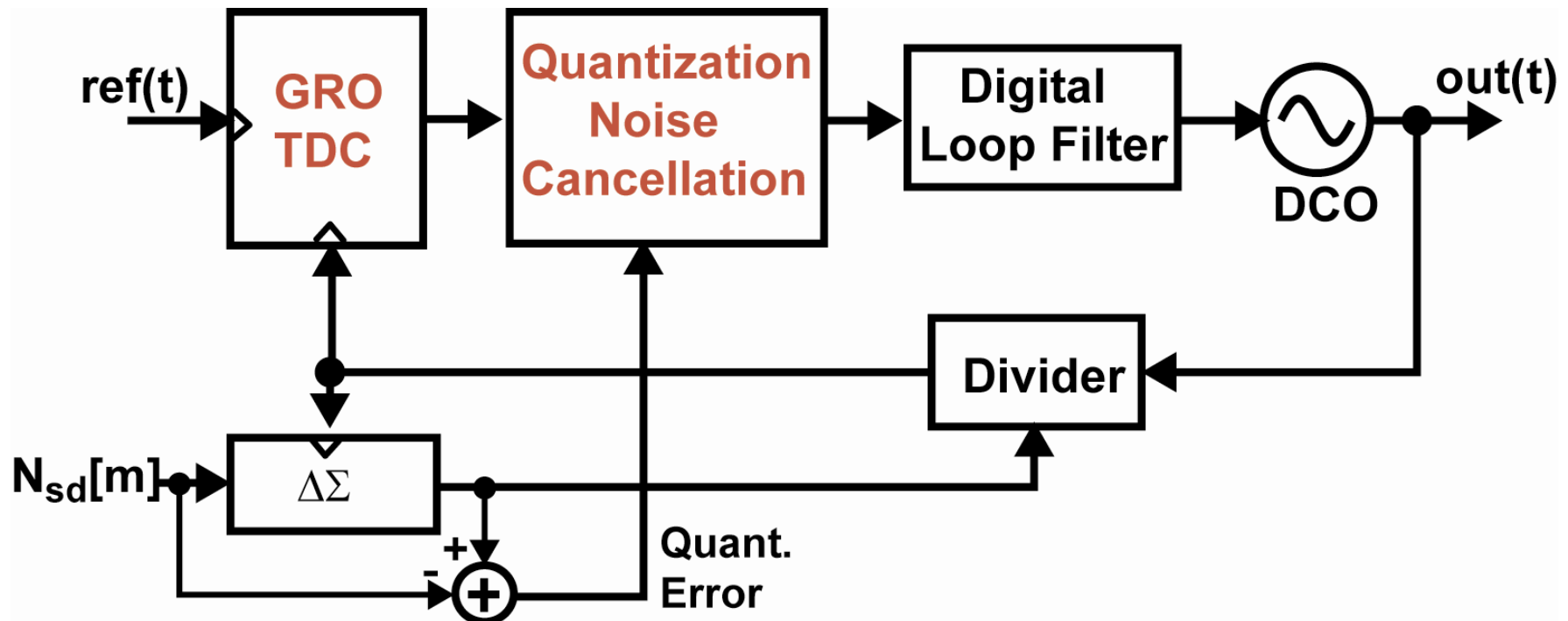


- **Gated-ring-oscillator (GRO) TDC** achieves low in-band noise
- **All-digital quantization noise cancellation** achieves low out-of-band noise
- **Design goals:**
 - 3.6-GHz carrier, 500-kHz bandwidth
 - $<-100\text{dBc/Hz}$ in-band, $<-150\text{ dBc/Hz}$ at 20 MHz offset

Overall Synthesizer Architecture

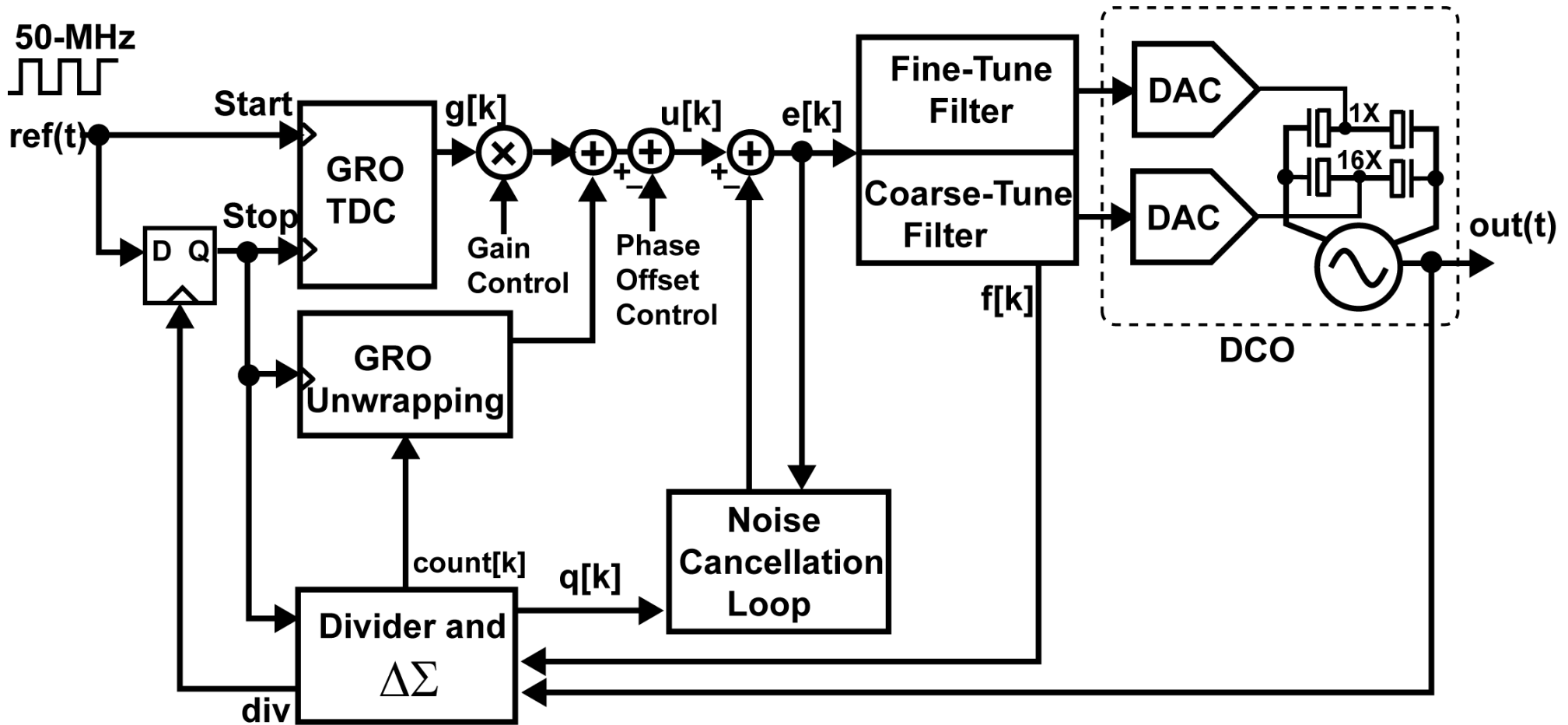

Note: Detailed behavioral simulation model available at <http://www.cppsim.com>


Dual-Port LC VCO

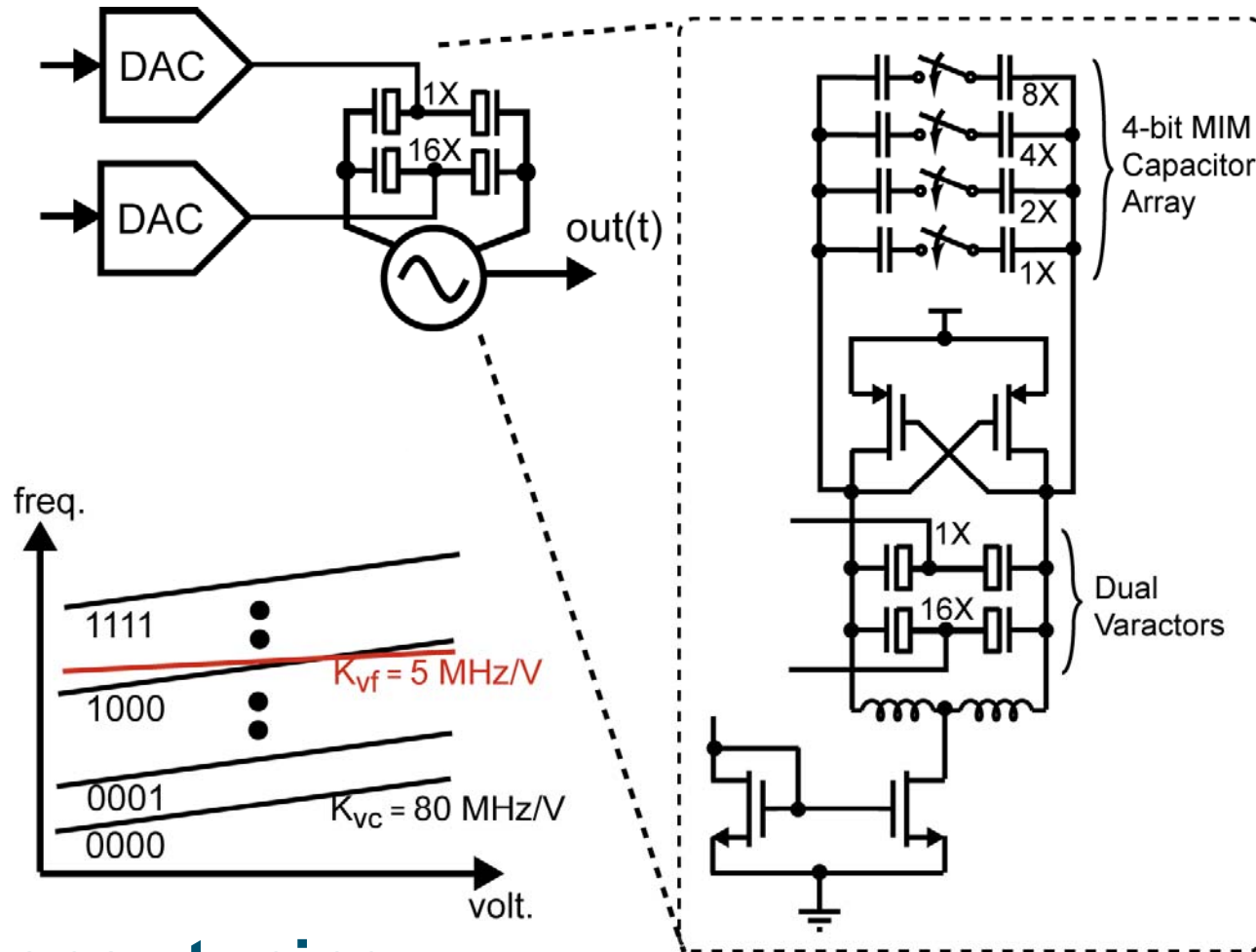

■ Frequency tuning:

- Use a small 1X varactor to minimize noise sensitivity
- Use another 16X varactor to provide moderate range
- Use a four-bit capacitor array to achieve 3.3-4.1 GHz range

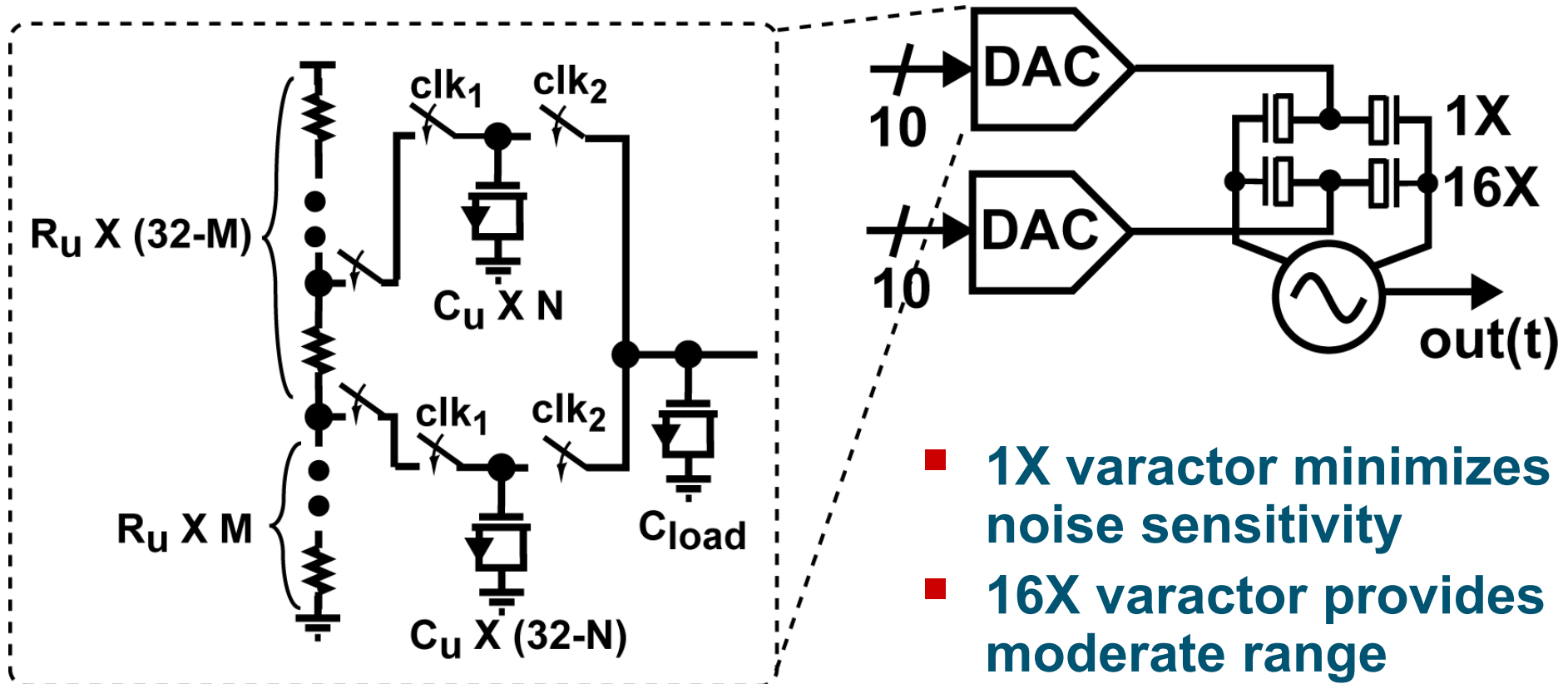Digitally-Controlled Oscillator with Passive DAC




- **Goals of 10-bit DAC**

- Monotonic
- Minimal active circuitry and no transistor bias currents
- Full-supply output range


- **1X varactor minimizes noise sensitivity**
- **16X varactor provides moderate range**
- **A four-bit capacitor array covers 3.3-4.1GHz**

Operation of 10-bit Passive DAC (Step 1)

 


- 5-bit resistor ladder; 5-bit switch-capacitor array
- Step 1: *Capacitors Charged*
 - Resistor ladder forms $V_L = M/32 \cdot V_{DD}$ and $V_H = (M+1)/32 \cdot V_{DD}$, where M ranges from 0 to 31
 - N unit capacitors charged to V_H , and $(32-N)$ unit capacitors charged to V_L

Operation of 10-bit Passive DAC (Step 2)

 


- **Step 2: Disconnect Capacitors from Resistors, Then Connect Together**
 - Achieves DAC output with first-order filtering
 - Bandwidth = $32 \cdot C_u / (2\pi \cdot C_{load}) \cdot 50\text{MHz}$
 - Determined by capacitor ratio
 - Easily changed by using different C_{load}

Dual-Path Loop Filter

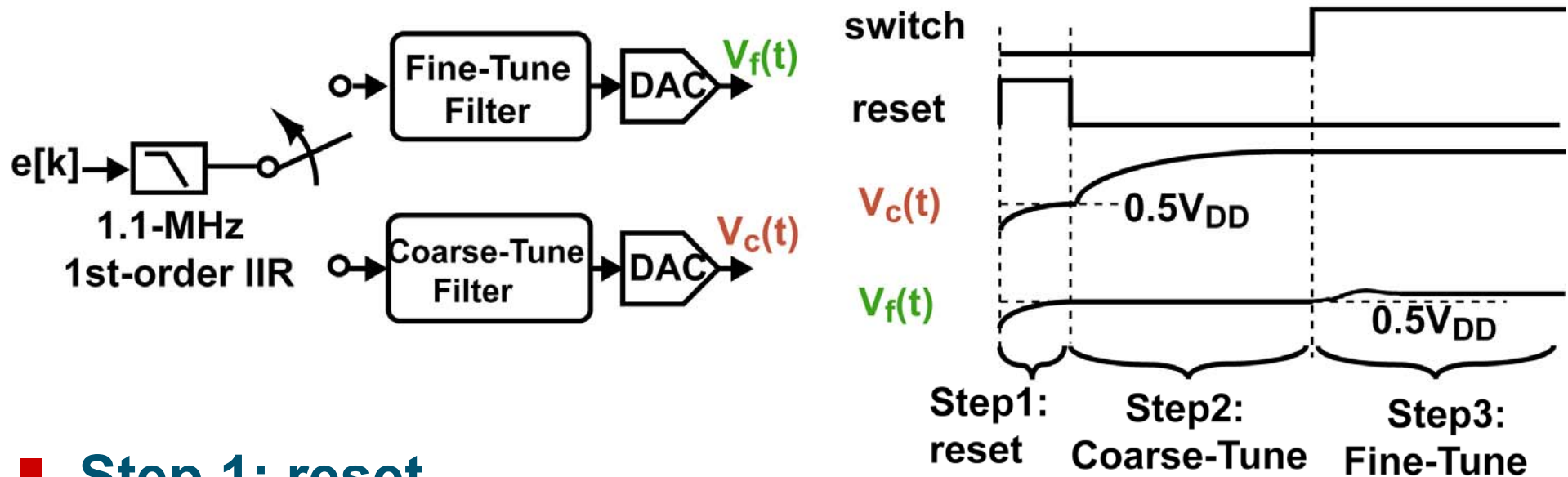


- **Step 1: reset**
- **Step 2: frequency acquisition**
 - $V_c(t)$ varies
 - $V_f(t)$ is held at midpoint
- **Step 3: steady-state lock conditions**
 - $V_c(t)$ is frozen to take quantization noise away
 - $\Delta\Sigma$ quantization noise cancellation is enabled

Fine-Path Loop Filter

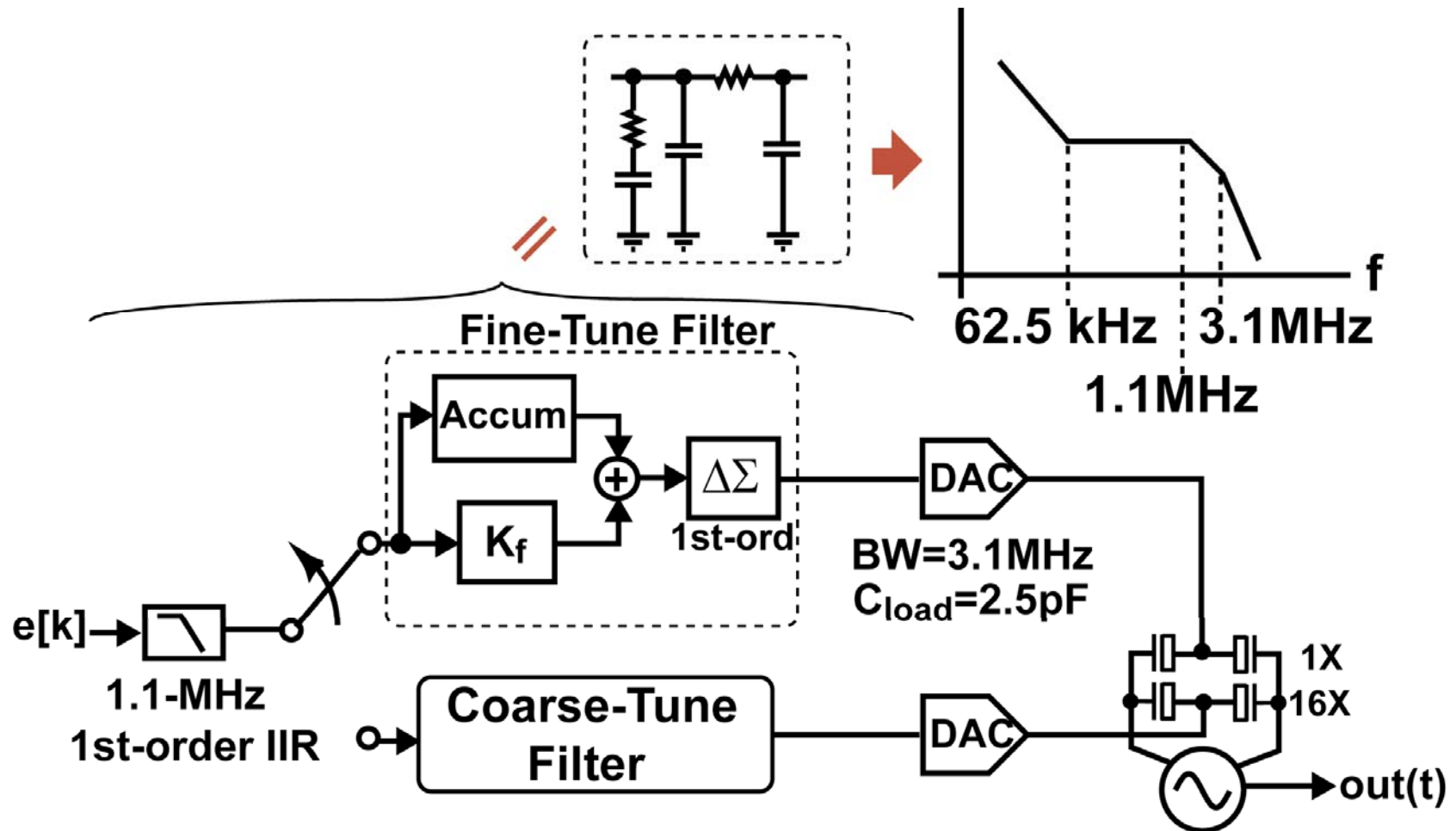


- Equivalent to an analog lead-lag filter
 - Set zero (62.5kHz) and first pole (1.1MHz) digitally
 - Set second pole (3.1MHz) by capacitor ratio
- First-order $\Delta\Sigma$ reduces in-band quantization noise

A Closer Look at the Frequency Divider

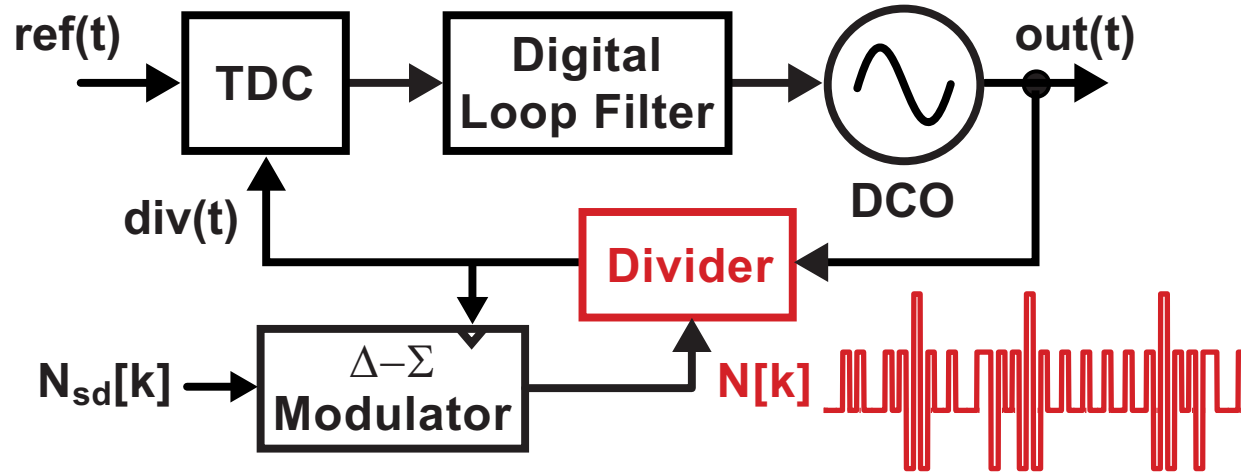


- **Delta-Sigma modulator dithers the divider value**
 - Divider must support a range of divide values
 - Want to maintain low jitter as divide value changes

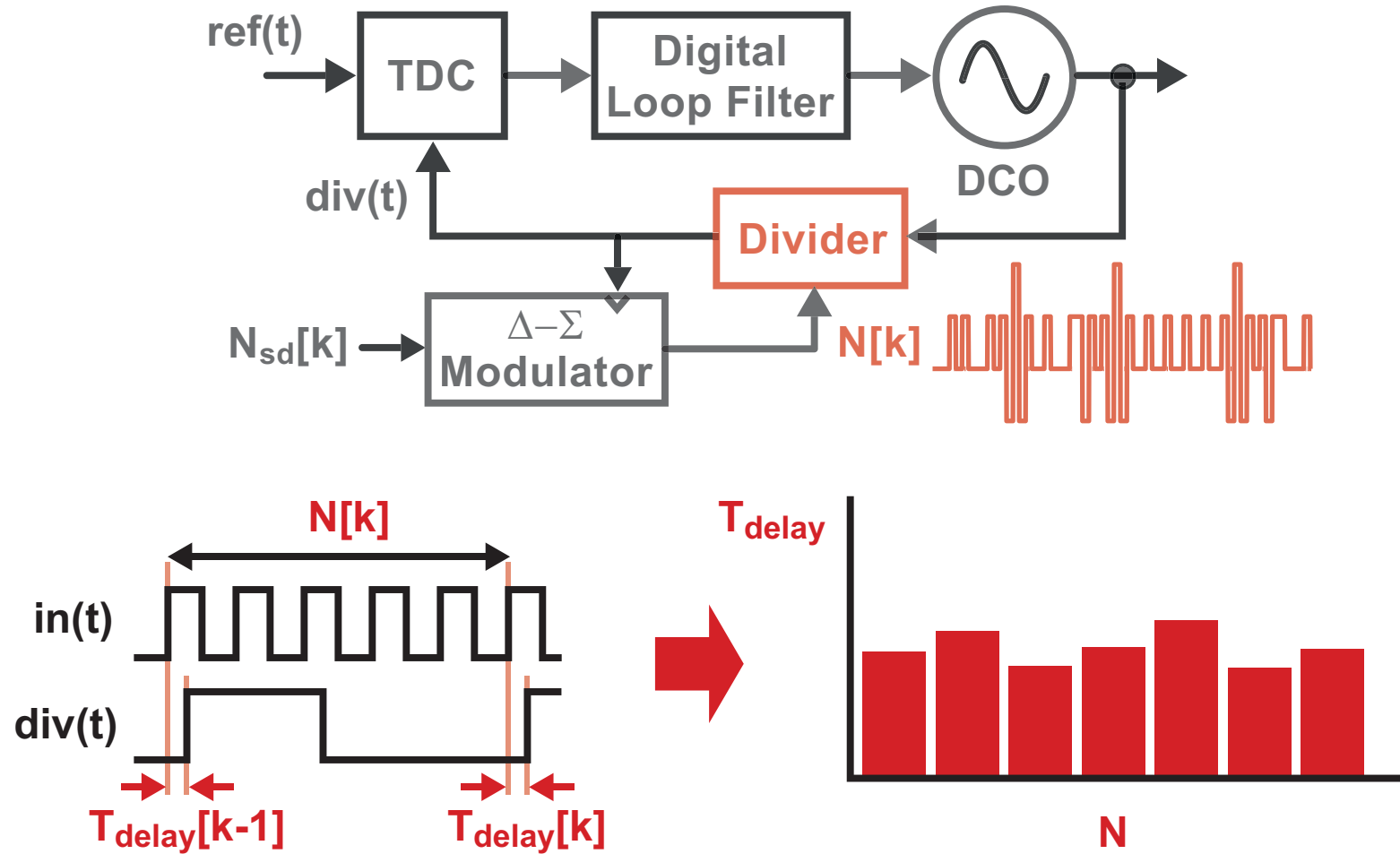The Issue of Divide Value Delay Variation




- Divider input to output delay is a function of divide value
 - ▀ Adds significant jitter for dynamic divide value variation

Key Observation

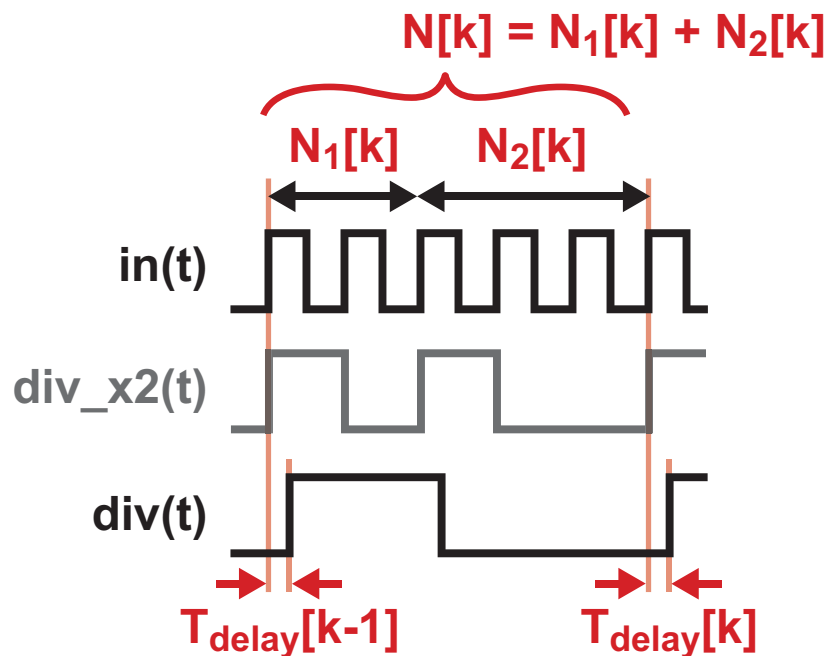


- We can realize a given divide value as the sum of lower divide values
 - Only pass select edges from higher frequency divider

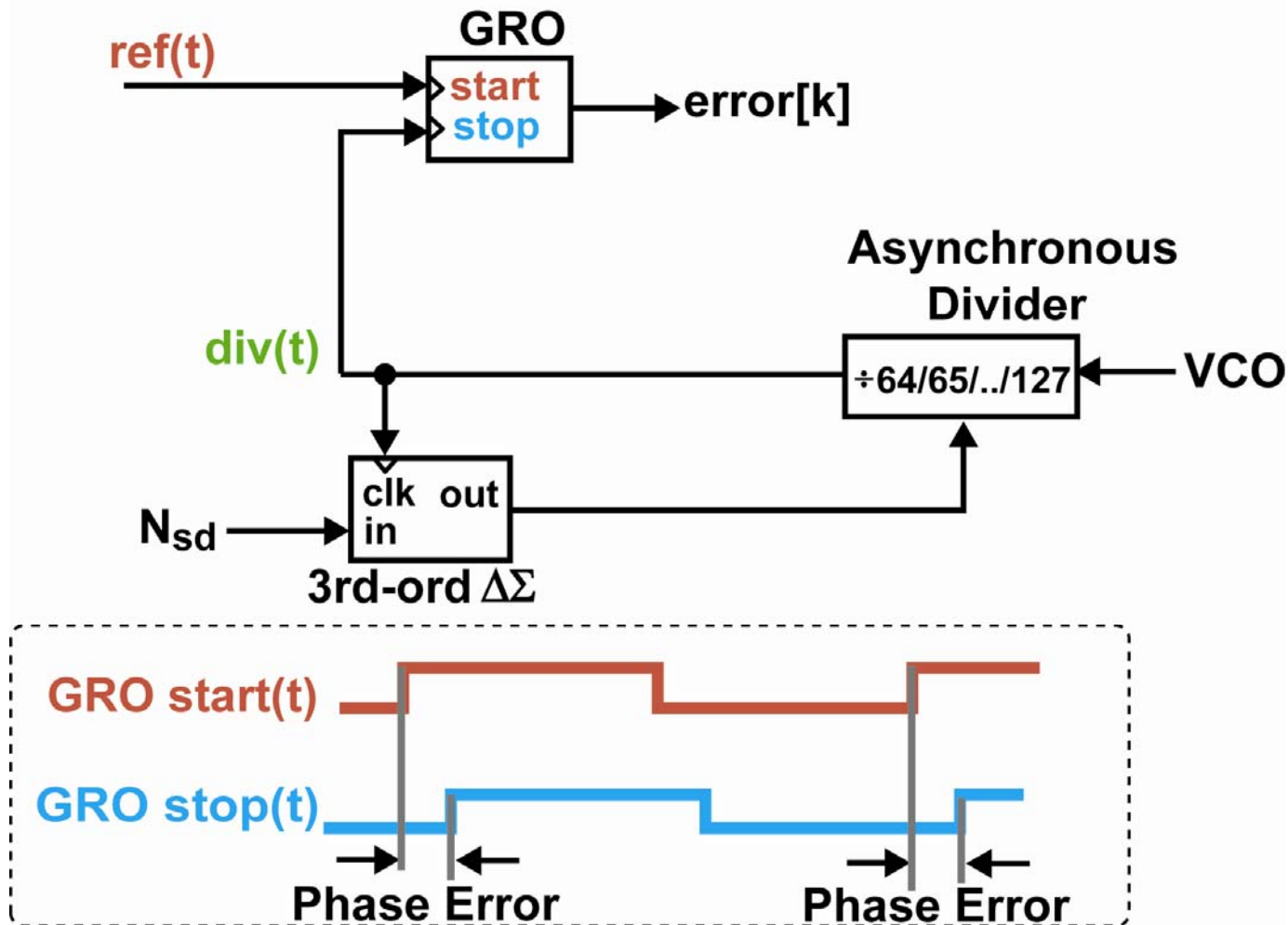Application of Divider Concept to Digital PLL



- Example: desired frequency division range is 64 to 127
 - Dithered by a third order Delta-Sigma modulator


Proposed Divider Structure

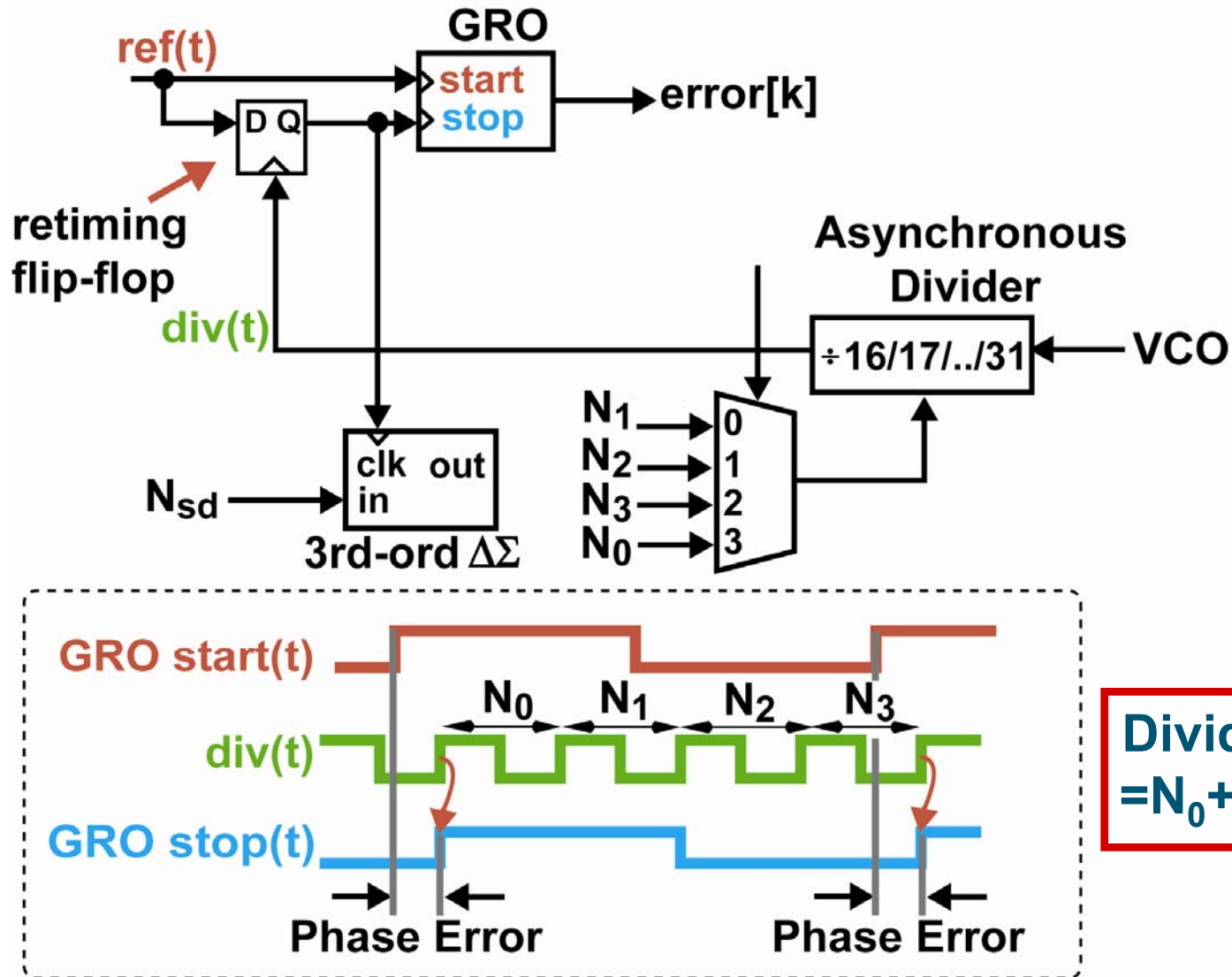

Divide value
 $= N_0 + N_1 + N_2 + N_3$


- Increase division frequency by a factor of 4
 - Only pass one of four divider edges to GRO TDC

Removal of Divide Value Delay Variation

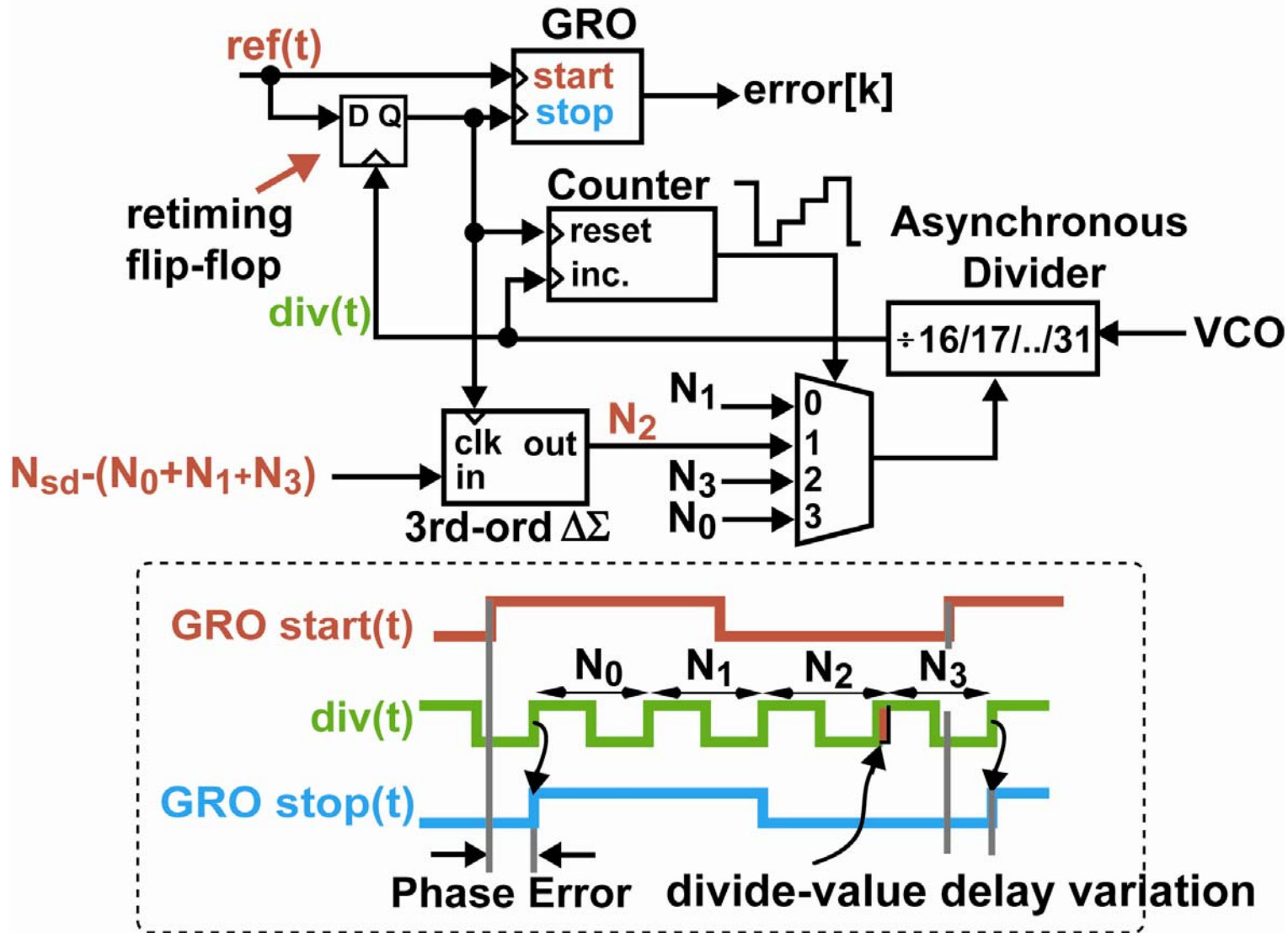

- Place $\Delta\Sigma$ dithered edge (N_2) on edge *not* passed to GRO
 - Divide value (N_3) is *constant* for edge that passes to GRO

Die Photo of Prototype

 


- 0.13- μm CMOS
- Active area: 0.95 mm²
- Chip area: 1.96 mm²
- V_{DD} : 1.5V
- Current:
 - 26mA (Core)
 - 7mA (VCO output buffer at 1.1V)

GRO-TDC:

- 2.3mA
- 157X252 μm^2


Power Distribution of Prototype IC

 

Total Power: 46.1mW


- Notice GRO and digital quantization noise cancellation have only minor impact on power (and area)

Measured Phase Noise at 3.67GHz

 

- Suppresses quantization noise by more than 15 dB
- Achieves 204 fs (0.27 degree) integrated noise (jitter)
- Reference spur: -65dBc

Calculation of Phase Noise Components

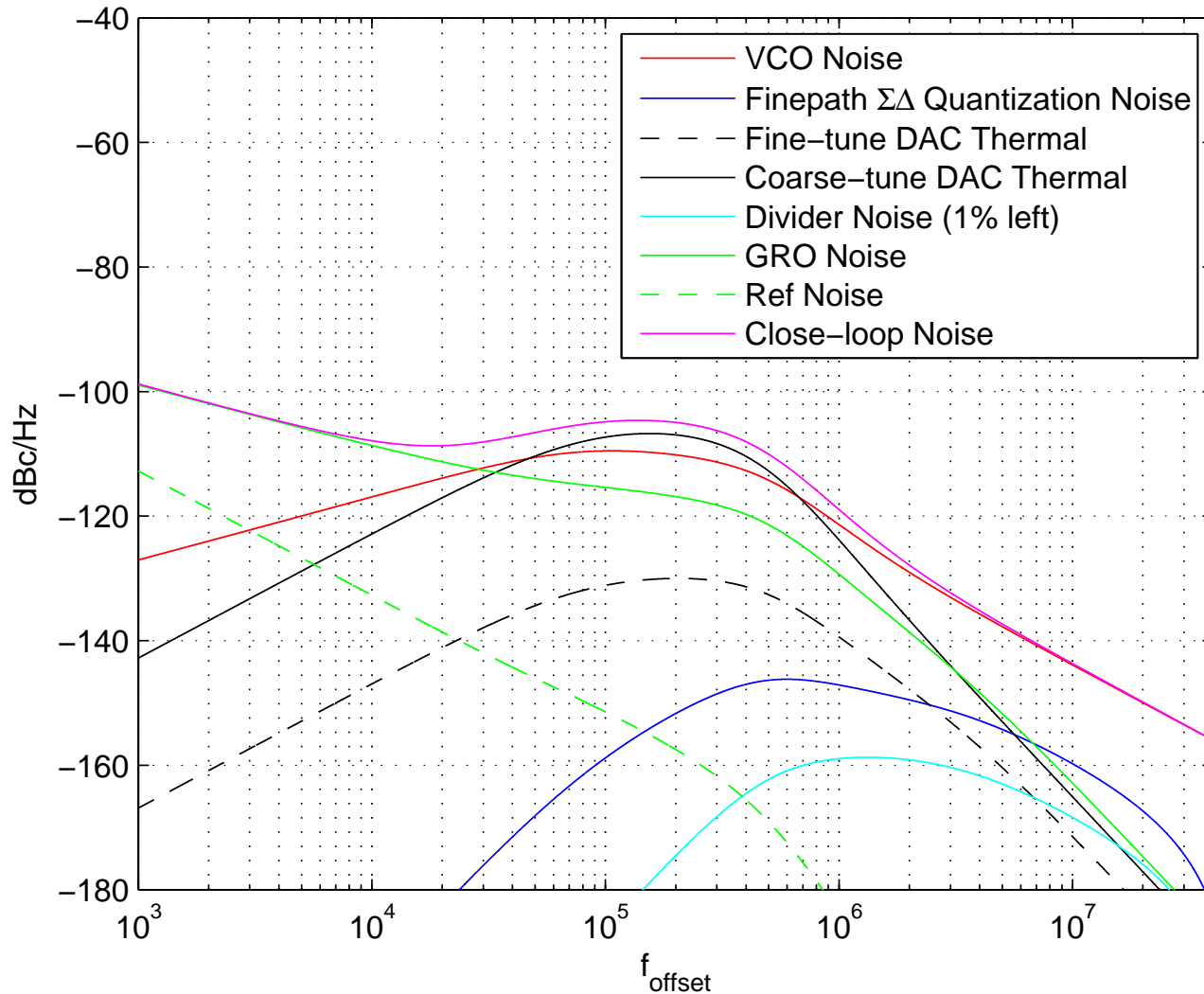

- See wideband digital synthesizer tutorial available at <http://www.cppsim.com>

Conclusions

- **Digital Phase-Locked Loops look extremely promising for future applications**
 - Very amenable to future CMOS processes
 - Excellent performance can be achieved
- **A low-noise, wide-bandwidth digital $\Delta\Sigma$ fractional-N frequency synthesizer is achieved with**
 - High performance *noise-shaping* GRO TDC
 - Quantization noise cancellation in *digital* domain
- **Key result: < 250 fs integrated noise with 500 kHz bandwidth**

Innovation of future digital PLLs will involve joint circuit/algorithm development