


Overview

- Sigma-Delta Basics
 - Theory
 - General characteristics
 - Design methods
 - Recent activity
- Genetic Algorithm based analysis method


What is a Sigma-Delta

- ADC architecture that uses oversampling and shaping of the quantization noise out of the signal band to trade resolution for bandwidth
- Uses digital filtering of output to remove out of band quantization noise
- Applicable for effective sample rates in the KHz to low MHz ranges
- CMOS friendly

First-Order Sigma-delta



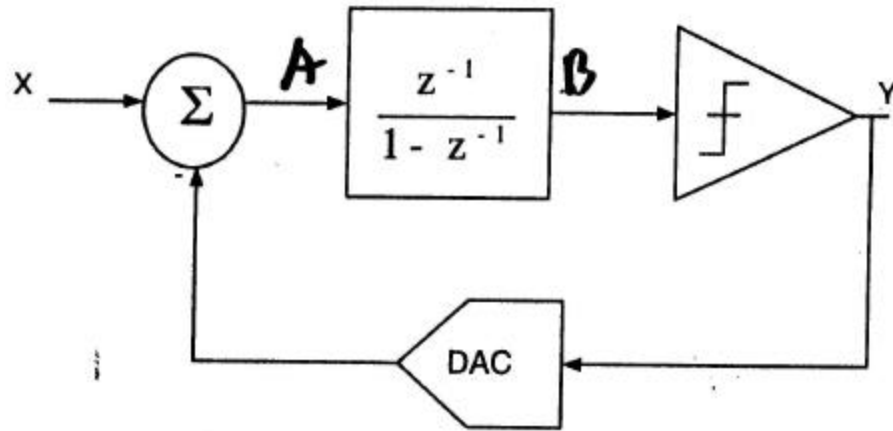

 
$$B = A \frac{z^{-1}}{1-z^{-1}}$$
$$B = A z^{-1} + B z^{-1}$$



$$Y(z) = z^{-1}X(z) + E(1-z^{-1})$$

Quantization Error Becomes Noise

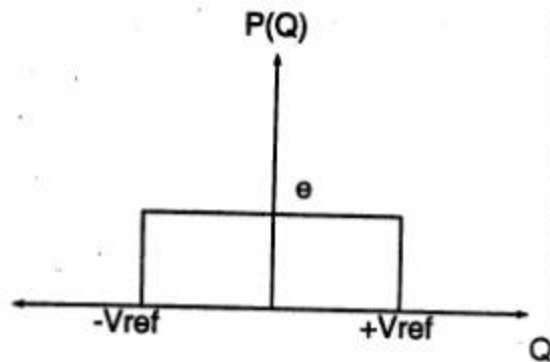  

$$Q^2_{rms} = \frac{1}{2V_{ref}} \int_{-V_{ref}}^{+V_{ref}} e^2 de = \frac{1}{3} V_{ref}^2$$

Noise power


$$E(z) = Q_{rms} \sqrt{\frac{2}{f_s}} = \sqrt{\frac{2}{3}} V_{ref} \sqrt{T_s} = V_{ref} \sqrt{\frac{2T_s}{3}}$$

Spectral density

$$N(f) = E(1 - z^{-1}) = 2V_{ref} \sqrt{\frac{2T_s}{3}} \sin(\pi f T_s)$$

Shaped by NTF


NTF for Higher Order Modulators

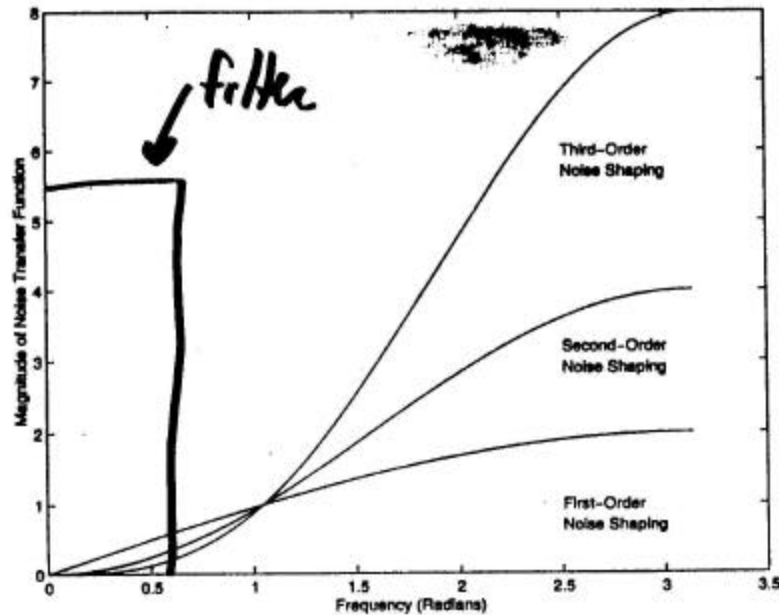


$$Y(z) = z^{-1}X(z) + E(1 - z^{-1})^L$$

$$\# \text{ Bits} = (L + 0.5) \log_2 \text{OSR} - \log_2 \left[\frac{\pi^L}{\sqrt{2L+1}} \right] + \log_2 (2^Q - 1)$$

TFOC

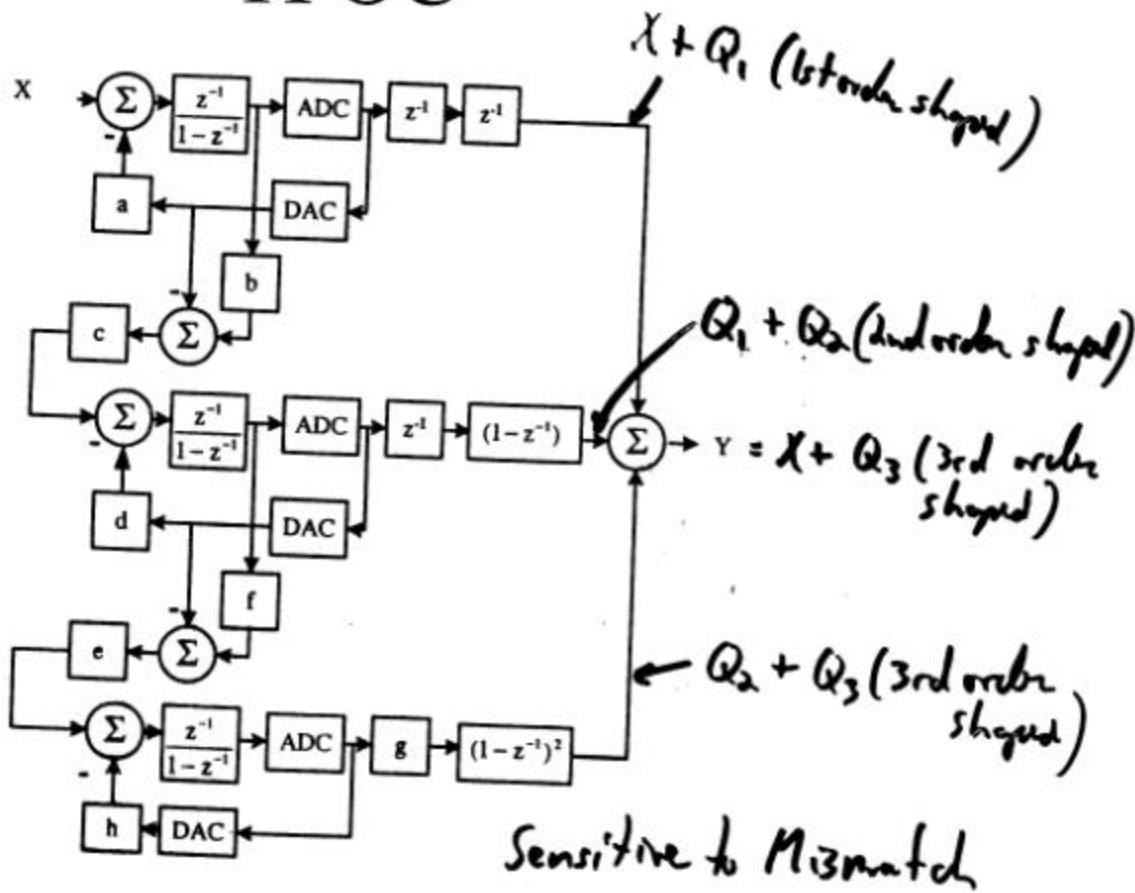

Single Loop

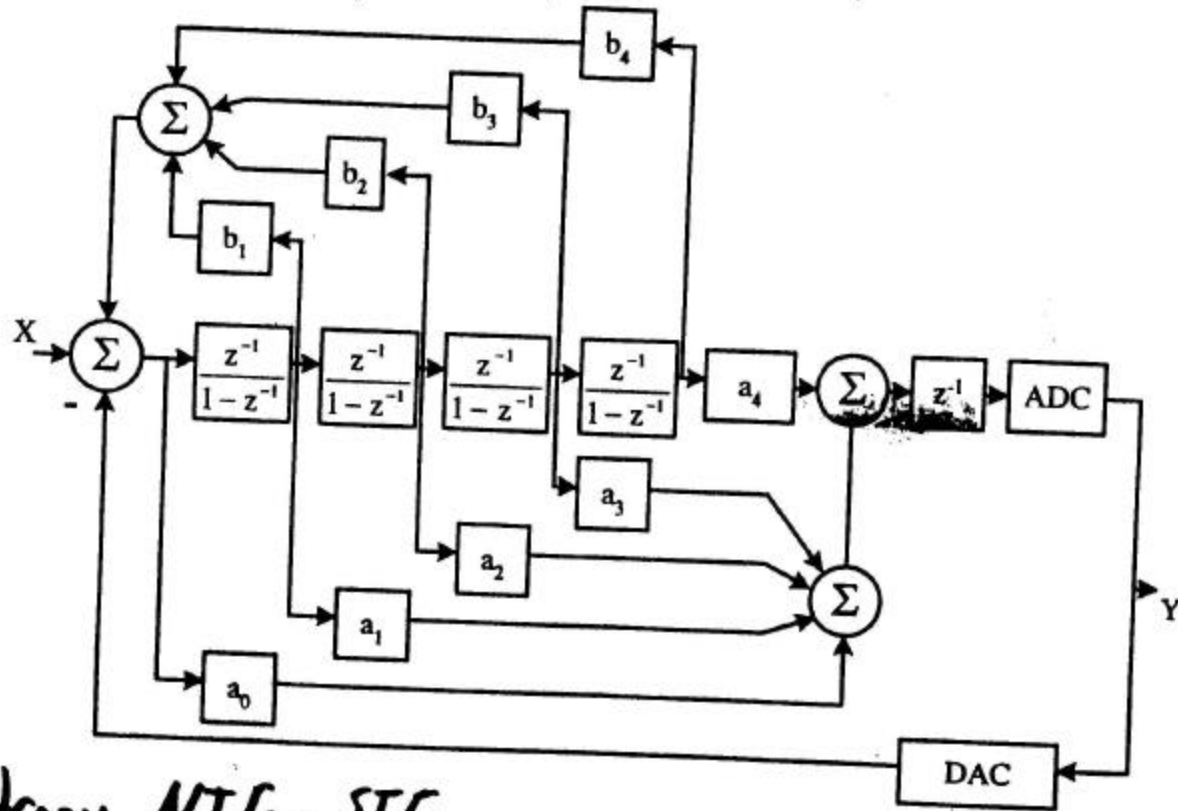


Arbitrary NTF, STF
Complex
Large ratios


Conditionally Stable

SOFOC1

Second Order

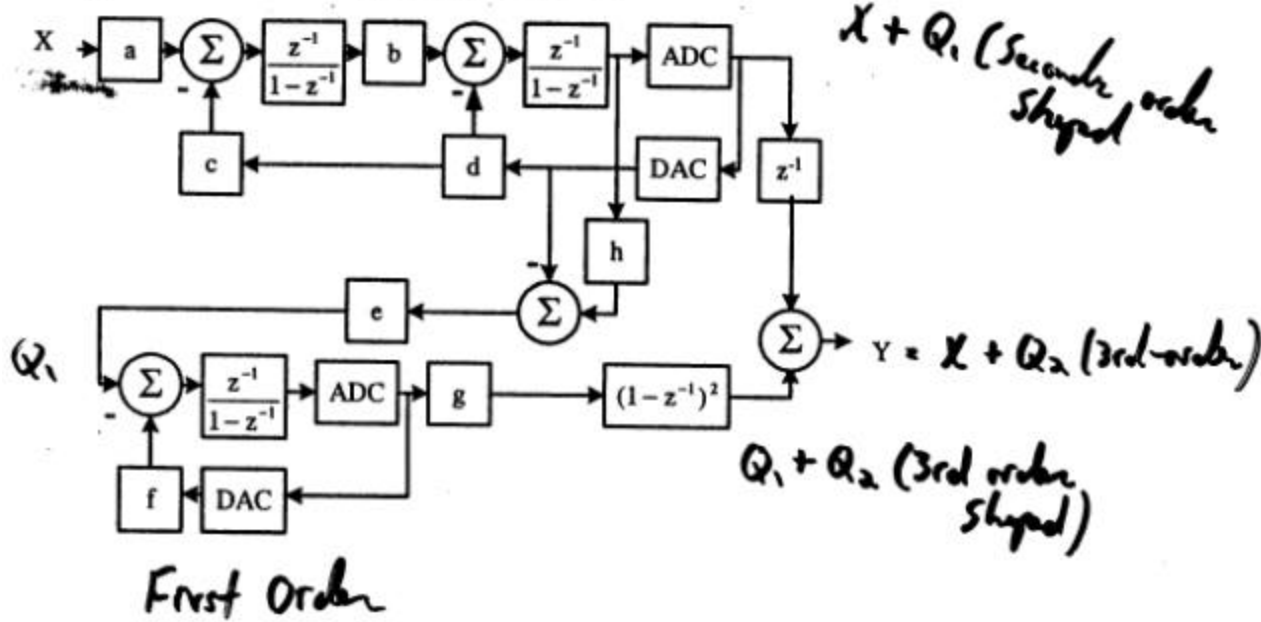

SOFOC2

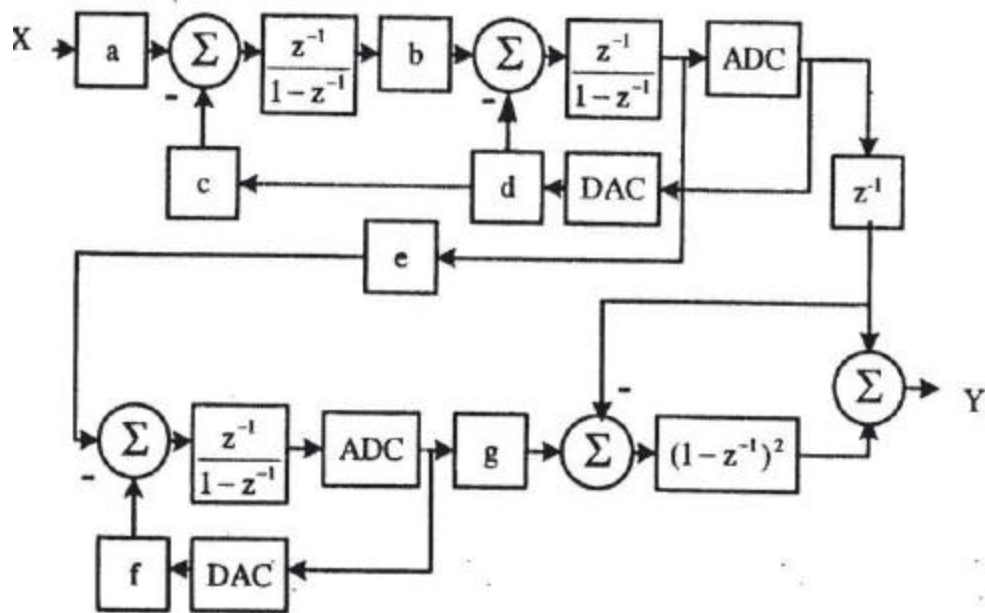

General Characteristics

- Very high resolution – 24-bits not uncommon
 - Use FETs and capacitors – 1% matching on caps
 - No special anti-aliasing filters needed
 - First integrator dominates performance
 - Noise (flicker and thermal)
 - Settling
 - Gain
 - offset
 - Very tolerant to comparator characteristics
 - Opamp gains on order of OSR
 - No missing codes
 - High linearity
 - Inputs overload modulator (SNR/SDR plummet) as input approaches V_{ref} – some architectures do not recover well
 - Idle-channel tones are inherent – dithering eliminates
-

Design Methods

- Numerical simulation in C, Matlab, etc. to explore architecture and sensitivity to non-idealities
- Simulations of integrators
- Simulations of modulator and FFT output bit-stream – time consuming
- Integrator characteristic table based methods help

Recent Activity

- A 12mW ADC Delta-Sigma Modulator With 80dB of Dynamic Range Integrated in a Single Chip Bluetooth Transceiver
- A 1.8V Delta-Sigma Modulator Interface for an Electret Microphone With On-Chip Reference
- A 5mW Sigma-Delta Modulator With 84dB Dynamic Range for GSM/EDGE
- A Wideband CMOS Sigma-Delta With Incremental Data Weighted Averaging
- A 13.5mW 185Msps Delta-Sigma Modulator for UMTS/GSM Dual-Standard IF Reception
- A 2.5V Sigma-Delta Modulator for Broadband Communications Applications
- A Fourth-Order Bandpass Delta-Sigma Modulator Using Second-Order Bandpass Noise-Shaping Dynamic Element Matching
- A 1V 10MHz Clock Rate 13-bit CMOS Delta-Sigma Modulator Using Unity Gain Reset Opamps
- A 113dB DSD Audio ADC Using a Density Modulated Dithering Scheme
- A 10-300MHz IF-Digitizing IC With 90-105dB Dynamic Range and 15-333KHz Bandwidth
- A 3.3mW Sigma-Delta Modulator for UMTS in 0.18um CMOS With 70dB Dynamic Range in 2MHz Bandwidth
- A 64MHz Clock Rate Sigma-Delta ADC with 88dB SNDR and -105dB IM3 Distortion at 1.5MHz Signal Frequency
- A 0.7V MOSFET-Only Switched Opamp Sigma-Delta Modulator in Standard Digital CMOS Technology
- Superconducting Bandpass Delta-Sigma Modulator With 2.23GHz Center Frequency and 42.6GHz Sampling Rate

Low-Power, Multi-bit with DEM, Non switched-cap are current areas of interest

Quiz

- Sigma-Delta are attractive because
 - It is a cool fraternity
 - It is used in telecommunications
 - It is easily integrable in CMOS
 - It requires no analog design

Quiz

- Sigma-Delta can be difficult to design because
 - Computers are not big enough or fast enough
 - They are non-linear circuits with no closed form solution
 - They use capacitors
 - No one really knows how they work


Quiz

- Which limits Sigma-Delta distortion most
 - Capacitor non-linearity
 - Integrator settling
 - Finite opamp gain
 - Comparator offset
 - noise

Research Objective

- Advance Σ - Δ Design and Test Methods
- Improve Design Methods for Automated Optimization of Σ - Δ
- Provide Insight into the Critical Integrator Non-Linearities which Degrade Σ - Δ Performance
- Develop Signal-to-Distortion Ratio (SDR) and Signal-to-Noise Ratio (SNR) Prediction Methods for Improved Σ - Δ Design and Test

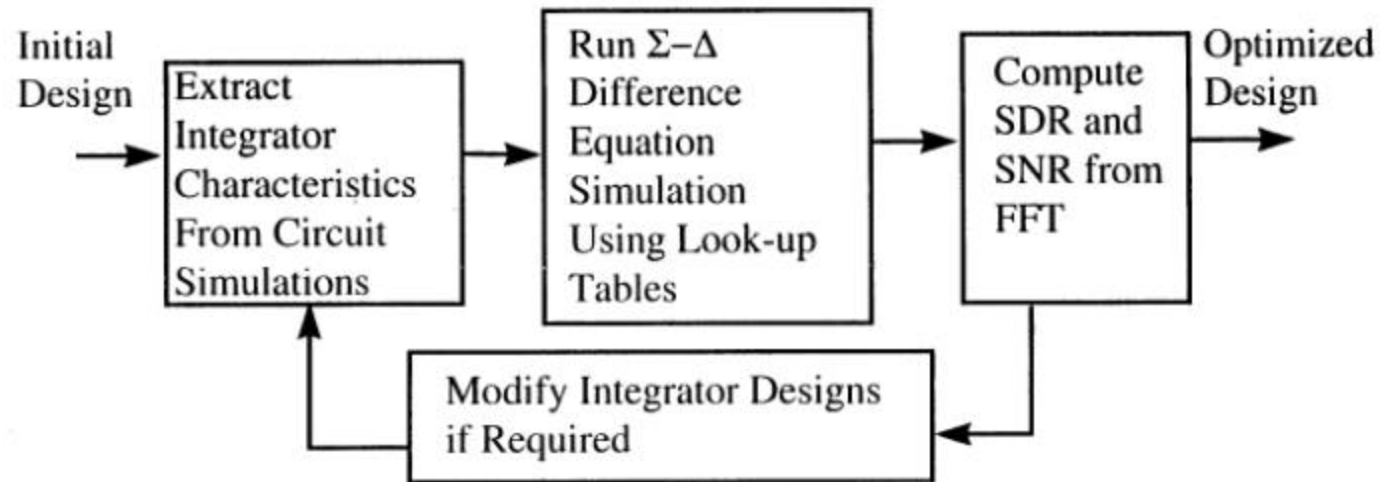Limitations of Current Methods for Σ - Δ Design Optimization





- Requires Σ - Δ Difference Equation Simulation and FFT for Many (64K) Clock Cycles
- Integrator Design Modification Guided by Performance Gradients Only
- Look-up Table Data Cannot Directly Guide Design Optimization


Techniques Employed

- **Non-Linear Integrator Model**
 - Models Realistic Integrator Non-Linearities
 - Accurately Represents Integrator Transfer Function Compared to SPICE Simulation
 - Captures Nature of Non-Linearities; Aids in Guiding Design Optimization
- **Multi-Parameter Sampling Methods**
 - Linear Search Sampling
 - Improved Linear Search Sampling
 - Gibbs Sampling
- **Genetic Algorithm Surface Fit Optimizer**
 - Determine Optimal Surface Equation Terms for Predicting SDR and SNR

Approach Overview

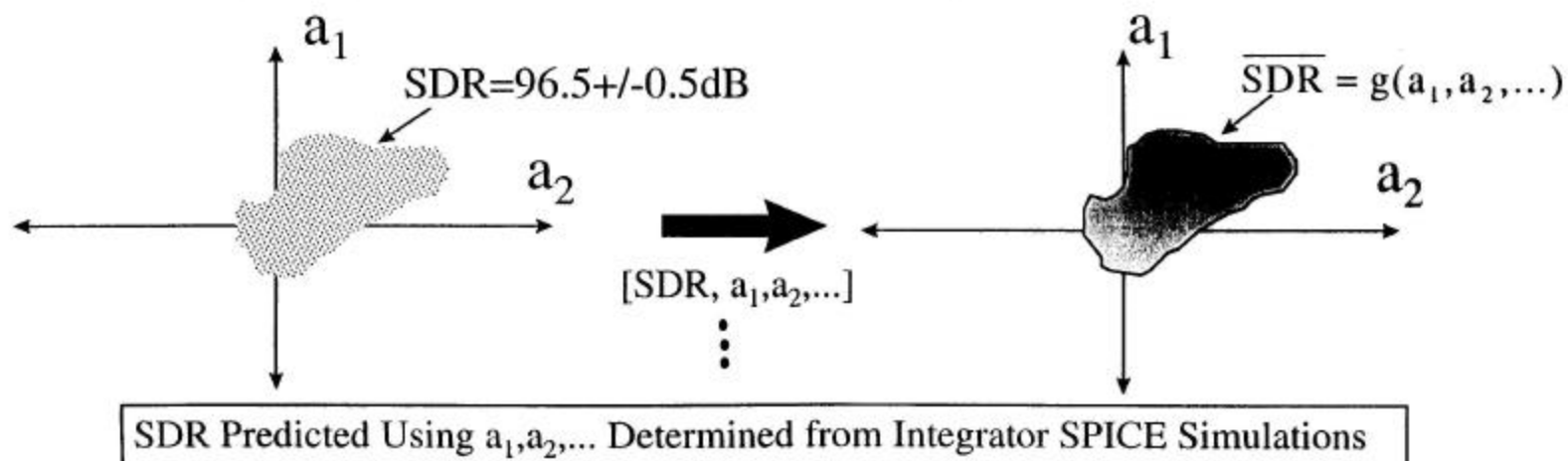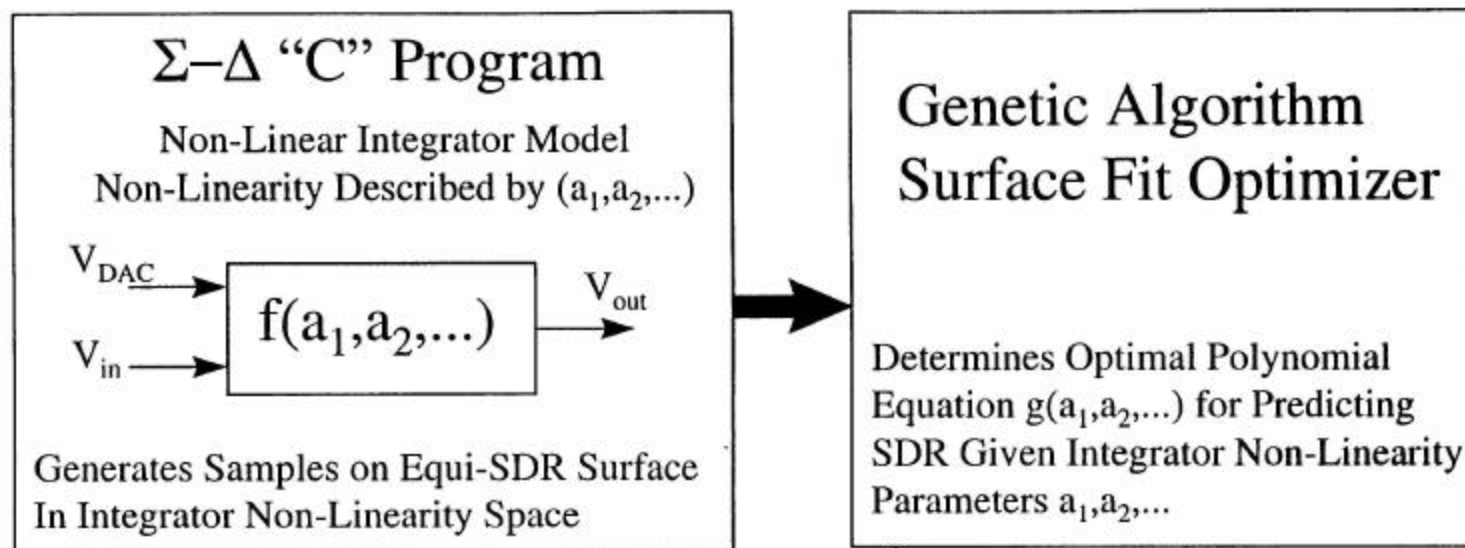


Effects of Integrator Non-Linearity

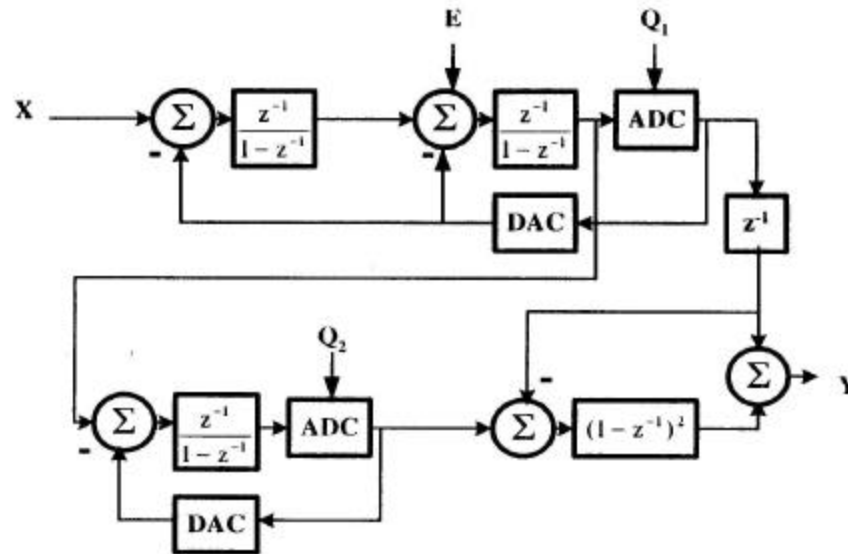

$$Y = z^{-3}X + Q_2(1 - z^{-1})^3 + E(1 - z^{-1})^2$$

- Errors Due to Integrator Non-Linearity Add Spectrally Shaped Noise
- Modulator Noise Transfer Function “Leaks” Lower Order Shaped Noise to Output
- Effects Difficult to Analyze Due to Non-Linearity of Quantizer
- Difference Equation Numerical Simulations Extensively Used to Determine SNR and SDR Performance


Switched Capacitor Integrator

 

$$V_{out} = \frac{C_A}{C_F} V_{in} - \frac{C_B}{C_F} V_{ref} + V_{out} z^{-1}$$

- Effects Such as Non-Linear Capacitors and Channel Charge Injection from Sampling Switches Contribute to Sampling Related Non-Linearity
- Incomplete Settling and Opamp Non-Linearity Contribute to Integration Related Non-Linearity
- These Non-Linearities Degrade SDR and SNR


New Integrator Model

 

$$f_1 = f(a_1, a_2, n_3)$$
$$f_2 = f(a_4, a_5, a_6, a_7)$$


- Numerical Model for Use in “C” Program Difference Equation Σ - Δ Simulator
- Add Non-Linearity to Ideal Integrator
- Sampling Related Non-Linearity $f_1(V_{in})$
- Integration Related Non-Linearity $f_2(V_{in} - V_{DAC})$
- Parameters of f_1 and f_2 are a_1, a_2, \dots

Model Testing

 


- Three Integrators Simulated to Obtain Model Coefficients for Eight Case Screening DOE (Seven Process and Environmental Factors)
- Aggregate Error of Less Than $10\mu\text{V}_{\text{rms}}$ in Fit to Simulation Data
- Coefficients of f_1 Substantially Larger for Single Ended Input Cases from DOE - Reflect Even Ordered Harmonics Due to Capacitor Non-Linearity
- Coefficients of f_2 Substantially Larger for Low Bias Current, High Capacitance, and High Temperature Case in DOE - Reflects Slow Settling

SOFOC2 With Non-Linear Integrators

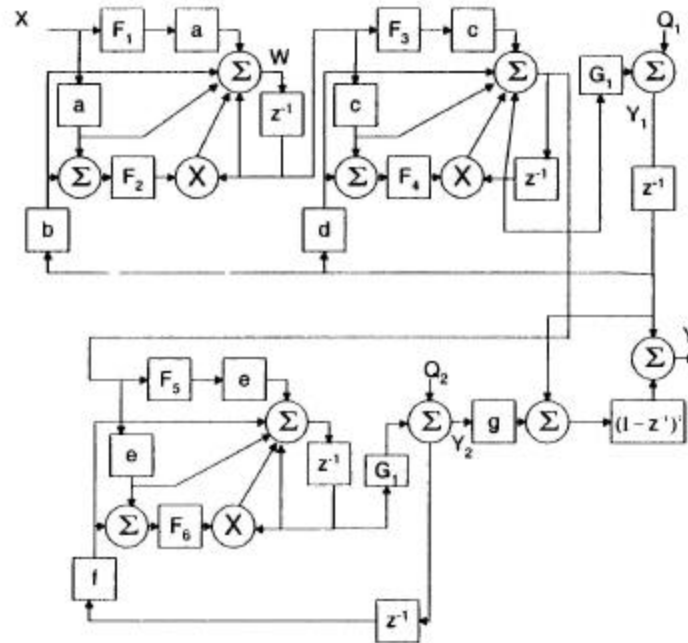


$$\begin{aligned}
 Y &= gQ_2(1 - (1 + F_6)z^{-1})(1 - z^{-1})^2 \\
 &+ Q_1z^{-1} \left[(1 - (1 + F_4)z^{-1})(1 - (1 + F_2)z^{-1}) - (1 - z^{-1})^2 \right] \\
 &+ Xz^{-3} + F_1z^{-3} + G_1F_3z^{-1}(1 - (1 + F_2)z^{-1}) + G_2eF_5(1 - z^{-1})^2
 \end{aligned}$$

Linear Search Sampling

 


- Sample Space of Coefficients (a_1, a_2, \dots) of f_1 and f_2 for Integrators
- Monte Carlo Based Linear Search Sampling Method
- Random Vector Chosen in Coefficient Space of f_1 and f_2 for the Integrators in Difference Equation Σ - Δ Simulator
- Vector Extends or Contracts Until SDR/SNR Near Goal
- 2000 Modulator Instances - Integrator Non-Linearity Coefficients (a_1, a_2, \dots) and Resulting SDR/SNR

Improved Linear Search Sampling

 


- Applies Random Weight to f_1 and f_2 Before Linear Search
- Increases Sampling Along Minor Axis
- Allows Less Sensitive Parameters to Impact SNR and SDR Improving Their Representation in the Sampled Data

Gibbs Sampling

 


- Markov Chain Monte Carlo Sampling Method
- Uses Prior Distributions and Desired SDR/SNR Distribution
- Uses Conditional PDFs of Generated Samples to Improve Likelihood that Drawn Samples are From Desired Distribution
- Converges to Desired Distribution (Metropolis and Hastings)
- Modified MCSIM (Bois and Maszle) Program to Call Difference Equation Σ - Δ Simulator
- Provides Better Control Over Range of Non-Linearity Coefficients (a_1, a_2, \dots) Sampled than Linear Search Methods

Effect of FFT Length

 

512pts

 

8192pts


Surface Prediction Equation Fit

- Potentially Many Terms in Polynomial with Several Independent Variables

$$g(a_1, a_2, \dots) = B_0 + B_1 a_1 + B_2 a_2 + B_3 a_1^2 + B_4 a_2^2 + \dots$$

- Desire Minimum Number of Terms in Prediction Equation
- Genetic Algorithm Implemented to Determine Optimal Terms for Prediction Equation (Shen and Chen)

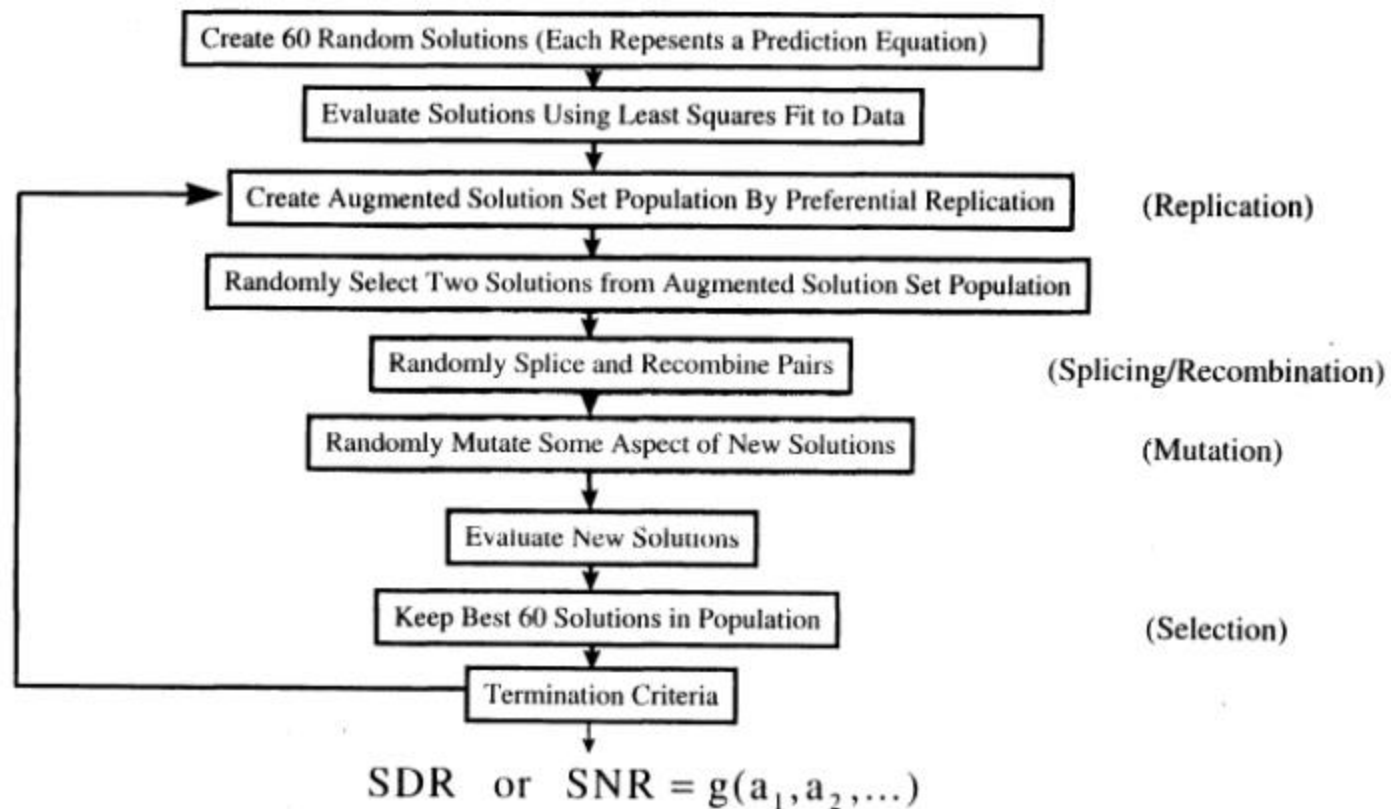Genetic Algorithm Prediction Equation Fit




Each Solution Consists of a String of Ones and Zeros Representing the Set of All Possible Terms in Prediction Equation (1=Include, 0=Exclude)

SDR Prediction Equation Terms

Term	Coefficient
a_{11}	-0.029
a_{12}	-0.006
a_{13}	0.050
a_{15}	0.009
a_{17}	-0.004
a_{11}^2	7.300
a_{12}^2	5.758
a_{13}^2	9.972
a_{14}^2	0.004
a_{16}^2	0.002
a_{17}^2	0.001
$a_{11}a_{12}$	-0.003
$a_{11}a_{13}$	-12.701
$a_{11}a_{14}$	0.098
$a_{11}a_{16}$	-0.249
$a_{12}a_{15}$	-0.025
$a_{12}a_{17}$	0.110
$a_{13}a_{14}$	-0.091
$a_{13}a_{16}$	0.201
$a_{13}a_{17}$	0.001
$a_{14}a_{16}$	-0.002

a_{11}, a_{12}, a_{13}
Sampling related
errors in 1st integrator

SDR Prediction Equation Accuracy

 


- Tested with 2000 Modulators with Randomly Chosen f_1 and f_2 Coefficients (a_1, a_2, \dots) Generated Using “C” Program Difference Equation Simulator (Ranged 87dB to 111dB)
- Linear Search Sampling Makes Gross SDR Prediction Errors (10dB)
- Improved Linear Search Sampling and Gibbs Sampling Predict SDR with +/-0.5dB Accuracy When Non-Linear Relationship Compensated
- Optimal Prediction Equation is a Strong Function of Input Sampling Non-Linearity of First Integrator

SOFOC2 Σ - Δ Test Circuit

- SOFOC2 Third Order Σ - Δ Test Circuit Designed and Fabricated in AMI 0.6 μ m CMOS Process
- 16-Bit Designed Performance
 - 5MHz Clock Rate (40Ksps at OSR=128)
 - SDR > 96dB
 - SNR > 96dB
- Test Modes for Measuring SDR and SNR Response to Conditions which are Expected to Degrade SDR and SNR
 - Bias Current in First and Second Integrators
 - Common-Mode Output Voltages of First and Second Integrators


SDR Versus Input Level

 

Comparison of Measured, Simulated, and Predicted SDR/SDR

- Determined (a_1, a_2, \dots) from SPICE Simulation of Integrator Circuits Used in SOFOC2 Test Chip for Various Integrator Bias Currents and Common-Mode Output Voltage
- Determine Simulated SDR/SNR Using “C” Program $\Sigma-\Delta$ Simulator with (a_1, a_2, \dots) from SPICE Simulation
- Calculate Predicted SDR/SNR from Prediction Equations Using (a_1, a_2, \dots) from SPICE Simulation
- Measure Modulator SDR/SNR for Various Integrator Bias Currents and Common-Mode Output Voltages

 SDR Response to First Integrator Common-Mode Output



- SDR Approximately 100dB Between +/-1.5 Volts
- Good Agreement Between Measured, Simulated, and Predicted SDR Versus First Integrator Common-Mode Output Voltage
- Difference at Extremes Due to Integrator Overload

Summary

- Overview of Sigma-Delta
- Method which uses
 - Multidimensional sampling
 - Genetic algorithms
- Showed first stage sampling is critical
- Demonstrated SDR prediction method is reasonably accurate with respect to simulation and measurements