



Custom IC Blocks for Enabling Digital Control in Switching Power Converters

Dragan Maksimovic and Regan Zane

July 11, 2003

Colorado Power Electronics Center
University of Colorado, Boulder



Outline

- Motivations & CoPEC directions
- “Buffalo switcher”
 - Complete 1 MHz digital PWM controller IC
 - Hybrid digital PWM
 - Delay-line A/D
- CoPEC research highlights
- Education:
 - focus on power electronics & mixed-signal IC design



Power Electronics Applications



Portable devices

- On-chip power management /mW
- Power supplies for LCD-s / hundreds of mW
- Switching voltage regulators/ up to tens of Watts

Computers and Consumers Electronics

- Power supplies for components/ several watts
- Micro-processor supplies: Voltage Regulator Modules (VRMs)/ up to hundreds of Watts
- Off-line power supplies / up to kW


Telecomm. equipment

Industrial

Automotive


Lighting (HID, fluorescent)

Aerospace

 





PDA Example: Power Management

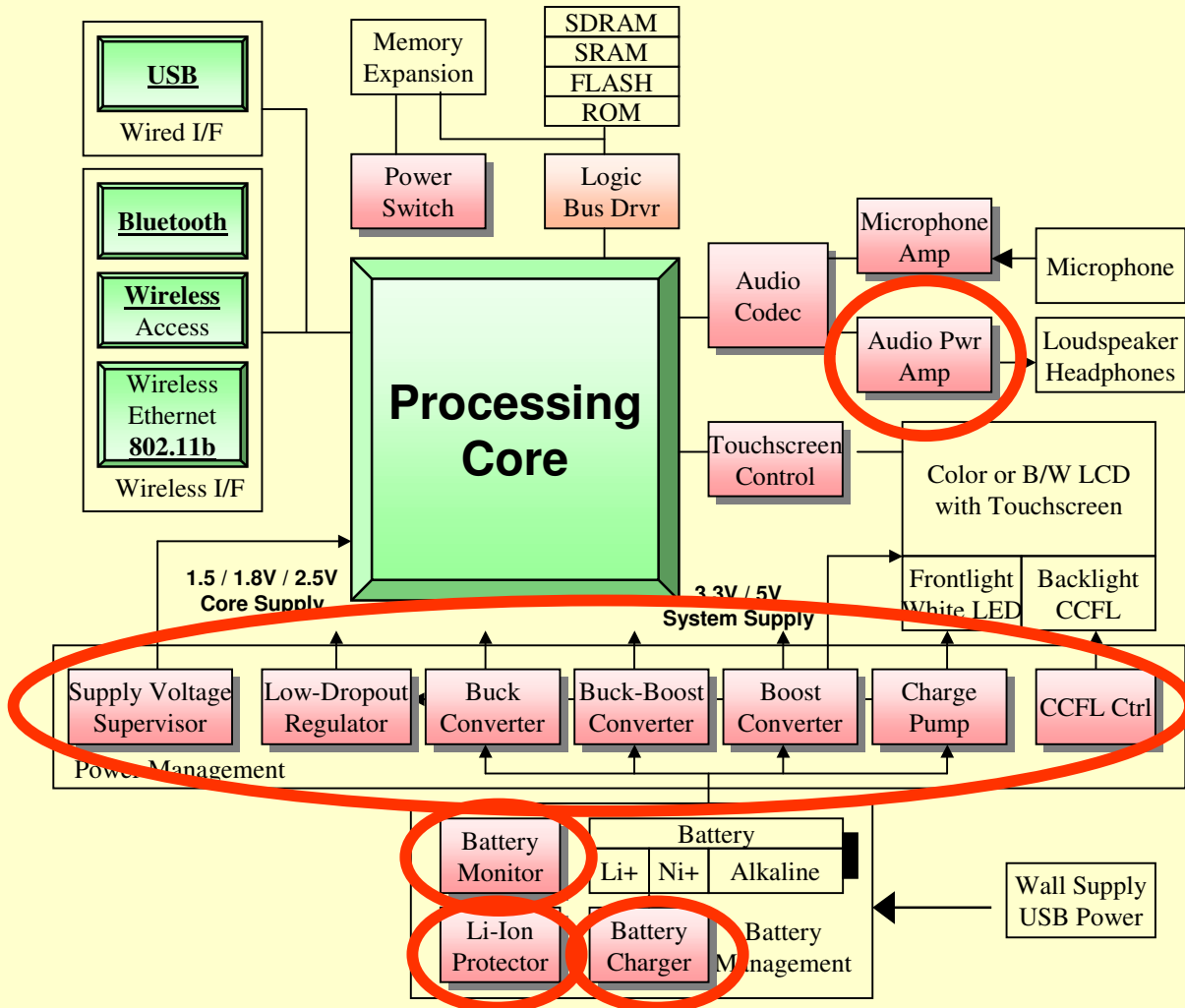



Buck Switching Converter Example

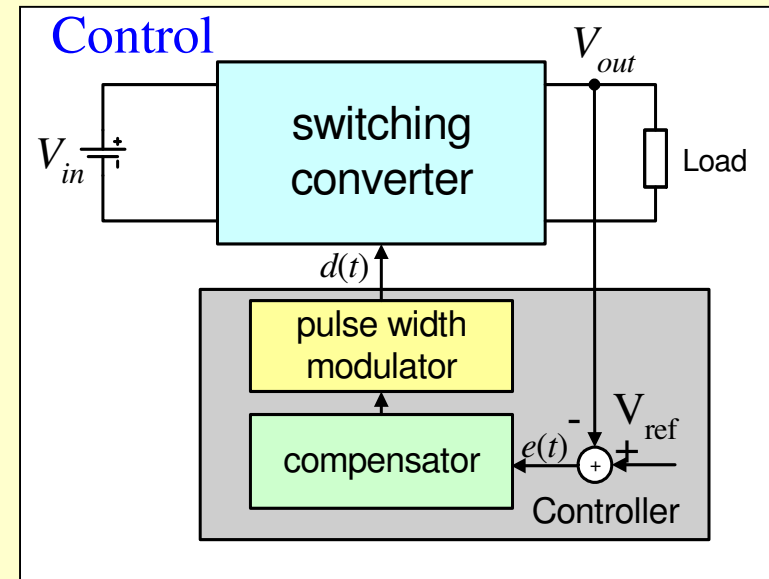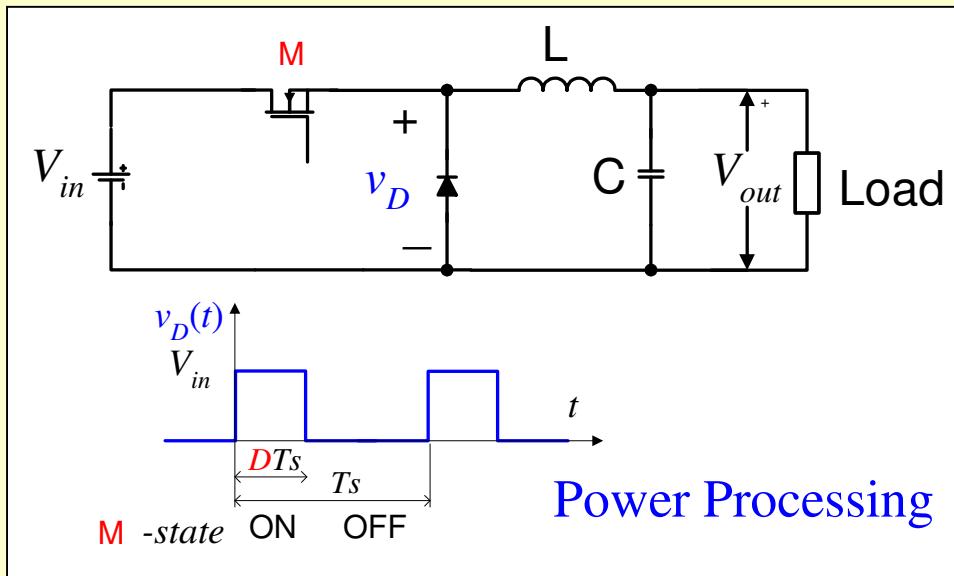

$$V_{out} = DV_{in}$$


← Duty ratio

- Switching operation controls the average value of v_D
- LC low-pass filter reduces the voltage ripple in the dc output V_{out}
- High switching frequency (hundreds of kHz to MHz), small size
- Ideally lossless, very high efficiency in practice
- Tightly regulated V_{out} through a feedback loop




Controller Implementation: Analog vs. Digital

Analog Implementation

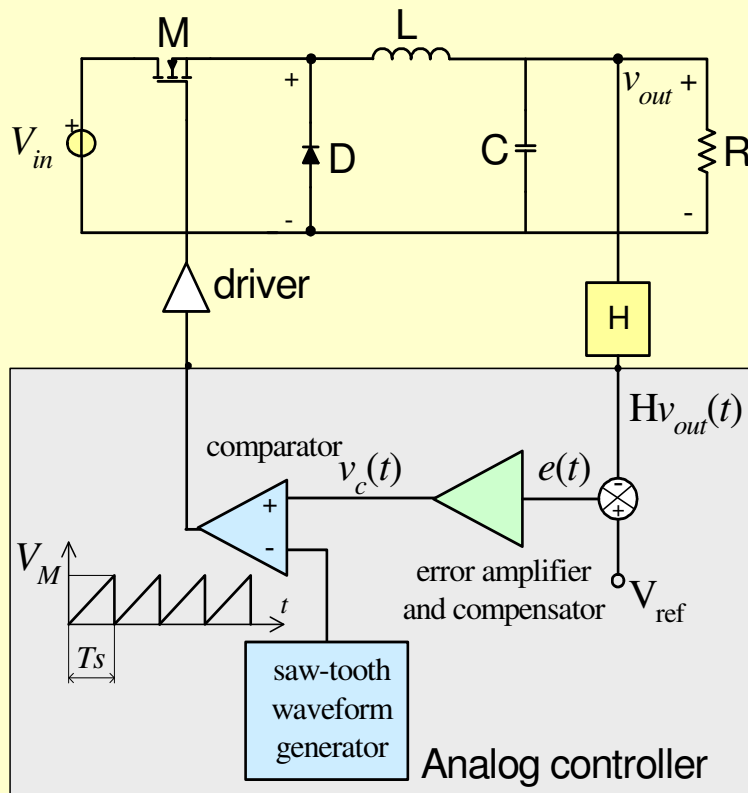

Digital Implementation

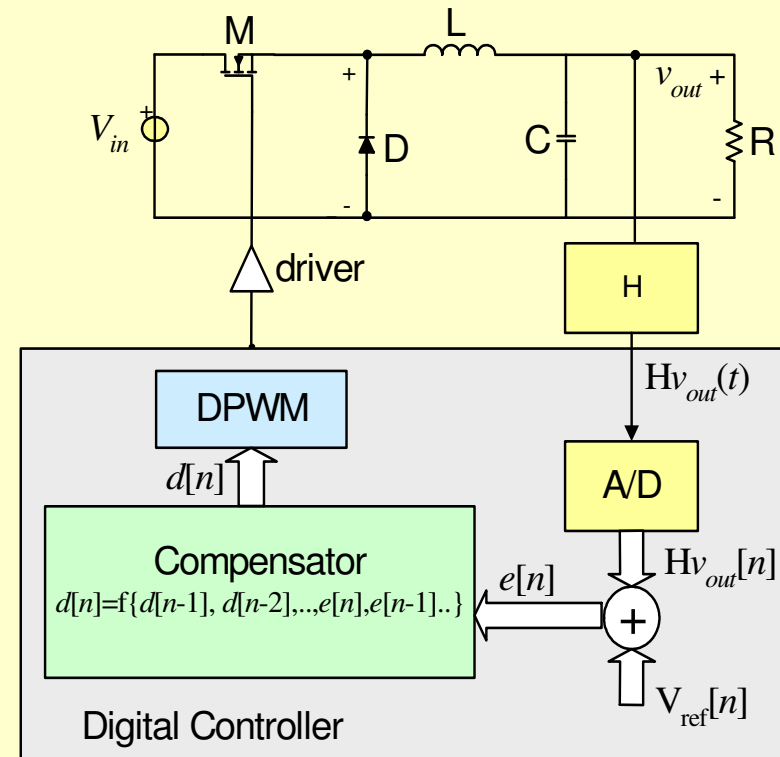




Research Motivation – Why Digital?

- Analog PWM controllers (30 year old technology)
 - Simple, low-cost
 - Well established design practices
- What can be accomplished with digital control in power electronics applications?
 - Programmability (e.g. one controller can serve a much wider range of applications)
 - Elimination or reduction of the number of passive components
 - System integration (e.g. dynamic voltage scaling), diagnostics, etc.
 - Static and dynamic performance (e.g. through adaptive control techniques)
 - Reduced sensitivity to tolerances, process and temperature variations
 - Reduced cost



Practical Limitations

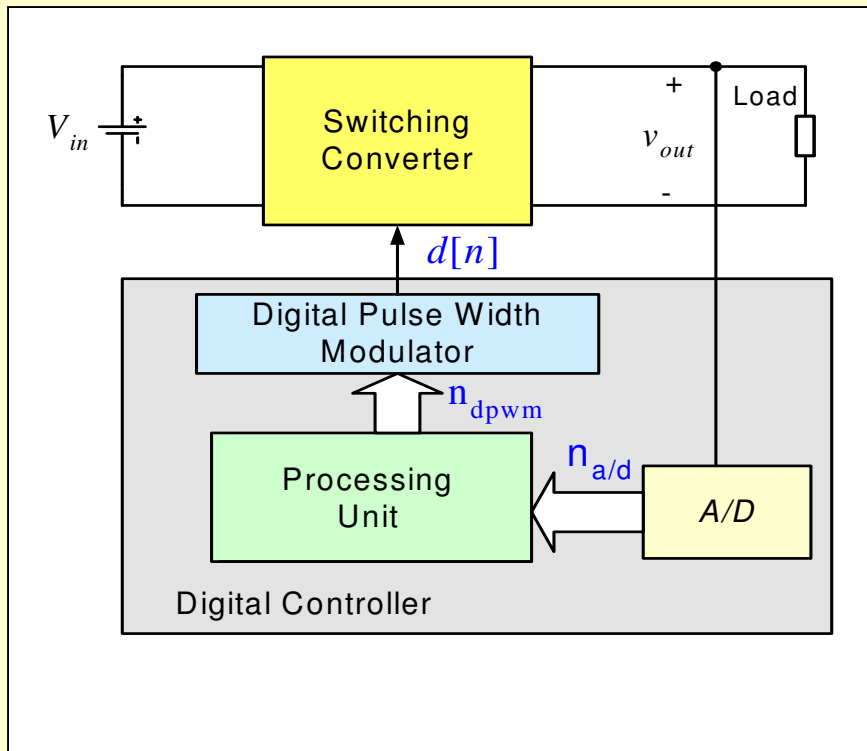

- **A/D** – A complete analog controller could be simpler than a high-speed, high-resolution A/D
- **Processing unit** - Available microcontroller/DSP systems are still too slow, or too complex/costly
- **DPWM** – High-speed/ High-resolution (ns) digital pulse width modulators are needed

New design and implementation approaches for all functional blocks are needed



CoPEC Research Program


CoPEC

Power Electronics and Mixed-Signal IC Design

New SMPS-specific controller building blocks

New converter configurations tied to more sophisticated control techniques

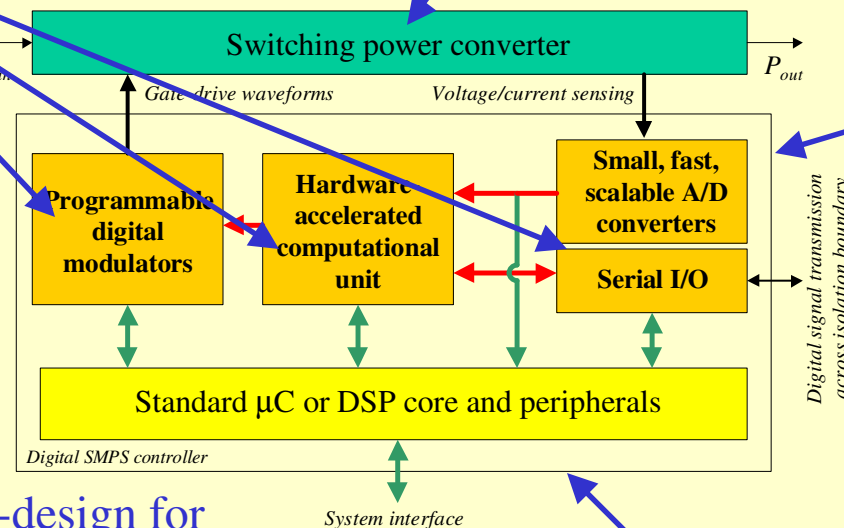New controller architectures for wide range of applications



Converter/controller co-design for significant gains in performance, size and/or cost:

- reduced size of passive components
- improved efficiency
- improved dynamic responses, etc.

New control algorithms

- parameter/state estimation
- adaptive control
- nonlinear control, etc.

Modeling techniques





Examples of CoPEC Research Results

- **Complete 1 MHz digital PWM controller IC**
 - small size, programmable compensator, no discretes
- **Standard-cell based A/D converter ICs**
 - small size, fast sampling, scalable with digital technology
- **Digitally controlled 3.3 V, 20 A DC power supply**
 - chipset for isolated DC power supplies
- **Digital predictive current-mode control**
 - very fast response
 - applications to PFC and DC-DC converters
- **Digitally-controlled power-factor correction rectifiers**
 - order-of-magnitude improvement in dynamic response



Buffalo Switcher

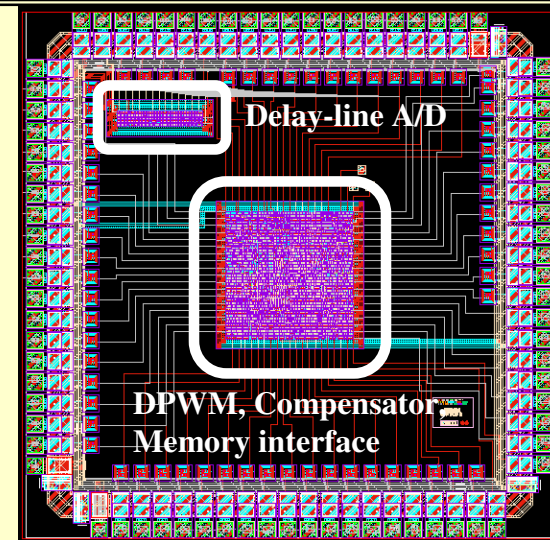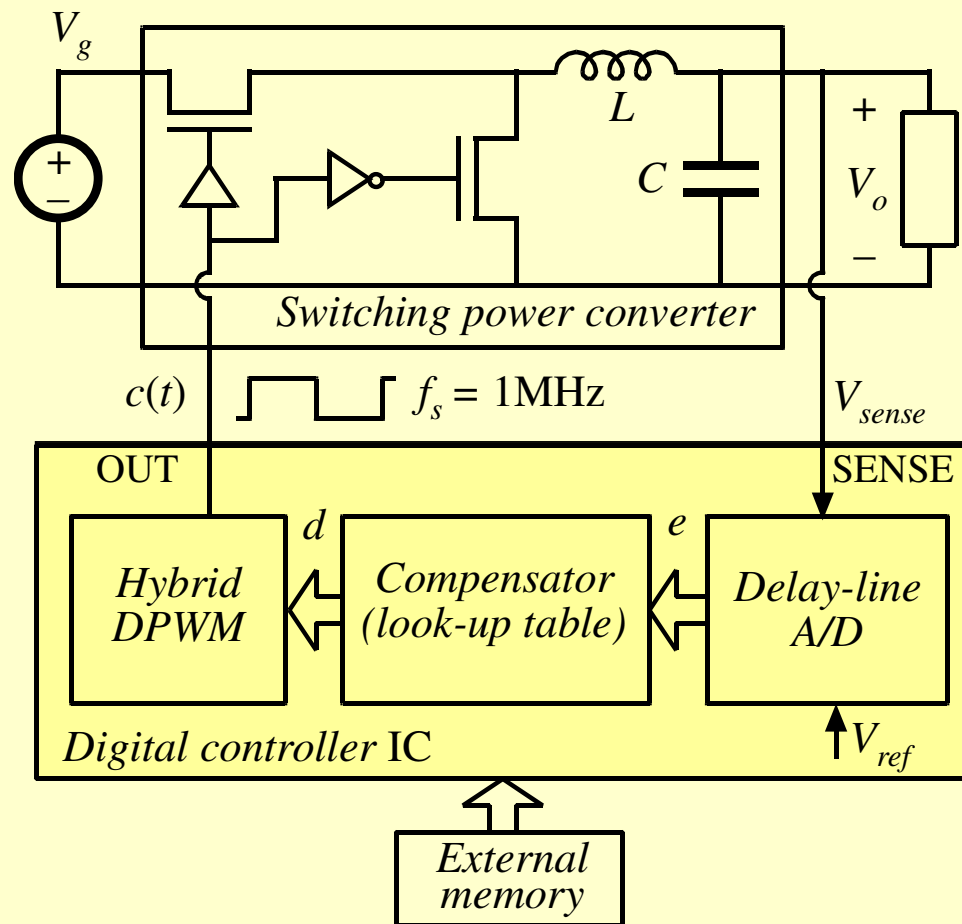
Complete High-Frequency Digital PWM Controller IC



- 1 MHz switching frequency
- Programmable compensator
- 0.5 μ CMOS technology
- Chip area: 0.96 mm²
- All-digital, HDL-based design
- Standard digital design flow:
 - HDL (Verilog) based design
 - Synthesis to standard-cell gates
 - Automated place & route



Chip architecture

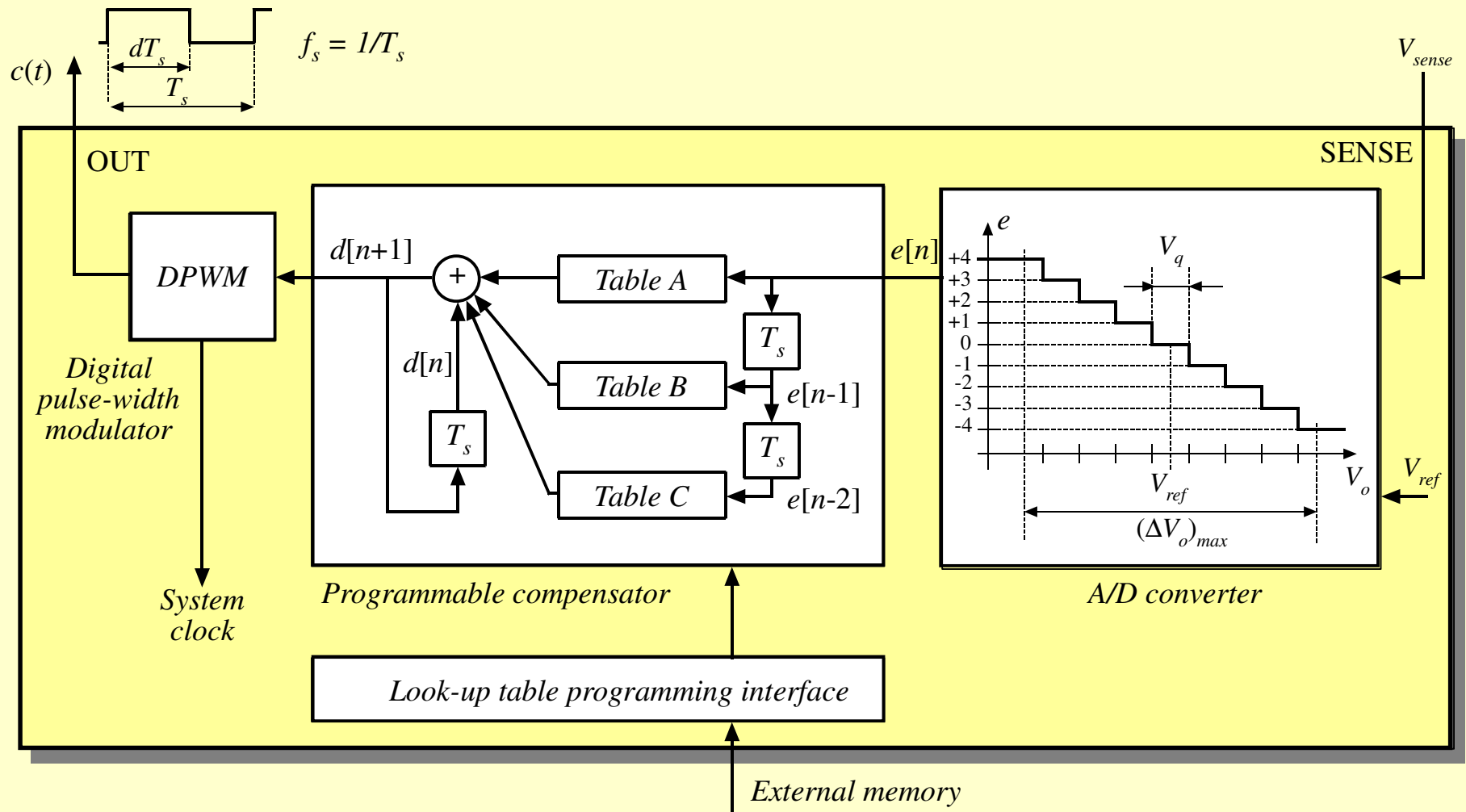




A/D requirements

Static voltage regulation $\Rightarrow V_q \leq \Delta V_o$

Only a few
digital error
outputs
needed

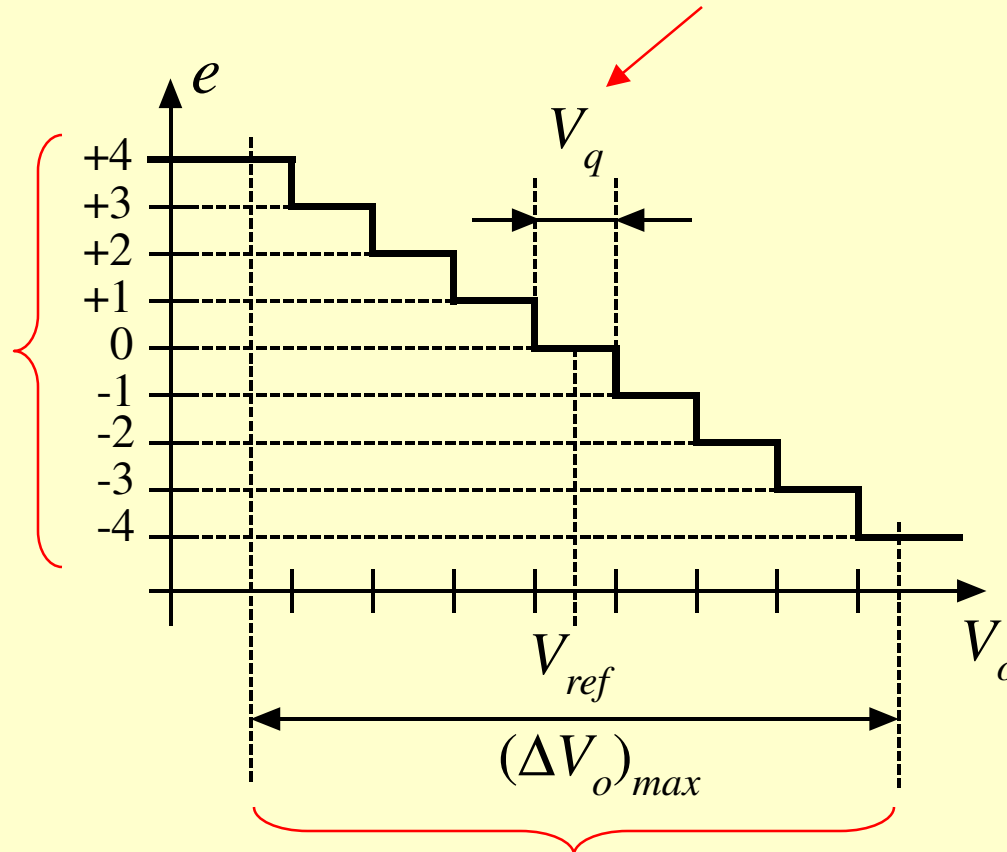


Dynamic voltage regulation \Rightarrow small conversion range




Delay-line A/D

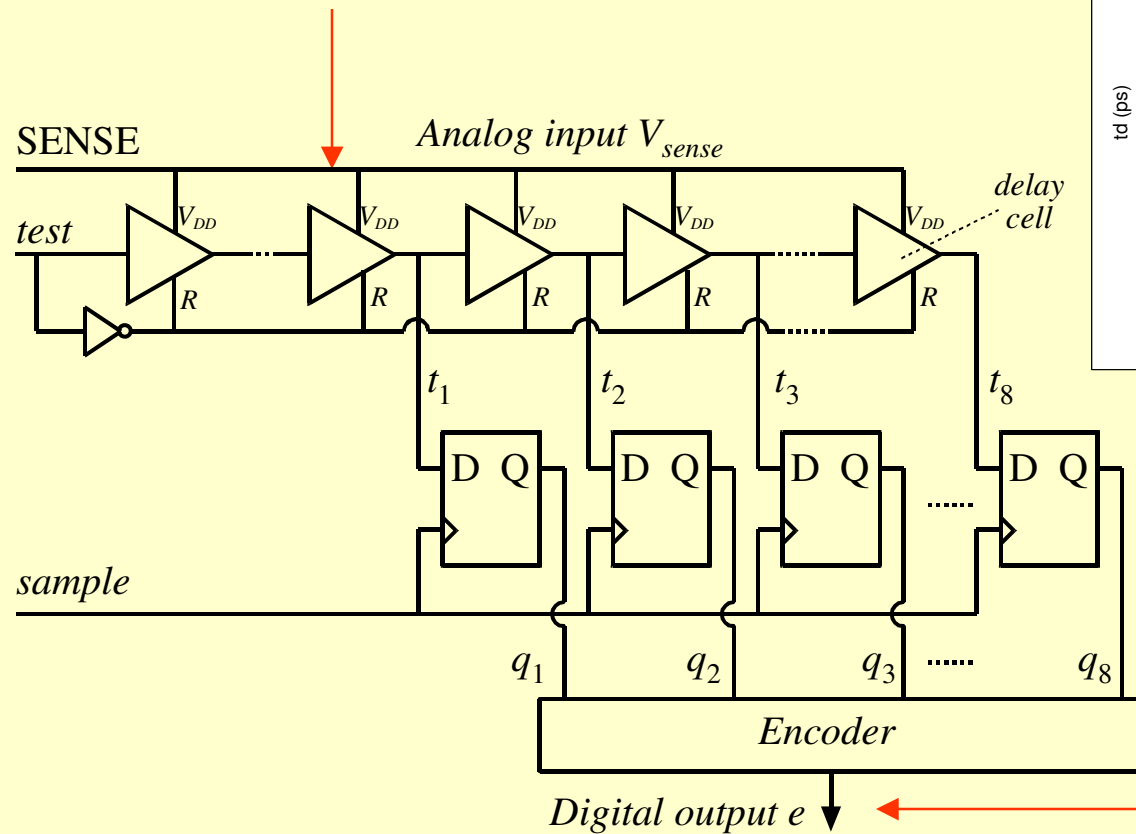Analog input is the supply voltage VDD for a chain of logic gates



Delay t_d versus VDD

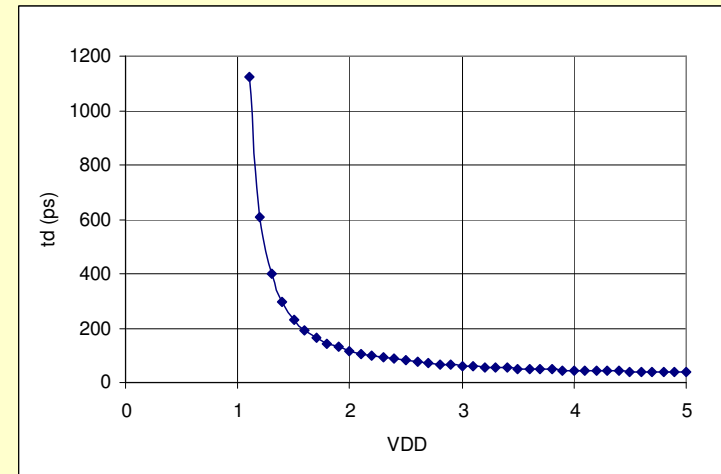


Digital output q (in "thermometer" code)

Digital output e




Delay-line A/D Operation

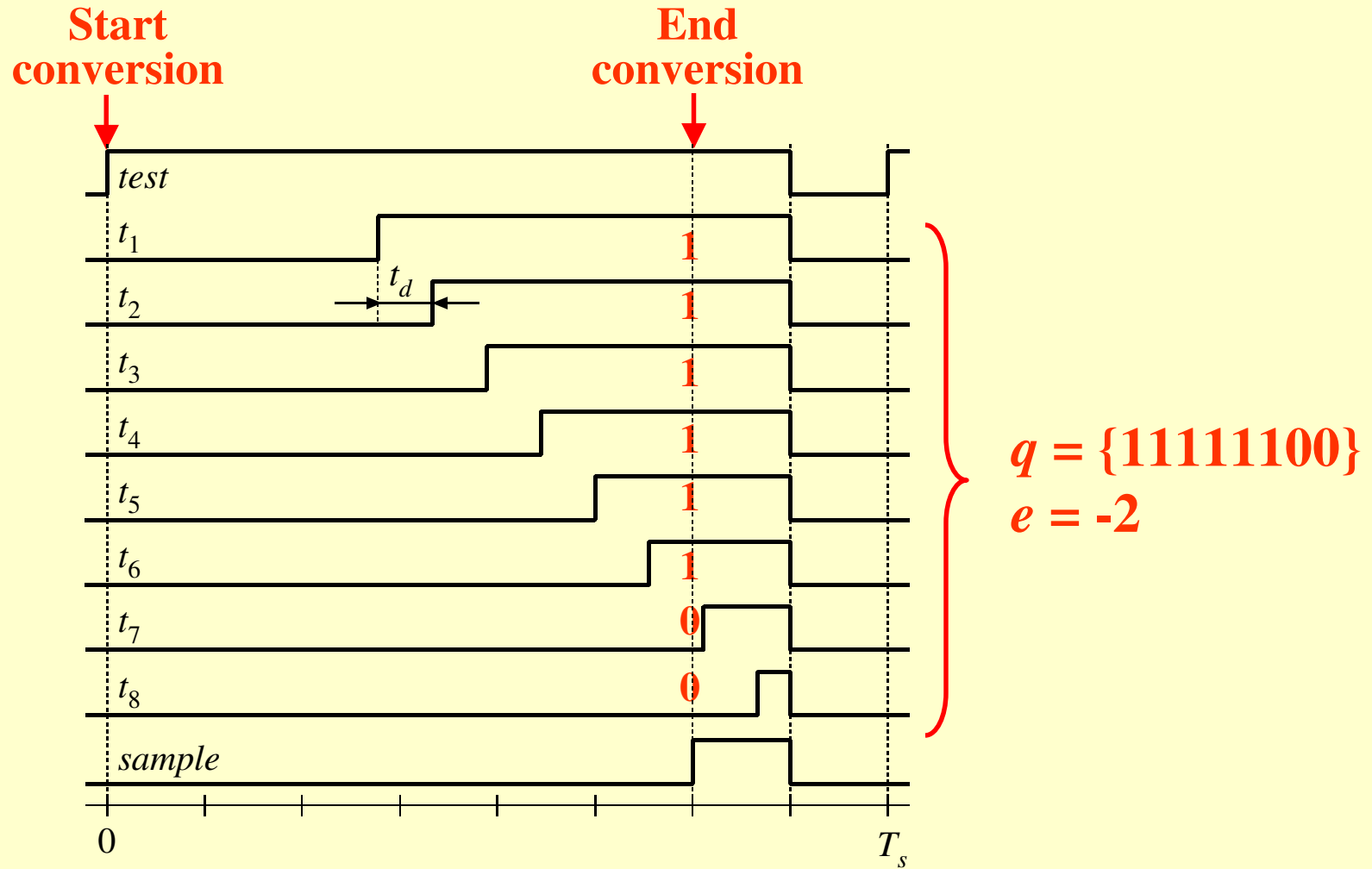



Delay-line A/D Experimental Results

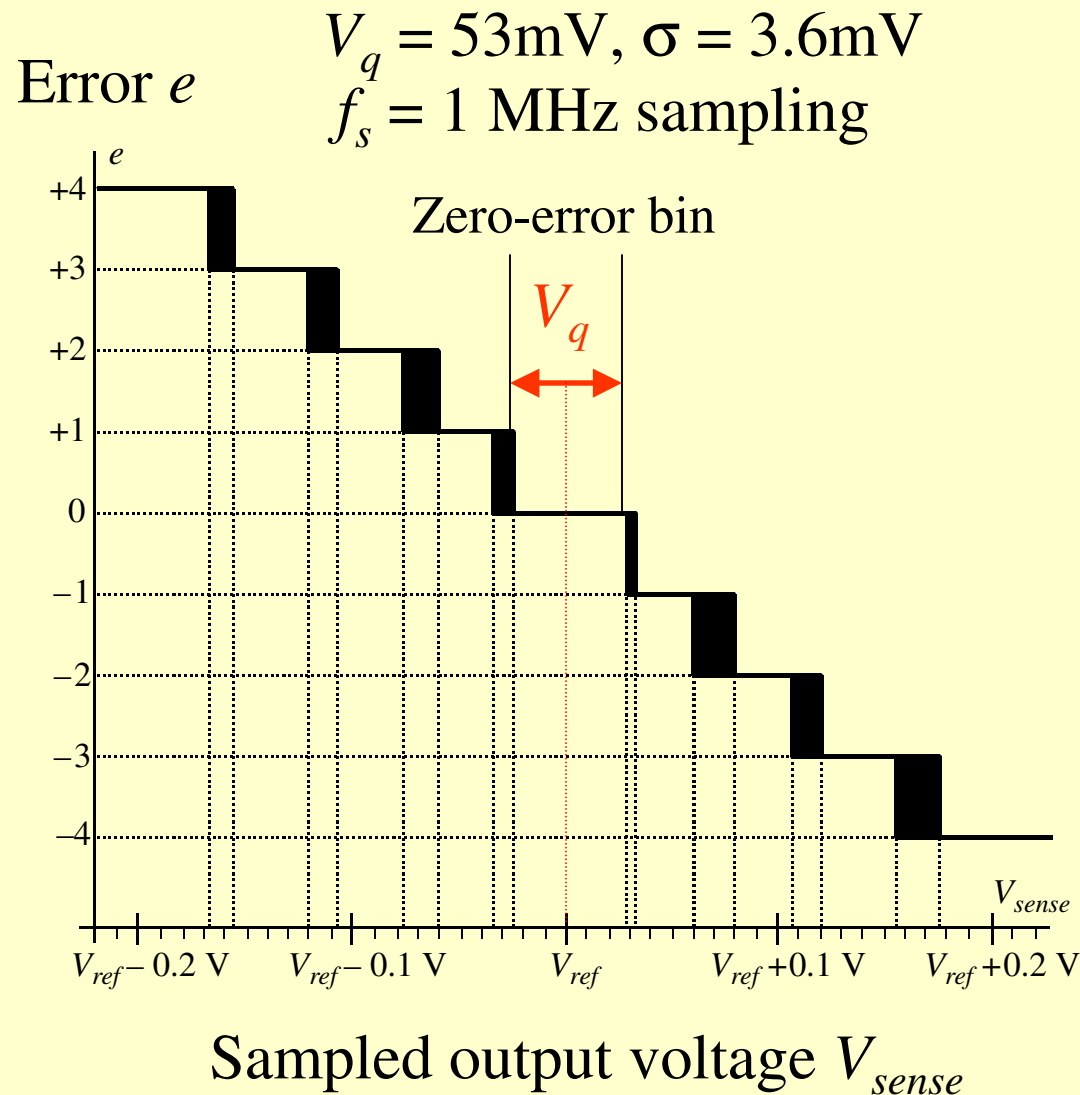

Advantages:


- Small area/low power
- Averaging over conversion time
- All digital implementation

Problem:

- Basic configuration is highly susceptible to process/temperature
- How to implement calibration to a reference voltage?



Strobe-Calibrated Delay-Line A/D


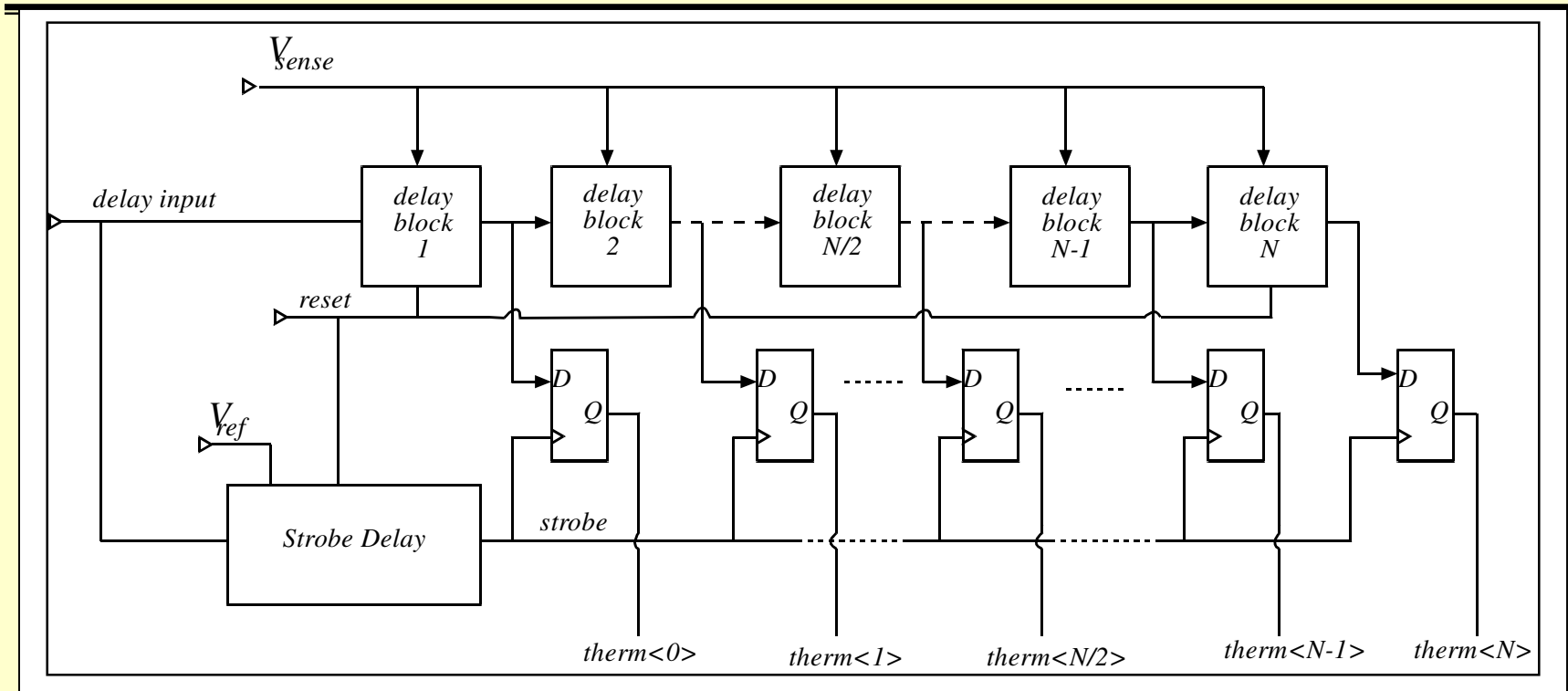


- Delay blocks constructed with standard cells
- Matched “strobe delay” added to provide self-calibrated reference point



Strobe-Calibrated Delay-Line A/D Exp Results

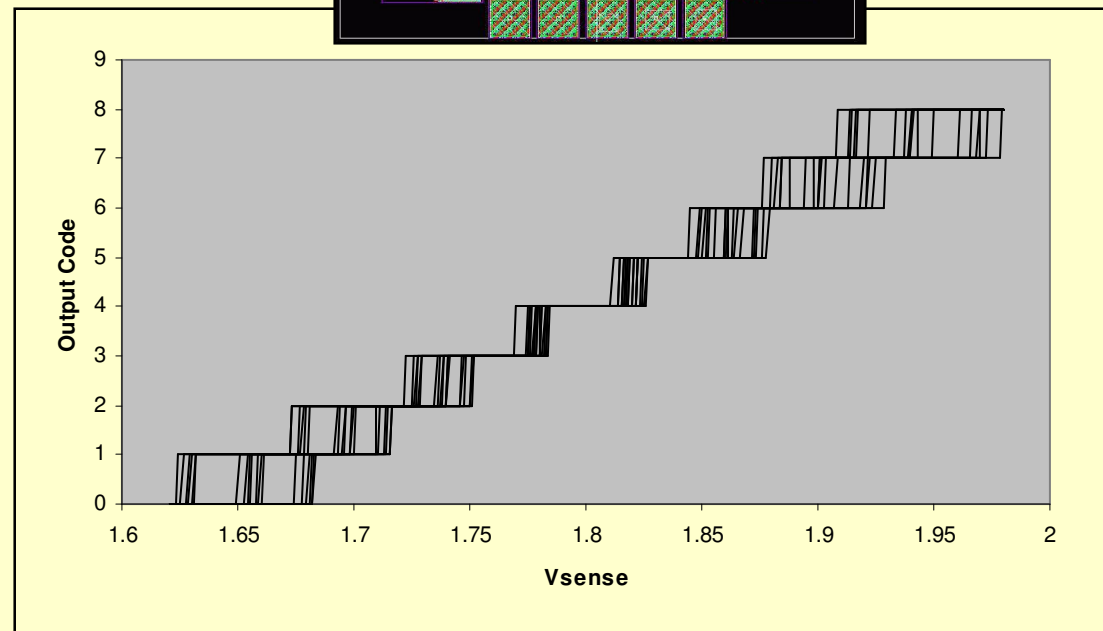 
- 1.8 V reference
- 250ns typical conversion time (500ns worst case)
- Standard-cell HDL-based design, 0.5 μ CMOS process
- Automated place-and-route of primary and matched delay lines
- Tested over the temperature range from -40°C to 100°C



Experimental characteristics over temperature



 Strobe-Calibrated Delay-Line A/D Exp Results




Histogram of the measured offset over 18 prototype chips

- Average offset: 1.56mV (4% LSB)
- 11 of 18 chips < 2 mV offset
- Good performance holds over temperature
- The worst offset prototype chip of 18 samples at the worst temperature corner: -7.3 mV offset
- Total current consumption:
 - less than 100 μ A



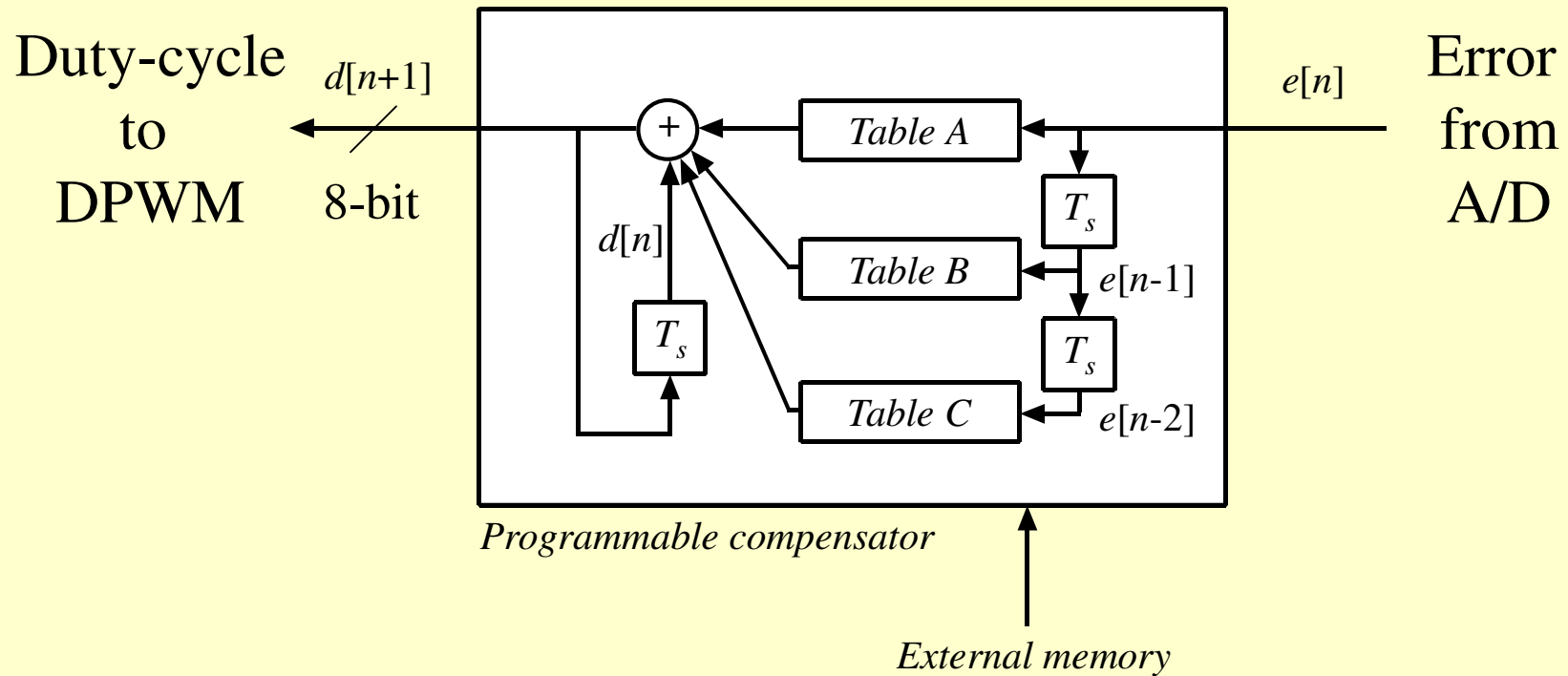Look-up Table Based Programmable Compensator




$$\text{PID compensator: } d[n+1] = d[n] + \underbrace{a e[n]}_{\text{Table A}} + \underbrace{b e[n-1]}_{\text{Table B}} + \underbrace{c e[n-1]}_{\text{Table C}}$$

- “Zero” steady-state error
- Programmable response
- Very small area, very low power

Table A Table B Table C



Conventional Counter-based DPWM Design

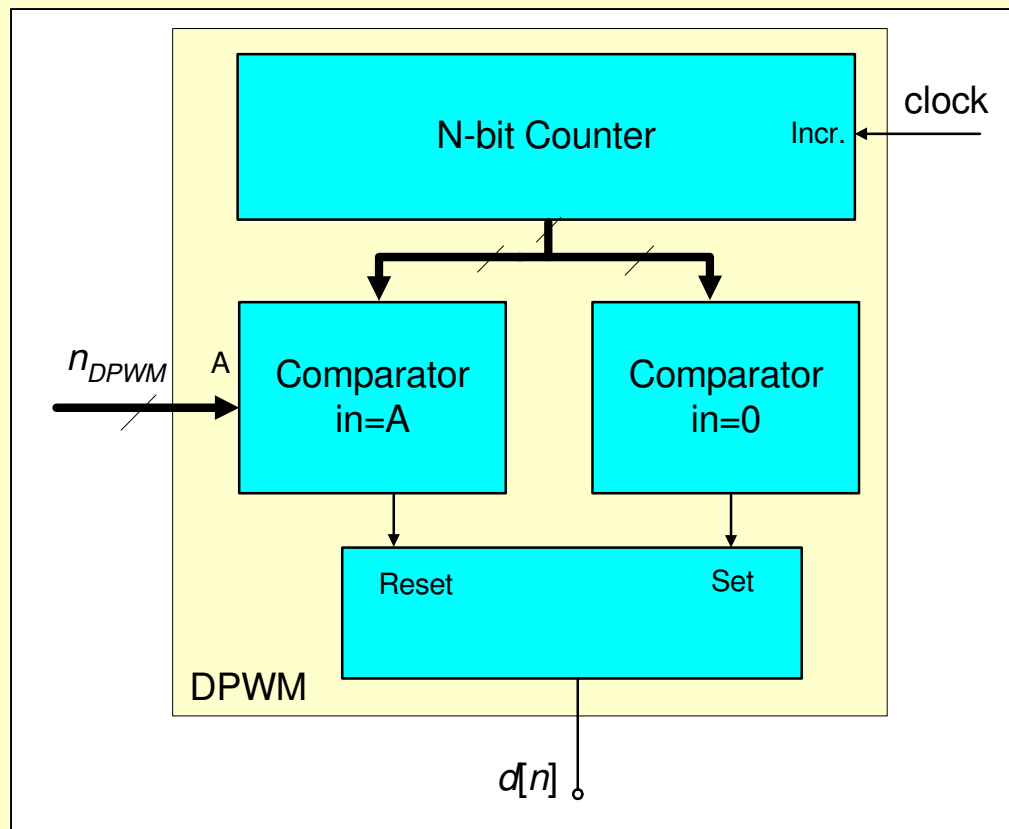

$$f_{clk} \geq 2^{N_{DPWM}} \cdot f_s$$

f_{sw} : switching frequency

f_{clk} : processor clock frequency

n_{DPWM} : number of bits of DPWM

10-bit @ 1 MHz => 1 GHz clock signal!?



High-Resolution Hybrid DPWM

Combines a **delay line** (ring oscillator) with a **counter** to reduce the maximum clock speed

Conventional DPWM:

$$f_{clk} = 2^n \cdot f_s$$

Hybrid DPWM:


$$f_s \leq f_{clk} \leq 2^n \cdot f_s$$

Prototype:

$$n = 8 \text{ bits}$$

$$f_s = 1 \text{ MHz}$$


$$f_{clk} = 8 \text{ MHz}$$

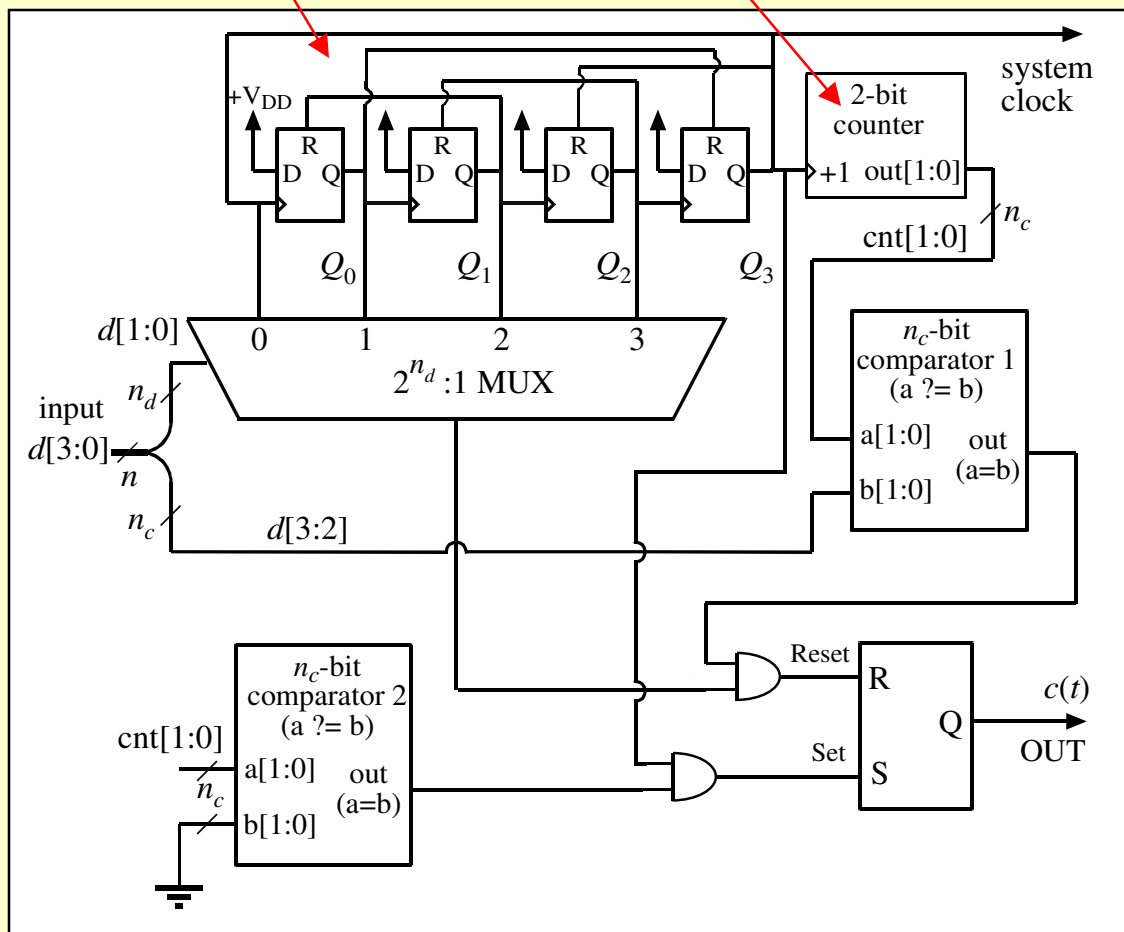



DPWM Experimental Results

Output duty ratio [%]

 



High-Resolution Hybrid DPWM

Hybrid DPWM combines a delay line (ring oscillator) with a counter to reduce the maximum clock speed

Conventional DPWM:

$$f_{clk} = 2^n \cdot f_s$$

$$n = 8 \text{ bits}$$

$$f_s = 1 \text{ MHz}$$

$$f_{clk} = 256 \text{ MHz}$$

Hybrid DPWM:


$$f_s \leq f_{clk} \leq 2^n \cdot f_s$$

Buffalo switcher hybrid DPWM prototype:

$$n = 8 \text{ bits}$$

$$f_s = 1 \text{ MHz}$$


$$f_{clk} = 8 \text{ MHz}$$

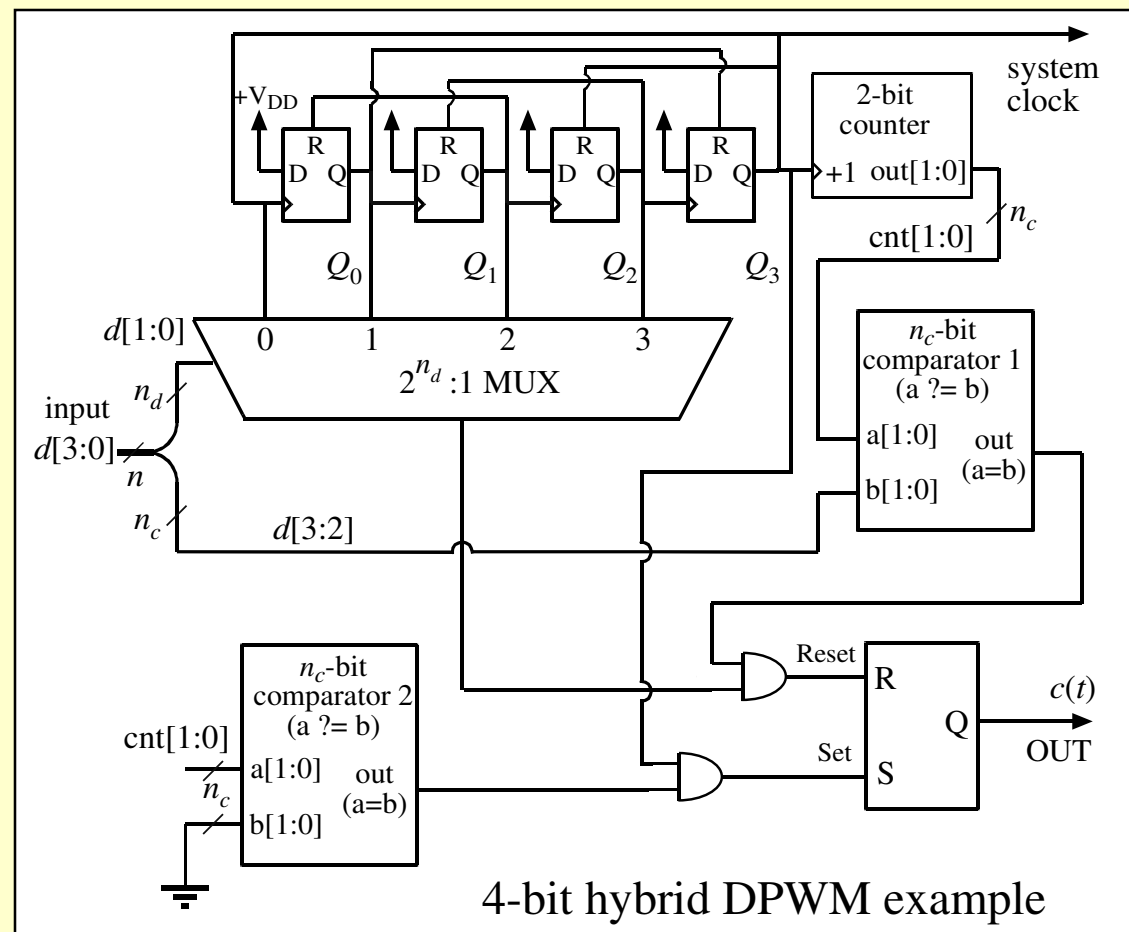




10-Bit Hybrid DPWM Implementation

 - 10-bit resolution
- Programmable switching frequency: 750 kHz, 400 kHz, 200 kHz and 100 kHz/ 1.3 ns resolution
- 32 times higher clock frequency
- 0.5 μ CMOS
- Active chip area: 0.16 mm²
- Completely HDL coded





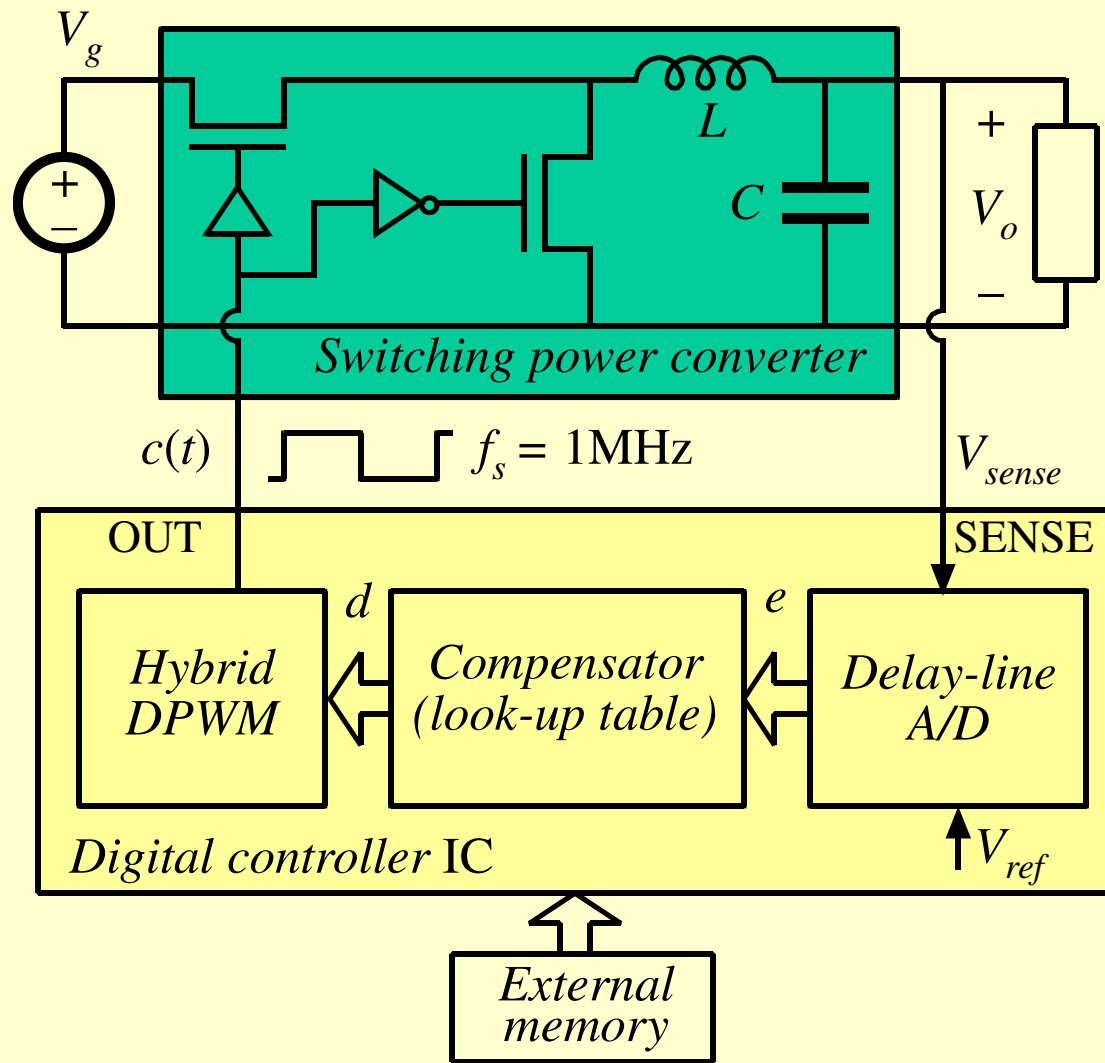Experimental Digitally Controlled Power Supply



$$L = 1 \mu\text{H}, C = 22 \mu\text{F}$$

$$4 \text{ V} < V_g < 6 \text{ V}$$




$$V_o = 2.7 \text{ V} \pm 25 \text{ mV}$$

$$0 < I_o < 1.5 \text{ A}$$

$$f_s = 1 \text{ MHz}$$



Experimental Results

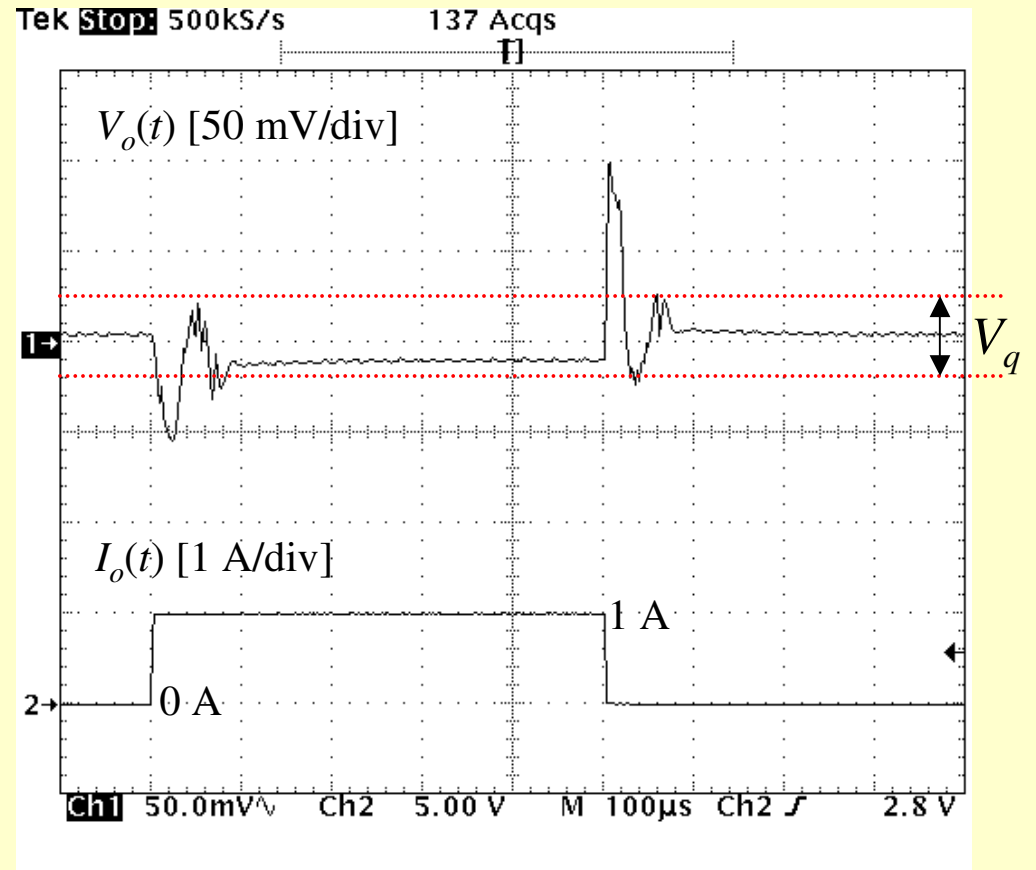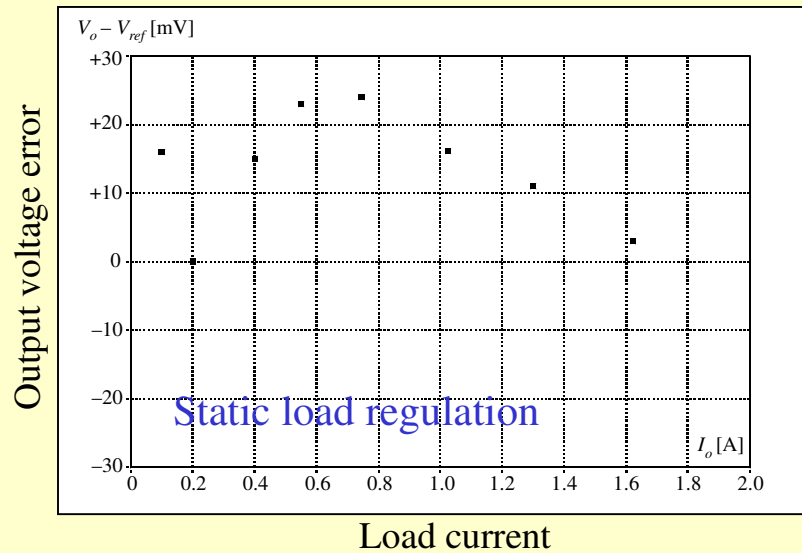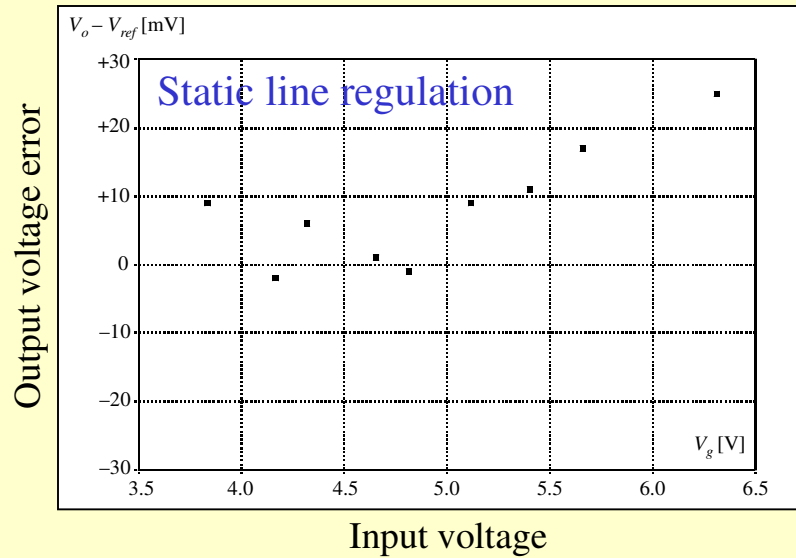

Load Transient Response




Conclusions

- Complete 1 MHz digital PWM controller IC
- New architecture and HDL-based design of the key building blocks:
 - Calibrated delay-line A/D
 - Programmable look-up table compensator
 - Hybrid DPWM
- Small area, low power, fast response
- Design scales with digital technology
- Open possibilities for a new generation of controller ICs (standard parts and ASICs) for power electronics




Extension: Digital Chipset for Isolated Power Supply

Analog implementation

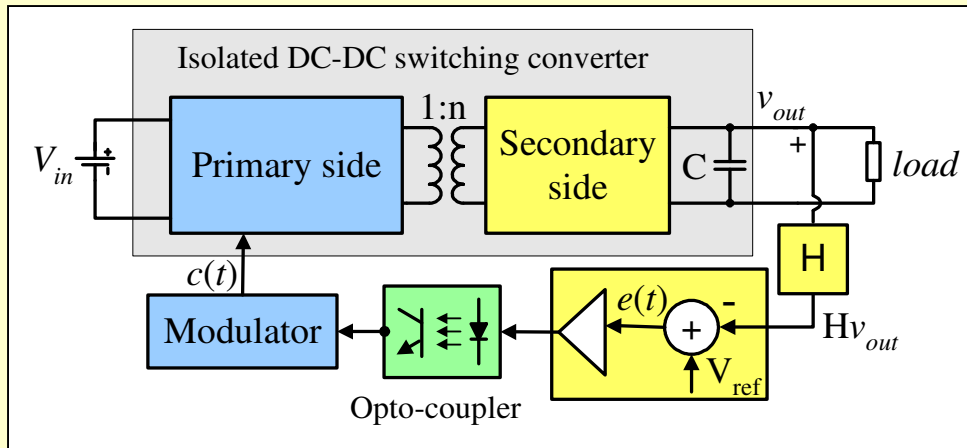

- Opto-coupler operates in linear mode

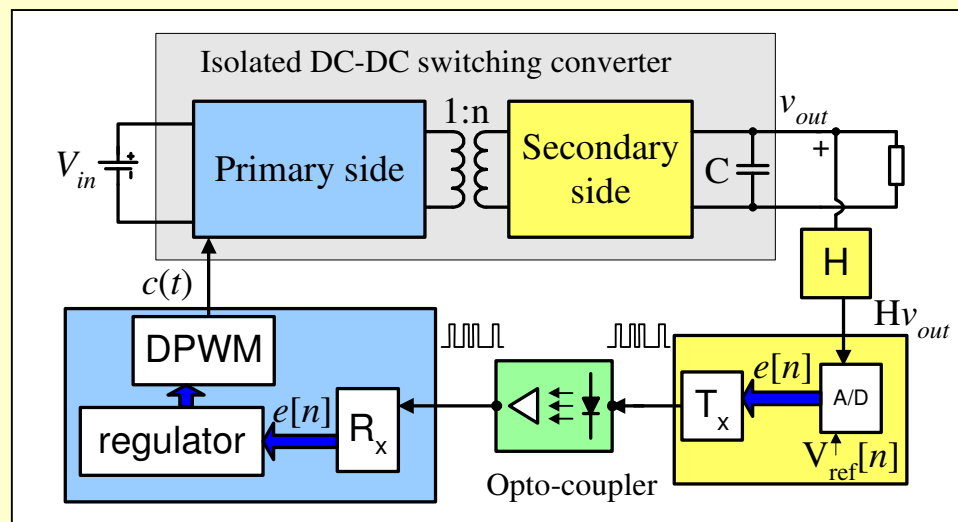
Digital solution based on serial communication



- Opto-coupler operates in digital mode (as a logic gate)
- Transfers just the error signal
- Potential for less conservative design of the feedback loop



Isolated DC-DC: Test System

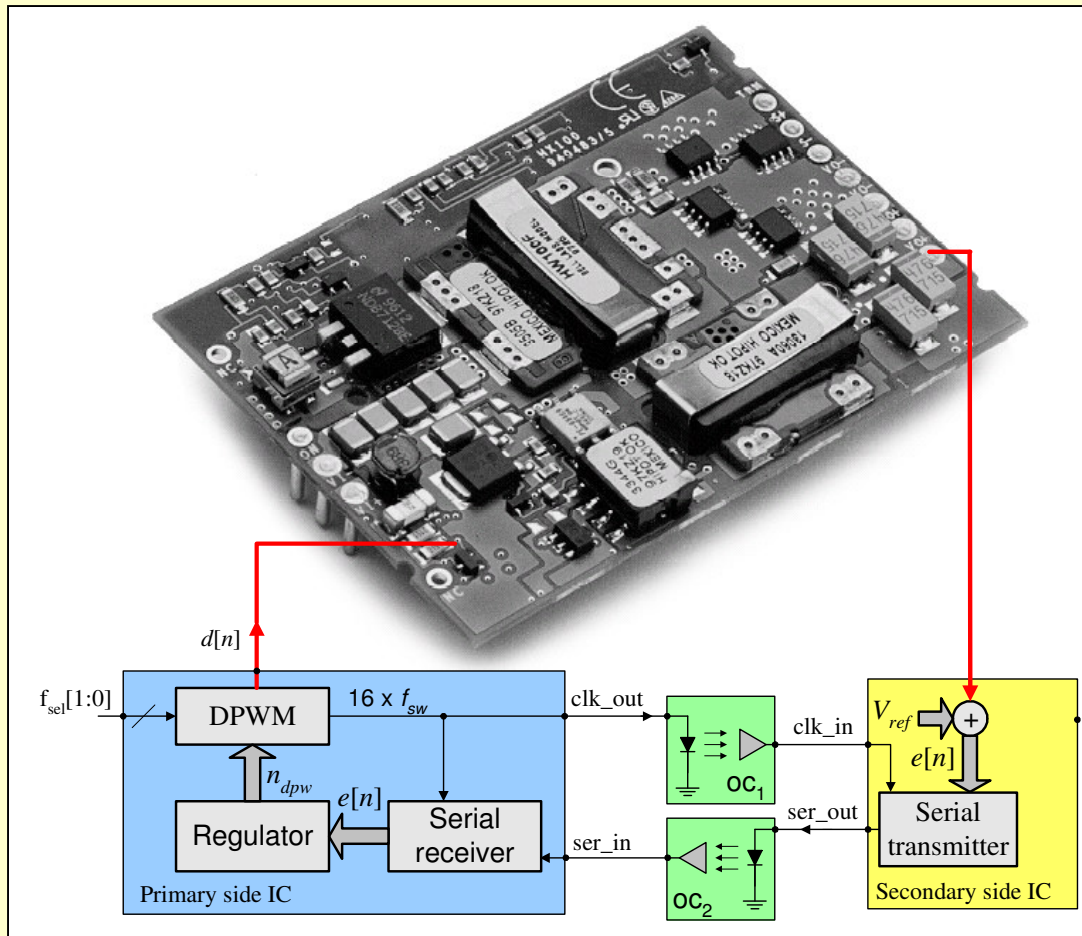


Tyco HW 100F

- Isolated converter
- $36\text{ V} \div 72\text{ V}$ to 3.3 V
- up to 20 Amps load
- 400 kHz switching frequency
- Replaced original analog current-mode controller on the board




Experimental Results

 





Digital Controller for AC/DC PFC

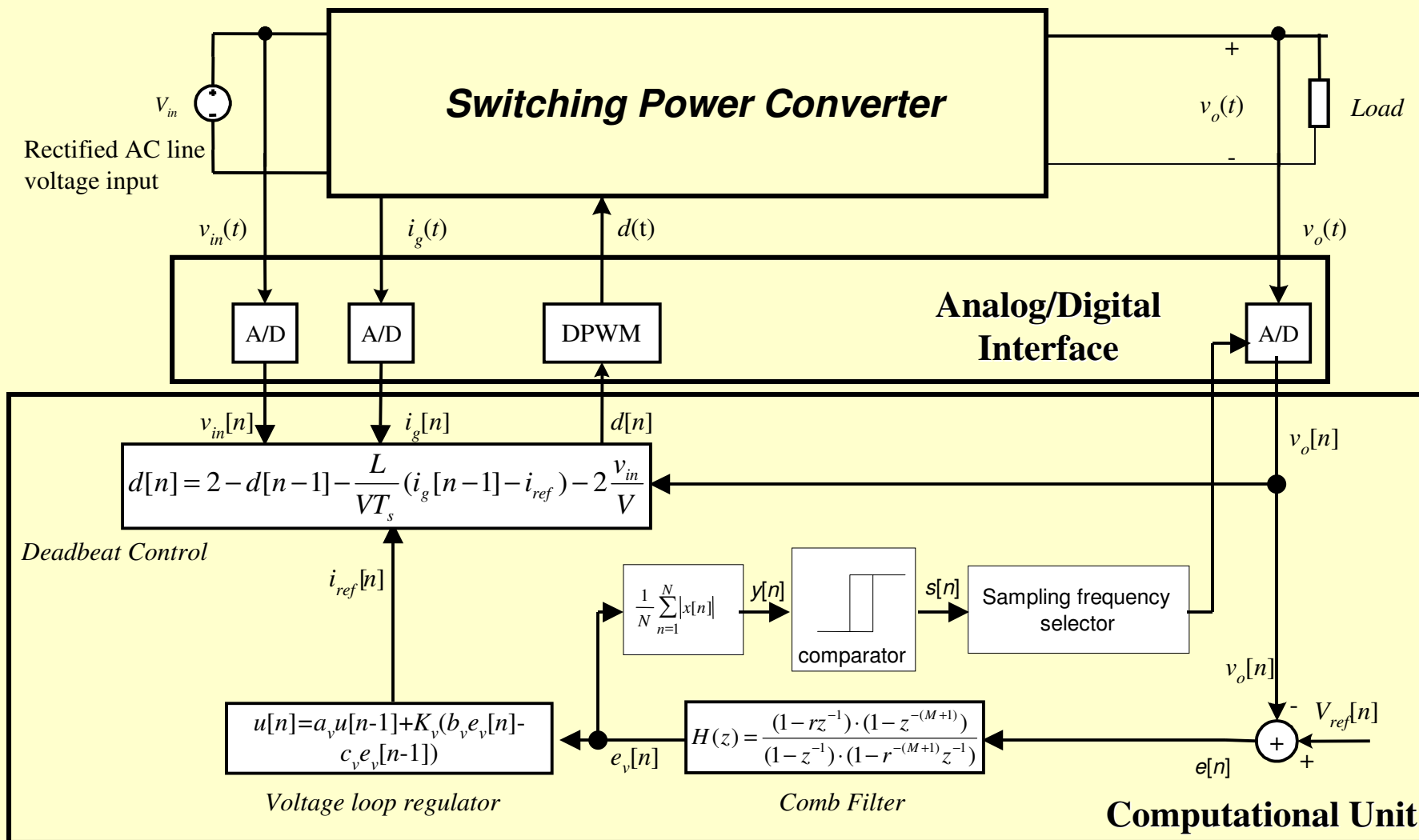



PFC Experimental Results (current loop)

Line frequency: 800Hz

  

Switching frequency: 200KHz
THD: 2.2%


Switching frequency: 100KHz
THD: 2.4%

Dead-beat digital current mode control: near-perfect PFC
even in demanding next-generation avionics applications
(AC system with the line frequency up to 800 Hz)




PFC Experimental Results (voltage loop)


Conventional
voltage loop

 

With STCF

 

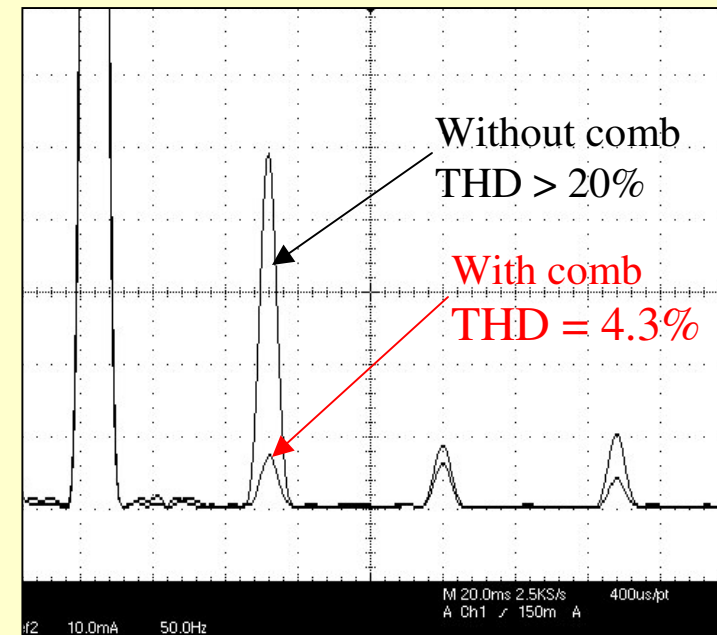High-bandwidth loop with and
without a notch filter





Other CoPEC Research Projects (2003)

- **Advanced digital control of DC-DC converters**
 - High-performance predictive digital current-mode control for DC-DC converters (TI)
- **Power management for low-power electronics**
 - Digital DC-DC switcher for battery-powered systems (NSC)
 - Adaptive DC-DC converters for RF power amplifiers (DARPA)
 - Adaptive DC-DC converters and power management architecture for base-band μ P/DSP (NSF, NSC)
 - Energy harvesting for wireless sensors and Implantable sensors for neuronal recording (Coleman Institute)
- **Microprocessor power supplies**
 - Multi-phase digital controller for microprocessor power supplies (Artesyn)
- **Off-line switching power supplies**
 - Modular mixed-signal control for electronic ballasts (GE)
 - Digital controllers for solar/utility power system (Philips)
 - Digitally controlled matrix converters for wind power system (NREL)





CoPEC Educational Program Objectives

- Strong undergraduate and graduate programs in power electronics and mixed-signal IC design
- Internship and job opportunities for students
- Continuing education
 - Courses available through CATECS
 - Certificate program in power electronics
- Technology transfer to CoPEC sponsors
 - Jointly defined and directed projects
 - Access to CoPEC IP



Growth of Program: Enrollment

  


Enrollment for Analog IC Design, Spring 2002: **31**, Spring 2003: 66
Enrollment for Mixed-Signal IC Design, Fall 2002: **15**

Our visibility is increasing, and we are attracting more students to the power electronics and micro-electronics areas




Growth of Program: Graduate Students

 

With increased visibility and availability of projects, we are able to attract better students into our program



Mixed-Signal IC Design Flow

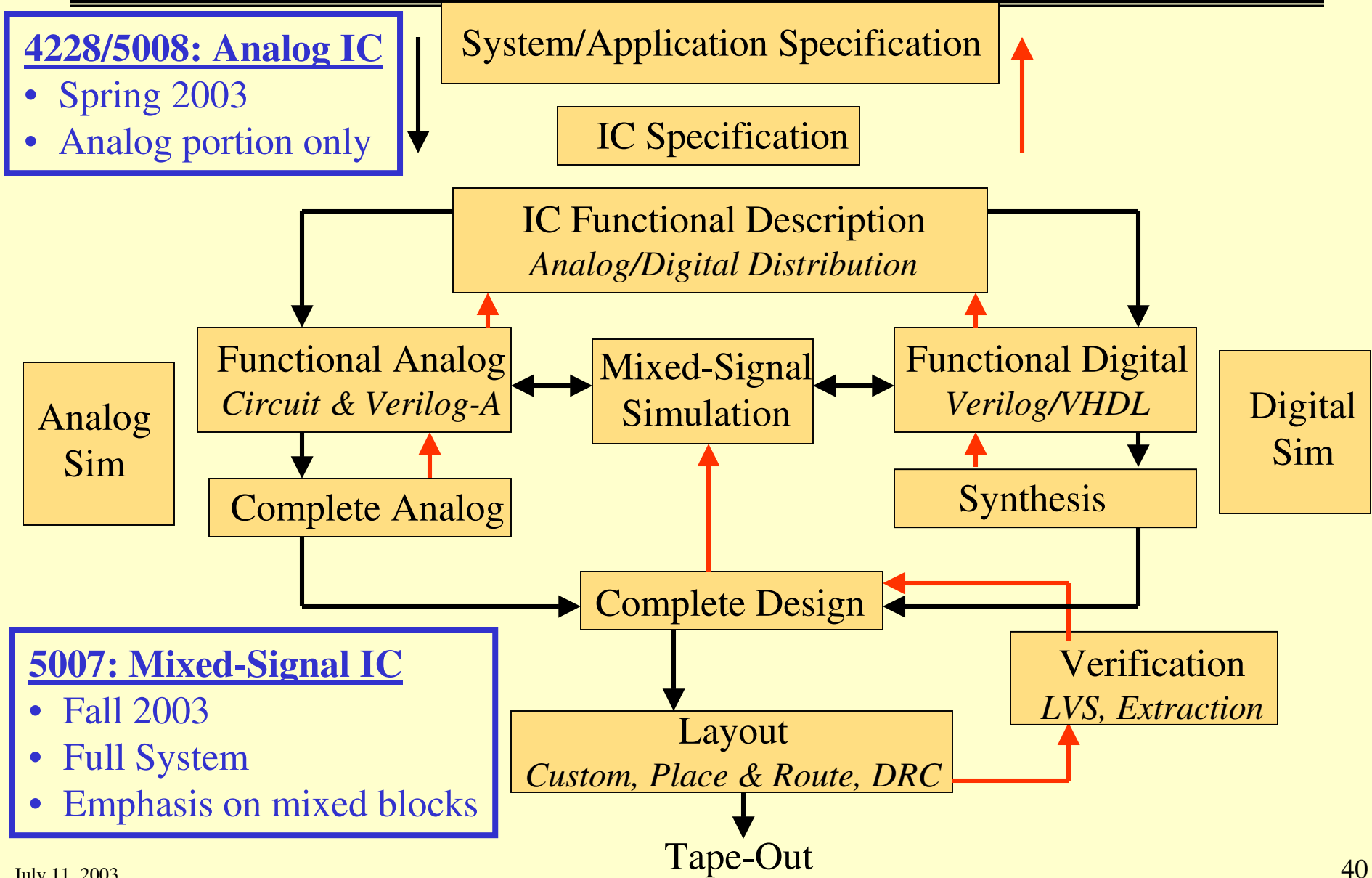



Analog IC Course Outline

- *Week 1:* **Review circuits I-II**
 - Text Ch. 1, Appendix A & C; Supplementary notes
- *Week 2:* **Review CMOS technology and device models**
 - Text Ch. 2-3
- *Weeks 3-4:* **Analog CMOS sub-circuits**
 - Text Ch. 4
- *Weeks 5-7:* **CMOS amplifiers**
 - Text Ch. 5
- *Weeks 8-10:* **CMOS operational amplifiers**
 - Text Ch. 6
- *Weeks 11-13:* **High-performance CMOS op-amps**
 - Text Ch. 7
- *Weeks 14-15:* **Comparators and select advanced topics**
 - Text Ch. 8, Supplementary notes

Text used: Allen/Holberg, Gray/Meyer, Johns/Martin



Mixed-Signal IC Lecture Topics

Comparators

- 2-stage amp, hysteresis, latched, high-speed
- Sample & Hold Circuits

Discrete-Time Signals (Fundamentals)

Sampled-Data Circuit Techniques

- SC & SI Circuits: Filter Design, Amplifiers, Applications
- Non-idealities: clock-feedthrough, matching

Data Converters

- Fundamentals
- Nyquist Rate D/A, A/D
- Oversampling Converters

System Level IC Design

- System Description & Specification
- IC Functional Specification
- Top Down & Bottom Up Methodologies
- System Planning: fabrication options, foundry selection, silicon area estimation, packaging options, prototype and production cost & time estimation
- Design for Testability
- Reviews: data sheet preparation, design reviews, risk analysis

System Simulation

- Software Preparation: technology files, model files, standard cell libraries, software setup
- Functional Simulation: Verilog-A and Verilog HDL languages, hierarchical designs with multiple cell-views
- Mixed-Signal Simulation: co-simulation of analog & digital, functional and circuit level blocks in the Cadence tools
- Ballast Controller & PLL Case Studies

Physical Layer (time & setup permitting)

- Floorplanning & Layout: custom and semi-custom layout in Cadence
- Practical Considerations: matching, digital/analog isolation, latch-up, ESD and pad design, power distribution, noise coupling
- Verification: LVS, DRC, extracted simulation
- Fabrication: GDSII extraction to foundry



Mixed-Signal IC Final Project

- Select a mixed-signal project that targets a specific application
- Work in teams of 1 to 4
- Deliverables include:
 - **Proposal:** Create a final project website with an overview of the target application, project goals, and a timeline of the digital & analog design process.
 - **Functional Design:** Complete a functional block diagram and schematic, which must include at least one custom functional block. The design must include at least one custom functional block at the circuit level block. Your project website must include a link to your project website.
 - **Final Design Review:** Final in-class presentation on your project. The complete “front-end” design of the projects must be complete, ready for transition to a layout engineer. Time permitting, various phases of layout and verification may be required as well.

Local Industry Involvement (?)

- Suggest relevant project/research topics
- Be involved with design and/or final reviews
- Fund fabrication of best designs → hold competition?