

# **60-GHz CMOS Transceivers: Why and How?**

**Behzad Razavi**

**Electrical Engineering Department**

**University of California, Los Angeles**

# Outline

---

- **Introduction**
- **Receiver Front End**
- **Transmitter Front End**
- **Frequency Divider**
- **Reflections**
- **Conclusion**


# Why 60 GHz?

---

- **7 GHz of Unlicensed Band**
- **Possibility of Realizing (Multiple) On-Chip Antennas:**
  - **Low-Cost Packaging**
  - **Differential Operation → Higher Output Power**
  - **No Need for T/R Switch**
  - **No Need for AC Coupling**
  - **No Need for High-Frequency ESD Devices**
- **Possible Applications:**
  - **Gb/s Networks, e.g., Video Streaming**
  - **Highly-Interconnected Networks**

# Highly-Interconnected Networks

---

 

# Why CMOS?

---

- **Need Complex Modulation Techniques:**
  - OFDM
  - QAM
  - Frequency Hopping?
- **Need Sophisticated Analog Calibration:**
  - I/Q Matching at 60 GHz?!
  - Wideband Analog Baseband Filters
  - Multitude of High-Speed ADCs
- **Large Fractional Bandwidth (>10%):**
  - Several Staggered High-Q Signal Paths
  - Multiple VCOs and Tuned Dividers


# Challenges

---


- **Limited transistor speed → Need for inductors and transmission lines.**
- **Inductor footprints → Long interconnects**
- **Inductor Q's tend to saturate around 25.**
- **Varactor Q's likely to be lower than inductor Q's.**
- **Lossy on-chip antennas → Beamforming**
- **Passive and active device modeling**
- **Gain and phase mismatches, etc.**

# Transceiver Building Blocks


**Receiver  
Front End**

 

**Transmitter  
Front End**

 


**Frequency  
Divider**

 

**Designed in 0.13- $\mu\text{m}$  CMOS; migrating to 90-nm process.**


# Receiver Architecture

 




# Raw Speed of MOS Devices


---

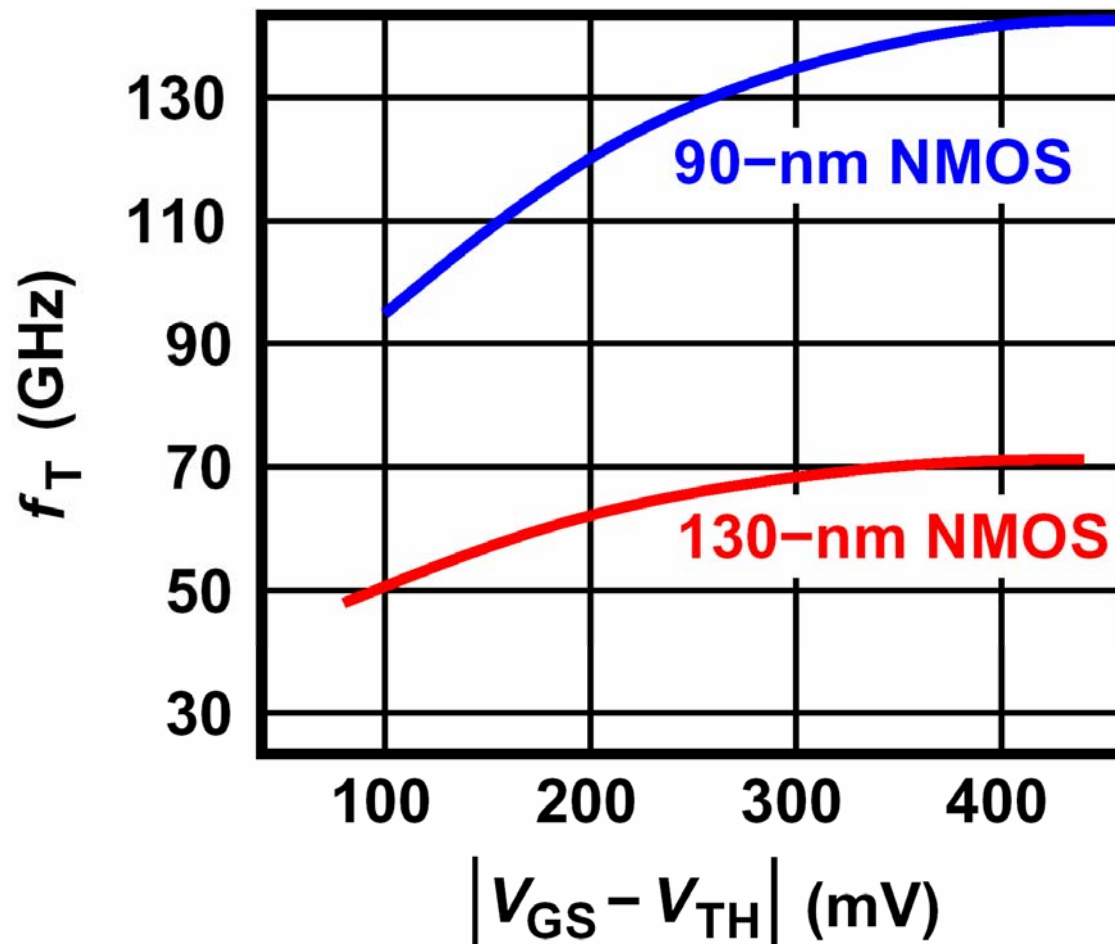
 
# Spiral Inductors vs. Transmission Lines




**Coplanar Line**

 




**Substrate**

**Microstrip Line**


 


**Substrate**

# Folded Microstrip

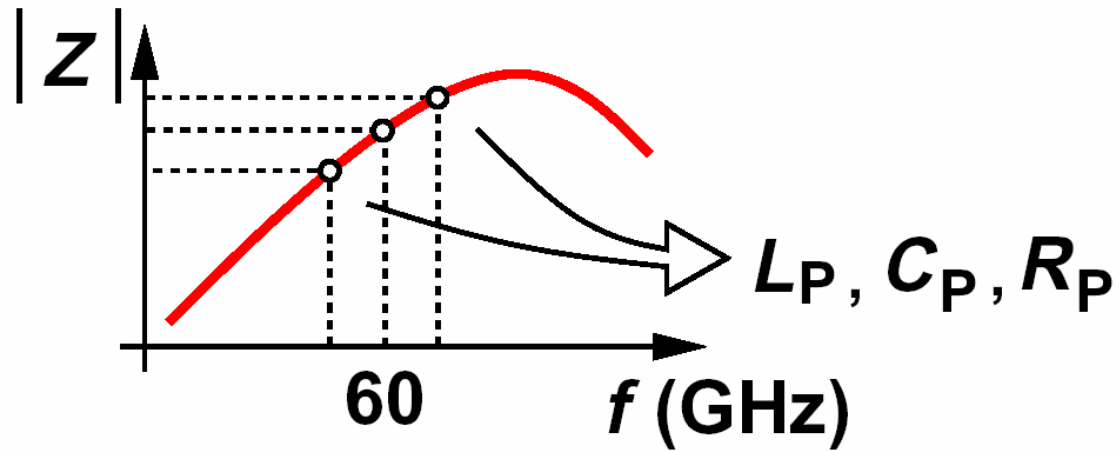  


# Choice of Linewidth

  

$L_P$  (pH)

220  
200  
180  
160  
140  
120

 


$C_P$  (fF)

12  
10  
8  
6  
4  
2


$R_P$  ( $\Omega$ )

720  
700  
680  
660  
640

 


Absorbable  
Capacitance


(fF)  
40  
35  
30  
25

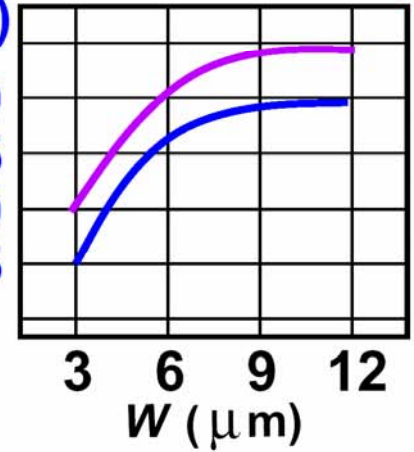



# Choice of Line Spacing

 


 
**Current  
Density  
(mA/  $\mu\text{m}$ )**




# Choice of Line Spacing

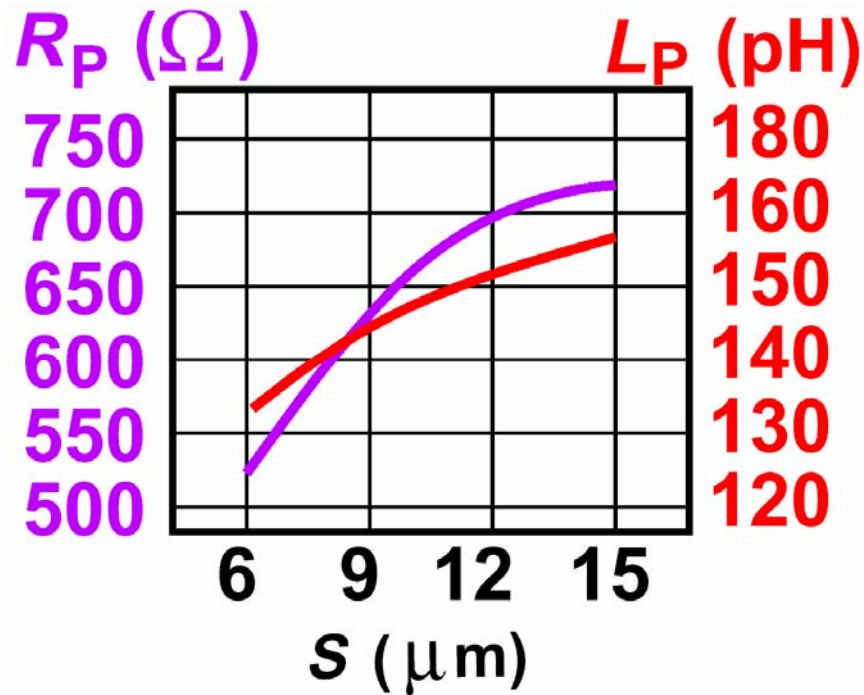 

# Cascode vs. Common-Gate LNA

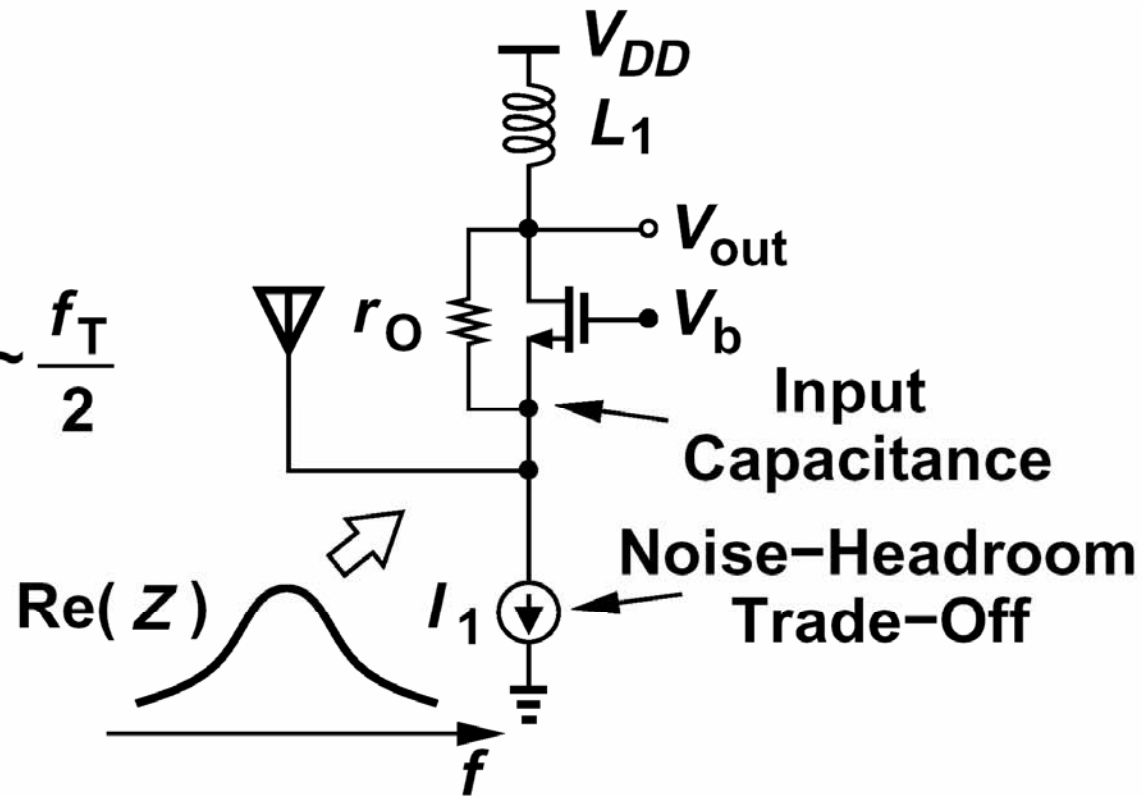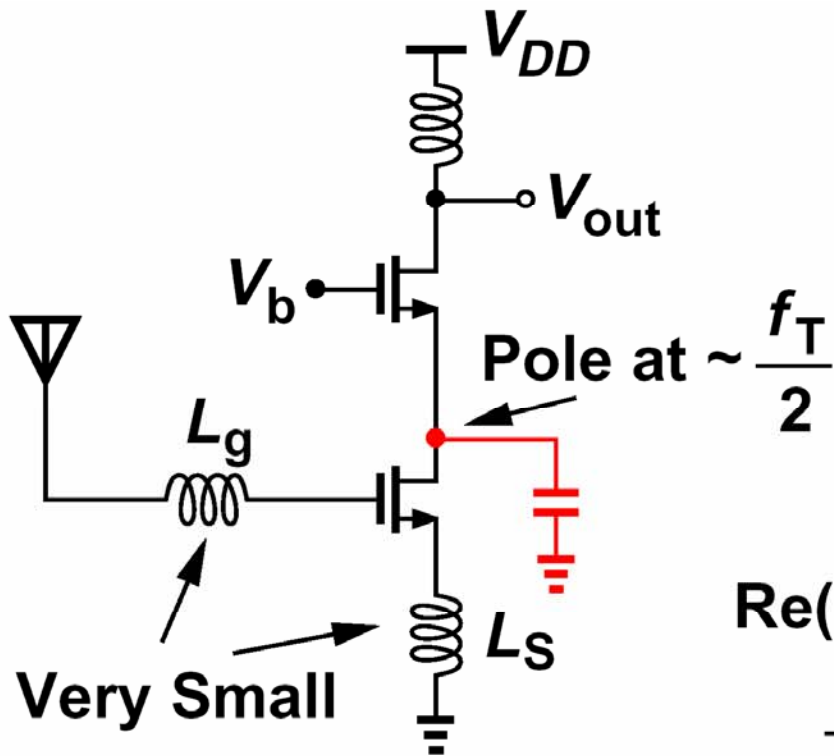


# Simplified LNA

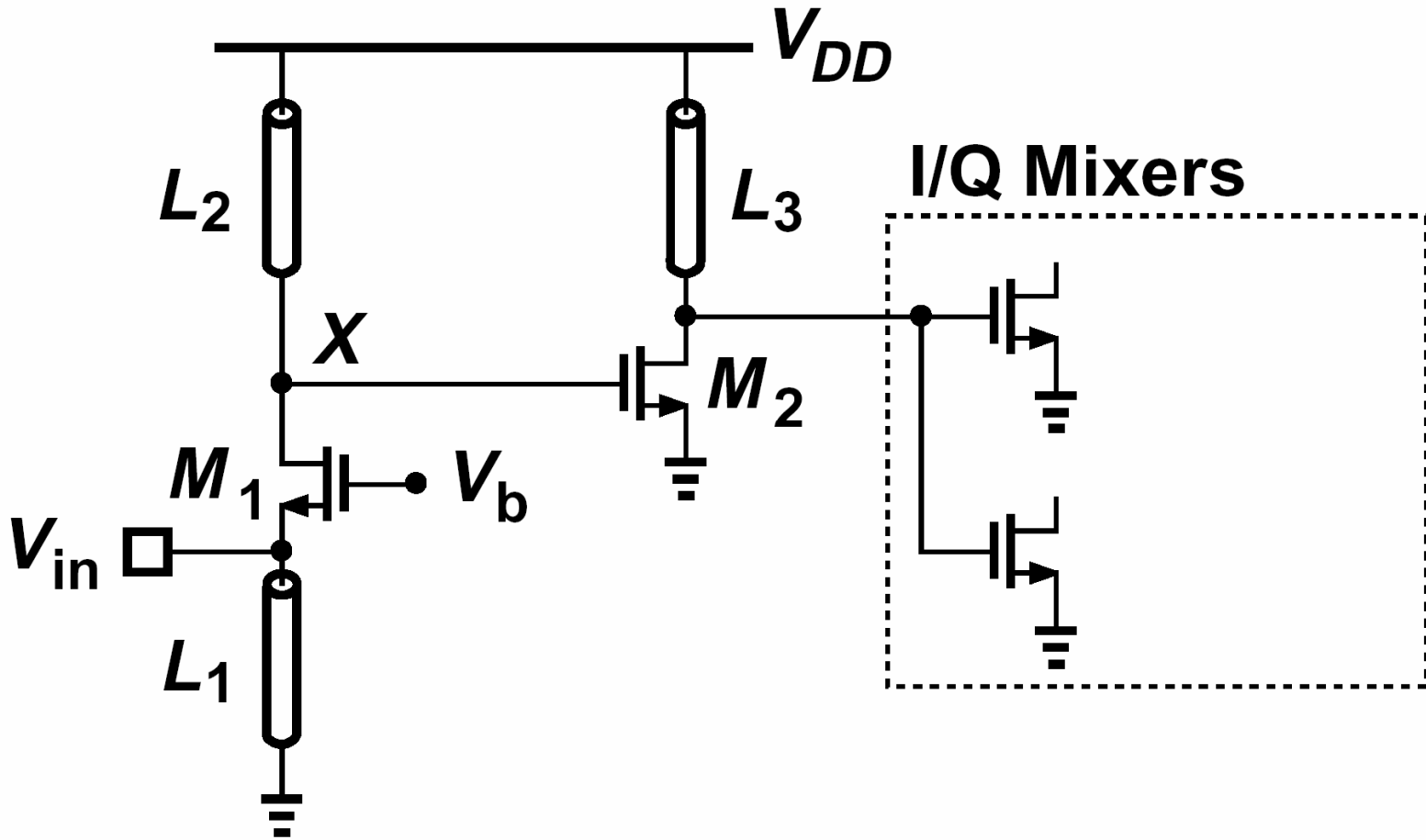



# Complete LNA

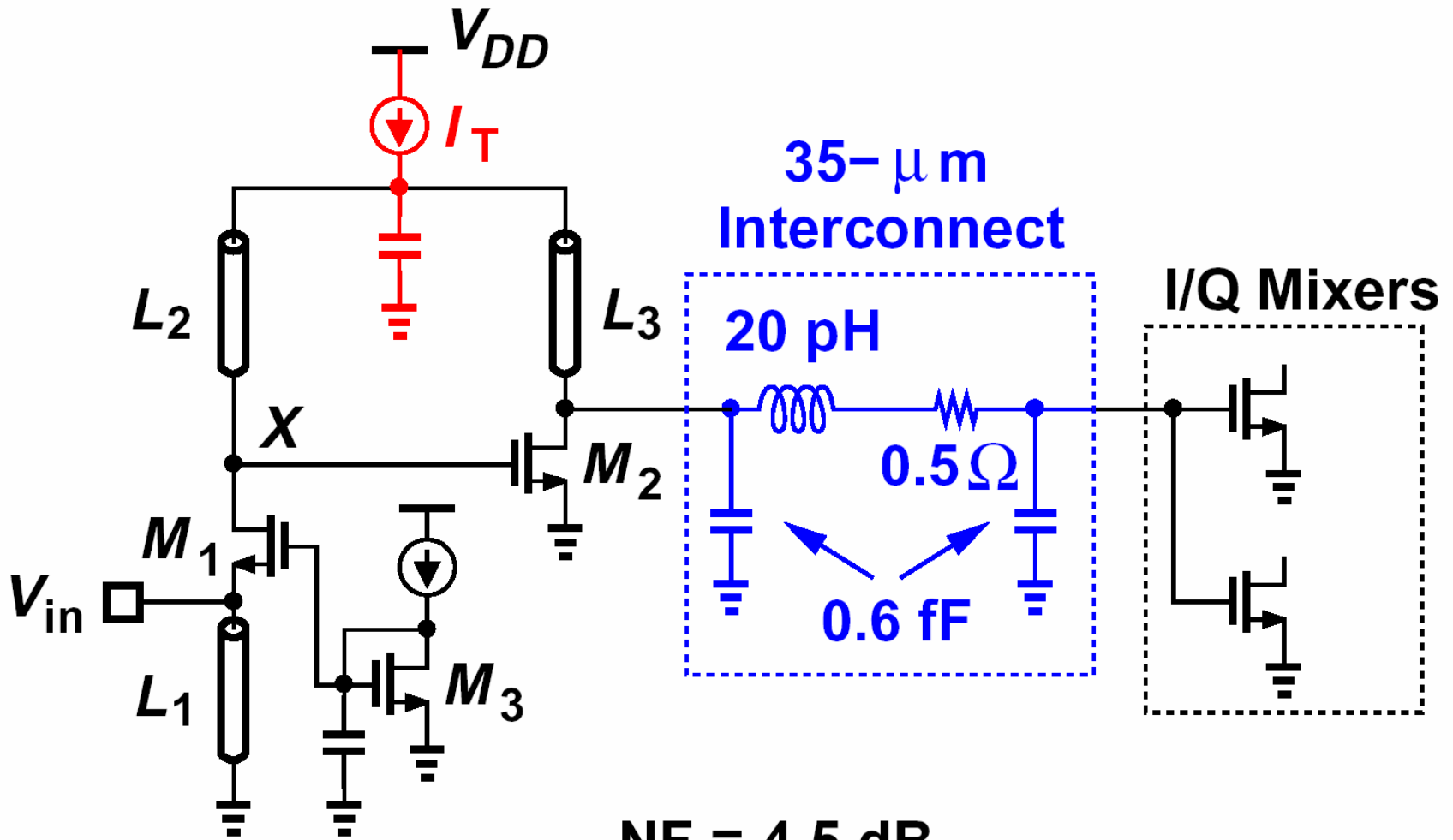


NF = 4.5 dB

Voltage Gain = 12 dB

# Mixer Design


## Conventional Mixer

 

NF = 26 dB

Conversion Gain = 0 dB


## Proposed Mixer

 

NF = 17 dB

Conversion Gain = 12 dB


# On-Chip Balun

 

$$C_1 = C_2 = C$$


$$\frac{V_X}{V_Y} = 1 - L_1 C \omega^2$$
$$= -1 @ \omega_0 = \frac{1}{\sqrt{L_1 \frac{C}{2}}}$$

# Receiver Floor Plan

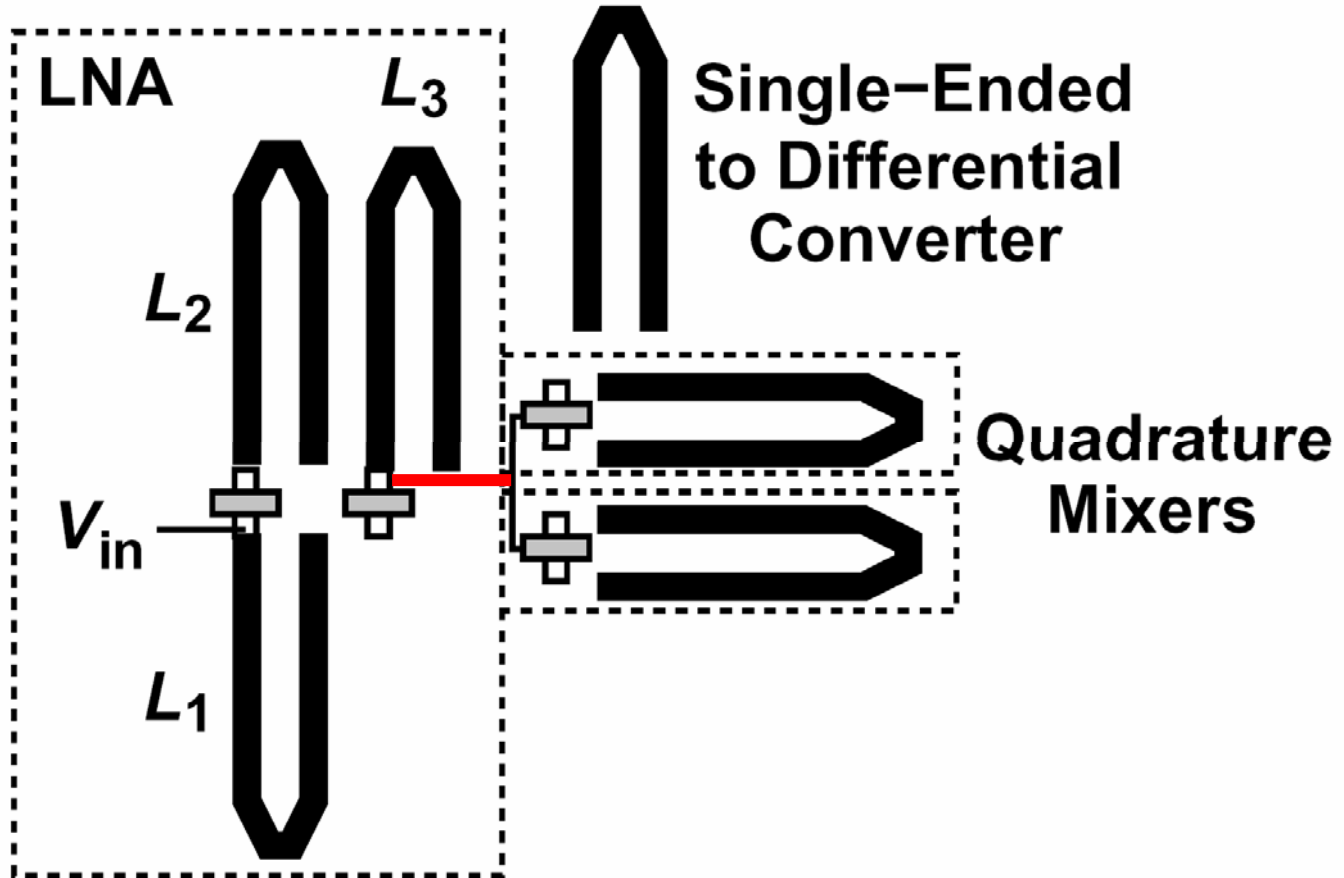

# Die Photograph

---

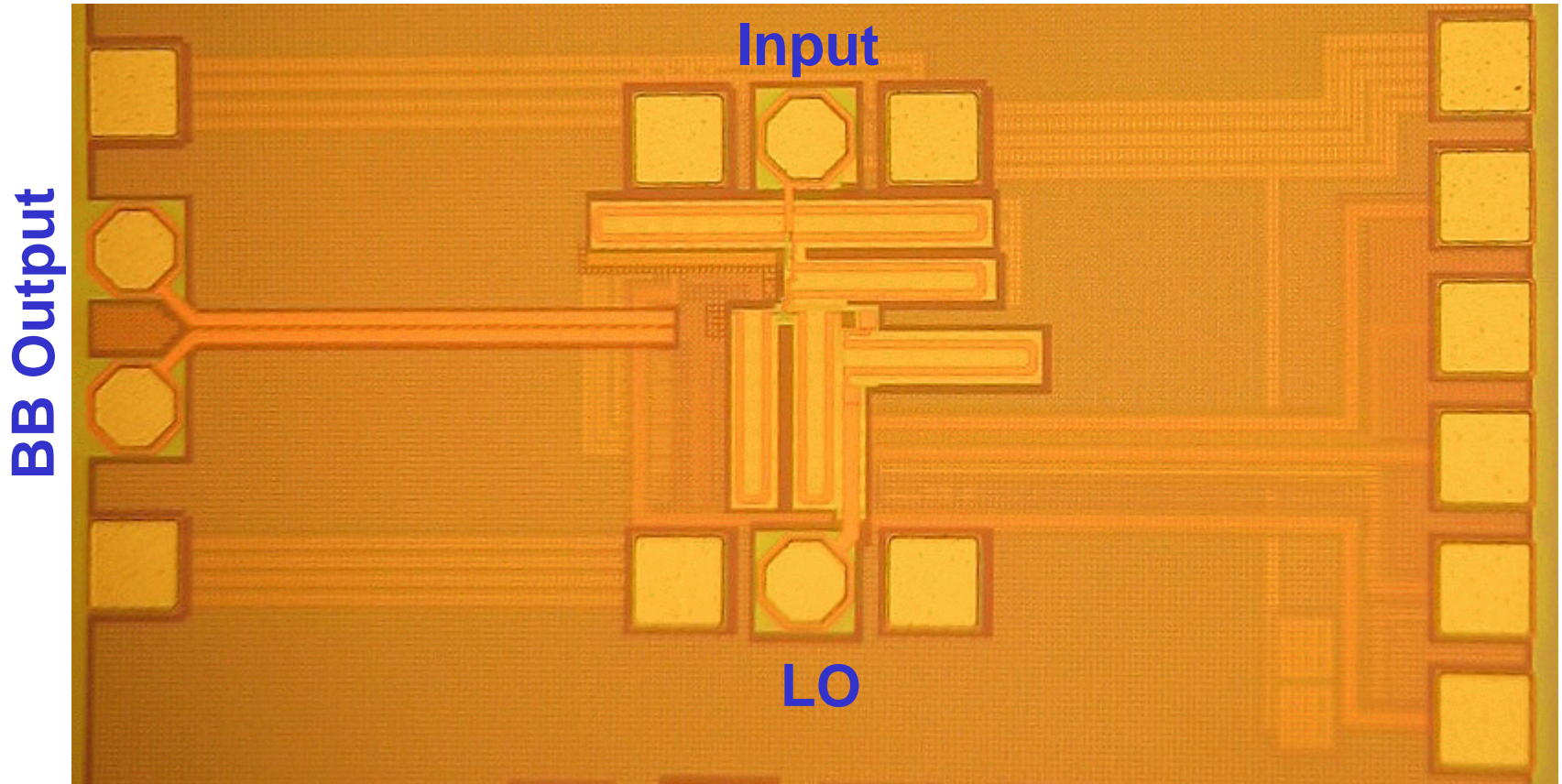

**Active Area = 300 um x 400 um**

# Measured Performance

---


---

<b>Voltage Gain</b>	<b>28 dB</b>
<b>Noise Figure</b>	<b>12.5 dB</b>
<b>1-dB Compression Point</b>	<b>-22.5 dBm</b>
<b>Power Dissipation</b>	<b>9 mW</b>
<b>Supply Voltage</b>	<b>1.2 V</b>
<b>Active Area</b>	<b>300 <math>\mu\text{m}</math> x 400 <math>\mu\text{m}</math></b>
<b>Technology</b>	<b>0.13-<math>\mu\text{m}</math> CMOS</b>

---

# Other Thoughts


---

 

- **3-dB improvement in SNR for twice the power consumption and area.**

# Transmitter Front End

---

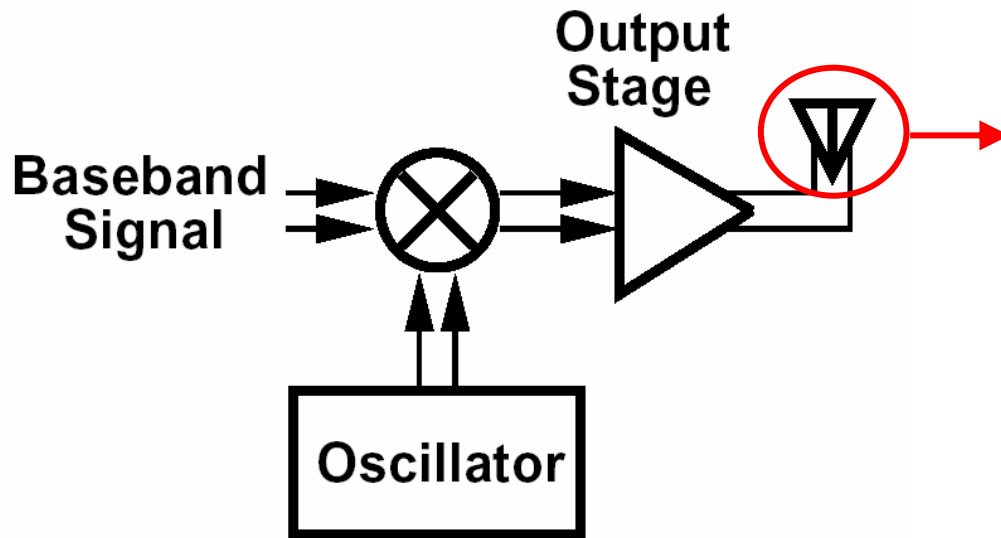


- **Slot Antenna**
  - Large Area
  - High Loss
- **Dipole**
  - Narrow Footprint
  - Moderate Loss (~6 dB)




# Transmitter Design

$$P_{\text{out}} = -10 \text{ dBm}$$

$$P_{\text{supp}} = 44 \text{ mW}$$

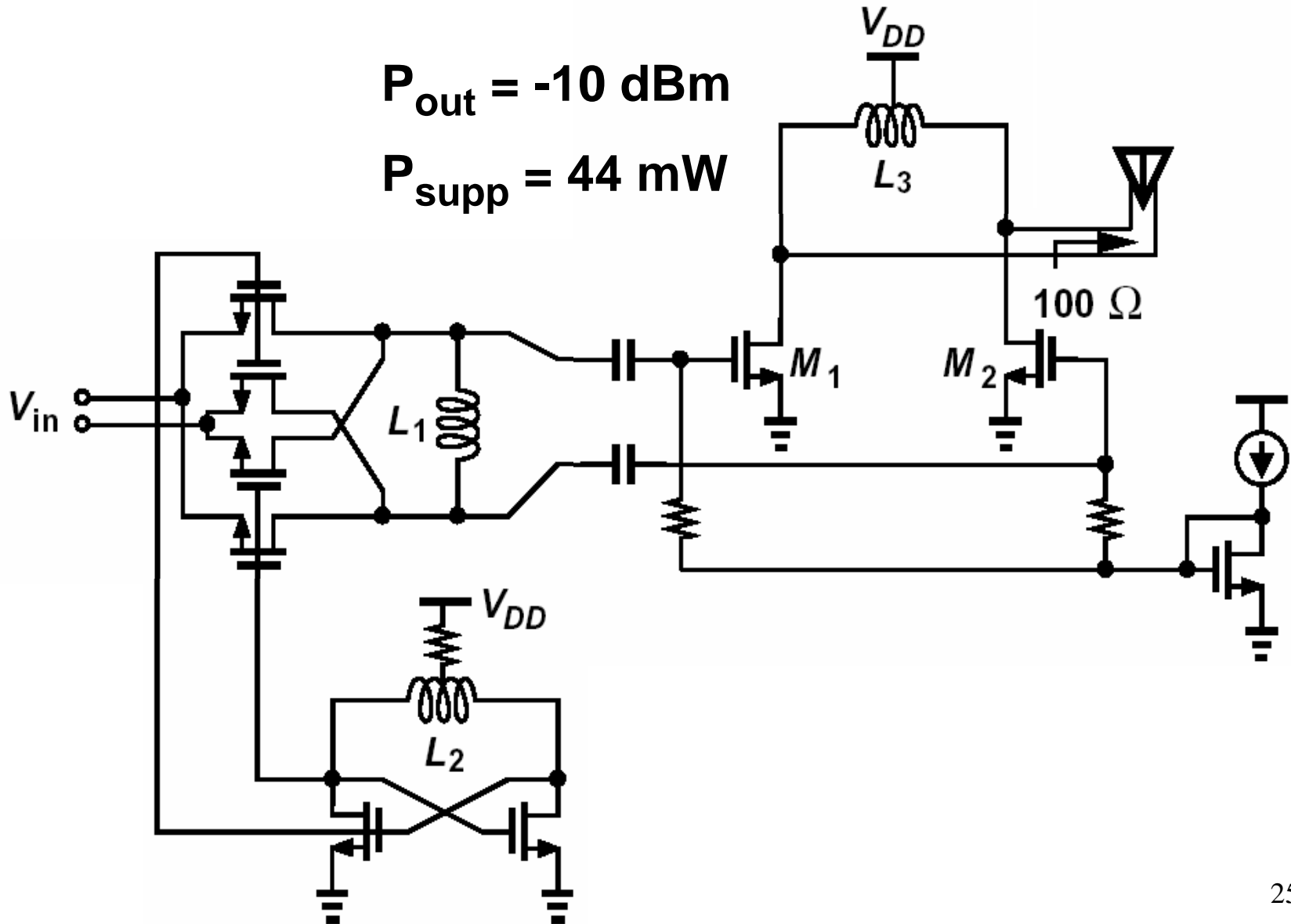


# Nested Inductors

 


# Effect of Mutual Coupling

---


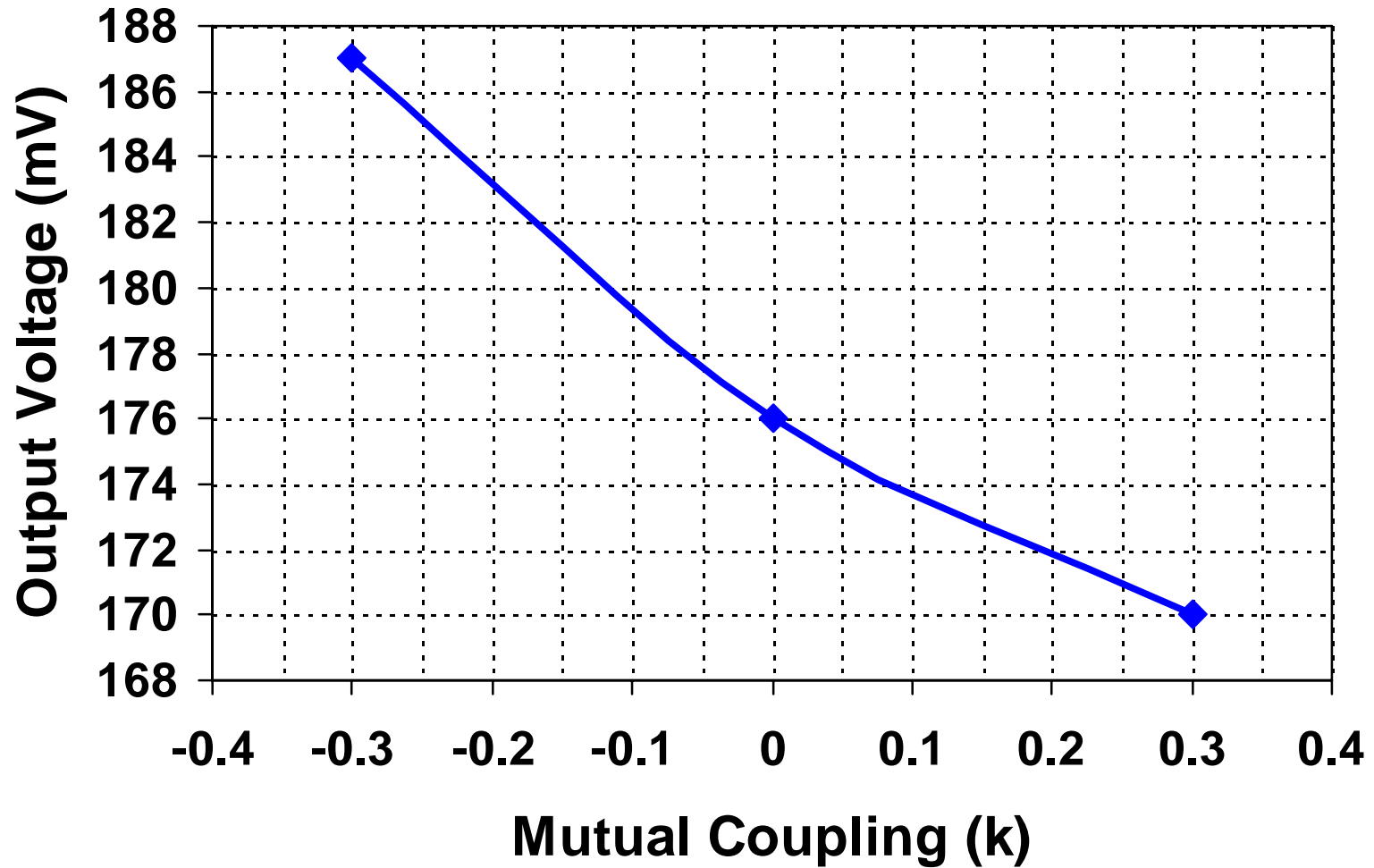


# Die Photograph


---

 

# Measurement Setup

 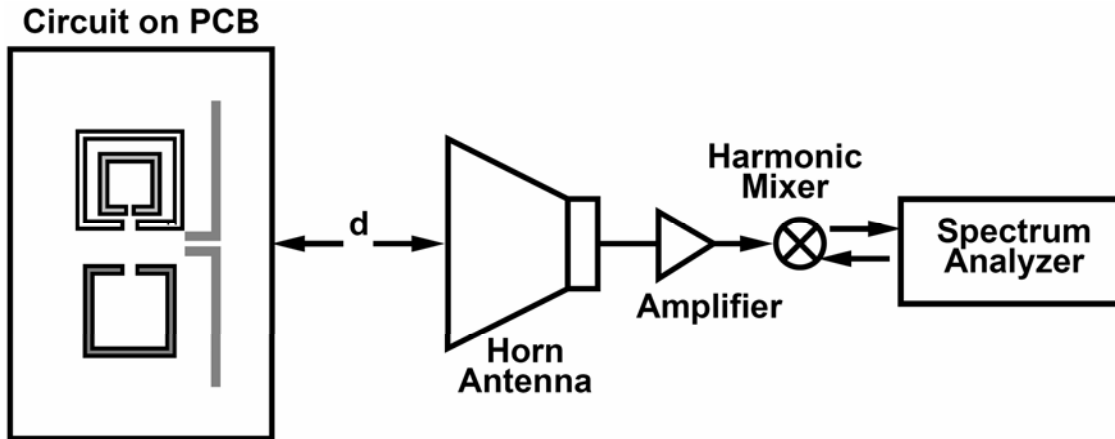

# Antenna Radiation Pattern

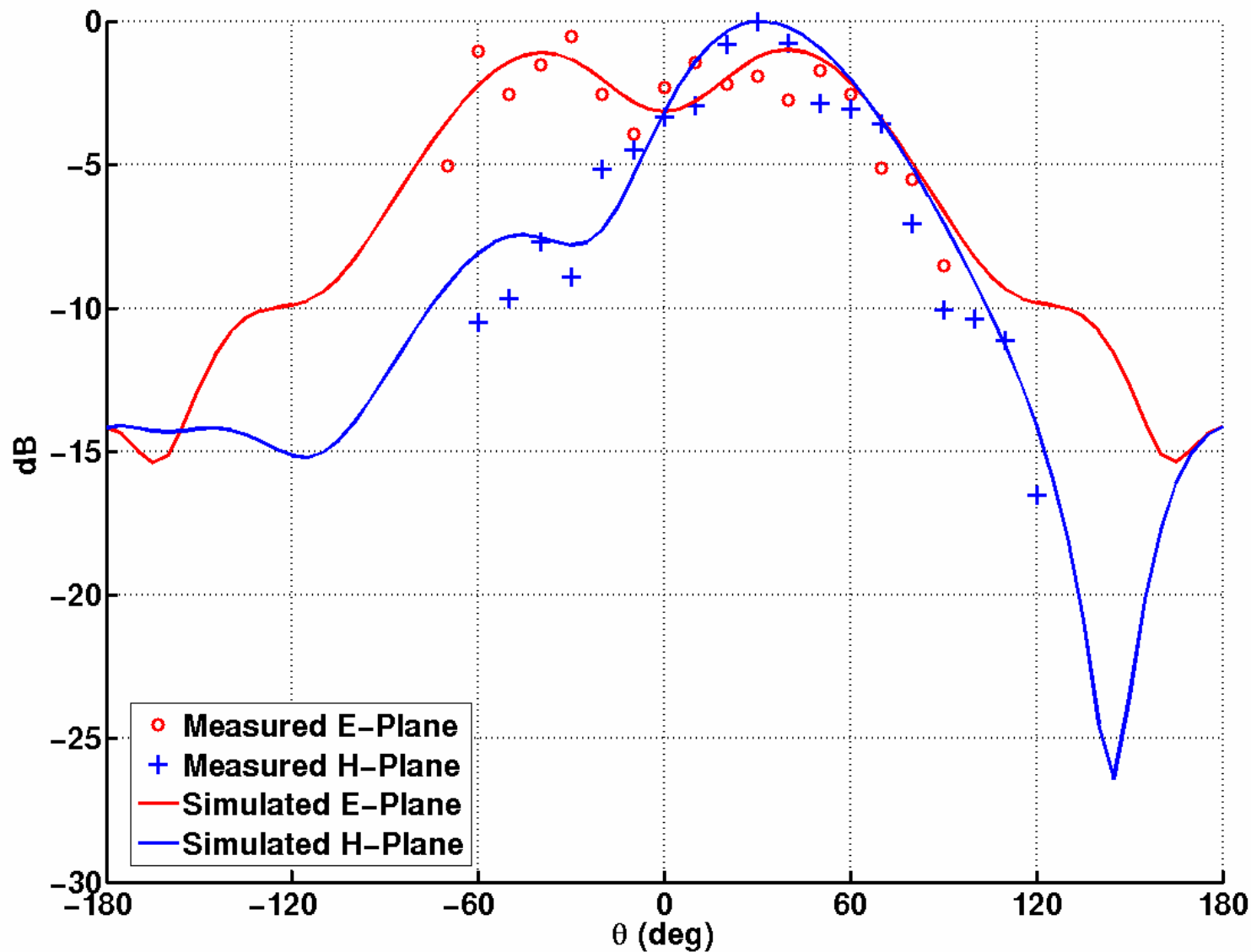


# Conventional Divider Topologies

---

- **Flipflop-Based Dividers**
- **Miller Divider**
- **Injection-Locked Divider**

# Injection-Locked Divider

 


- **Narrow frequency range; inversely proportional to tank Q:**

$$\Delta\omega = \frac{I_{inj}}{I_{osc}} \cdot \frac{\omega_0}{2Q} \cdot \frac{4}{\pi}$$





# Phase Noise Degradation

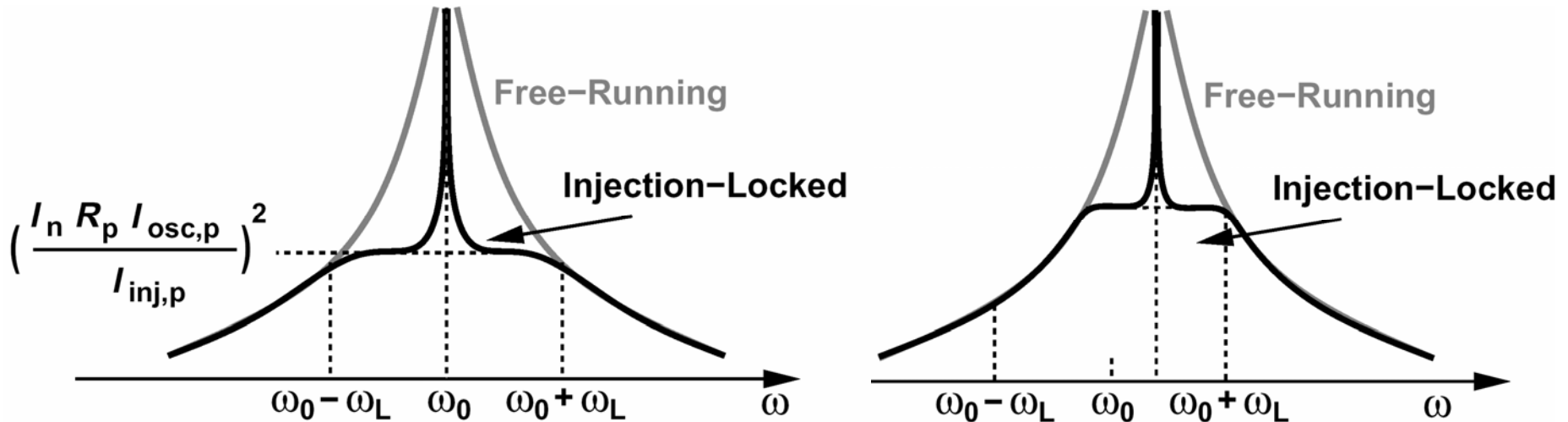

- Phase noise degrades if, due to mismatches, input frequency is not equal to  $2\omega_0$ .

# Increasing the Range

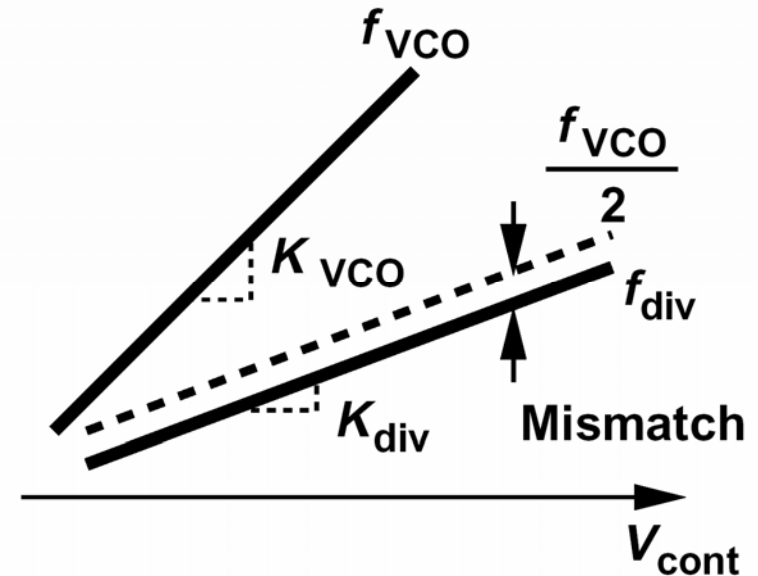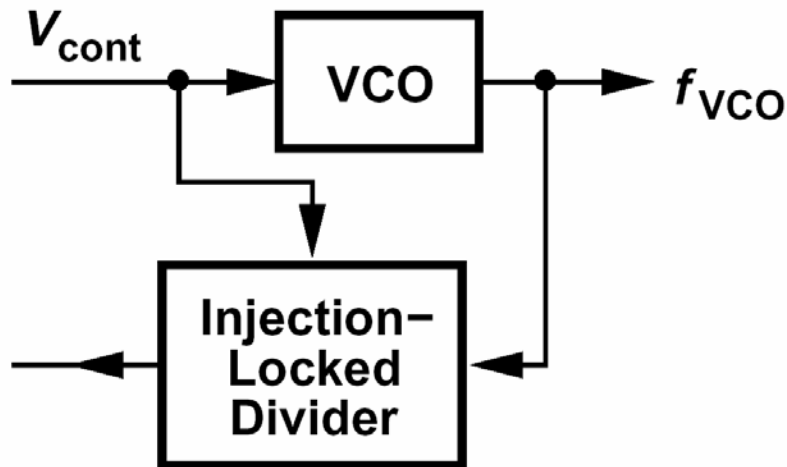


[Rategh et al, JSSC, May 00]

- ❑ Ganged tuning does not overcome frequency mismatch.
- ❑ Difficult to guarantee natural frequency of divider tracks that of VCO.


# Tracking Issues

---

 


# Phase-Locked Divider

---

 


- Constant phase noise across range if gain of PD remains constant.
- No trade-off with tank Q.
- PD circuit must be very simple and experience complete switching.

# Phase-Locked Divider

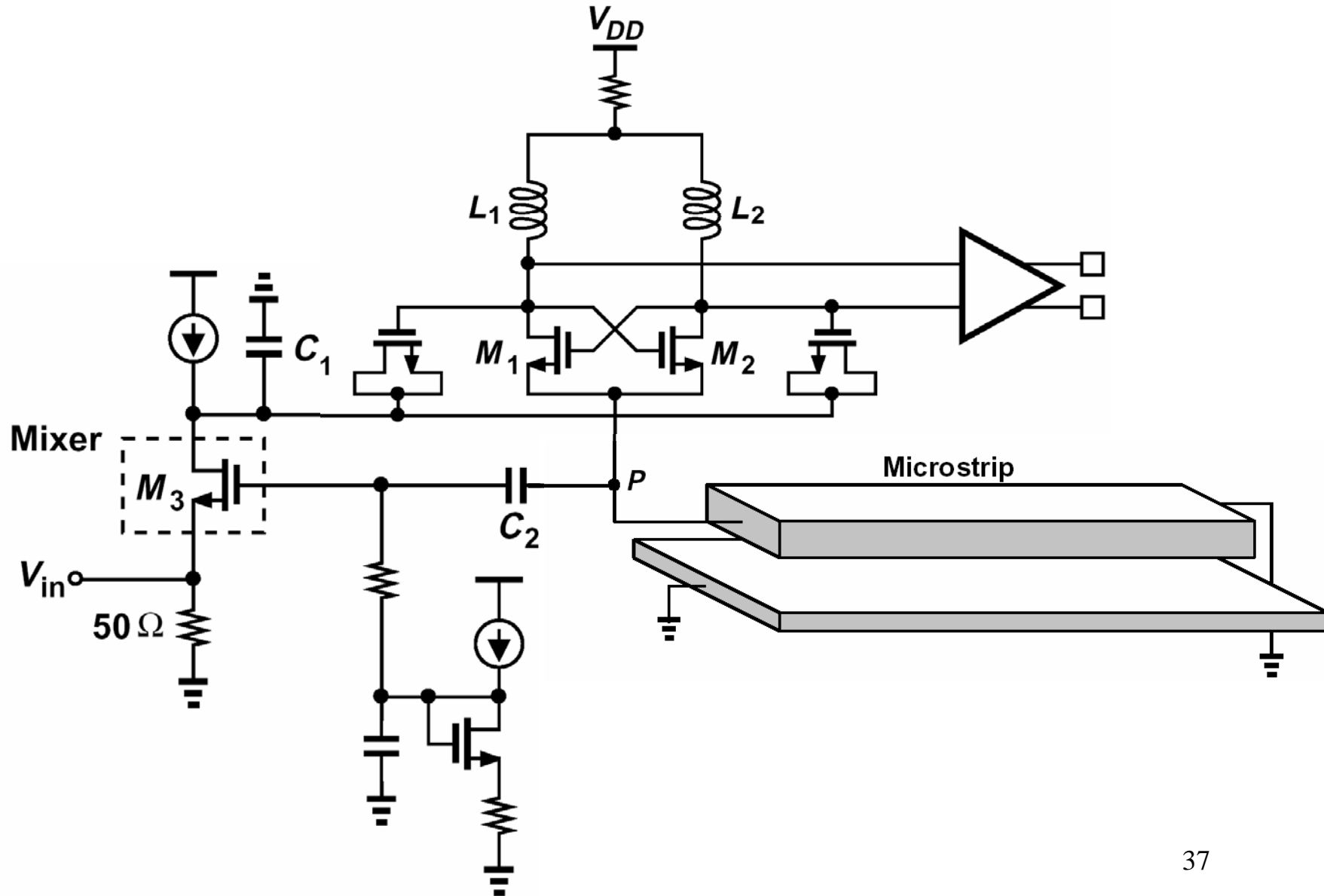


# Die Photograph


---

 

# Measured Output

 

# Phase Noise across Range

 



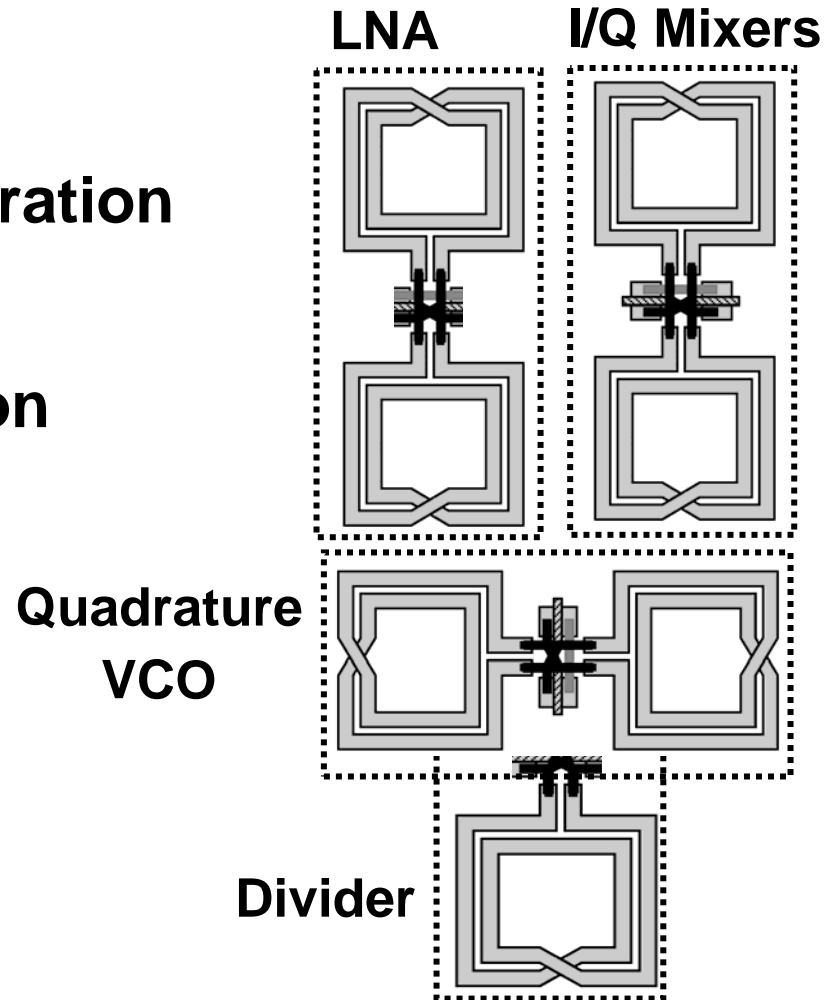
# Challenges Revisited

---

- LO (I/Q) Generation
- LO Division
- LO Distribution



# Conclusion

---

- **60-GHz transceivers can form highly-interconnected networks carrying high data rates.**
- **Nested inductors allow compact layout and shorter interconnects.**
- **Phase-locked dividers can provide a wide frequency range.**
- **Direct-conversion transceivers face difficult issues with respect to LO generation, division, and distribution.**