



IBM Research

Topics in Design and Analysis of High Data Rate SERDES Systems

Troy Beukema
IBM T. J. Watson Research Center
Yorktown Heights, NY

Table of Contents

- **Introduction**
- **S-Parameter Overview**
- **Link Models**
- **Performance Analysis**
- **Line Equalization**
- **Clock and Data Recovery**
- **Jitter Analysis**
- **20-25Gb/s I/O Systems**
- **Digital/ADC I/O**
- **Appendix**

Introduction : Drivers of High Data Rate Interconnect


Observation : there is **no end** to the desire for higher interconnect bandwidth!

“Video” Internet
Driving exponential bandwidth growth


3D memory $\geq 2\text{Gb}$
GP GPU $\geq 1\text{Tflop}$
driving PCI BW and GPU memory BW

Multiple Tb storage and SSD driving disk I/O BW

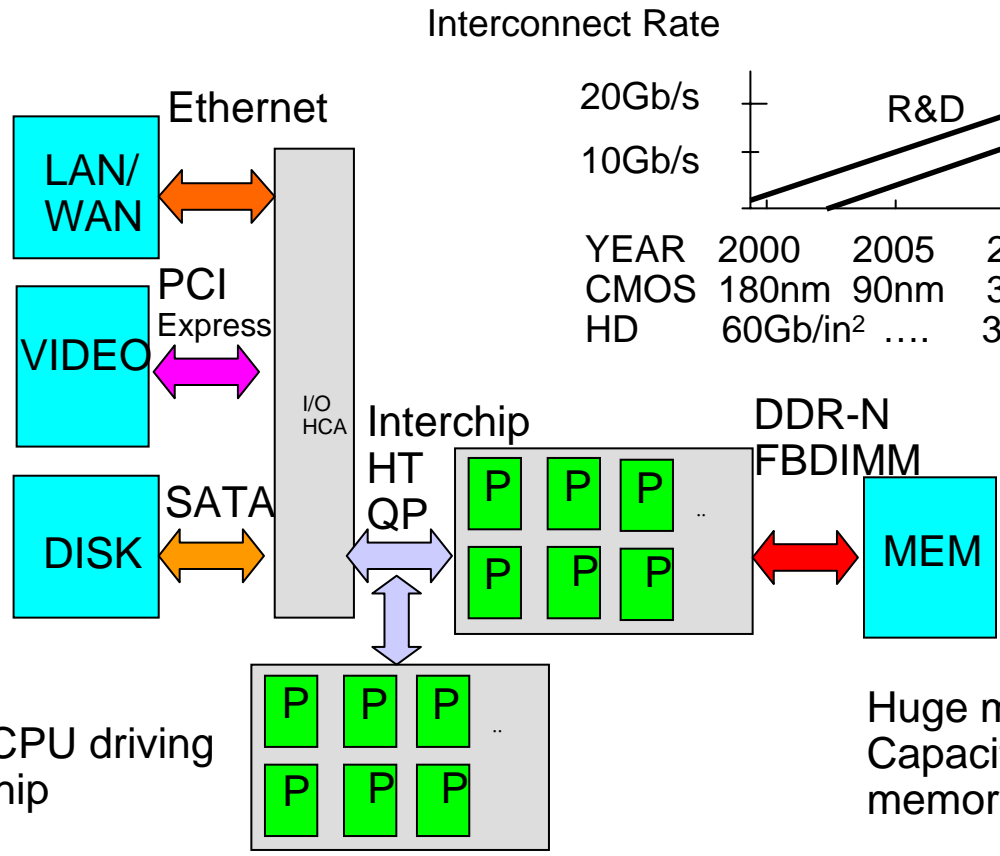Multiple Processor CPU driving memory and inter-chip communication BW




Interconnect Rate

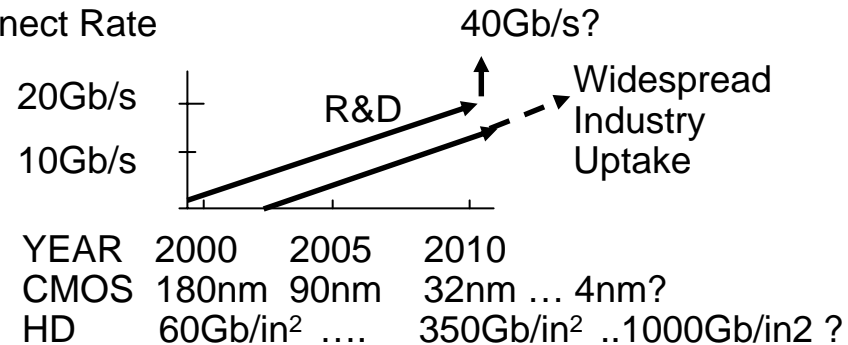

#P <- 1, 2, 4, 6, 8, 12, 16, 32, 64,


Data Interconnect Applications

Chip-To-Chip : C2C

 


HyperTransport, QuickPath (6G)

Chip-To-Mem : C2M

 


GDDR5 (6G), FB-DIMM

Chip-To-Board : C2B

 


PCI Express Gen 3 (8G)

Chip-To-Peripheral : C2P

 

SATA3 (6G) USB 3.0 (4.8G) 1394b 3200

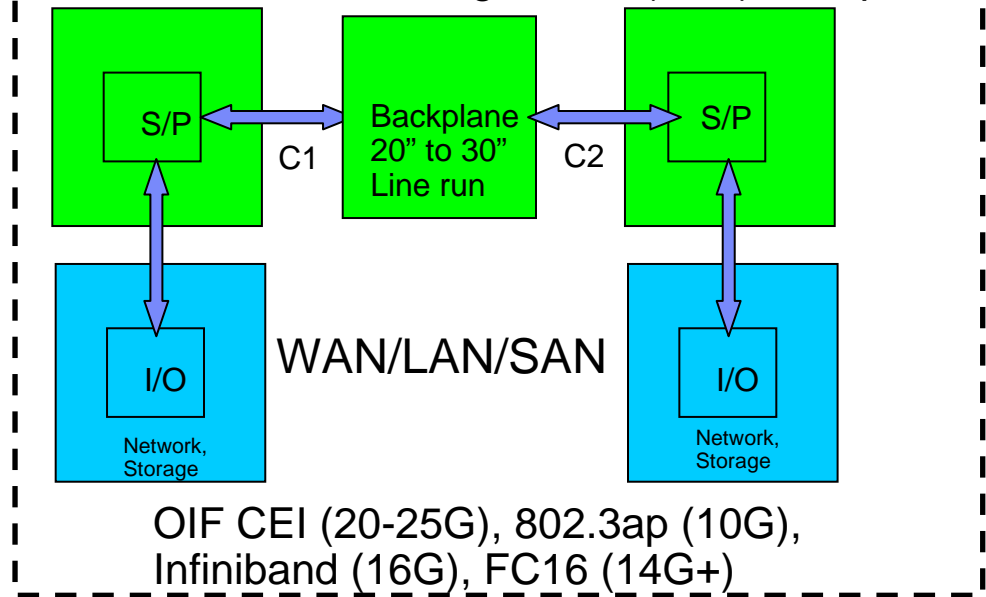
Board-To-Board : Long Reach ("LR") Backplane



OIF CEI (20-25G), 802.3ap (10G),
Infiniband (16G), FC16 (14G+)

Focus of presentation


Point-to-Point SERDES I/O Architecture

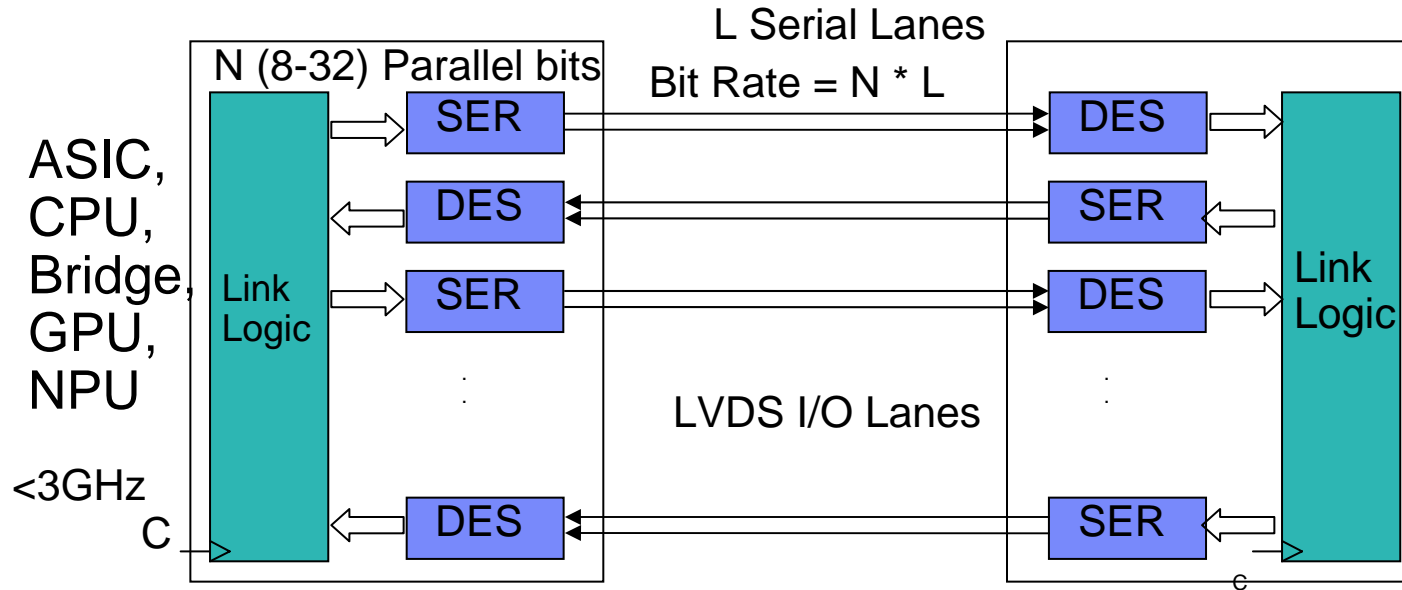

Why Use SERDES I/O Architecture?

 - 1) Impossible to escape chip with $N * L$ parallel lines due to package pin density limits
- 2) Data skew for wide parallel synchronous buses becomes a problem at high data rates
- 3) Clock Recovery/Equalization on L lines needed instead of $N * L$ lines : Simplifies receiver
- 4) Point-to-Point impedance-controlled I/O eliminates signal degradation from parallel "stub bus"

Anatomy of a Backplane Serial Interconnect System



Processor/Network Model


 
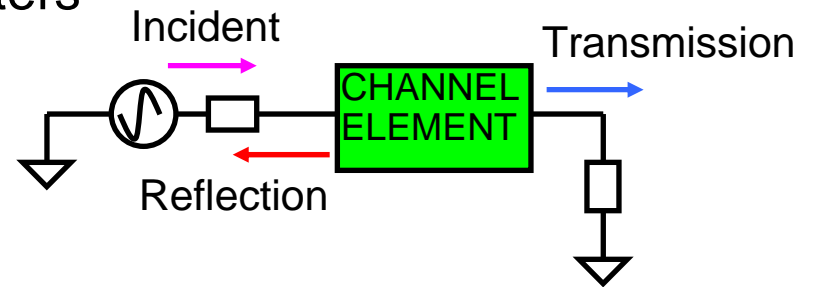
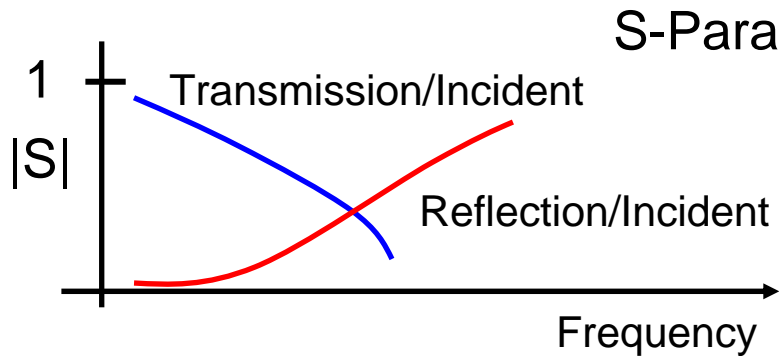


Table of Contents


- Introduction
- **S-Parameter Overview**
- Link Models
- Performance Analysis
- Line Equalization
- Clock and Data Recovery
- Jitter Analysis
- 20-25Gb/s I/O Systems
- Digital/ADC I/O
- Appendix

Channel Models with S-Parameters

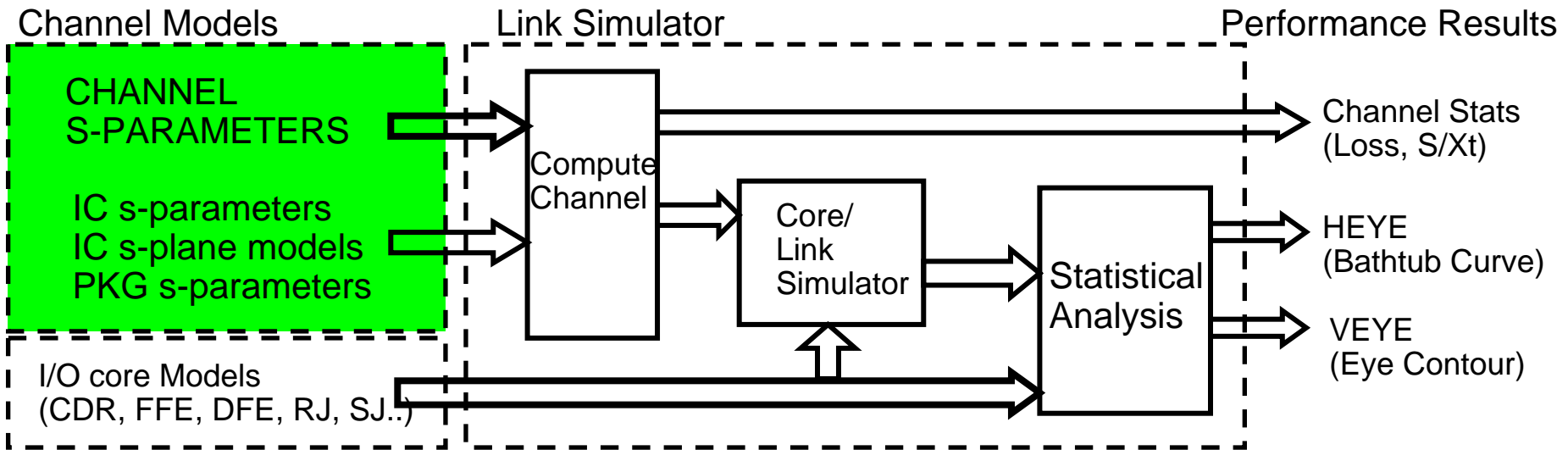I/O system performance analysis typically starts with Scattering (S)-parameter descriptions of the frequency response of the application channel and I/O core.



 S-Parameter/Frequency-Domain Based Link Modeling



Basic “End-to-End” Serial Channel


Each component of the serial link is modeled as an S-parameter, or possibly a rational s-plane pole/zero model

The “End-to-End” channel is found by cascading the S-parameters


After cascading the S-parameters, the channel time-domain impulse response is found using a Frequency to Time Transform.

S-parameter models are typically created by a combination of the IC Manufacturer (IC and package models) and the system OEM (backplane+daughter-cards)

 Power of S-Parameters : Efficiently Describe Parallel Bus N-Port Models



32-Port S-Parameter L

 


$FEXT = [1,14,3,16]L,$
 $[5,14,7,16]L,$
 $[9,14,13,16]L = \text{FAR END CROSSTALK}$

$THRU = [13,14,15,16]L = \text{“VICTIM” LINE}$

$NEXT = [18,14,20,16]L,$
 $[22,14,24,16]L,$
 $[26,14,28,16]L,$
 $[30,14,32,16]L = \text{NEAR END CROSSTALK}$

Sources of S-Parameters

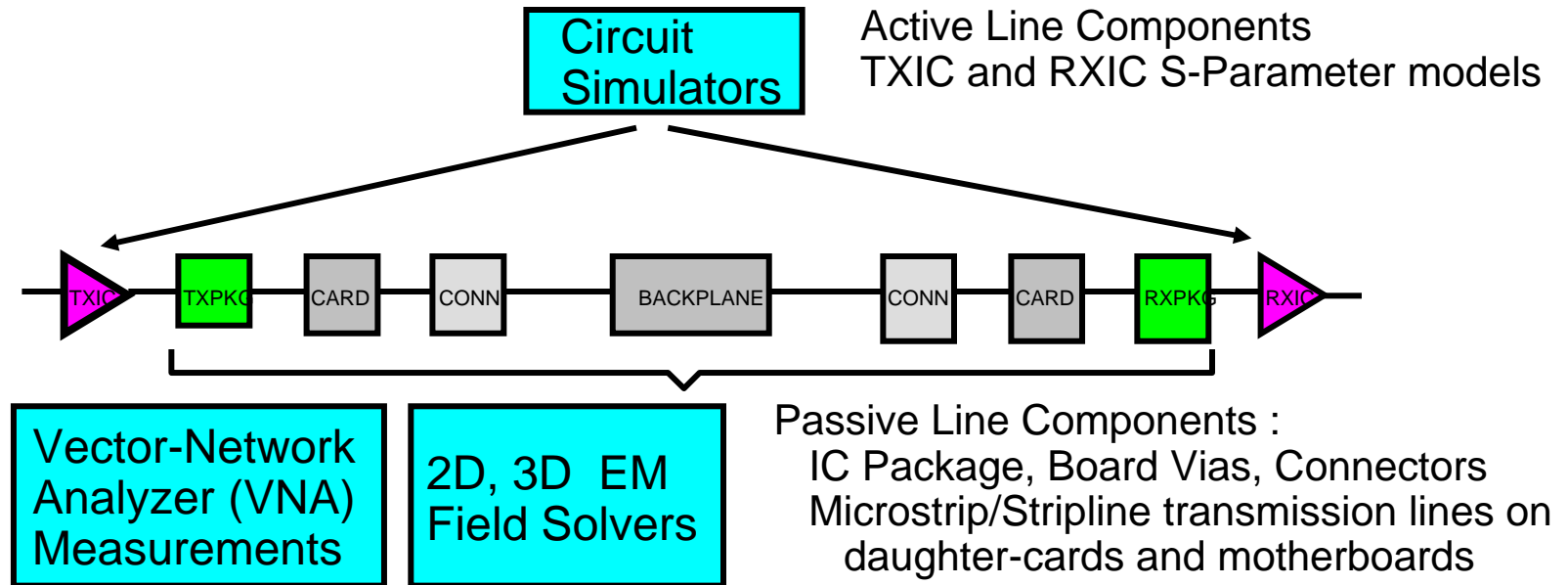

Advantages of S-parameters based channel analysis :

- “Real” hardware brought into computer simulations through VNA measurements
- Unifies disparate link building blocks to one common format


Disadvantages :

- Need linear channel assumption
- Invalid s-parameters easy to generate
(bad/noisy/miscalibrated measurements or invalid 2D/3D EM models)
- May require causality-passivity correction before use

Formal S-Parameter Definition and N-Port Matrix Representation

S-Parameters are defined as the ratio of a signal level transmitted out of a port to an incident signal sent into an excitation port, where all ports are terminated in a fixed impedance called the reference impedance.

Reflection Parameter

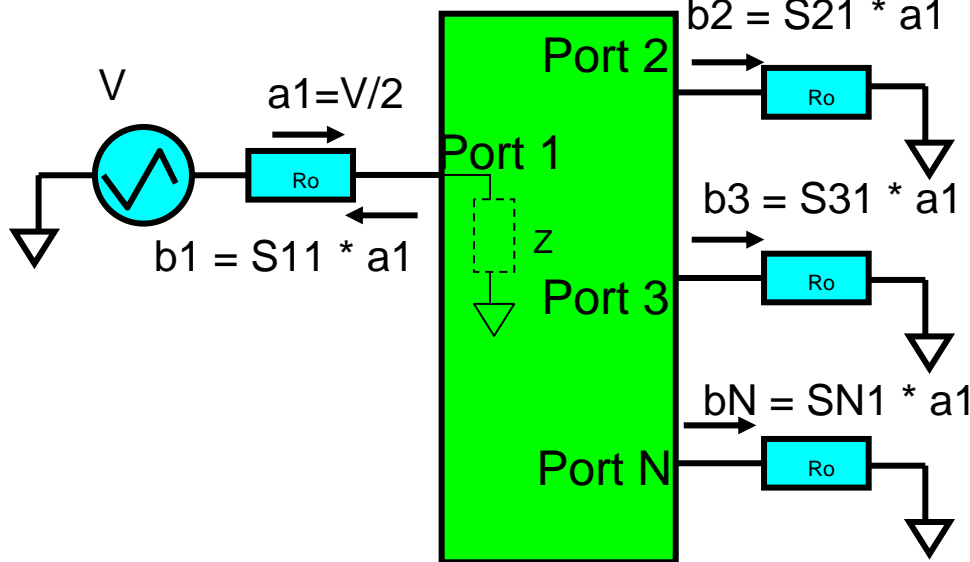


Transmission Parameters

Outputs S-parameter matrix Incident Voltages

$$\begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_N \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1N} \\ S_{21} & S_{22} & \dots & S_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ S_{N1} & S_{N2} & \dots & S_{NN} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ \vdots \\ a_N \end{bmatrix}$$

Nomenclature :

 


See Appendix A.1 for Derivation of S-Parameters from Port Node Voltages

4-port S-parameters and Mixed-Mode S-Parameter Representation

Most high rate SERDES systems use differential signaling, where a signal is Encoded as P-N where P is the voltage on a positive line and N is the voltage on a negative line. A 4-port S-parameter can describe this differential channel.

 Odd In / Even Out preferred port numbering convention :



D = Differential Port Voltage $\triangleq (V_p - V_n)$
 C = Common Port Voltage $\triangleq (V_p + V_n)$

Nomenclature :

Destination Port Source Port

SDD21

Destination
Port Mode
(C or D)

Source Port Mode
(C or D)

See Appendix A.2 for conversion between single-ended and mixed-mode s-parameter formats

Mixed Mode Matrix Representation

There is no standard convention for storing mixed-mode S-parameters!

All of these matrices represent the same S-parameter information in different formats :

Single-Ended S-parameters Matrix

$$\begin{array}{c}
 1 \quad 2 \quad 3 \quad 4 \\
 \begin{bmatrix}
 1 & S_{11} & S_{12} & S_{13} & S_{14} \\
 2 & S_{21} & S_{22} & S_{23} & S_{24} \\
 3 & S_{31} & S_{32} & S_{33} & S_{34} \\
 4 & S_{41} & S_{42} & S_{43} & S_{44}
 \end{bmatrix}
 \end{array}$$

Mixed-Mode S-parameters Matrix #1

$$\begin{array}{c}
 D1 \quad D2 \quad C1 \quad C2 \\
 \begin{bmatrix}
 D1 & S_{DD11} & S_{DD12} & S_{DC11} & S_{DC12} \\
 D2 & S_{DD21} & S_{DD22} & S_{DC21} & S_{DC22} \\
 C1 & S_{CD11} & S_{CD12} & S_{CC11} & S_{CC12} \\
 C2 & S_{CD21} & S_{CD22} & S_{CC21} & S_{CC22}
 \end{bmatrix}
 \end{array}$$

Mixed-Mode S-parameters Matrix #2

$$\begin{array}{c}
 D1 \quad C1 \quad D2 \quad C2 \\
 \begin{bmatrix}
 D1 & S_{DD11} & S_{DC11} & S_{DD12} & S_{DC12} \\
 C1 & S_{CD11} & S_{CC11} & S_{CD12} & S_{CC12} \\
 D2 & S_{DD21} & S_{DC21} & S_{DD22} & S_{DC22} \\
 C2 & S_{CD21} & S_{CC21} & S_{CD22} & S_{CC22}
 \end{bmatrix}
 \end{array}$$


Mixed-Mode S-parameters Matrix #3

$$\begin{array}{c}
 11 \quad 12 \quad 21 \quad 22 \\
 \begin{bmatrix}
 D1D2 & S_{DD11} & S_{DD12} & S_{DD21} & S_{DD22} \\
 D1C2 & S_{DC11} & S_{DC12} & S_{DC21} & S_{DC22} \\
 C1D2 & S_{CD11} & S_{CD12} & S_{CD21} & S_{CD22} \\
 C1C2 & S_{CC11} & S_{CC12} & S_{CC21} & S_{CC22}
 \end{bmatrix}
 \end{array}$$

Use of mixed-mode S-parameters in model data-bases, or as input to simulators is not recommended : **Probability (getting wrong answer) = ~1**, with no warnings!

Transport Parameters

 Transport Parameters re-arrange the s-parameter port variables so inputs are on LHS and outputs on RHS. This enables two series transport-parameters to be cascaded.



$$\begin{matrix} \text{INPUT} \\ \text{OUTPUT} \end{matrix} \begin{bmatrix} B1 \\ B2 \end{bmatrix} = \begin{bmatrix} S11 & S12 \\ S21 & S22 \end{bmatrix} \begin{matrix} \text{INPUT} \\ \text{OUTPUT} \end{matrix} \begin{bmatrix} A1 \\ A2 \end{bmatrix}$$

$$\begin{matrix} \text{INPUT} \\ \text{INPUT} \end{matrix} \begin{bmatrix} B1 \\ A1 \end{bmatrix} = \begin{bmatrix} T11 & T12 \\ T21 & T22 \end{bmatrix} \begin{matrix} \text{OUTPUT} \\ \text{OUTPUT} \end{matrix} \begin{bmatrix} A2 \\ B2 \end{bmatrix}$$


$$\begin{aligned} B1 &= S11 A1 + S12 A2 \\ B2 &= S21 A1 + S22 A2 \end{aligned}$$

$$\begin{aligned} B1 &= T11 A2 + T12 B2 \\ A1 &= T21 A2 + T22 B2 \end{aligned}$$

See Appendix A.3 for conversion between 2-port T and S parameters

Intermediate Line Probes with S-Parameters

Intermediate Line Probe at RxBGA

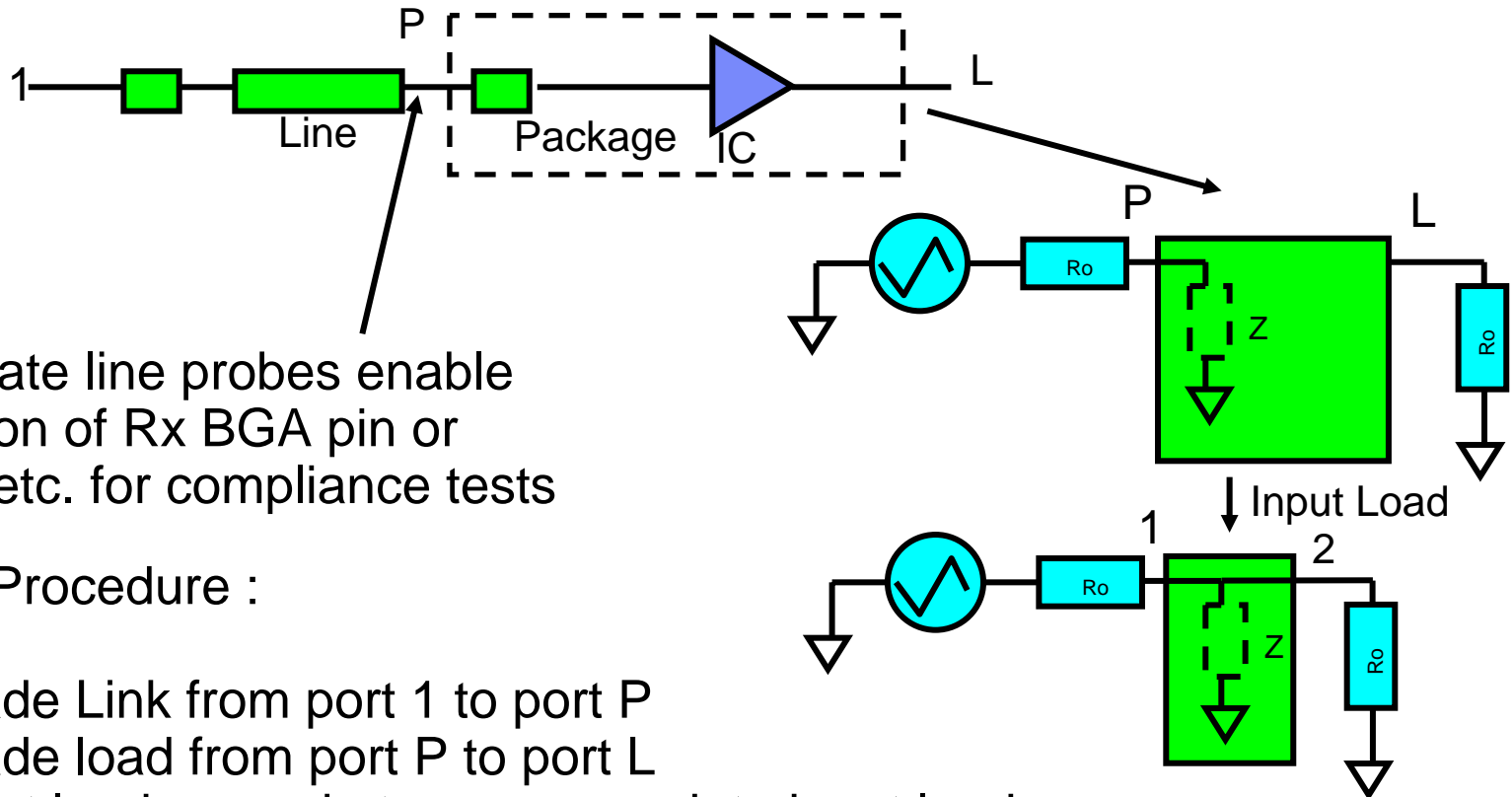


Intermediate line probes enable observation of Rx BGA pin or Tx BGA, etc. for compliance tests

Analysis Procedure :

 - 1) Cascade Link from port 1 to port P
- 2) Cascade load from port P to port L
- 3) Convert load cascade to an appropriate input load
- 4) Cascade input load to end of first cascade
- 5) Cascade -50 ohm load to remove s-parameter probe impedance at probe point

Multidrop Cascading with S-Parameters

Multi-Drop Cascade (“Stub” Channel Analysis)




Multi-Drop Cascades enable analyzing 1-to-Many bus structures, typically found in “legacy” interconnect designs

Analysis Procedure :

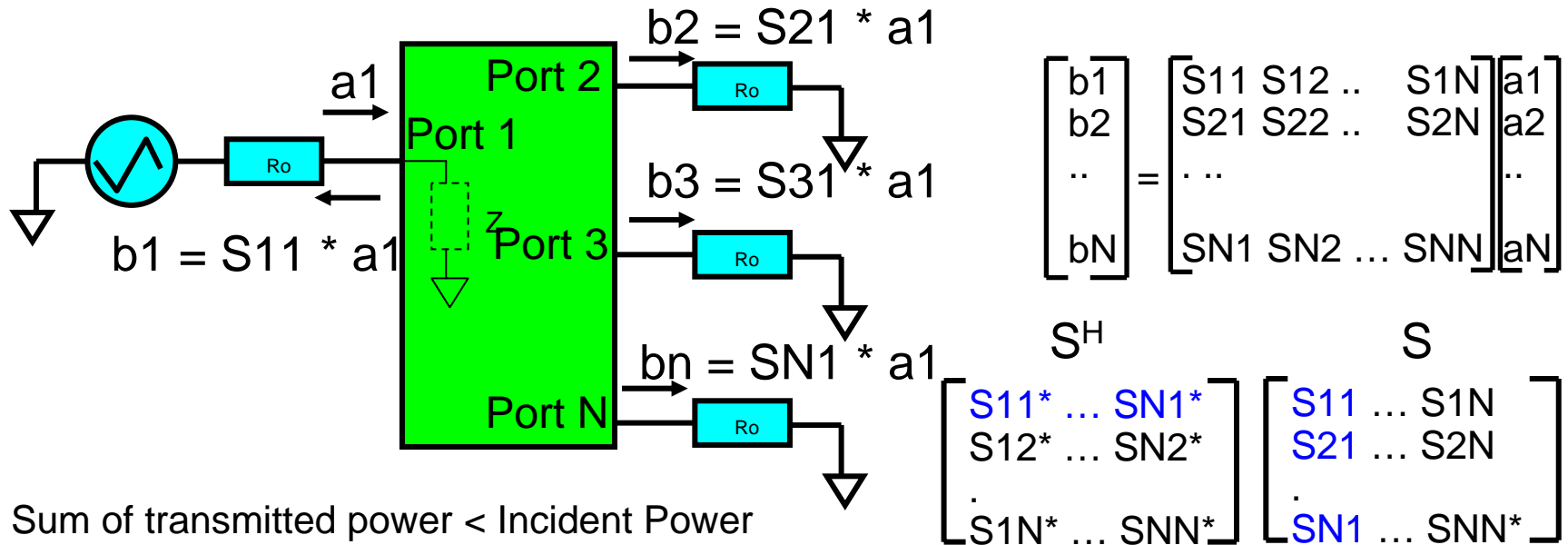- 1) Cascade Link from port 1 to port M
- 2) Cascade multidrop load from port M to port 3
- 3) Convert load cascade to an appropriate input load
- 4) Cascade input load of M->3 load
- 5) Finish cascading link from port M to 2

Checking Validity of S-Parameters : Passivity Requirement



1) Sum of transmitted power < Incident Power

$$\rightarrow |b1|^2 + |b2|^2 + \dots |bn|^2 < |a1|^2$$

$$\rightarrow \text{Re}\{S11 * \text{conj}(S11)\} + \text{Re}\{S21 * \text{conj}(S21)\} + \dots \text{Re}\{\text{conj}(SN1) * SN1\} < 1$$


In the general case, $\sum |bi|^2 \leq \sum |ai|^2 \rightarrow S^H S \leq I$, where S^H = conjugate-transpose

2) all the S-parameter frequency responses must satisfy causality constraints (non-causal -> non-passive)

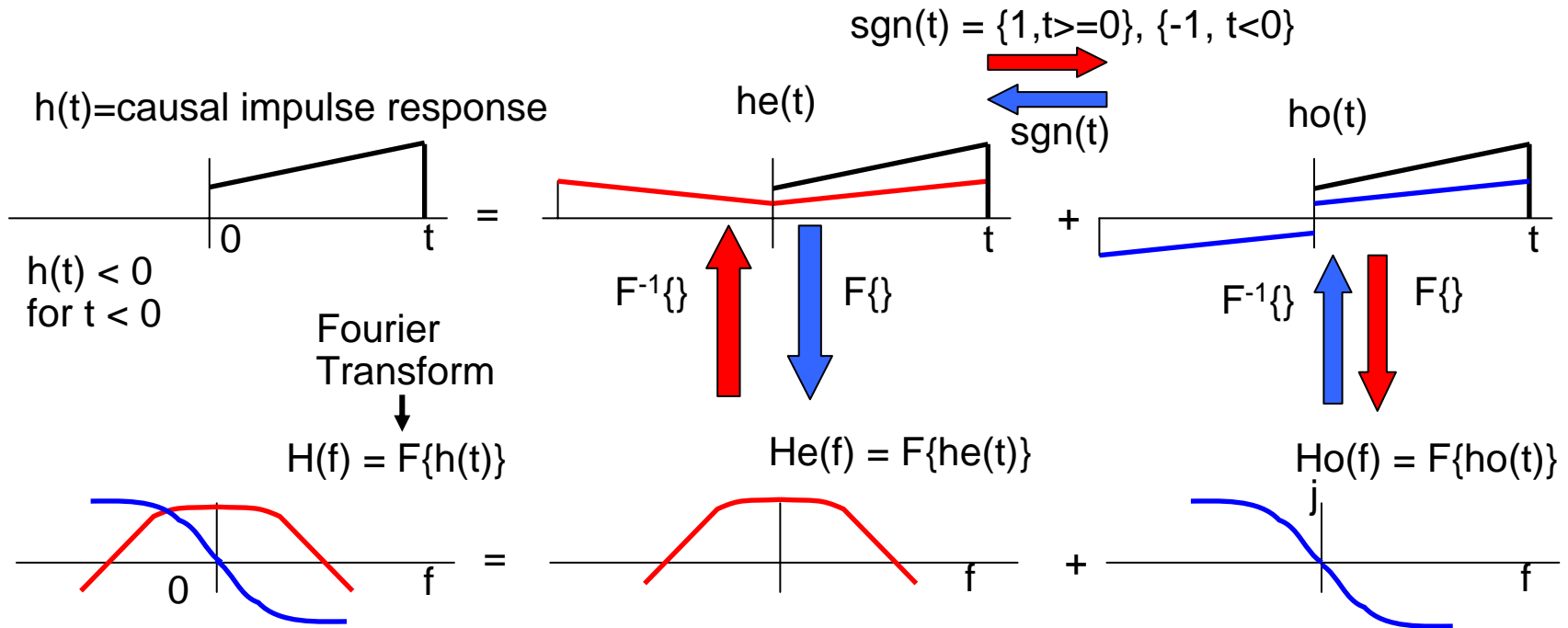3) All the S-parameter frequency responses must satisfy :
 $S_{ij}(j\omega) = \text{conj}(S_{ij}(-j\omega))$

Reference : "Stability, Causality, and Passivity in Electrical Interconnect Models", Triverio et. al. , IEEE TRANSACTIONS ON ADVANCED PACKAGING, VOL. 30, NO. 4, NOVEMBER 2007, pp. 801-803

Causality of (S-Parameter) Frequency Responses



For causality to hold, $h_o(t) = \text{sgn}(t) h_e(t)$, $\rightarrow H_o(f) = F\{\text{sgn}(t) h_e(t)\} = F\{\text{sgn}(t)\} \text{ conv } H_e(f)$
 also, $h_e(t) = \text{sgn}(t) h_o(t)$, $\rightarrow H_e(f) = F\{\text{sgn}(t) h_o(t)\} = F\{\text{sgn}(t)\} \text{ conv } H_o(f)$


Hilbert Transforms

Hazard :


Many model-generated and measured S-parameters do not satisfy the causality constraint and require numerical correction! Non-causality can arise from “non-causal” models or measurement errors.

Some S-parameter Mistakes to Avoid

 1) Cascading differential 2-ports is not the same as a 4-port differential cascade




 2) Do not use floating sources to measure differential s-parameters in simulators




This has been seen in commercial EDA tools!

 3) Do not leave ports floating when making crosstalk measurements



Victim and aggressor ports need termination on both input and output for valid crosstalk measurements

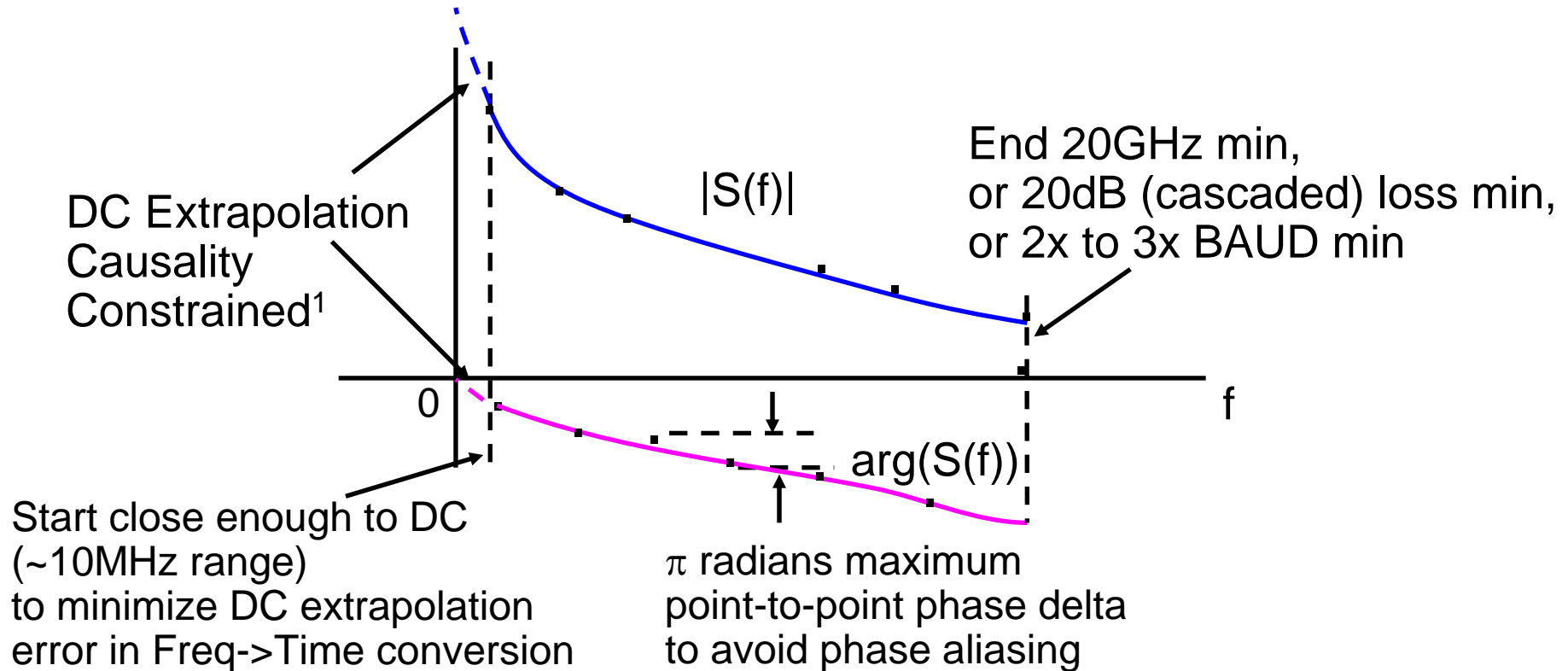Frequency Sampling Grid and DC Extrapolation for S-Parameters




USEFUL SAMPLING GRIDS (START and STEP the same) :

- 5MHz to 20GHz in 5MHz STEPS (4000 POINTS)
- 10MHz to 20GHz in 10MHz STEPS (2000 POINTS)
- 20MHz to 20GHz in 20MHz STEPS (1000 POINTS)


¹P. Triverio, S. Grivet-Talocia, "Causality-constrained interpolation of tabulated frequency responses"
<http://www.emc.polito.it/publications/file/cnf-2006-eep-DCreconstruction.pdf>

 Efficiency of S-Parameter Cascade Analysis vs. Nodal Analysis



CHANNEL CASCADE : ~17 Elements

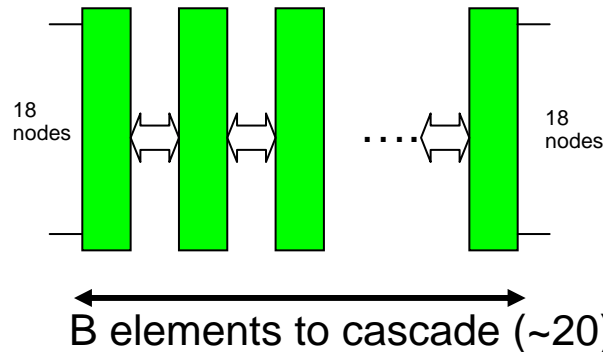N (36) port s-parameters
to describe 9 diff
pairs (4 aggressors on
either side of a victim)



Cascade analysis : $B * O(3)$ for N-ports = $B * N^3$

Nodal Analysis : $(B+1) * (N/2)$ NODES $\sim BN/2$ NODES, $O(3) \leftarrow (BN/2)^3$

Complexity Ratio = $B^2 / 8$, for $B = 10-20$ elements, speed ratio = 10-50

S-Parameter Cascade Analysis 10X to 50X faster than Nodal Analysis

36-port cascades readily concatenated on 2G SSE Laptops in ~minutes

Summary of S-Parameters for Link Modeling

Major Advantages :

- +Describes “real” hardware measurements in addition to models
- +Models coupling in wide data buses
- +Can describe both passive line elements and active circuits : captures the “end-to-end” link.
- +Versatile analysis capability : multidrop links, intermediate line probes
- +Computationally efficient in solving wide bus problems

Some Disadvantages :

- Linear channel assumption
- Finite frequency range, accuracy of s-parameters at low and high frequency can degrade in both measurements and models



Some Caveat Emptors :

- *Beware of invalid passivity and causality, undersampling, and insufficient frequency range : many s-parameters in the wild are inconsistent / invalid due to one or more of these problems.
- *No standard storage convention for Differential Mode : confusing and prone to resulting in misuse/wrong answers

Table of Contents


- Introduction
- S-Parameter Overview
- **Link Models**
- Performance Analysis
- Line Equalization
- Clock and Data Recovery
- Jitter Analysis
- 20-25Gb/s I/O Systems
- Digital/ADC I/O
- Appendix

  A Parametric RLGC Transmission Line Model



$$Z_o(\omega) = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

Characteristic impedance

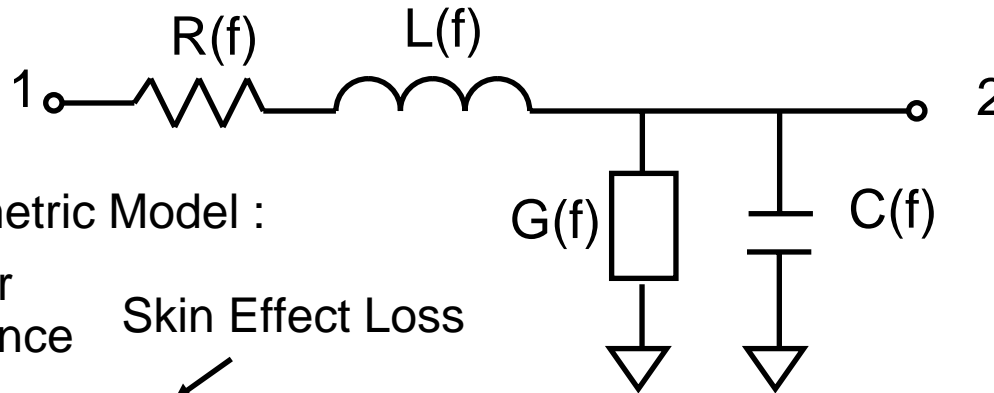

$$\gamma(\omega) = \sqrt{(R+j\omega L)(G+j\omega C)}$$

Propagation Constant

Parametric Model :

Copper resistance

Skin Effect Loss

$$R(f) = R_o + \text{sqrt}(f) * R_f$$

$$L(f) = L_o - L_f * \text{sqrt}(f) / (L_f^2 + \text{sqrt}(f))$$


$$G(f) = G_o + f * G_f$$

$$C(f) = C_o$$

Dielectric Loss


L_o at low freq, $(L_o - L_f)$ at high freq

S-Parameter Derivation from RLGC Models

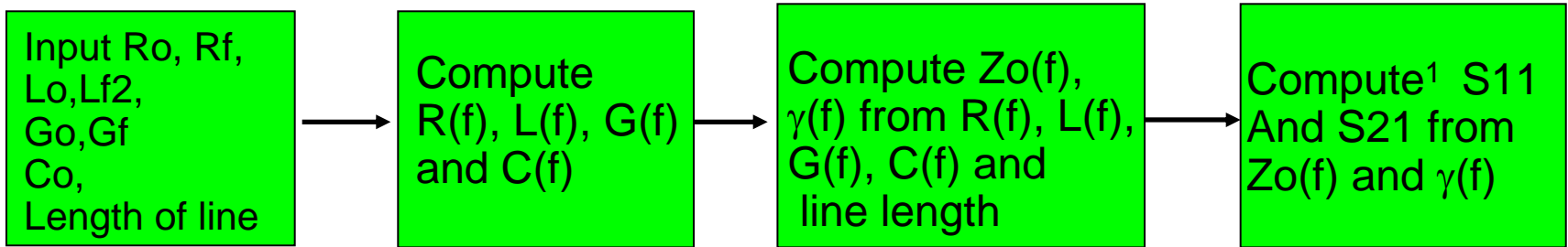

 Example Parameters :


- Ro=2 ohm/meter
- Lo=4.428e-7 henry/meter
- Go=0
- Co=1.25e-10F/meter
- Rf=1.63e-03
- Lf=1.4386e-7
- Gf=8e-12
- Lf2=3500
- l = 30inches



Causality Correct S11, S21


¹See Appendix A.4 for computation of S11 and S21 from Zo and γ

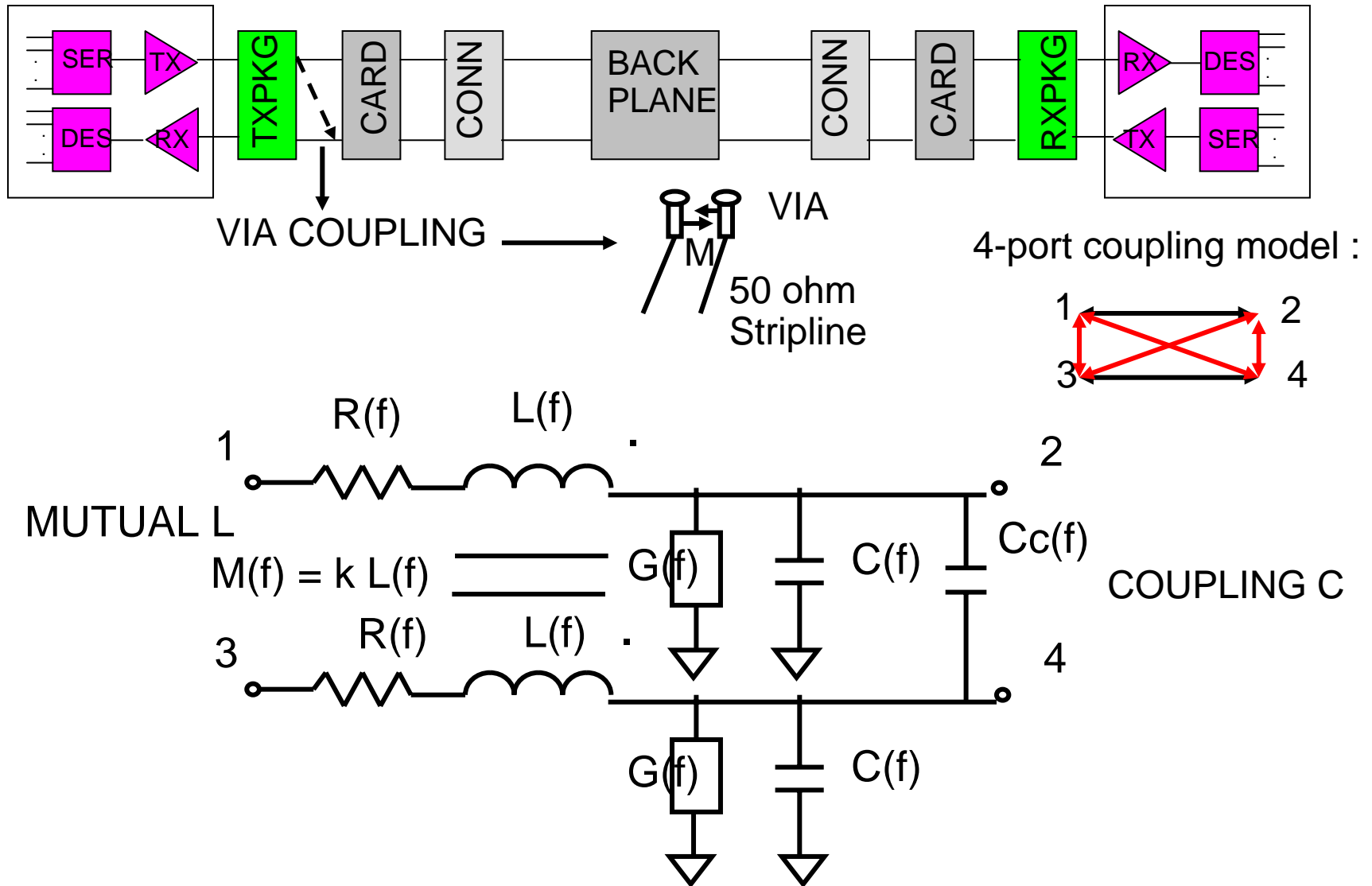A Coupled Line RLGC Transmission Line Model



Capacitive and Inductive Coupling Responses

 INDUCTIVE COUPLING (VIA) 3mm line, $M(f) = 0.3L(f)$, $C_c=0$




FREQ->TIME




Inductive coupling :
Initial impulse falls

IMPULSE RESPONSE

 


 CAPACITIVE COUPLING 3mm line, $M(f) = 0$, $C_c=26fF/mm$




+11mV Peak

 capacitive coupling :
Initial impulse rises



A Differential Signaling Coupling Example

 8-port differential coupling model built from 3 4-port coupled lines



3mm line

$$M(f) = 0.3L(f), C_c=0$$



|SDD23|

[5,2,7,4]L Channel Response

Crosstalk reduced 6dB
Compared to SE

IMPULSE RESPONSE



[5,2,7,4]L Impulse Response

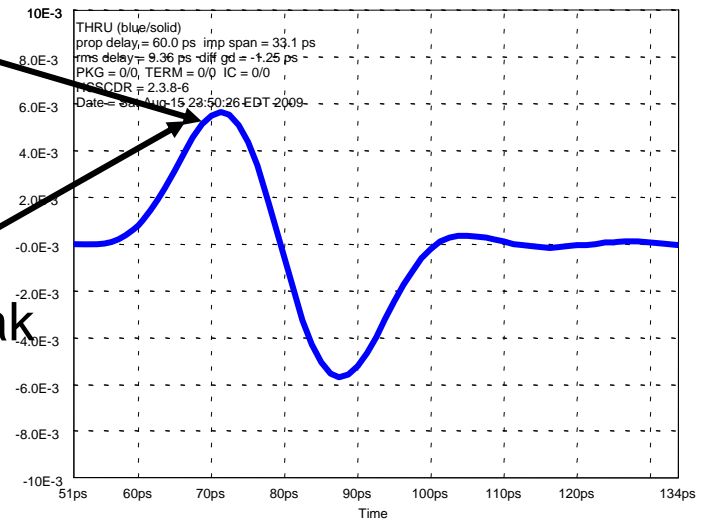 


6mVpd Peak
Inverted
Polarity

Concatenated 8-Port Net Model with Via Coupling FEXT and NEXT


 
 
FEXT is normally much smaller than NEXT since it is attenuated along with signal on line.



S/Xt

 

Impedance Discontinuity from Via

   


Via is not a uniform transmission line model.... can cause significant impedance discontinuity if via geometry/stub becomes significant with respect to data transition frequency.

Closely spaced vias in a "via field" "breakout region" can also introduce significant crosstalk.


Via length and number must be minimized in high data rate systems!

IC Modeling with S-Parameters

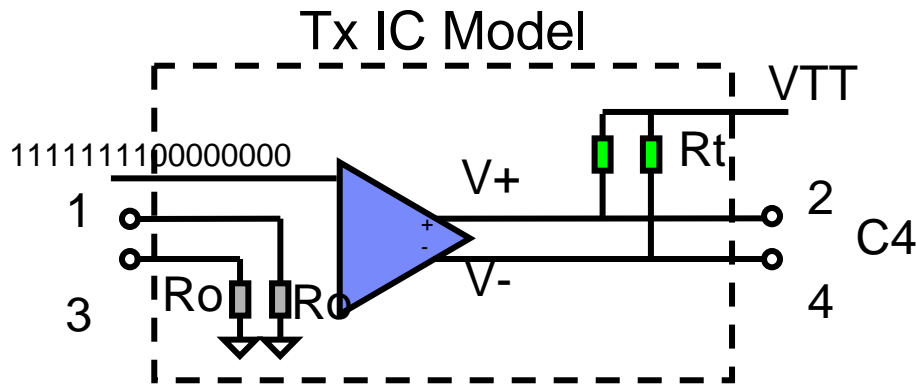

Forward Transmission :
 Derive S_{21}/S_{42} from
 Step Response
 (1111111100000000 data)

 Output Reflection :
 Measure 2-port S-parameters
 at ports 2 and 4
 to get S_{44} , S_{22} , S_{42} , S_{24}




HI-Z TERMINAL NODES

S-Parameters Computation :
 Probe latch with ideal VCVS
 terminated in R_o

Measure 4-port S-Parameters

 Pole-Zero Behavioral Models for IC Response Modeling




Pole-Zero models are useful to represent programmable Continuous-Time Equalizers (CTEs) in SERDES ICs. In discrete-time simulators, they are easily converted to time domain digital filters via the (bilinear) Z-transform.

Pole-Zero models can also be fit to s-parameter responses, to enable transient simulators to incorporate s-parameters models.

Table of Contents



- Introduction
- S-Parameter Overview
- Link Models
- **Performance Analysis**
- Line Equalization
- Clock and Data Recovery
- Jitter Analysis
- 20-25Gb/s I/O Systems
- Digital/ADC I/O
- Appendix

System Performance Analysis

 


System Performance Analysis steps performed by Link Simulator :

  - 1) Compute end-to-end channel response from channel models :
 - Cascade S-parameters
 - Combine Pole-Zero models, if any, with S-Parameters
 - Determine time-domain impulse response of channel
- 2) Determine HEYE and VEYE from channel impulse response combined with I/O core behavioral model using either pure statistical analysis, or discrete-time system simulation




Time Conversion Example : Impulse Response of 30" RLGC T-Line

[THRU,30i] Channel Response

 

Impulse Response

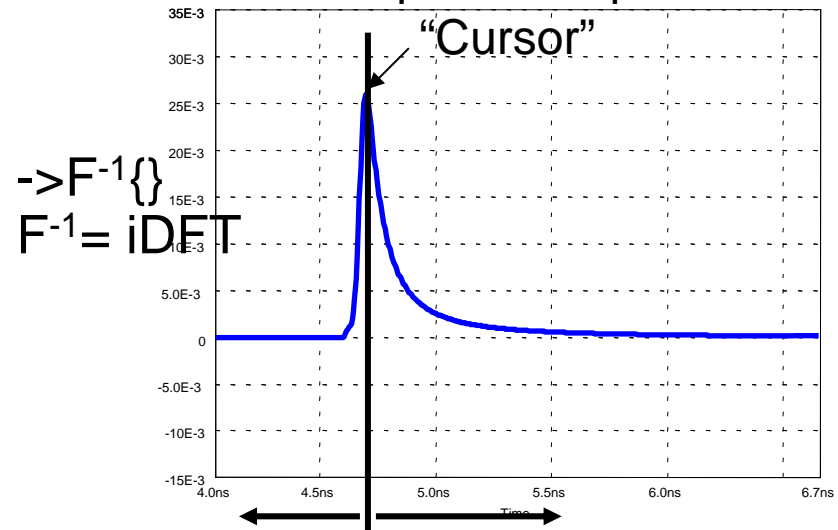

$$\begin{aligned} &\rightarrow F^{-1} \} \\ F^{-1} &= \text{iDFT} \end{aligned}$$


Pre-Cursor Time Dispersion Post-Cursor Time Dispersion

Sanity checks in time conversion :

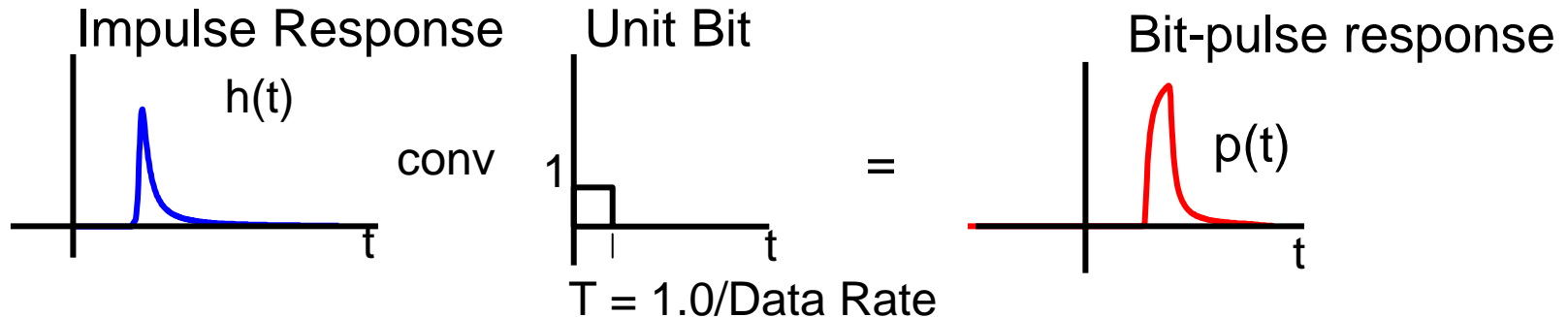
- 1) No significant energy in impulse for $t \ll T_{\text{cursor}}$
(indicates possible causality problem in data)
- 2) No significant energy in impulse for $t \gg T_{\text{cursor}}$
(indicates possible aliasing into negative time/phase undersampling)
- 3) Rise time normally \gg Fall time in a long T-line
- 4) Back-translate to frequency domain via FFT to compare accuracy of transform

Bit Pulse Response of Channel

Bit Pulse response = Channel Impulse Response convolved with unit bit




 Data response is generated by convolving signed data (impulses) with bit-pulse response. This convolution is computationally efficient and forms the basis for a fast discrete time simulator.




Data transmission viewed as a superposition of signed bit pulses

 The transmitted data stream under a linear time-invariant (LTI) channel assumption is a superposition of time-delayed data-signed bit pulse responses. The ISI at data detection time is deterministic and can be derived directly from the bit-pulse response.



Derivation of Inter Symbol Interference (ISI) from Bit-Pulse Response

 D(M) ... D(1) D(0) D(-1) D(-2) D(-3) D(-4) D(-N) Data bits




$$\text{POST-CURSOR ISI} = \sum_{j=1}^N h(j) D(-j)$$

← DESIRED SIGNAL = D(0) h(0)

$$\text{PRE-CURSOR ISI} = \sum_{j=1}^M h(-j) D(j)$$

“Vertical Eye” Deterministic ISI Statistics

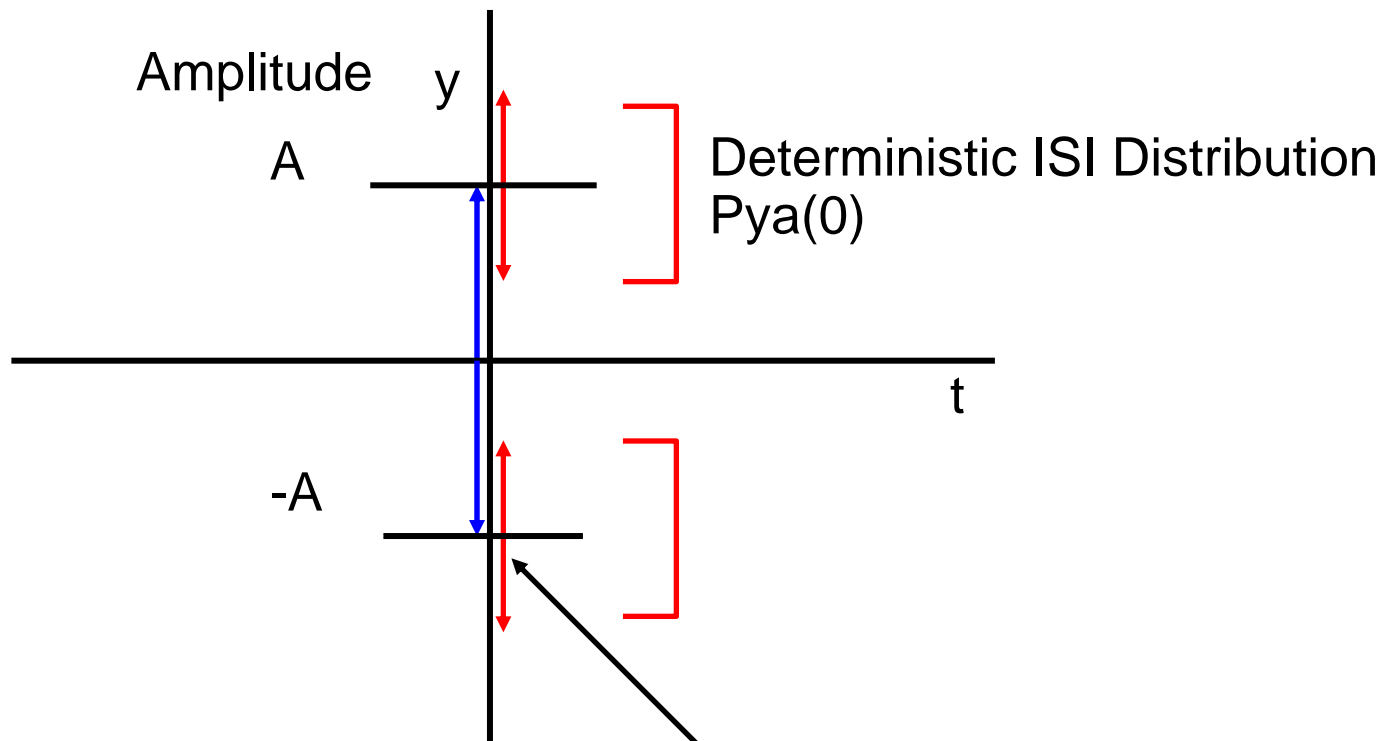
The amplitude distribution from ISI can be computed from the bit-pulse response by forming all possible combinations of ISI sums.




ISI Occurs at locations : $+-h(-M)+-h(-M+1)\dots+-h(-1) +-h(1)+- \dots h(N) +- A$
 $= 2^{**}(M + N)$ discrete ISI points centered about $A, -A$

Non-Deterministic Noise and Crosstalk Noise Addition

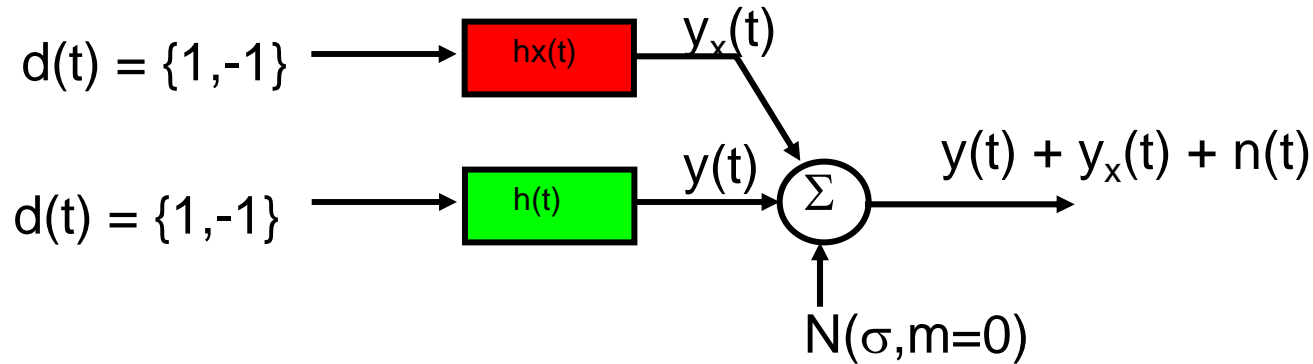
Non-Deterministic amplitude noise and crosstalk noise can be added to the deterministic ISI distribution by convolving the deterministic distributions together with a Gaussian noise distribution




Deterministic Data ISI Distribution

 

 Deterministic Crosstalk Noise Distribution



Non-Deterministic Noise Distribution

 


CONV

CONV

=

Sample Time Jitter Addition to Vertical Eye Statistics

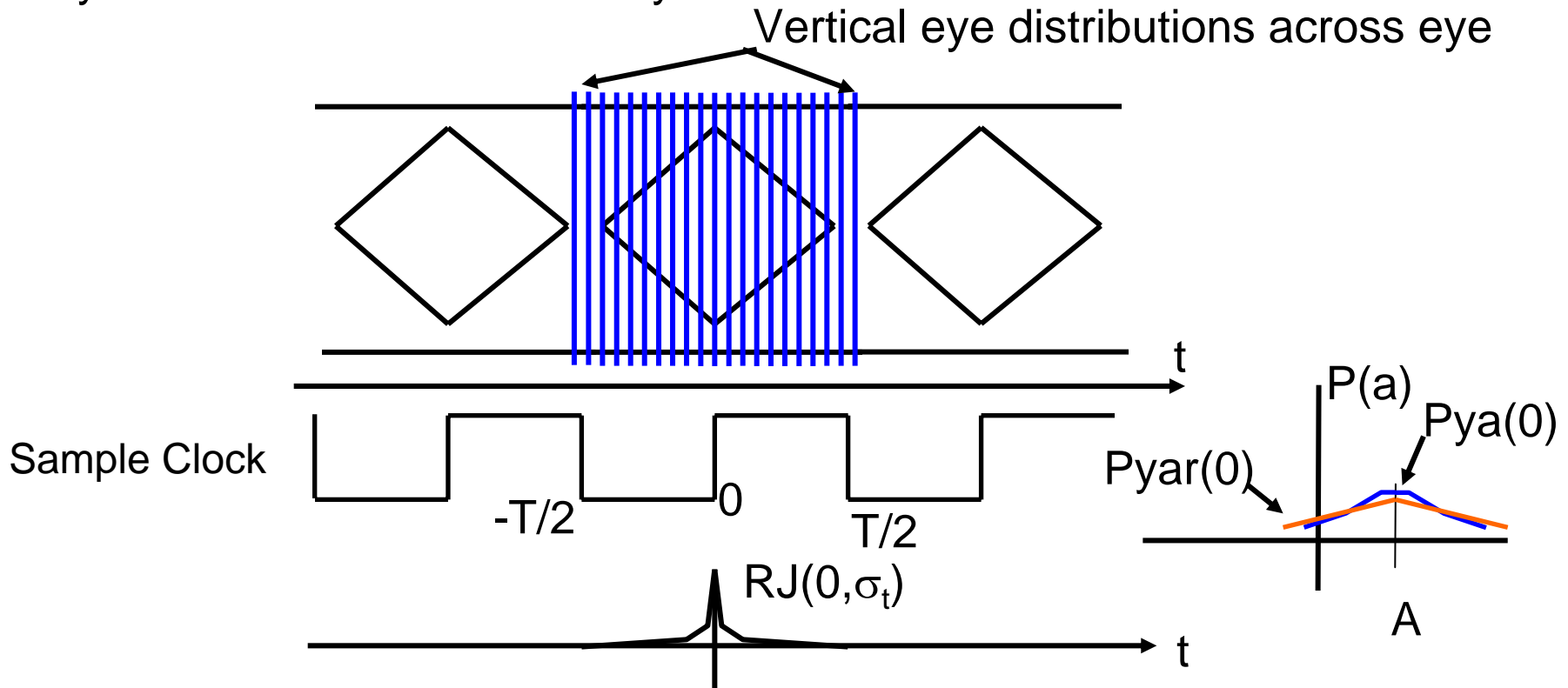
The effect of clock jitter is incorporated into the HEYE and VEYE analysis by computing time-jitter weighted averages of the vertical eye distributions across the eye



For center vertical eye distribution : $P_{yar}(0) = \sum_{t = -T/2 \text{ to } T/2} P_{ya}(t) RJ(t)$

HEYE and VEYE Computation

 The final vertical amplitude distribution at eye center ($t=0$) is $P_{yar}(0)$




$$BER(AO, t) = \int_{-\infty}^{AM+AO} P_{yar_t}(a) da$$

VEYE(t) = AO which results in $BER(AO, t) = \text{target BER}$
 VEYE = VEYE(0)


HMIN = t which results in $BER(0, t) = \text{target BER}$ for $t < 0$
 HMAX = t which results in $BER(0, t) = \text{target BER}$ for $t > 0$
 HEYE = $2 * \min(|\text{HMIN}|, \text{HMAX})$ (Minimum P-P Jitter Tolerance)
 HEYEPP = HMAX - HMIN (Maximum P-P Jitter Tolerance)

Eye Contour and Bathtub Curve

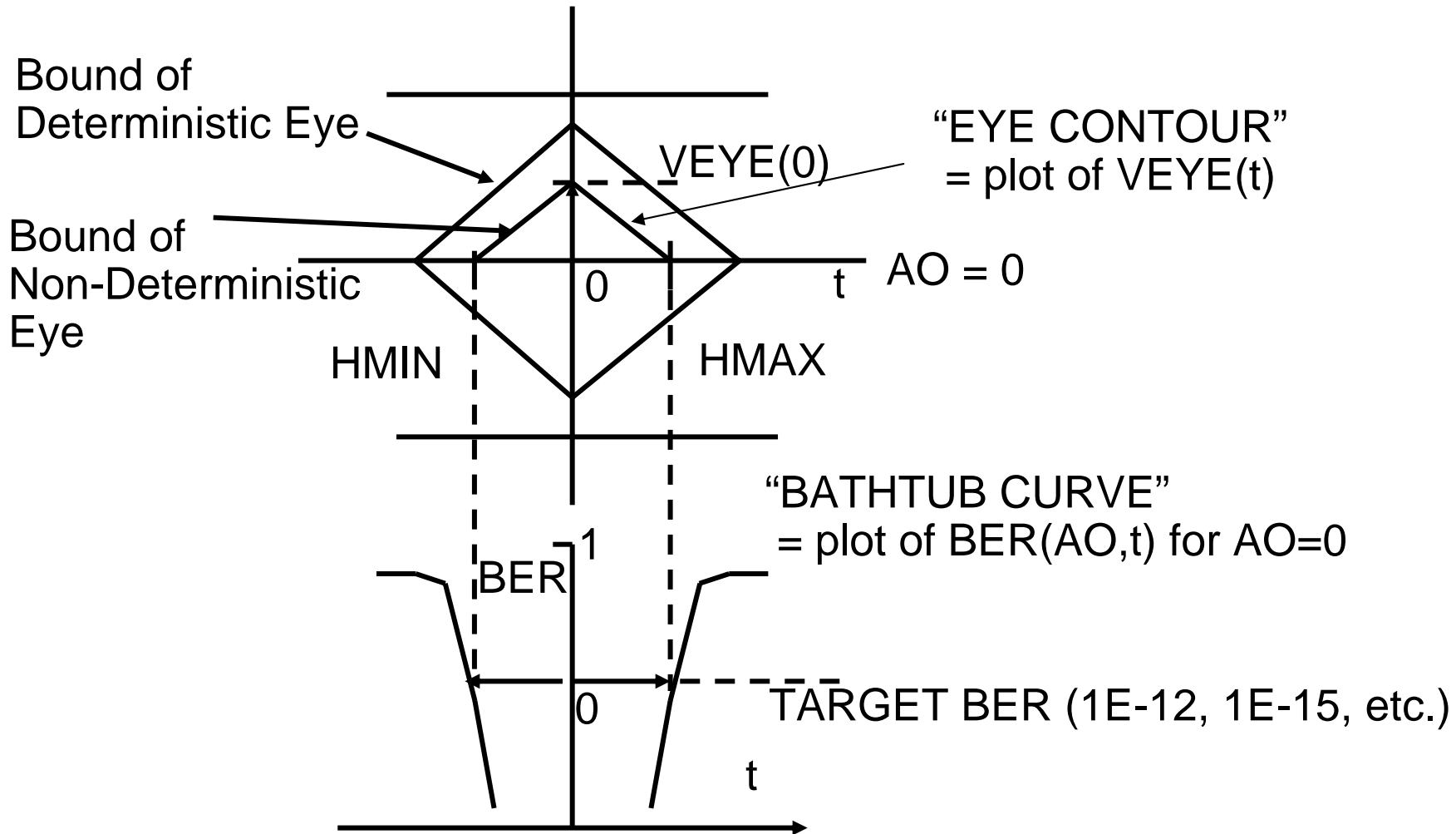
The eye contour directly shows vertical eye margin at a desired BER confidence
 The bathtub curve directly shows horizontal eye margin at a desired BER confidence



 Final Goal! Eye Diagram + Bathtub + Eye Contour + HEYE + VEYE



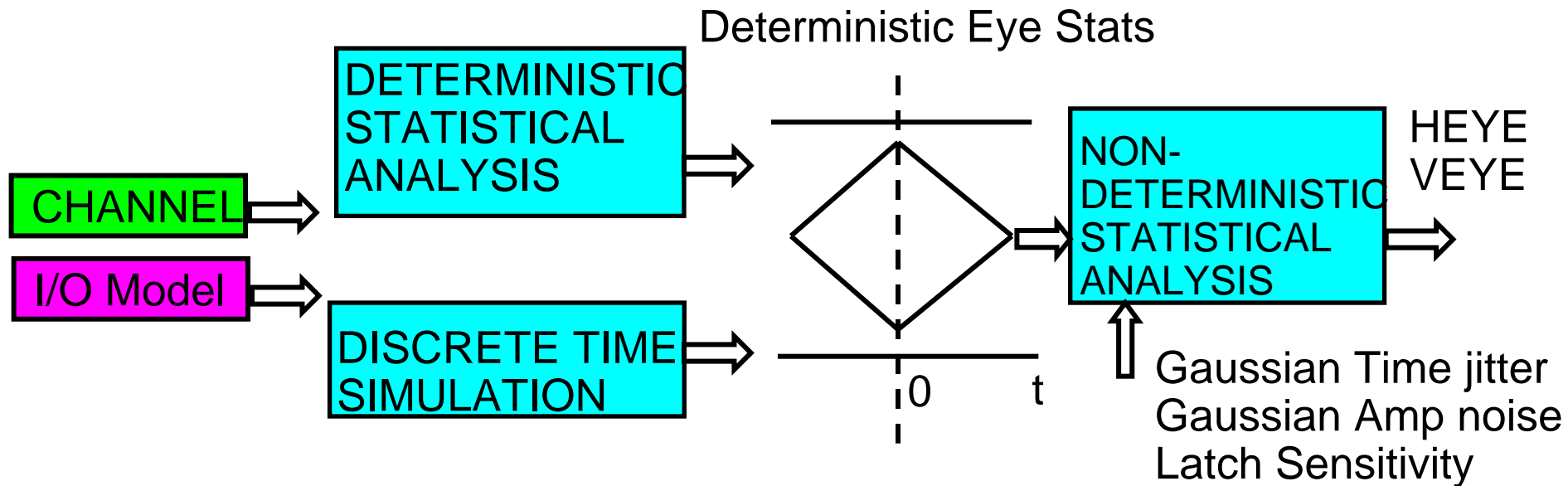Statistical Analysis vs. Discrete-Time Simulation Analysis



Advantage of Discrete-Time Simulation analysis :


- +Automatically incorporates “algorithmic jitter” of receiver clock-recovery function
- +Can add non-linear compression easily if desired
- +Can easily find effect of special data patterns (8/10 code, etc.)
no assumption of uniform random data needed

Disadvantage of Discrete-Time Simulation analysis :

- Slower : must simulate 10M bits or more before statistics start to converge
- Does not guarantee coverage of all data combinations, although “worst case” data combinations can be “forced” into the discrete-time simulation


Worst-Case Data Pattern Analysis

 “Worst Case” data patterns exist for both in-channel ISI and crosstalk excitation. They are found by lining up data bit polarities with the sign of the bit-pulse responses.



“Random” Data

Eye FFE1 25.0Gb/s [THRU,12] No Xtalk

 

“Worst-Case” ISI

Eye FFE1 25.0Gb/s [THRU,12] No Xtalk


 


Table of Contents


- Introduction
- S-Parameter Overview
- Link Models
- Performance Analysis
- **Line Equalization**
- Clock and Data Recovery
- Jitter Analysis
- 20-25Gb/s I/O Systems
- Digital/ADC I/O
- Appendix

Line Equalization Building Blocks



Feed-Forward Equalizer

 


Continuous Time Linear Equalizer

 


Non-Linear Decision-Feedback Equalizer

  

Closed eye at Rx input
HEYE = 0%

 


Open eye at Rx Sense amp
HEYE = 60% Open

 

General Equalization Error Criteria for NRZ Signaling

Equalization Goal

 
Minimize error at Edge crossover to Maximize HEYE



Minimize error at data sample time to maximize VEYE

HEYE and VEYE Error Criteria:

Edge Sample, Drive to 0

 


Data Sample, Drive to +-A

Minimum-Mean-Square-Error (MMSE) Equalization

MMSE Equalization finds FFE/DFE taps to minimize a mean-square error metric at the output of the equalizer

τ = delay through channel + ffe

Minimize Mean Square Error

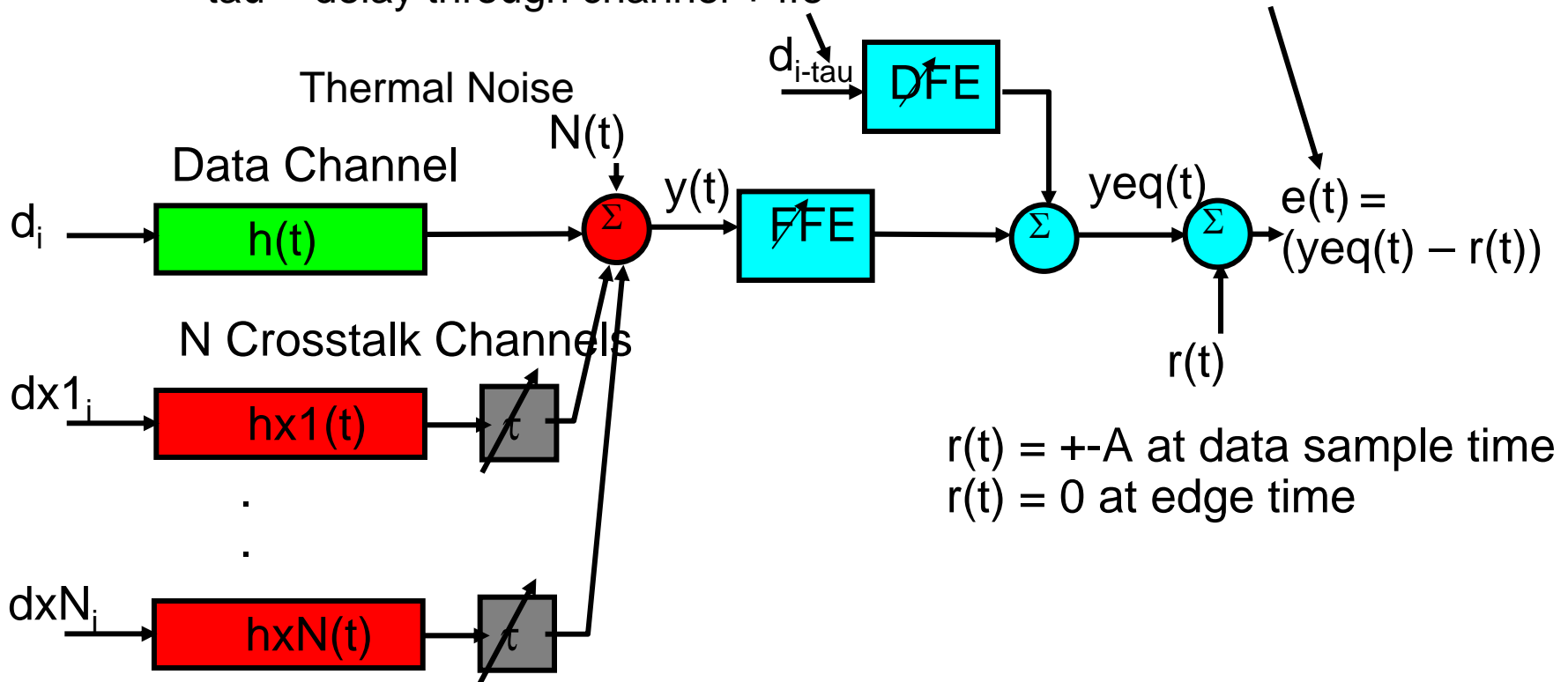


$r(t) = \pm A$ at data sample time
 $r(t) = 0$ at edge time

Optional Variable Delay From 0..T

Zero-Force ISI Equalization

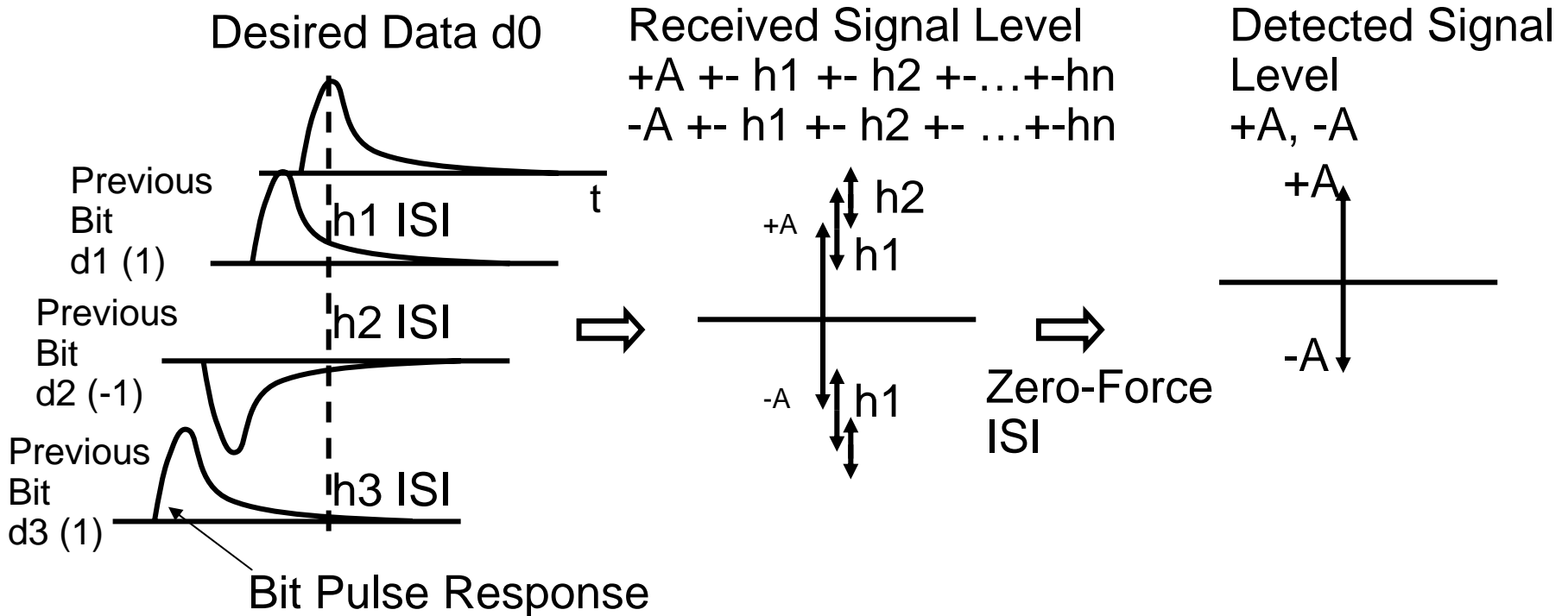“Zero-Force” ISI minimizes error at data and/or edge crossing¹ through ISI cancellation



¹T. Toifl, et.al “Low-Complexity Adaptive Equalization for High-Speed Chip-to-Chip Communication Paths by Zero-Forcing of Jitter Components”, IEEE TRANSACTIONS ON COMMUNICATIONS, VOL. 54, NO. 9, SEPTEMBER 2006

Zero-Force Equalization Adaptation

“Zero-Force” ISI Error Criteria drives correlation of averaged ISI sign error with data to 0:

$$E\{e * d_i\} = 0 \quad (\text{data history does not correlate with error})$$


Solution :

$$h_i = \int e * d_i = k \int \text{sgn}(e) * d_i$$

Data History

Small Integration Constant ($\ll h_i$)

Limited Level Sample Error

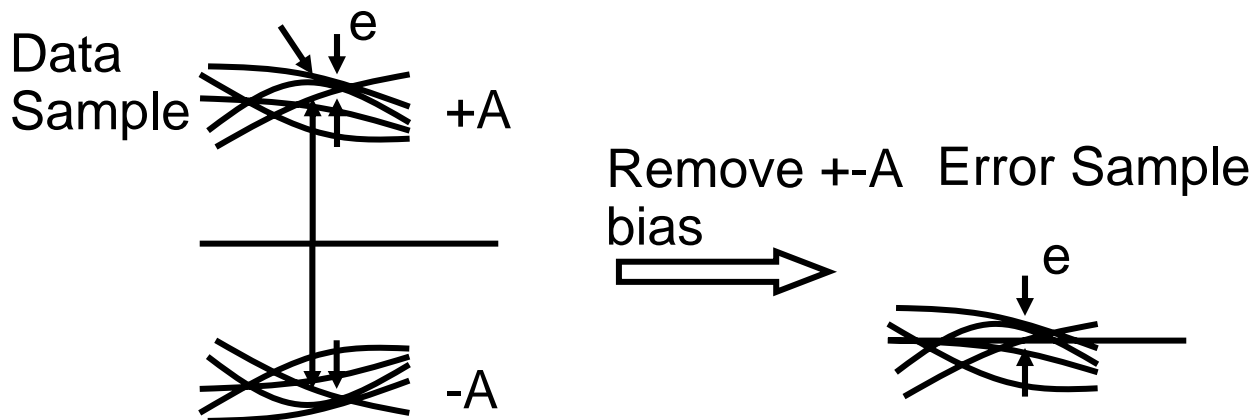


Data Correlation Problem for Zero-Force Adaptation

If two (or more) data bits which are driving a zero-force ISI adaptation are fully correlated, the ISI error is in turn fully correlated between these bits.

As a result :

 - 1) There is no unique solution for single-tap ISI convergence
- 2) Data correlated tap values can wander around almost anywhere
- 3) Taps can bias from ISI far removed from actual tap




Convergence to unique solution at tap “i” requires that
 $E\{d_i * d_j\} < 1$ for all $j \neq i$

-> Do not run adaptive equalization if 100% (or extremely high) data correlation found among data bits!

Equalization of Lossy Channels


Use of receiver CTE provides a bigger received signal, since less de-emphasis needed @ Tx, and also directly helps keep a Tx FFE from running out of post-cursor equalization range.

43dB loss at 12.5GHz

 

Large De-Emphasis Needed At Transmitter

15mV signal level with no Rx CTE

 


30mV signal level with Rx CTE

$\geq 6\text{dB}$ Peak Rx CTE



 
6dB less de-emphasis needed at Transmitter



Equalization of High Crosstalk Channels

CHANNEL :
 24" 2Connector LR BP
 4FEXT model
 BAUD/2
 LOSS : 25dB
 S/Xt : 12dB

 I/O :
 FFE 3 DFE 5
 ASYNC CDR
 1% UI RMS RJ
 2% Mean VEye AN
 25Gb/s



NO CROSSTALK

S/Xt = 12dB : CLOSE TO LIMIT OF OPERATION


 
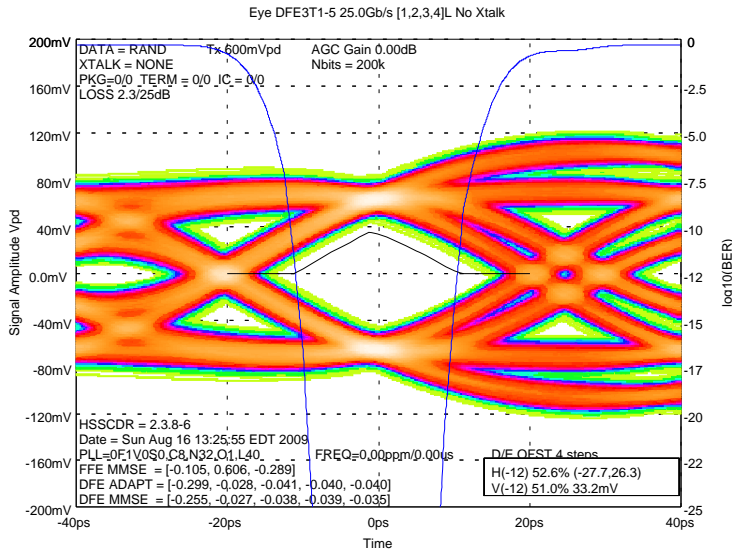


Table of Contents

- Introduction
- S-Parameter Overview
- Link Models
- Performance Analysis
- Line Equalization
- **Clock and Data Recovery**
- Jitter Analysis
- 20-25Gb/s I/O Systems
- Digital/ADC I/O
- Appendix

Clock and Data Recovery

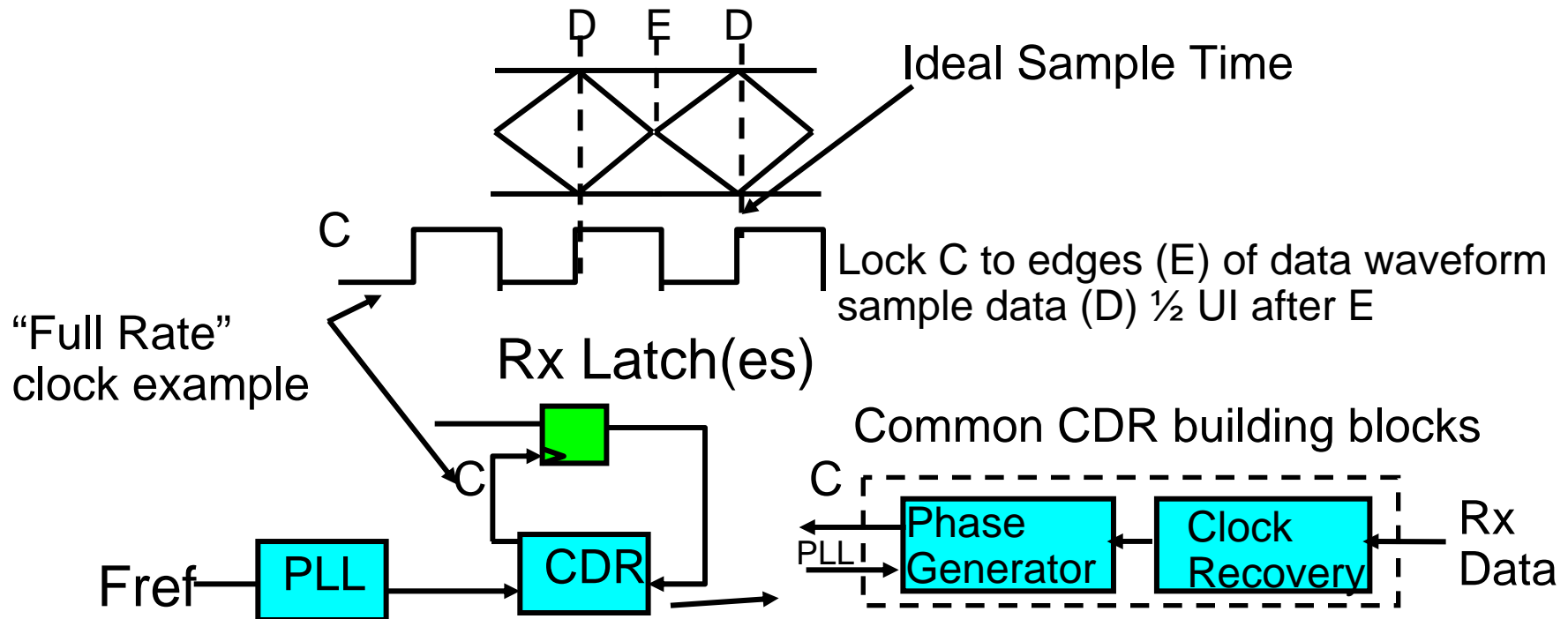
Clock and Data recovery in the receiver determines a sample time for the received signal which provides optimum data detection.




Synchronous and Asynchronous CDR Systems

Transmit and Receive clocks may be synchronous via forwarded clock, synchronous via PLL locked to a common reference, or fully asynchronous

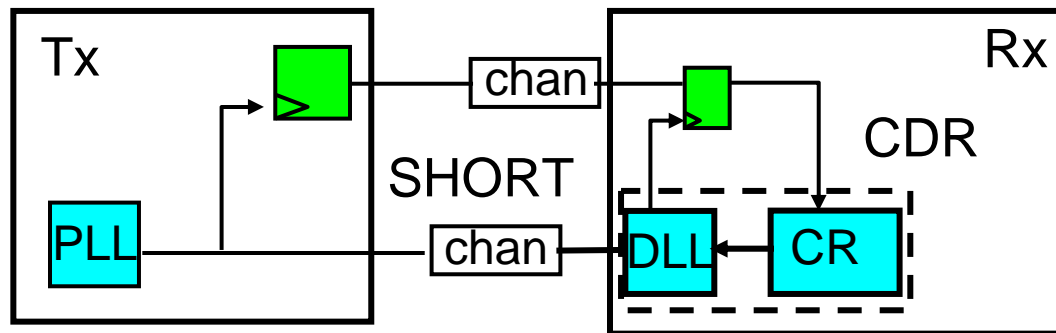Forwarded Clock (source synchronous) (Memory systems or C2C)




 Local PLL Clock (asynchronous or shared ref) (B2B/ Long Reach systems)



Early/Late Second-Order CDR for Asynchronous I/O


 
A second-order digital CDR is derived from a second-order analog PLL :



Translate block diagram from analog to digital domain :


$1/s$ = Analog integrator

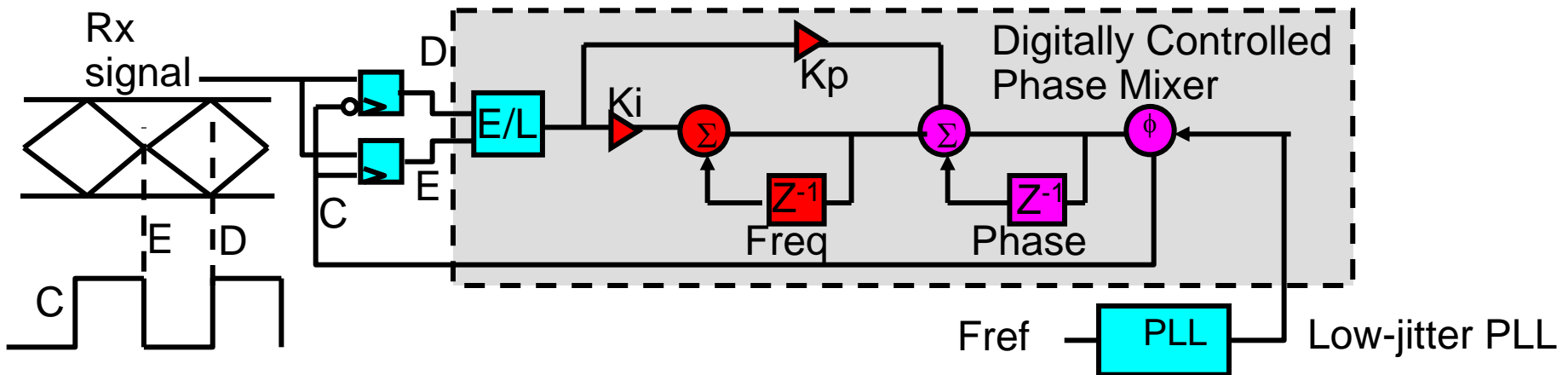 $y(n) = y(n-1) + x(n)$ = digital integrator



Source of Latency in Digital CDR Loops

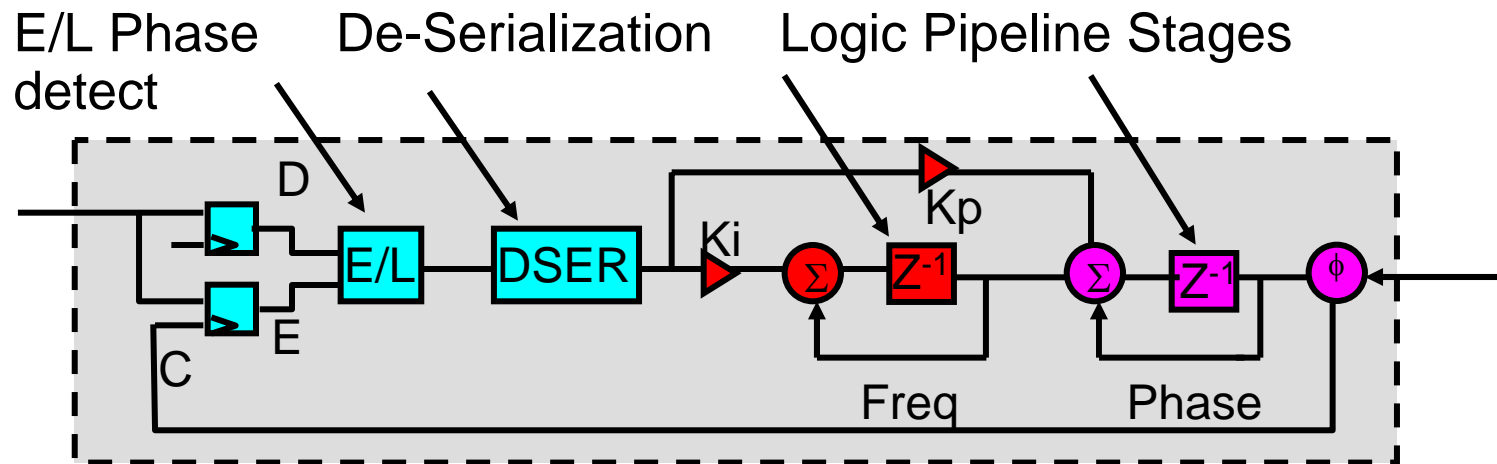
Practical digital CDR adds latency to CDR loop through E/L phase detection, deserialization and logic pipelining.




DSE must slow clock down enough that the digital CDR logic/adders can time.

Effect of Latency in PLL/CDR Loops

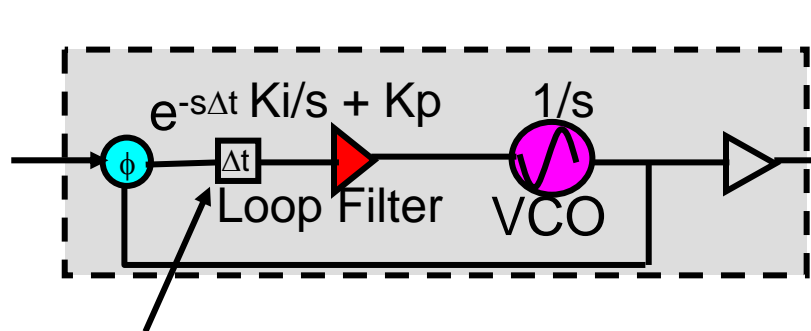Excess loop latency de-stabilizes the PLL or CDR loop and results in jitter transfer peaking.




Time delay in analog elements

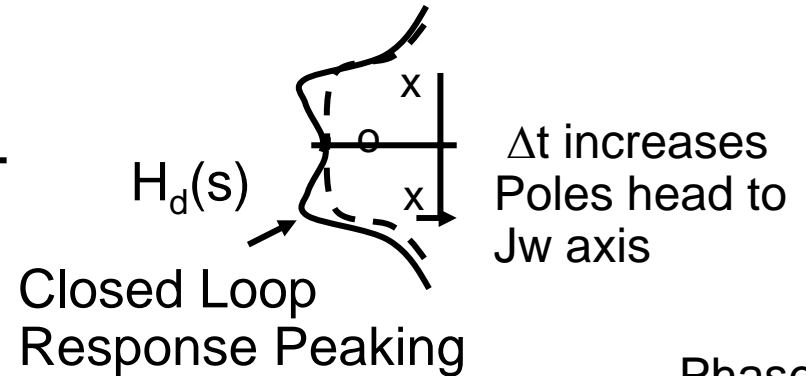

$$A(s) = e^{-s\Delta t} (Ki/s + Kp)/s = \text{Open-Loop Gain}$$

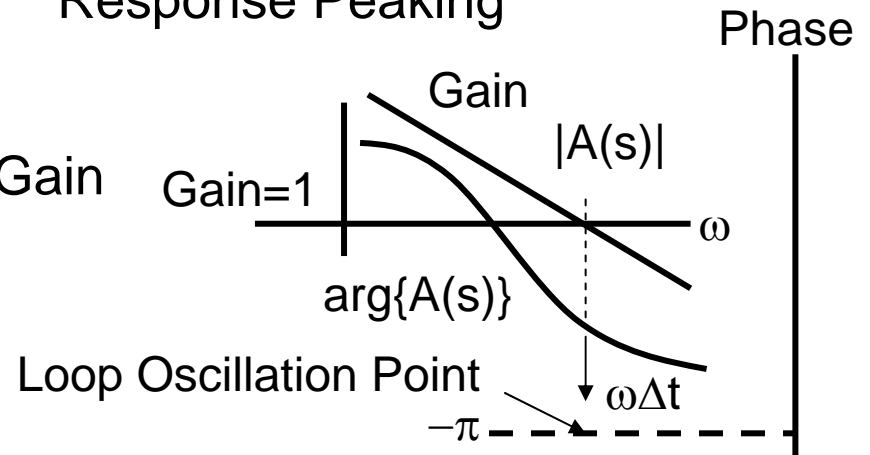No gain loss + added phase delay = direct hit on phase margin





$\omega_o \Delta t = \text{Loss in phase margin}$, $\omega_o = \text{frequency where the open loop and closed loop gain meet}$

Jitter Transfer Function and Jitter Multiplier Function of a CDR Loop

The CDR can eliminate or attenuate the effect of jitter within its tracking bandwidth. The amount of jitter attenuation is quantified by the jitter multiplier function.

Jitter Transfer Function = CDR output clock jitter / Input clock jitter = $H(s)$

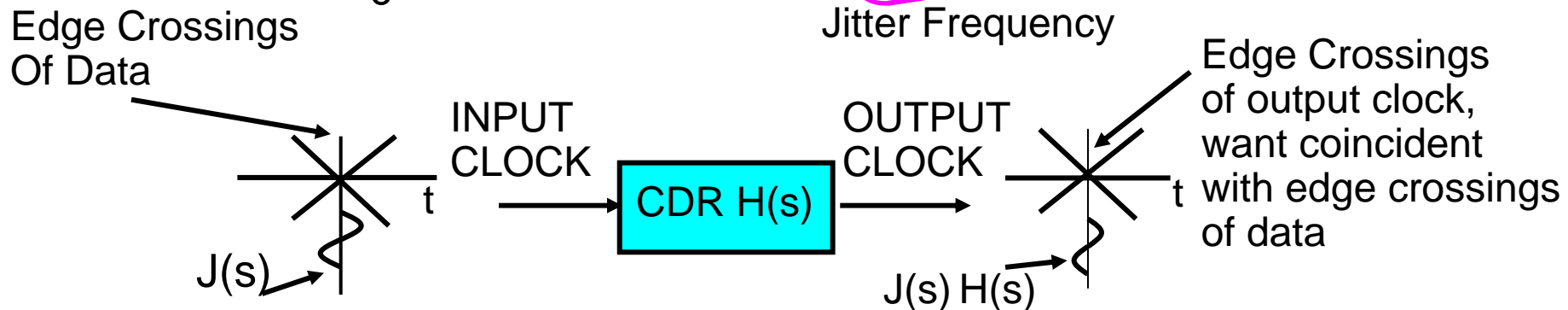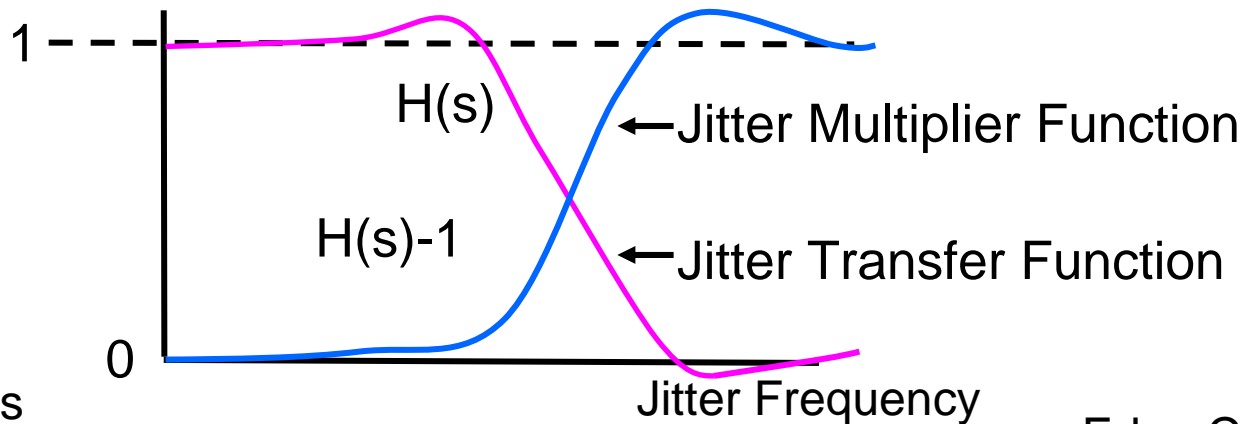
Jitter Multiplier Function \triangleq (CDR output clock jitter – Input clock jitter) / Input clock jitter
 $= H(s) - 1$





Jitter Magnitude Dependent Transfer Function of Early/Late CDR

The Early/Late CDR jitter transfer function depends on the magnitude of the input jitter due to non-linear phase detector.

LINEAR ϕ DETECT :
LOOP GAIN \sim ERR

 

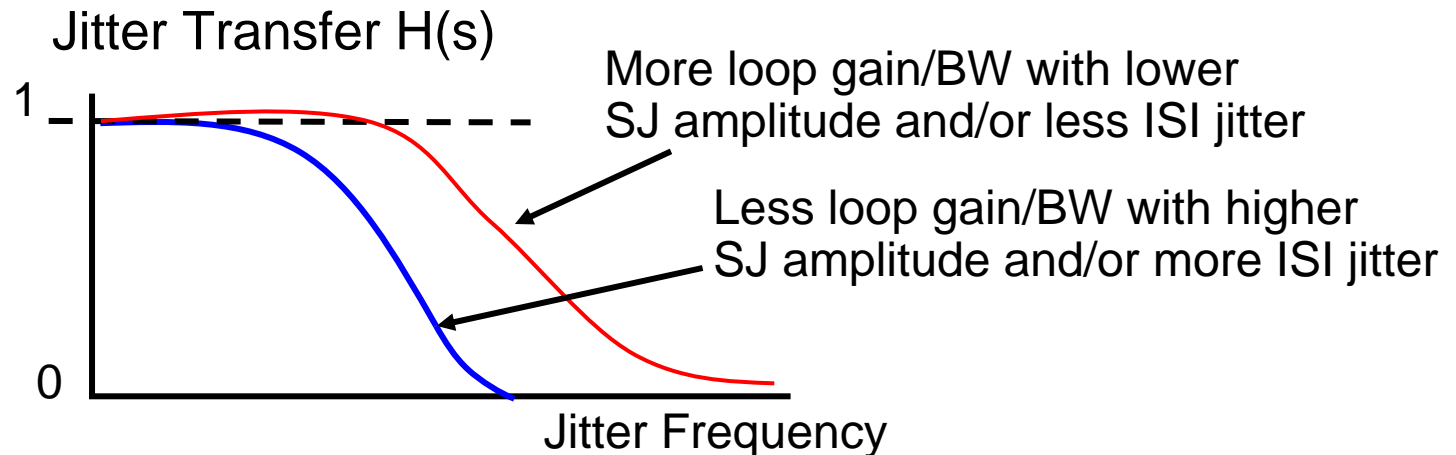 
LIMITING ϕ DETECT :
LOOP GAIN \sim SGN(ERR)



Jitter Tolerance Optimization for an Asynchronous CDR

CDR JTOL Optimization for Async CDR is accomplished by tuning the design latency and loop parameters (proportional and integral path gain) to meet the required JTOL mask.

 Beyond CDR tracking bandwidth, JTOL is dominated by system high-frequency SJ, DJ, RJ, and receiver sensitivity.



Non-Linearity in CDR Phase Generation Subsystem

Non-Linearity in a local CDR Clock Phase Generator can generate un-trackable excess jitter if the frequency offset between source and receiver is large.

Spread-Spectrum Clocking (SSC)


 
 
 
 


Table of Contents

- Introduction
- S-Parameter Overview
- Link Models
- Performance Analysis
- Line Equalization
- Clock and Data Recovery
- **Jitter Analysis**
- 20-25Gb/s I/O Systems
- Digital/ADC I/O
- Appendix

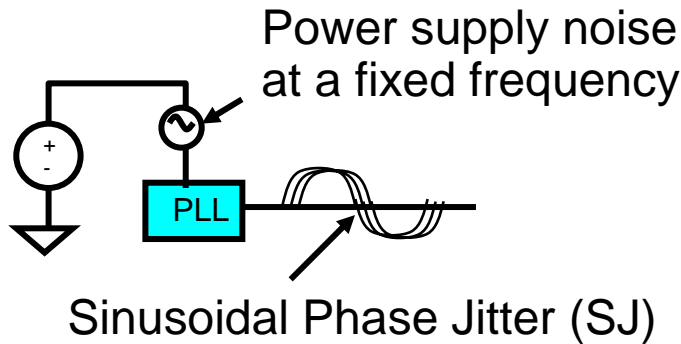Time Jitter Computation From Phase Noise + SJ Tones



$$\text{Time Jitter (RMS)} = \frac{1}{2\pi f_c} \sqrt{2 \int_{f_1}^{f_2} L(f) df + 2 \sum LSJ_i}$$

Non-Deterministic Phase Noise Power arising from noise


Bounded Peak-Peak Phase Noise Power arising from spurs (power sum valid if all are de-correlated)

If one (or more) SJ terms greatly dominates $L(f)$ over its integration range, SJ tones can be separated from clock RMS RJ and added separately to the system jitter analysis as bounded SJ.

See Appendix B for PLL phase noise model and jitter formula derivations

Time Jitter Contribution from Phase Noise Floor

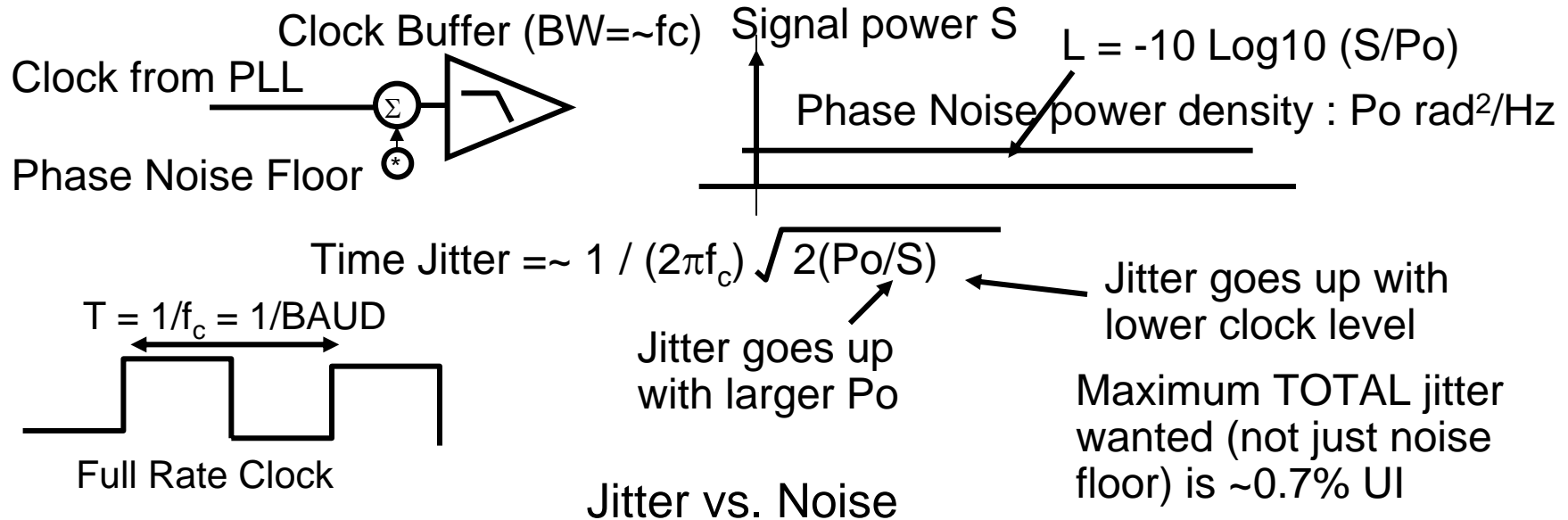Clock buffer noise floor can contribute significant integrated jitter since it is present over wide bandwidth. Lowering the clock signal level increases the dBc noise in direct proportion to loss in level.





Jitter vs. Noise

Phase noise (dBc/Hz)	f_c	Jitter (ps RMS)	BAUD (Gb/s)	Jitter (% UI RMS)
-140/-134/-128	6GHz	0.3/0.6/1.2	6	0.17/0.35/0.7
-140/-134/-128	12GHz	0.2/0.4/0.8	12	0.25/0.5/1
-140/-134/-128	24GHz	0.15/0.3/0.6	24	0.35/0.7/1.4

See appendix B.5 for derivation of phase noise power density from broadband additive thermal noise

Random Jitter Analysis for an Asynchronous PLL + CDR System

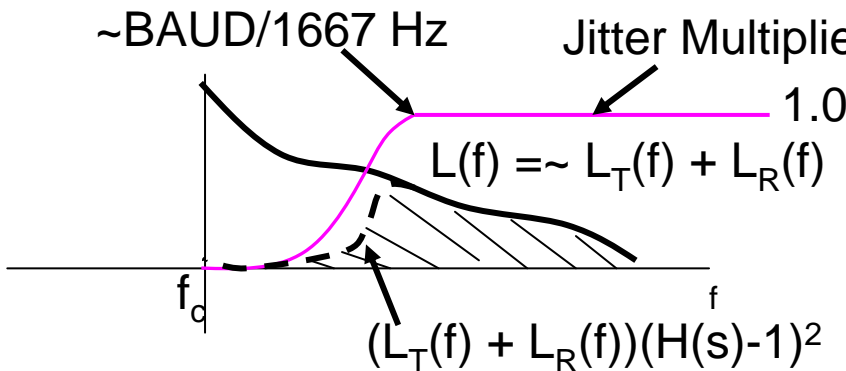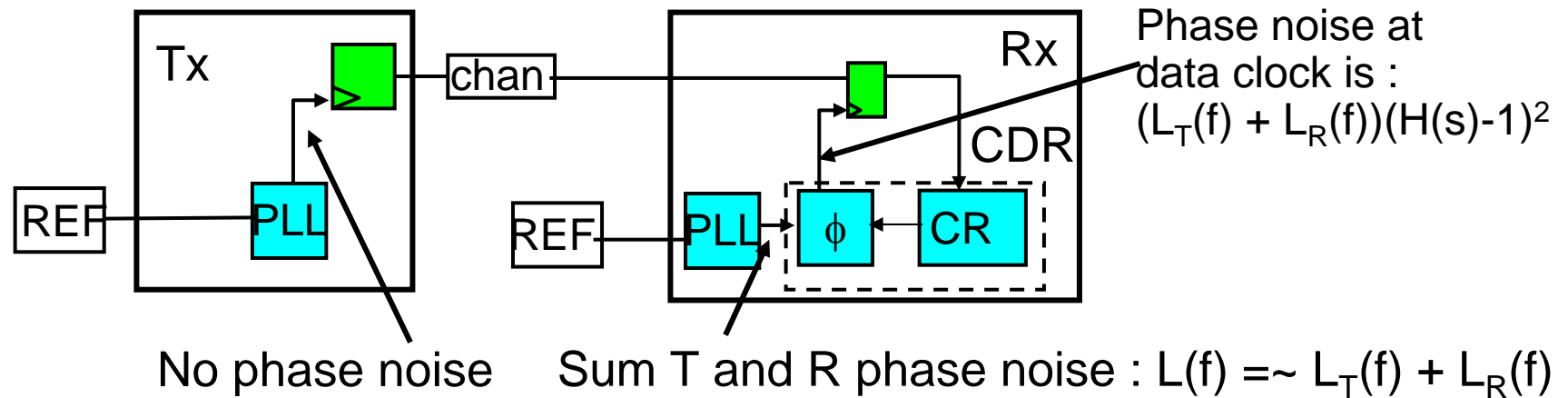Combined T-R Random Jitter Analysis Approximation : In dominant Noise part of phase noise power spectrum (<1GHz), channel is flat...
 -> power sum T and R phase noise @ Rx.



$$RJ = \frac{1}{2\pi f_c} \sqrt{2 \int_0^\infty [H(s) - 1]^2 L(f) df}$$


Table of Contents

- Introduction
- S-Parameter Overview
- Link Models
- Performance Analysis
- Line Equalization
- Clock and Data Recovery
- Jitter Analysis
- **20-25Gb/s I/O Systems**
- Digital/ADC I/O
- Appendix


Evolution to 25Gb/s Applications

Industry standards/work groups driving rate evolutions : OIF-CEI, 802.3ba, ITU-T


40G Systems

 

First Generation 100G Systems

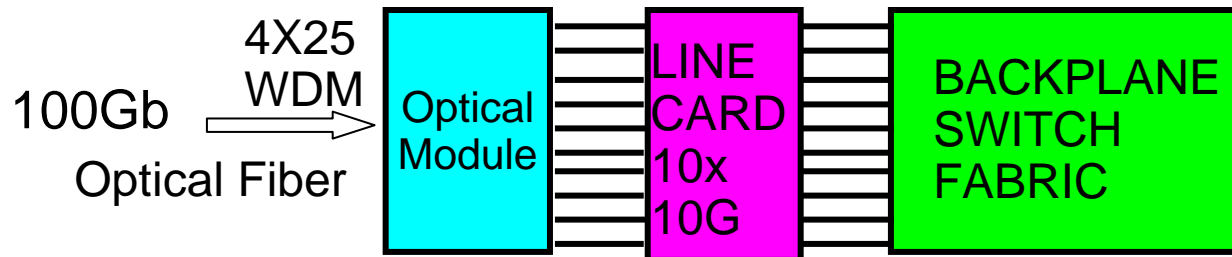


Second Generation 100G Systems¹

 

¹http://www.oiforum.com/public/documents/OIF_CEI-28G_WP_Final.pdf

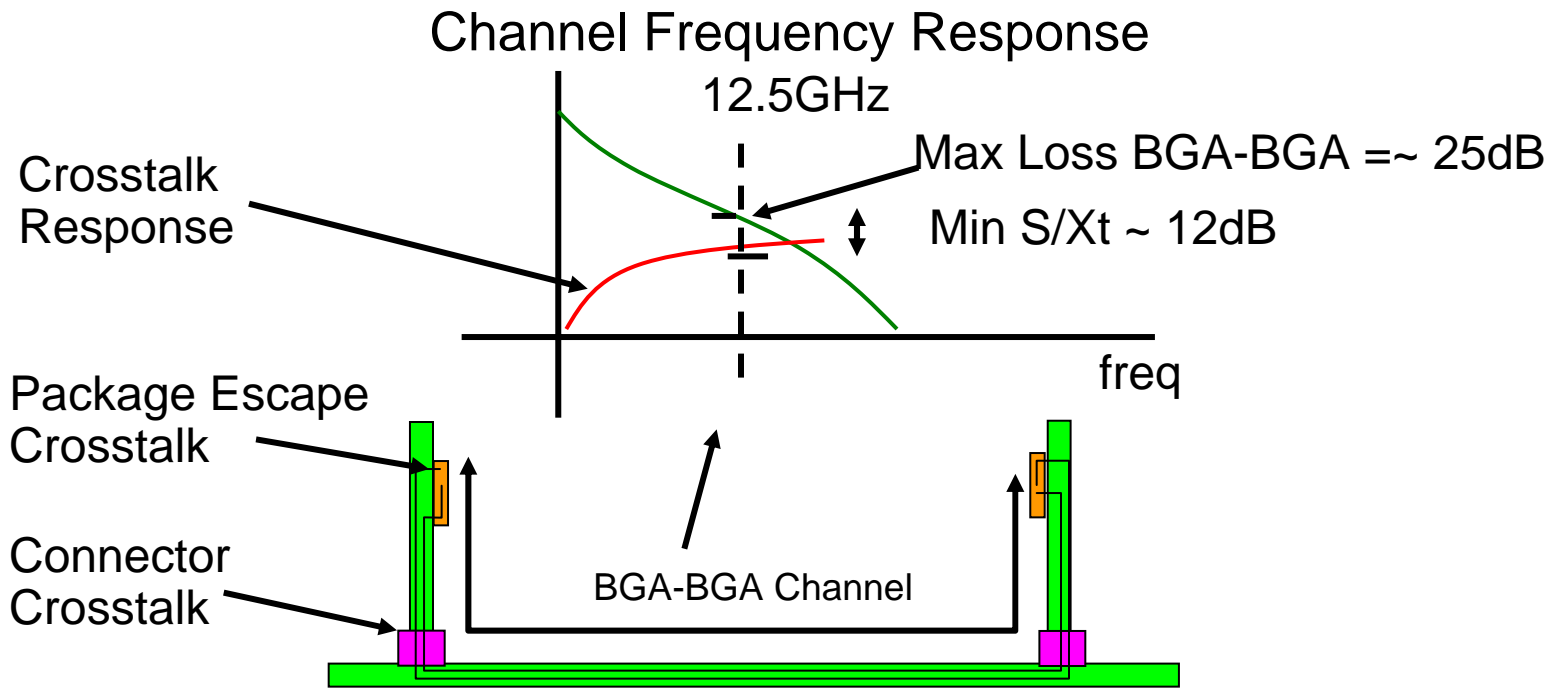
Channel Optimization Requirements for 20-25G Systems



Key Optimizations required for 25G physical channels :

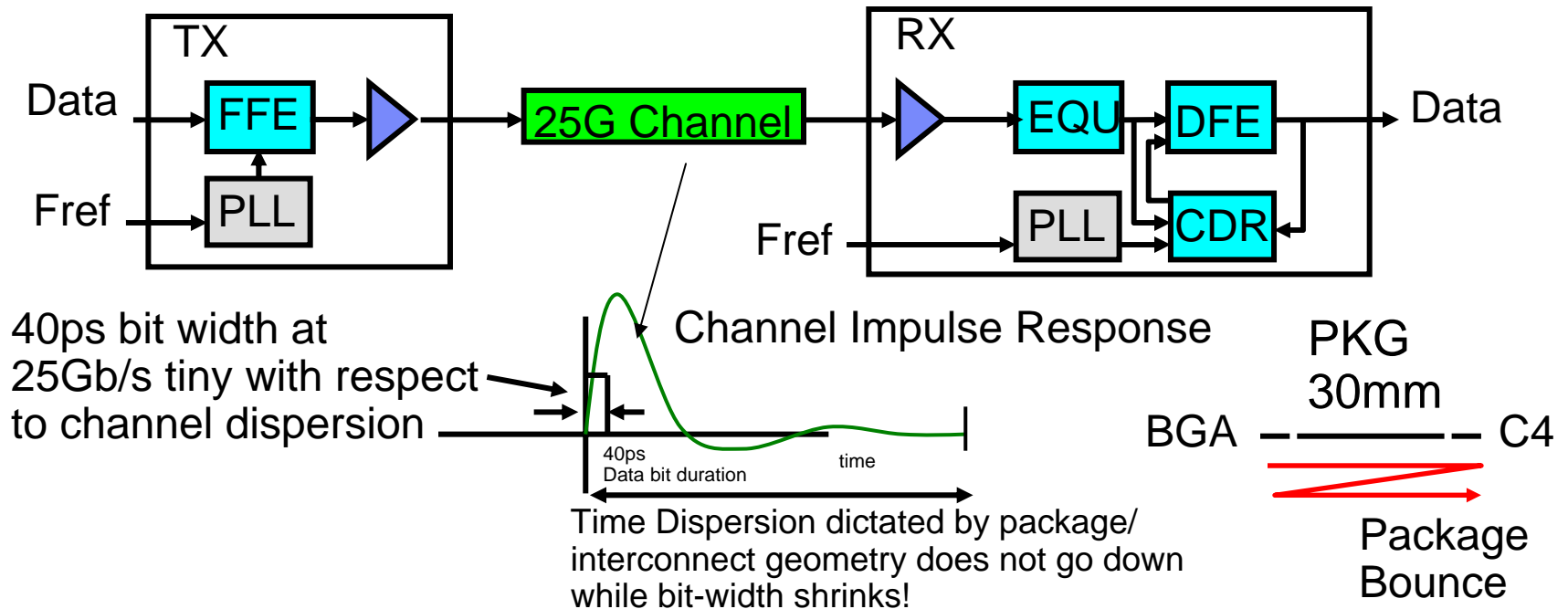- 1) Use low-loss dielectric material for Daughter Card and Backplane
- 2) Minimize crosstalk in connectors
- 3) Eliminate all stubs in channel... no extra resonance loss acceptable
- 4) Minimize number and length of via drops and associated impedance discontinuities
- 5) Minimize impedance discontinuity between package/board/connector/backplane
- 6) Maximize T-R isolation by physical design : minimize NEXT by design!
-optimize keep T and R buses isolated/separated in connectors

SERDES Optimization Requirements for 20-25G Systems



Key Optimizations required for 25G SERDES :

- 1) Increase equalization capability : Enhance line equalizers to handle channel dispersion
- 2) Lower jitter on launch and sample clocks to as close to 0 jitter as possible ($\ll 40\text{ps bit!}$)
-Optimize CDR design to meet JTOL with BAUD/1667 (15MHz) jitter tracking bandwidth
- 3) Provide needed bandwidth for transmitter and receiver to minimize end-to-end loss
-> Equalization system must handle combined loss of channel + package + I/O
- 4) Minimize noise in wide receiver bandwidth
- 5) Maximize T-R isolation on-die and in package escape region by physical design.
-optimize ground/signal ratio in off-die pin escape¹


¹D. Kam et. Al , "Is 25Gb/s on-board signaling viable?" IEEE Transactions on Advanced Packaging, vol 32, no. 2, May 2009

Table of Contents

- Introduction
- S-Parameter Overview
- Link Models
- Performance Analysis
- Line Equalization
- Clock and Data Recovery
- Jitter Analysis
- 20-25Gb/s I/O Systems
- **Digital/ADC I/O**
- Appendix

Backplane I/O ADC-Based System Designs


Analog T/Digital R Hybrid

 

Optimized for NRZ signaling line standards

Benefit limited to any extra performance the ADC+DSP decode can provide, and potential elimination of need for use of Tx FFE

 Digital T/Digital R : "Wildcard" for 25Gb/s and higher Backplane I/O




Unlimited line signaling variations possible

Supports complex Tx modulations such as TCM/OFDM, other dense symbol constellations

Use of complex modulation/coding requires industry standardization for widespread use!

Analog vs. ADC/Digital I/O Architecture Tradeoffs

 Classic Analog Signal Processing Equalization Chain




NRZ Partial Response Line Signaling

- +Low complexity data encode/decode
- +Very good power efficiency
- +No inherent quantization in binary slicer

- Non-optimal data detection with simple data slicer
- Most efficient with NRZ data transmission, bounds spectral efficiency

 Digital Signal Processing Equalization Chain




Trellis-Coded Modulation, OFDM,
Convolutionally Encoded data

- +Closer to optimum data detection possible (using maximum likelihood sequence estimation, etc.)
- +Spectral efficiency improvement potential

- Complexity and decode latency go (way) up with modulation/coding complexity.
- Higher power and area than an optimized analog core (uncompetitive in NRZ I/O applications at 20% more power)
- Quantization noise/sample error of ADC


Example ADC-based NRZ Line Equalization

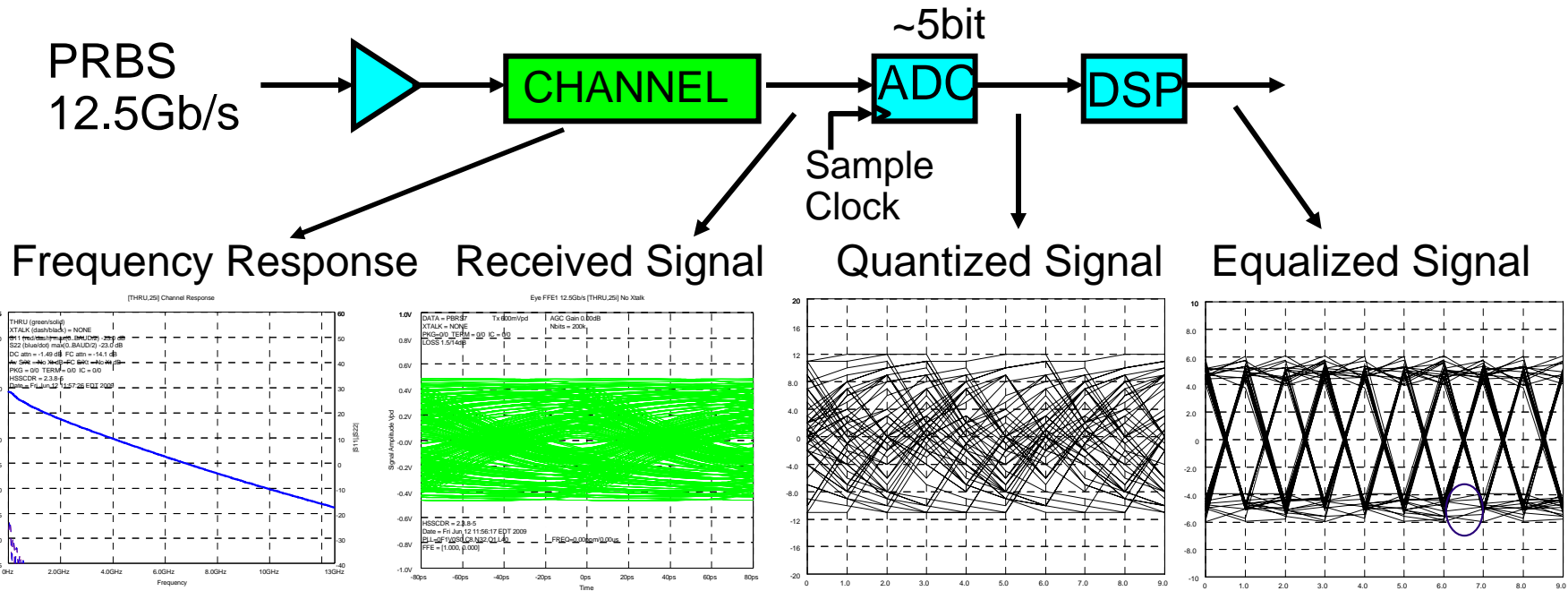

Nominal ADC Characteristics for Backplane I/O :
 ~4.5 bit Enob
 Effective sample rate = BAUD rate (1 sample per UI)
 2X to 4X interleaved converter

Nominal DSP for moderately dispersive backplane I/O :
 FFE3 + DFE5

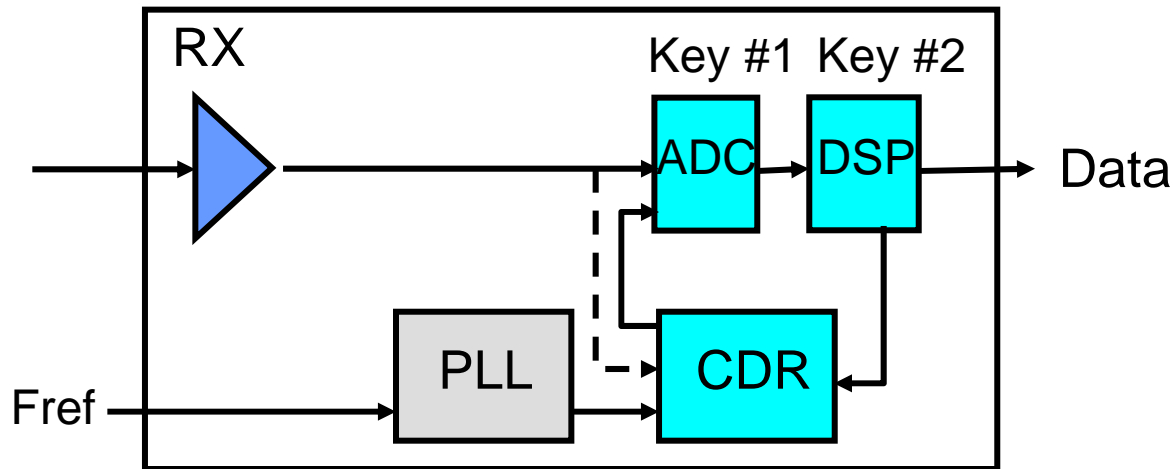Advances Needed to unlock potential of ADC-based High-Density SERDES



Key #1 ADC :

converter power must be lowered through a combination of efficient architecture and advanced technology (45nm, 32nm...)

sample error due to non-idealities and fundamental quantization noise must be minimized to avoid degrading NRZ detection sensitivity

Key #2 DSP:

Post-Processing power must be lowered through a combination of efficient processing algorithms and technology improvements, again leaning heavily on advanced CMOS technology for low digital power

Summary and Conclusions

Electrical interconnect data rates are heading to 20Gb/s and higher as advances in IC technology, storage technology and internet growth continue to drive demand for higher information bandwidth.

S-parameters are an extremely useful behavioral modeling tool which can capture both IC and passive line model characteristics. Many pitfalls await in generating and applying them accurately.

End-to-end system analysis techniques which incorporate accurate behavioral models of the channel and I/O core are needed to design and optimize electrical links.

Key components of the Electrical I/O are :

PLL : to generate low jitter clocks

CDR : to provide optimum jitter-suppressed data sampling

Equalization : to compensate ISI from line dispersion

Comprehensive System Jitter Analysis is necessary to optimize performance of high data rate serial interconnect systems.

Co-optimization of both electrical I/O core and channel is needed at higher and higher data rates... it is not possible to move to extremely high data rates with only one of these two pieces!

Digital / ADC I/O architecture can become interesting for backplane I/O as ADC power and digital logic power go down with advanced architectures and CMOS technology, opening up the possibility of more spectrally efficient line coding and optimal decoding algorithms to increase link operating margins.

Appendix/Backup

A. S-Parameter Topics :

1. Derivation of S-Parameters from Port Node Voltages
2. Mixed-Mode to Single-Ended S-Parameter conversion
3. 2-port S-parameter to T parameter conversion
4. Determination of S21 and S11 from a T-Line Z_0 and γ
5. Other useful line element S-Parameters
 - Open-circuit stub
 - Series Z (Series R, series L)
 - Shunt Z (Shunt G, shunt C)

B. PLL/Jitter Topics


1. 2nd Order PLL Response
2. Simplified PLL Phase Noise Model
3. Time Jitter Derivation for an SJ Tone
4. Time Jitter Computation From SSB Phase Noise
5. Time Jitter Derivation for additive noise

C. Digital Modulation Examples

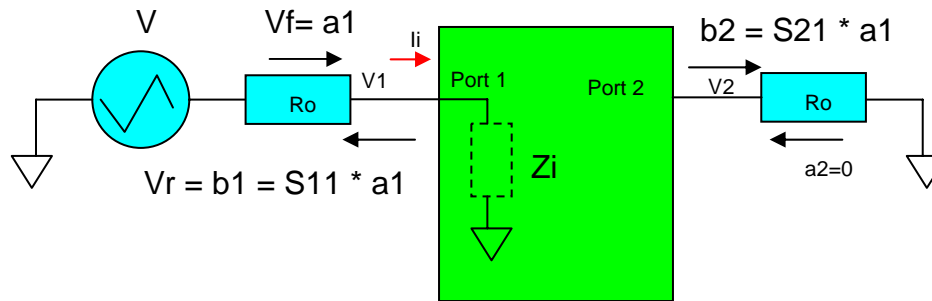1. Digital Line-Coding/Modulation : TCM
2. Subchannel Modulation : OFDM

A.1 Derivation of S-parameters from Port Node Voltages

S-Parameters can be derived in circuit simulators from node voltages as follows :



$$V_1 = V_f + V_r, V_r/V_f = S_{11} \rightarrow V_1 = V_f(1 + S_{11}) \rightarrow V_1/V_f = 1 + S_{11} \rightarrow \mathbf{S_{11} = V_1/V_f - 1}$$

$$Z_i = V_1 / i_i = R_o * V_1 / (V - V_1) \rightarrow R_o/Z_i = (V - V_1)/V_1 = V/V_1 - 1$$

$$S_{11} = \Gamma = (Z_i - R_o) / (Z_i + R_o) = (1 - R_o/Z_i) / (1 + R_o/Z_i) = (1 - (V/V_1 - 1)) / (1 + (V/V_1 - 1)) = (2 - V/V_1) / (V/V_1) = 2V_1/V - 1 = V_1/(V/2) - 1$$

-> $V_f = V/2 = a_1$ = incident voltage a_1 for a source excitation of V , by definition of s-parameters

-> $S_{11} = V_1 / (V/2) - 1 \rightarrow V_1 = (1 + S_{11}) * (V/2) \rightarrow$ **If V is set to 2, S_{11} = port 1 node voltage - 1**

$S_{21} = b_2 / a_1 = V_2 / (V/2) \rightarrow V_2 = S_{21} * (V/2) \rightarrow$ **If V is set to 2, S_{21} = port 2 node voltage**


Note also that :

$$S_{21} = V_2 / V_f \quad V_1 = V_f + V_r = V_f(1 + S_{11}) \rightarrow V_f = V_1 / (1 + S_{11}) \rightarrow \mathbf{S_{21} = (1 + S_{11}) * V_2 / V_1}$$

-> S_{21} is a voltage transfer from output to input only if input is perfectly matched

-> $\mathbf{S_{21} = (1 + S_{11})}$ if Node 1 and Node 2 are the same, so $V_2 = V_1$ (load impedance only)

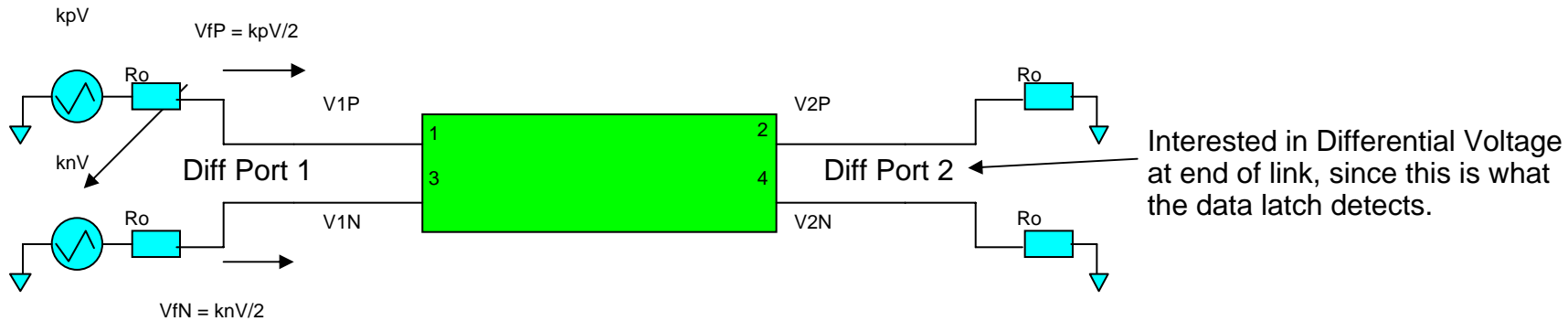A.2 Mixed-Mode to Single-Ended S-Parameter conversion



Differential Input Reflection Coefficient :

$$\begin{aligned} \text{SDD11} &= \text{Differential Input reflection} / \text{Differential excitation} = (b1 - b3) / (a1 - a3) \\ &= ((S11 * a1 + S13 * a3) - (S33 * a3 + S31 * a1)) / (a1 - a3) \end{aligned}$$

$$a1 = V/2 \quad a3 = -V/2$$

$$\text{SDD11} = 0.5 * (\text{S11} - \text{S13} + \text{S33} - \text{S31})$$

Differential Transmission Parameters :

$$\begin{aligned} \text{SDD21} &= \text{Differential Transmission} / \text{Differential excitation} = (b2 - b4) / (a1 - a3) \\ &= ((S21 a1 + S23 a3) - (S43 a3 + S41 a1)) / (a1 - a3) \end{aligned}$$

$$a1 = V/2 \quad a3 = -V/2$$

$$\text{SDD21} = 0.5 * (\text{S21} - \text{S23} + \text{S43} - \text{S41})$$

$$\begin{aligned} \text{SDC21} &= \text{Differential Transmission} / \text{Common excitation} = (b2 - b4) / (a1 + a3) \\ &= ((S21 a1 + S23 a3) - (S43 a3 + S41 a1)) / (a1 + a3) \end{aligned}$$

$$a1 = V/2 \quad a3 = V/2$$

$$\text{SDC21} = 0.5 * (\text{S21} + \text{S23} - \text{S43} - \text{S41})$$

For Differential excitation:

$$kp = 1, kn = -1, VfD = V/2 - (-V/2) = V$$

For Common excitation :

$$kp = 1, kn = 1, VfC = V/2 + V/2 = V$$

By definition these are normalized to the same incident voltage by defining the input common-mode voltage as $V_{iP} + V_{iN}$

Remainder of Mode Conversion and conversion from Diff to SE formulas presented on next page.

A.2 Mixed-Mode to Single-Ended S-Parameter conversion (cont.)



$$\text{Differential Voltage} \triangleq V^+ - V^-$$

$$\text{Common Voltage} \triangleq V^+ + V^-$$

$$\begin{aligned} \text{SDD11} &= 0.5 * (\text{S11} - \text{S13} + \text{S33} - \text{S31}) \\ \text{SDD12} &= 0.5 * (\text{S12} - \text{S32} + \text{S34} - \text{S14}) \\ \text{SDD21} &= 0.5 * (\text{S21} - \text{S23} + \text{S43} - \text{S41}) \\ \text{SDD22} &= 0.5 * (\text{S22} - \text{S24} + \text{S44} - \text{S42}) \end{aligned}$$

$$\begin{aligned} \text{SDC11} &= 0.5 * (\text{S11} + \text{S13} - \text{S33} - \text{S31}) \\ \text{SDC12} &= 0.5 * (\text{S12} + \text{S32} - \text{S34} - \text{S14}) \\ \text{SDC21} &= 0.5 * (\text{S21} + \text{S23} - \text{S43} - \text{S41}) \\ \text{SDC22} &= 0.5 * (\text{S22} + \text{S24} - \text{S44} - \text{S42}) \end{aligned}$$

$$\begin{aligned} \text{SCD11} &= 0.5 * (\text{S11} - \text{S13} - \text{S33} + \text{S31}) \\ \text{SCD12} &= 0.5 * (\text{S12} - \text{S32} - \text{S34} + \text{S14}) \\ \text{SCD21} &= 0.5 * (\text{S21} - \text{S23} - \text{S43} + \text{S41}) \\ \text{SCD22} &= 0.5 * (\text{S22} - \text{S24} - \text{S44} + \text{S42}) \end{aligned}$$

$$\begin{aligned} \text{SCC11} &= 0.5 * (\text{S11} + \text{S13} + \text{S33} + \text{S31}) \\ \text{SCC12} &= 0.5 * (\text{S12} + \text{S32} + \text{S34} + \text{S14}) \\ \text{SCC21} &= 0.5 * (\text{S21} + \text{S23} + \text{S43} + \text{S41}) \\ \text{SCC22} &= 0.5 * (\text{S22} + \text{S24} + \text{S44} + \text{S42}) \end{aligned}$$

$$\begin{aligned} \text{S11} &= 0.5 * (\text{SDD11} + \text{SDC11} + \text{SCD11} + \text{SCC11}) \\ \text{S12} &= 0.5 * (\text{SDD12} + \text{SDC12} + \text{SCD12} + \text{SCC12}) \\ \text{S21} &= 0.5 * (\text{SDD21} + \text{SDC21} + \text{SCD21} + \text{SCC21}) \\ \text{S22} &= 0.5 * (\text{SDD22} + \text{SDC22} + \text{SCD22} + \text{SCC22}) \end{aligned}$$

$$\begin{aligned} \text{S13} &= 0.5 * (-\text{SDD11} + \text{SDC11} - \text{SCD11} + \text{SCC11}) \\ \text{S32} &= 0.5 * (-\text{SDD12} + \text{SDC12} - \text{SCD12} + \text{SCC12}) \\ \text{S23} &= 0.5 * (-\text{SDD21} + \text{SDC21} - \text{SCD21} + \text{SCC21}) \\ \text{S24} &= 0.5 * (-\text{SDD22} + \text{SDC22} - \text{SCD22} + \text{SCC22}) \end{aligned}$$

$$\begin{aligned} \text{S33} &= 0.5 * (\text{SDD11} - \text{SDC11} - \text{SCD11} + \text{SCC11}) \\ \text{S34} &= 0.5 * (\text{SDD12} - \text{SDC12} - \text{SCD12} + \text{SCC12}) \\ \text{S43} &= 0.5 * (\text{SDD21} - \text{SDC21} - \text{SCD21} + \text{SCC21}) \\ \text{S44} &= 0.5 * (\text{SDD22} - \text{SDC22} - \text{SCD22} + \text{SCC22}) \end{aligned}$$

$$\begin{aligned} \text{S31} &= 0.5 * (-\text{SDD11} - \text{SDC11} + \text{SCD11} + \text{SCC11}) \\ \text{S14} &= 0.5 * (-\text{SDD12} - \text{SDC12} + \text{SCD12} + \text{SCC12}) \\ \text{S41} &= 0.5 * (-\text{SDD21} - \text{SDC21} + \text{SCD21} + \text{SCC21}) \\ \text{S42} &= 0.5 * (-\text{SDD22} - \text{SDC22} + \text{SCD22} + \text{SCC22}) \end{aligned}$$

A.3 Translating Between 2-Port T-Parameters and S-Parameters

$$\begin{array}{c} \text{INPUT} \\ \text{OUTPUT} \end{array} \begin{bmatrix} B1 \\ B2 \end{bmatrix} = \begin{bmatrix} S11 & S12 \\ S21 & S22 \end{bmatrix} \begin{bmatrix} A1 \\ A2 \end{bmatrix} \begin{array}{c} \text{INPUT} \\ \text{OUTPUT} \end{array}$$

$$\begin{array}{c} \text{INPUT} \\ \text{INPUT} \end{array} \begin{bmatrix} B1 \\ A1 \end{bmatrix} = \begin{bmatrix} T11 & T12 \\ T21 & T22 \end{bmatrix} \begin{bmatrix} A2 \\ B2 \end{bmatrix} \begin{array}{c} \text{OUTPUT} \\ \text{OUTPUT} \end{array}$$

$$\begin{aligned} B1 &= S11 A1 + S12 A2 \\ B2 &= S21 A1 + S22 A2 \rightarrow A1 = (B2 - S22 A2) / S21 \end{aligned}$$

$$\begin{aligned} B1 &= S11 (B2 - S22 A2) / S21 + S12 A2 \\ A1 &= (B2 - S22 A2) / S21 \end{aligned}$$

$$\begin{aligned} B1 &= (S12 - S11 S22 / S21) A2 + S11 / S21 B2 \\ A1 &= -S22 / S21 A2 + 1.0 / S21 B2 \end{aligned}$$

$$\begin{bmatrix} B1 \\ A1 \end{bmatrix} = \begin{bmatrix} S12 - S11 S22 / S21 & S11 / S21 \\ -S22 / S21 & 1.0 / S21 \end{bmatrix} \begin{bmatrix} A2 \\ B2 \end{bmatrix}$$

$$\begin{aligned} \cdot & T11 = S12 - (S11 * S22 / S21) \\ \cdot & T12 = S11 / S21 \\ \cdot \cdot & T21 = -S22 / S21 \\ & T22 = 1.0 / S21 \end{aligned}$$

$$\begin{aligned} B1 &= T11 A2 + T12 B2 \\ A1 &= T21 A2 + T22 B2 \rightarrow B2 = (A1 - T21 A2) / T22 \end{aligned}$$

$$\begin{aligned} B1 &= T11 A2 + T12 / T22 (A1 - T21 A2) \\ B2 &= (A1 - T21 A2) / T22 \end{aligned}$$


$$\begin{aligned} B1 &= T12 / T22 A1 + (T11 - T12 T21 / T22) A2 \\ B2 &= 1.0 / T22 A1 - T21 / T22 A2 \end{aligned}$$

$$\begin{bmatrix} B1 \\ B2 \end{bmatrix} = \begin{bmatrix} T12 / T22 & T11 - T12 T21 / T22 \\ 1.0 / T22 & -T21 / T22 \end{bmatrix} \begin{bmatrix} A1 \\ A2 \end{bmatrix}$$

$$\begin{aligned} \cdot & S11 = T12 / T22 \\ \cdot & S12 = T11 - (T12 * T21 / T22) \\ \cdot \cdot & S21 = 1.0 / T22 \\ & S22 = -T21 / T22 \end{aligned}$$

This translation can be generalized to N-port T and S parameters, for any N even (i.e. # port outputs = # port inputs)

 Cascading S-Parameter Elements using T-Parameters



$$\begin{bmatrix} B1 \\ A1 \end{bmatrix} = \begin{bmatrix} T11 & T12 \\ T21 & T22 \end{bmatrix} \begin{bmatrix} A2 \\ B2 \end{bmatrix}$$

$$\begin{bmatrix} B3 \\ A3 \end{bmatrix} = \begin{bmatrix} T33 & T34 \\ T43 & T44 \end{bmatrix} \begin{bmatrix} A4 \\ B4 \end{bmatrix}$$

$$\begin{bmatrix} B1 \\ A1 \end{bmatrix} = \begin{bmatrix} T11 & T12 \\ T21 & T22 \end{bmatrix} \begin{bmatrix} T33 & T34 \\ T43 & T44 \end{bmatrix} \begin{bmatrix} A4 \\ B4 \end{bmatrix}$$

$$\begin{bmatrix} B1 \\ A1 \end{bmatrix} = \begin{bmatrix} TC11 & TC12 \\ TC21 & TC22 \end{bmatrix} \begin{bmatrix} A4 \\ B4 \end{bmatrix}$$


T-Parameters of Cascaded Link

$$\begin{bmatrix} B1 \\ B4 \end{bmatrix} = \begin{bmatrix} SC11 & SC12 \\ SC21 & SC22 \end{bmatrix} \begin{bmatrix} A1 \\ A4 \end{bmatrix}$$

S-Parameters of Cascaded Link

This procedure is generalized to N-port dimension for wide bus models.

 A.4 Determination of S21 and S11 from a T-Line Zo and γ



$$V(z) = Vf(0) e^{-\gamma z} + Vr(0) e^{\gamma z}$$

$$\Gamma_L = (Z_L - Z_0) / (Z_L + Z_0) = Vr(0) / Vf(0) \quad (\text{note } Vr(0) = Vf(0) \text{ for } Z_L = \text{infinity})$$

$$V(z) = Vf(0) (e^{-\gamma z} + \Gamma_L e^{\gamma z})$$

$$Z_i = Z_0 * (Z_L + Z_0 \tanh(\gamma l)) / (Z_0 + Z_L \tanh(\gamma l))$$

$$\Gamma_S = (Z_i - Z_S) / (Z_i + Z_S) = Vr(-l) / Vf(-l) \quad (\text{note } Vr(-l) = Vf(-l) \text{ for } Z_i = \text{infinity})$$

$$S_{11} = b_1/a_1 = Vr(-l) / Vf(-l) = \Gamma_S$$

S11 = $\Gamma_S |_{Z_S=Z_L=R_0}$ where R_0 = S-parameter reference impedance (normally 50 ohm)

$$S_{21} = b_2 / a_1 = V(0) / Vf(-l)$$


$$V(0) = Vf(0)(1 + \Gamma_L)$$

$$V(-l) = Vf(0) (e^{-\gamma l} + \Gamma_L e^{\gamma l}) = Vf(-l) + Vr(-l) = Vf(-l) (1 + \Gamma_S), \rightarrow Vf(-l) = Vf(0) (e^{-\gamma l} + \Gamma_L e^{\gamma l}) / (1 + \Gamma_S)$$

$$\mathbf{S21} = (1 + \Gamma_L) (1 + \Gamma_S) / (e^{\gamma l} + \Gamma_L e^{-\gamma l}) |_{Z_S=Z_L=R_0}$$

A.5 Other useful line element S-Parameters

Open Stub

 


$$\begin{aligned}
 S_{11} &= (Z_i || R_o) - R_o / ((Z_i || R_o) + R_o) \\
 &= (Z_i R_o - R_o(Z_i R_o)) / \\
 &\quad (Z_i R_o + R_o(Z_i + R_o)) \\
 &= -R_o / (R_o + 2Z_i) \\
 &= -1 / (1 + 2Z_i/R_o)
 \end{aligned}$$

$$\begin{aligned}
 Z_i &= Z_o * (Z_L + Z_o \tanh(\gamma l)) / \\
 &\quad (Z_o + Z_L \tanh(\gamma l)) \quad | \quad Z_L = \text{inf} \\
 &= Z_o / \tanh(\gamma l)
 \end{aligned}$$

$$\begin{aligned}
 \rightarrow S_{11} &= -1 / (1 + 2Z_o/(R_o * \tanh(\gamma l))) \\
 S_{21} &= (1 + S_{11})
 \end{aligned}$$

Shunt Z

 

$$\begin{aligned}
 S_{11} &= (Z || R_o) - R_o / ((Z || R_o) + R_o) \\
 &= (Z R_o - R_o(Z + R_o)) / \\
 &\quad (Z R_o + R_o(Z + R_o)) \\
 &= -R_o / (R_o + 2Z) \\
 &= -1 / (1 + 2Z/R_o)
 \end{aligned}$$


If $Z = 1/sC$ (shunt cap)

$$\begin{aligned}
 S_{11} &= -1 / (1 + 2/(sCR_o)) \\
 S_{21} &= (1 + S_{11})
 \end{aligned}$$

If $Z = 1/G$ (shunt conductance)

$$\begin{aligned}
 S_{11} &= -1 / (1 + 2/(G * R_o)) \\
 S_{21} &= (1 + S_{11})
 \end{aligned}$$

Series Z

 

$$\begin{aligned}
 S_{11} &= ((Z + R_o) - R_o) / ((Z + R_o) + R_o) \\
 &= Z / (Z + 2R_o) \\
 &= 1 / (1 + 2R_o/Z)
 \end{aligned}$$

$$\begin{aligned}
 S_{21} &= 2R_o / (2R_o + Z) \\
 &= 1 / (1 + Z/(2R_o))
 \end{aligned}$$


If $Z = sL$ (series L)

$$\begin{aligned}
 S_{11} &= 1 / (1 + 2R_o/(sL)) \\
 S_{21} &= 1 / (1 + sL / (2R_o))
 \end{aligned}$$

If $Z = R$ (series R)

$$\begin{aligned}
 S_{11} &= 1 / (1 + 2R_o/R) \\
 S_{21} &= 1 / (1 + R/(2R_o))
 \end{aligned}$$

B.1 2nd Order PLL Response

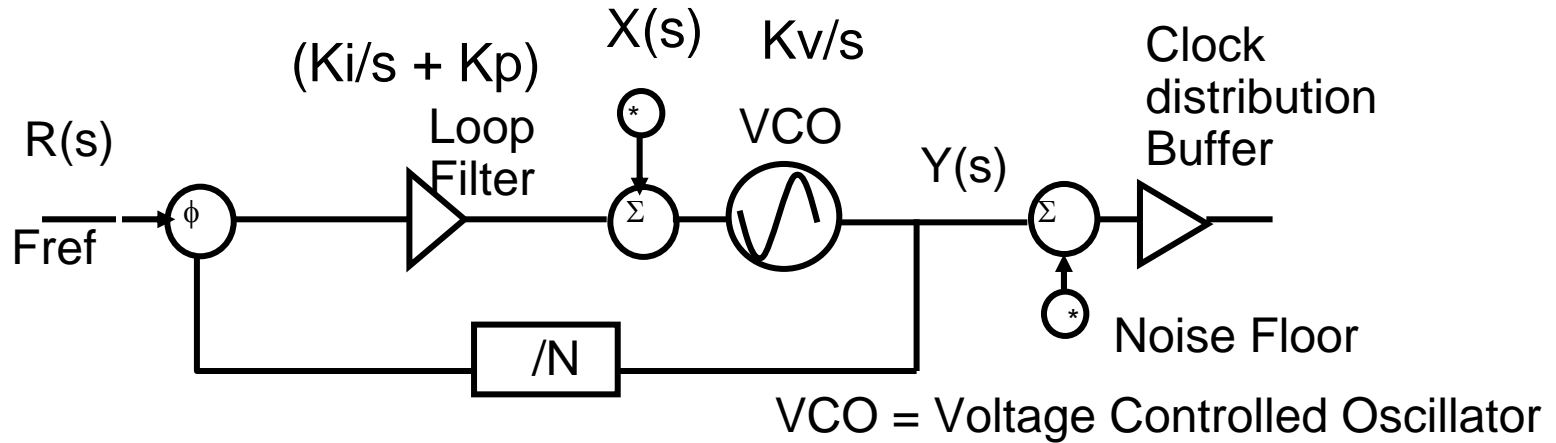

$$Y(s) = \underbrace{R(s) A(s) / (1 + A(s)\beta(s))}_{\text{Response from input}} + \underbrace{X(s) (Kv/s) / (1 + A(s)\beta(s))}_{\text{Response from VCO noise}}$$

$$A(s) = (Ki/s + Kp)(Kv/s)$$

$$\beta(s) = 1.0/N$$

$$\rightarrow H(s) \triangleq Y(s) / R(s) \mid X(s)=0 = \text{Transfer Function}$$


$$= Kv(Kp s + Ki) / (s^2 + KvKp/N s + KvKi/N)$$

$$V(s) \triangleq Y(s) / X(s) \mid R(s) = 0$$

$$= Kv s / (s^2 + KvKp/N s + KvKi/N)$$

$$= Kv / s \quad (s \leftarrow \text{large})$$

$$= 0 \quad (s \leftarrow 0)$$

 


As K_p gets smaller, poles migrate To $j\omega$ axis and de-stabilize loop


B.2 Simplified PLL Phase Noise Model

For $R(s) = R_o / s$ (integrated noise) and $X(s) = N_o$ (white noise)
 
$$Y(s) = K_v (R_o * (K_p + K_i/s) + sN_o) / (s^2 + K_v K_p / N s + K_v K_i / N)$$



 B.3 Time Jitter Derivation for an SJ Phase Tone



$$\text{Power ratio} = L = (A/4)^2 / (1/2)^2 = (A/2)^2$$

$$L \text{ (dBc)} = 10 * \log_{10}(\text{Power ratio}) = 10 * \log_{10}((A/2)^2) \text{ dBc}$$

$$L \text{ (numeric)} = (A/2)^2$$

$$y(t) = \sin(\omega t + \phi_n(t)) \quad \leftarrow \text{Phase jitter}$$

$$= \sin(\omega t)\cos(\phi_n(t)) + \cos(\omega t)\sin(\phi_n(t))$$

Let $\phi_n(t) = \text{SJ tone} = A * \cos(\omega_n t)$, where $A \ll 1$

-> $y(t) \approx \sin(\omega t) + \cos(\omega t)A\cos(\omega_n t)$, using $\sin(\phi) \approx \phi$ and $\cos(\phi) \approx 1$ for $\phi \ll 1$

$$\text{Jitter (in radians)} = A\cos(\omega t)\cos(\omega_n t) = (A/2)\cos(\omega + \omega_n t) + (A/2)\cos(\omega - \omega_n t)$$

$$\text{RMS value of total jitter} = 2 * (A/2) / \sqrt{2} = A / \sqrt{2}$$

$$\text{Power of total jitter (in rad}^2\text{)} = A^2 / 2$$

$$L = (A/2)^2, \rightarrow A^2/2 = 2L$$

$$\text{Power / 1Hz of total jitter (in rad}^2 / \text{1Hz)} = 2 * L$$

$$\text{Integrated Jitter (in rad}^2\text{)} = 2 * L$$

$$\text{RMS phase jitter (in rad)} = \sqrt{2 * L}$$



With $\omega = 2 * \pi * f$, $T = 1/f$, there are $(T \text{ seconds of time}) / (2 * \pi)$ radians

$$\rightarrow \text{Total Time Jitter RMS (in seconds)} = T / (2 * \pi) * \sqrt{2 * L} = 1 / (2 * \pi * f) * \sqrt{2 * L} = 1 / \omega * \sqrt{2 * L}$$

Generalization :

$$\text{Jitter} = 1 / \omega * \sqrt{2 * \text{integrated SSB phase noise}}$$

  B.4 Time Jitter Integration From SSB Phase Noise



$$\sigma_N^2 = 2 \int_{f_1}^{f_2} L(f) df \text{ rad}^2$$

rad T seconds of time = 2π rad
 1 rad = $T / (2\pi)$ seconds of time


$$\rightarrow \text{Time Jitter (RMS)} = \frac{T}{2\pi} \sqrt{2 \int_{f_1}^{f_2} L(f) df} = \frac{T}{2\pi f_c} \sqrt{2 \int_{f_1}^{f_2} L(f) df}$$

B.5 Time Jitter Derivation for additive noise


$$\sin(\omega t) \xrightarrow{\Sigma} y(t) = \sin(\omega t) + A \sin((\omega + \omega_n)t + \phi_1(t)) + A \sin((\omega - \omega_n)t + \phi_2(t)), \quad A \ll 1$$

$N(t)$


Randomized phases

 

Baseband signal,
scale x2

 


Phase noise from one ssb tone :

 

$$\sin(\phi) \approx A / 1, \quad \phi \approx A$$

- Peak phase noise = A rad
- RMS phase noise = $A / \sqrt{2}$ rad
- RMS phase power = $A^2 / 2$ rad²
- Total phase power from 2 ssb tones : A^2 rad²
 
$$\rightarrow \text{Jitter} = 1.0 / (2\pi f) * A \text{ seconds}$$



$$L = (A/\sqrt{2})^2 \text{ rad}^2/\text{Hz} = A^2/2 \quad (\text{see note 1})$$

$$\text{Total Phase noise power} = A^2 \text{ rad}^2 / \text{Hz} = 2L$$

$$\rightarrow \text{Jitter} = 1.0 / (2\pi f) * \sqrt{2L}$$

note1 1/2 of noise power goes onto phase noise,
1/2 of noise power goes onto amplitude noise

C.1 Digital Line-Coding/Modulation : TCM

Trellis-Coded Modulation (TCM)

Advantages :

Add coding gain with no bandwidth extension


Disadvantages :

Complexity

Constellation moves away from NRZ, increases Peak/Average power

Used in :

Phone modems
Cellular standards

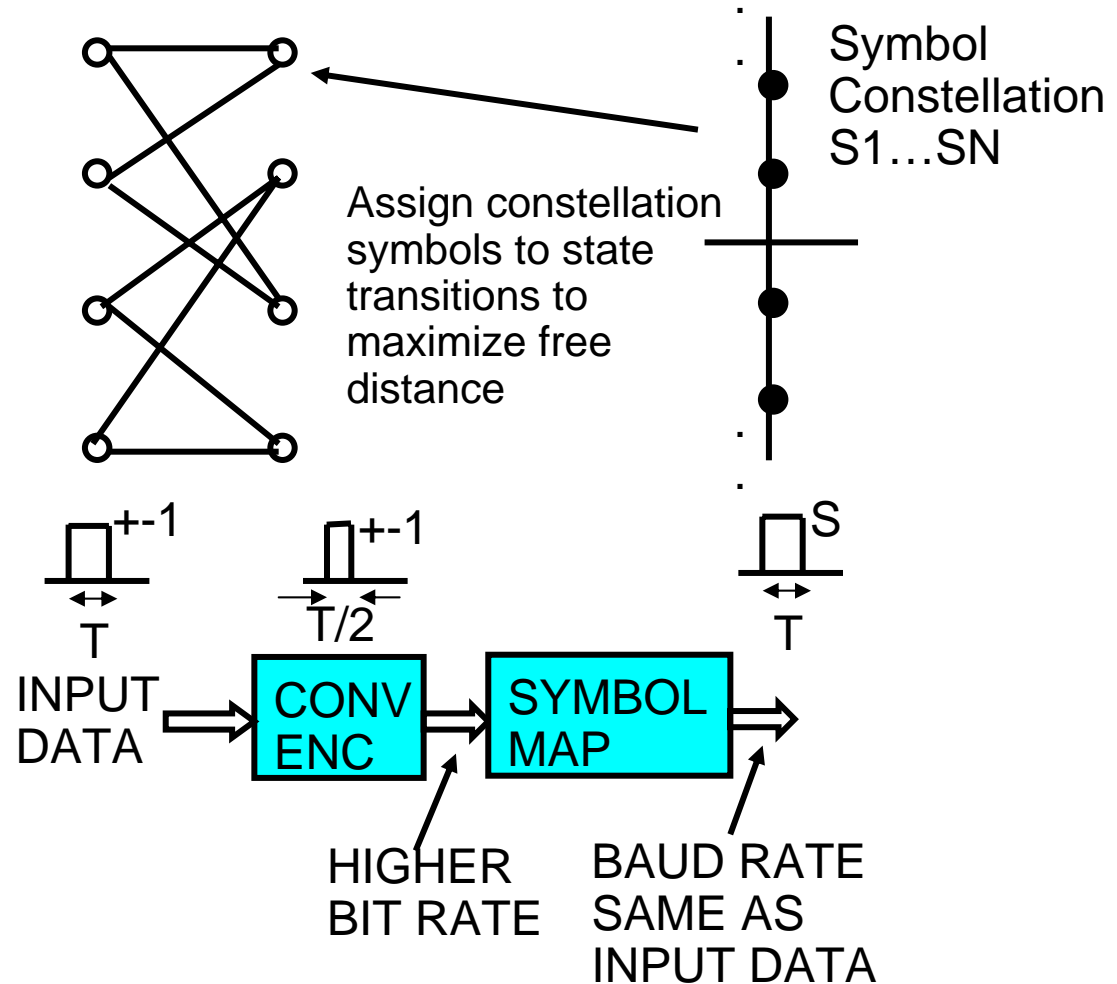

C.2 Subchannel Modulation : OFDM



Orthogonal Frequency Divison Multiplexing (OFDM)

Advantages :

Handles dispersive channel well


Disadvantages :

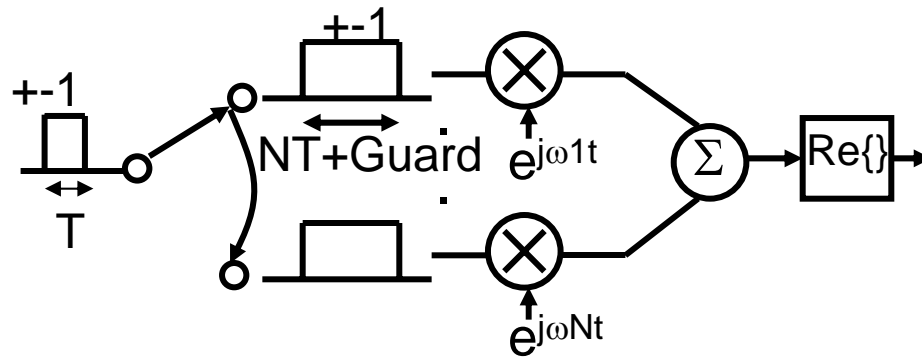 - Complexity
- High Peak/Average Power
- “Guard time” needed to maintain subchannel orthogonality



Used in :

- DSL Broadband
- 802.11a/g Wireless

 

SUBCHANNEL BAUD RATE
 $\sim 1/N$ AS FAST AS INPUT DATA