



SSCS DLP, Fort Collins

Wide band RF CMOS circuit design techniques

Domine Leenaerts



Semiconductors, The Netherlands


Content

- **Why wide band RF design?**
- **How to make a wide band LNA?**
- **What about the wide band Rx architecture?**
- **What about the technology?**
- **Conclusions**

History: SpeakEasy project (1992)

- Large scale military software defined radio
 - motivated in large part by the communications interoperability problems that resulted from different branches of the military services having dissimilar (non-interoperable) radio systems
 - ten different radio waveforms in software on a single platform operating in frequency bands between 2 and 2000 MHz
 - Operated initially at the TMS320C40 processor

History: SpeakEasy project (1992)

 

Final result in 1994:


**several hunderd processors and
the 'radio' filled the back of a truck**

Today: 10 different standards?





There is a convergence of standards ongoing, but still...

Today: 10 different standards?

 

Today in industry

 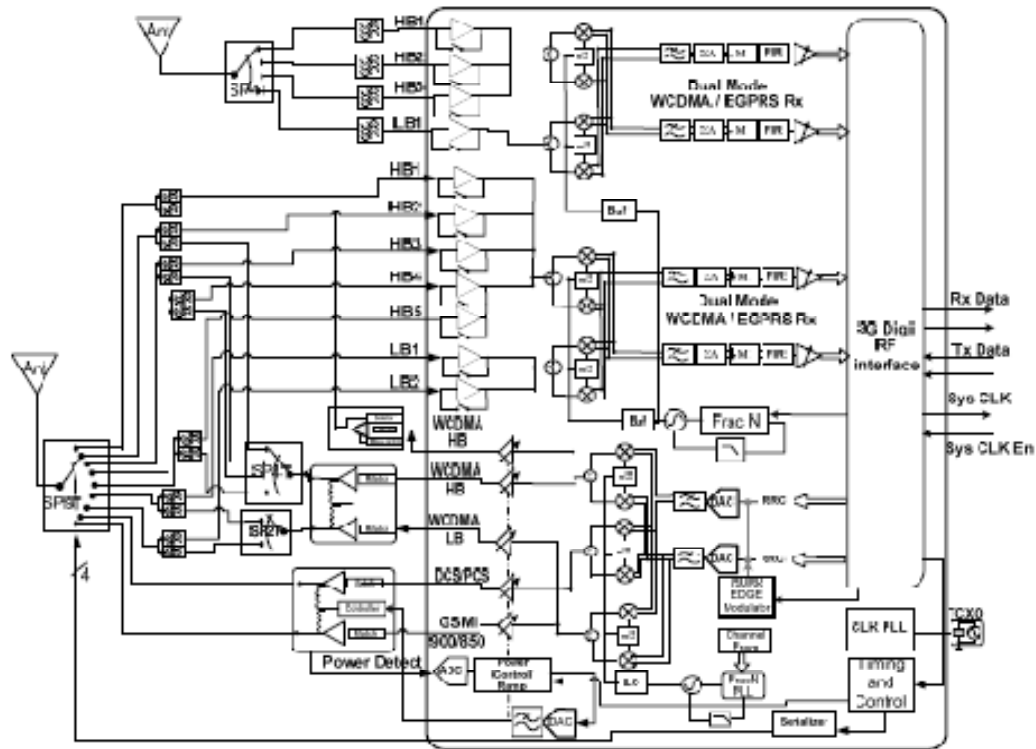


130nm cmos

WCDMA/HSDPA/HSUPA/EGPRS, Skyworks

ISSCC 2009

Today in industry

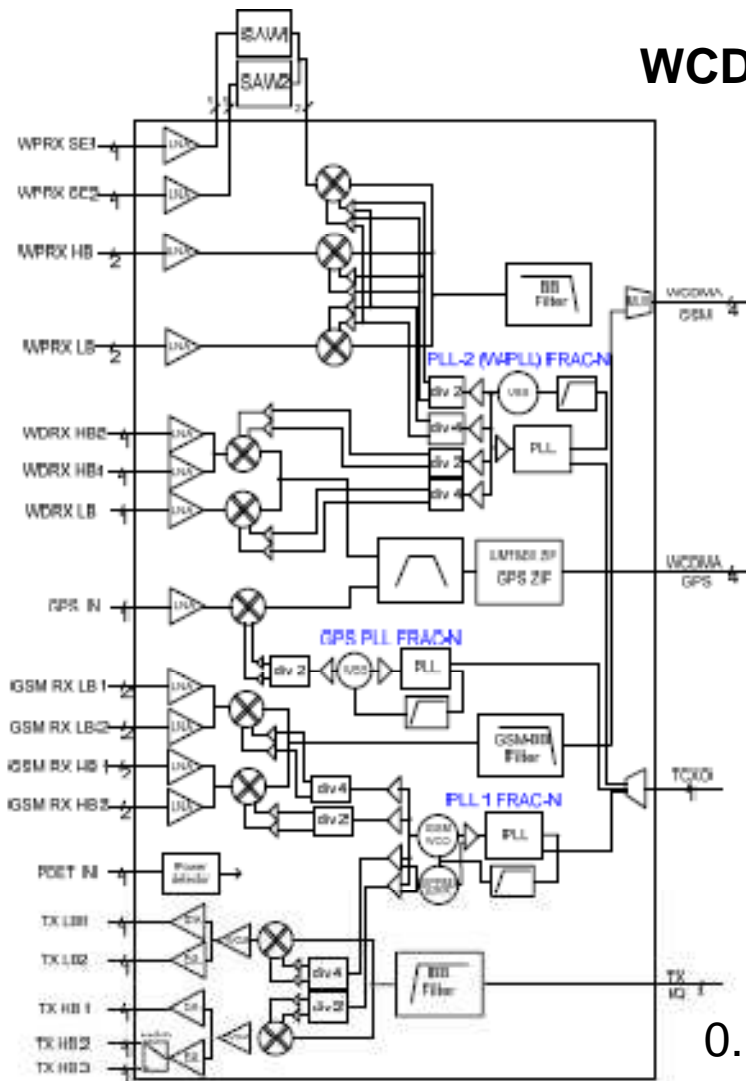

WCDMA/HSPA/EGPRS+ GPS and Rx diversity

WCDMA:4-LNA Primary Rx (2 SAW-less)

WCDMA:3-LNA diversity


Quad-Band GSM/EDGE (800-900-1800-1900)

Qualcomm

0.18um CMOS

ISSCC 2009

Today in industry

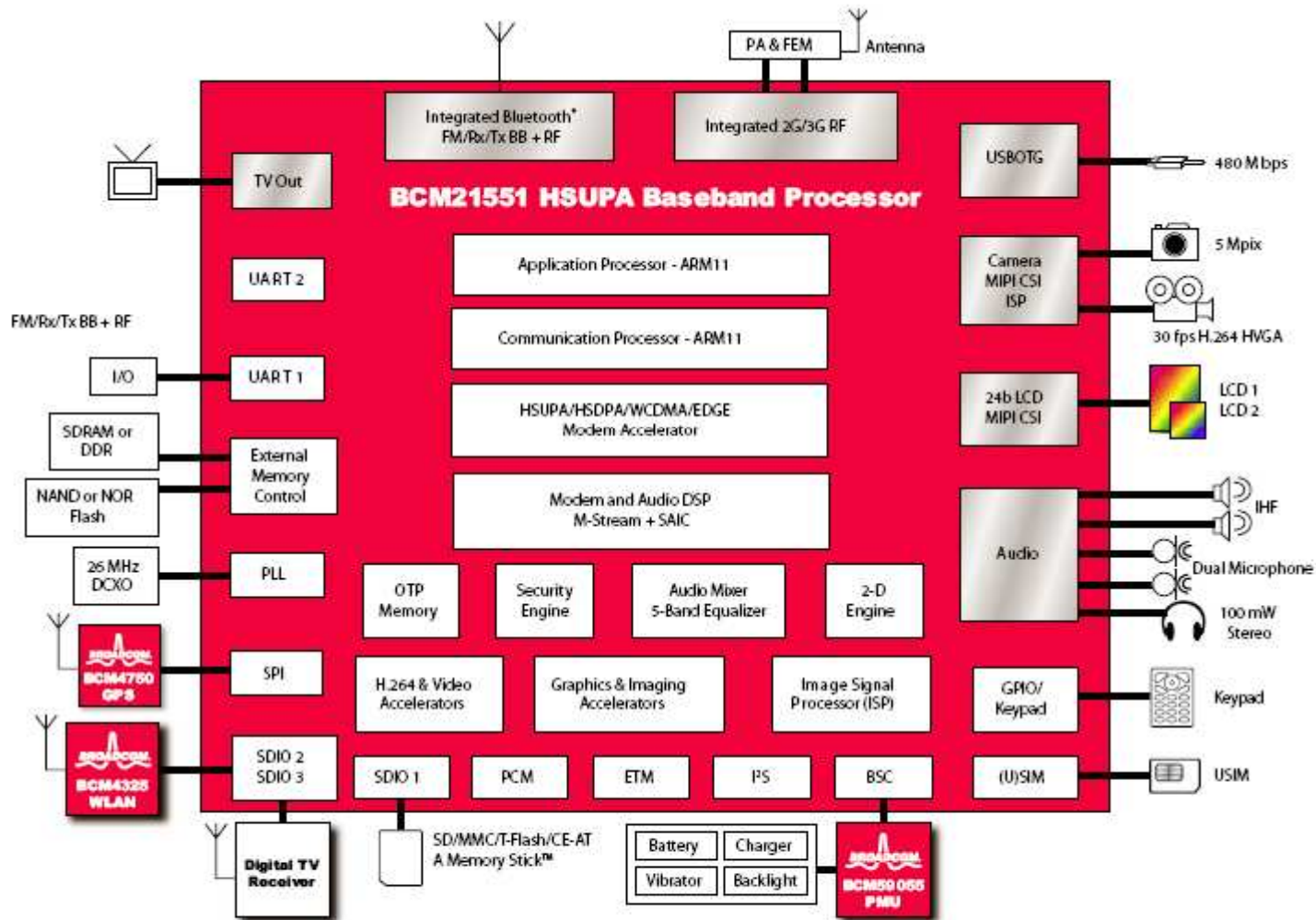

Chip Block Diagram

Source: www.broadcom.com


HSUPA+BT+FM in 65nm CMOS

Today in industry

- Industrial focus is on
 - Multi-band / multi-mode
 - Selectivity at RF
 - Front-end module by means of antenna filters
 - Selective LNA's
 - LO generation per mode or band


Software-defined radio (SDR)

 - Based on signal processing
 - A/D requirements
 - Digital processing



Use Reconfigurable radio instead

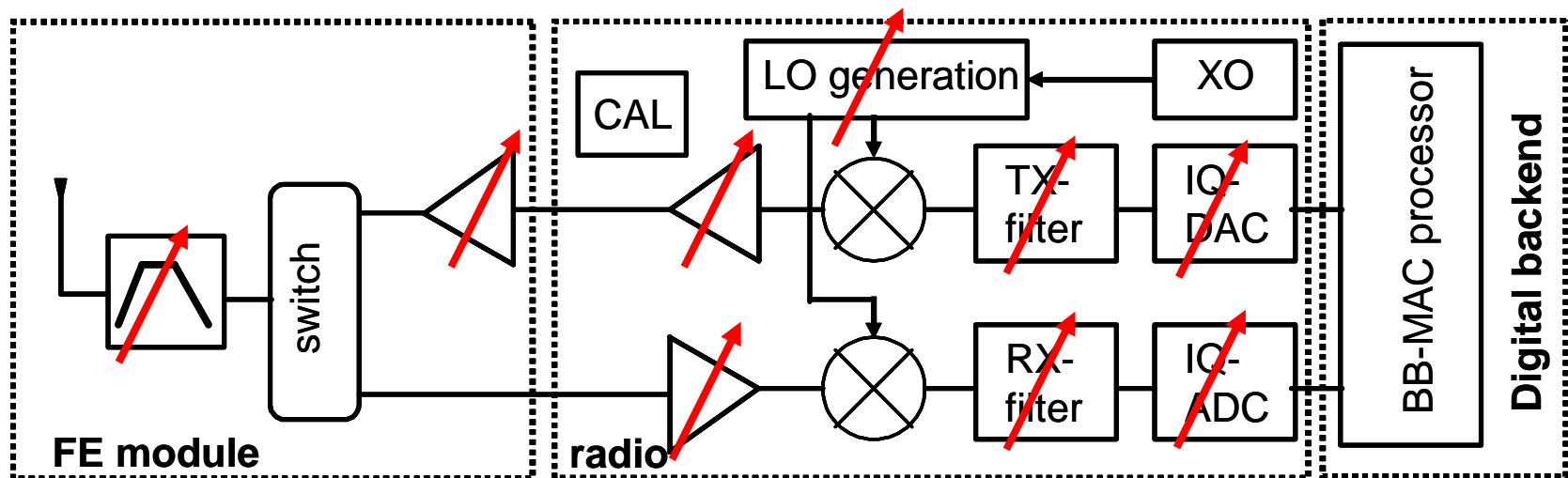- Analog selectivity
 - A/D requirements more relaxed
 - Wide-band RF front-end
 - Digitally assisted radio / FE module



Need of Wide-band RF front-ends

- First attempts were made by the development of UWB chipsets
 - 3 – 10 GHz
 - Started in 2003 with LNA design (see ISSCC 2004)
- Now focus on reconfigurable front-ends for 0 – 5 GHz operation
 - Started around 2005 (see ISSCC 2006)


Wide band LNA: What's the problem?

Impedance match

$$Z_s = Z_i^* \Rightarrow P_{s,av} = P_{i,del}$$

Noise match

$$Z_s = Z_{opt}$$

 


Z_i is mainly capacitive

$\text{Im}(Z_{opt})$ is inductive in nature

**How to obtain power match and noise match
over wide bandwidth?**

What is the problem?


Wide band
impedance match

 

$$F \geq 2 + \frac{4\gamma}{\alpha} \frac{1}{g_m R_s}$$

NF >> 3dB


Narrow band
impedance match

 

$$F \geq 1 + \frac{2}{3} \frac{\omega L_s}{Q R_s}$$


$$Z_{in} \approx \frac{g_m L_s}{C_{gs}} + sL_s + \frac{1}{sC_{gs}}$$

Possible solution

 

Wide band impedance match using filter as impedance converter


The first attempts

 

ISSCC2004: Bevilacqua

Band-pass LC matching network

NF: 5.5dB (3-8GHz)

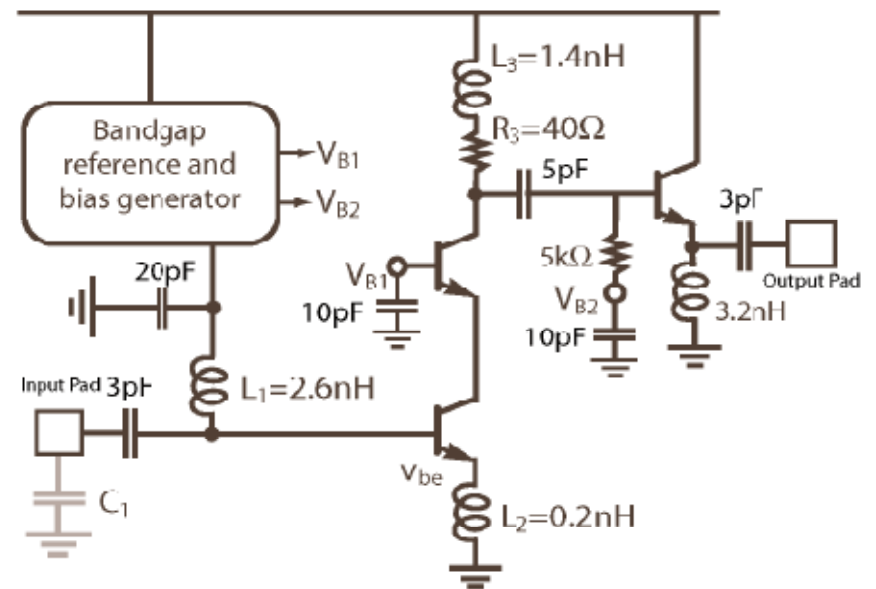


ISSCC2004: Ismail

Band-pass LC matching network

NF: 4.5dB (2-10GHz)

**Both are bulky due to # integrated inductors
and single-ended input/output**


Other possible solution

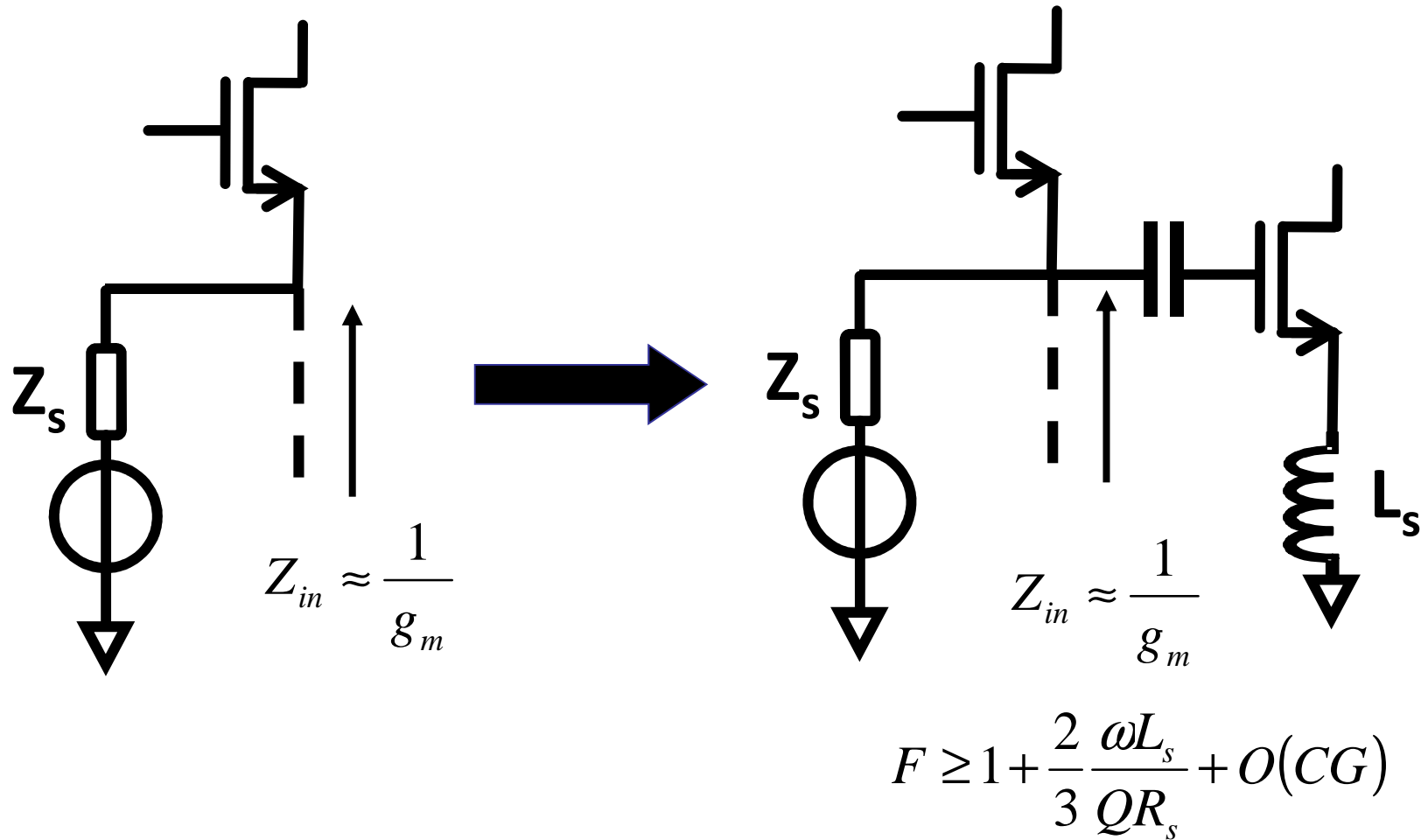

Note: inherent single-to-differential conversion


'Second' Generation

90nm CMOS

 

**decouple the noise and input impedance match
but still bulky**

Next generation: starting point

 


Simultaneous:

- Single-to-Differential
- Balanced Gain
- Broadband input match ($\sim 1/g_{mCG}$)
- Noise Canceling
- Distortion Canceling

[Blaakmeer et al. ESSCIRC '07]

LNA: noise canceling

 

Noise canceled, signal amplified at differential output

LNA: limited bandwidth


- Limited bandwidth at output CG-stage:

$$\left. \begin{aligned} R_{CG} &= A_{V,CG} \cdot R_S \\ &= 200 \Omega \quad @ \quad A_{V,CG} = 4 \\ f_{-3dB} &= \frac{1}{2 \cdot \pi \cdot R_{CG} \cdot C_{Load}} = 10 \text{ GHz} \end{aligned} \right\} \rightarrow \mathbf{C_{Load} < 80 \text{ fF}}$$


- Inductive peaking required
 - Contrasts aim: no on-chip inductors

Solution: don't make voltage gain @ RF!


Solution: insert mixer

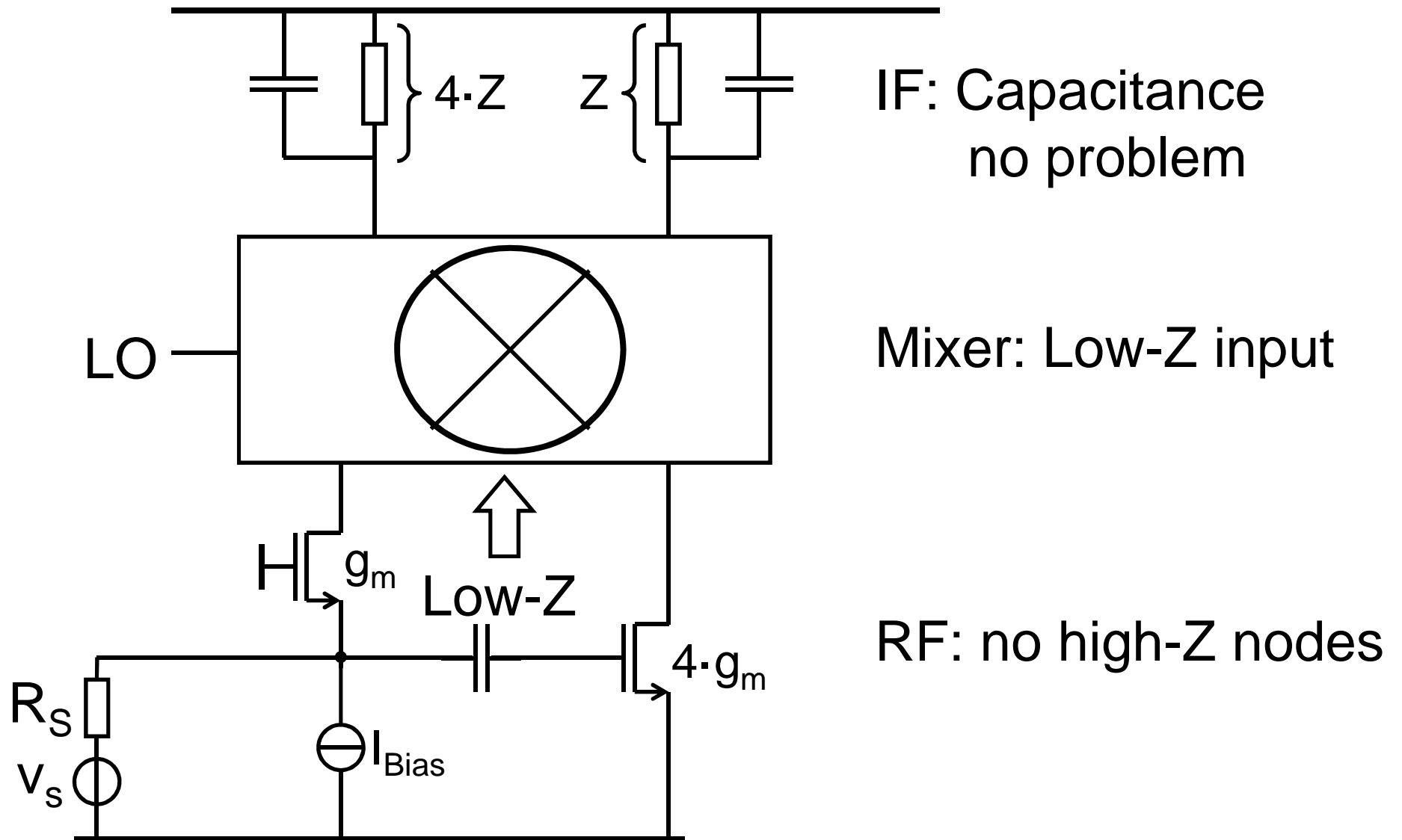


Solution: insert mixer

 


Solution: noise cancellation @ IF

 


BLixer: IQ balanced

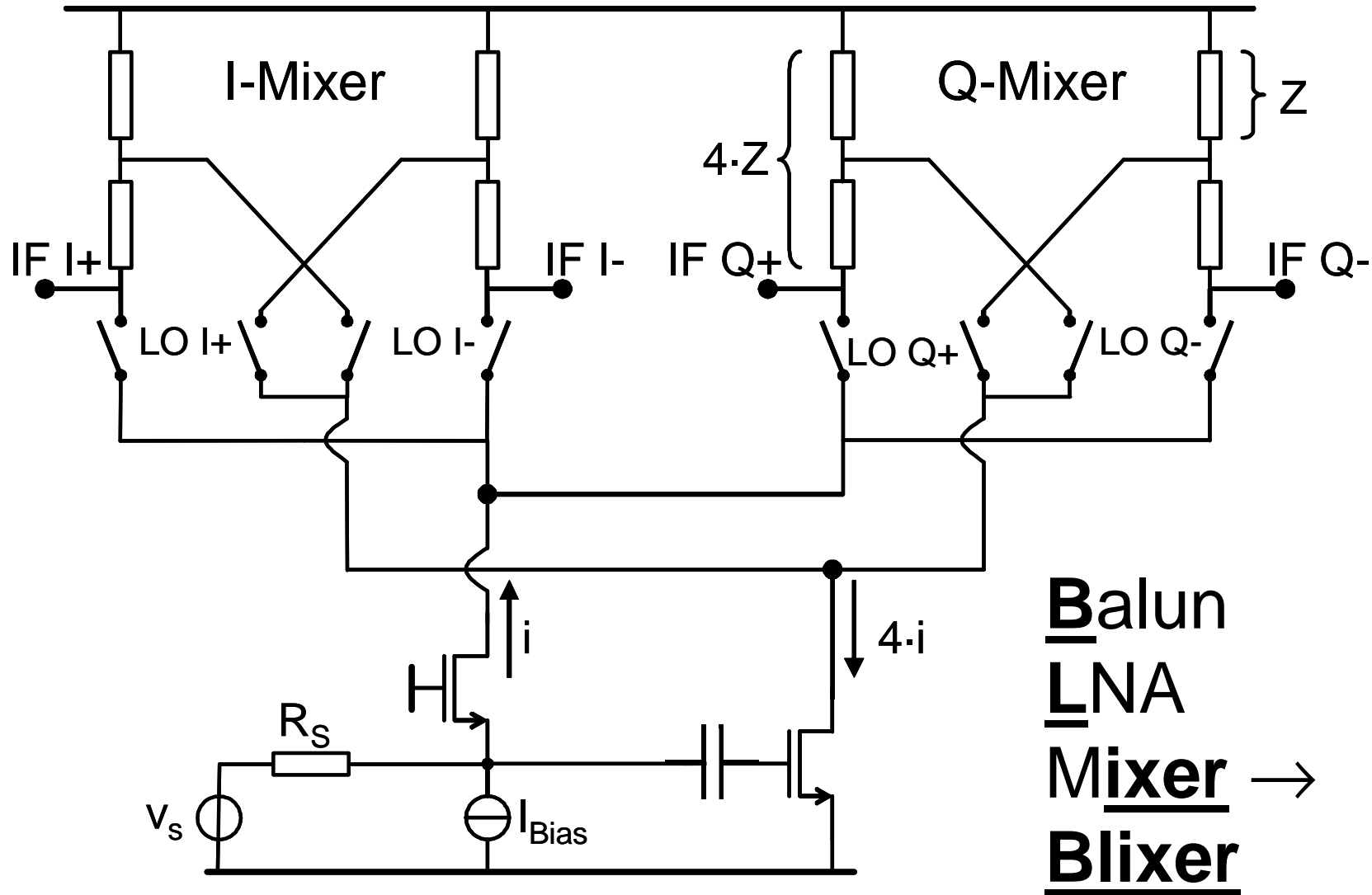


BLixer: 50% duty cycle

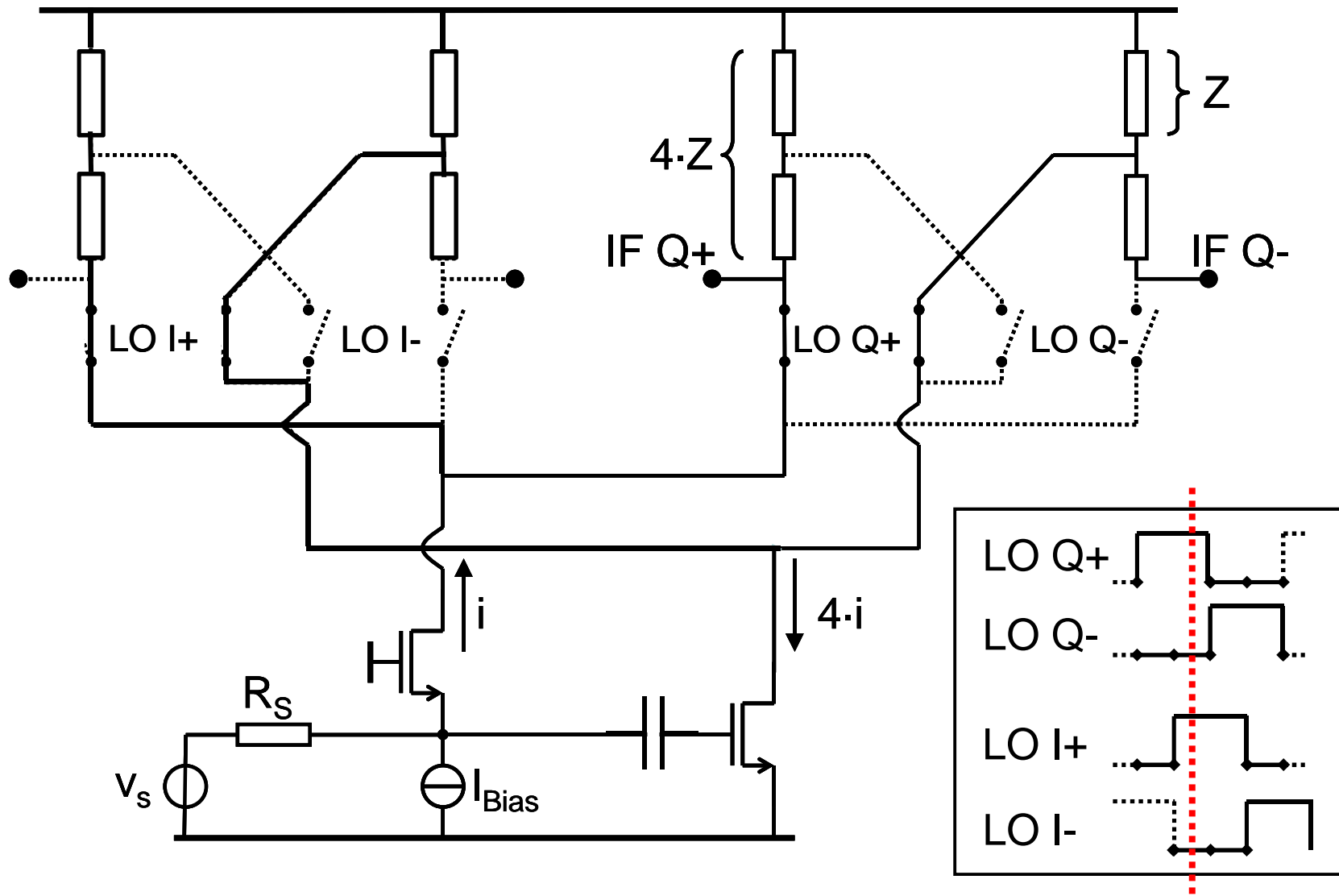

BLixer: 25% duty cycle

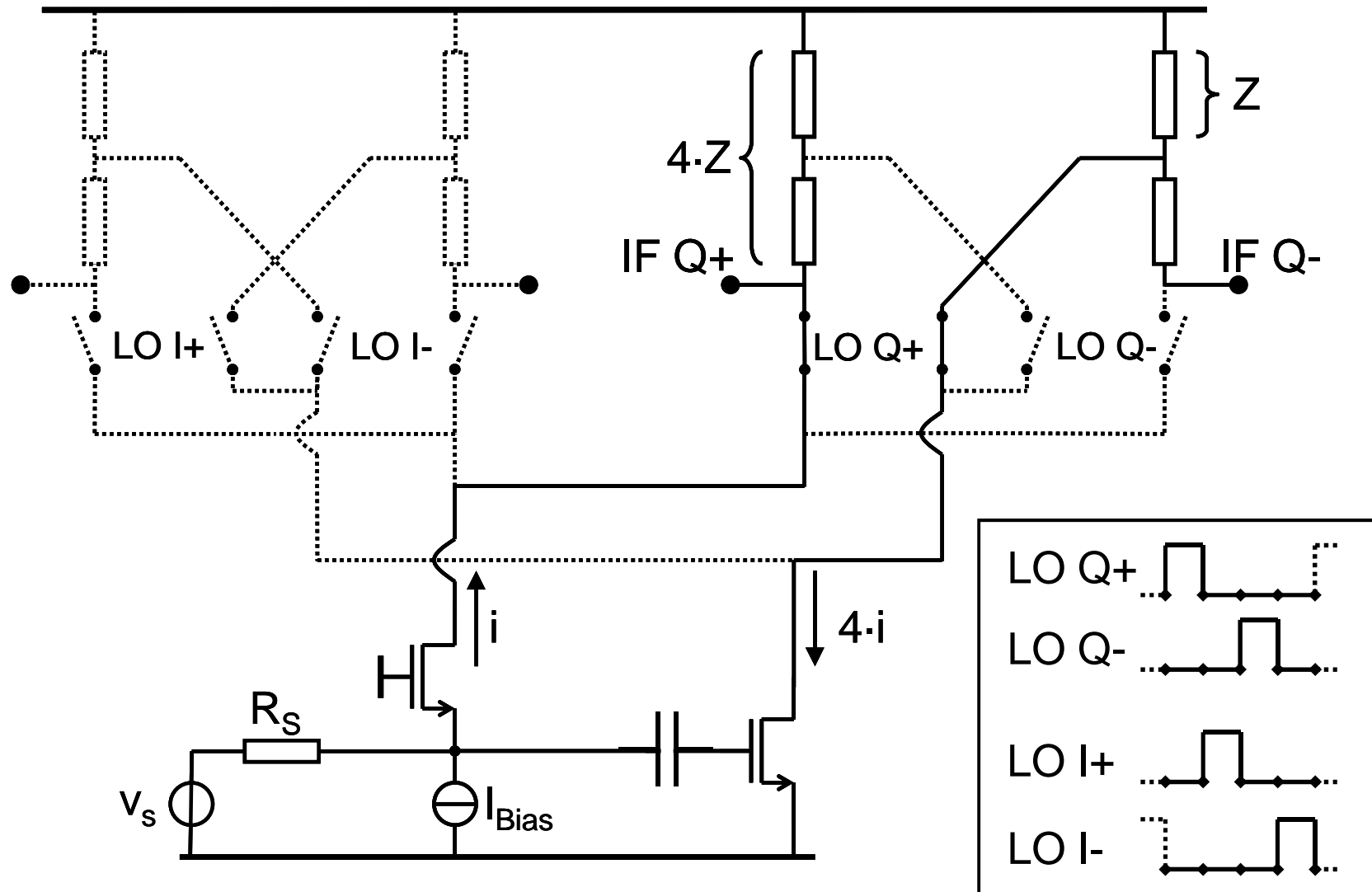

BLixer: silicon

 


Baseline
65nm CMOS
1.2V supply


Active area
< 0.02 mm²

[Blaakmeer et al. ISSCC '08]

BLixer: measured results

 

Wide band behavior at RF


 


... and at IF/BB

BLixer: measured results



- Linearity:
 - IIP3 @ RF: -3 dBm (5.2 & 5.7GHz, $f_{LO} = 4.6$ GHz)
 - IIP2 @ RF: +20 dBm (2.4 & 5.7GHz, $f_{LO} = 3.2$ GHz)
 - IIP2 (Mix-leak.) $> +40$ dBm (5.7 & 5.8GHz, f_{LO} : 0.5 - 7 GHz)
- Quadrature accuracy:
 - Phase error $< 3^\circ$
 - Gain error < 1 dB
- LO leakage < -50 dBm

What about inverters?

  


What about inverters?


Add package:
HVQFN

  

What about inverters?

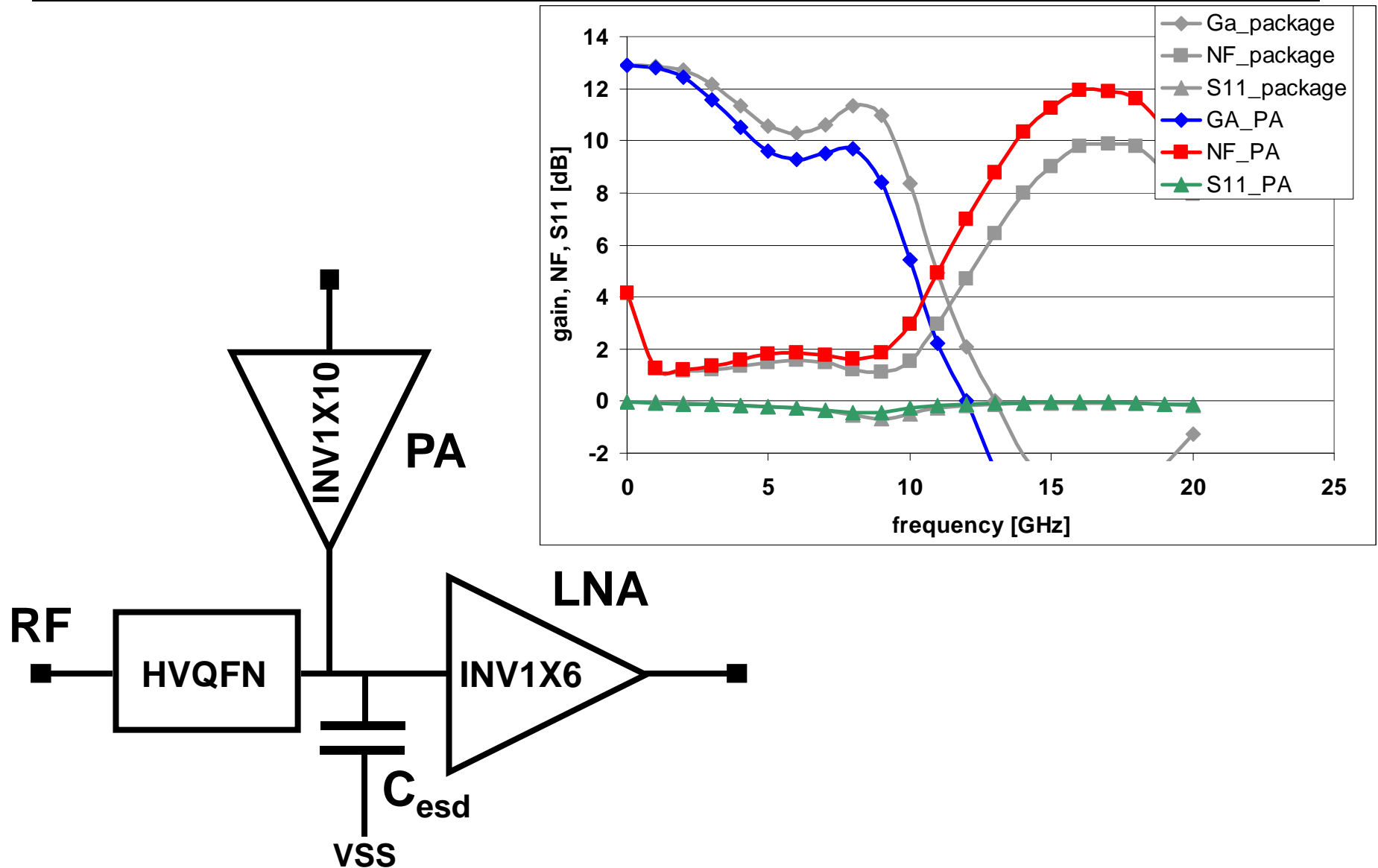


'Inverter-only' LNA

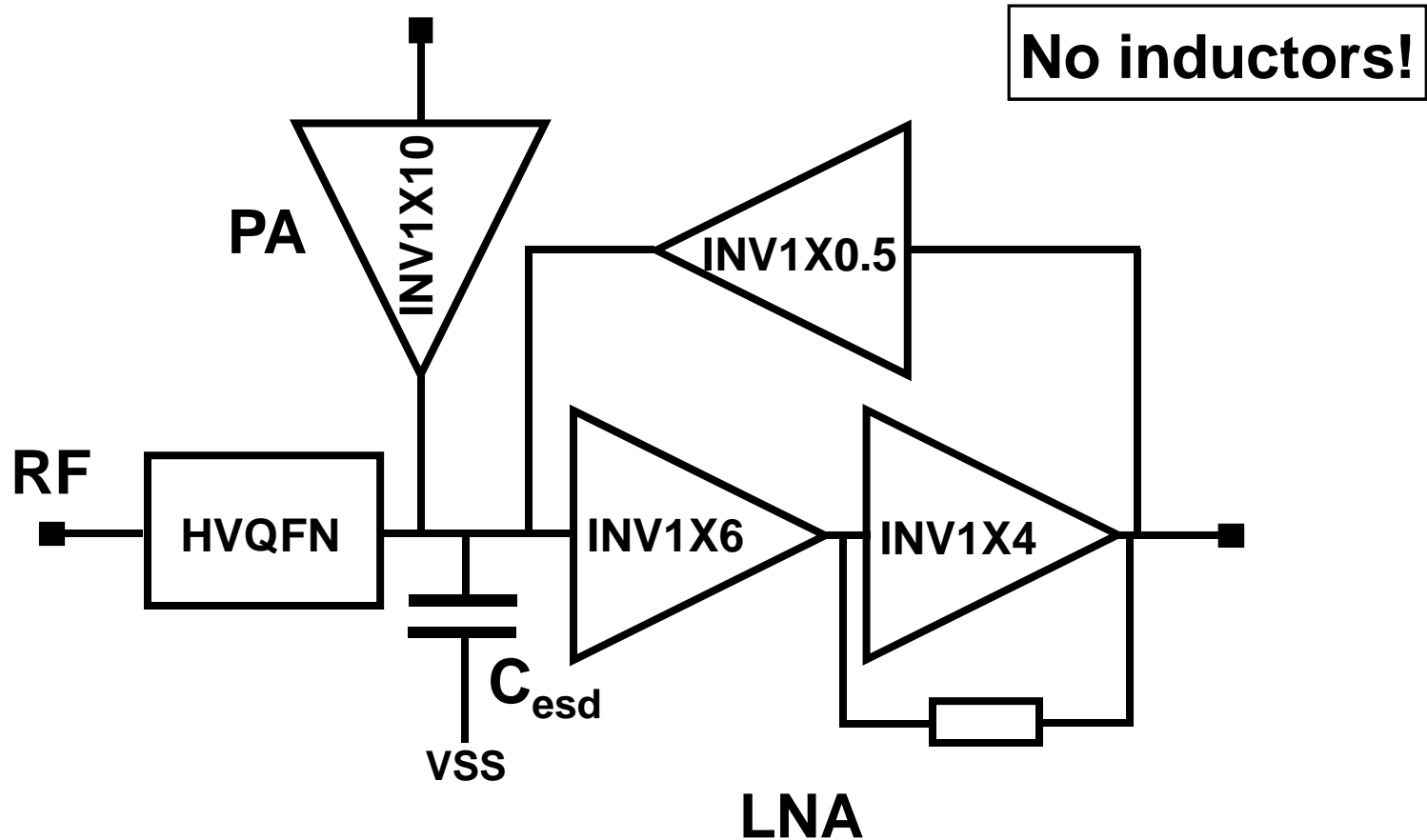


Add additional stage and feedback in LNA

'Inverter-only' LNA

 


'Inverter-only' PA


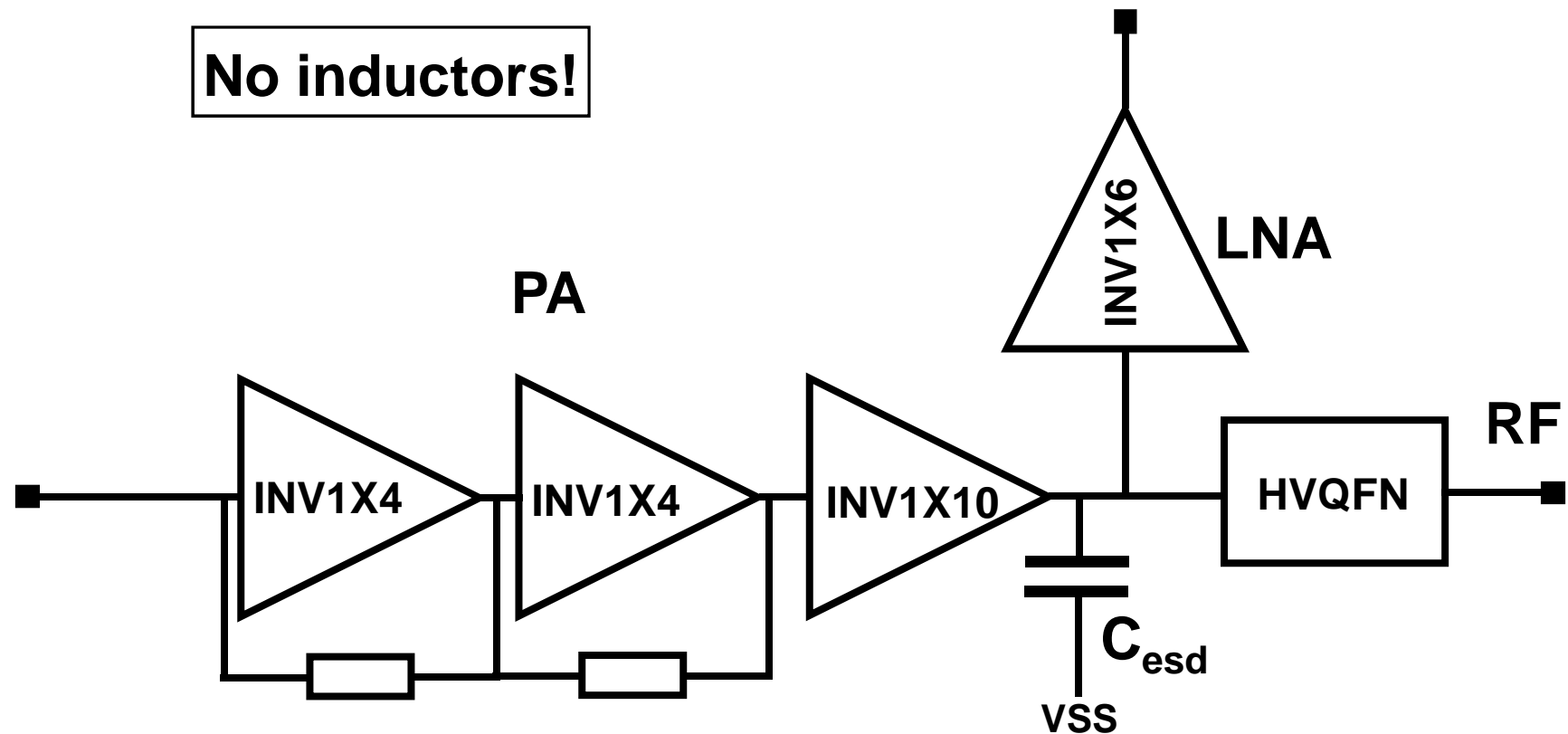


Add additional stages and feedback in PA

'Inverter-only' PA

 

RF front-end only with inverters!

  

radio



65nm (LP) CMOS

[Leenaerts et al. ISSCC '09]

-
- We can make wide band LNA's, but what about the receiver?


What about the RX architecture?

- Commodity is to use passive mixers
 - Inherently wide band nature as they act as switch only
 - Can be made very linear
- Followed by analogue wide band BB filters
 - Tunable in filter order, bandwidth

  


ISSCC 2009: IMEC, SDR in 45nm CMOS

... but how to handle interferers?

 

Wide band at RF give rise to interference issues


... but how to handle interferers?

 


and 'square-wave' LO results in harmonic mixing

... but how to handle interferers?

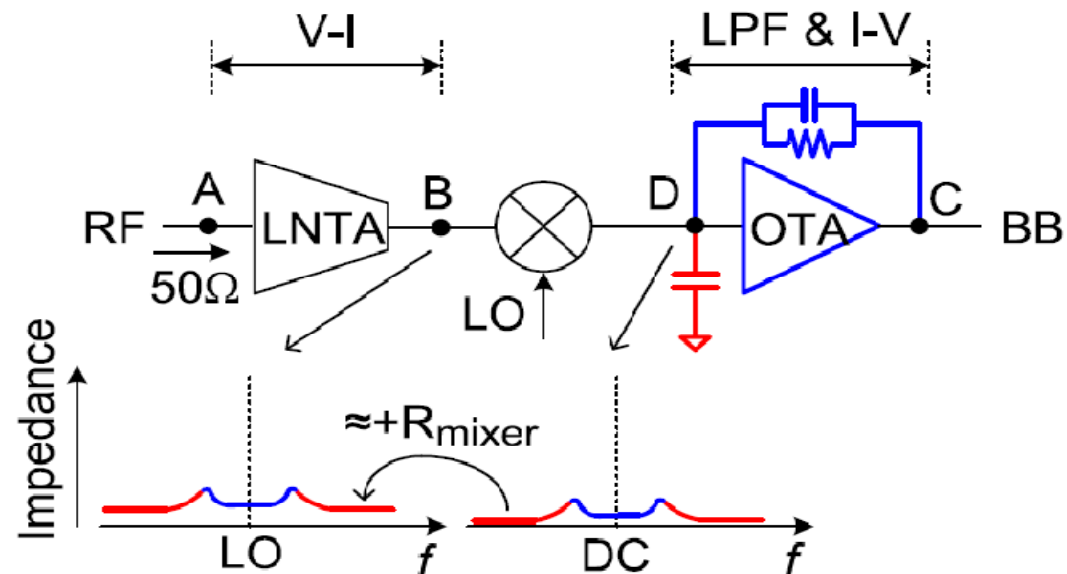- One solution is to use band-pass filters
 - Need tunable BP, difficult at RF
- Other solution is to NOT make (too much) gain at RF




... but harmonic mixing remains

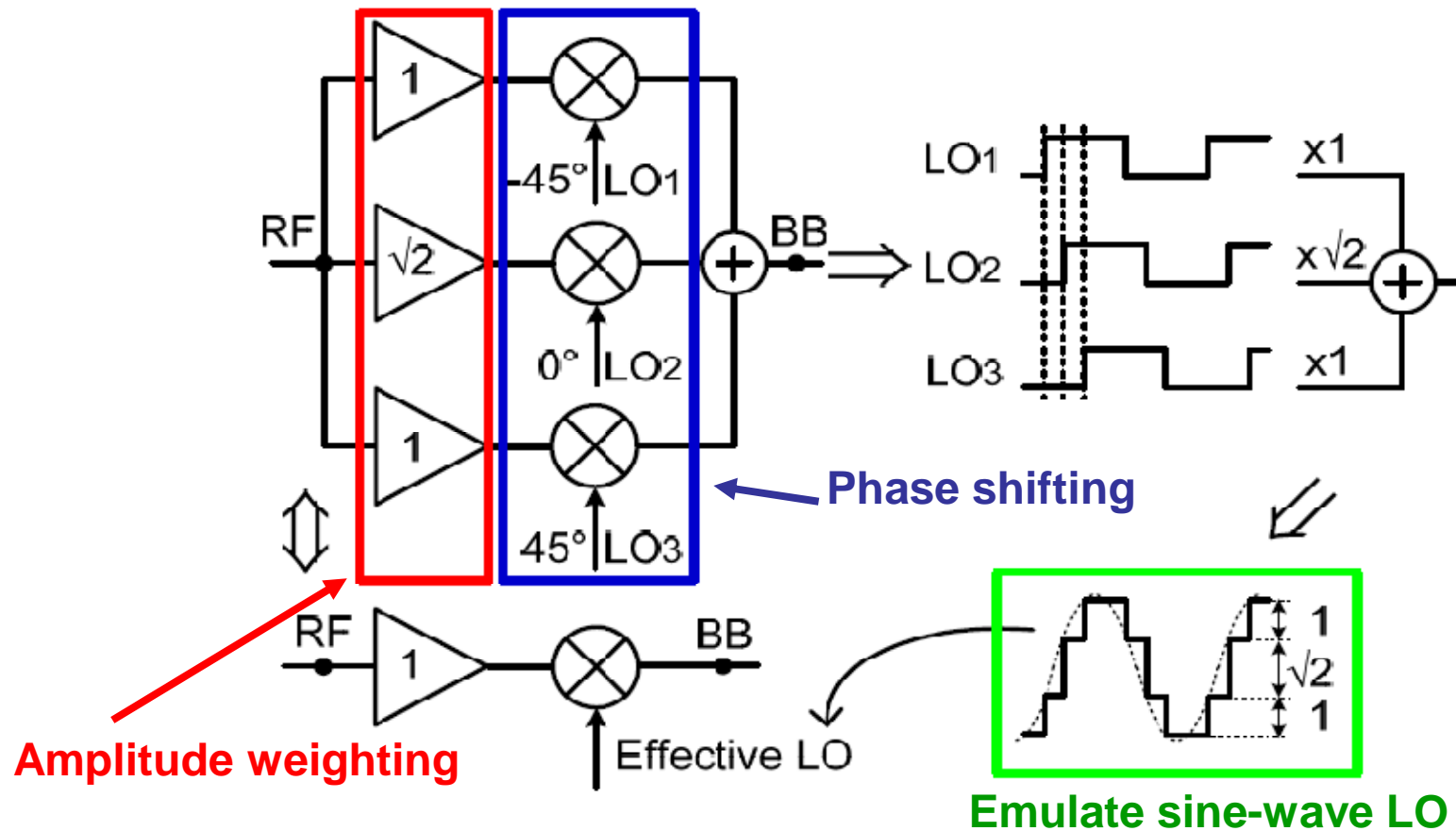

harmonic rejection mixer removes $3*LO$ and $5*LO$



... but how to make $\sqrt{2}$ accurate?

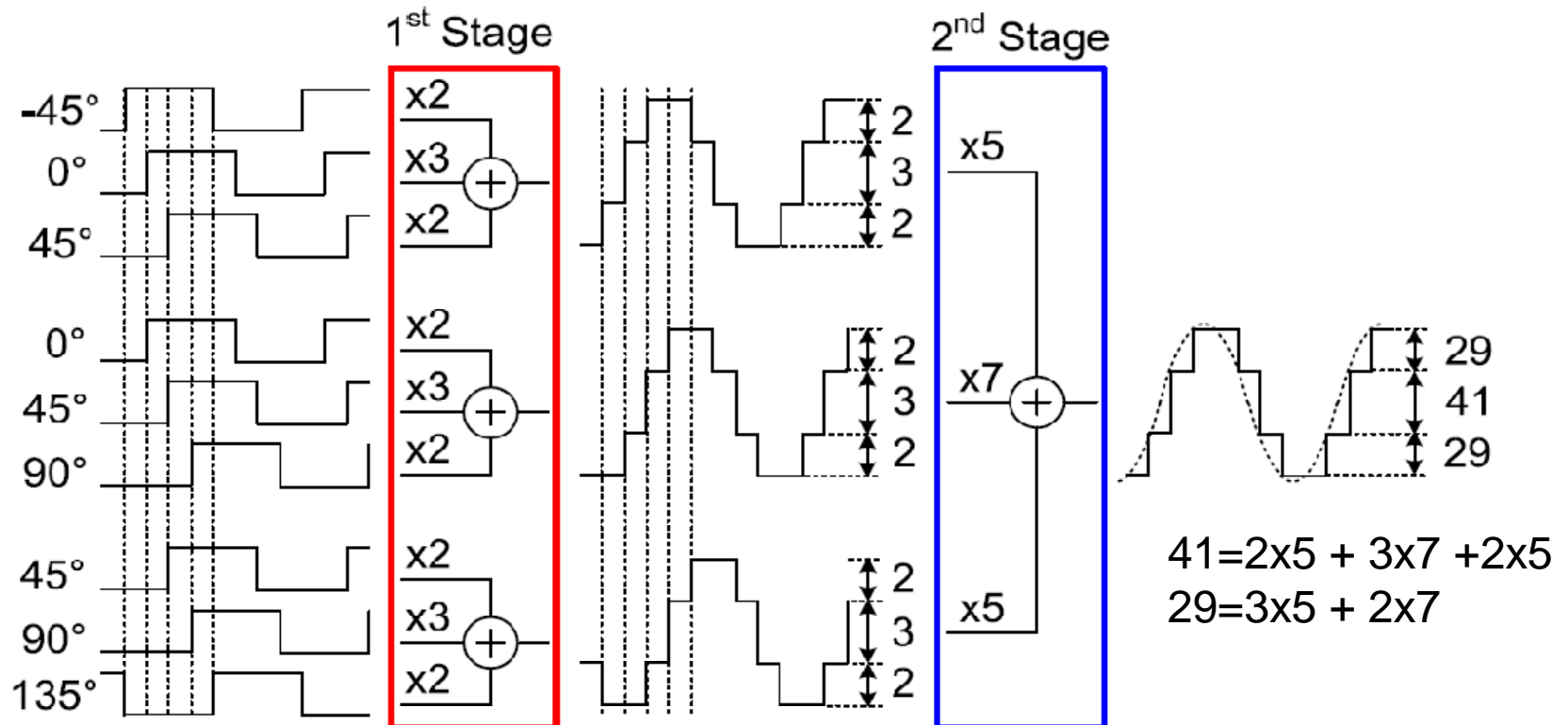


$41/29 = 1.4138$ and $\sqrt{2} = 1.4142$, so error is 0.03%

2-stage poly phase network

And the result ...

  

| | |
|----------------------------------|-----------------|
| LO Frequency | 0.4~0.9GHz |
| Gain | 34.4±0.2dB |
| DSB NF | 4dB±0.5dB |
| $S_{11} < -10$ dB | 80M~5.5GHz |
| In/Out-of-band IIP3 ¹ | +3dBm / +18dBm |
| In/Out-of-band IIP2 ² | +46dBm / +51dBm |
| IF Bandwidth | 12MHz |
| 1/f noise | 30kHz corner |

 


65nm CMOS


... but what about other interferers?

- Harmonic mixing helps only for interferers which are at harmonics of the used LO frequency
- How do we improve robustness against other interferers?
 - Make notch at RF

Notch at RF by translational loop

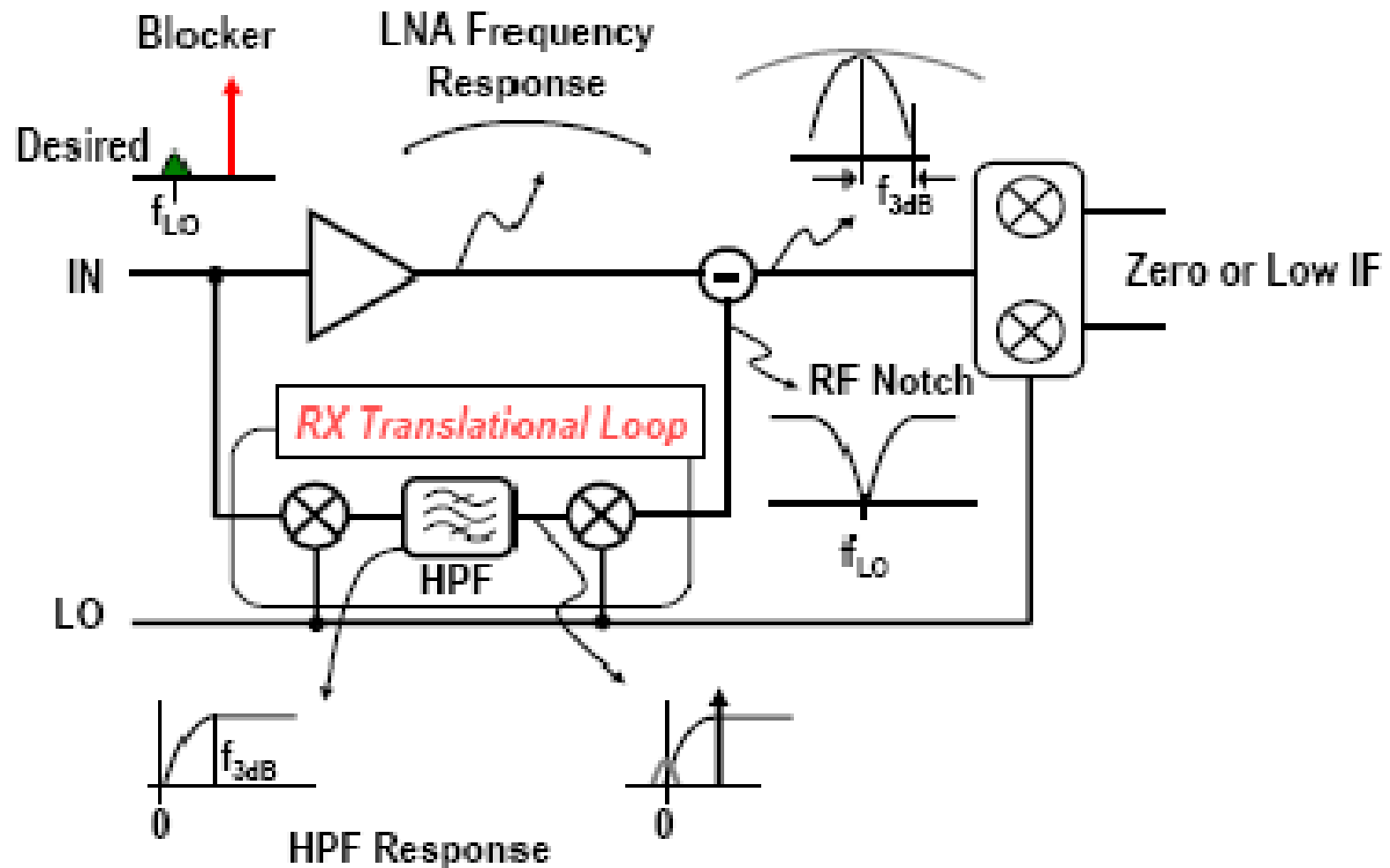

Notch at RF by translational loop

 

| Parameter | Measured, w/ filtering | Simulated, w/ filtering | Measured, w/o filtering | Simulated, w/o filtering |
|-----------------------|------------------------|-------------------------|-------------------------|--------------------------|
| Gain | 20.9 | 21.3dB | 23.4 | 23.5dB |
| NF | 6.8dB | 5.8dB | 3.9dB | 3.5dB |
| In-Band IIP3 | N/A | | 2.6dBm | 2.8dBm |
| 3-dB Bandwidth | 4.5MHz | 6MHz | 250MHz | 220MHz |
| Stop-band Rejection | > 21dB | > 23dB | 3dB | 3dB |
| S ₁₁ | < -10dB | < -10dB | < -10dB | < -10dB |
| Current Drain | 29mA | 29mA | 8mA | 8mA |
| Power Supply | 1.2/2.5V | | | |
| Operating Temperature | -20°C to 85°C | | | |
| Active Die Area | 0.28mm ² | | | |
| Technology | 65nm CMOS | | | |

Impact on NF of LNA is 3dB, so activate filter only in presence of interferer

Some conclusions

- Wide Band CMOS design is possible
 - Convergence towards a receiver comprising wide band LNA, passive mixers and BB filtering
 - Additional tricks added to cope with interference are still needed
- But which technology is favorable?

What about the technology?

Does CMOS scaling improves wide band behavior?

- Technology RF performance
 - 180nm, 90nm, 65nm, 45nm
- UWB CMOS circuits
 - 90nm, 65nm, 45nm (and SiGe BiCMOS)
- UWB receiver design
 - 65nm, 45nm

Used technology

- All experiments have been done in a low standby power process node, i.e. LP CMOS

| CMOS | 90nm | 65nm | 45nm |
|---------------------------------------|---------|---------|---------|
| Lgate [um] | 0.1 | 0.06 | 0.04 |
| Vdd [V] | 1.2 | 1.2 | 1.1 |
| I _{em,M1,minW} [mA@110°C] | 0.21 | 0.11 | 0.07 |
| #metal | 6 + ALU | 7 + ALU | 7 + ALU |



$$C = \epsilon_o \epsilon_r \frac{\text{Area}}{\text{distance}}$$

Some definitions

- Cut-off frequency f_T
 - unity gain current frequency for short-circuited output

$$f_T \sim \frac{g_m}{2\pi C_{gg}} \longrightarrow \text{input capacitance}$$

- Voltage gain bandwidth f_A
 - Frequency for 3-dB DC voltage gain drop, calculated for a resistive load making the DC voltage gain 2x

$$f_A \sim \frac{g_m}{2\pi A_{dc} C_{dd}} \longrightarrow \text{output capacitance}$$

Some definitions


- 1-dB minimum Noise Figure frequency (f_{NF1dB})
 - frequency for which this NF is still reached assuming optimum NF matching
- Finger width W_f
 - Folded device finger width: $W_f = W/FOLD$

Difference schematic - layout


- Schematic
 - MOS model takes into account *naked device* behavior.
- Layout
 - parasitics due to metal connections, especially CO-M1
 - metal layers to fulfill current reliability

Layout has major impact in deep sub-micron



Difference schematic - layout

 

 - NMOS device
- $L = 0.18 \mu\text{m}$
- $W = 32 \mu\text{m}$
- contact = 2
- @ fold = 8
 - $f_T = 70 \text{ GHz}$
 - $f_T = 60 \text{ GHz}$




Comparison of this effect

  


- For both devices: single finger, double gate contact
 - Purple: schematic (naked device)
 - Blue: layout extraction
- Serious impact of metallization
 - 90nm: 70%
 - 65nm: 55%

65/45nm: ft obtained after layout

 

65nm LP: ft naked device: 160GHz

 
($W_f = 0.5\text{ }\mu\text{m}$ for 1 and 10 μm)




45nm LP: ft naked device: 270 GHz

($W_f = 0.5\text{ }\mu\text{m}$ for 2 and 10 μm)

Comparison for f_t : scaling helps

 

65nm: influence of finger-width

 

seems optimal

layout includes only M1

RF performance incl. all layout effect

| CMOS | f_t [GHz] | f_a [GHz] | f_{NF1dB} [GHz] | Wf opt. |
|-------|-------------|-------------|-------------------|----------------|
| 180nm | 41 | 39 | 10 | ≈ 3 |
| 90nm | 80 | 72 | 40 | ≈ 1.7 |
| 65nm | 120 | 110 | 44 | ≈ 1 |
| 45nm | 200 | 130 | 53 | ≈ 0.67 |




$Wf/L_{min} \approx 16$

How realistic is peak f_t , f_a ?

- Peak values are normally reached for V_{gs} close to V_{dd}
 - happens for instance in cross-coupled diff pair in most VCO topologies
- But what happens in more realistic situations, e.g. $V_{gs} = 1/2V_{dd}$?
 - e.g. situation in frequency divider, LNA, ...

How realistic is peak f_t , f_a ?

 

How realistic is peak ft, fa?


| CMOS | 90nm | 65nm | 45nm |
|--------------|---------|-----------|-----------|
| Naked device | 115 | 160 | 270 |
| Vgs=Vdd | 80 / 72 | 120 / 110 | 200 / 130 |
| Vgs=1/2Vdd | 49 / 38 | 51 / 41 | 47 / 28 |

x / y = ft / fa [GHz / GHz]

Scaling and wide band RF

- **LNA performance**
- **Frequency divider performance**
- **Dual band receiver in 65nm**
- **Dual band receiver in 45nm**

A CMOS wide band LNA

 


Transformer:

- Single-ended \rightarrow differential
- Impedance matching
- Voltage feedback


Resistor:

- Current feedback

A CMOS wide band LNA: 65nm

 

[ISSCC2007]

 



Gain: 11dB

3-dB BW: 7.5GHz

NF: 2.5dB

iIP2: +25dBm

A CMOS wide band LNA: 45nm

  

Gain: 8dB

3-dB BW: 11GHz


NF: 3dB

iIP2: +25dBm

CMOS LNA: comparison

- Input device (for roughly same g_m)
 - W/L 90nm: 200/0.1 $\mu\text{m}/\mu\text{m}$
 - W/L 65nm: 240/0.06 $\mu\text{m}/\mu\text{m}$
 - W/L 45nm: 200/0.04 $\mu\text{m}/\mu\text{m}$


x2
x1.25

 


CMOS LNA: comparison

| LNA | 90nm | 65nm | 45nm |
|------------|------|------|------|
| Gv [dB] | 9 | 11 | 10 |
| BW [GHz] | 7.5 | 7.5 | 11 |
| NF [dB] | 2.5 | 2.5 | 3 |
| iIP2 [dBm] | +15 | +25 | +25 |
| iIP3 [dBm] | 0 | +12 | +6 |
| Pdiss [mW] | 18 | 20 | 30 |

CMOS LNA versus BiCMOS

 


[ISSCC2005]

 


| LNA | 65nm | SiGe 0.25um |
|------------|------|-------------|
| Gv [dB] | 11 | 20 |
| BW [GHz] | 7.5 | 12 |
| NF [dB] | 2.5 | 3 |
| iIP2 [dBm] | +25 | +25 |
| iIP3 [dBm] | +12 | +10 |
| Pdiss [mW] | 20 | 12 |

65nm and 45nm divider chain

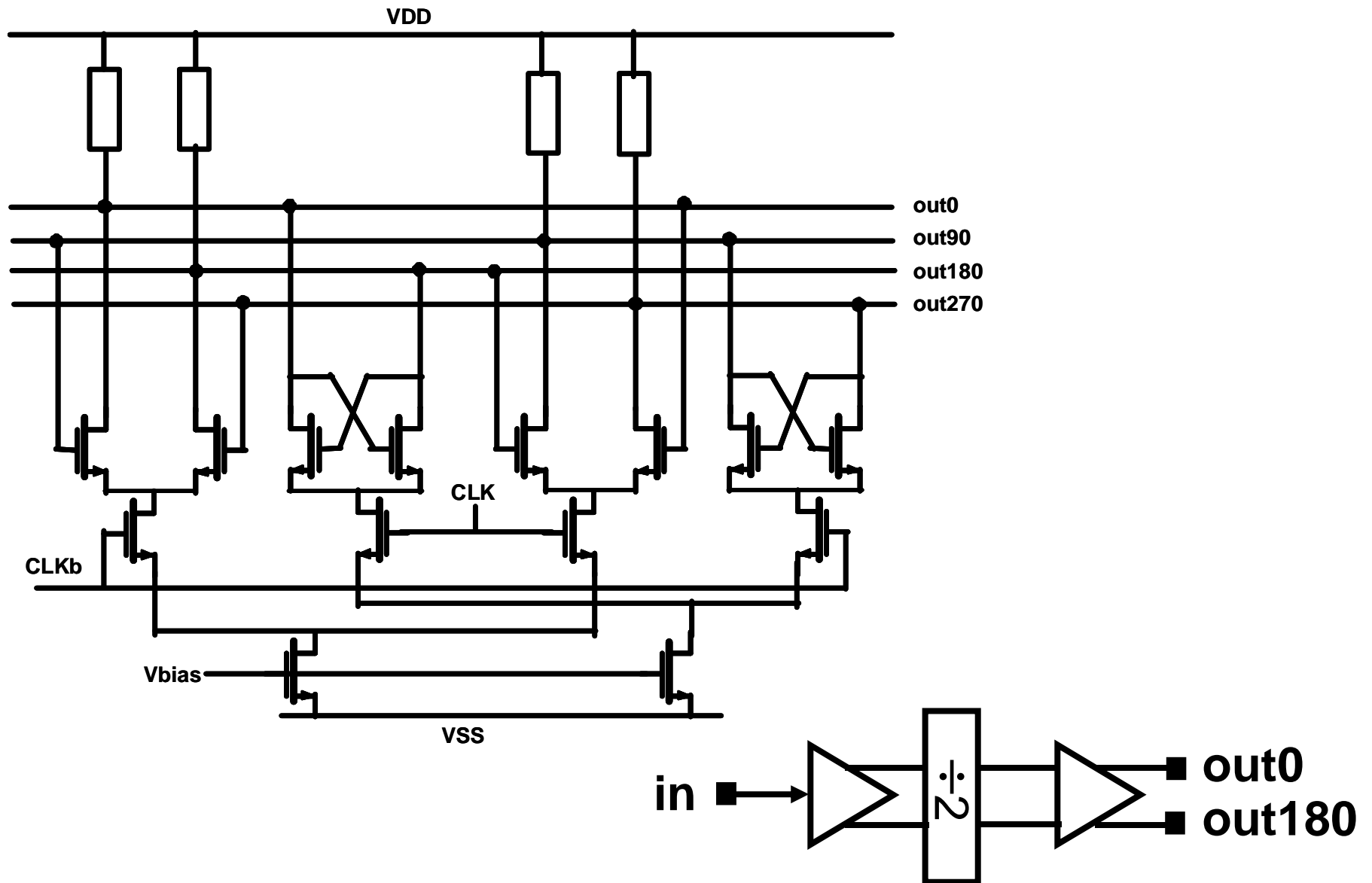


divider measurements

 


divider measurements

| CMOS | 65nm | 45nm |
|-----------------|--------|-------|
| Self resonance | 14GHz | 18GHz |
| Max input freq. | 18GHz | 21GHz |
| Pin | -14dBm | -9dBm |
| Pdiss | 18mW | 24mW |

UWB transceiver in 65nm

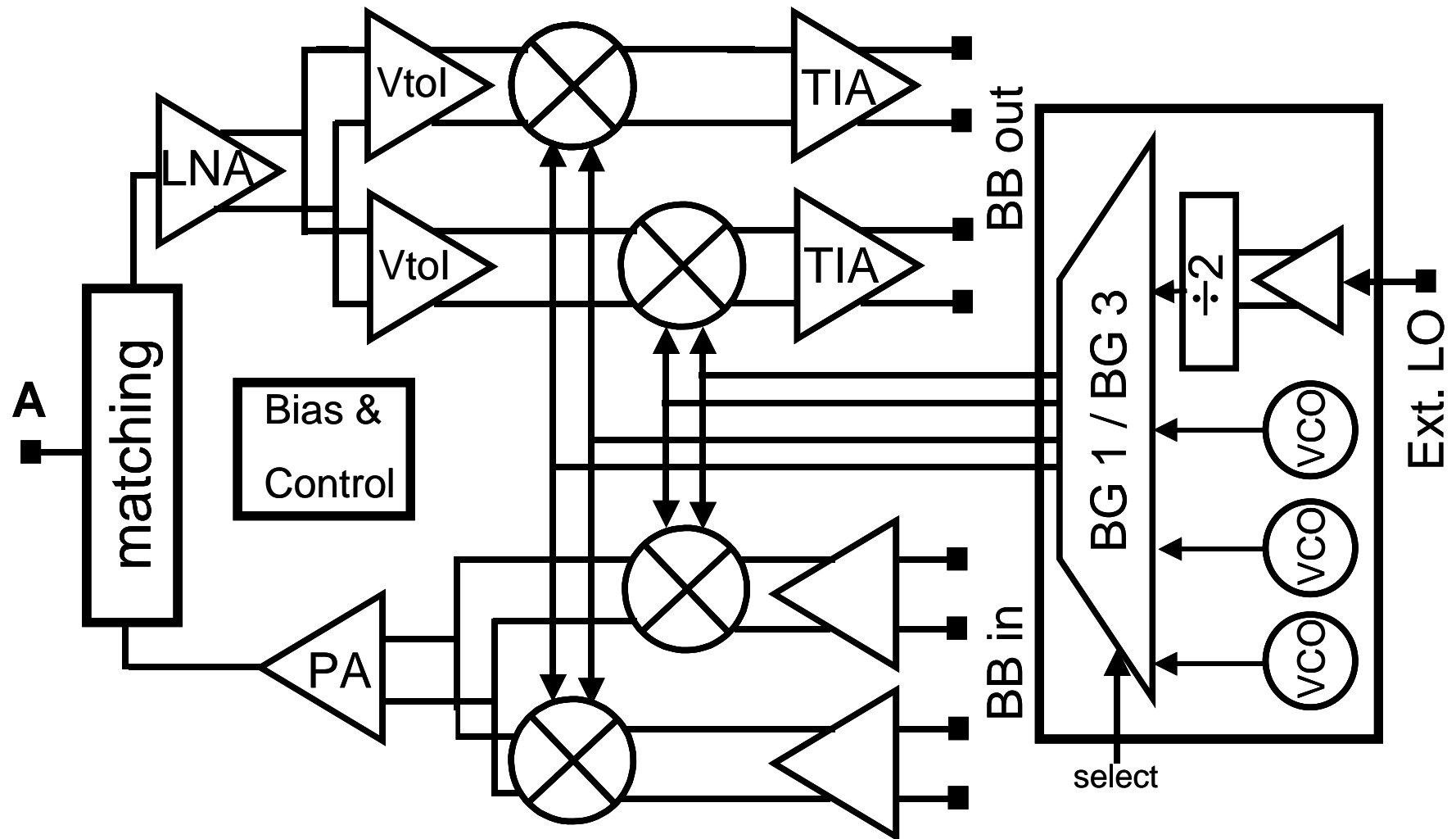


UWB transceiver in 65nm

 


1mm

| Parameter | Value | Comment |
|--------------------|-------------------------|---|
| Rx noise figure | 5.0 / 5.5 dB | $f_{in} = 4 \text{ GHz} / 7 \text{ GHz}$ |
| Rx Gain | 20 dB | Voltage gain, RF input to IF-output |
| Rx IIP2 | +25 dBm | Two-tone: $f_{in1} = 2.4 \text{ GHz}$, $f_{in2} = 5.2 \text{ GHz}$ |
| Rx IIP3 | +6 dBm | Two-tone: $f_{in1} = 1.8 \text{ GHz}$, $f_{in2} = 2.4 \text{ GHz}$ |
| Tx gain | +52 dB | IF-input to mixer output, w/o PA |
| Tx output EVM | 4 % | At mixer output, w/o PA |
| Tx output flatness | < 2 dB | At mixer output, 3.2 -- 7.7 GHz |
| Dissipation @ 1.2V | 52 mW 48 mW 63 mW | Receiver Transmitter LO generation |


UWB transceiver in 65nm

 


UWB transceiver in 65nm

 


UWB receiver in 45nm

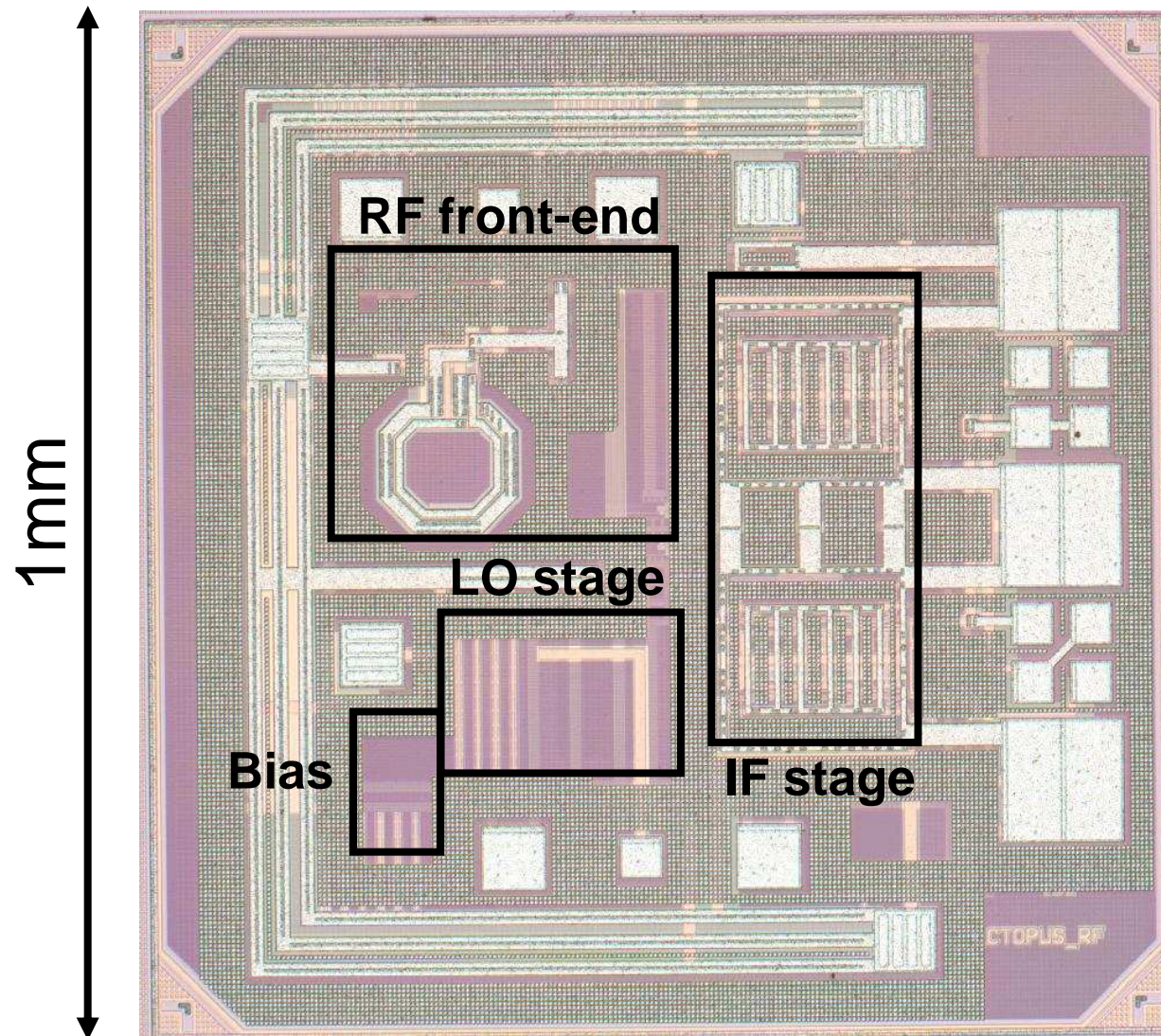

UWB receiver in 45nm

 

Comparison of 65nm-45nm RX

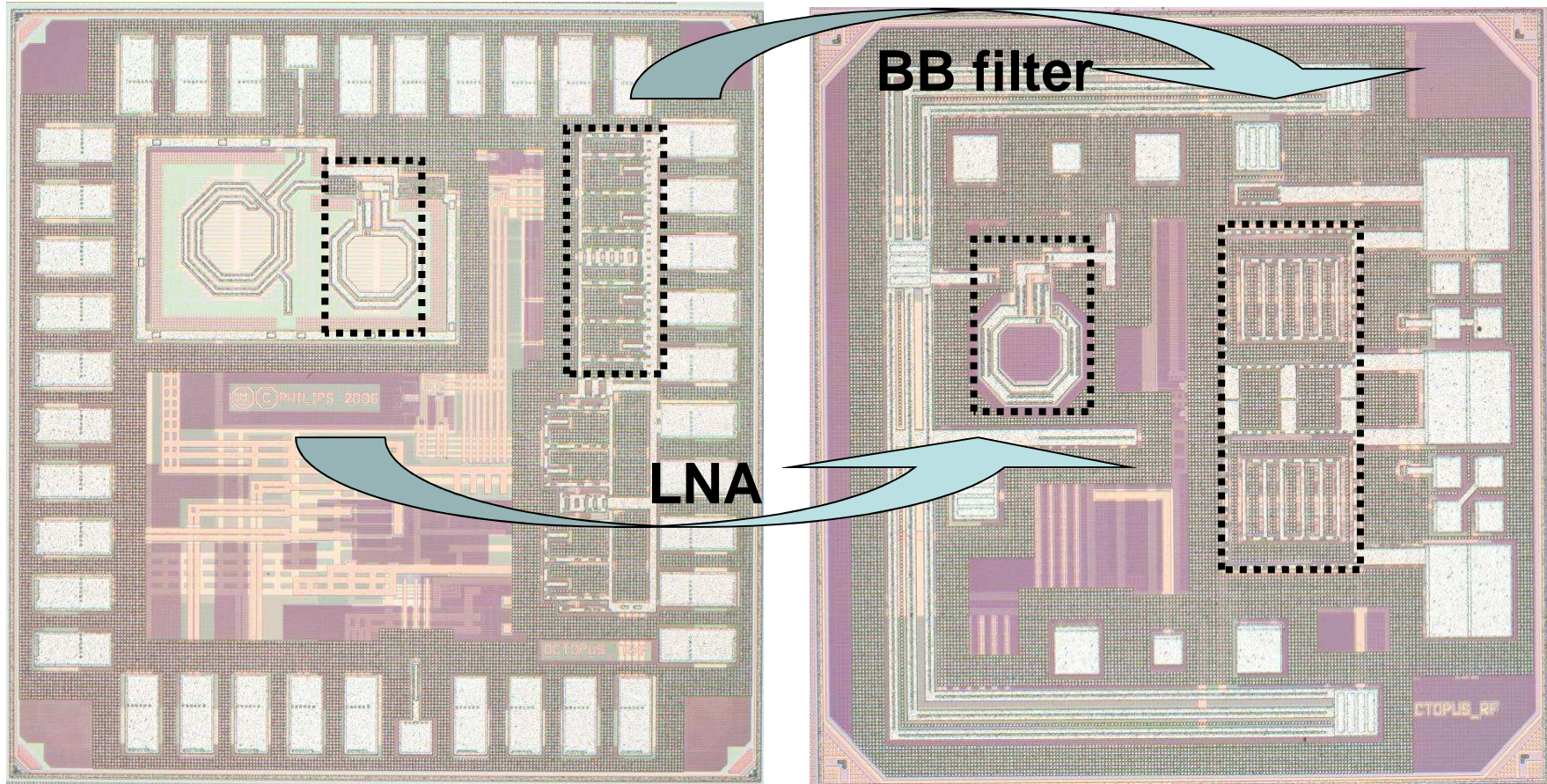

65nm LP CMOS

45nm LP CMOS

Dies on scale: analog does not necessarily scale!

Comparison of 65nm-45nm RX

| Rx performance | 65nm | 45nm |
|-----------------------|-------------|-------------|
| Gain [dB] | 20 | 14 |
| 3-dB BW [GHz] | 7 | 10 |
| NF [dB] | 5.5 | 7 |
| iIP3 [dB] | +5 | 0 |
| iIP2 [dB] | +25 | +20 |
| Pdiss [mW] | 52 | 90 |

Where do we stand nowadays?

- Wide Band CMOS design is possible
 - Convergence towards a receiver comprising wide band LNA, passive mixers and BB filtering
 - Additional tricks added to cope with interference are still needed
- Impressive f_T of naked device due to scaling does not tell the complete story
 - Layout influence becomes more and more dominant

Thank you for your attention!

Hope you learned something