
Spur-Free Switching Power Converters for Analog and RF Loads

Solid State Circuits Society Visit, Fort Collins Chapter, March 8, 2013

Ayman Fayed, Assistant Professor
Director, Power Management Research Lab
Electrical & Computer Engineering, Iowa State University



Outline

- ◆ Personal Background & Research Group
- ◆ Power Management → The story
- ◆ The Switching Noise Problem
 - Types of power supplies
 - Spectral characteristics of switching noise
 - Impact on noise-sensitive Analog/RF Loads
- ◆ Switching Noise Mitigation Techniques
 - Time-domain Approaches
 - Frequency-domain Approaches
- ◆ Constant Cycle Frequency Hopping for Spur-Free Operation
- ◆ Power Management and Formal Education → If time permits

Personal Background & Research Group

- ◆ M.Sc. and Ph.D. from The Ohio State University, Columbus, Ohio
- ◆ Nine years at multiple business units at TI → High-speed wire-line transceivers, ADCs for RF CODECs, PM for multi RF cores SoCs
- ◆ Assistant Professor and Director of the Power Management Research Lab (PMRL) at the Dept. of Electrical & Computer Engineering at Iowa State University since Jan. of 2009
- ◆ 6 Ph.D. Students working on projects sponsored by NSF, RCI, State of Iowa, TI, and National Semiconductors
- ◆ Alumni at TI and Broadcom

Research Interests

◆ Areas of expertise & Research Interests

- Embedded Power management circuit and system design for Mixed-signal/RF SoCs and multi-core processors
- Supply Modulators for RF Polar PAs
- Class-D Audio Power Amplifiers
- Energy Harvesting for power-restricted systems
- Particular emphasis on fully integrated implementations in nanometer CMOS and GaN technologies

Power Management: What is it?

- ◆ A System Designer → Task oriented
- ◆ A Digital Designer → Dynamic Voltage Scaling
- ◆ A Chip Architect → Power Delivery
- ◆ Analog/PM Designer → It is not only about “managing” how power is being used, conserved, or distributed

Power Conversion, Regulation, and Monitoring

Reemergence of Power Management

◆ Gaining a front seat role in VLSI systems today

➤ Isn't it just the traditional good old power electronics!! What's new?

◆ The battery life challenge

➤ Slow pace battery technology development

➤ Focus has been on power consumption reduction → technology scaling, low voltage/power design → diminishing returns?


➤ The efficiency of how power is converted and delivered from the battery to the system must be revisited for any further improvement

Reemergence of Power Management

◆ Cost & Size challenge → The SoC era

- Analog/Digital/RF is successfully fully integrated with minimal external components → Cost-effective & Compact
- Large passive components → Expensive, Bulky, not integrate-able
- Many package pins are needed

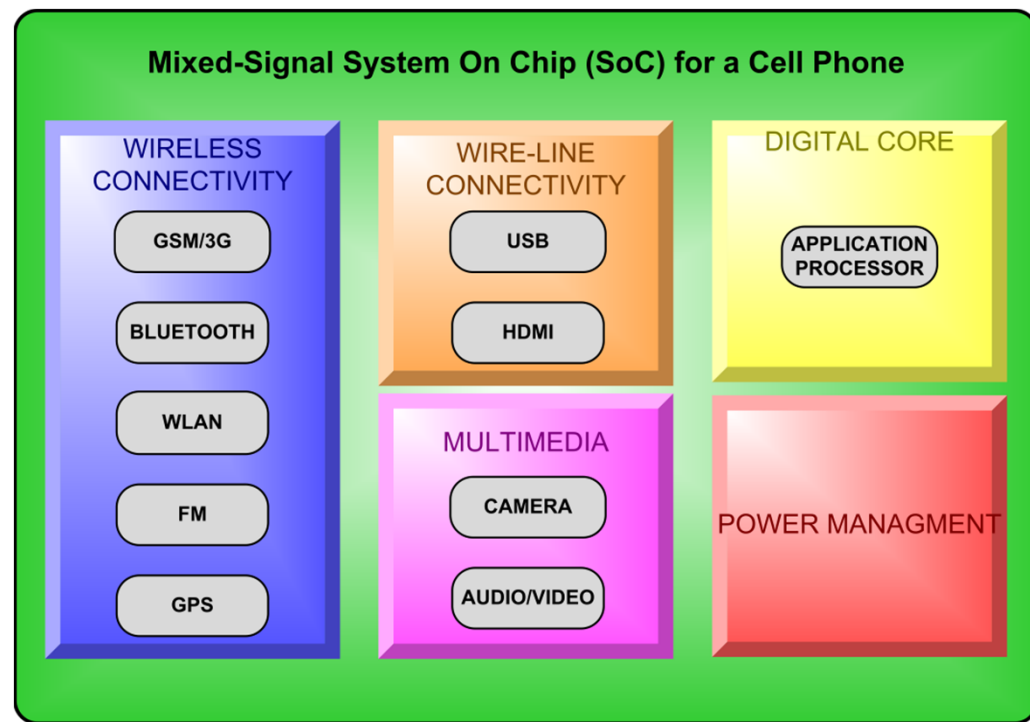PM is becoming a real cost, size, and performance bottleneck



Reemergence of Power Management



◆ Design & Performance challenge

- Adaptability to different power sources
- Large number of independent on-chip power domains → in order to further reduce power
- With massive integration, there is not enough package pins to deliver all required power supply domains externally
- Thermal efficiency
- Efficiency often contradicts noise → Analog/RF loads are victims

Outline

- ◆ Personal Background & Research Group
- ◆ Power Management → The story
- ◆ The Switching Noise Problem
 - Types of power supplies
 - Spectral characteristics of switching noise
 - Impact on noise-sensitive Analog/RF Loads
- ◆ Switching Noise Mitigation Techniques
 - Time-domain Approaches
 - Frequency-domain Approaches
- ◆ Constant Cycle Frequency Hopping for Spur-Free Operation
- ◆ Power Management and Formal Education → If time permits

Power Supplies: Basic Circuits

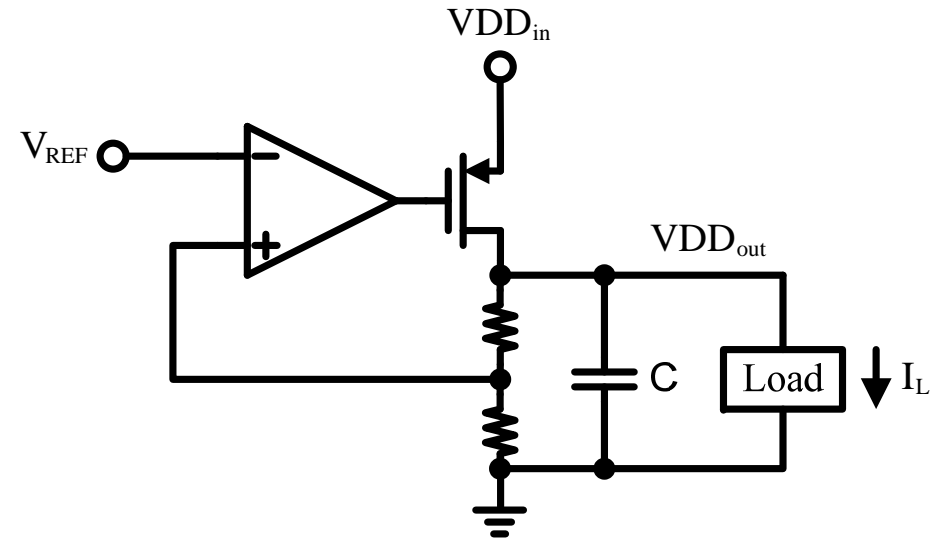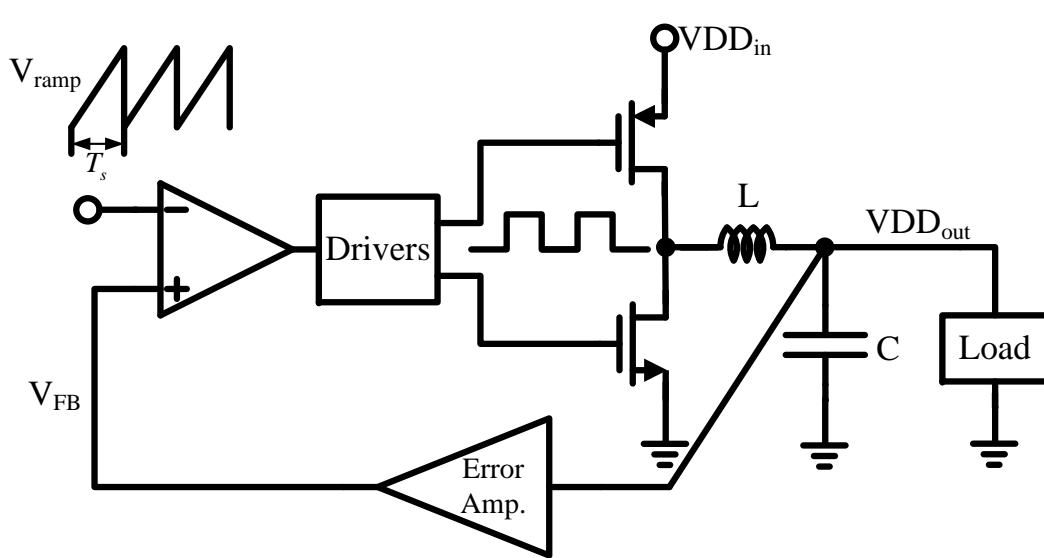

◆ Switching Regulators



- Step up, down or both
- Efficient, noisy, large cost/size overhead

◆ Linear Regulators

- Only step-down
- Inefficient, low noise, relatively small cost/size overhead


Power Supplies: Basic Circuits

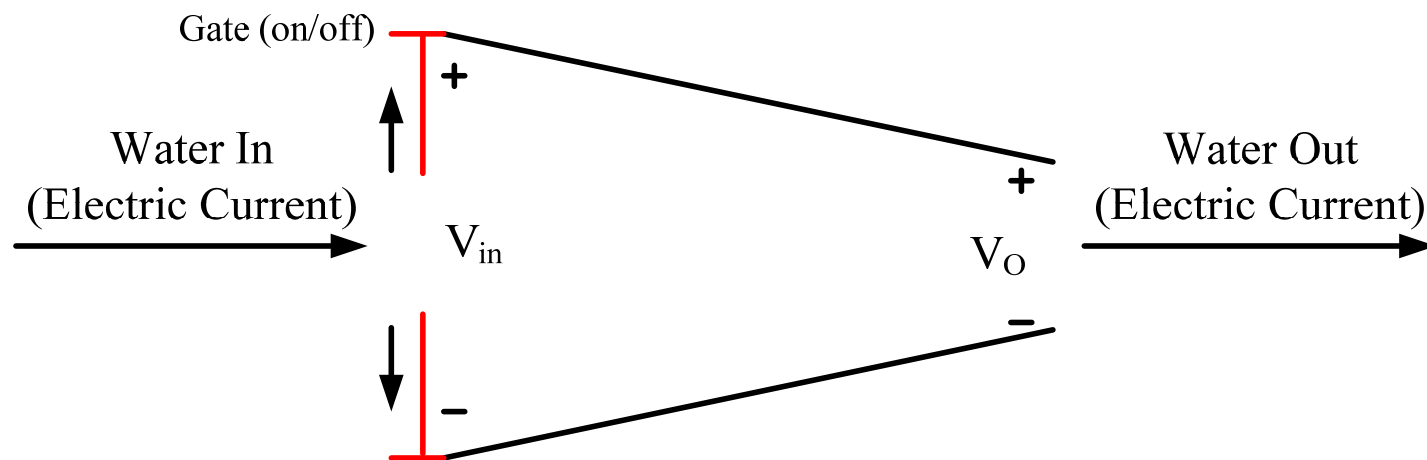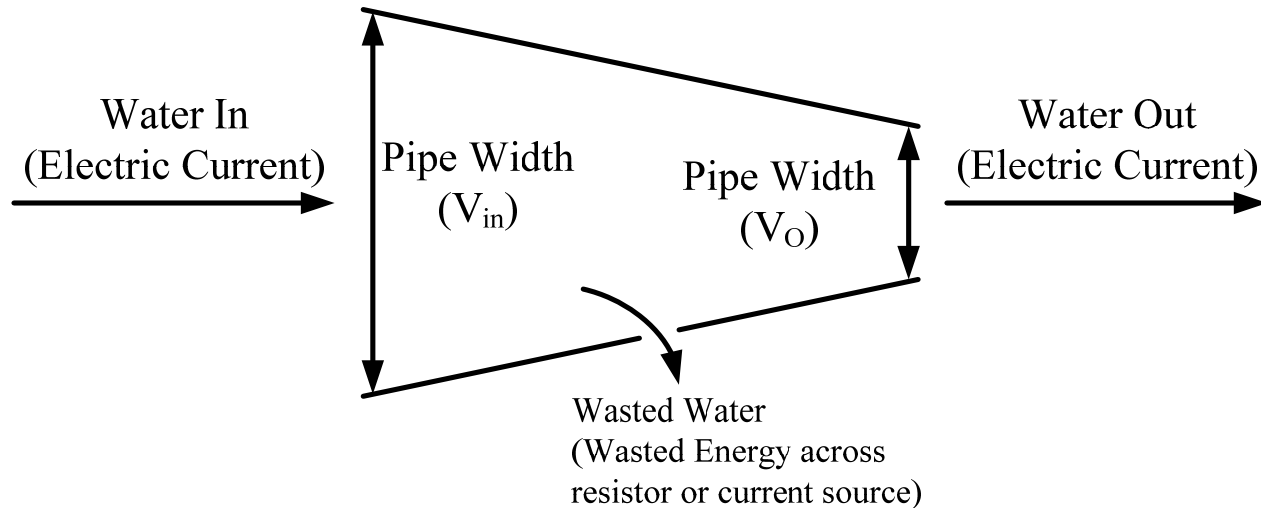◆ From efficiency and noise point of view








Linear Power Supplies: Efficiency

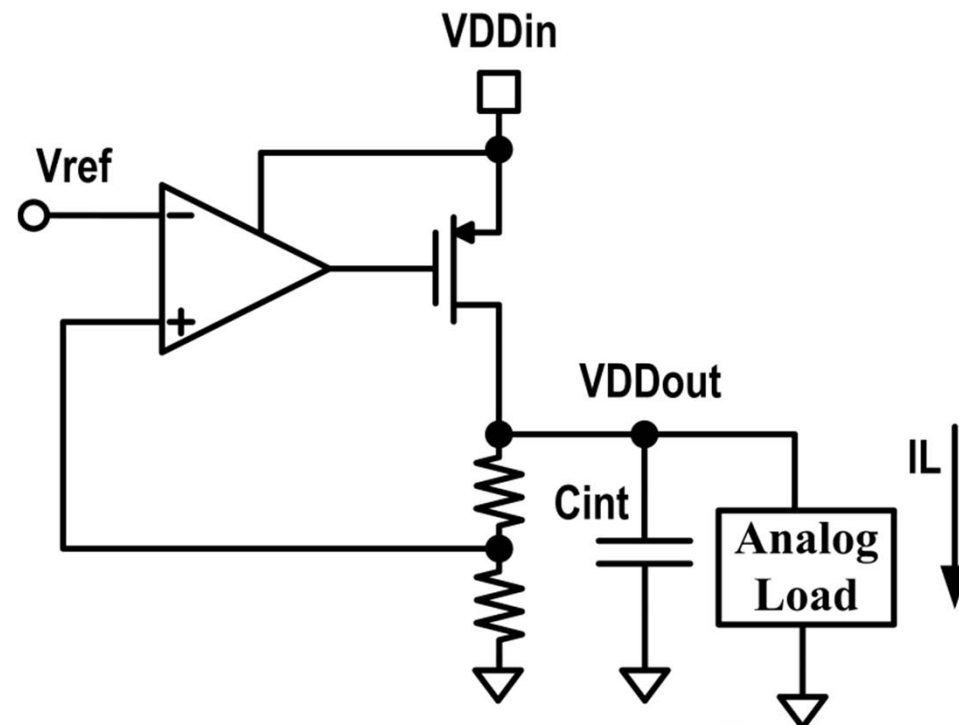- ◆ Voltage scaling is often needed to improve the efficiency of many analog/RF circuits → Supply-switched PAs and polar modulation
- ◆ Linear regulators render voltage scaling ineffective for Analog/RF loads




Switching Power Supplies: Noise

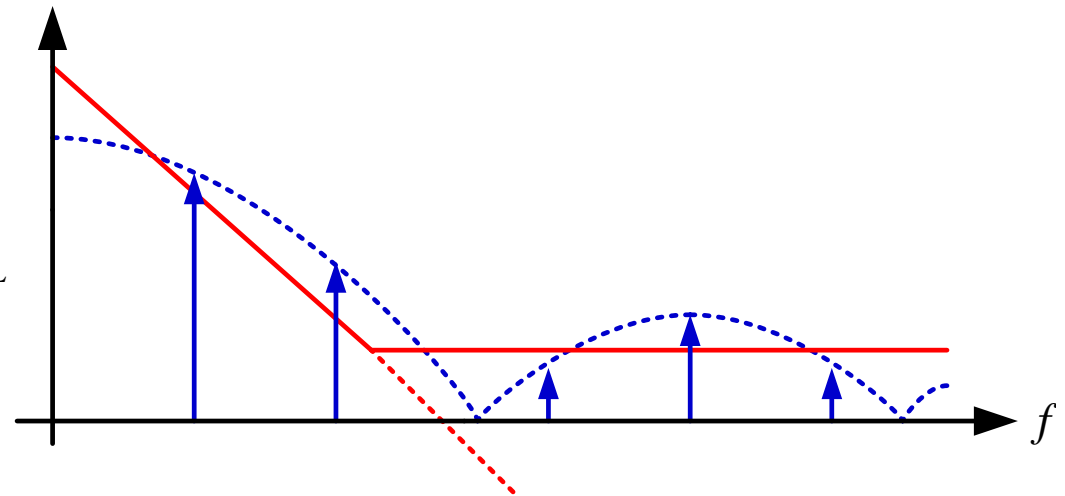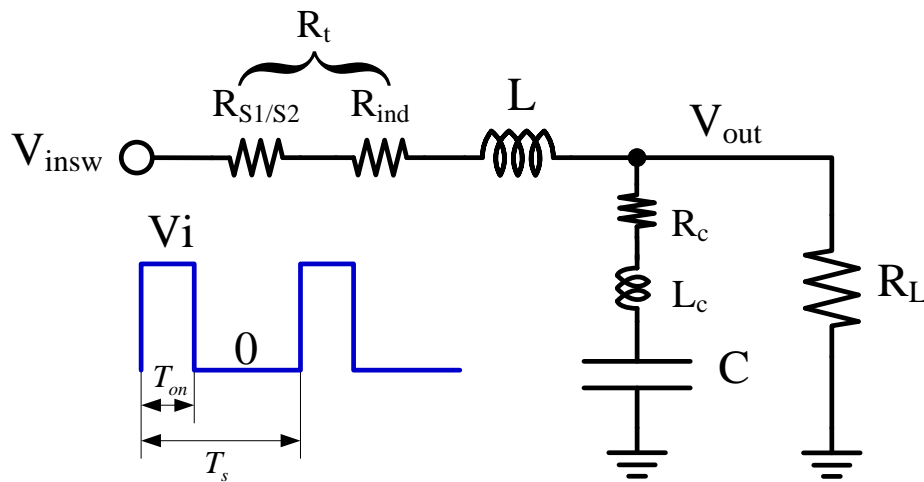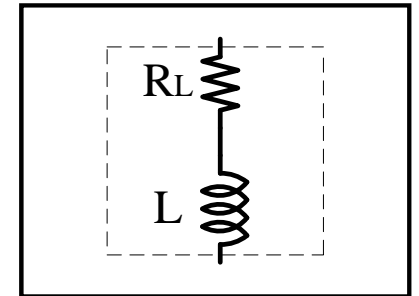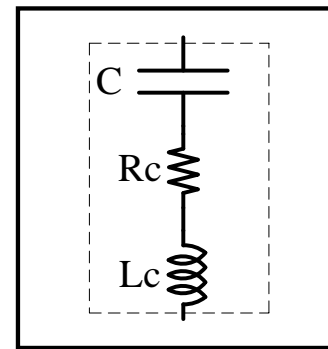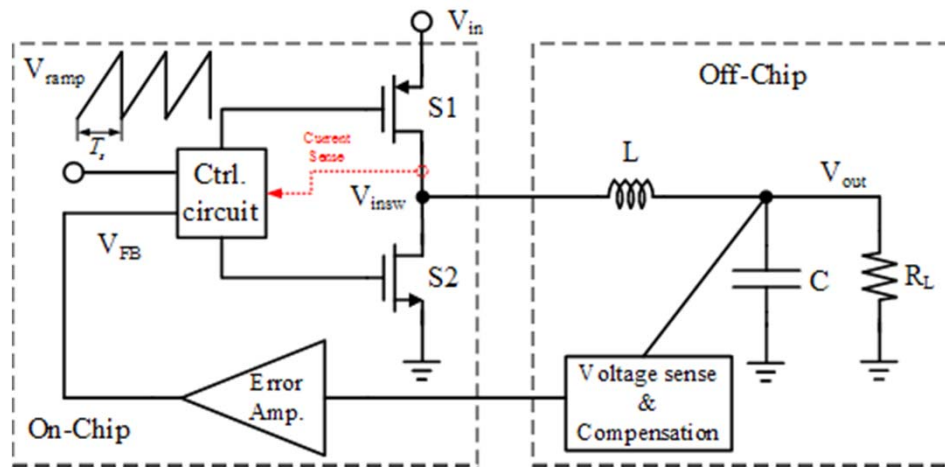
- ◆ The switching node is supposed to be filtered out by a sharp second-order low-pass function



Switching Noise: Frequency-Domain

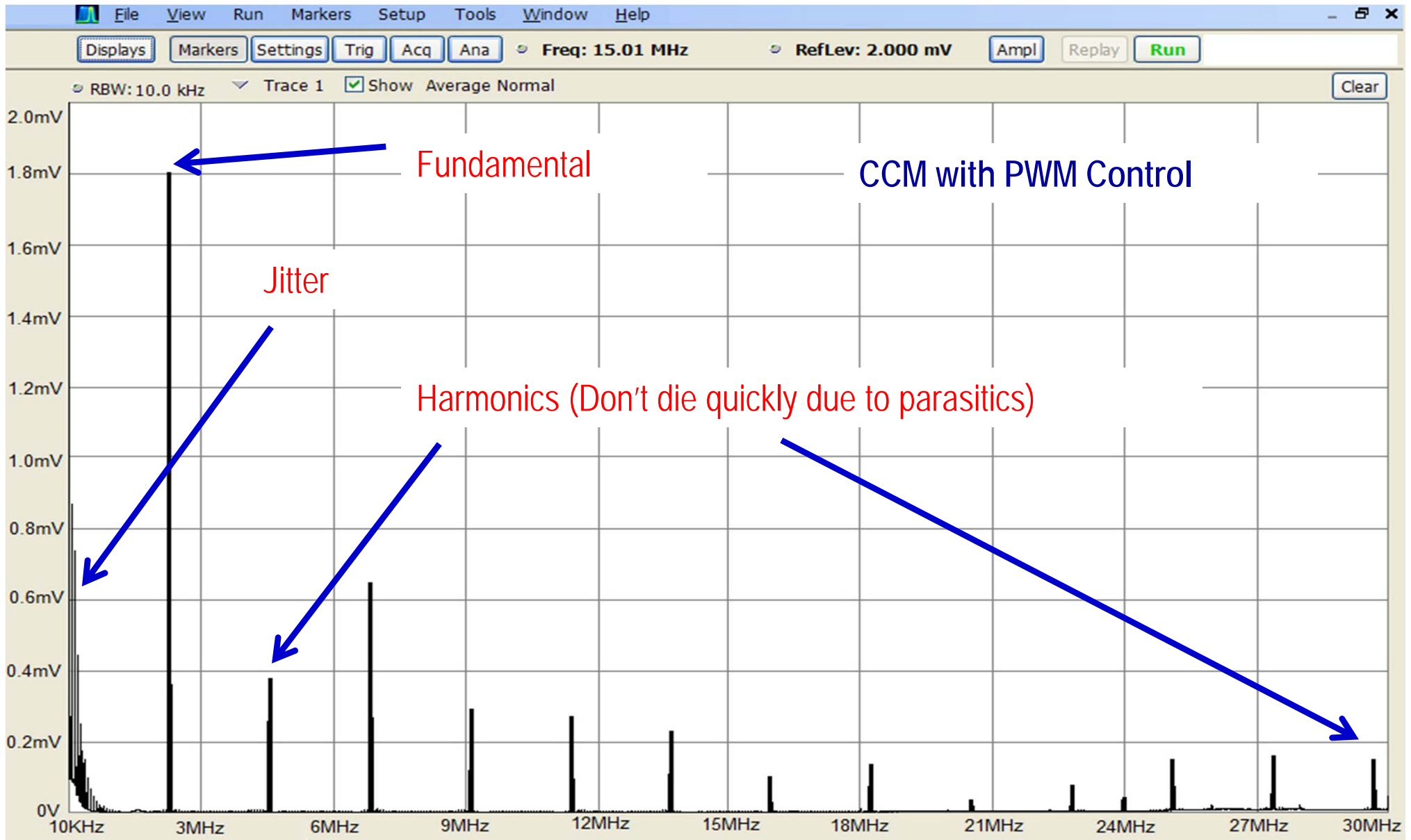


Switching Noise: Frequency-Domain

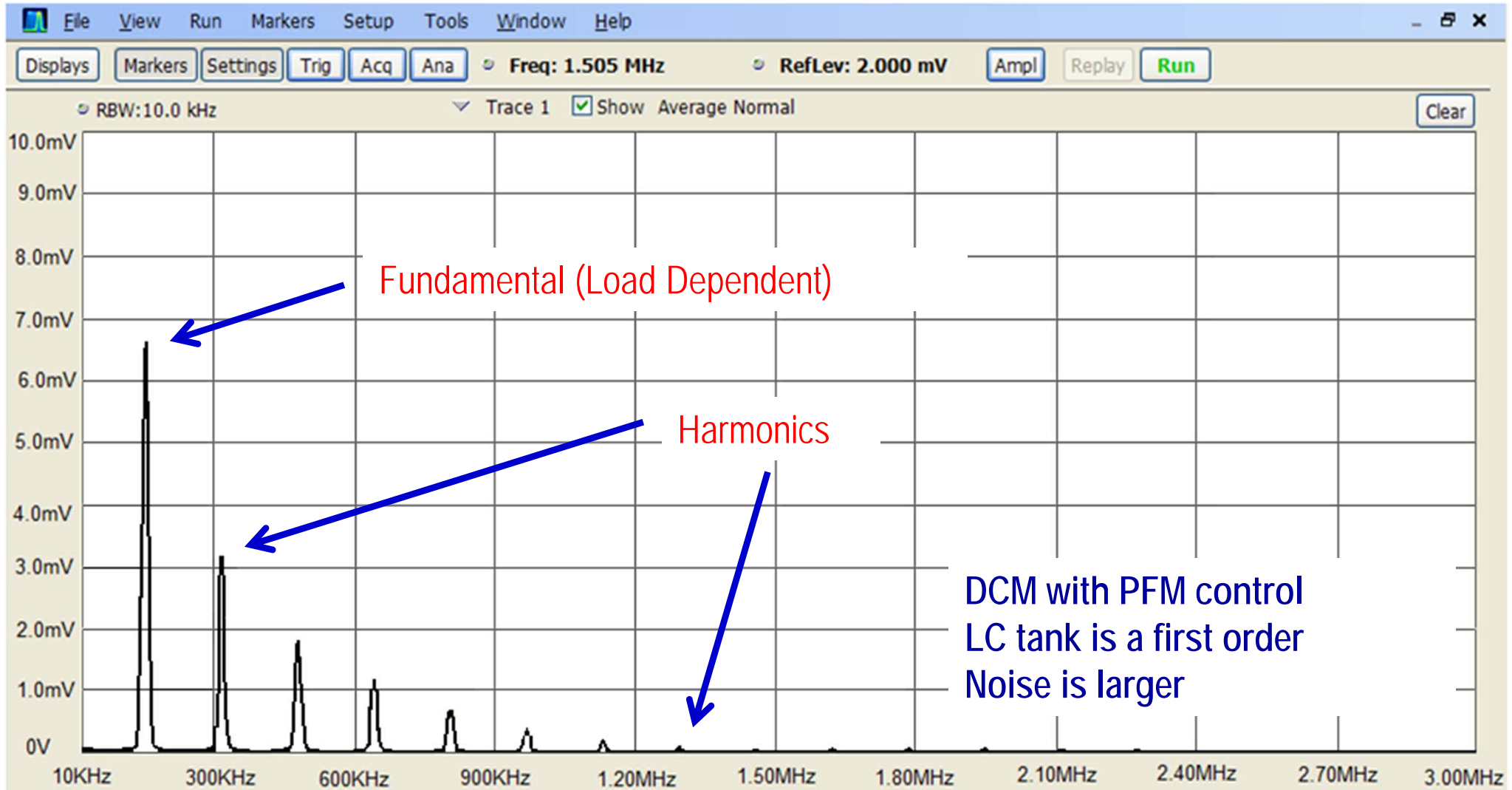


Impact of Switching Noise: Direct Powering

◆ A GSM PA example

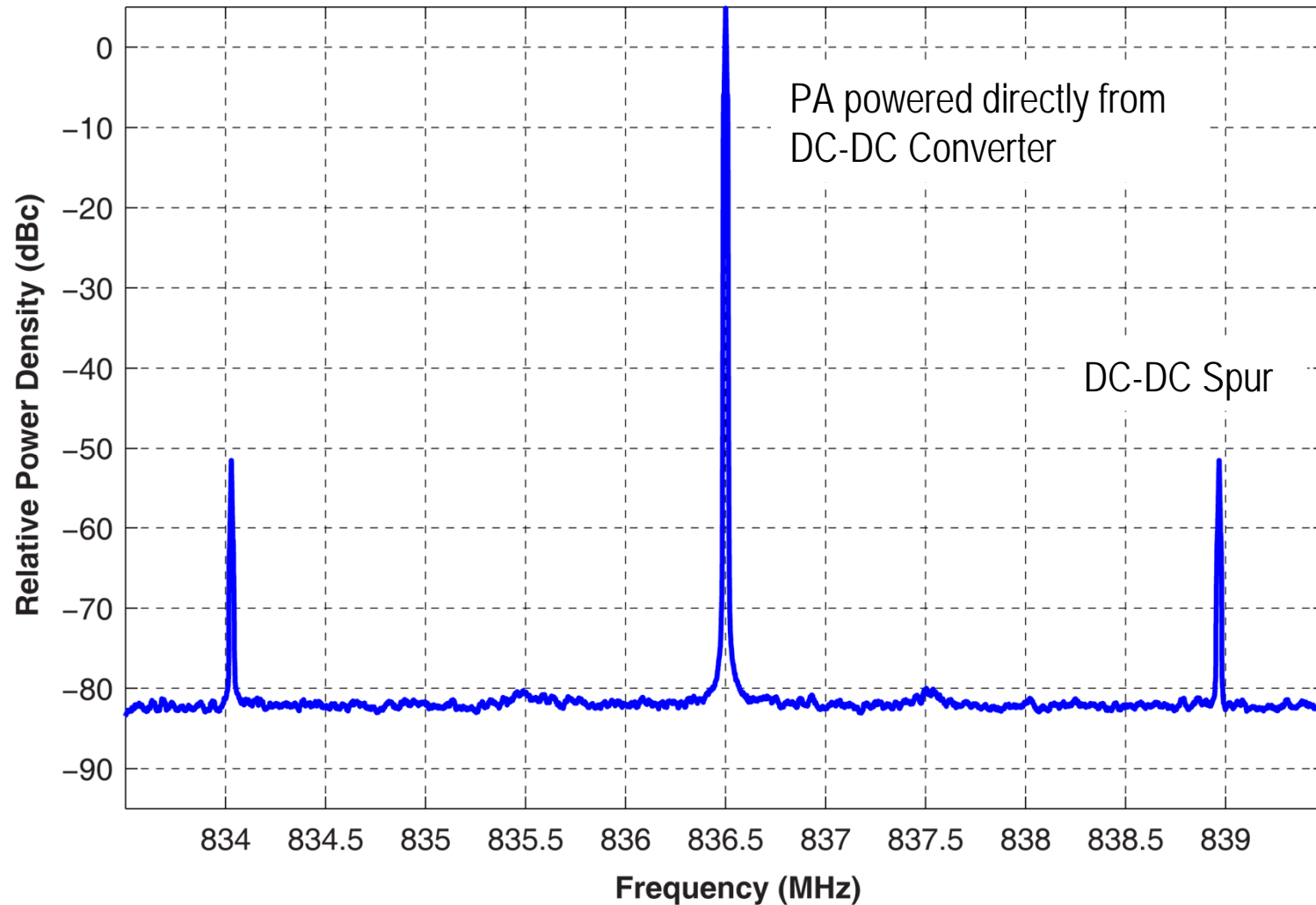


Impact of Switching Noise: Power Rails Sharing

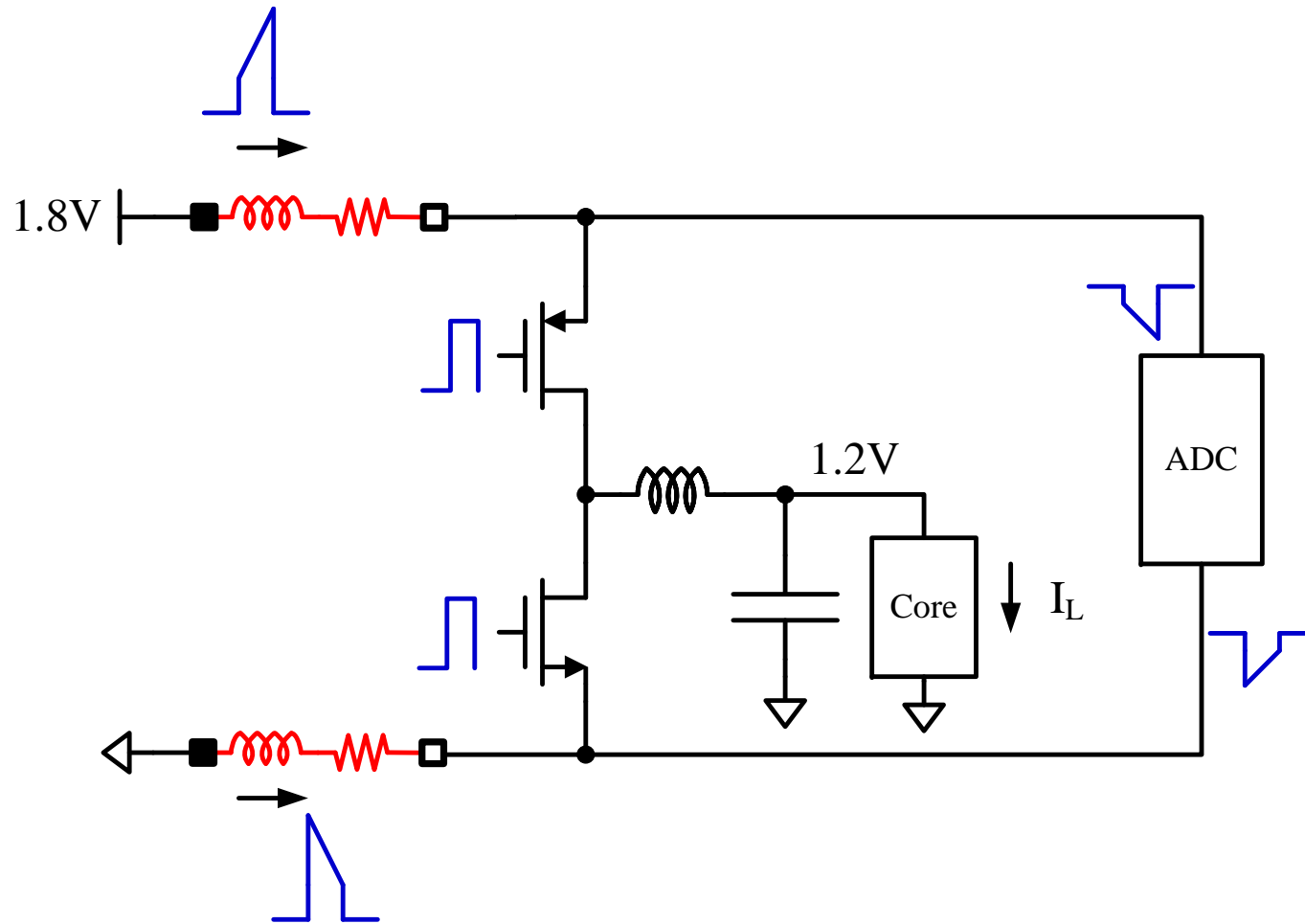- ◆ Problematic in pin-limited applications → Low-power DSPs




Impact of Switching Noise: Substrate Sharing

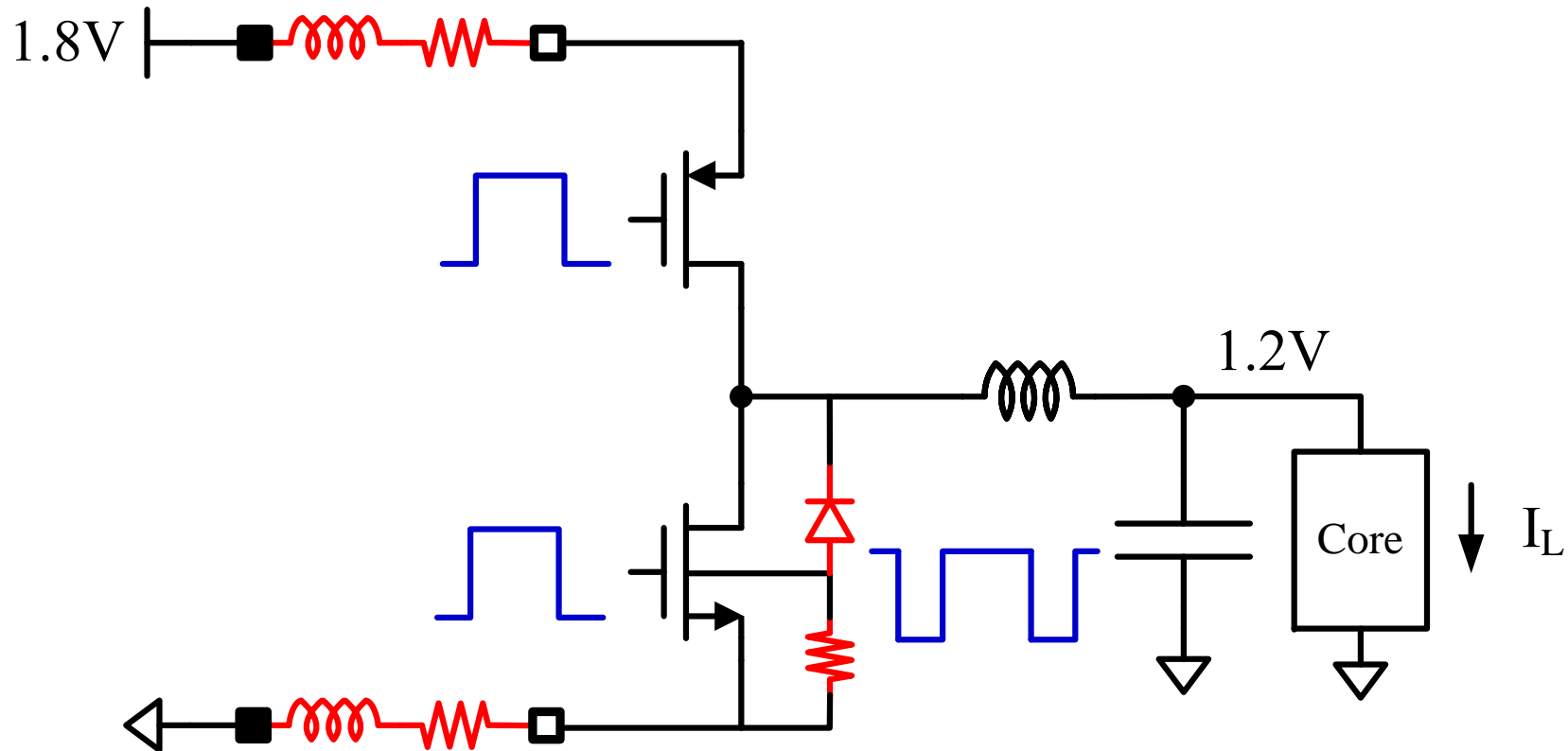- ◆ Quite problematic when integrated in an SoC



Impact of Switching Noise: EMI & Reliability

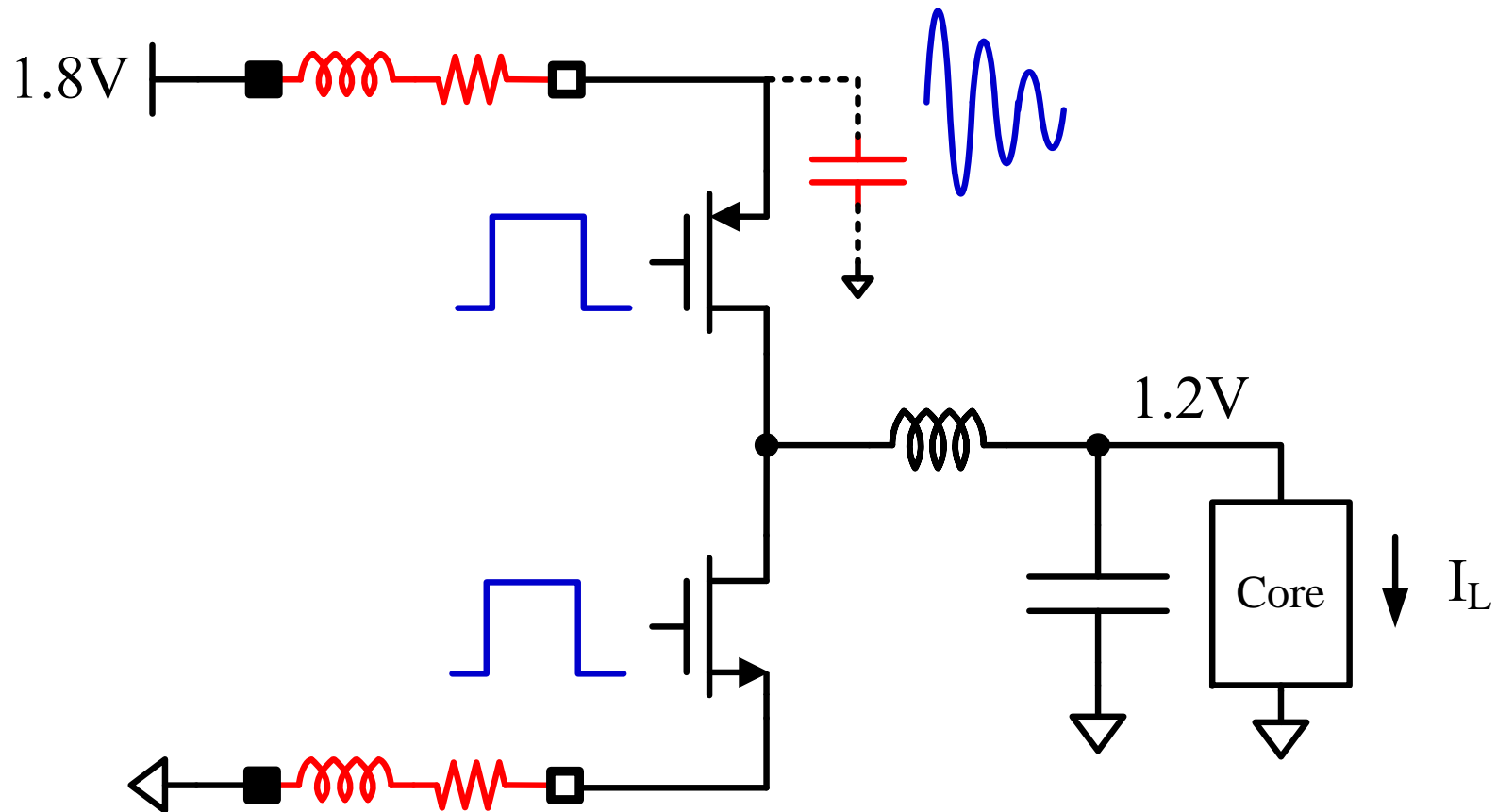- ◆ EMI is an issue and also device reliability in low-voltage CMOS



Accommodating Switching Noise

- ◆ Switching noise is spurious → It is arguable whether this is better or worse than random
- ◆ Spurious → Self/Cross mixing, Interference, Folding
- ◆ Random → SNR degradation
- ◆ But we know where the spurs are, isn't that good?
 - Not if they continue to exist with a significant magnitude up to very high frequencies
 - Location may be known with PWM control, but not PFM → Often need to tolerate both


Outline

- ◆ Personal Background & Research Group
- ◆ Power Management → The story
- ◆ The Switching Noise Problem
 - Types of power supplies
 - Spectral characteristics of switching noise
 - Impact on noise-sensitive Analog/RF Loads
- ◆ Switching Noise Mitigation Techniques
 - Time-domain Approaches
 - Frequency-domain Approaches
- ◆ Constant Cycle Frequency Hopping for Spur-Free Operation
- ◆ Power Management and Formal Education → If time permits



Switching Noise: Mitigation Techniques

- ◆ Brute force time-domain techniques versus smart frequency-domain techniques

- ◆ Efficiency
- ◆ Cost
- ◆ Performance

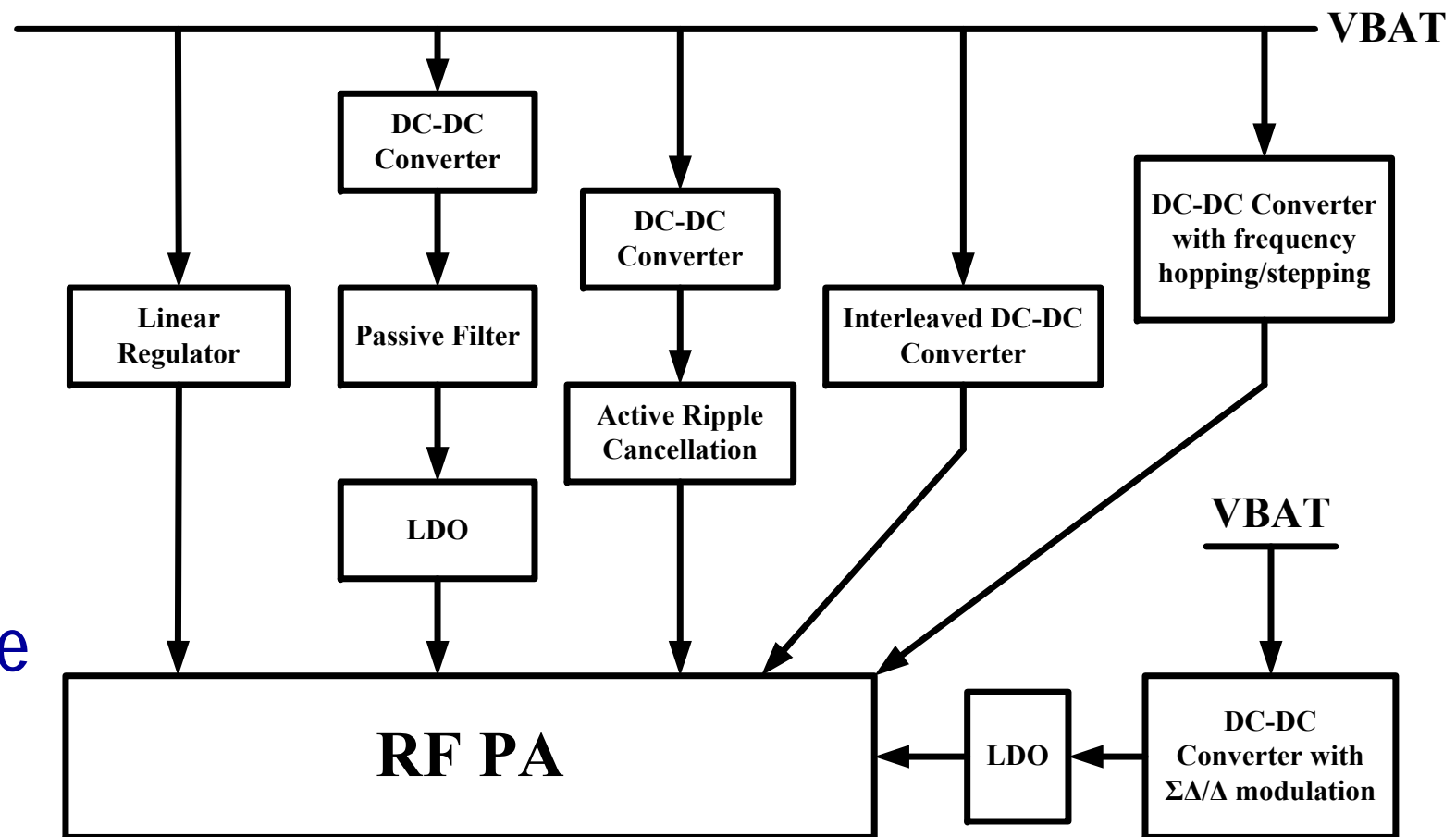


Do LDOs Really Help?

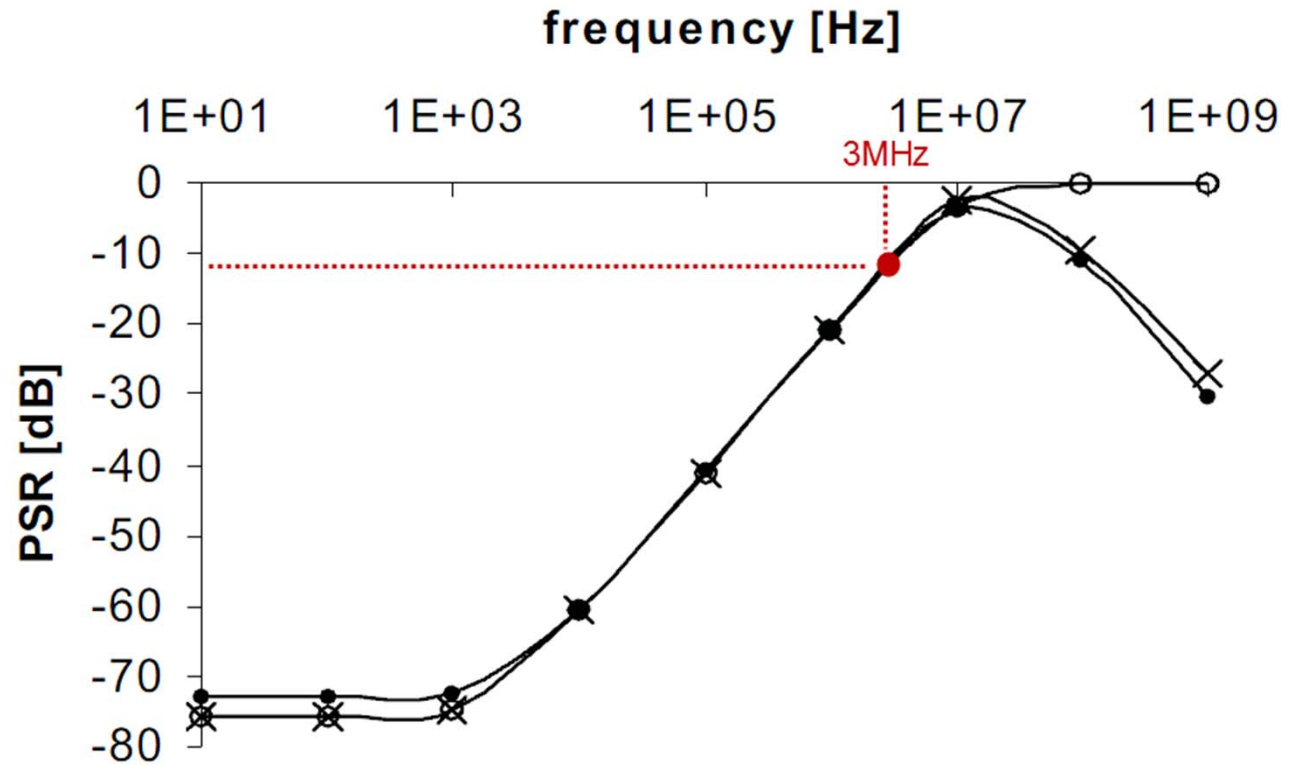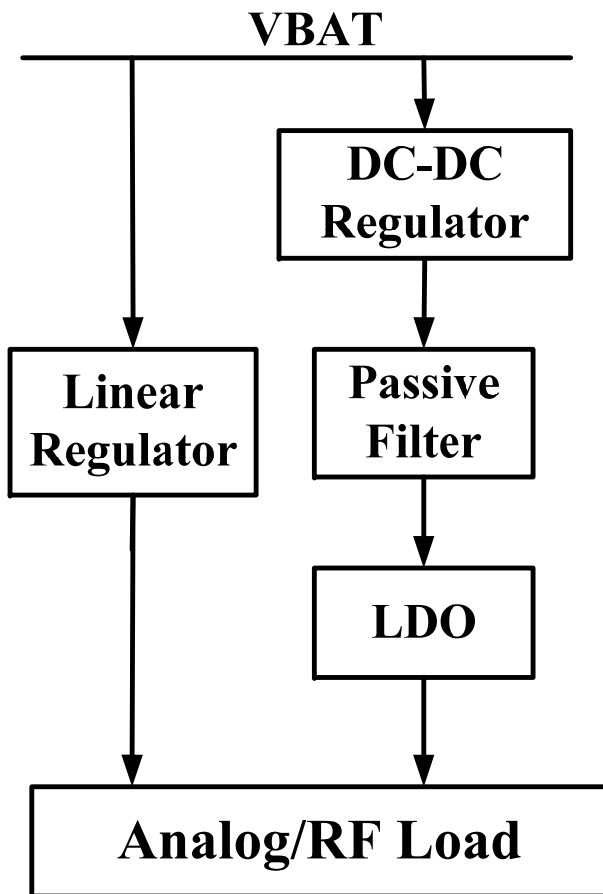

V. Gupta, G. A. Rincon-Mora, P. Raha, "Analysis and Design of Monolithic, High PSR, Linear Regulators for SoC Applications", IEEE International SOC Conference, 2004.


Brute Force: Time-Domain Approaches

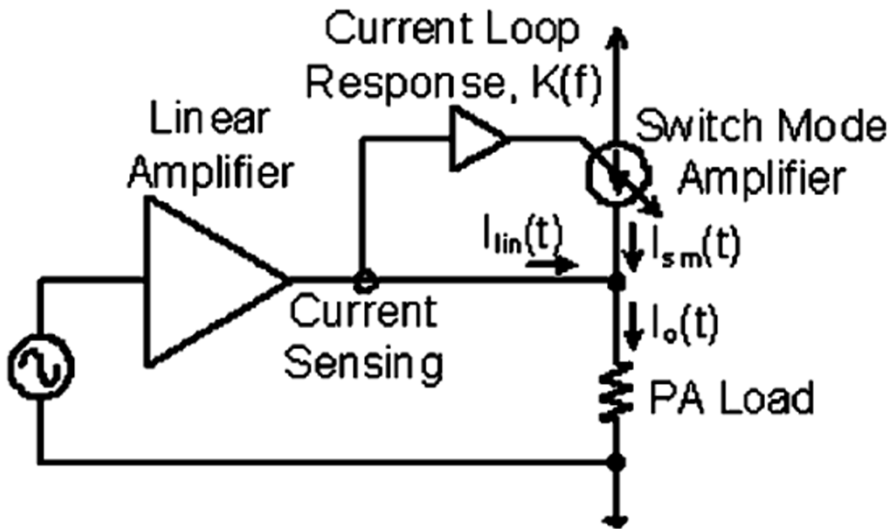

Wing-Yee Chu, Bertan Bakkaloglu, and Sayfe Kiaei, "A 10 MHz Bandwidth, 2 mV Ripple PA Regulator for CDMA Transmitters," *IEEE JSSC*, vol. 43, no. 12, pp. 2809-2819, Dec. 2008.


Active Ripple Cancellation

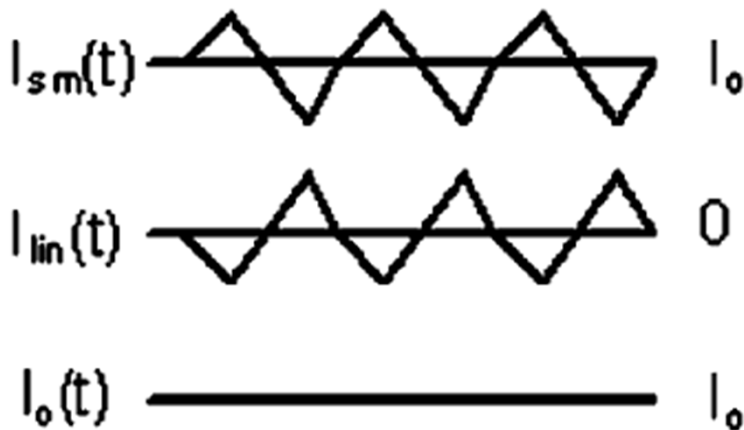- Cancel the voltage ripple by compensating for inductor current ripple
- A class AB Linear amplifier is needed → source and sink current
- Amplifier has to be as fast as the switching frequency of the switching regulator → Power consumption
- Sensing inductor current is not simple
- Can result is significant efficiency loss if the inductor used is not large specially at low load conditions




Brute Force: Time-Domain Approaches

Interleaved Regulators

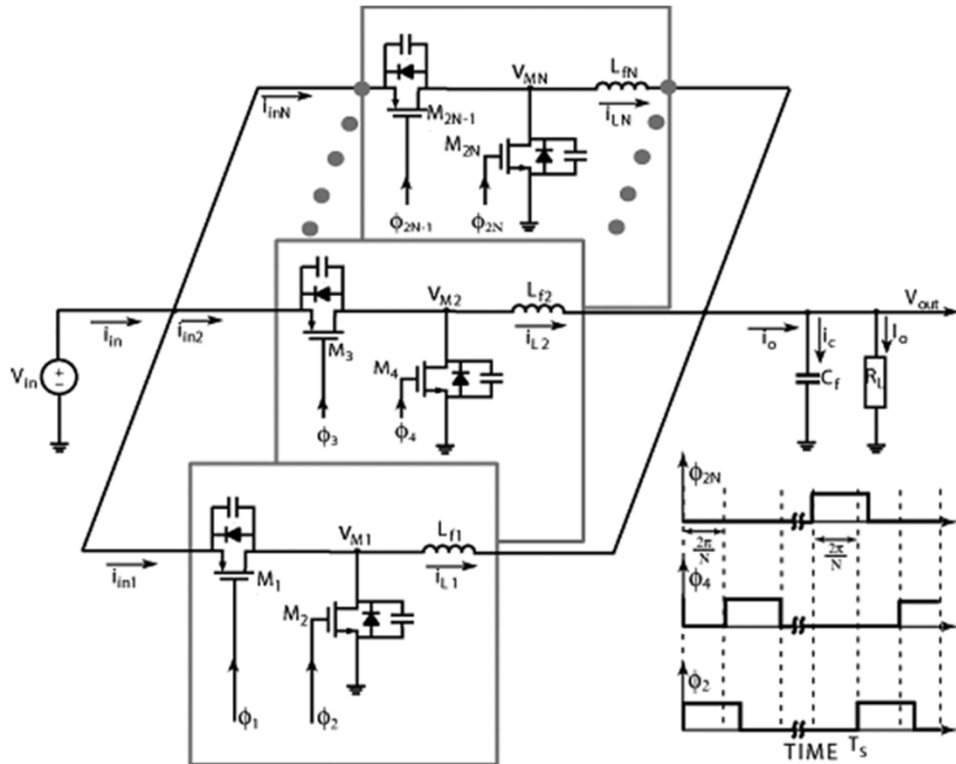

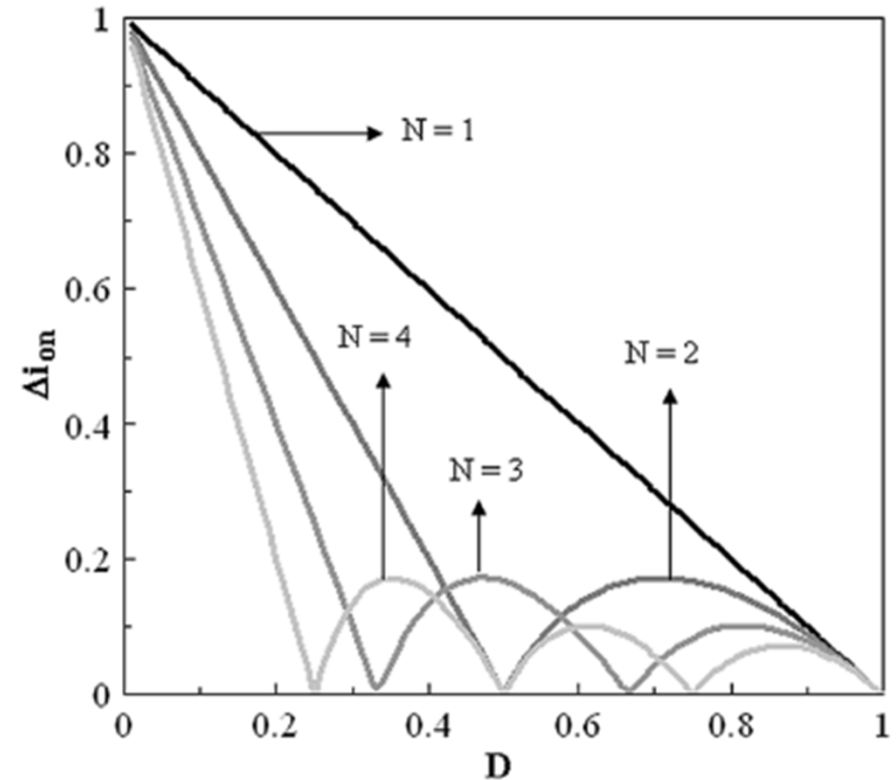Siamak Abedinpour, Bertan Bakkaloglu, and Sayfe Kiaei, "A Multistage Interleaved Synchronous Buck Converter With Integrated Output Filter in 0.18 μm SiGe Process," *IEEE Tran. on Power Electronics*, vol. 22, no. 6, pp. 2164-2175, Nov. 2007.





- Cancel the voltage ripple by switching multiple inductors with different switching phases to reduce overall current ripple
- Very expensive due to the inductors
- Complex to design due to accurate phase relation requirements

Spectrum Manipulation: Delta-Sigma


Steven K. Dunlap, and Terri S. Fiez, "A Noise-Shaped Switching Power Supply Using a Delta-Sigma Modulator," *IEEE TCAS-I*, vol. 51, no. 6, pp. 1051-1061, Jun. 2004.

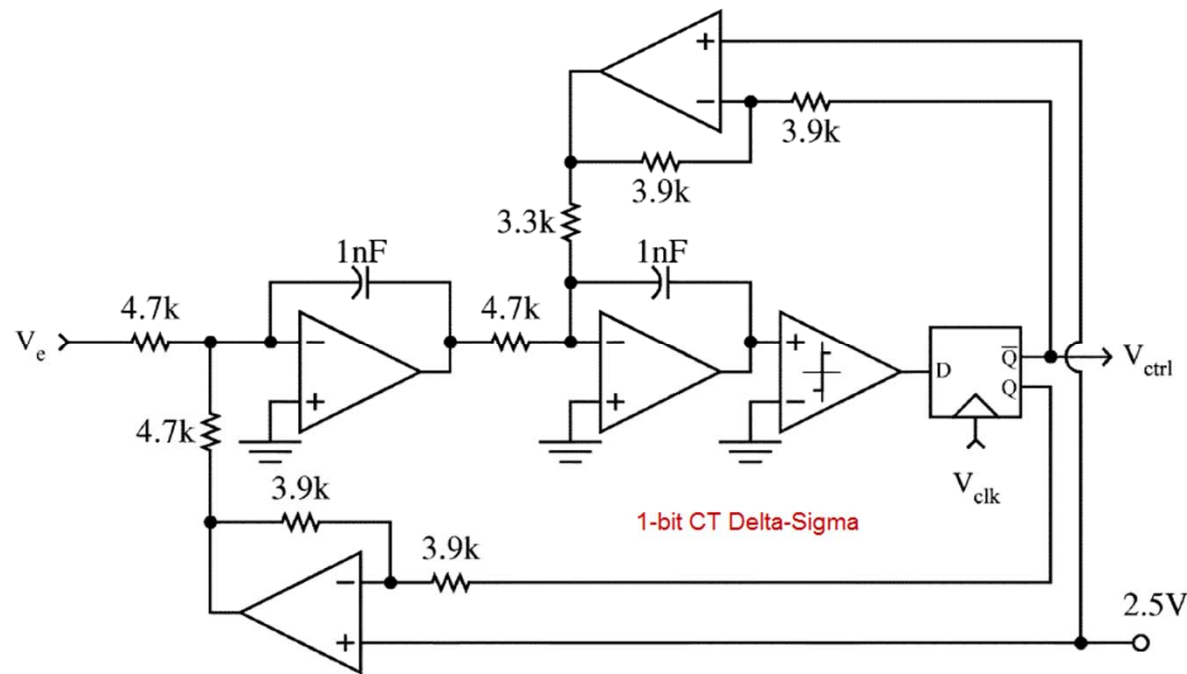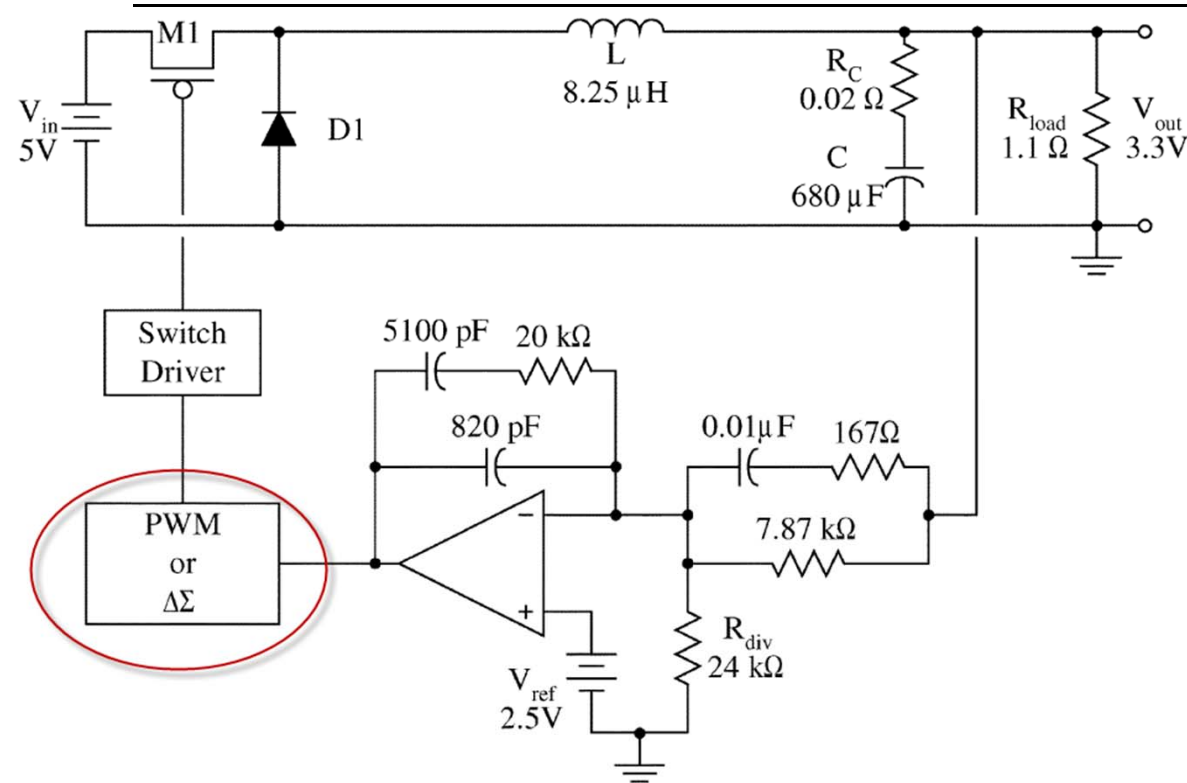➤ Replace PWM with a single-bit Delta-Sigma




Spectrum Manipulation: Delta-Sigma

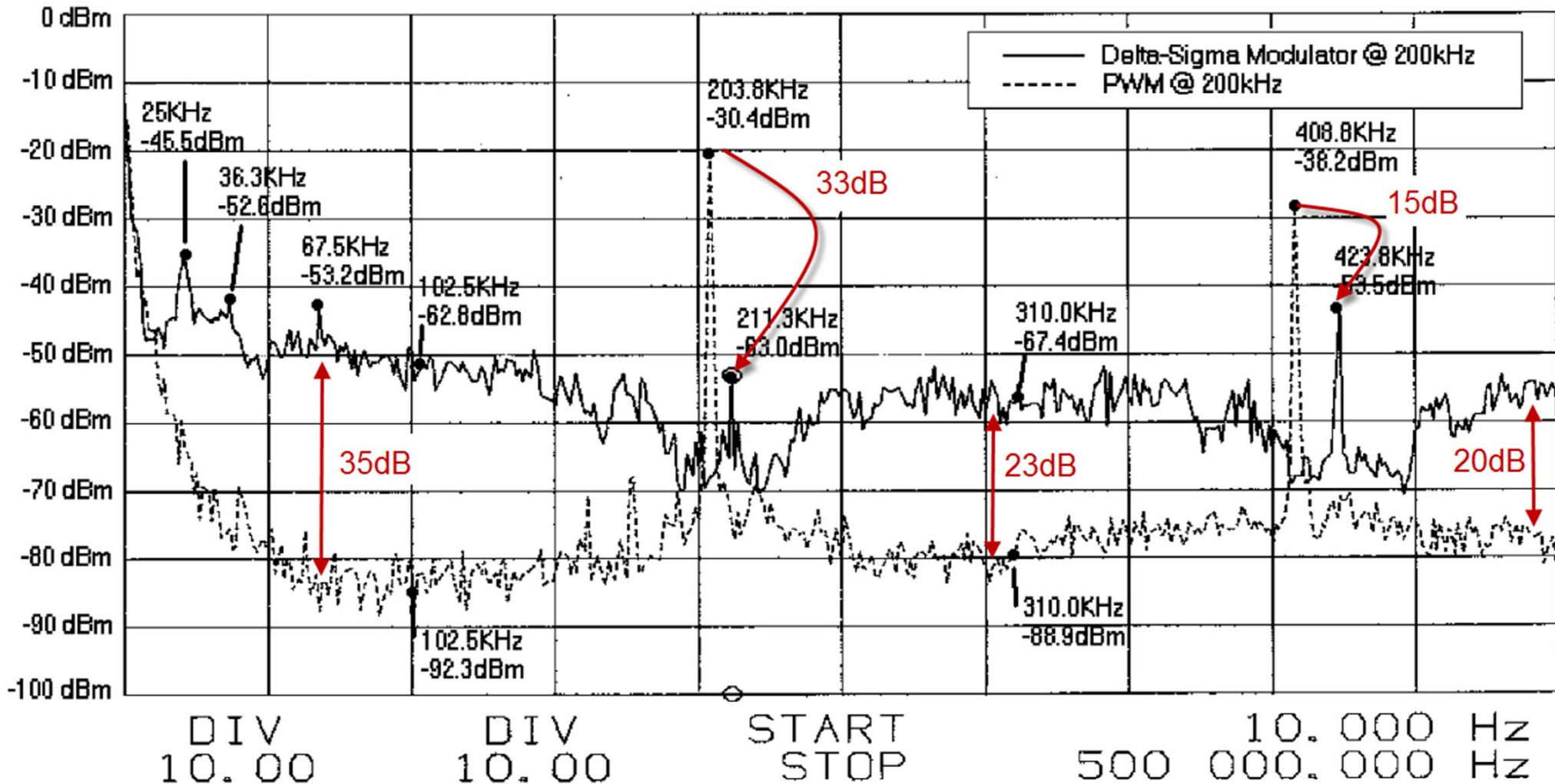
- Spurs are much lower, but still Spurs → Large broadband increase in the noise floor
- LDOs are still required but with relaxed PSR specs



Spectrum Manipulation: Delta-Sigma

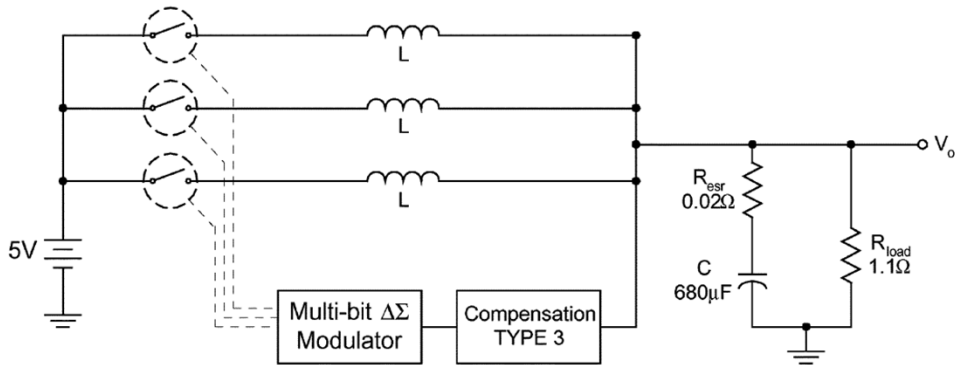


- Multi-bit Delta-Sigma
- Better Noise Floor, but several Inductors


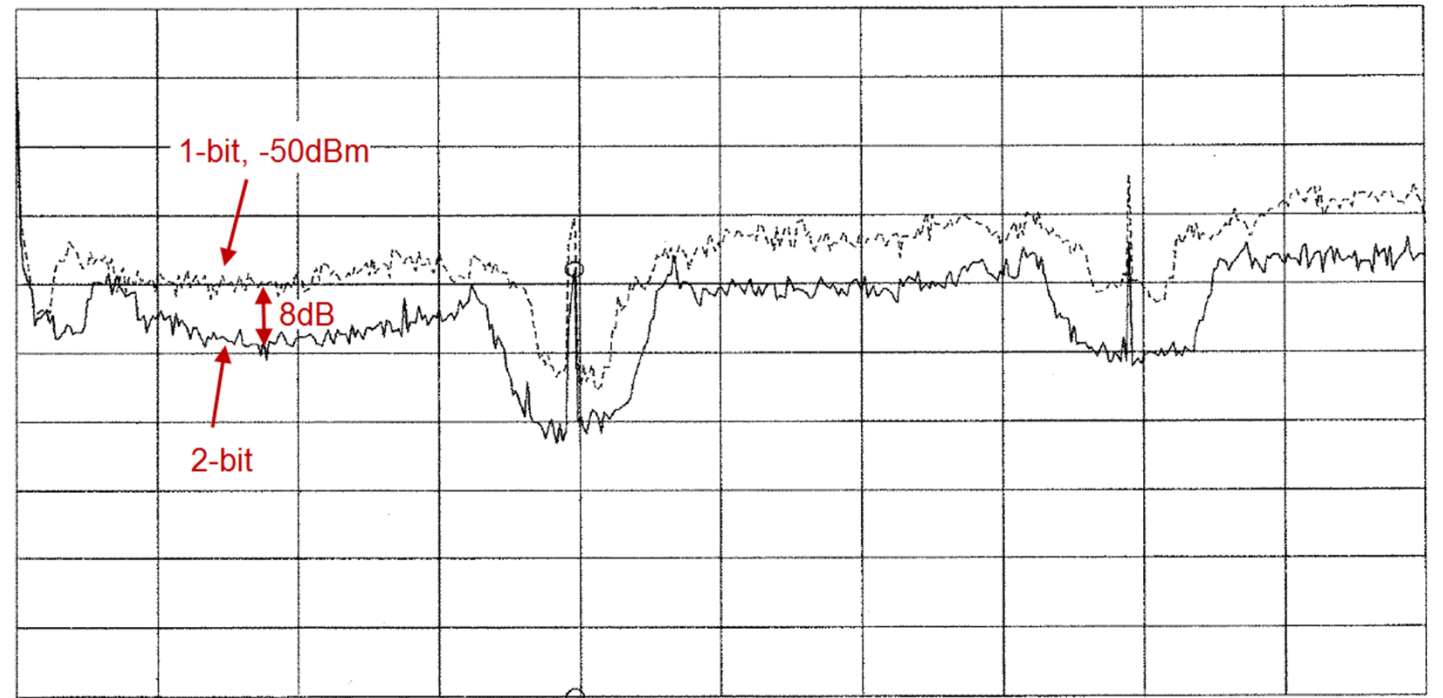


DIV 10.00 DIV 10.00 START STOP 500 1.000 Hz
 RBW: 300 Hz ST: 1.39 min RANGE: R= 10, T=-10dBm


Spectrum Manipulation: Frequency Hopping

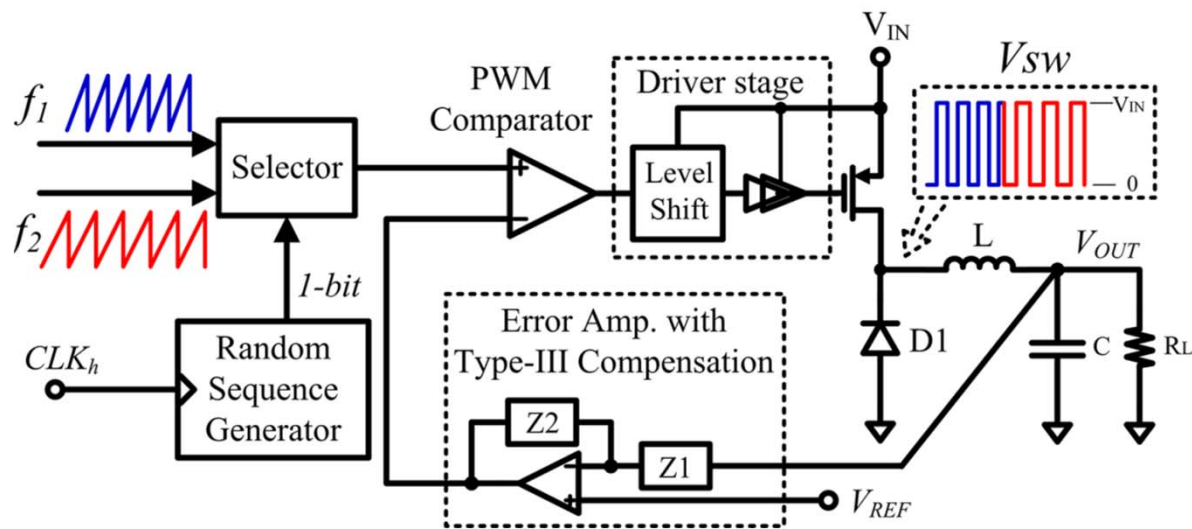

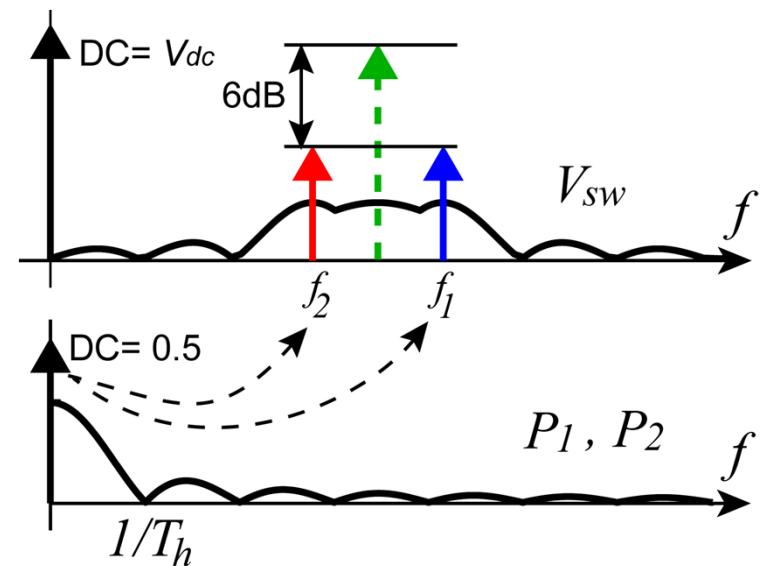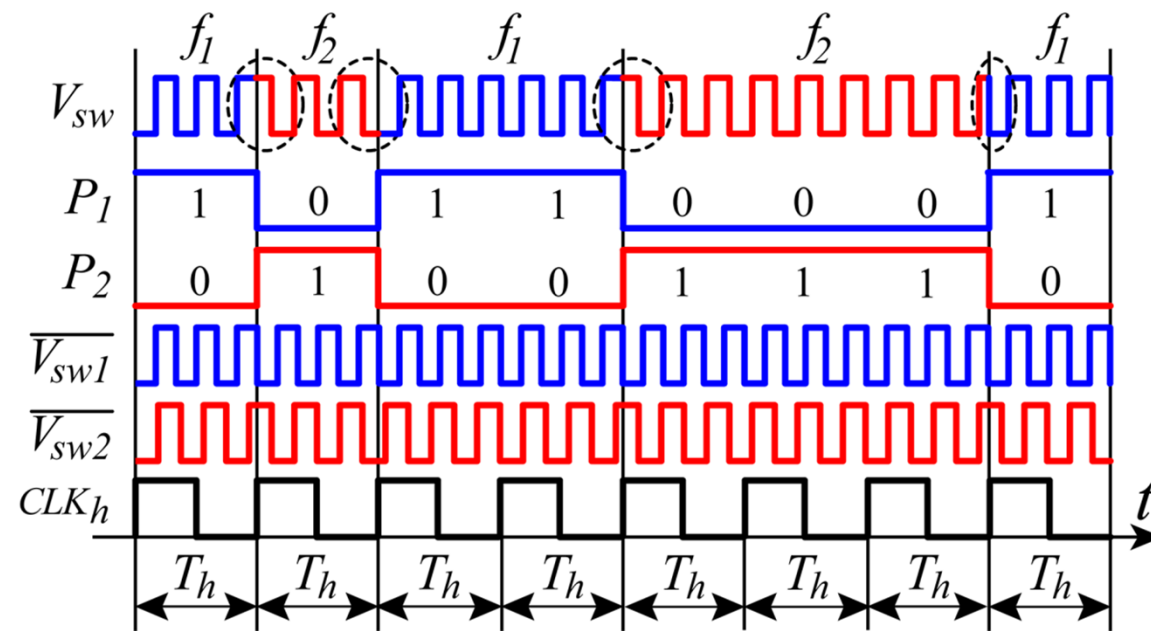Chengwu Tao and Ayman Fayed, "PWM Control Architecture for Spur-Free Operation in Buck Regulators," IEEE Transactions on VLSI, Accepted.





Spectrum Manipulation: Frequency Hopping


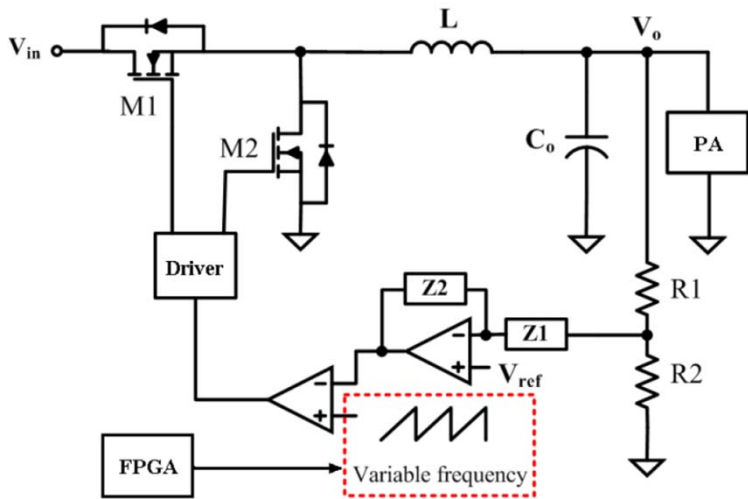


Jau-Hong Chen, Pang-Jung Liu, Y.-J.E. Chen "A spurious emission reduction technique for power amplifiers using frequency hopping DC-DC converters," IEEE RFIC, pp. 145-148, Jun. 2009.

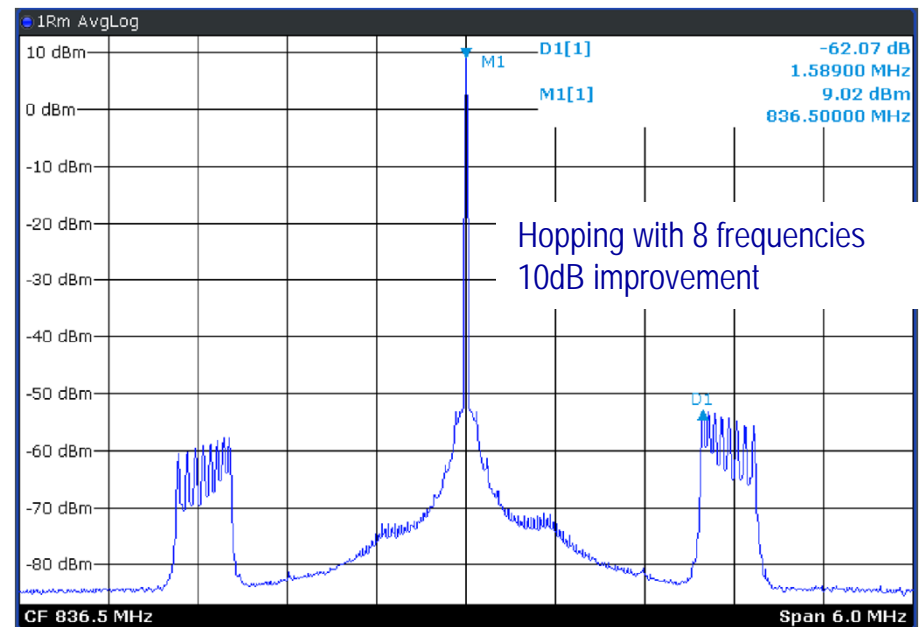
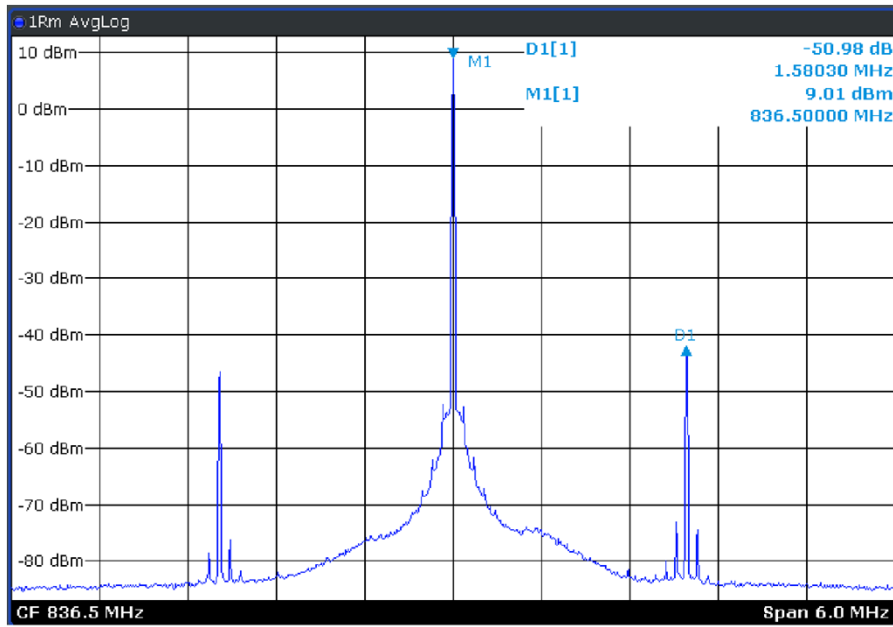
- Traditional random frequency hopping (Constant hopping rate)
- Spurs are lower, but still Spurs
- Large number of frequencies is needed to get significant reduction



Spectrum Manipulation: Frequency Hopping

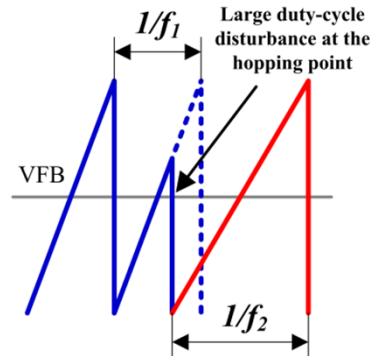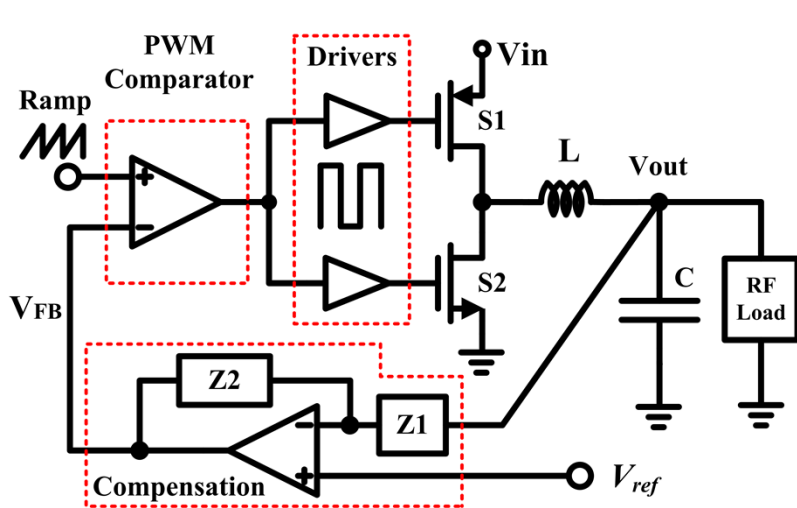


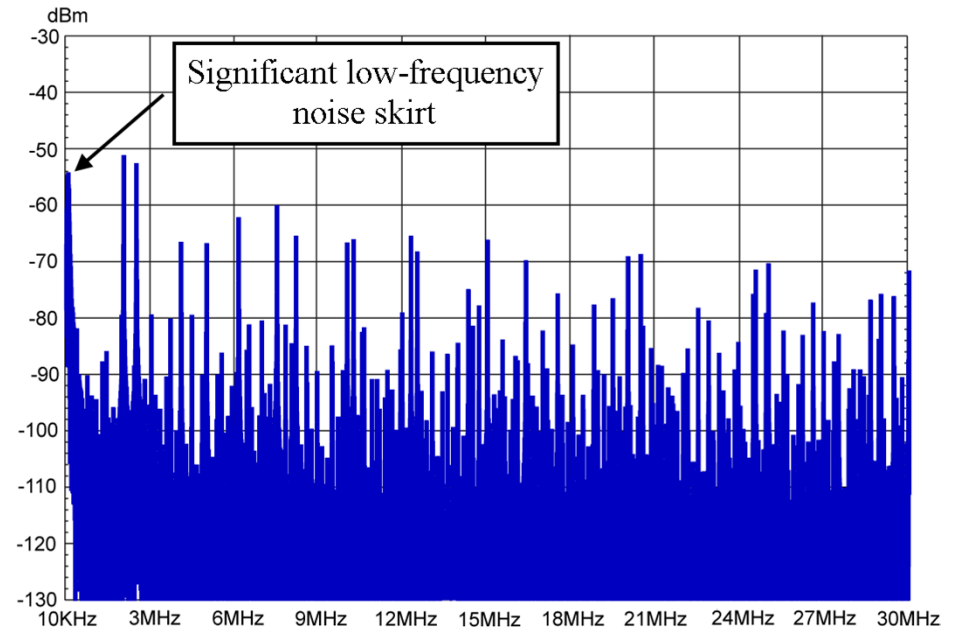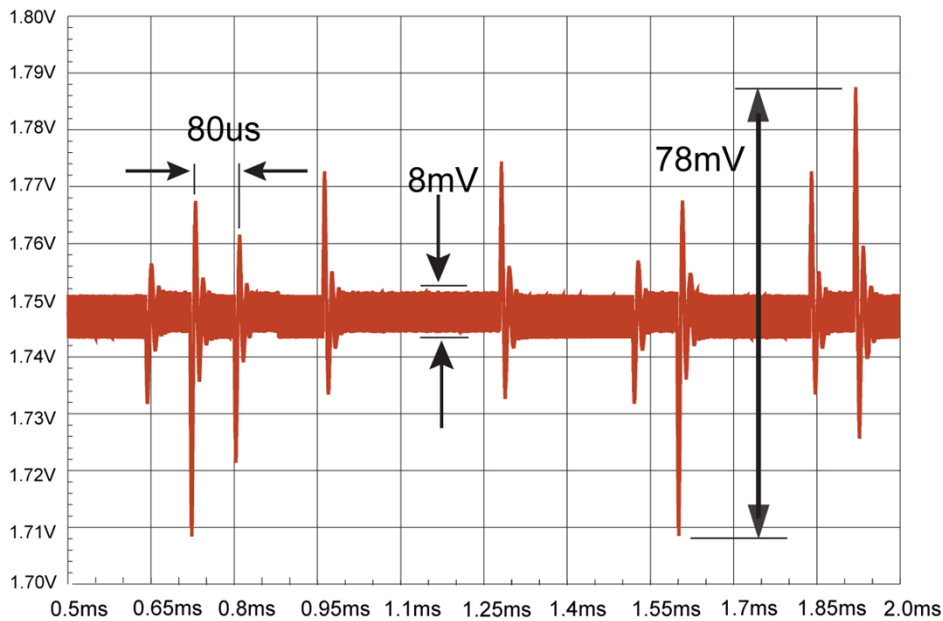- Duty Cycle disturbance is problematic for low frequency spectrum
- Can be mitigated by using a long hopping period → less spreading at high frequency





Spectrum Manipulation: Frequency Stepping

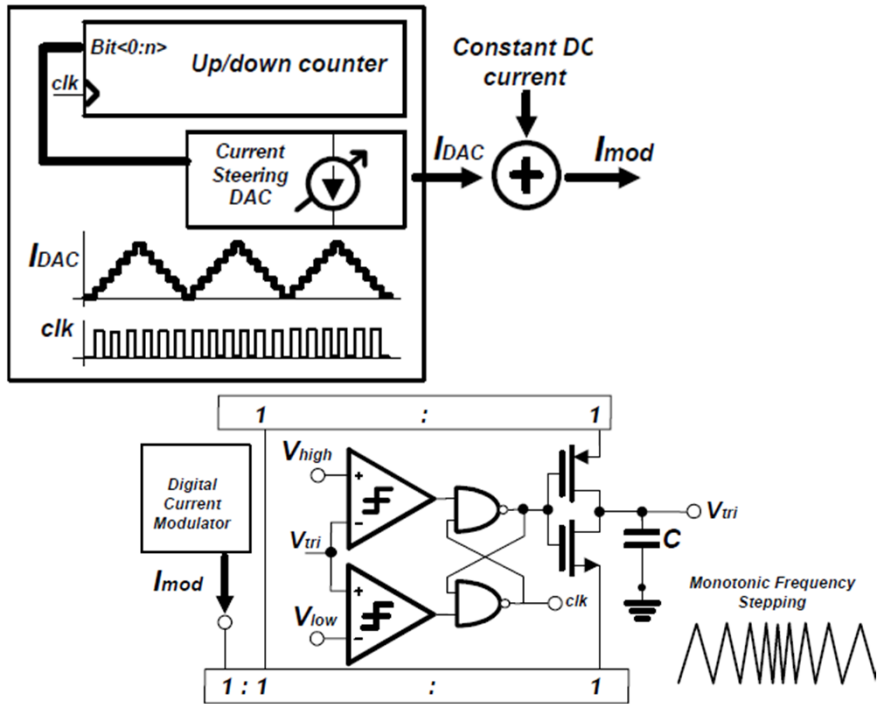Eung Jung Kim, Chang-Hyuk Cho, Woonyun Kim, Chang-Ho Lee, and Joy Laskar, "Spurious Noise Reduction by Modulating Switching Frequency in DC-to-DC Converter for RF Power Amplifier," IEEE RFIC Symposium, pp. 43-46, May 2010



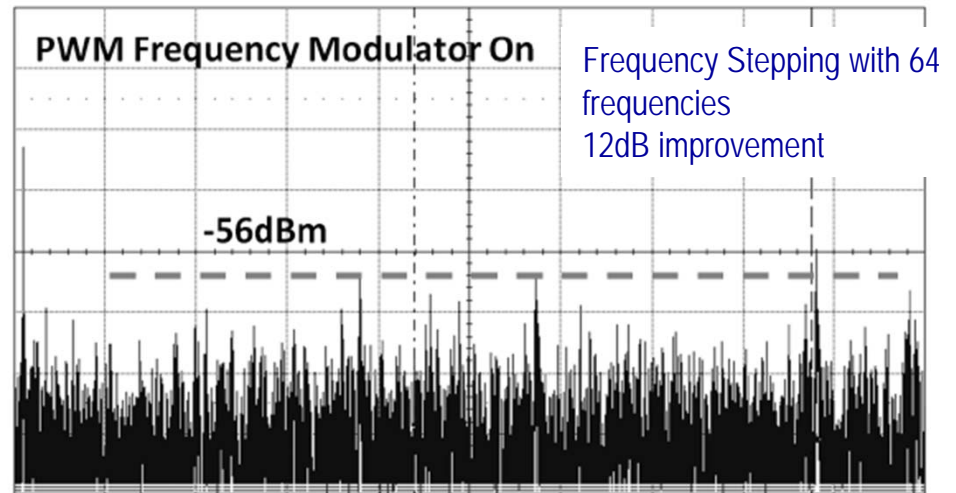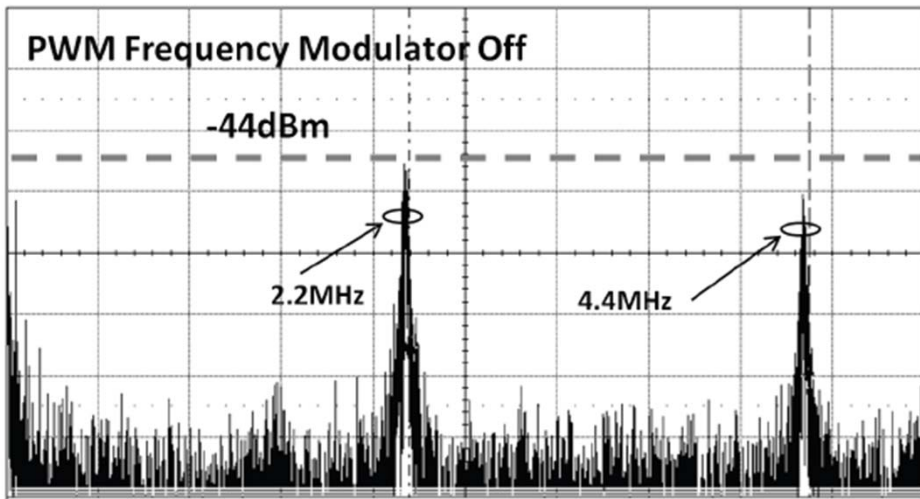- Monotonic periodic frequency stepping
- Resolves the issue of duty-cycle distortion
- Spurs are lower, but still Spurs
- Large number of frequencies is needed and many spurs are generated




Outline

- ◆ Personal Background & Research Group
- ◆ Power Management → The story
- ◆ The Switching Noise Problem
 - Types of power supplies
 - Spectral characteristics of switching noise
 - Impact on noise-sensitive Analog/RF Loads
- ◆ Switching Noise Mitigation Techniques
 - Time-domain Approaches
 - Frequency-domain Approaches
- ◆ Constant Cycle Frequency Hopping for Spur-Free Operation
- ◆ Power Management and Formal Education → If time permits

Constant Cycle Frequency Hopping (CCFH)

- ◆ Adopt random frequency hopping to avoid injecting extra noise in the system and to minimize the number of hopping frequencies needed
- ◆ CCFH (Variable Hopping Rate)
 - Minimizes duty-cycle disturbance during hopping
 - Maximizes hopping rate without transients
 - Maximum spur reduction with minimum noise floor peaking
- ◆ Add random phase chopping
 - Fully eliminates switching spurs at the output

CCFH: PWM Architecture

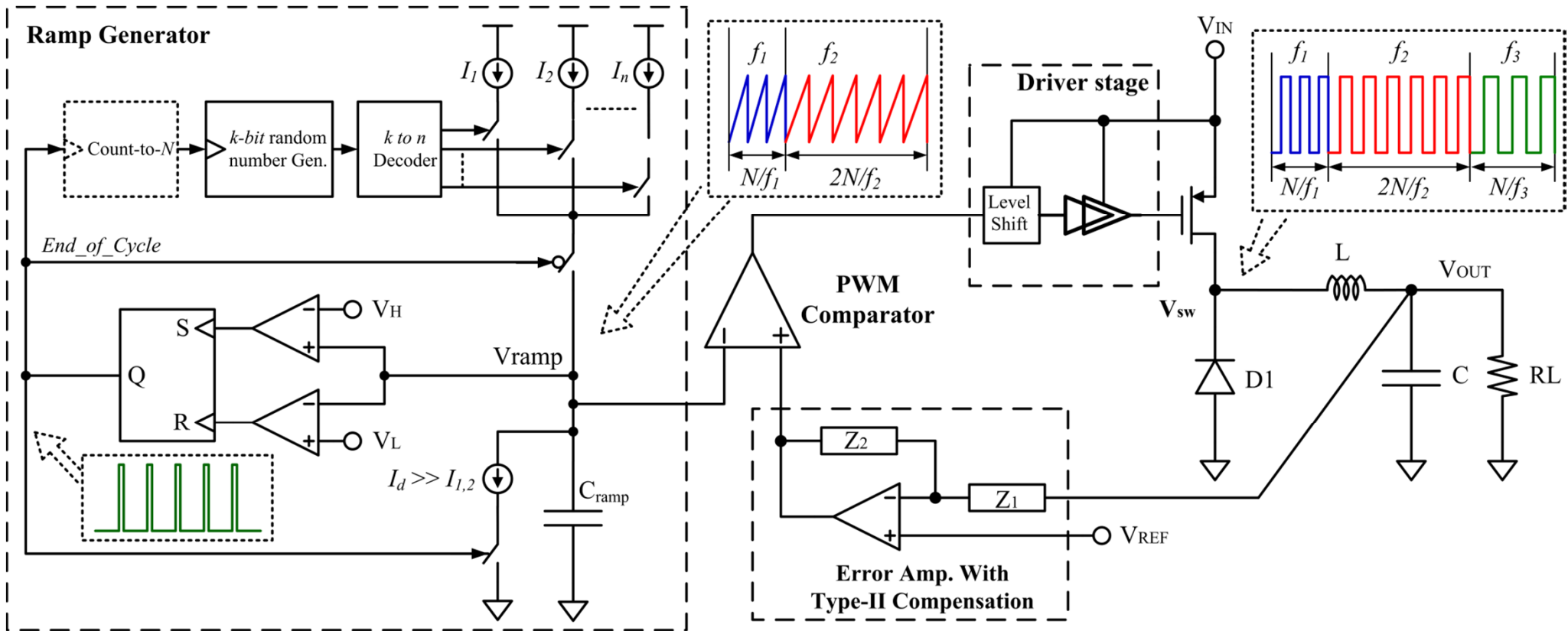


[1] Ayman Fayed and Chengwu Tao, "System and Method for Providing Power via a Spurious-Noise-Free Switching Device", US Patent Pending, Application # 13/397,251 Feb. 2012.

[2] Chengwu Tao, and Ayman Fayed, "Spurious-Noise-Free Buck Regulator for direct-powering of Analog/RF loads using PWM Control with Random Frequency Hopping and Random Phase Chopping," IEEE International Solid-State Circuits Conference (ISSCC 2011), pp. 396-397, Feb. 2010. Feb. 2011.

[3] Chengwu Tao and Ayman Fayed, "PWM Control Architecture for Spur-Free Operation in Buck Regulators," IEEE Transactions on VLSI, Accepted.

CCFH: Maximizing Hopping Rate

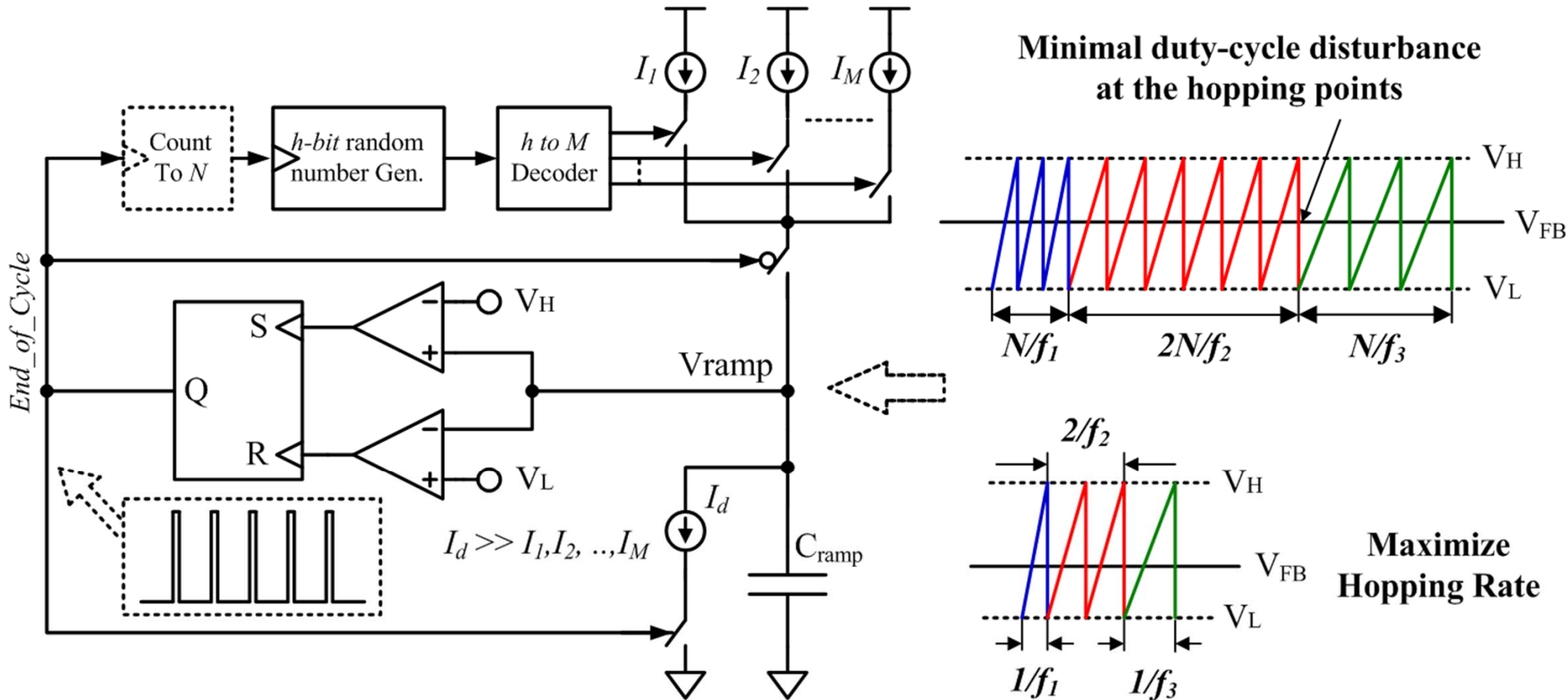


◆ Minimize duty-cycle disturbance

- Maintain ramp range regardless of frequency
- Custom-tailored hopping period → Constant-Cycle

Maximize Hopping Rate

CCFH: Spectral Analysis

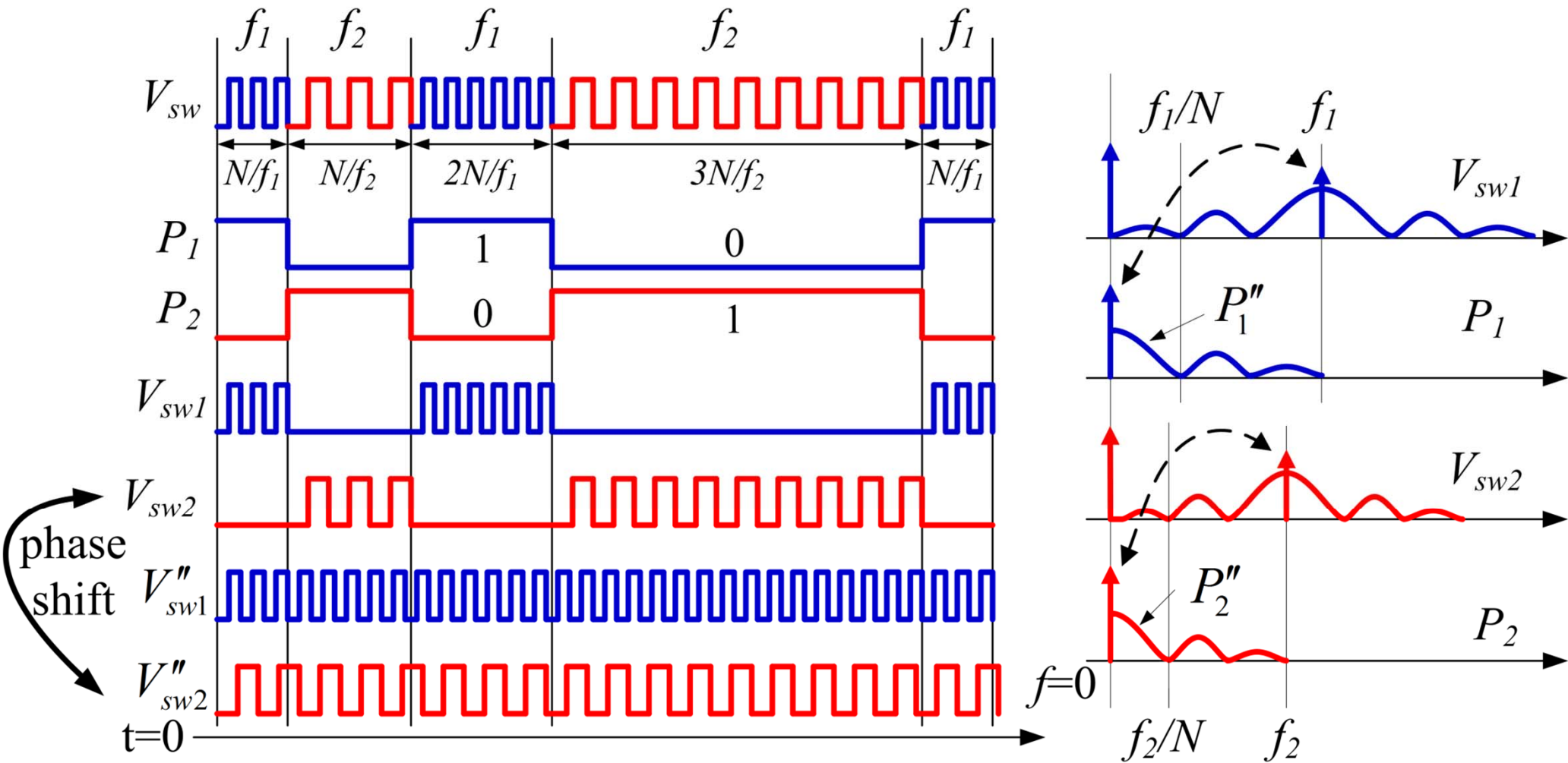

◆ Freq. hopping alone won't eliminate spurs


➤ Phase chopping $\rightarrow k \cdot f_1 \cdot N \cdot (1/f_1 - 1/f_2) = k \cdot f_1 \cdot N \cdot \Delta T$

CCFH: Phase Chopping

$$V_{sw1}(t) = \left[\left(\frac{f_2}{f_1 + f_2} \right) + P_1''(t) \right] \times \left[(V_{in} \cdot dc) + \sum_{j=1}^{\infty} \gamma_j \sin(2\pi j \cdot f_1 (t - k \cdot N \Delta T) + \phi_j) \right]$$

$$\left(\frac{f_2}{f_1 + f_2} \right) \times \sum_{j=1}^{\infty} \gamma_j \times \left[\begin{array}{l} \cos(2\pi j \cdot k \cdot f_1 N \Delta T) \times \sin(2\pi j f_1 t + \phi_j) - \\ \sin(2\pi j \cdot k \cdot f_1 N \Delta T) \times \cos(2\pi j f_1 t + \phi_j) \end{array} \right]$$

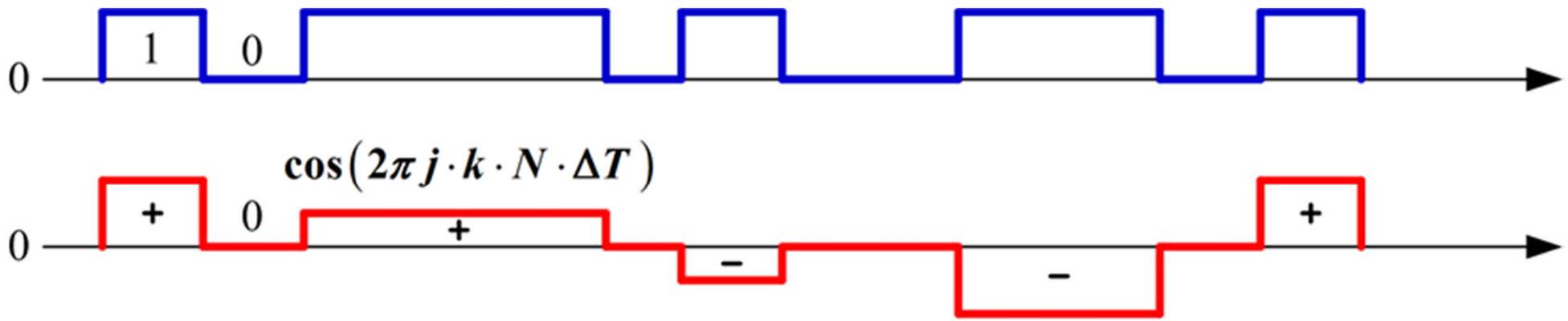◆ Phase chopping modulates the gating function



CCFH: Eliminating Spurs

- ◆ To achieve zero average

$$\sum_k \cos(2\pi j \cdot k \cdot f_1 N \Delta T) = \sum_k \sin(2\pi j \cdot k \cdot f_1 N \Delta T) = 0$$

- ◆ But k increases indefinitely \rightarrow zero average requires infinite period of time?
- ◆ Fortunately the modulating terms are periodic


$$f_1 N \Delta T = \frac{m}{n}$$



$$\sum_{k=1}^{k=n} \cos(2\pi j \cdot k \cdot f_1 N \Delta T) = \sum_{k=1}^{k=n} \sin(2\pi j \cdot k \cdot f_1 N \Delta T) = 0$$

CCFH: Eliminating Spurs

◆ Average = Zero → Dirichlet kernel

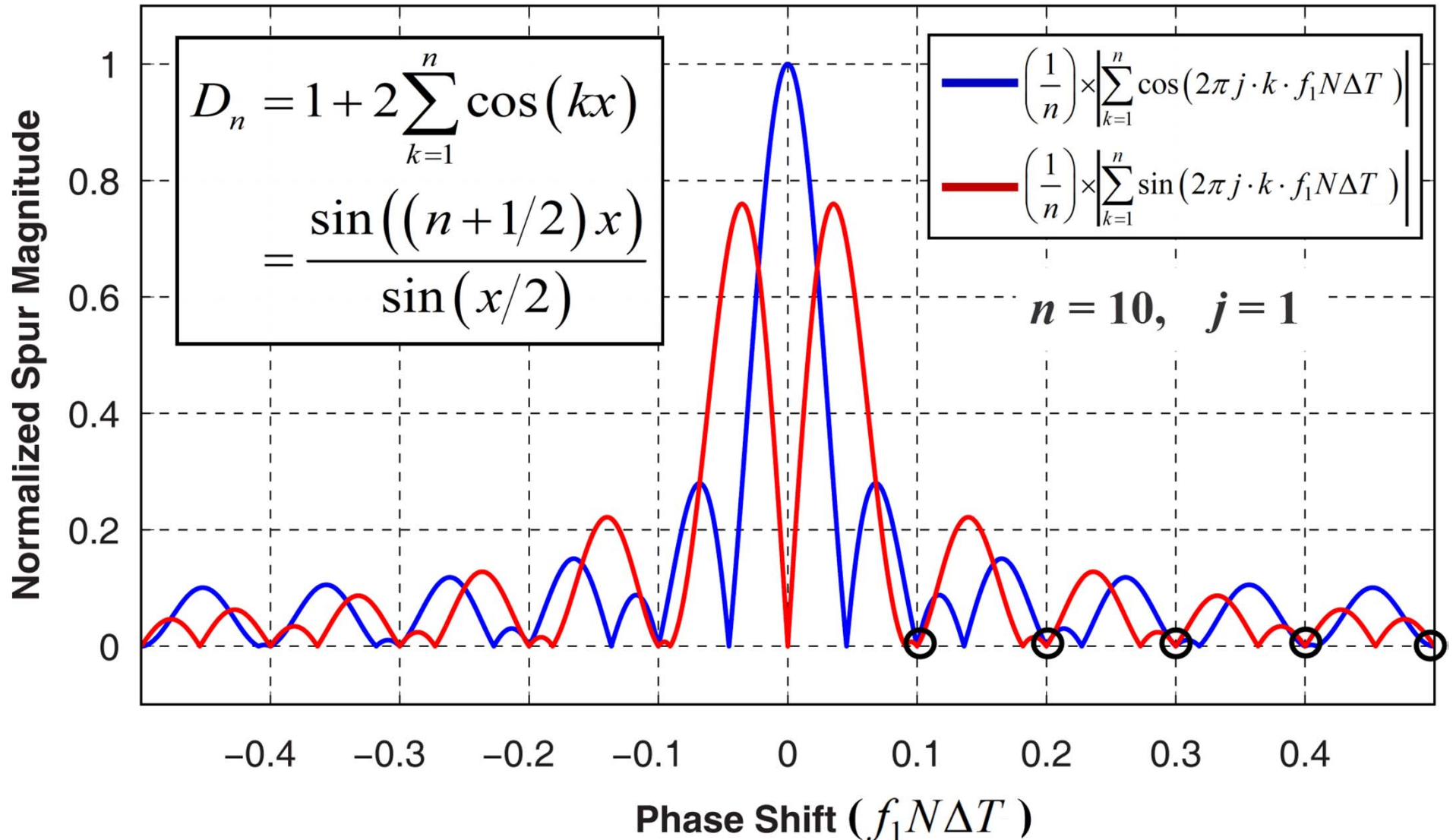

CCFH: Eliminating Spurs

◆ Condition for Spur Elimination → Two Frequencies

$$f_1 N \Delta T = \frac{m}{n} \neq \text{Integer} \quad f_2 N \Delta T = \frac{Nm}{Nn + m} \neq \text{Integer}$$

↓ ↓ $N = 1$

$$f_1 N \Delta T = (m/n) \neq \text{Integer}$$
$$f_1 / f_2 = \frac{n + m}{n}$$

◆ Condition guaranteed at maximum hopping rate $N=1$

- Easily implemented with segmented current mirrors → Current Steering DAC

CCFH: Eliminating Spurs

- ◆ Condition for Spur Elimination → Multiple Frequencies

$$f_i N \Delta T_{ji} = \frac{m}{n} \neq \text{Integer} \qquad f_j N \Delta T_{ji} = \frac{Nm}{Nn + m} \neq \text{Integer}$$


↓ ↓ $N = 1$

$$f_M N \Delta T_{iM} = (m_i / n_i) \neq \text{Integer}$$
$$f_M / f_i = \frac{n_i + m_i}{n_i}$$


- ◆ It is sufficient for the condition to be met between each frequency and at least one other frequency in the set

Implementation

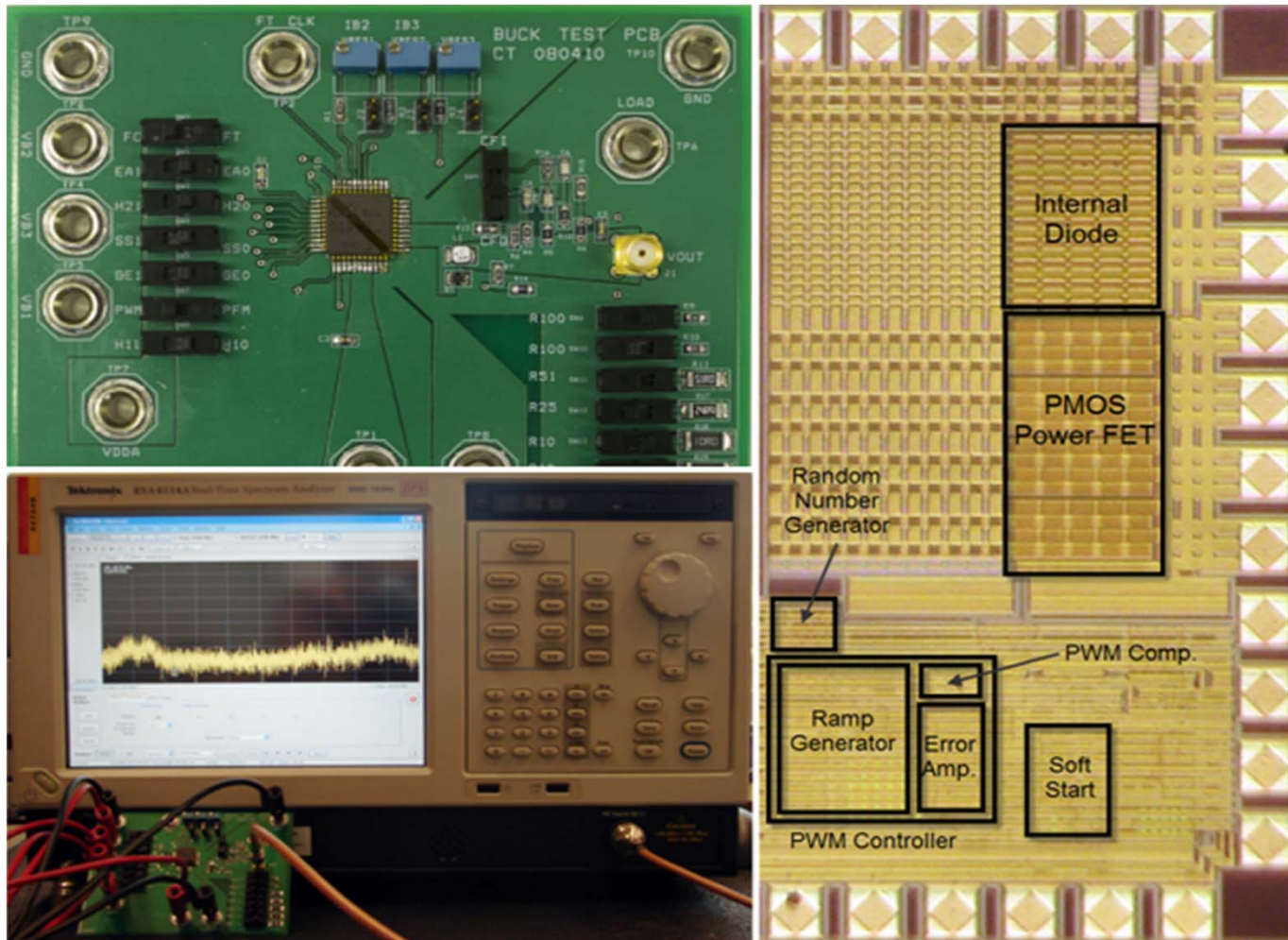
- ◆ In 0.35- μm \rightarrow Single Switching Frequency Mode, and CCFH mode with 2, 4, or 8 frequencies




Output Spectrum: 16MHz (8 Frequencies)

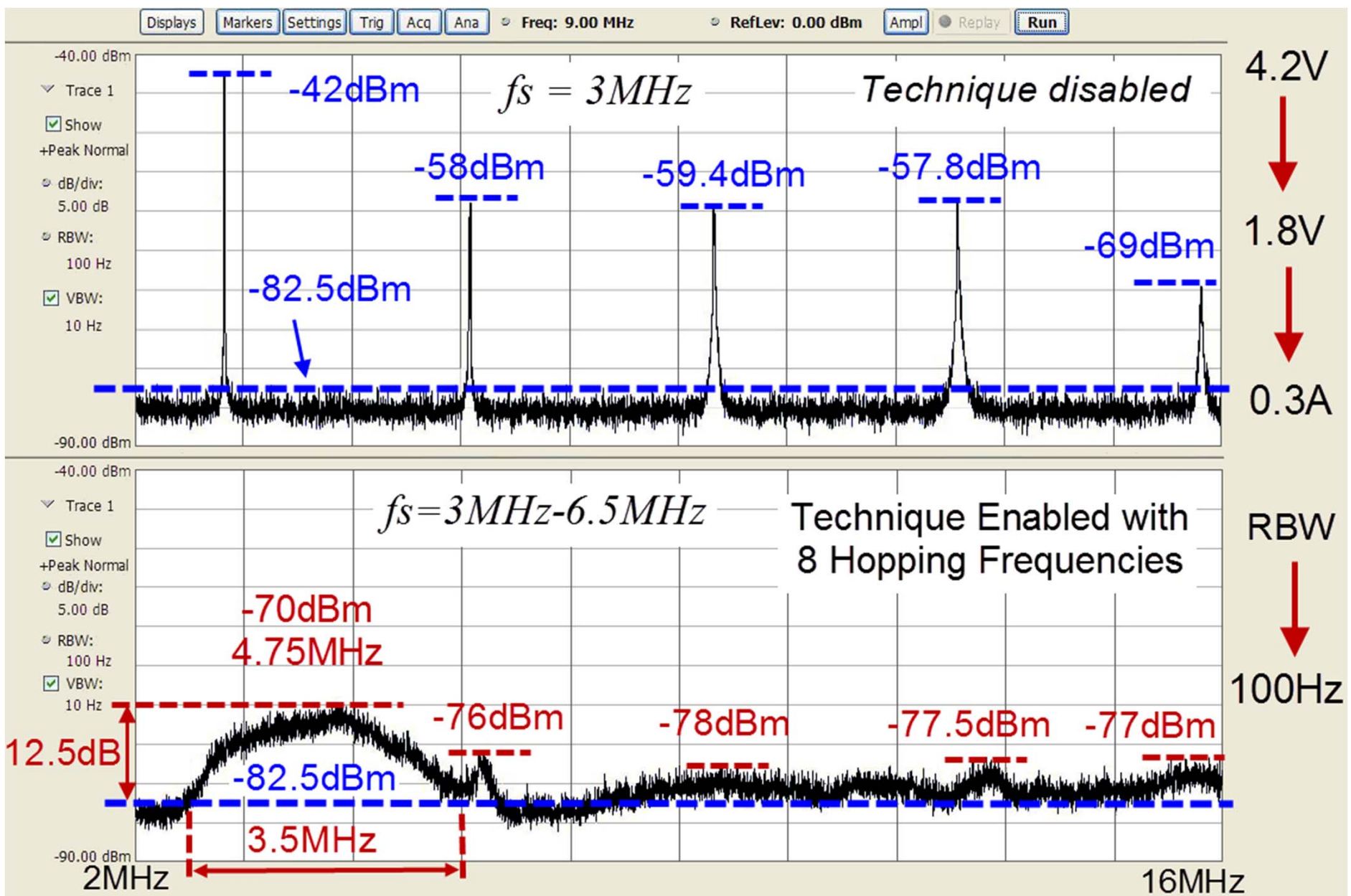


Output Spectrum: 60MHz (8 Frequencies)

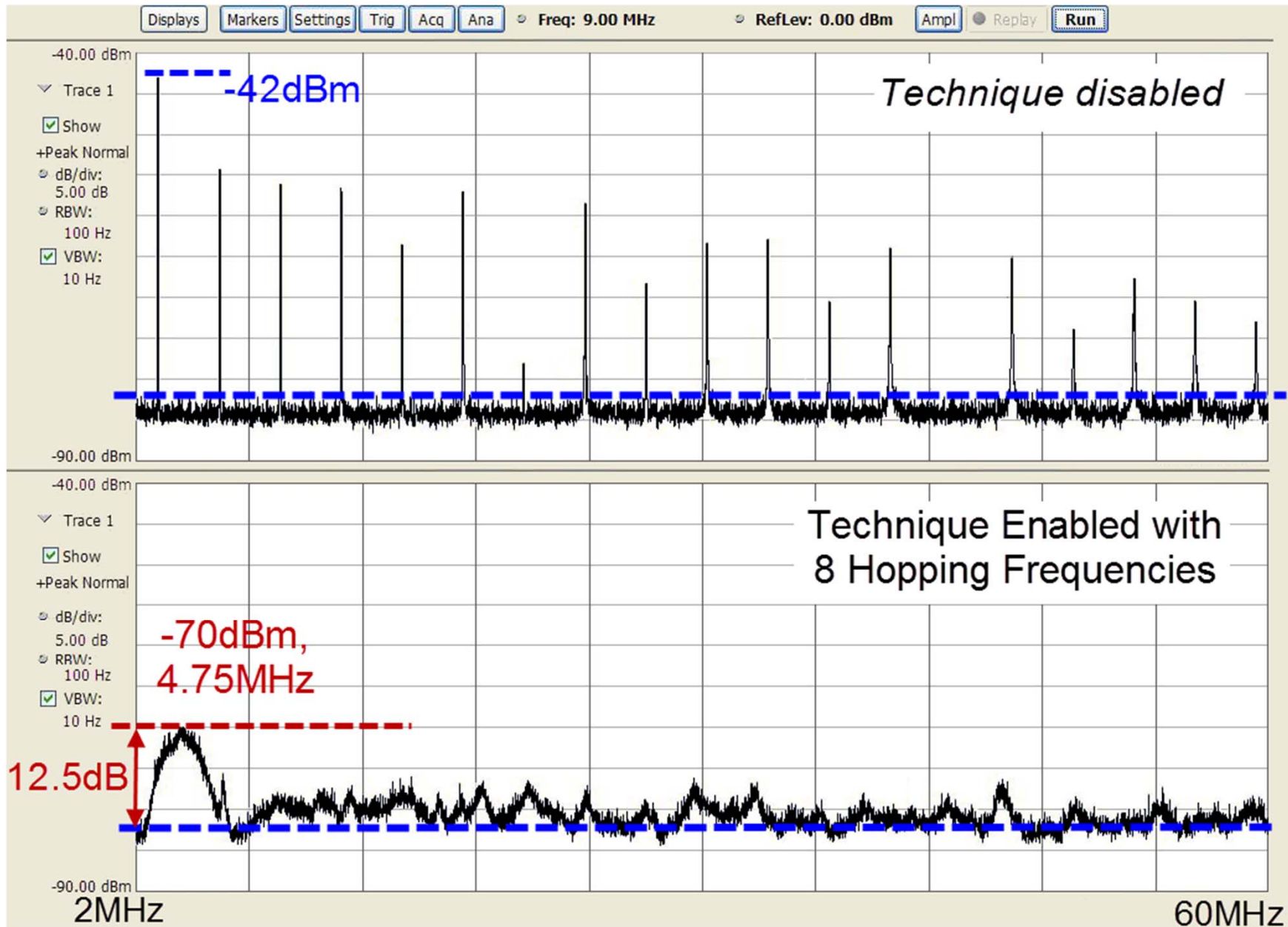


Output Spectrum: 16MHz (2,4 Frequencies)

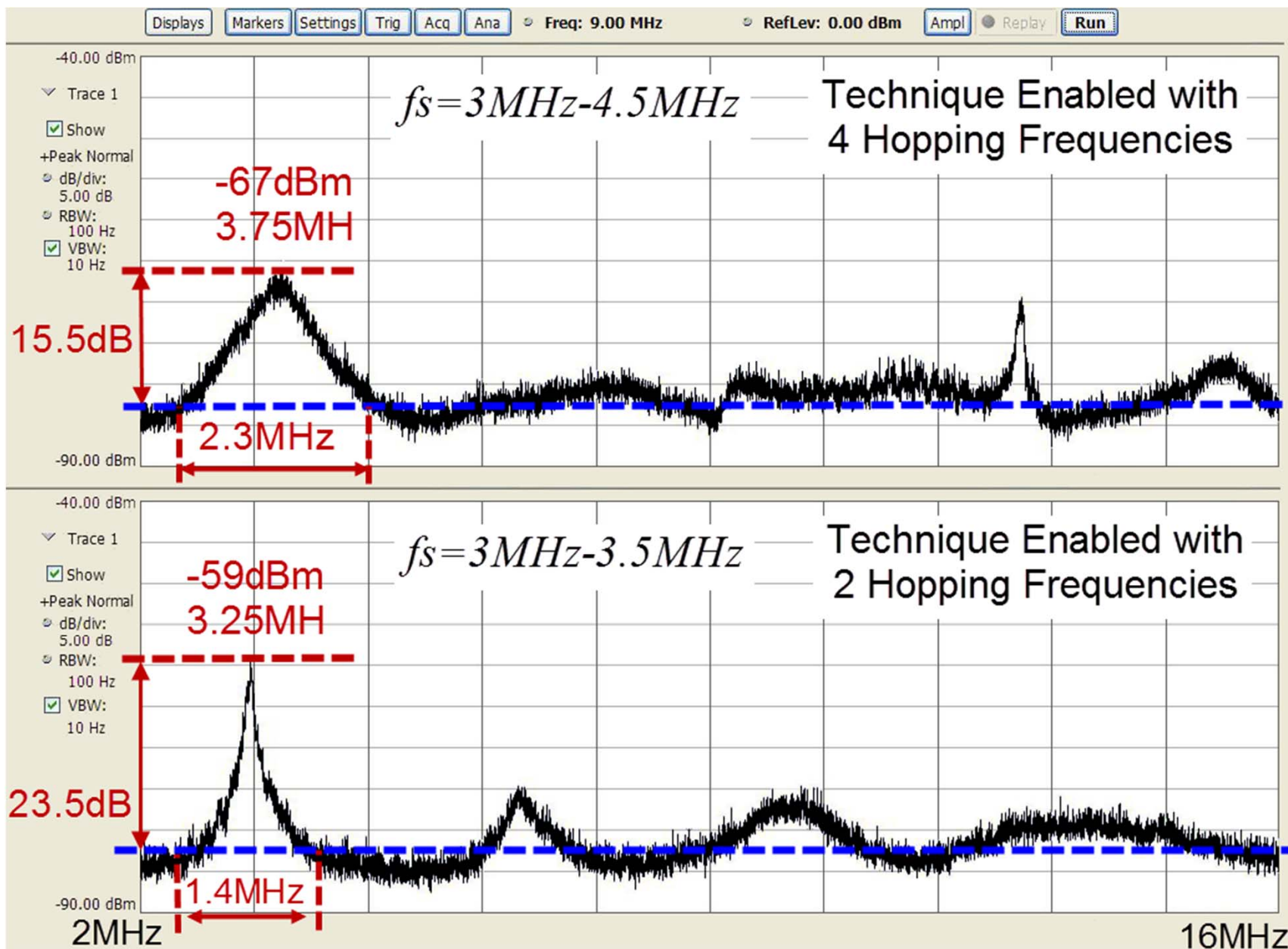


Output Spectrum: Low Frequency

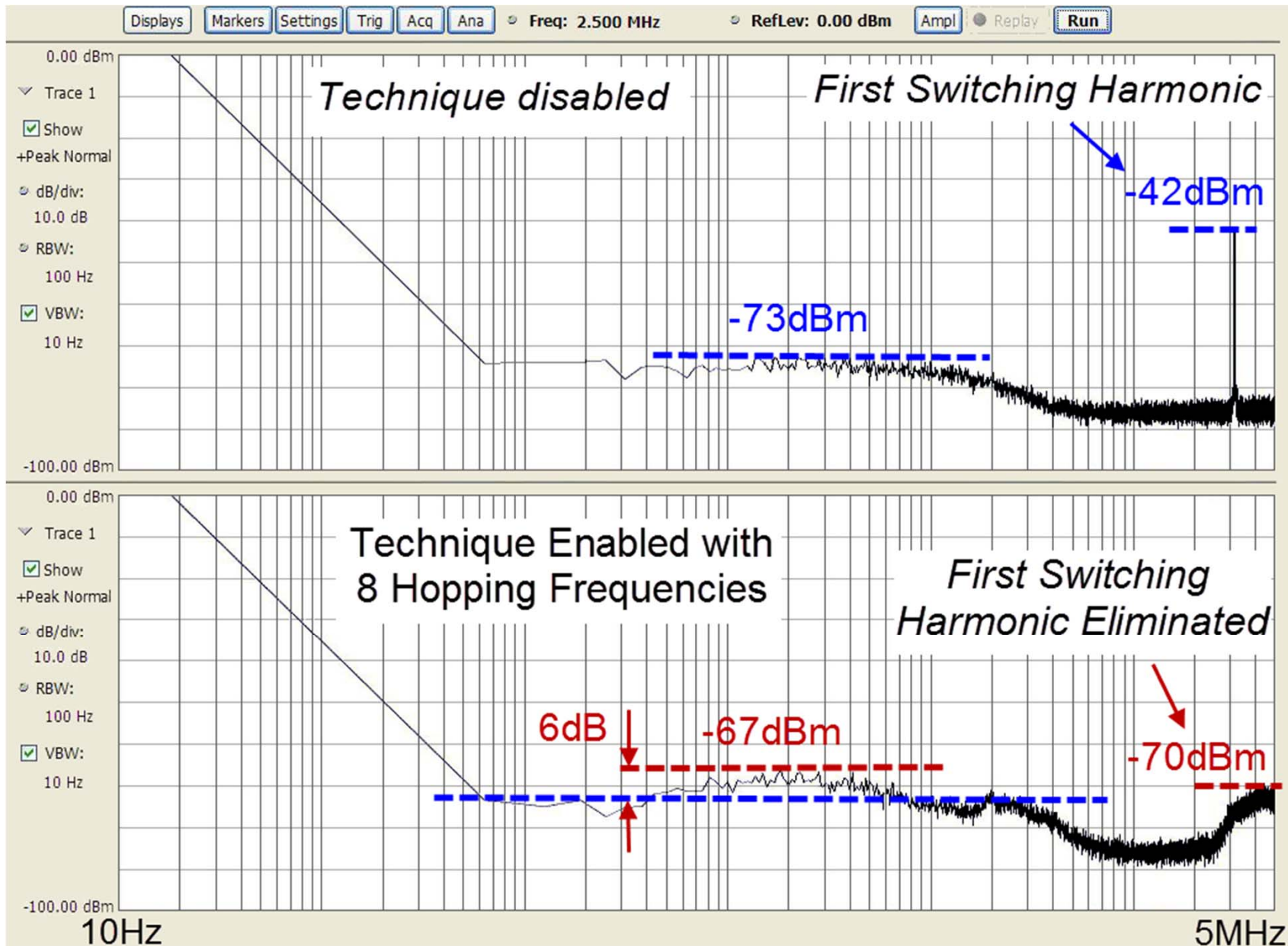


CCFH: Distortion

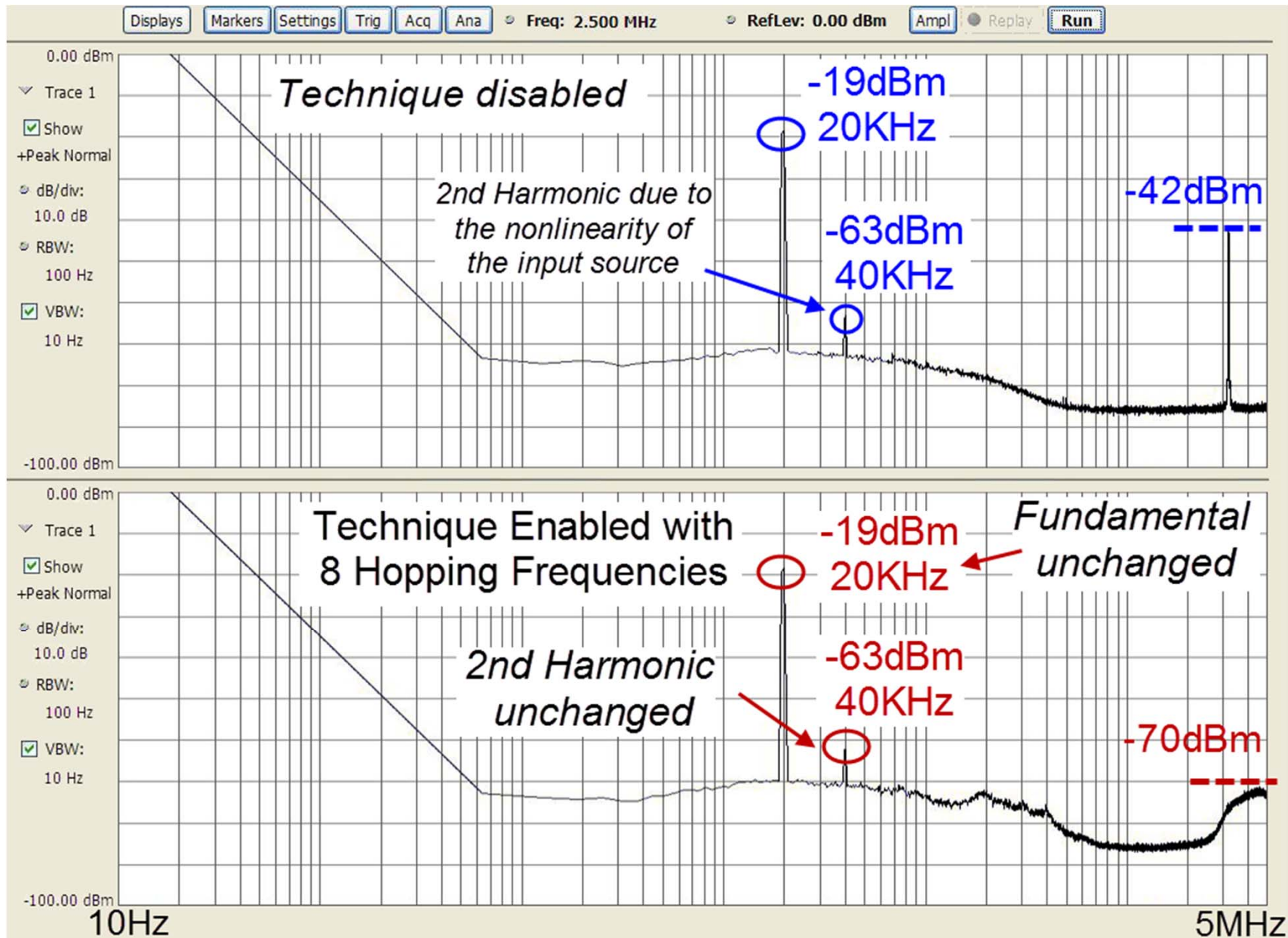


CCFH: Output Ripple

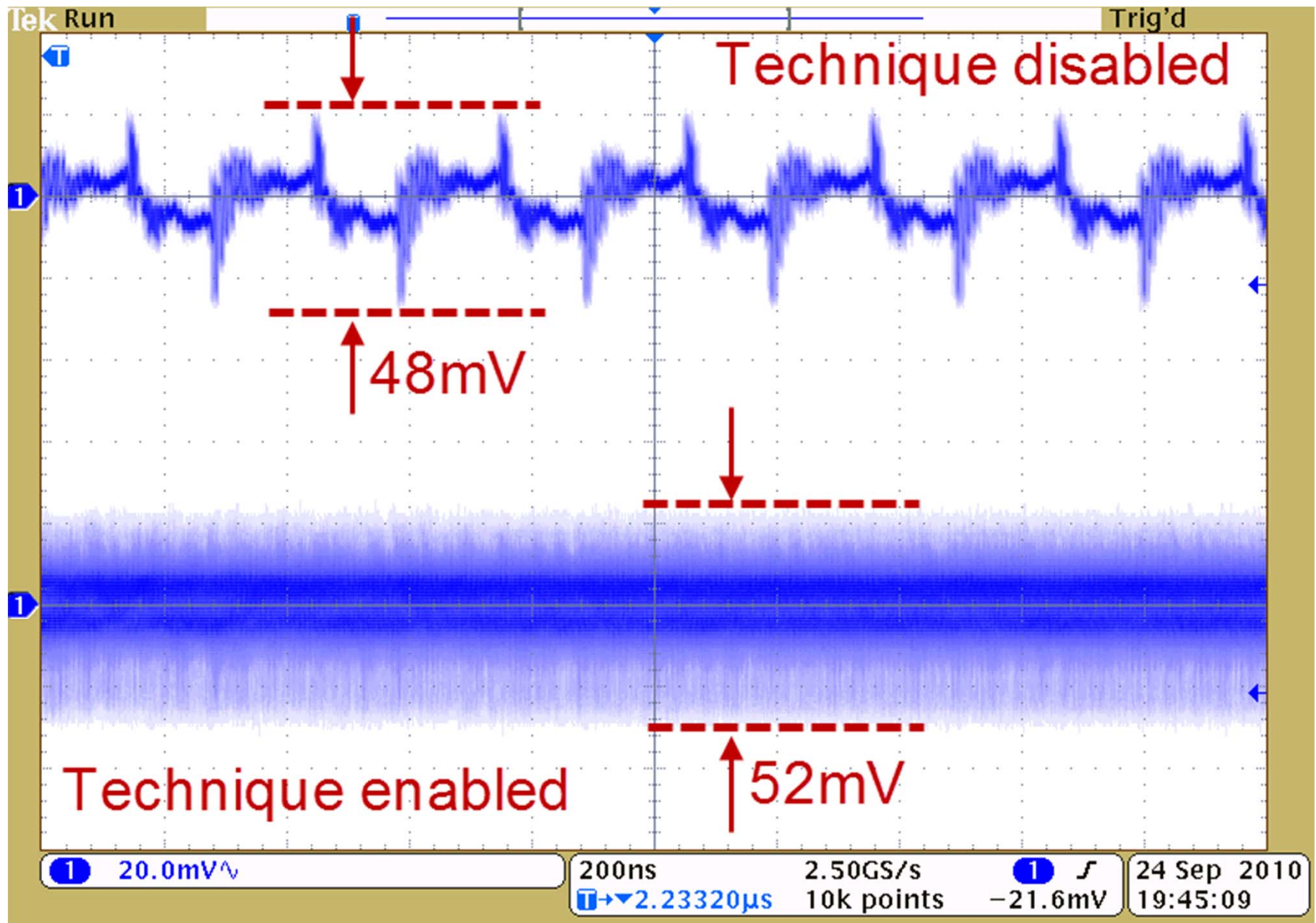


CCFH: Transient Response

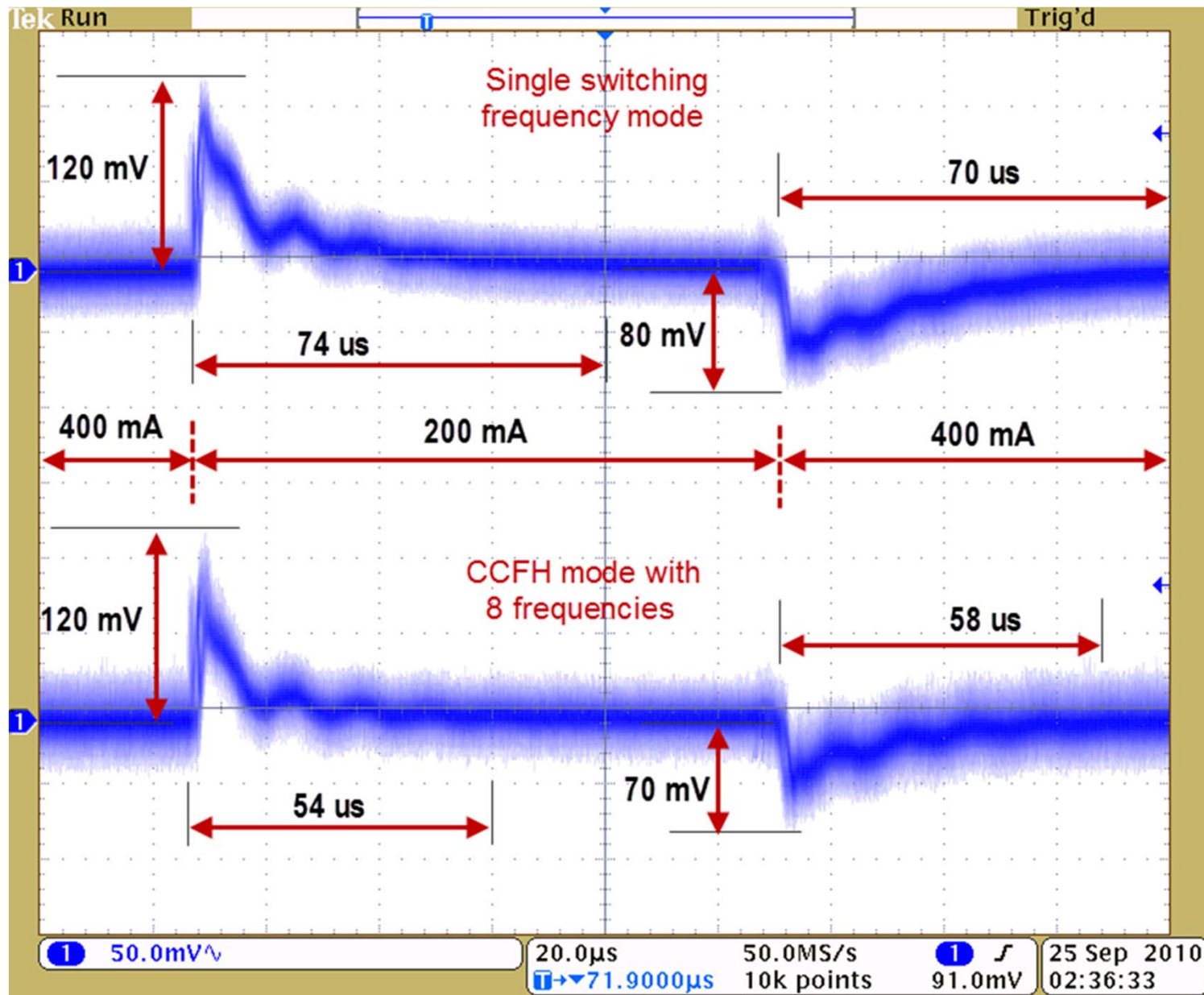

Verification with a GSM PA

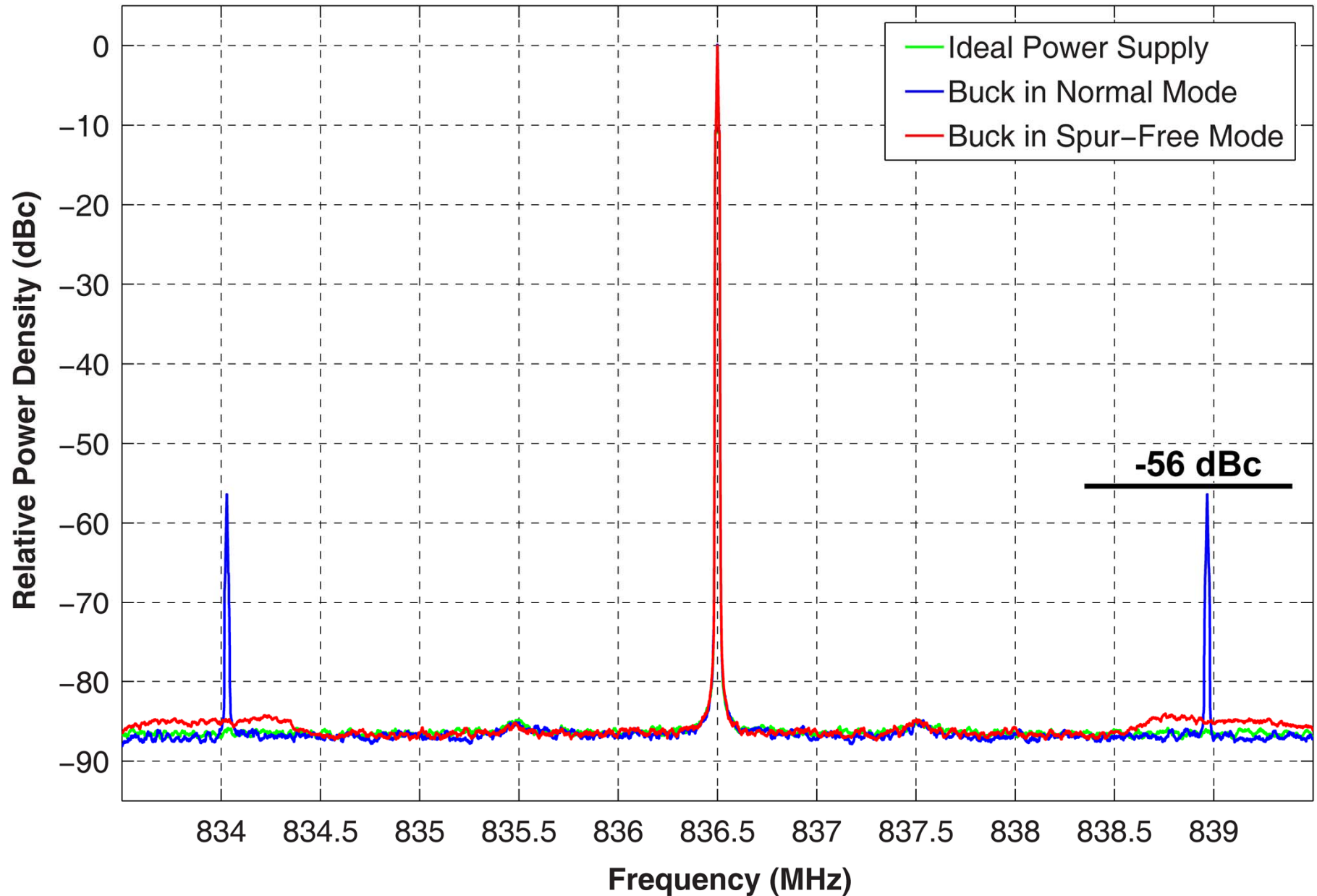

Verification with a GSM PA

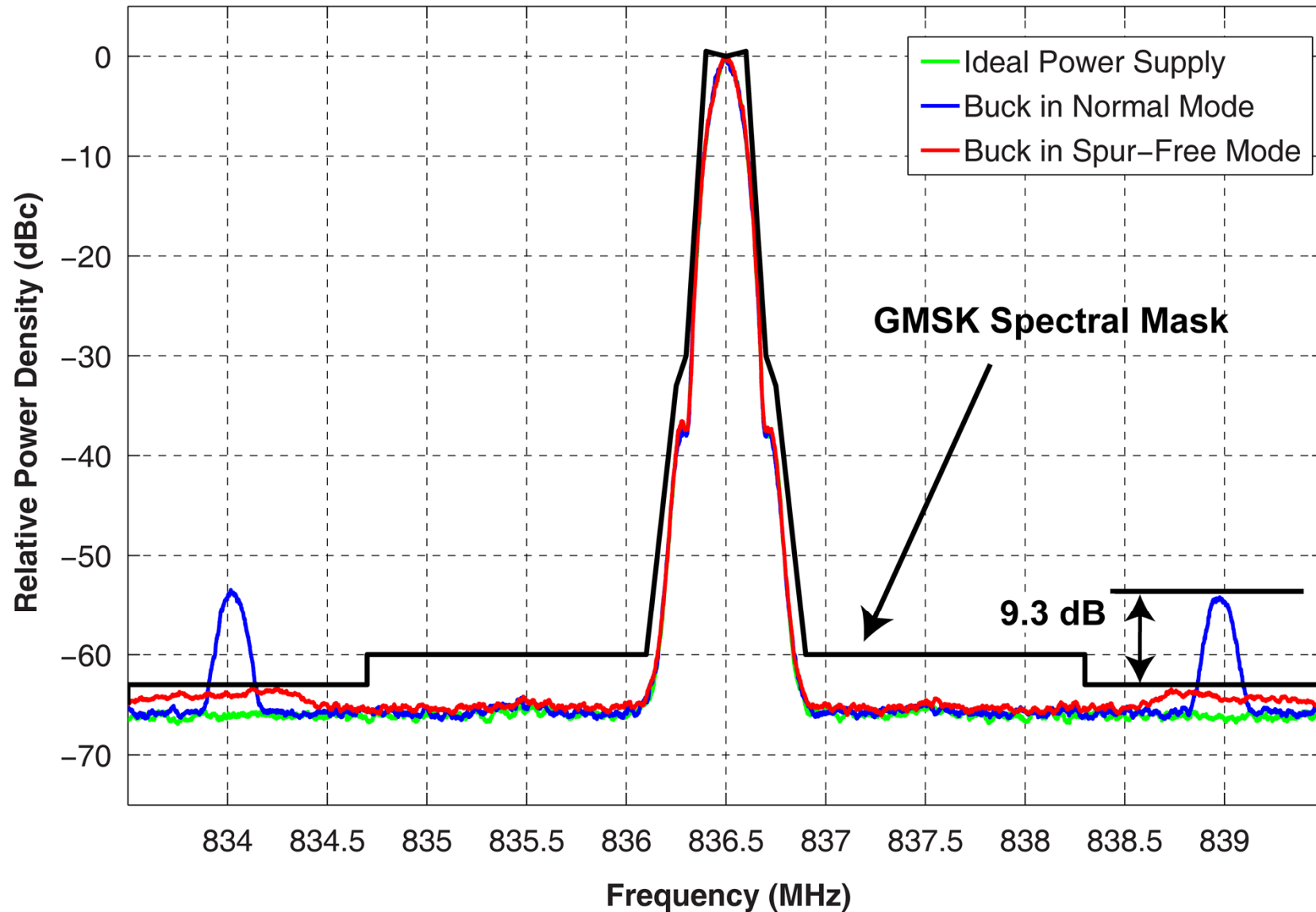




Chengwu Tao and Ayman Fayed, "A GSM Power Amplifier Directly-Powered from a DC-DC Power Converter,"
IEEE Microwave and Wireless Components Letters, vol. 22, no. 1, pp. 38-40, Jan. 2012.

CCFH in PFM Architectures

- ◆ PFM is popular at light load to improve efficiency
- ◆ Not immediately obvious how to meet spur-elimination condition → Frequency varies with the load → No direct control over it!
- ◆ One must observe, though, that the spur-elimination condition is relative in nature and not absolute
- ◆ Meeting the condition between hopped on-times in COT topologies leads to meeting it between the frequencies → Despite the nonlinear relationship!


$$f_s = \frac{2 \times V_o \times L \times I_L}{V_{in} \times (V_{in} - V_o) \times T_{on}^2}$$

CCFH: PFM Architecture - COT

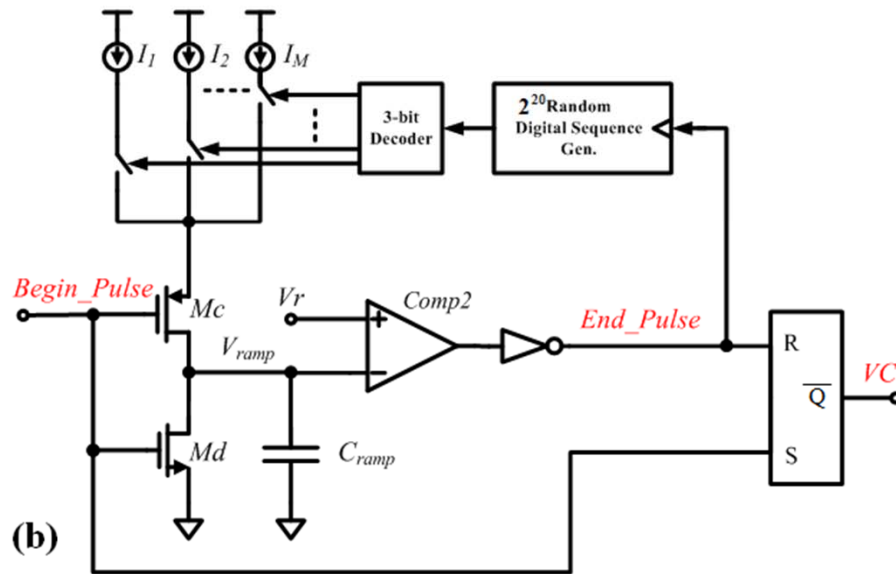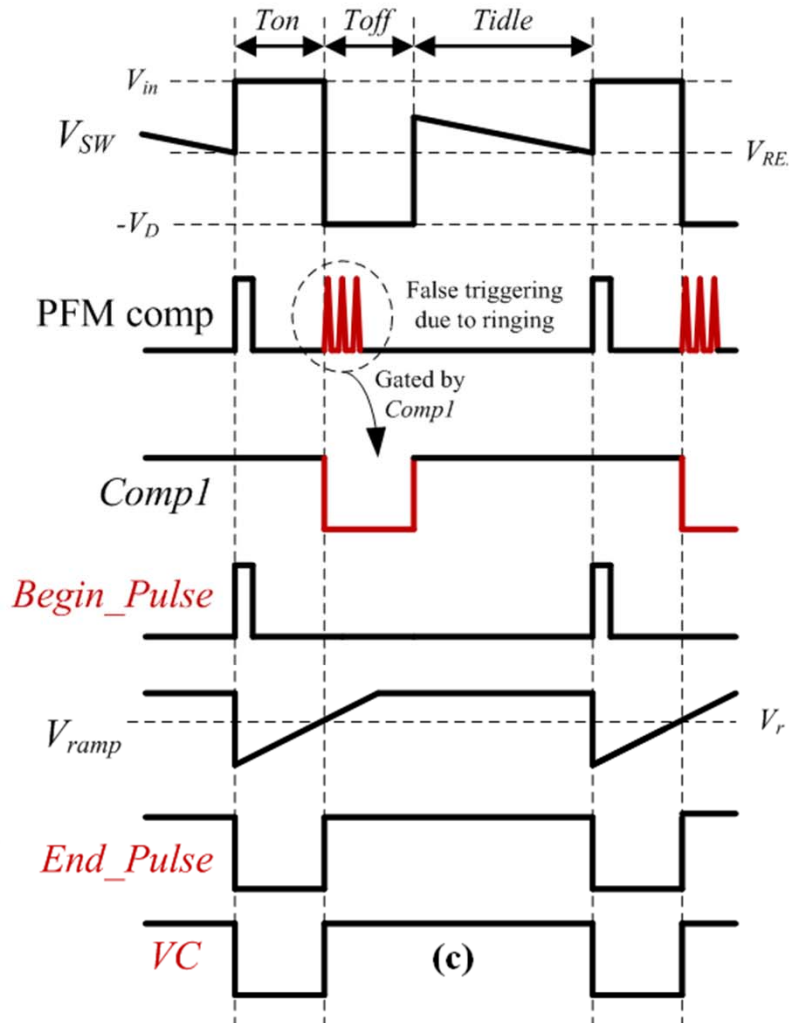
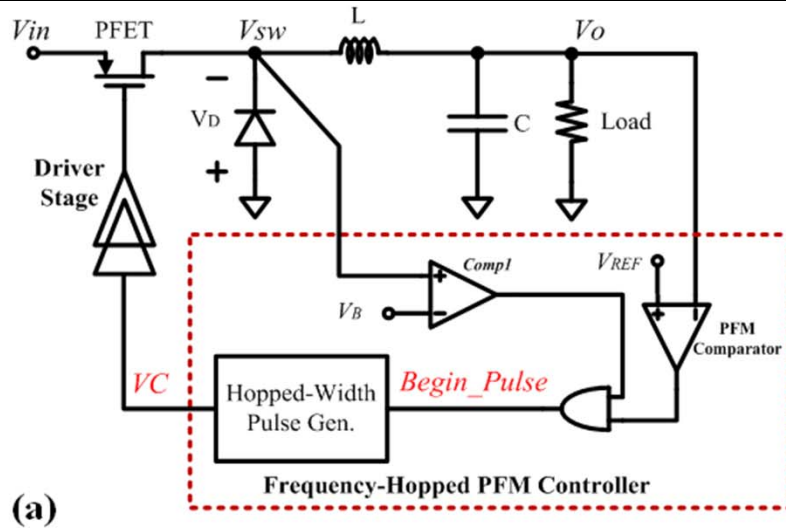


[1] Chengwu Tao and Ayman Fayed, "A Low-Noise PFM-Controlled Buck Converter for Low-Power applications," IEEE Transactions on Circuits and Systems I, vol. 59, no. 12, pp. 3071-3080, Dec. 2012.

CCFH-PFM-COT: Transient Performance

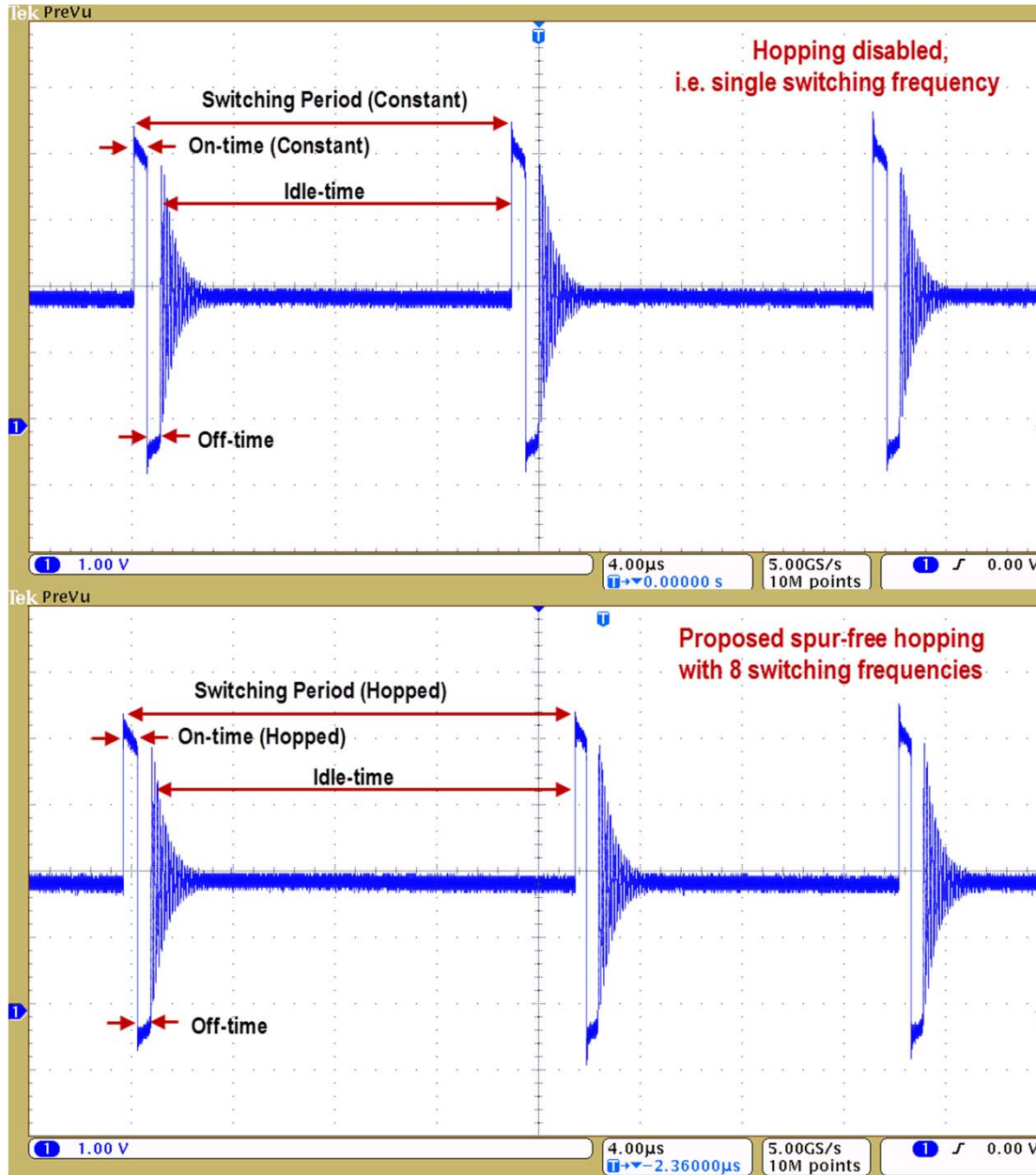

CCFH-PFM-COT: Output Spectrum

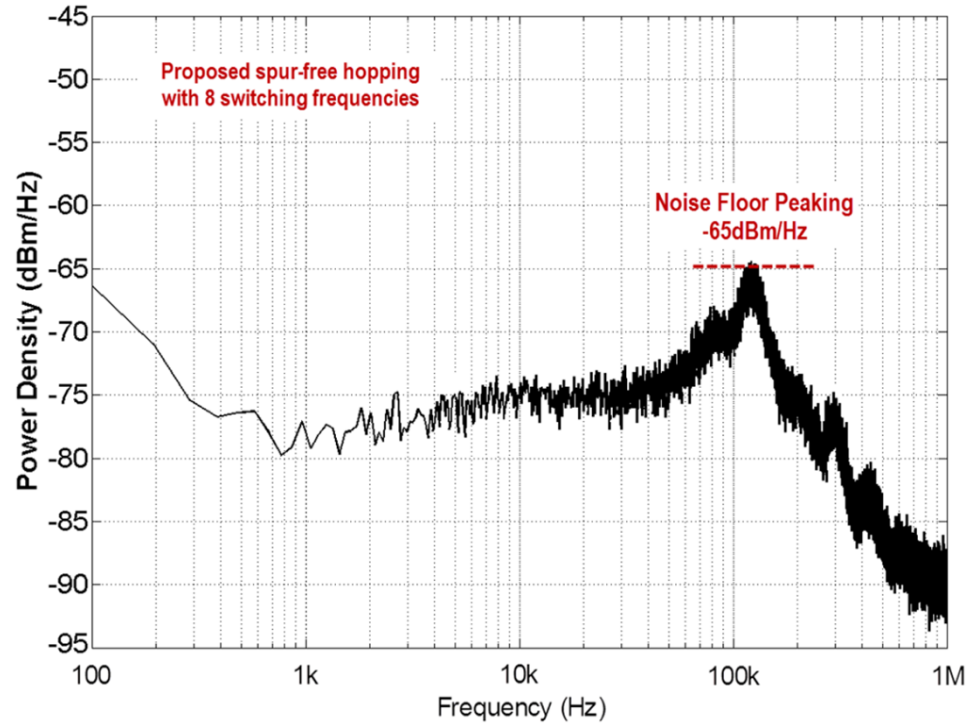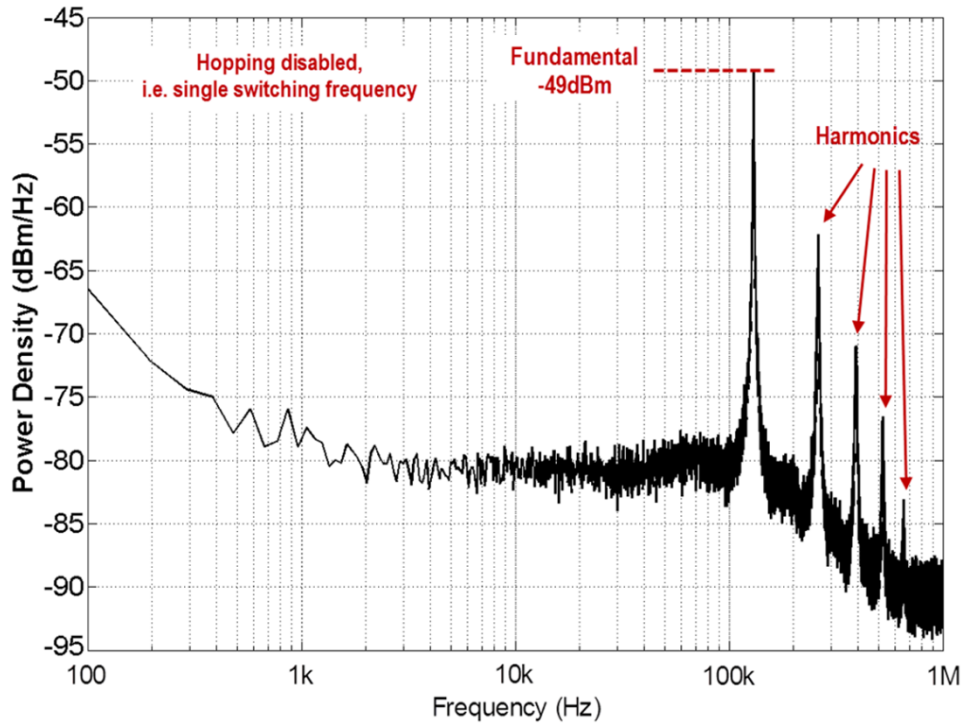

CCFH: Summary

◆ DC-DC Converters

- Spur-Free with minimum noise floor increase
- Minimal low-frequency noise impact
- Maintain time-domain ripple magnitude
- Spur-Free performance at every node → Integration and rail-sharing
- Works with both PWM and PFM Control

◆ Applications

- Direct powering of Analog/RF (e.g. PAs)
- Polar PAs and Class-D Amps
- Improvement in EMI