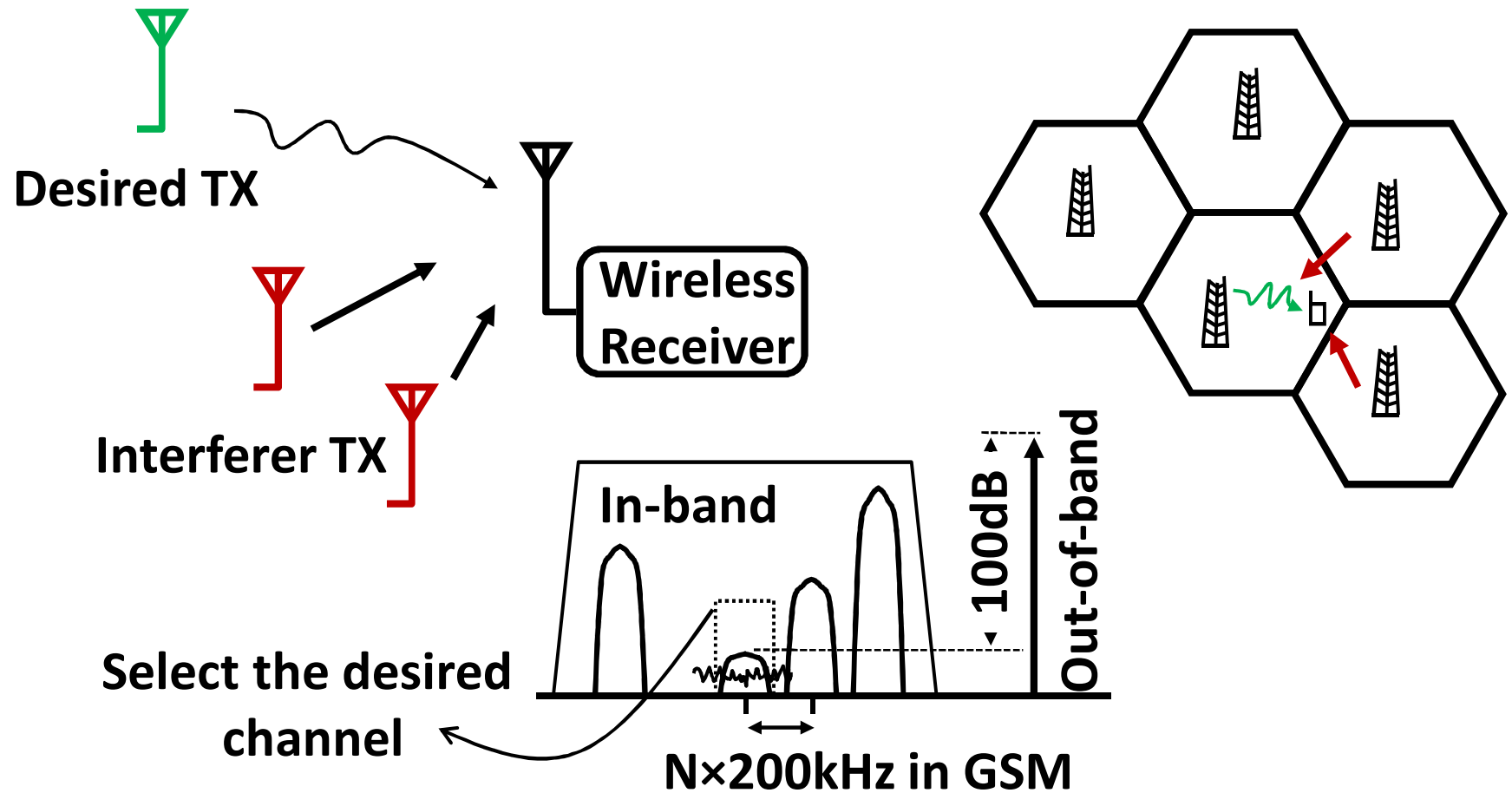


Transceivers Architectures for Mobile & Wireless Applications

Hooman Darabi

hdarabi@broadcom.com

Wireless Transceiver Challenges



- Stringent linearity, phase noise, selectivity on RX
- Stringent mask, far-out noise on TX


Receiver Requirements

- Receiver NF sets the sensitivity, range:

$$\text{Sensitivity} = -174 + \text{NF} + 10\text{Log}(\text{BW}) + \text{SNR}$$

$10\text{Log}(KT)$, dBm/Hz

Set by the standard

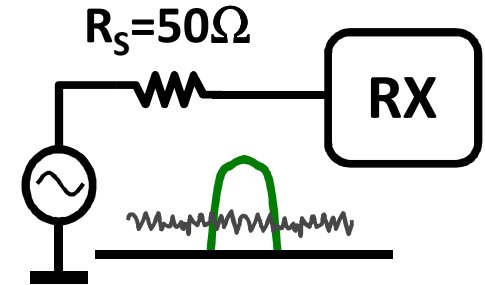

Blockers: In/Out-Band

- Small signal linearity:



- IIP₂, IIP₃

- Large signal linearity:

- Gain compression

- Harmonic mixing

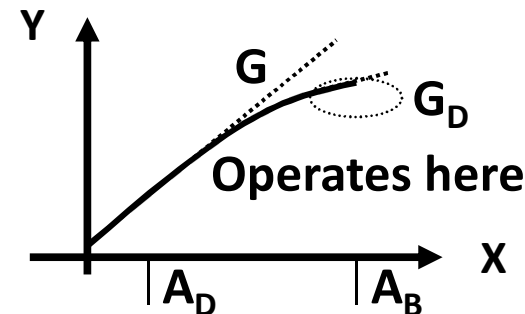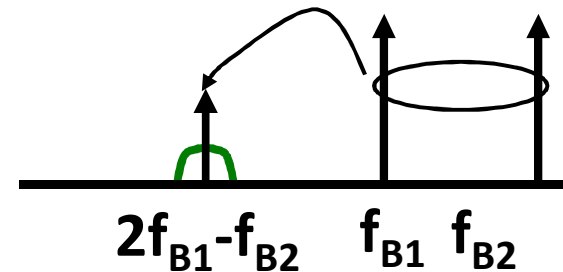- Reciprocal mixing: $\text{BNF} = 174 - P_B - \text{PN}$



Transmitter Requirements

RX Equivalent

NF:

Range


Blockers:

Co-existence


SNR:

Thru-put

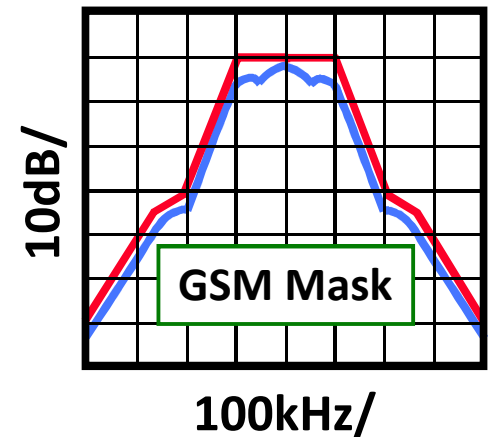- **Output power**
- **Spectrum Mask**
 - Sets the modulator quality
 - Sets the TX linearity
 - Determines TX phase noise
- **Far-out noise**
- **Modulation quality: PE, EVM**



- **Phase noise in transceivers:**

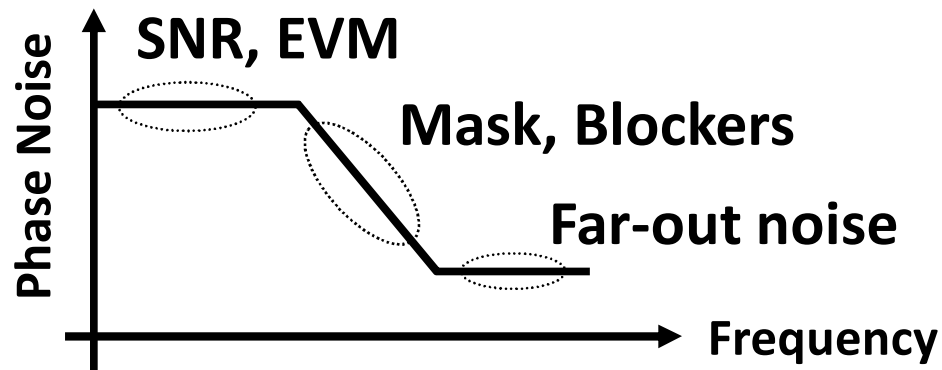


GSM/EDGE/WCDMA

- GSM/EDGE is TDMA, while 3G is CDMA. Both FDD.




- CDMA less sensitive to jammers:

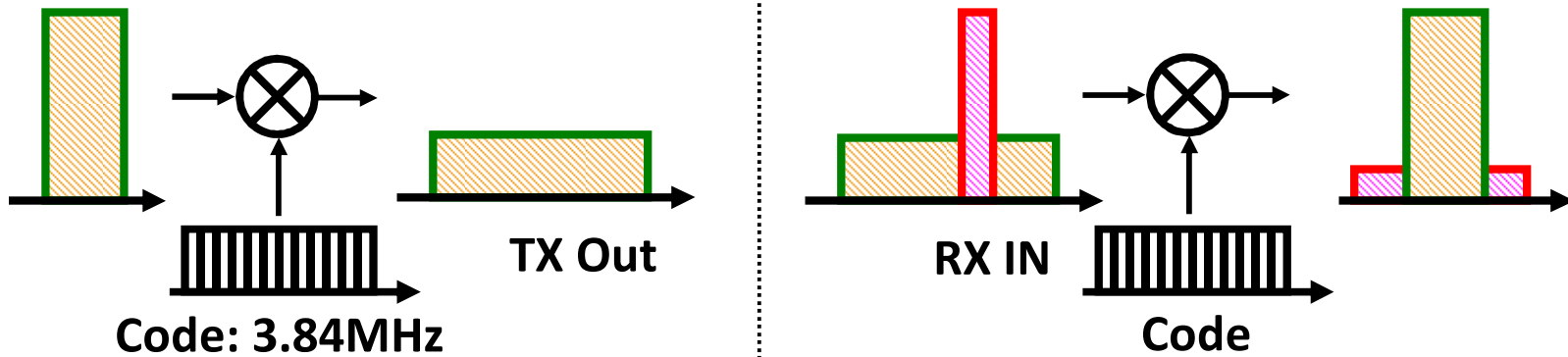

	Modulation	Bands	Thru-put	Challenges
GSM	GMSK: 270kbps	4	0.08	Blockers, TX mask, phase noise
EDGE	8PSK: 810kbps	4	0.236	
3G+ ¹	QPSK ... 64QAM	19	0.384-21	TX leakage


¹ HSPA, HSPA+, up to 21Mbps thru-put

3G Full-Duplex Problem

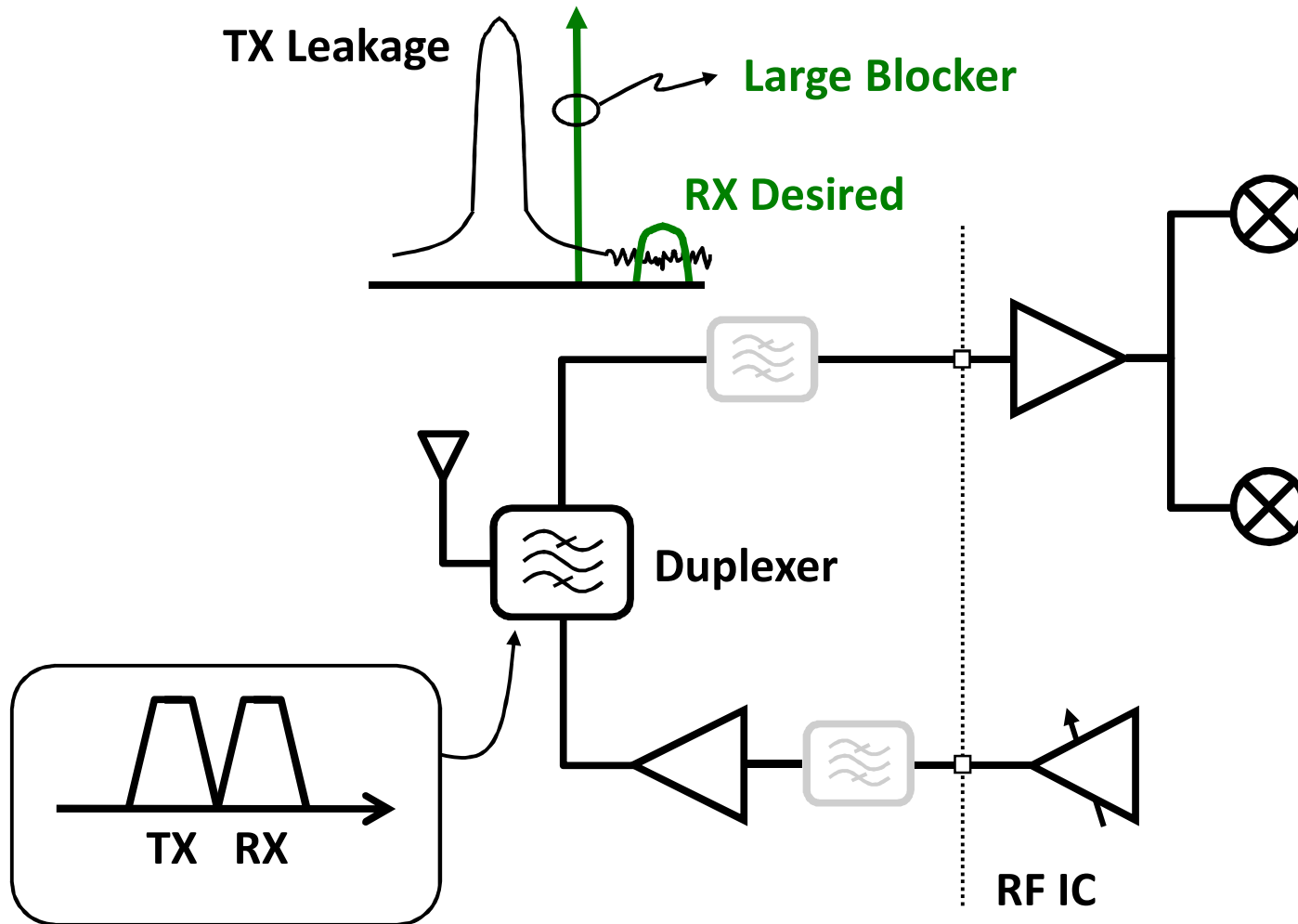

- Duplexer is a dual-band filter


Concept of MIMO

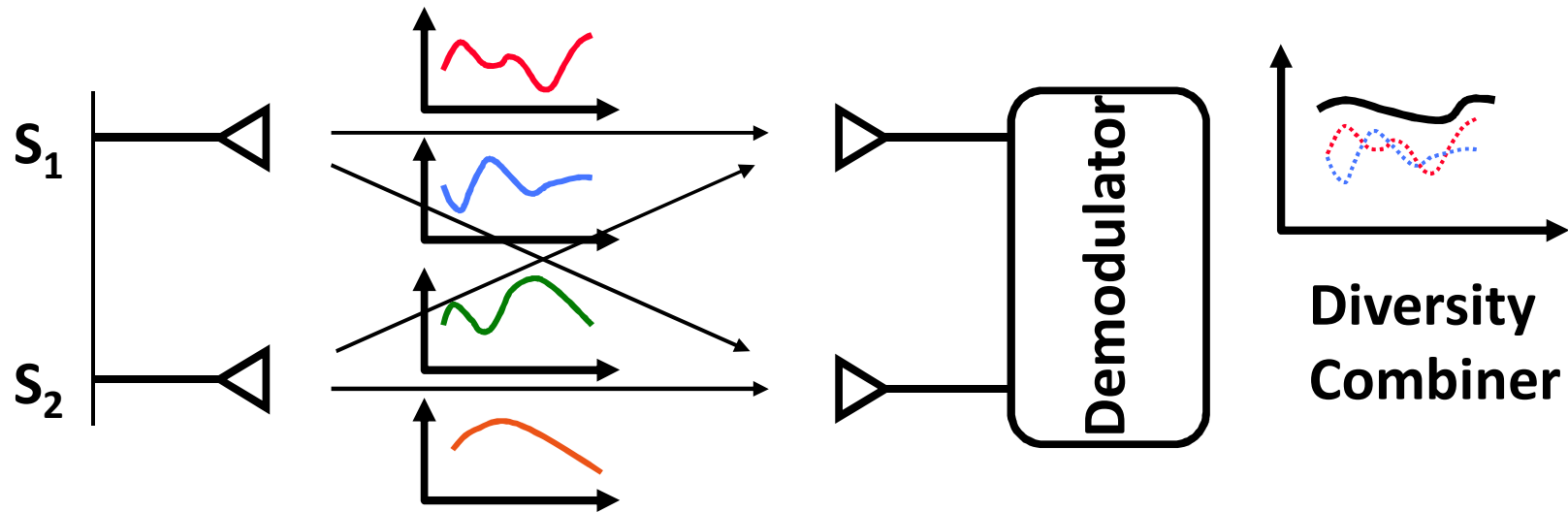

- **Signals received on multiple antennas combined to create a more benign composite channel**
 - Combined signal energy increases SNR
 - Variability across frequency reduces fading
- **Trading robustness for rate**

LTE Features

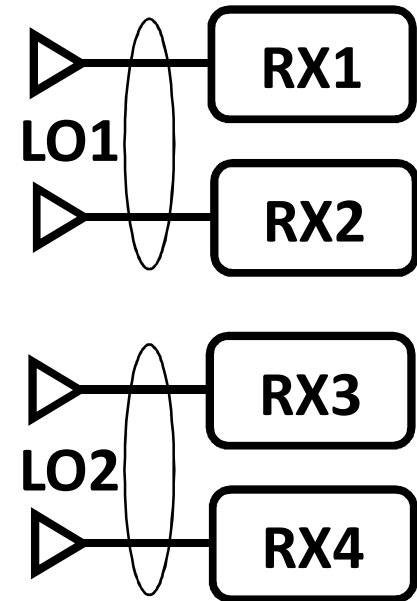- High data rate: DL 300Mbps, UL 75Mbps
- Flexible bandwidth and modes
 - Over 40 bands
 - 1.4 -20 MHz variable bandwidth
 - Flexible FDD, TDD, & FDD half duplex
- High mobility up to 120 km/h
- Carrier aggregation in LTE-A: 1Gbps



Contiguous



Non-Contiguous



Intra-Band



Band A




Band B

Inter-Band

WLAN Design Challenges

- **Bandwidth variability and detection**

- 20MHz up to 160MHz
- OFDM

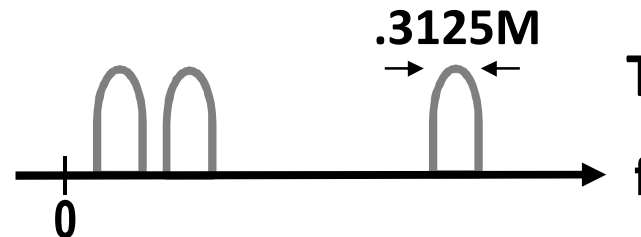

To help multi-path


- **TX PAR of 12dB for 64QAM**

- **High fidelity transmitters**



- -28dB EVM for 64QAM
- IQ and in-band phase noise

- **Receiver SNR and IQ imbalance**

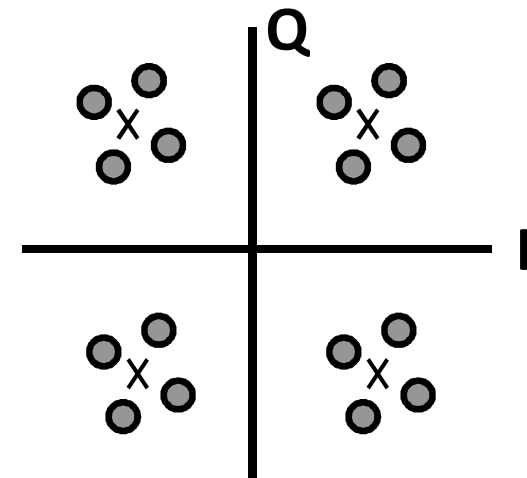- LO (fixed) & filters (variable over frequency)
- Sensitivity: -67dBm for .11g, SNR = 25dB: NF = 9dB



Ideal Transceiver

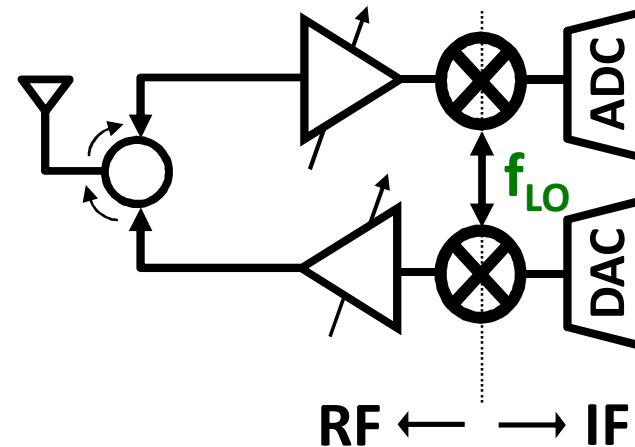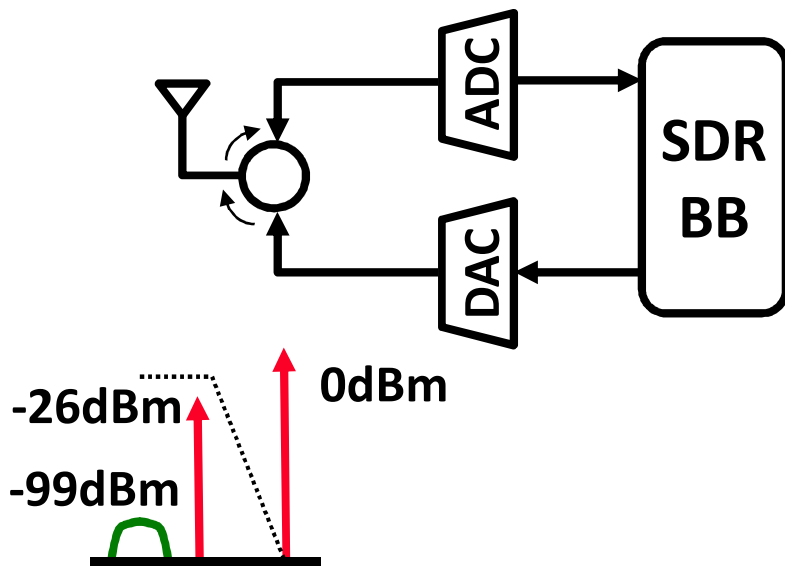



$$f_{IF} = f_{IN} - f_{LO}$$

- Filter only rejects out-of-band blockers
- In-band blockers require a high-resolution ADC
- Power hungry


- Invented by Armstrong in 1918
- *Frequency-conversion* relaxes IF signal processing
- Lower power

LO Harmonic Mixing Issue

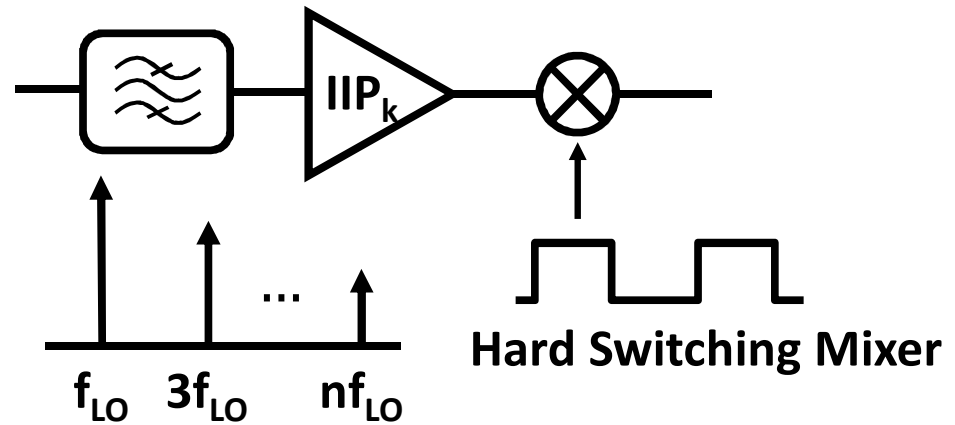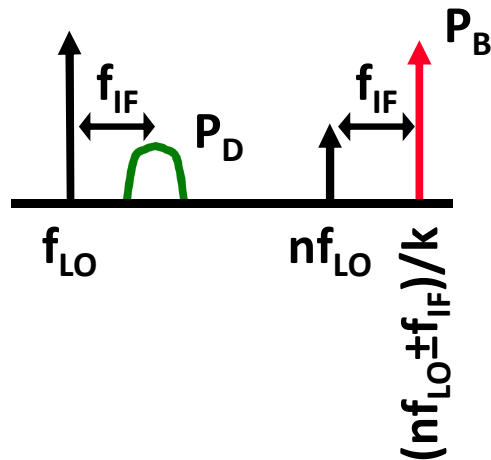
- In a perfectly linear RX, blockers still problematic



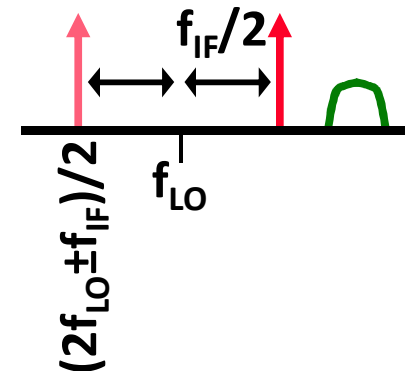- Sets LNA IIP_k , filter attenuation, range of acceptable IF
- Image: $n=k=1$, Only removed by filtering
- Half-IF: $n=k=2$, Differential helps




Super-Heterodyne Receiver

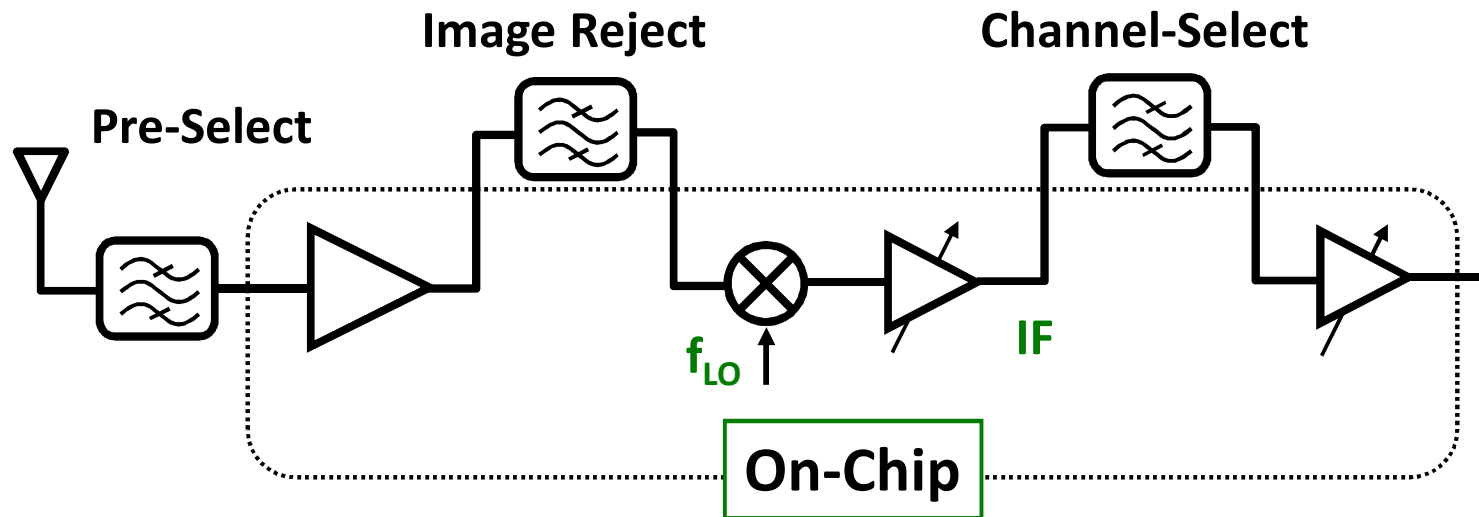

- Down-conversion relaxes the ADC
- High IF avoids DC offset & low frequency noise
- Needs external filters for image and other blockers

Zero-IF Receiver

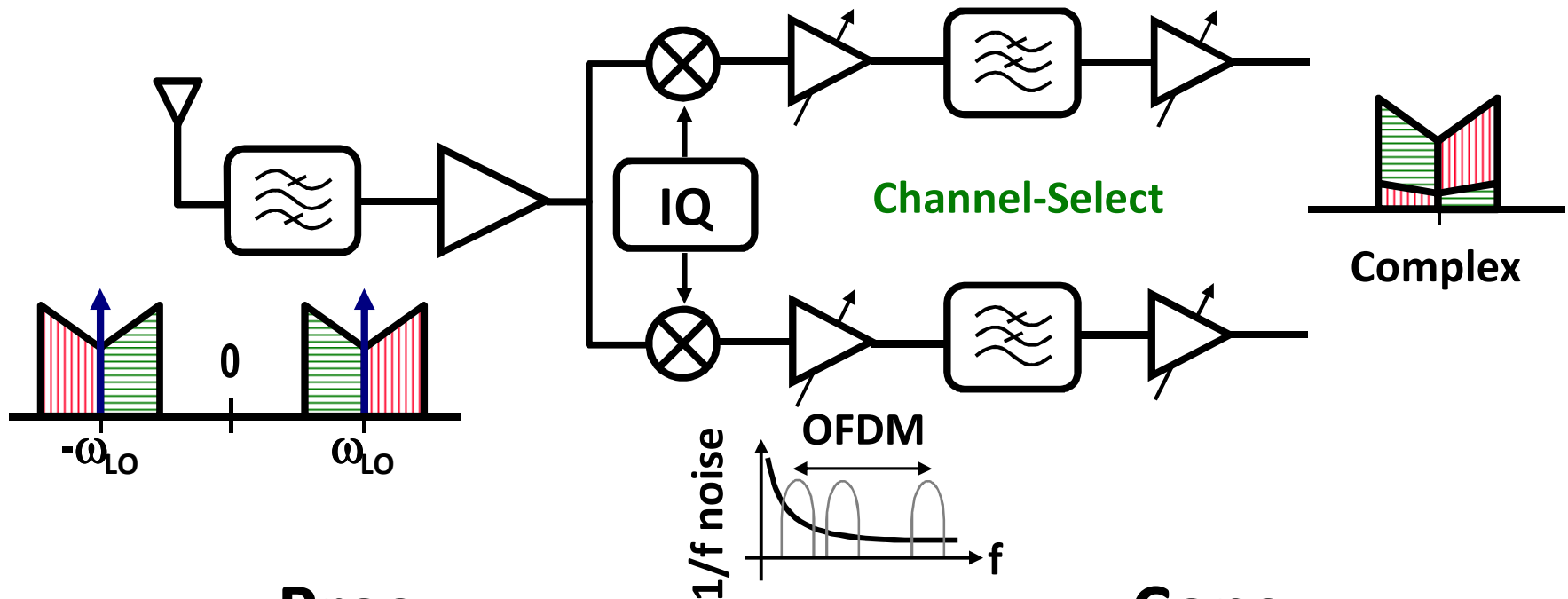

Pros


- Less severe image issue
- Channel selection on-chip
- Suitable for WB: LTE, WiFi

Cons

- Requires quadrature LO
- DC Offset, $1/f$ noise, IIP_2
- In band IRR


3G RX NF Requirement

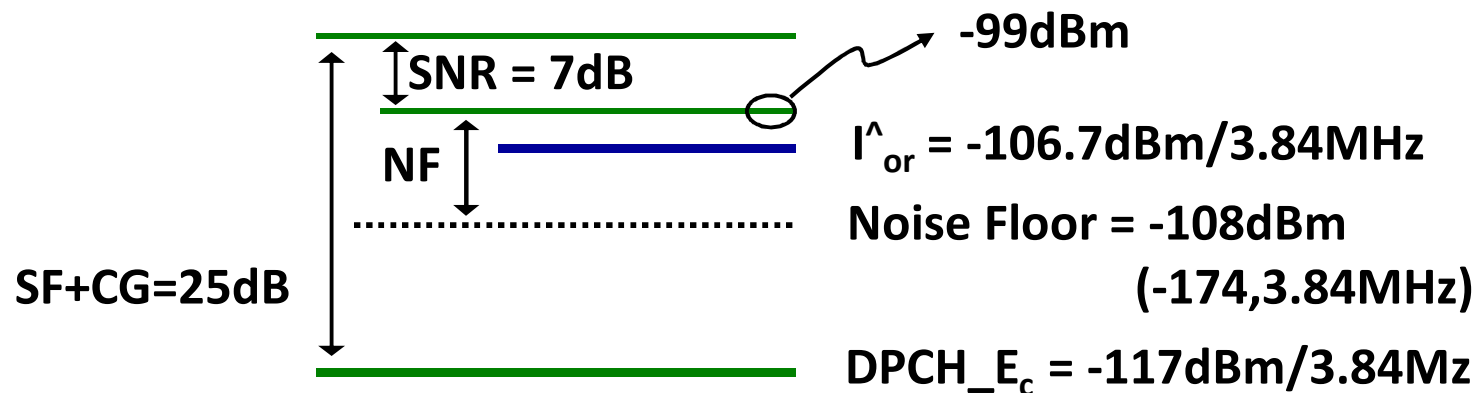- For 12.2kbps reference measurement, SF=128, -117dBm sensitivity, required NF = 9dB



- For a given duplexer, NF depends on:
 - RX thermal noise
 - RX 2nd-order nonlinearity
 - TX and PA noise at RX band

3G IIP₂ Requirements

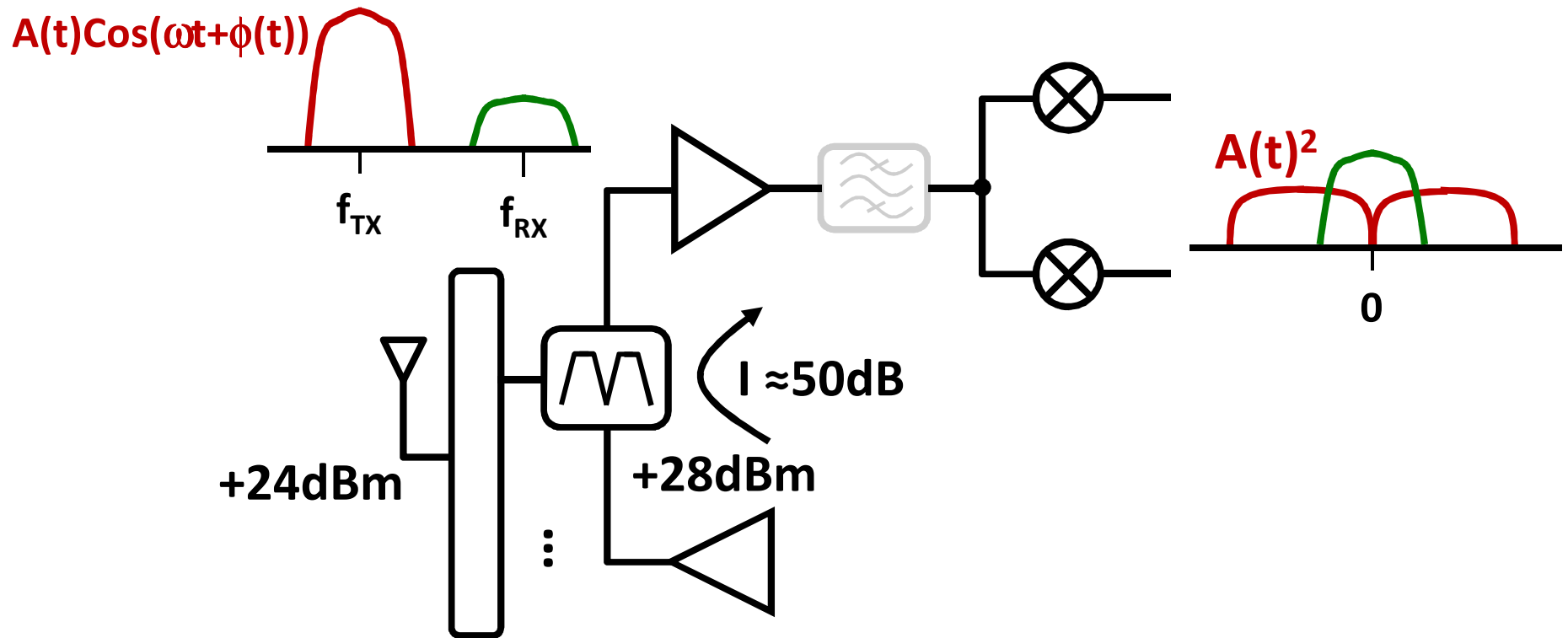


- TX leakage amplitude demodulated at zero IF
- In order not to affect sensitivity $IIP_2 > 50\text{dBm}$

$$IIP_2 = 2 \times (28\text{dBm} - I) - 13\text{dB} - -99\text{dBm} - 10\text{dB} = +52\text{dBm}$$

Desensitizes by 0.5dB

3G Out-of-Band IIP_3 Requirements

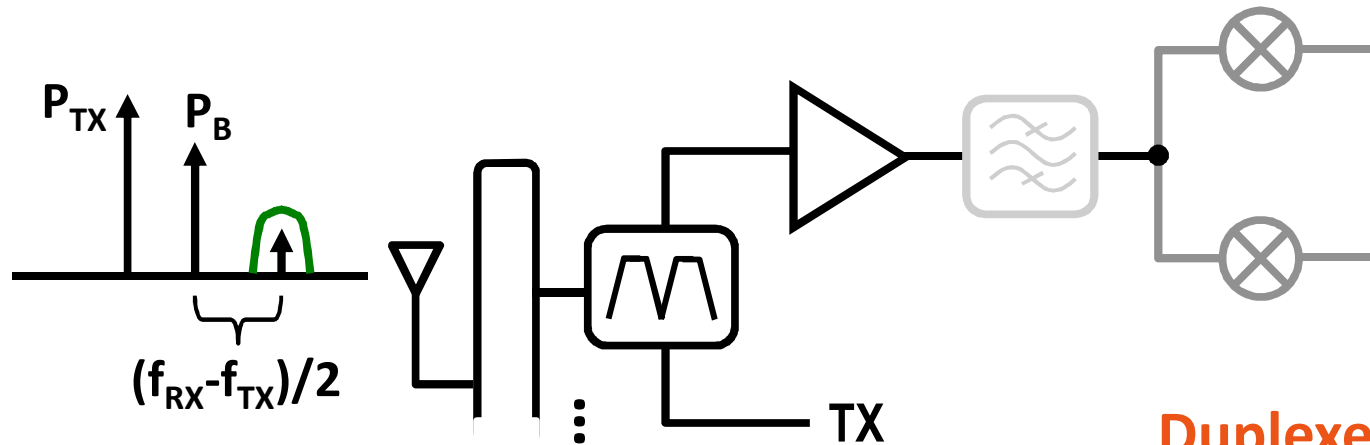


Duplexer Isolation: 50dB
Duplexer Filtering: 30dB

- Stringent IIP_3 due to TX leakage:

$$\underbrace{\text{Signal}}_{-99+3-5} = \underbrace{P_{TX}}_{28-50} + \underbrace{2 \times P_B}_{-15-30} - 2 \times IIP_3$$

- $IIP_3 = -5.5\text{dBm}$ at the LNA input
- Need room for TX noise, 2nd-order nonlinearity ...

Low-IF Receiver

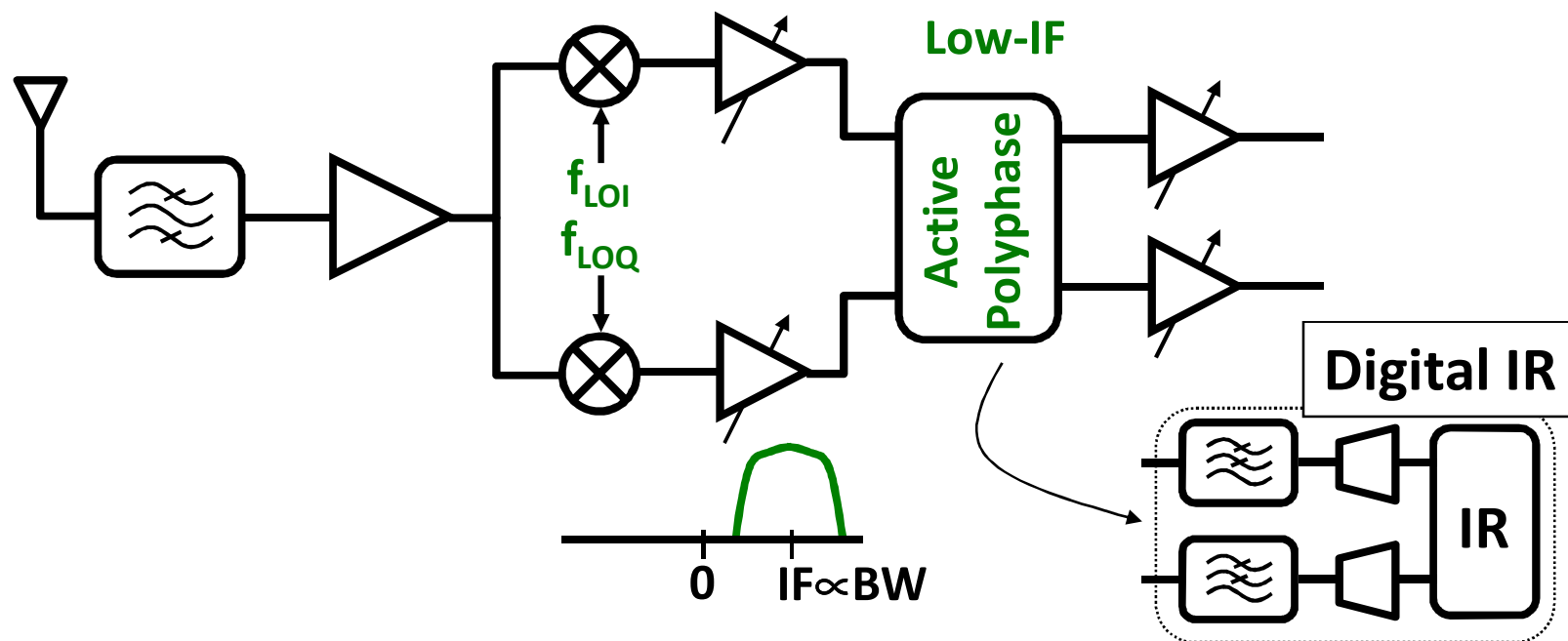

Pros


- IIP_2 , $1/f$ less problematic
- Image in-band
- Suitable for NB: GSM, BT

Cons

- Requires quadrature LO
- Higher IF, higher power
- Tighter IRR

GSM Noise Figure

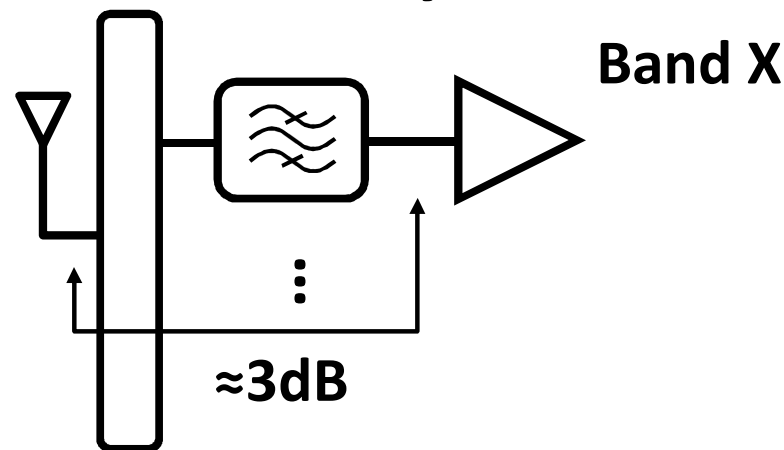
- The standard requires -102dBm
- Receiver NF sets the sensitivity:





$$\text{Sensitivity} = -174 + \text{NF} + \underbrace{10\text{Log}(\text{BW}) + \text{SNR}}_{\approx 59\text{dB for GMSK}}$$

- Most advanced receivers target for <-109dBm
- NF of < 3dB assuming *3dB loss at front-end*


Choice of IF: Adjacent Blockers

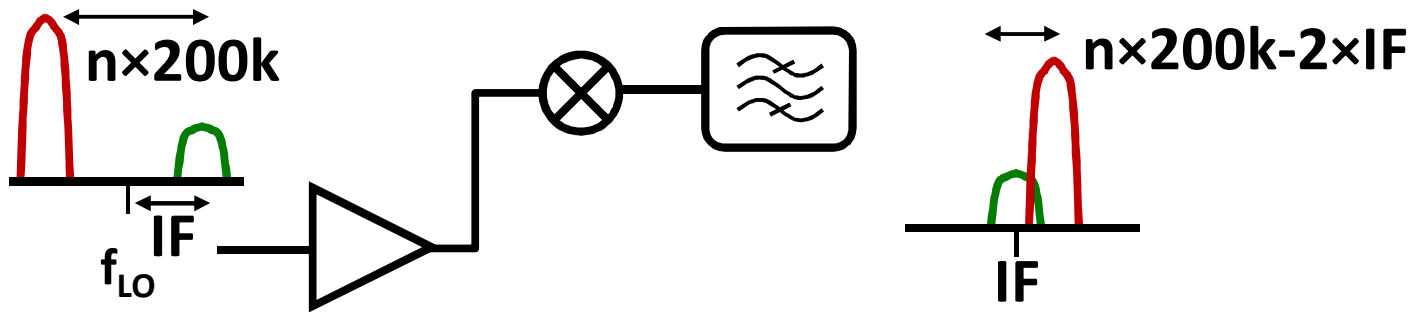


- Trade-off between $1/f$ noise, IIP_2 , ... vs. image rejection

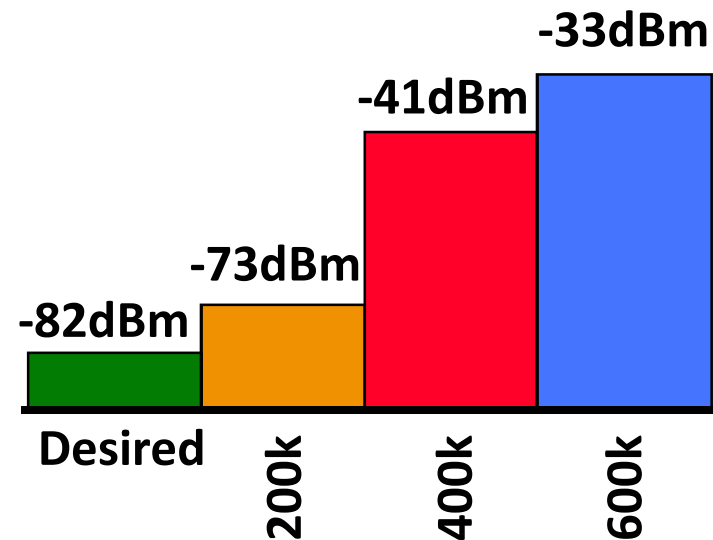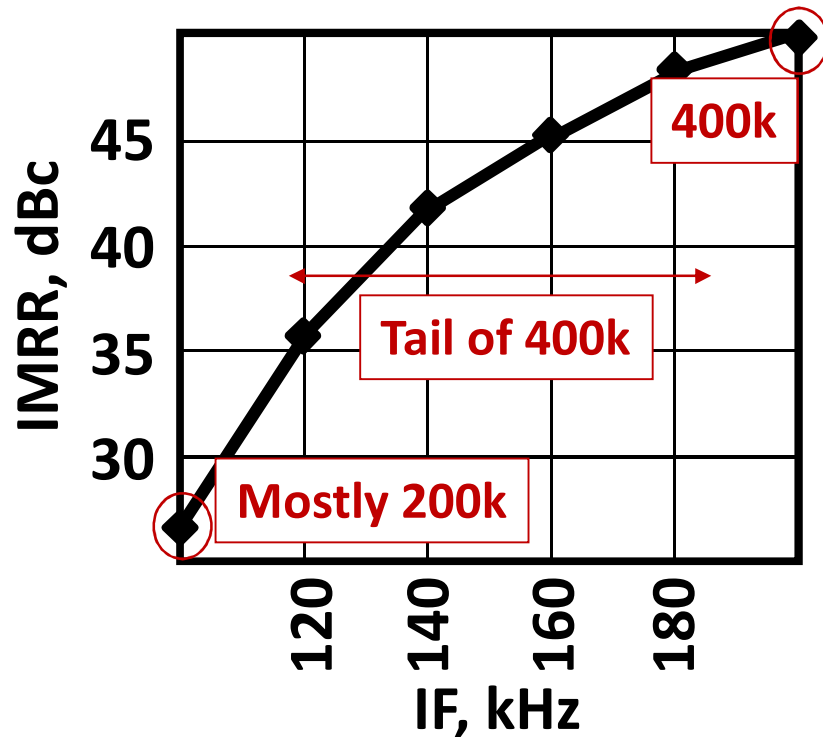

GSM In-Band Blocking Requirements

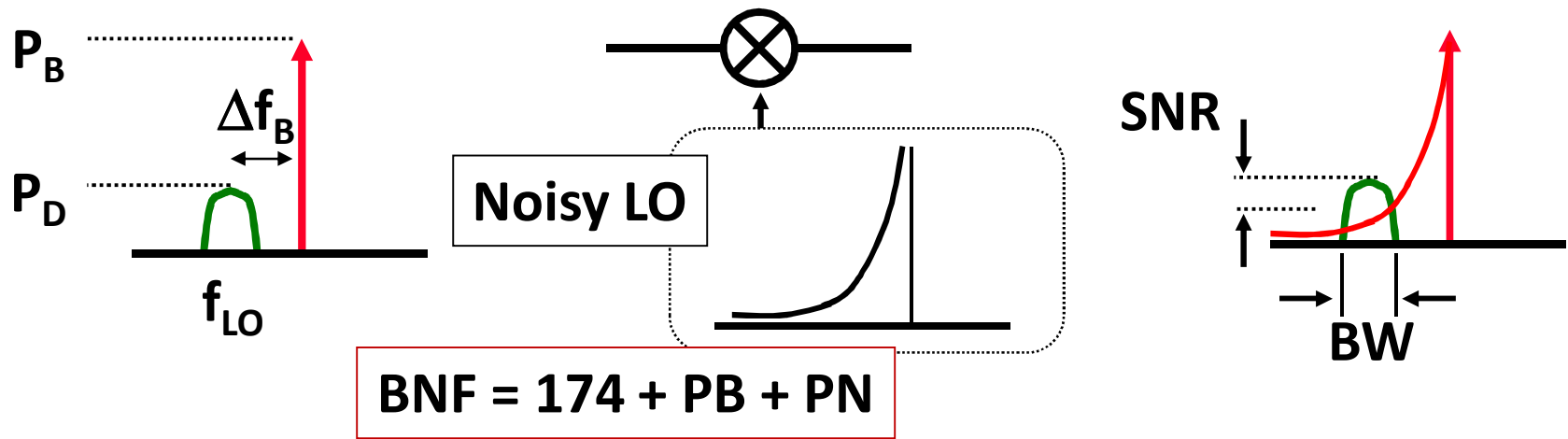


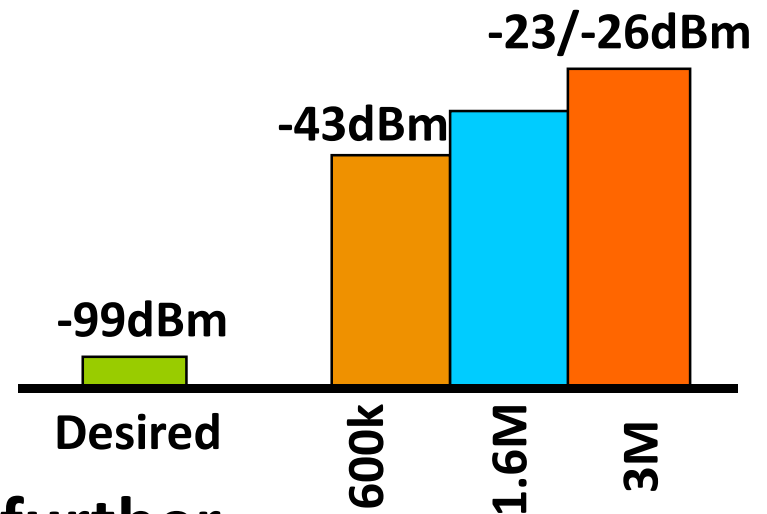- LO PN of -140dBc/Hz at 3MHz
- $BNF = 174 - 26 - 140 = 8\text{dB}$
- RX NF of 6dB: Total BNF $\approx 10\text{dB}$
- 3GPP NF requirement: 13dB
- Compression degrades the BNF further



– -26/-23dBm blocker can heavily compress the front-end

Dual-Conversion Receiver


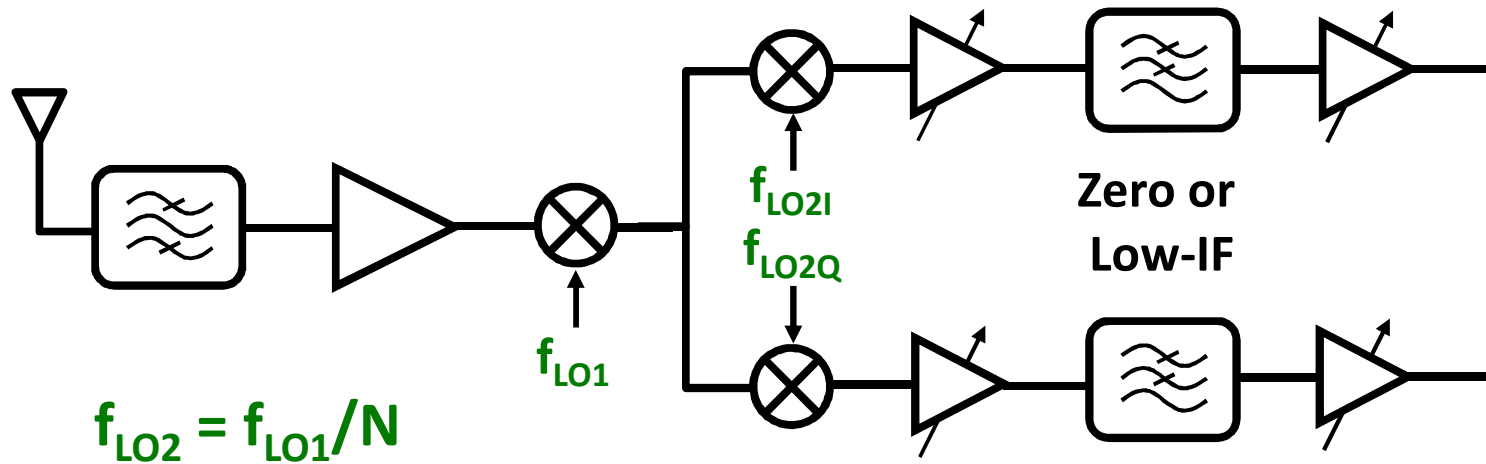


Sliding 1st IF = $f_{RF} / N+1$

- DC offset and 1/f noise issues less severe
- No high frequency quadrature LO
- Higher power due to 2 mixers in signal path
- First LO image


Gain Control & Receiver SNR

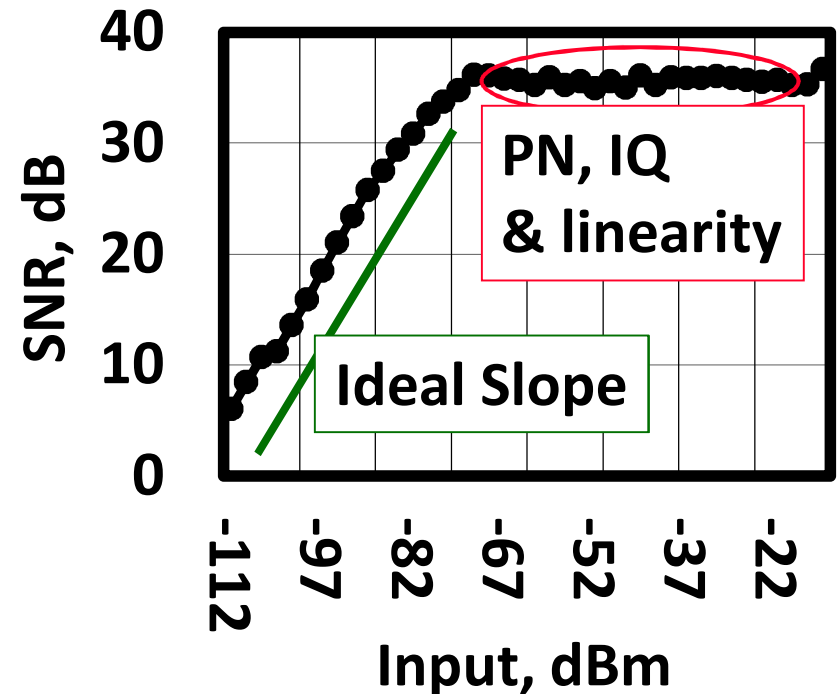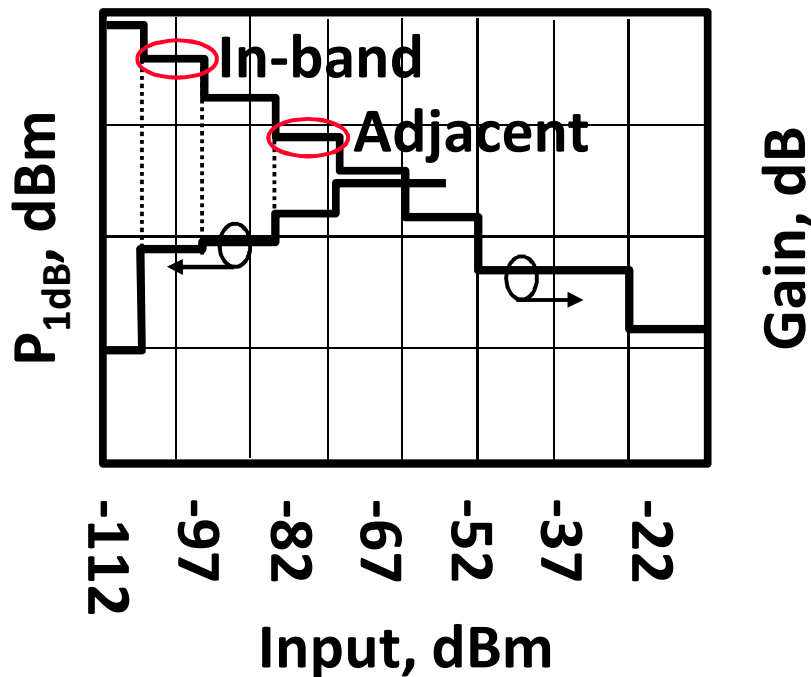- SNR determines through-put at high input powers




- *Front-end* gain reduction improves P_{1dB}
- But degrades SNR


ADC and Filtering

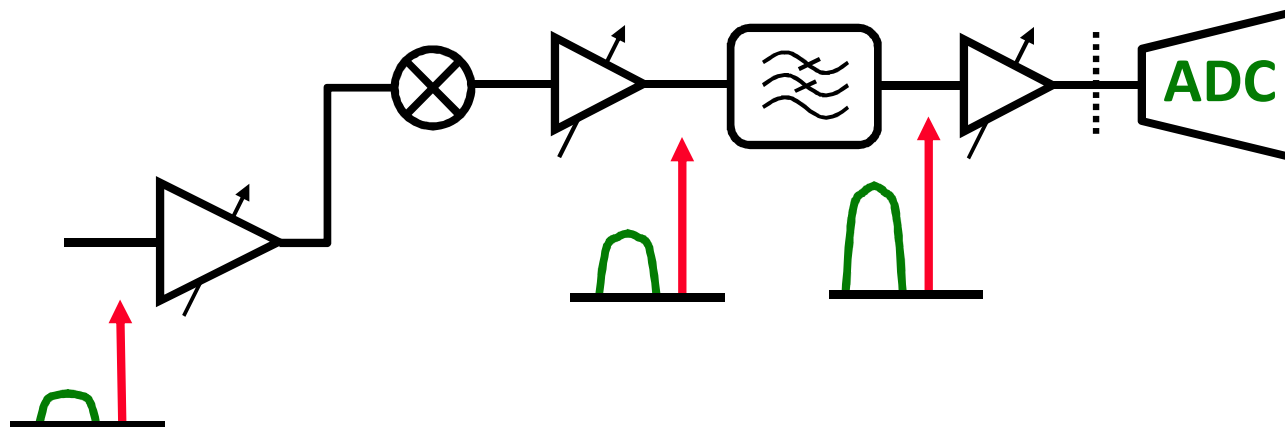

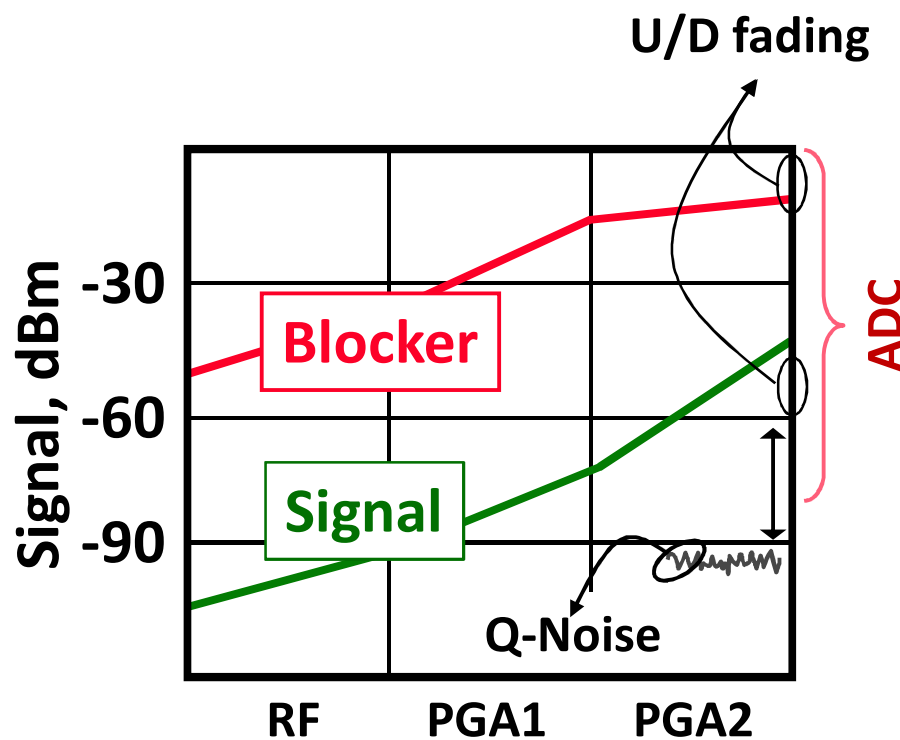- GC keeps desired signal close to ADC full scale
- Trade-off between filter & ADC
- ADC DR \gg receiver SNR




Example: 2G ADC Requirements

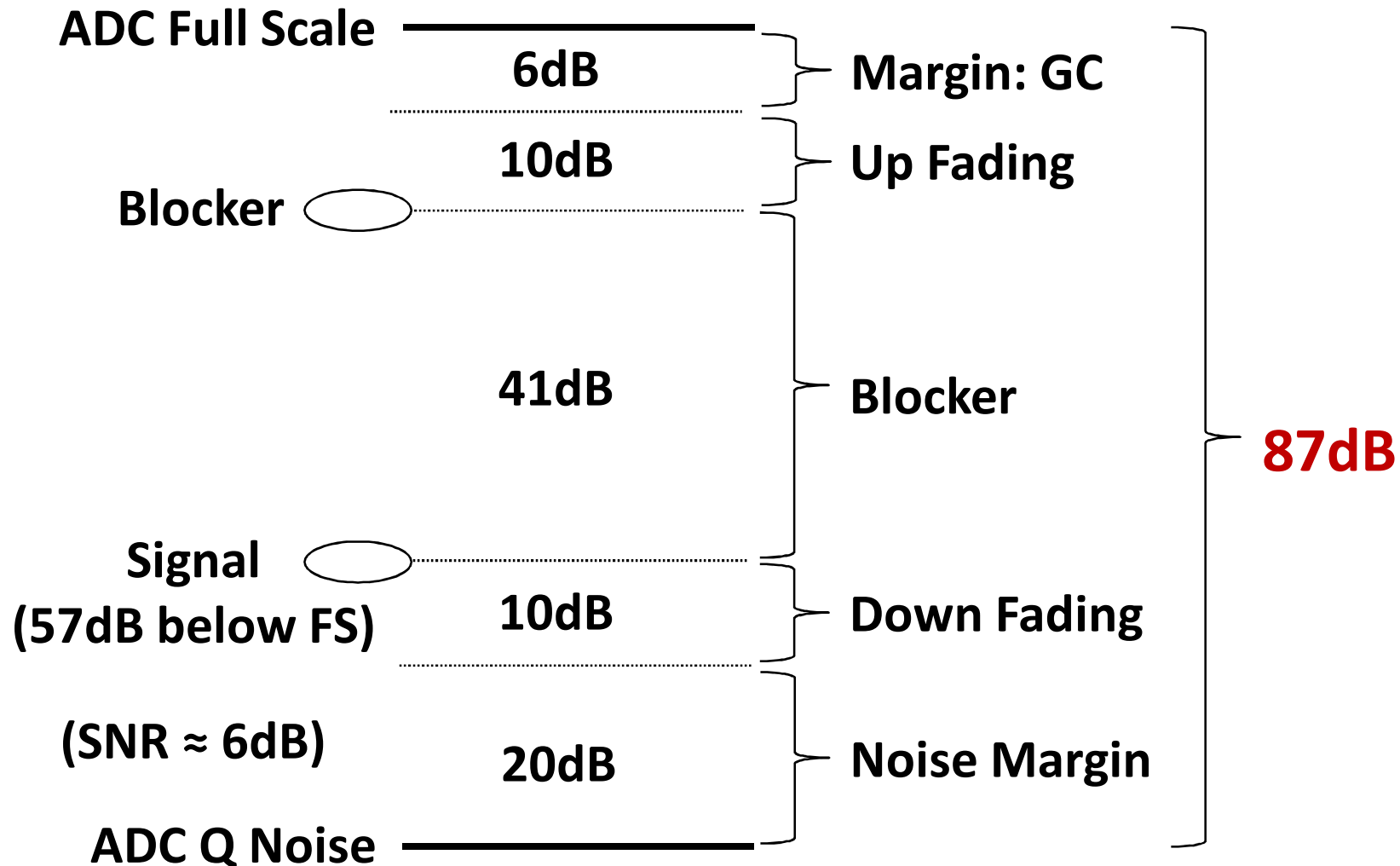

- -400kHz blocker dominant in low-IF



Out-of-Band Blocking Issue

GSM out-of-band blocker profile:

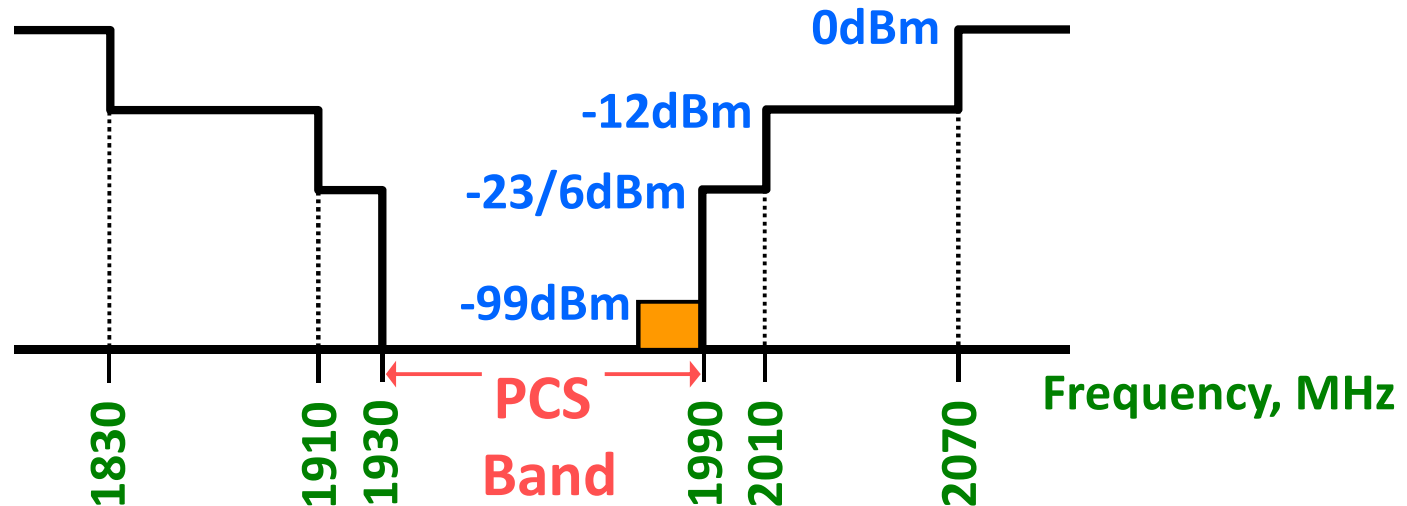




- External SAW filters attenuate out-of-band blockers
- The in-band blocker as high as -23dBm

Narrow-Band Filtering Concerns

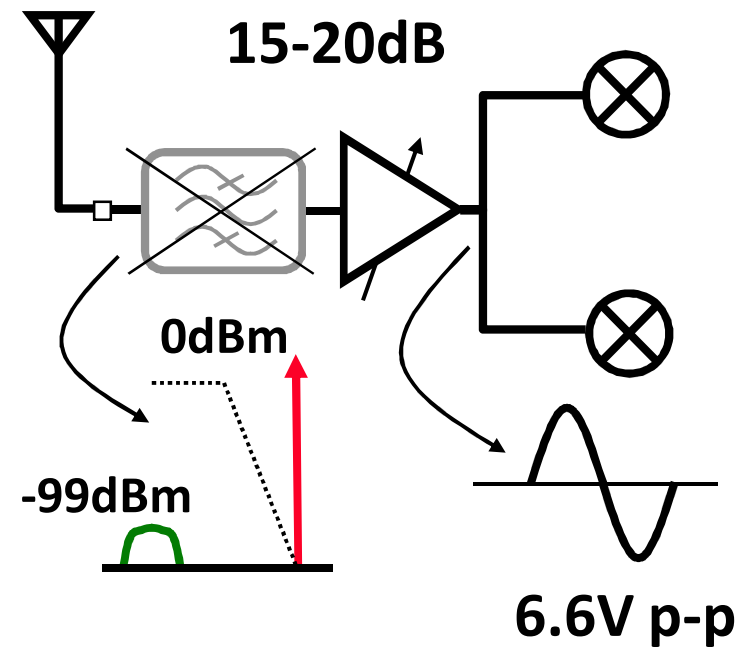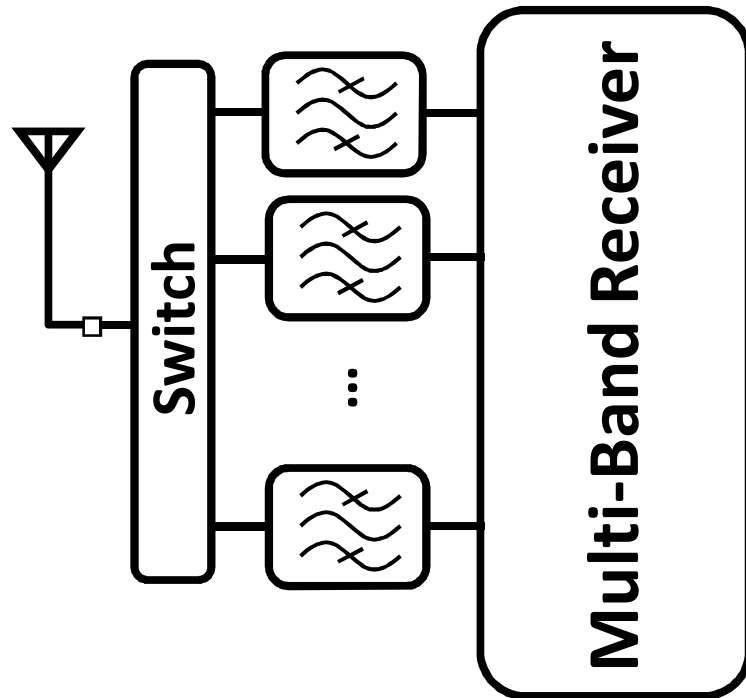

- Large blockers compress the receiver
- Impose stringent far-out phase noise
- External filtering is narrow-band and costly

Passive Mixers as N-Path Filters⁴

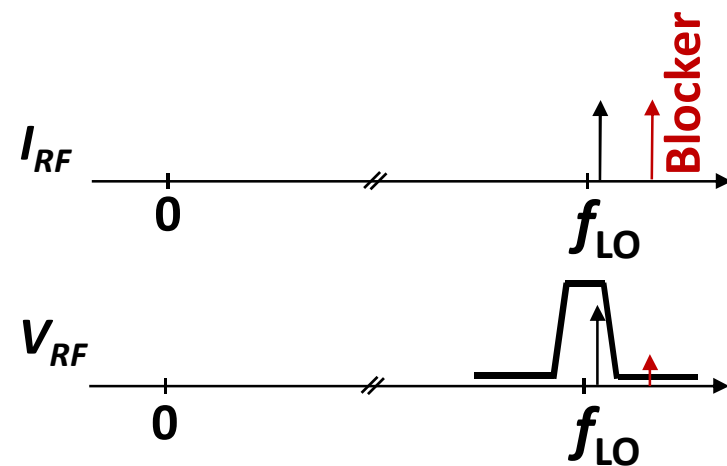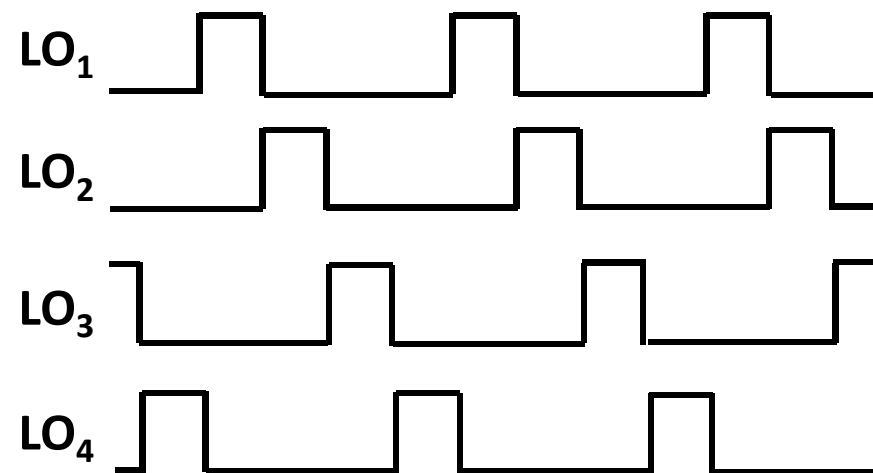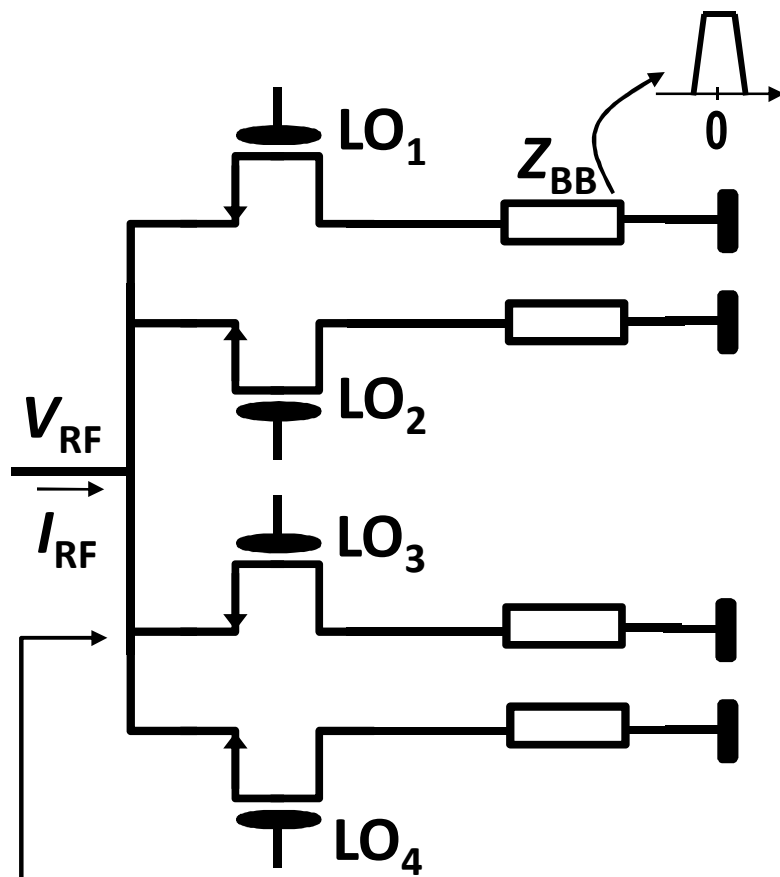


High-Q BPF from low-Q LPF

$$Z_{in}(s) \approx R_{SW} + \frac{2}{\pi^2} \{ Z_{BB}(s - j\omega_{LO}) + Z_{BB}(s + j\omega_{LO}) \}$$

⁴ L. Franks, Bell Syst. Tech. J., 1960



¹⁴ Mirzaei, TCAS 2010

Current-Mode Receivers

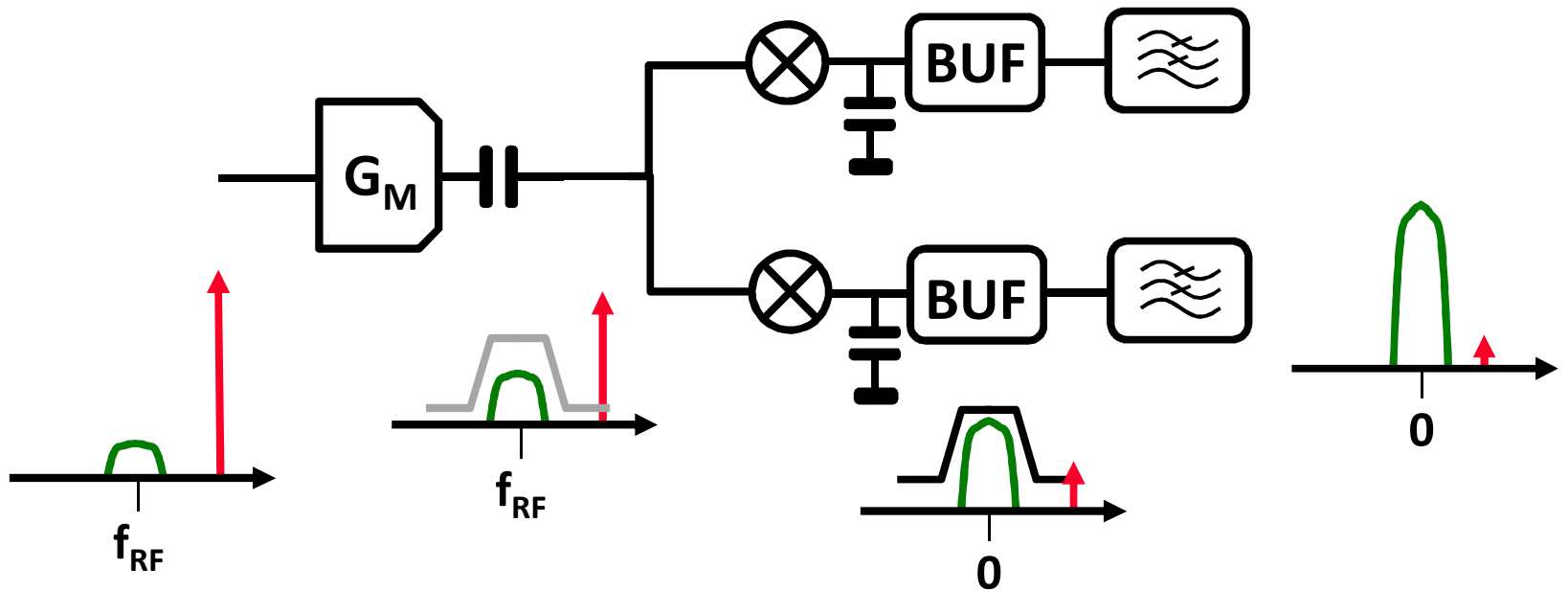

- Passive mixers to achieve high-Q filtering
- Current mode LNA: LNTA
- Enhance the blocker tolerance


Mixer-First Receivers

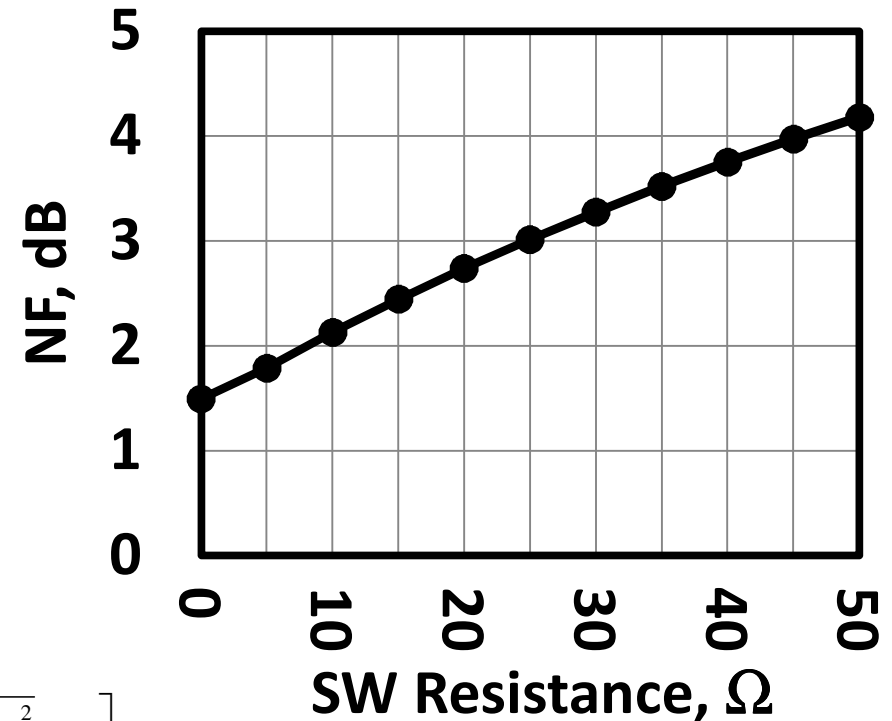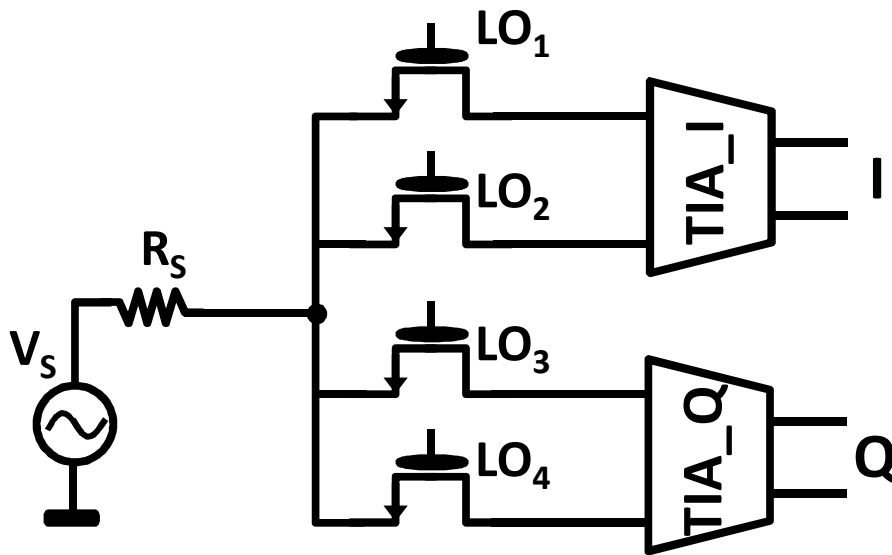

- For M phases:
$$F = \left[1 + \frac{r_{DS}(ON)}{R_S} + \frac{\overline{v_{bb}^2}}{M(4KTR_S)} \right] \times N_{Aliasing}$$
- At high frequency noise aliasing degrades NF significantly
- NF > 4dB in practice at GHz frequencies



Noise Cancelling Receivers

Noise and linearity bottleneck

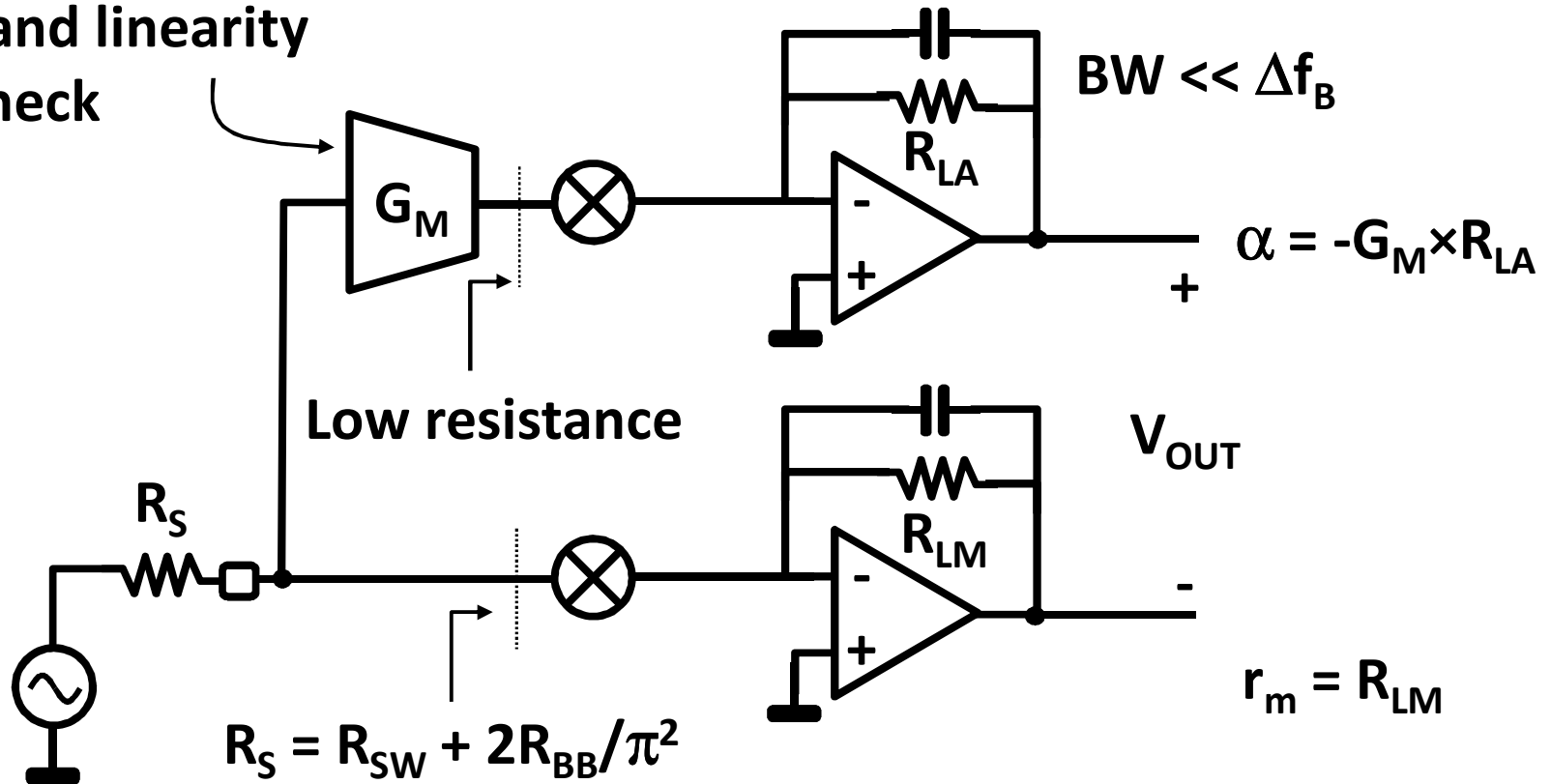

- Low noise and linear
- No Balun required


Over-Sampling Mixer Architecture

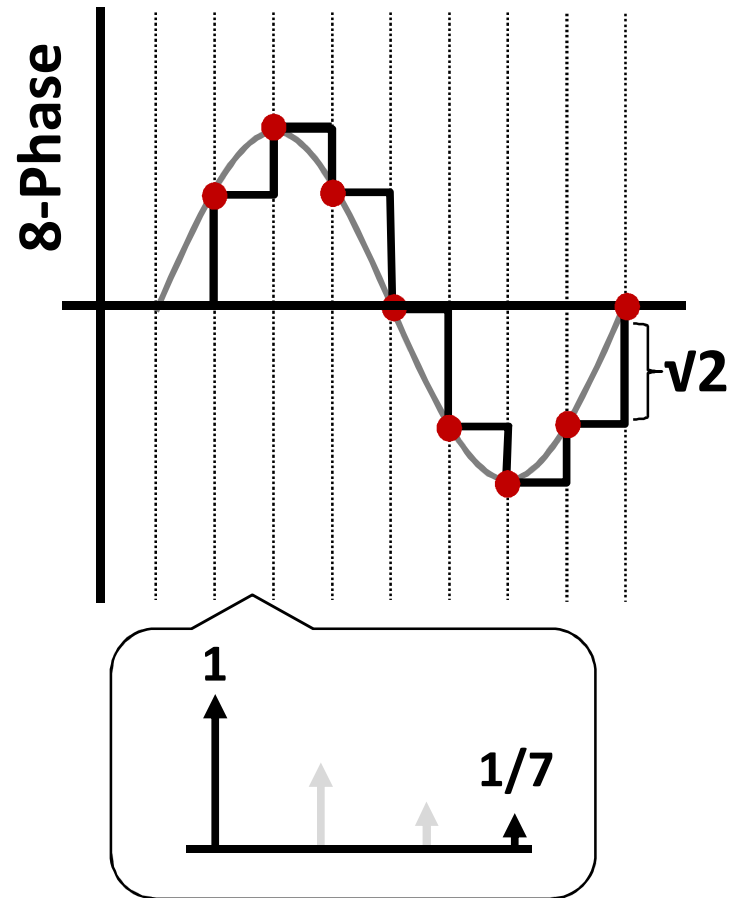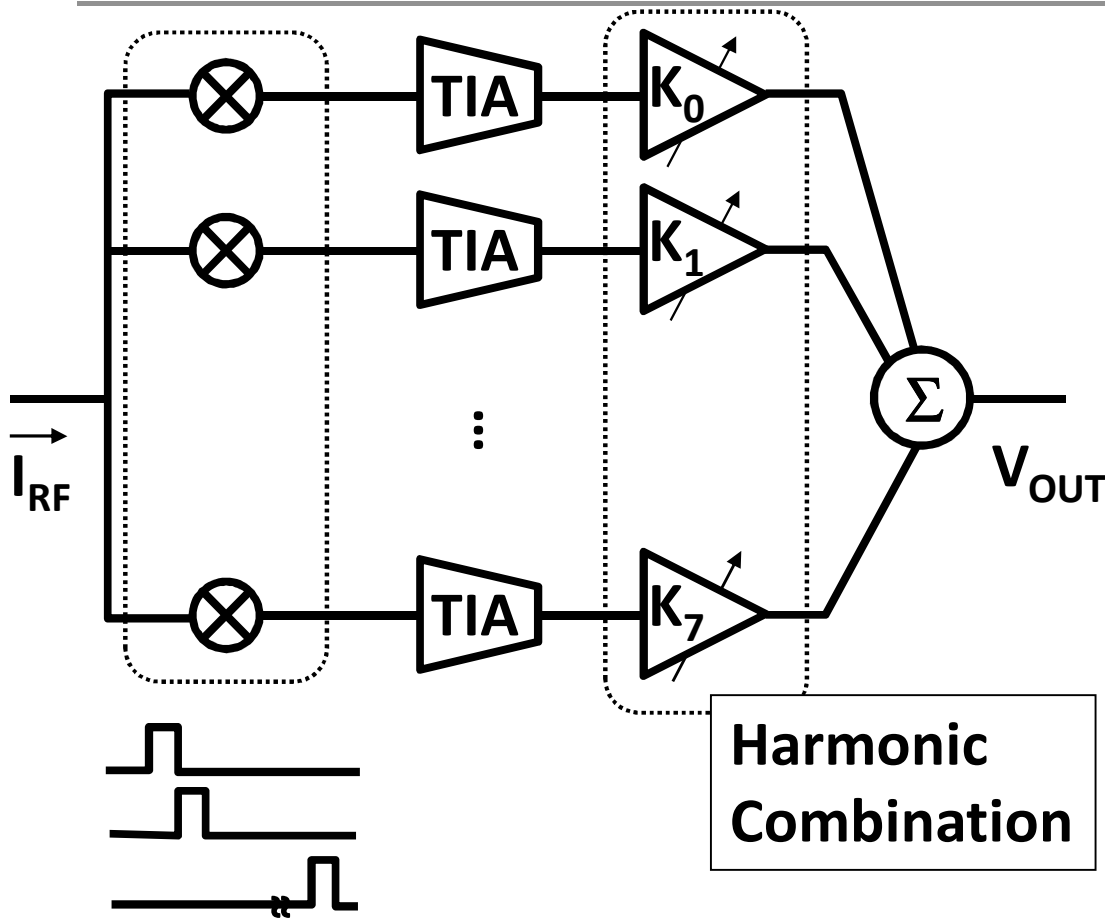


- Square-wave LO harmonically rich
- Synthesizes arbitrary 8-phase LO:

$$V_{OUT} = i_{RF}(t) \sum_{x=0}^7 K_x sw\left(t - \frac{x}{8T}\right)$$

Case Study: NC SDR Receiver

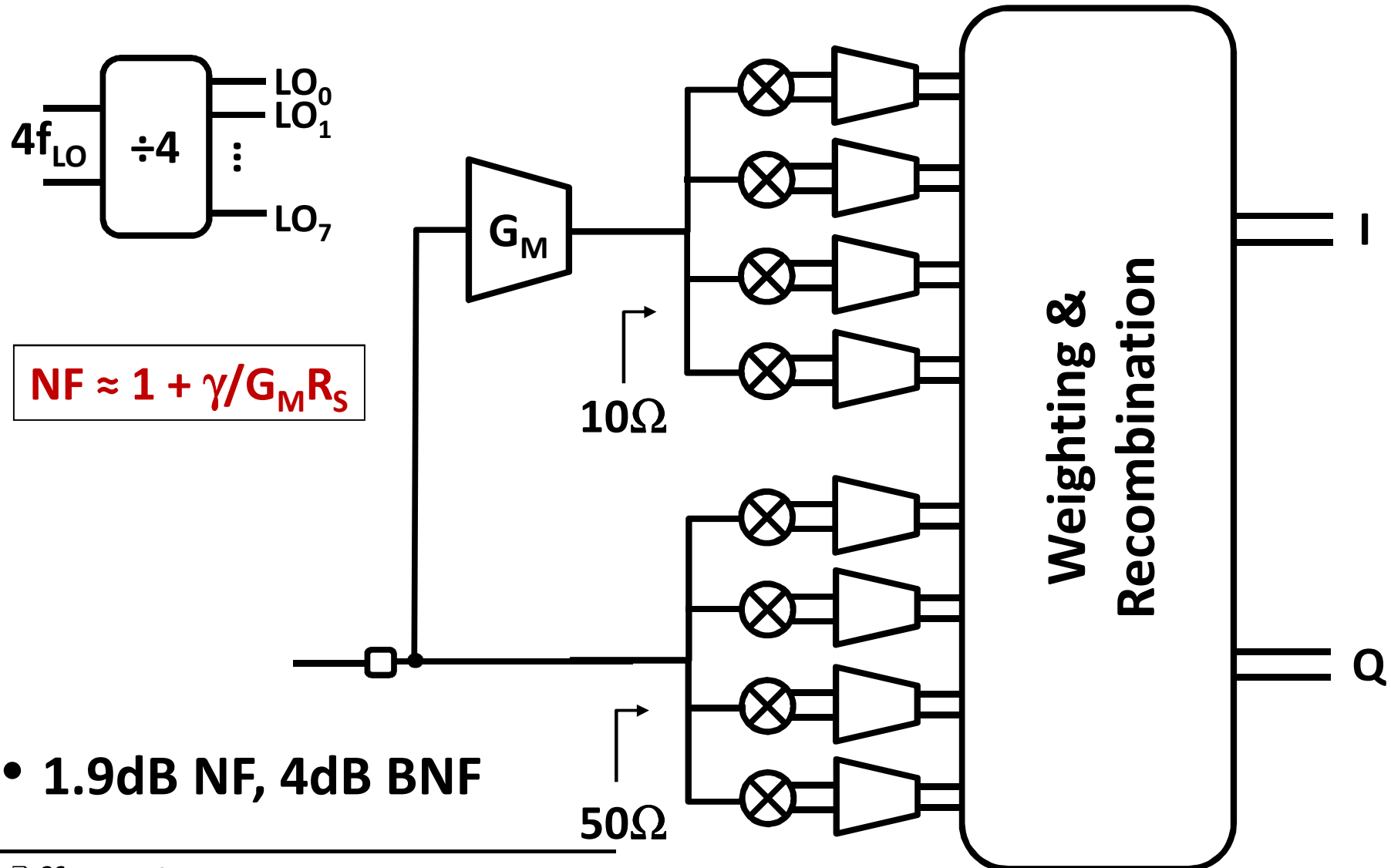

Direct-Conversion Transmitters

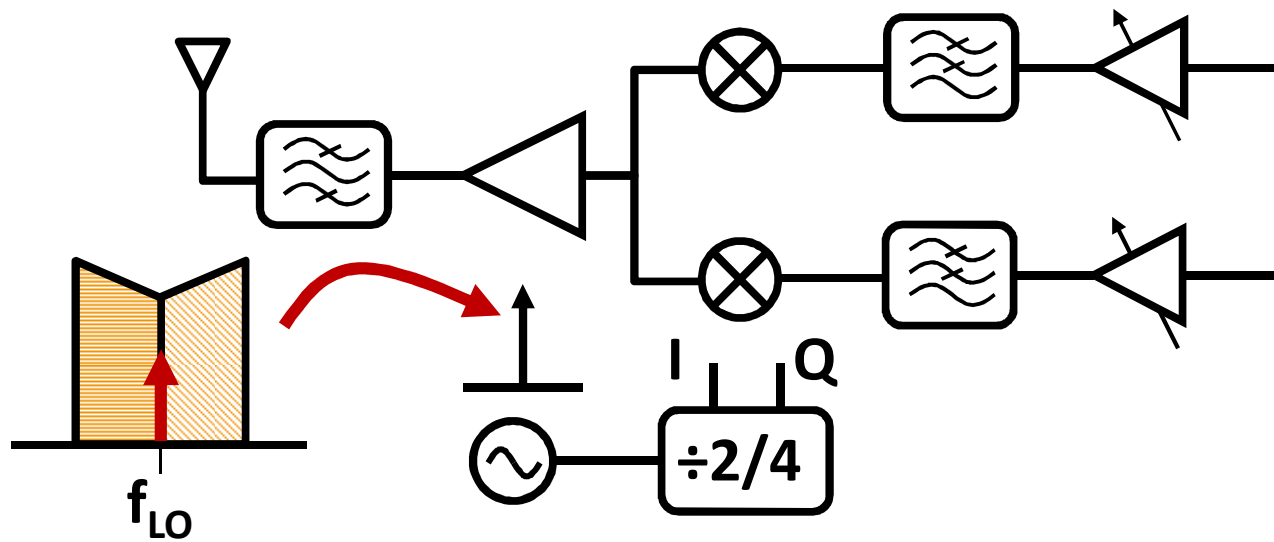


Pros

- Low power
- Versatile
- Highly integrated

Cons

- Suffers from pulling
- LOFT, IQ matching
- Far-out noise

Dual-Conversion Transmitters

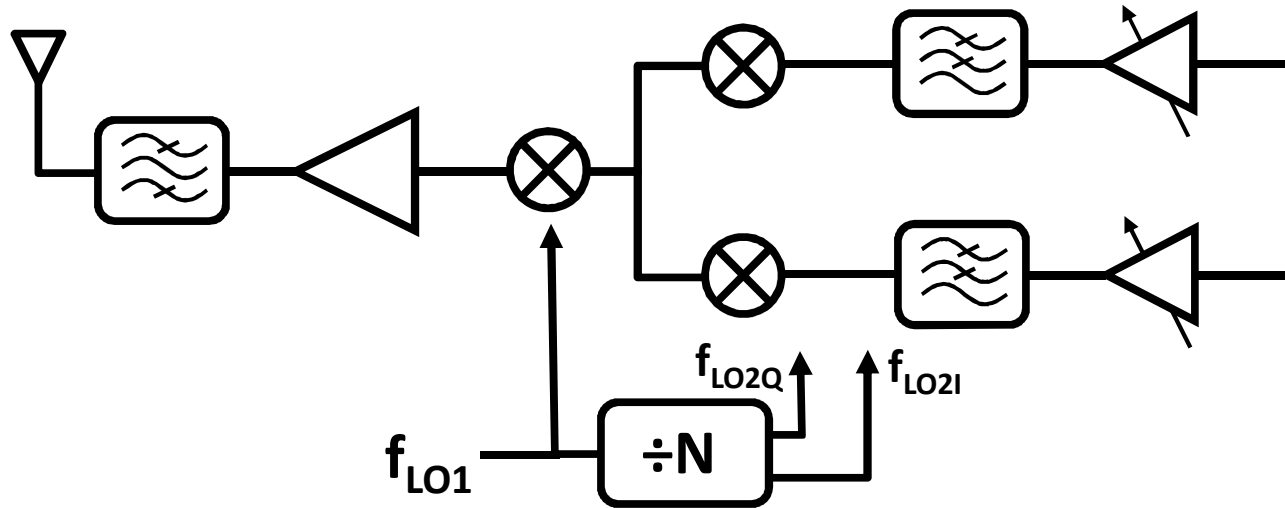

Pros


- No pulling
- LOFT/IR less problematic
- Sliding IF

Cons


- Higher power
- More complex filtering needed

Third Harmonic Folding

23 Mirzaei, TCAS 2011

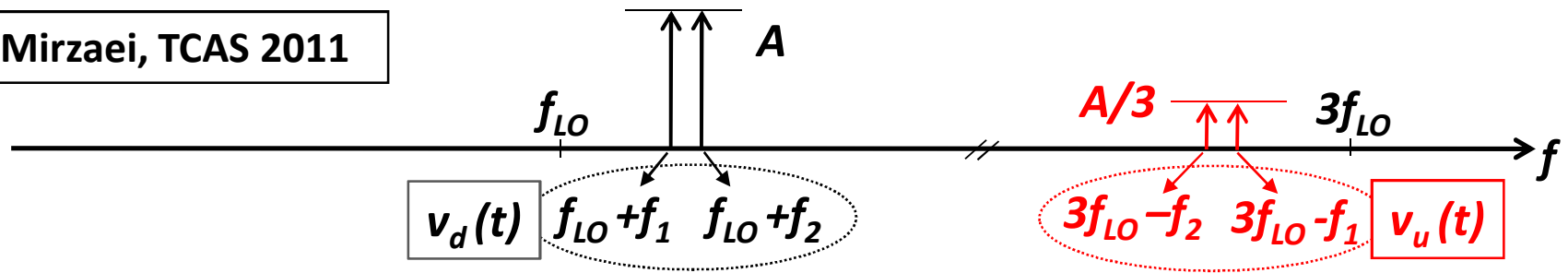

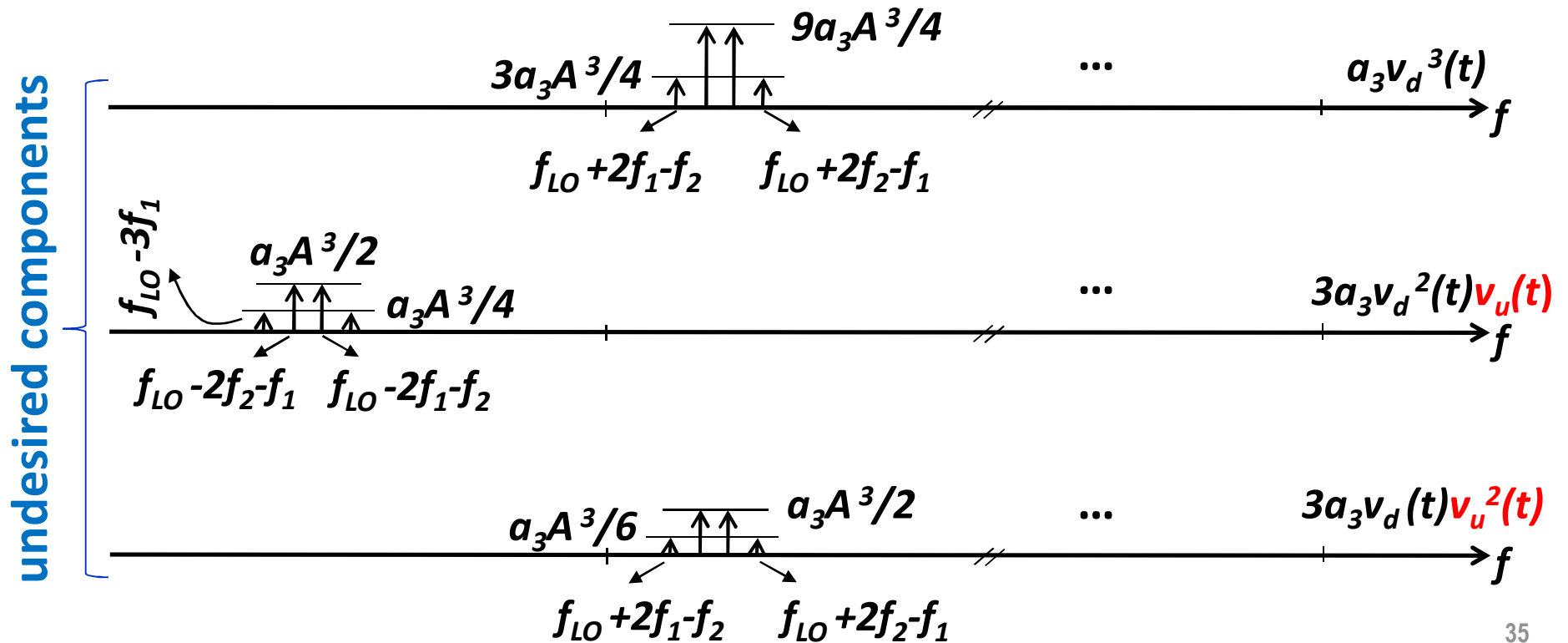PA driver nonlinearity: $y = a_1x + a_3x^3$




WCDMA TX General Requirements

- -160dBc/Hz RX-band noise results in 0.5dB NF degradation


Noise Floor = $28-50-160 = -182\text{dBm/Hz}$

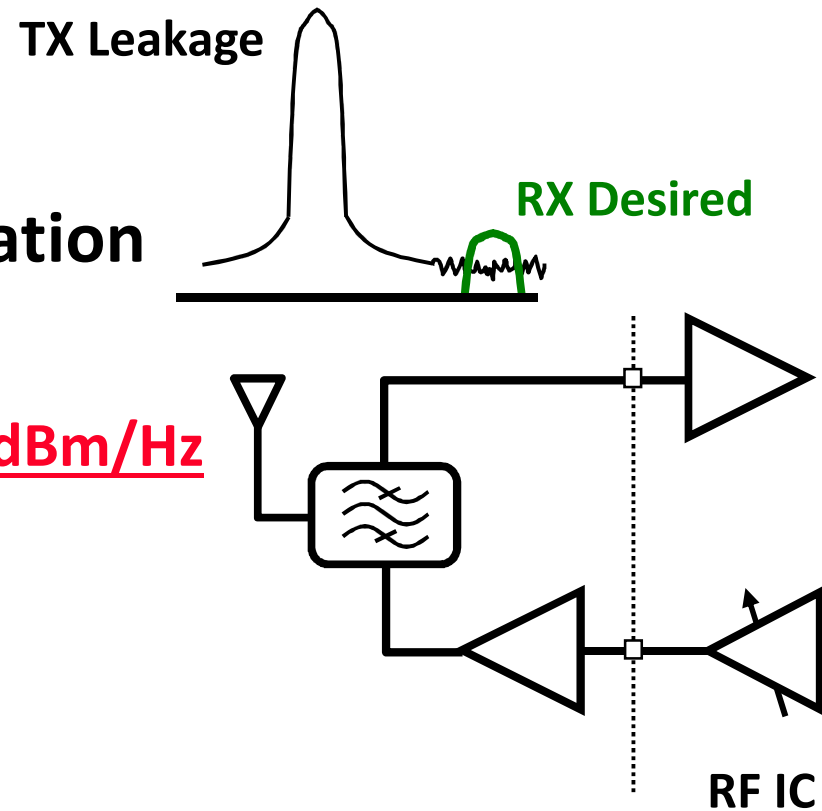- ACLR1 at 5MHz: -33dBc
- ACLR2 at 10MHz: -43dBc
- EVM: 19%




WCDMA TX EVM

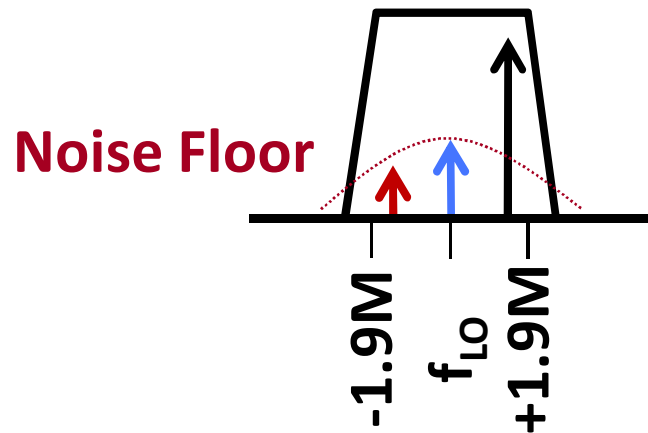- In linear TX, IQ imbalance, LOFT & PN dominate


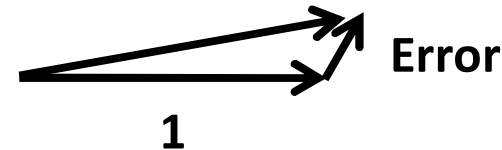
$$EVM (\%) = \sqrt{10^{\frac{IQ}{10}} + 10^{\frac{LOFT}{10}} + 10^{\frac{PN}{10}}}$$





- 40dBc equal contribution results in $\sqrt{3} = 1.7\%$ EVM
- Baseband filter ripple adds further
- Typical RF IC EVM around 3%

WCDMA TX ACLR


- Nonlinearity results in ACLR

- Depends on PAR, modulation

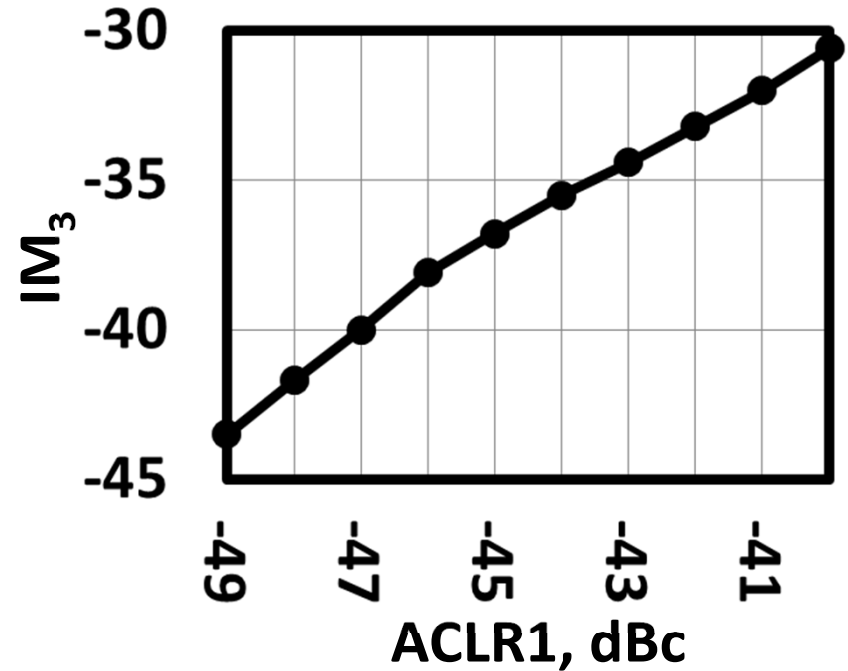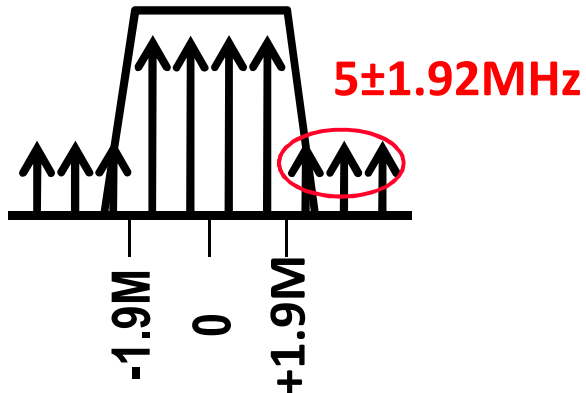



- ACLR1 requirement of -33dBc at the antenna

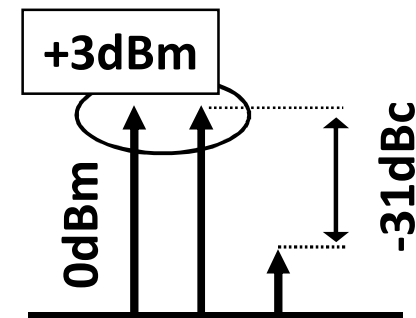- PA WC -37dBc (optimized for efficiency)
 - 2dB production margin
 - Leaves RFIC WC of -40dBc




OIP₃ = 15.5dBm

Folding Impact on PAD Linearity

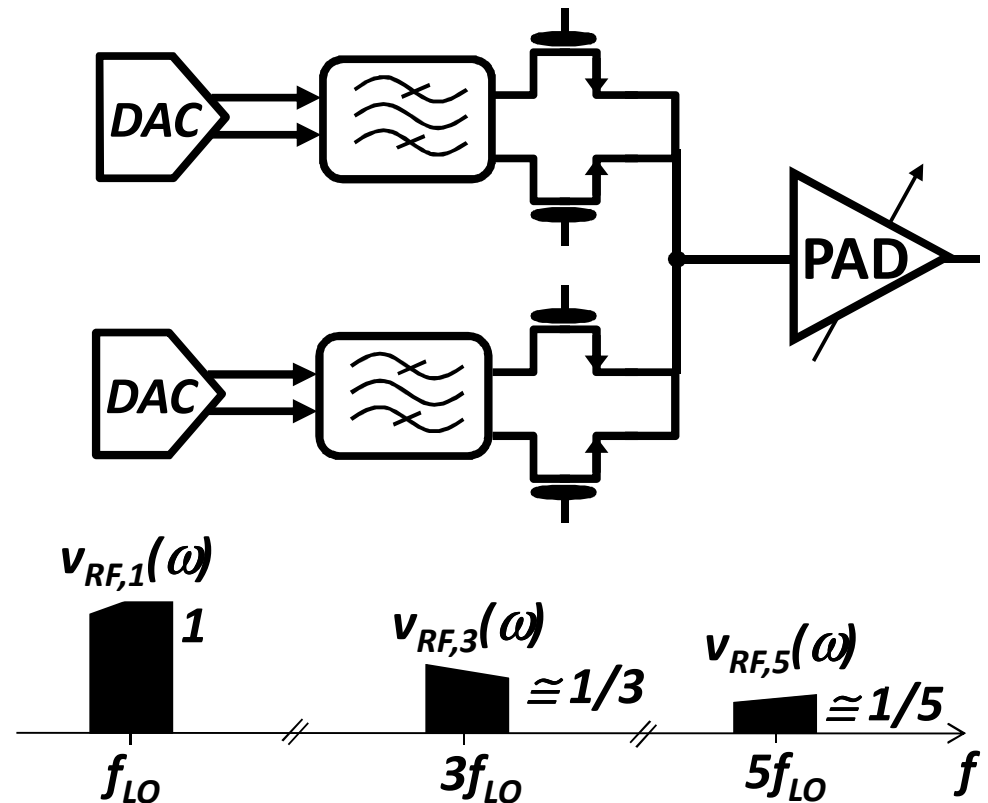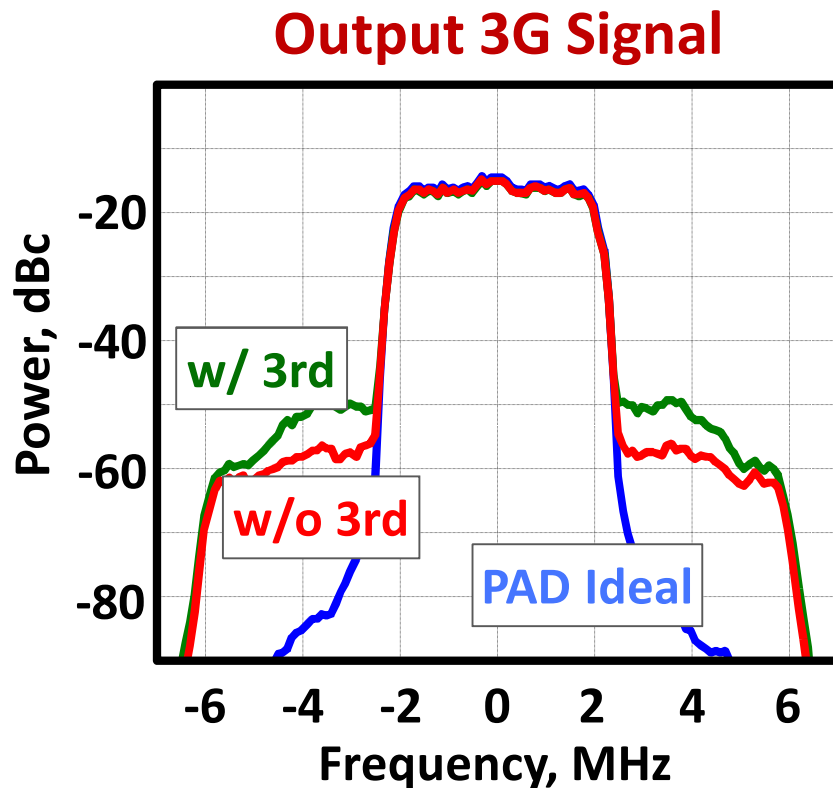


- With third harmonic present: ACLR = -38 dBc
- With third harmonic removed: ACLR = -44 dBc
- Makes the PAD linearity requirements more stringent

Case Study: Direct-Conversion 3G TX

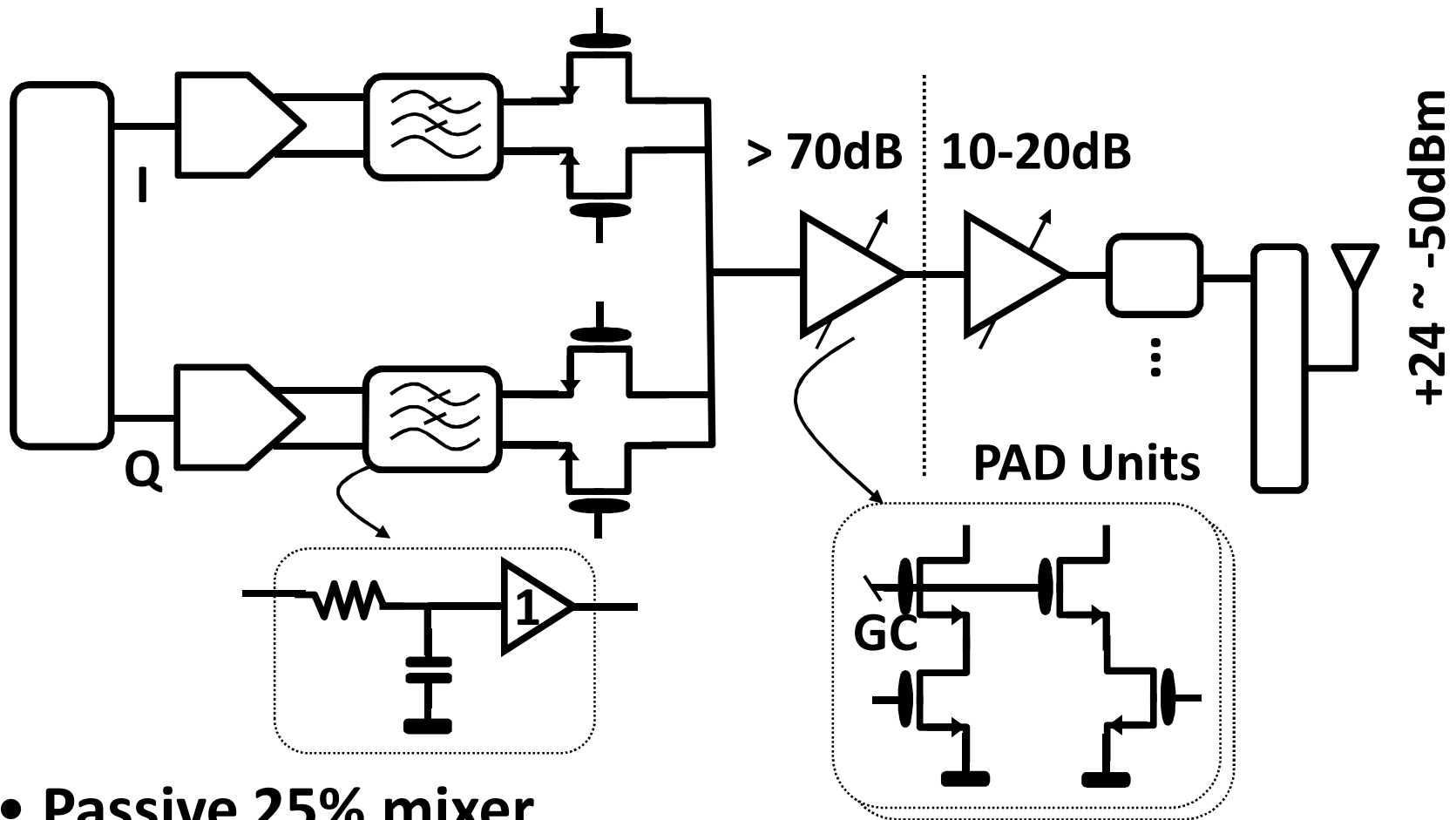


- **Passive 25% mixer**
- **LOFT scales w/ RF gain**

GSM RX-Band Noise Requirements

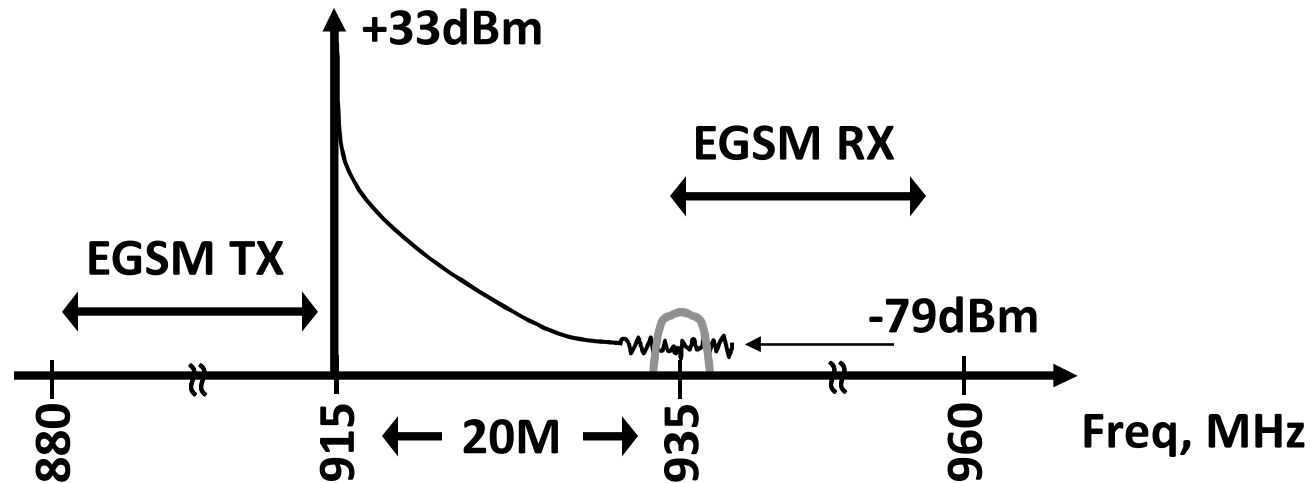


- TX noise in RX-band -79dBm not to mask adjacent RX
- Corresponds to a 20MHz phase noise of:
$$PN = -79\text{dBm} - 10\text{Log}(100\text{kHz}) - 33\text{dBm} = -162\text{dBc/Hz}$$
- Typical PA noise \approx -83dBm, leaving -165dBc for RF IC
- -112dBc spur, five exceptions allowed

Linear TX vs. Translational Loop


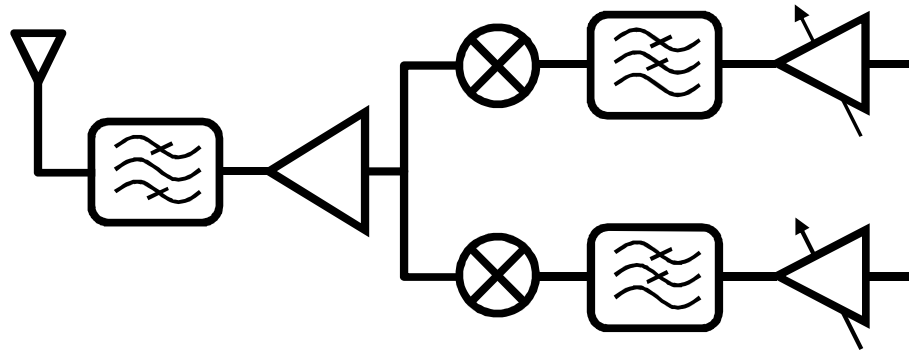


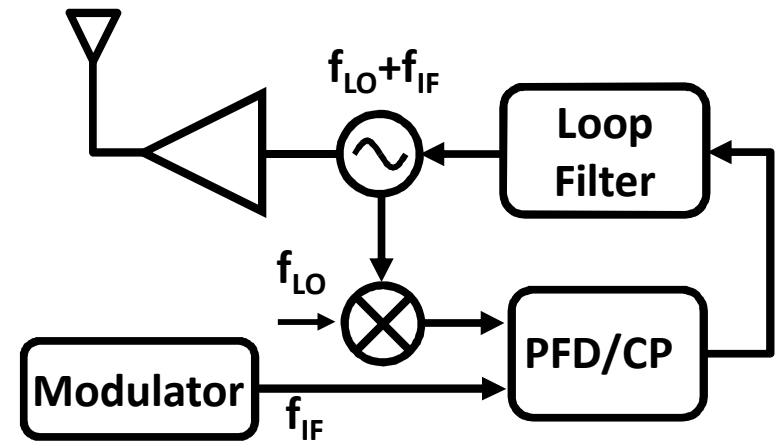- Sensitive to Pulling
- 20M noise an issue
- Simple
- Generic TX



- No pulling issue
- Relaxed filtering
- More complex
- Suitable for PM only

PLL-Based Transmitters

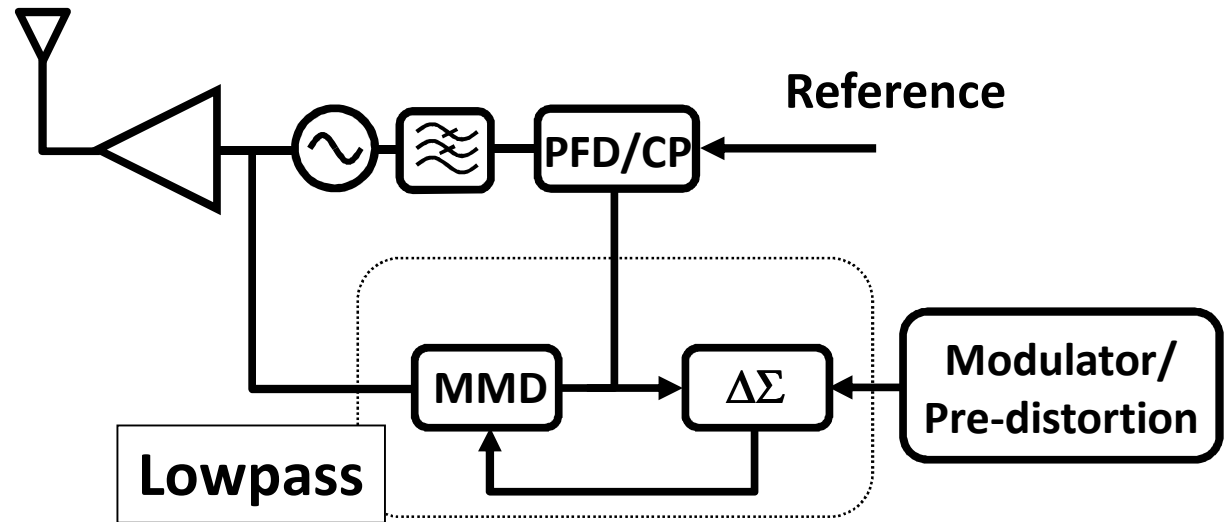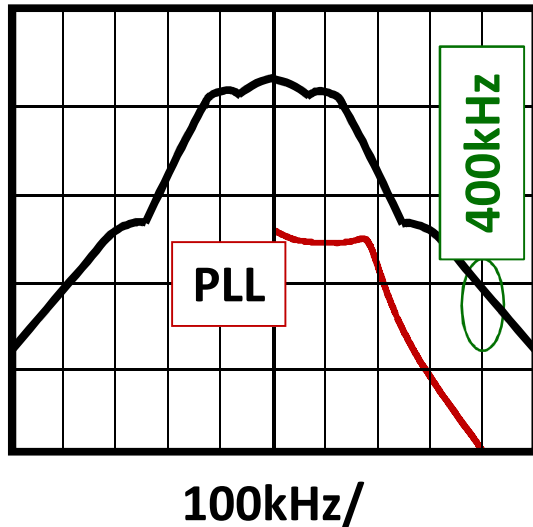

- Mixer/LO, analog modulator eliminated
- More sensitive to analog impairments
- Trade-off between BW and phase noise

GSM Mask & Phase Error Calculations

- -60dBc at 400kHz
 - 3dB production margin
 - 2dB PVT margin


Power integrated in 30kHz BW
 $\approx 10\text{Log}(200\text{k}/30\text{k})$

$$\text{PN} = -65 - 10\text{Log}(30\text{kHz}) - \textcircled{9} = -118.8\text{dBc/Hz}$$


- 5° RMS phase error

- 2° production margin
- 2° PVT, BW

0.0178 Radian

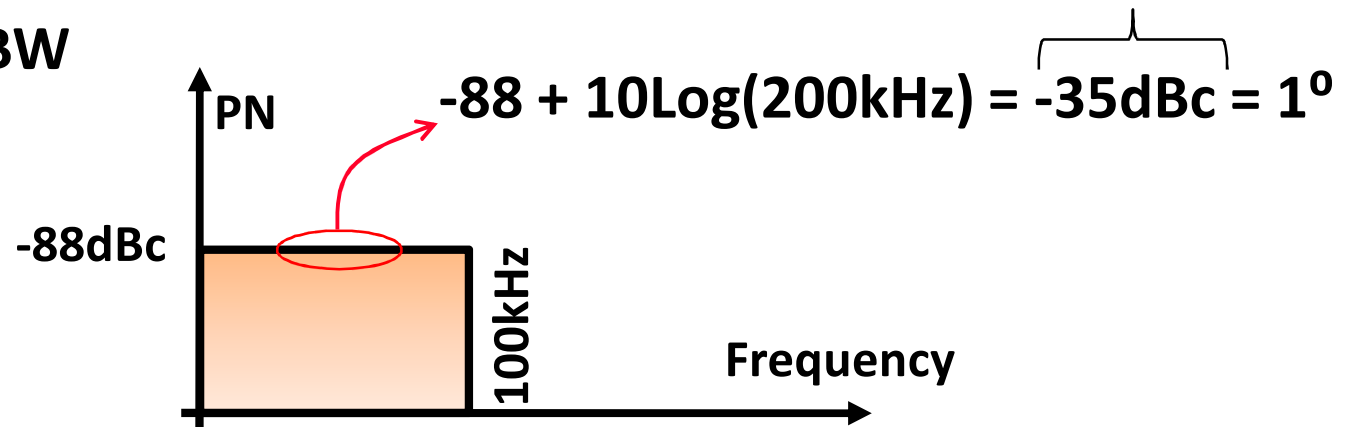


Basics of Polar Transmitters

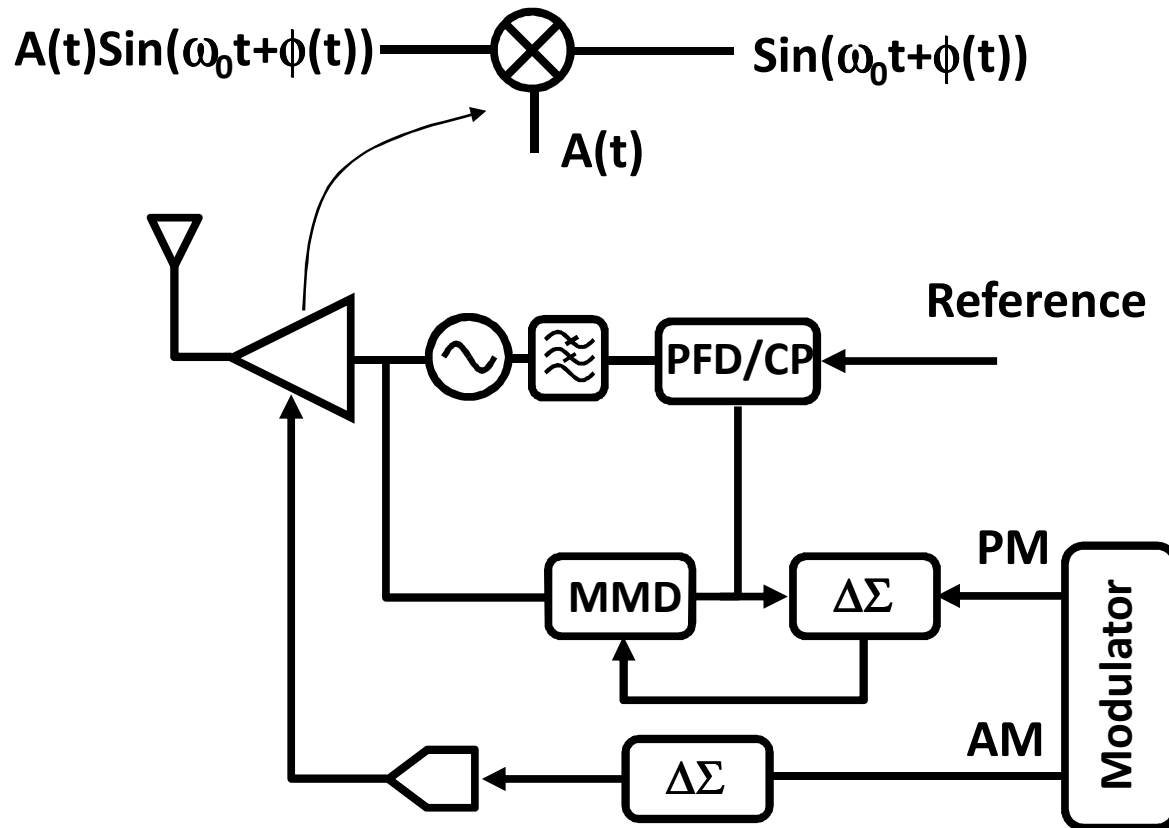



$$I + jQ = re^{j\theta}$$

EDGE Constellation

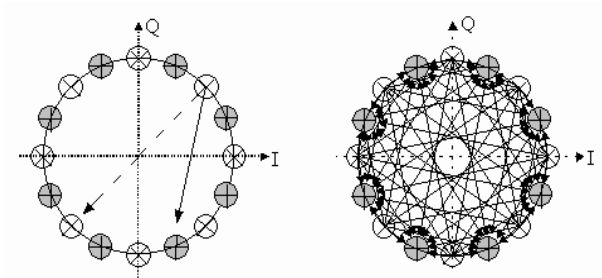



- Lower power consumption
- Compatible with GMSK TX
- Very sensitive to nonlinearities

EDGE AM & PM Signals Spectrum

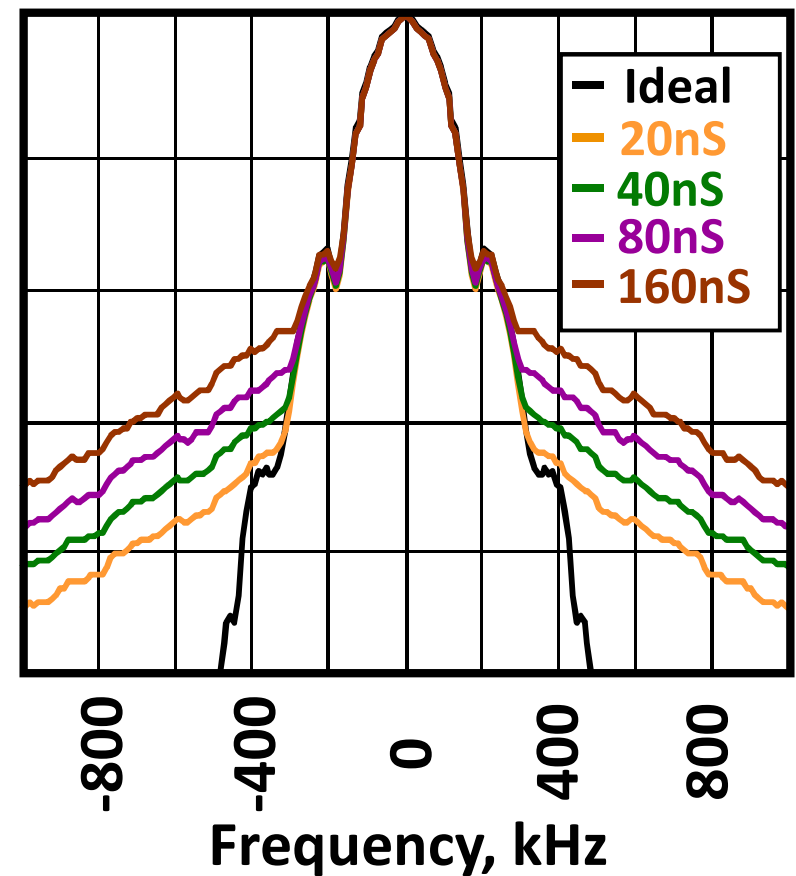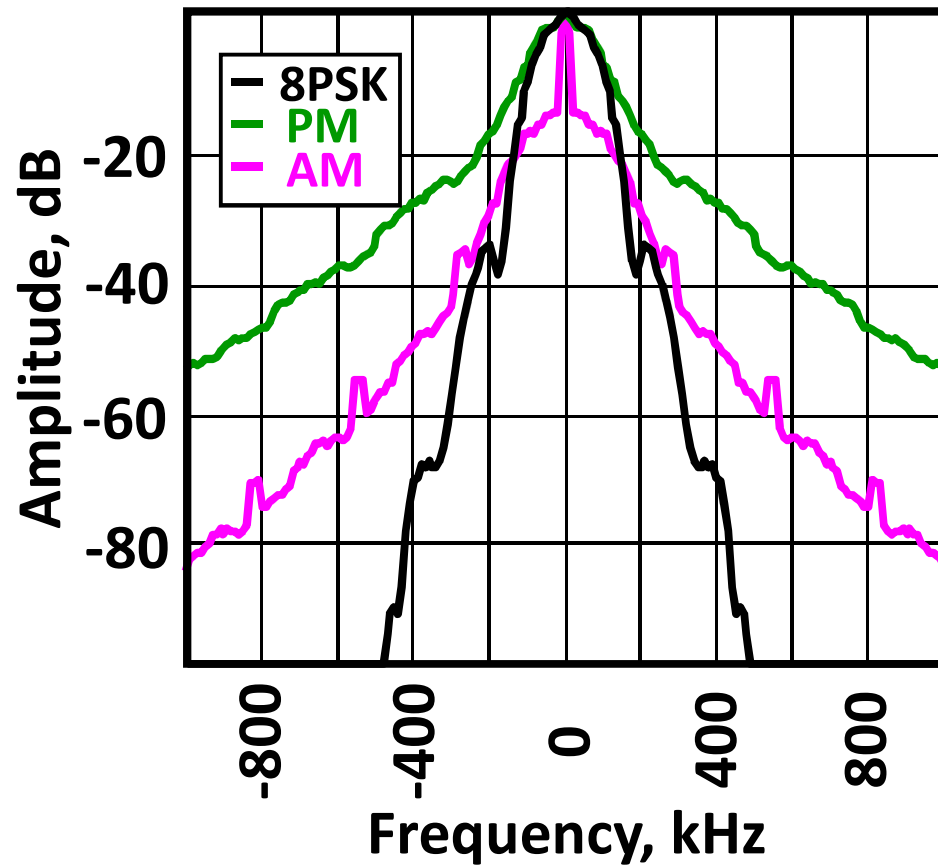



- AM & PM stand-alone signals much wider

PM Path Concerns

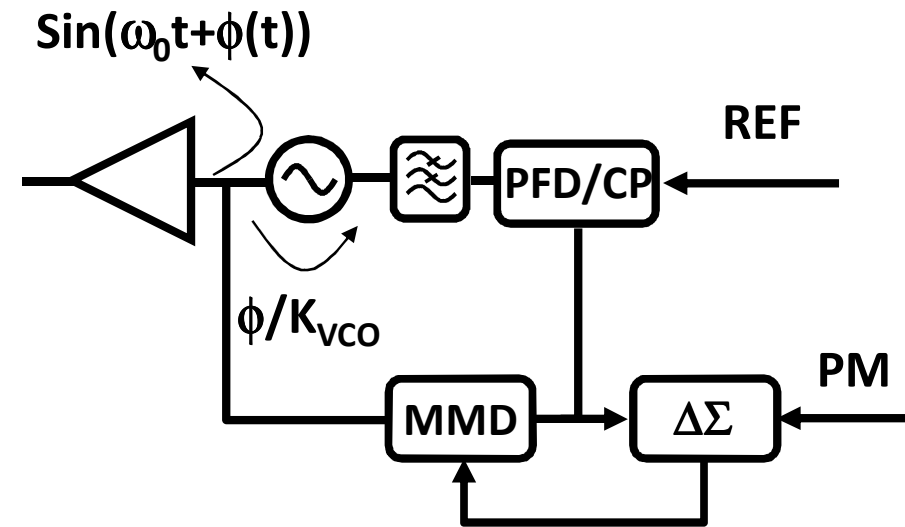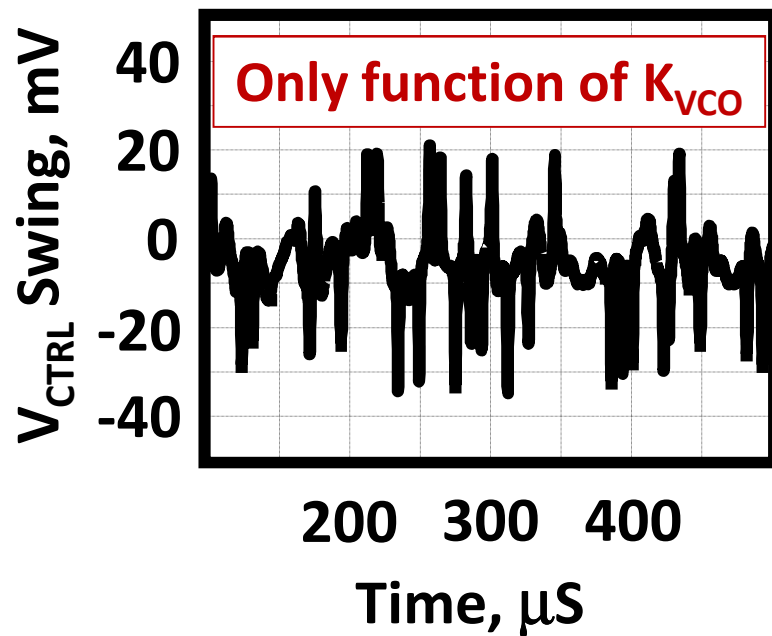

- Phase noise
- VCO & CP nonlinearity due to large swing, wide BW
- PLL BW needs to be accurately controlled
 - $\text{BW} \propto K_{VCO} \times R \times I_{CP}$: Measure K_{VCO} and adjust I_{CP}

AM Path Concerns

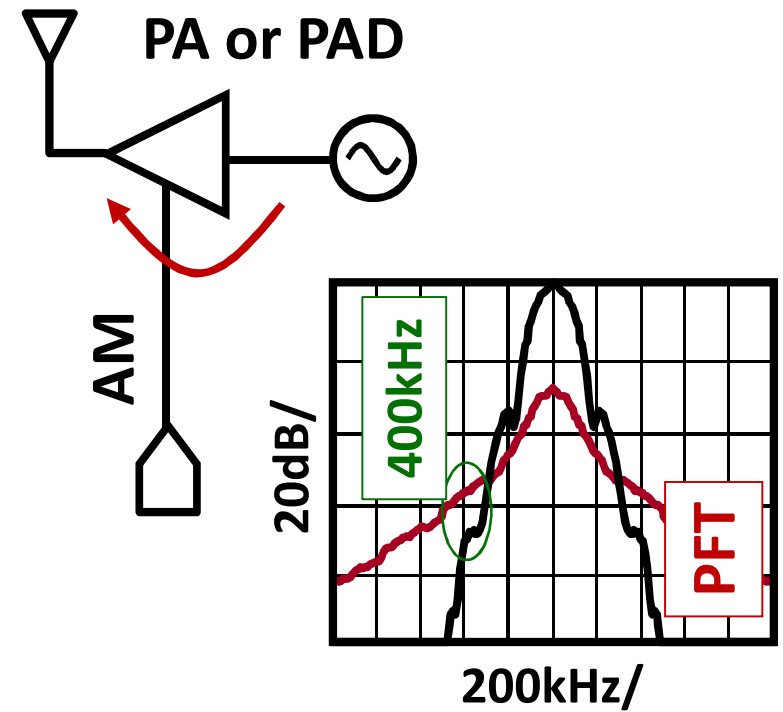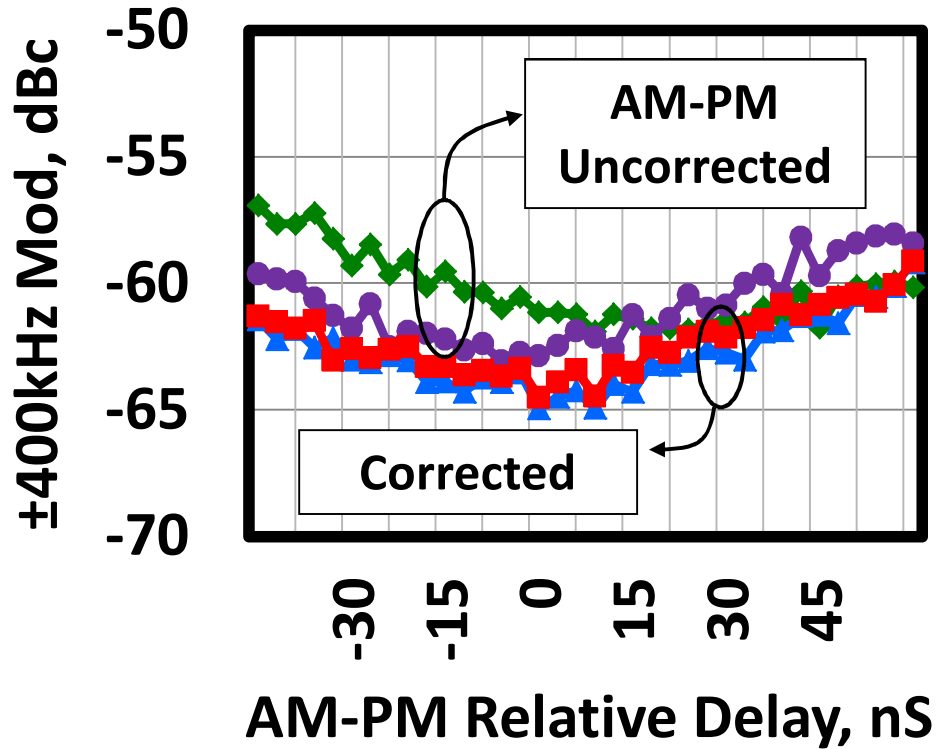



Mask Limiting Factors:

- AM-AM/PM distortion in PAD
- Phase feed-through


Static: AM-AM
Dynamic: AM-PM

2-Point PLL Based Polar Transmitters

3G AM & PM Signals

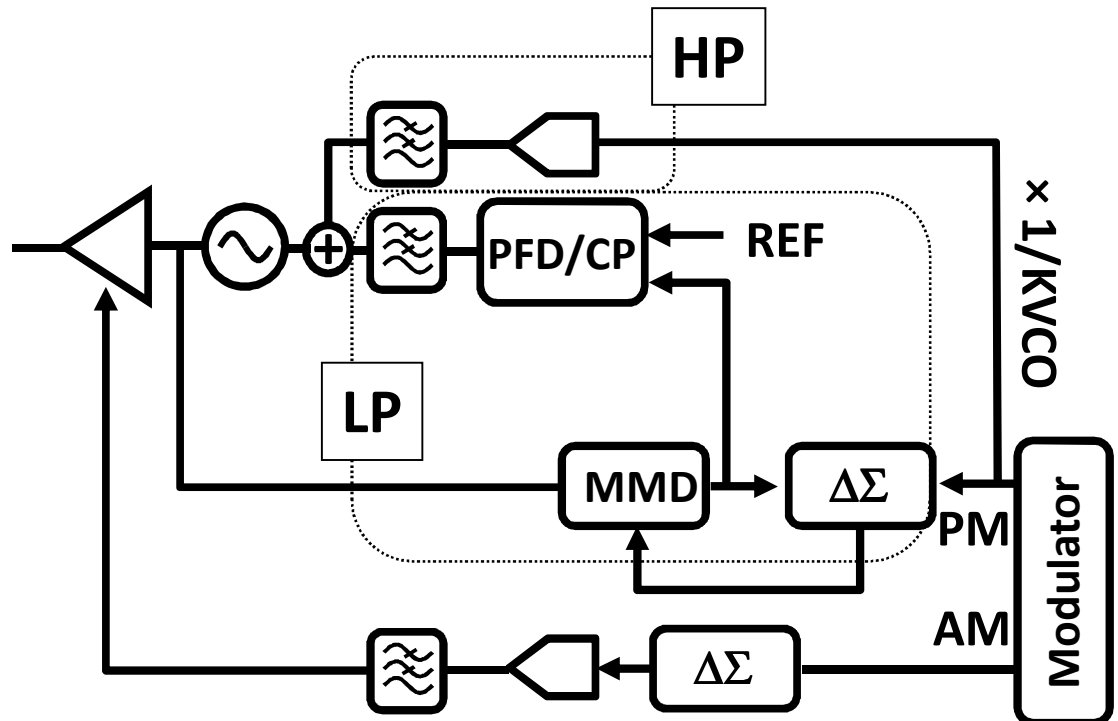
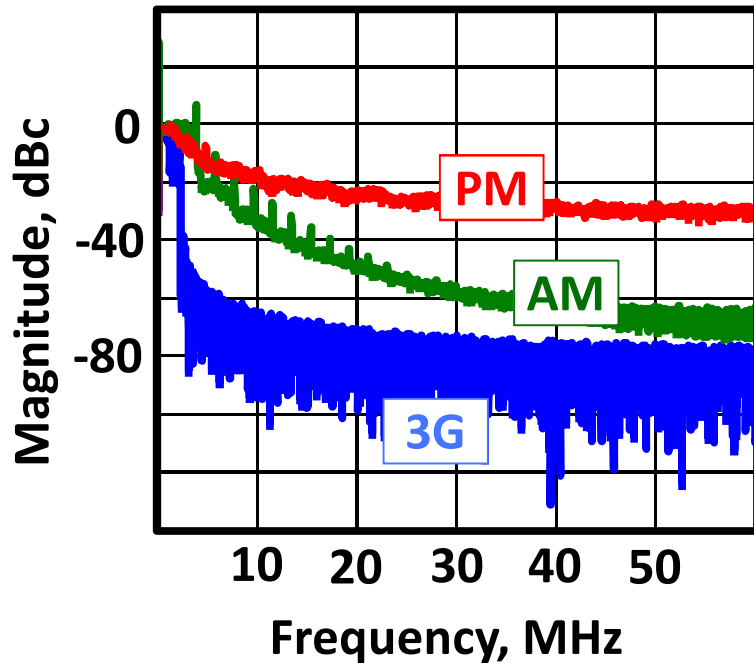


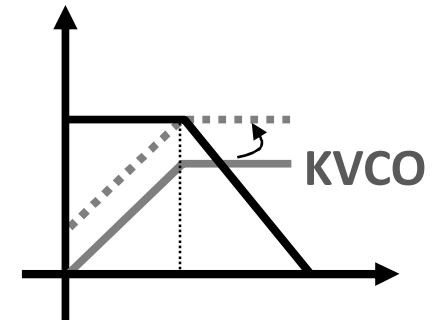- HP path to give a flat response
- Accurate K_{VCO} needed
- Accurate AM-PM matching needed




Impact of VCO Nonlinearity on 3G Signal

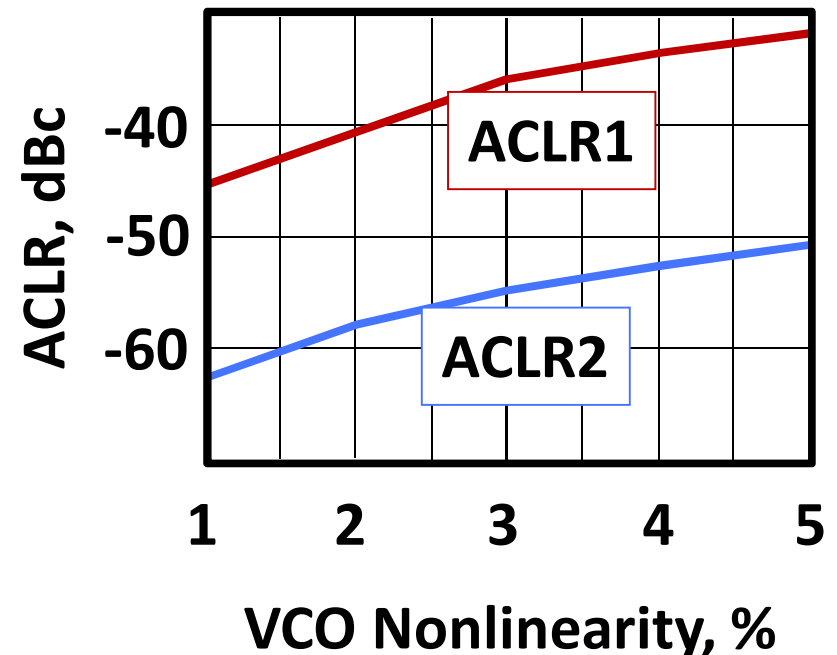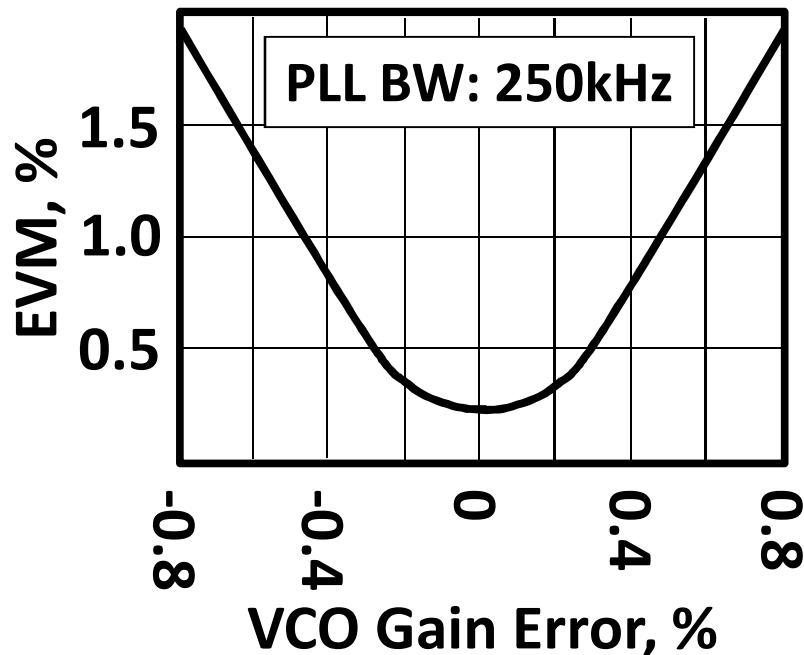- $K_{VCO} = d\omega/dV = 0.5 \times \omega_0^3 \times L \times \underbrace{(dC_{VAR}/dV)}_{\text{PVT Dependent}}$
- LC and C_{VAR} not modeled accurately



- K_{VCO} accuracy/linearity of better than 2% needed

Case Study: 3G Polar TX

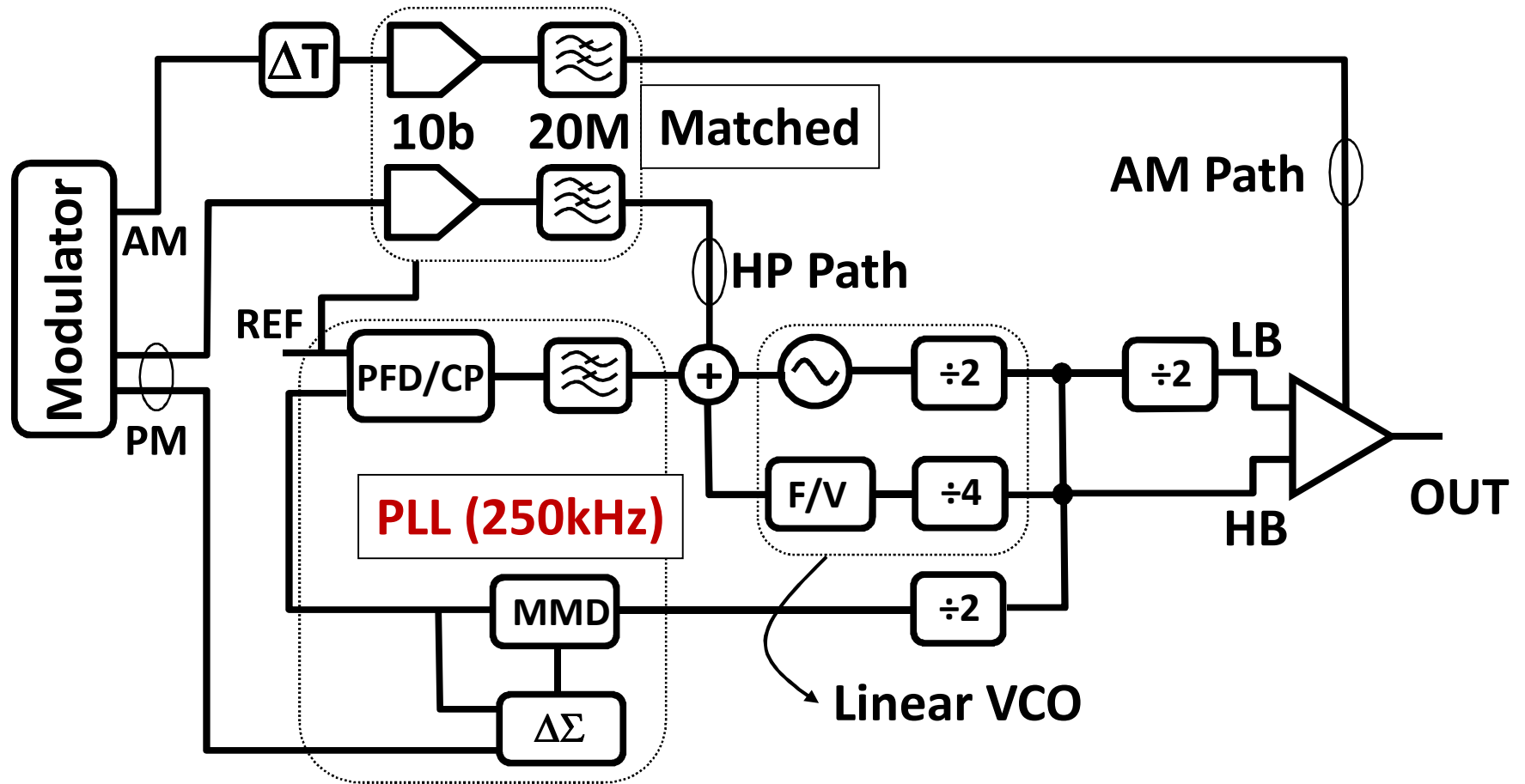

- $< -40\text{dBc}$ ACLR, $< 3\%$ EVM

Summary & Conclusions

- Standards set design parameters, radio architecture
- On receiver side:

Architecture	1/f, IIP ₂	IMR	Linearity	Limitations
Zero-IF	Poor	Self	Modest	WB
Low-IF	Modest	In-band	Modest	NB

- CM receivers improve linearity, relax filtering
- On transmitter side:

Architecture	Power	Noise	Pulling	Limitations
Direct	Modest	Poor	Poor	Generic
PLL	Lowest	Good	None	Only PM, NB
Polar	Lowest	Good	Good	Complex, NB

References

1. A. A. Abidi, "Direct-Conversion Radio Transceivers for Digital Communications," *IEEE J. of Solid-State Circuits*, vol. 30, no. 12, pp. 1399-1410, 1995
2. O. Erdogan, et. al., "A single-chip quad-band GSM/GPRS transceiver in 0.18mm CMOS," *ISSCC Digest of Technical Papers*, pp. 318-319, Feb. 2005.
3. O. Bonnaud, et. al., "A fully integrated SoC for GSM/GPRS in 0.13mm CMOS," *ISSCC Digest of Technical Papers*, pp. 482-3, Feb. 2006.
4. L. Franks and I. Sandberg, "An alternative approach to the realizations of network functions: N-path filter," in *Bell Syst. Tech. J.*, 1960, pp. 1321-1350.
5. H. Darabi, et. al., "A Quad-Band GSM/GPRS/EDGE SoC in 65nm CMOS," *IEEE J. of Solid-State Circuit*, no. 4, April 2011.
6. M. Youssef, et. al., "A Low-Power Wideband Polar Transmitter for 3G Applications," *ISSCC Digest of Technical Papers*, Feb. 2011.
7. E. H. Armstrong, "The Super-Heterodyne-Its Origin, Development, and Some Recent Improvements" *Proc. of the Institute of Radio Engineers* Volume: 12 , Issue: 5, 1924, pp. 539-552
8. Z. Boos, et. al., "A Fully Digital Multi-Mode Polar Transmitter Employing 17b RF DAC in 3G Mode," *ISSCC Digest of Technical Papers*, Feb. 2011.
9. H. Darabi, et. al., "Analysis and Design of Small Signal Polar Transmitters for Cellular Applications," *IEEE J. of Solid-State Circuit*, 2011.
10. J. Mitola, "The software radio architecture," *IEEE Communications Magazine*, vol. 33, no. 5, pp. 26-38, May 1995.
11. A. Mirzaei, et. al., "Analysis and optimization of current-driven passive mixers in narrowband direct-conversion receivers," *IEEE J. of Solid-State Circuit*, no. 10, pp. 2678-2688, October 2009.
12. D. Kaczman, et. al., "A single-chip 10-band WCDMA/HSDPA 4-band GSM/EDGE SAW-less CMOS receiver with DigRF 3G interface and 90dBm IIP3," *IEEE J. of Solid-State Circuit*, no. 3, pp. 718-739, 2009.
13. M. Zargari, et. al., "A 5-GHz CMOS transceiver for IEEE 802.11a wireless LAN systems", *IEEE J. of Solid-State Circuit*, no. 12, pp. 1688-1694, 2002.
14. A. Mirzaei, et. al., "Analysis and optimization of direct-conversion receivers With 25% duty-cycle current-driven passive mixers," *IEEE Trans Circuits & Systems I*, No. 9, Vo. 47, 2010, pp. 23530-2366.
15. E. Cijvat, et. al., "Spurious mixing of off-channel signals in a wireless receiver," *IEEE Trans Circuits & Systems II*, No. 8, Vo. 49, 2002, pp. 539-544.
16. A. Mirzaei, et. al., "A 65nm CMOS quad-band SAW-less receiver for GSM/GPRS/EDGE," *IEEE J. of Solid-State Circuit*, no. 4, April 2011.
17. J. Weldon, et. al., "A 1.75-GHz highly integrated narrow-band CMOS transmitter with harmonic-rejection mixers," *IEEE J. of Solid-State Circuit*, no. 12, pp. 2003-2015, Dec 2001
18. C. Andrews, et. al., "A passive-mixer-first receiver with Digitally Controlled and Widely Tunable RF Interface," *IEEE J. of Solid-State Circuit*, Vol. 45, no. 12, pp. 2696-2708, Dec 2010
19. M. Soer, et. al., "A 0.2-to-2GHz 65nm CMOS receiver w/o LNA achieving >11dBm IIP3 and <6.5dB NF," *ISSCC Digest of Tech. Papers*, pp. 222-3, Feb. 09
20. X. He, et. al., "A Low-Power, Low-EVM, SAW-Less WCDMA Transmitter Using Direct Quadrature Voltage Modulation," *IEEE J. of Solid-State Circuit*, vol. 44, no. 12, pp. 3448-3458, 2009.
21. A. Mirzaei, et. al., "A Frequency Translation Technique for SAW-Less 3G Receivers," *Proc. of IEEE Symp. VLSI Circuits*, pp. 280-281, 2009.
22. M. Mikhemar, et. al., "A 13.5mA Sub-2.5dB NF Multi-Band Receiver," *Proc. of IEEE Symp. VLSI Circuits*, 2012.
23. A. Mirzaei, et. al., "Analysis of Direct-Conversion IQ Transmitters With 25% Duty-Cycle Passive Mixers," *IEEE Trans Circuits & Systems*, No. 10, Vo. 58, pp. 2318-2331, 2011.
24. A. Abidi, "Linearization of Voltage-Controlled Oscillators using Switched Capacitor Feedback," *IEEE J. of Solid-State Circuits*, vol. 22, no. 3, pp. 494-496, June 1987.
25. F. Broccoleri, et. al., "Wide-band CMOS low-noise amplifier exploiting thermal noise canceling," *IEEE J. Solid-State Circuits*, vol. 39, no. 2, pp. 275-282, Feb. 2004.
26. D. Murphy, et. Al., "A blocker-tolerant wideband noise-cancelling receiver with a 2dB noise figure" *ISSCC Digest of Tech. Papers*, pp. 74-6, Feb. 12.