



A 700+ mW Class D Audio Amplifier with direct battery hookup in a 90 nm process

Brett Forejt, Vijay Rentala, Gangadhar Burra, and Jose Arteaga

Wireless Analog Technology Center

Texas Instruments Incorporated



Abstract

A “battery connect” compatible class D (switching) amplifier which is fully integrated in a 90 nanometer digital CMOS process is presented. The integration of the amplifier requires no additional masks, processing, or cost. This presentation includes a brief description of the circuit techniques that enable direct battery (2.7 – 5.4V) connection and allow support > 6.7 VP2P (700 mW into 8 ohms) output swing from a 4.2 V supply using devices that operate solely with low gate voltages. The achieved SNR over an audio (20Hz to 20 kHz) bandwidth > 98dB (1W) and the total harmonic distortion (THD) is better than 0.03% at 500 mW. Efficiency is greater than 75% above 375 mW. The power supply rejection ratio (PSRR), which is a crucial parameter in modules connected directly to the battery, is measured at 70dB at 217 Hz. The area of the switching amplifier is < 0.44mm², where the power devices occupy approximately 20% of the total.



Agenda

- Introduction
- Motivation
- PWM Modulation
- Architectures
- Deep Sub-Micron Technology Considerations
- Design Solution
- Testing Challenges
- Simulation & Measurement Results
- Conclusion



Introduction

- Audio output demands continue to increase for mobile devices
 - Poly-phonic Ringers
 - Handset Speakers
 - Stereo Outputs
 - Multi-channel 3D Audio
 - Speaker Phones
- Power Efficiency in Mobile Electronics
 - Heat Dissipation
 - Battery Life




Typical Application



Audio Demands

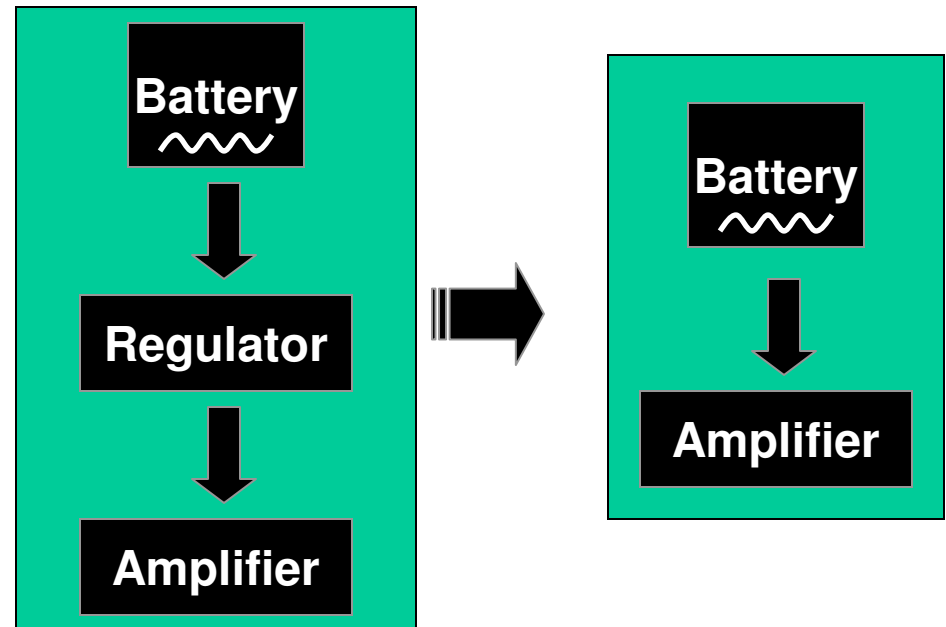- Specific challenges in battery supplied systems
 - PSRR
 - HEAT
 - Battery life
- Performance metrics
 - Output power
 - THD
 - SNR
 - Efficiency





Power Budget

– *The future of mobile devices* –

- Digital Processor Cores are even more power hungry
- More “Audio” power amplifiers for today’s typical mobile devices
 - Speaker phone
 - Polyphonic ringer
 - MP3 Stereo
 - Earphone
- Smaller area involves greater heat dissipation
- *Switching Amplifiers help alleviate thermal concerns*



Motivation: Class D...

- Has improved *Efficiency* across the range of power delivered with respect to Class A, AB, & B
- Can directly replace Class A, AB, or B in traditional systems
- Is advantageous for integration in 90nm technologies and beyond




Power Efficiency

$$Eff = \frac{\int_T I_{load}(t) * V_{load}(t) dt}{\int_T I_{battery}(t) * V_{battery}(t) dt + \int_T I_{ldo}(t) * V_{ldo}(t) dt}$$

$$Eff_{MAX-ClassD} = \frac{R_{load}}{R_{load} + R_{dsonNMOS} + R_{dsonPMOS} + R_{parasitic}}$$



Efficiency Comparison

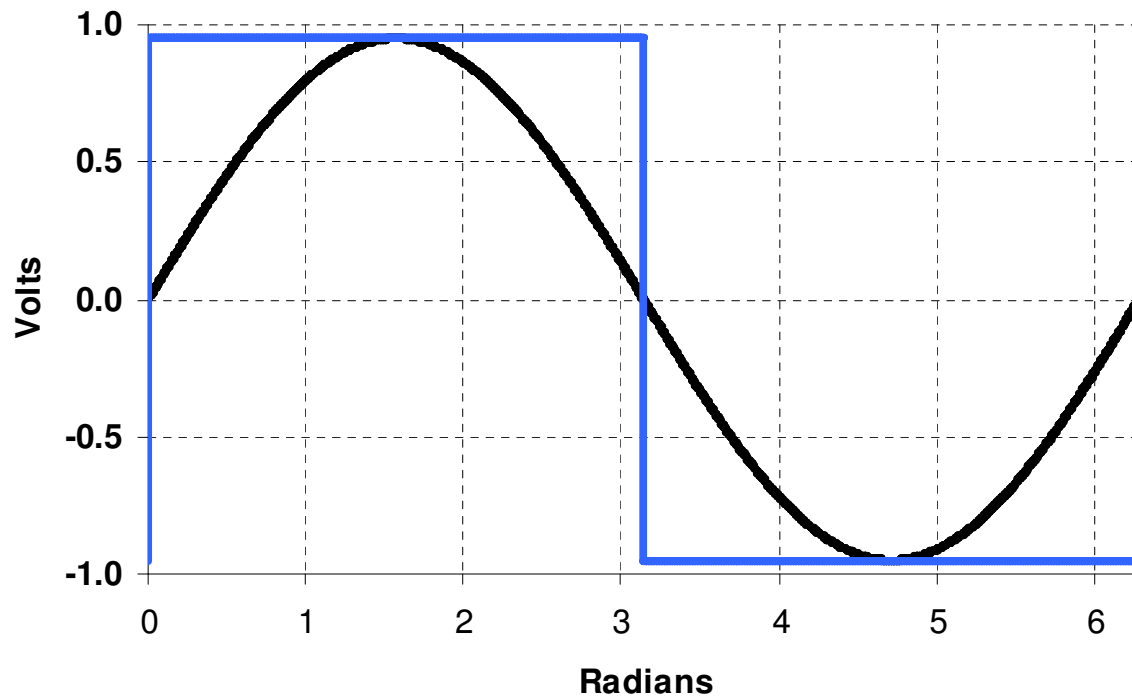

- Assuming a simple resistive load
- Class D output can be approximated as a square wave.
- Class D Efficiency is proportional to V_{\max}
- Class B Efficiency is proportional to the half sin wave integral


$$\eta_{\text{ClassB}} = \frac{\pi * V_{\text{amp}}}{4} \Rightarrow \eta_{\text{ClassB}} = 0.7854 * V_{\text{amp}} \quad \eta_{\text{ClassD}} = \frac{R_{\text{load}}}{R_{\text{load}} + R_{\text{dson}}}$$

3/14/2005

9



Efficiency Comparison

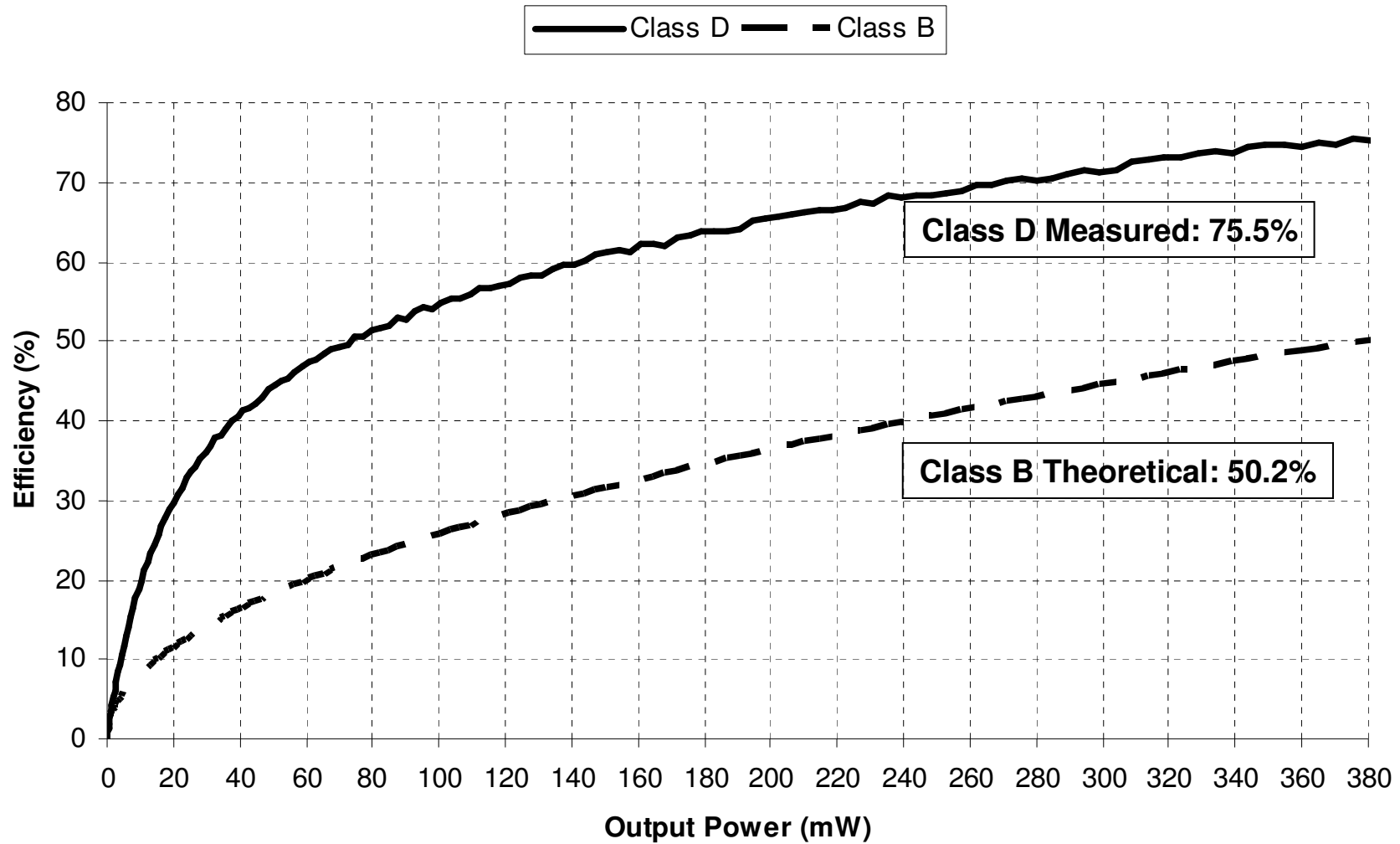

3/14/2005

“Energy not delivered to load is dissipated thermally”

10




Pulse Width Modulation


- Two basic types of modulation
 - Binary (or AD)
 - Ternary (or BD)
- Three ways to generate modulation
 - Leading edge
 - Trailing edge
 - Double edge
- Typical Schemes
 - Natural Sampling
 - Uniform Sampling
 - Hybrid Sampling ← Many possibilities




Pulse Width Modulation

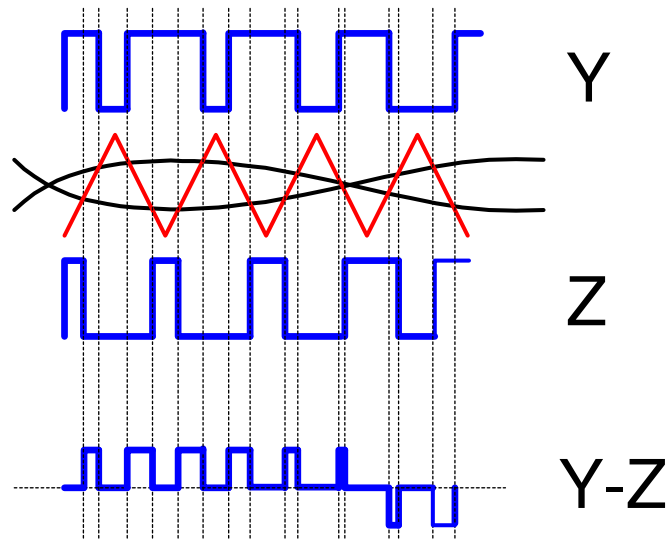

Modulation Levels

 

a) Two Levels

 


b) Three Levels

The two Configurations



Pulse Width Modulation

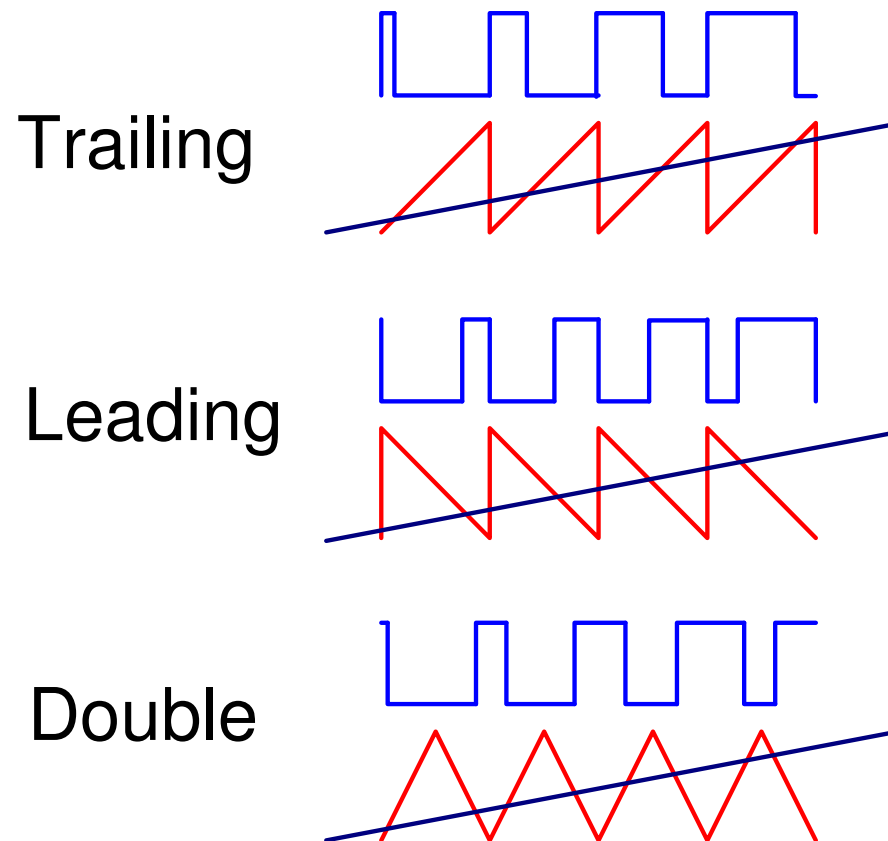

3/14/2005


Modulation Edges

13

*Graphics provided by Francisco Ledesma



Pulse Width Modulation

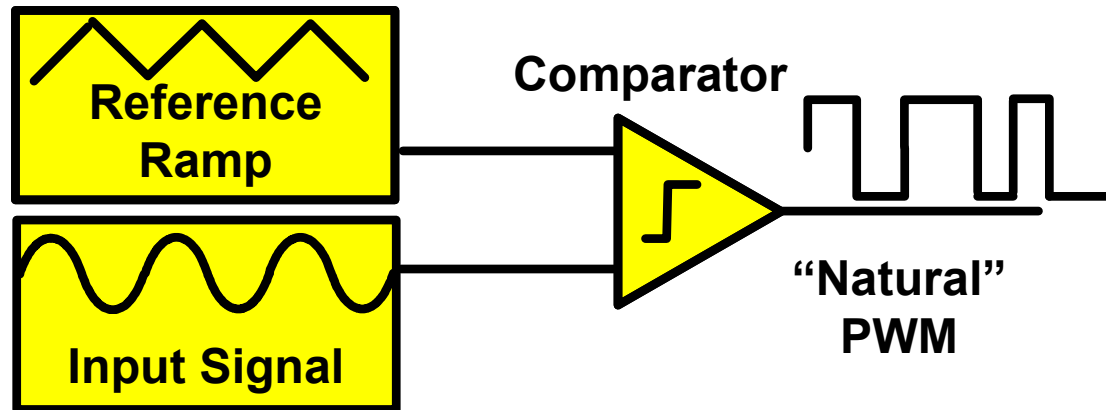


- Natural Sampling
 - Infinitely precise edges
 - No distortion added
 - Comparator performance
 - Reference linearity



Pulse Width Modulation

Comparison between a few modulation sampling schemes

 - Natural – Theoretically ideal
- Hybrid – Approaches Natural
 - Information lost
 - Faster Carrier → Increased Performance but lower efficiency
- Uniform – Sample and Hold
 - Information lost
 - Interpolation method impacts performance
 - Faster Carrier → Increased Performance but lower efficiency



3/14/2005

15


**Graphics provided by Francisco Ledesma from Karston Neilson's Thesis*




Pulse Width Modulation

Natural Sampling Spectrums


← Natural Single Sided Binary Modulation

 

 
Natural Single Sided Ternary Modulation →



← Natural Double Sided Binary Modulation

 

 Natural Double Sided Ternary Modulation →




**Graphics provided by Francisco Ledesma from Karston Neilson's Thesis*



Architectures

→ Open Loop Bridge

- More Efficient
- Smaller Area
 - ◆ Possibly Bridge Only if PWM data is pre-existing
- Approximately 0 PSRR
- Output Amplitude is proportional to power supply voltage and loading conditions → **no gain control**
- No error source correction method as with feedback system
 - ◆ THD may suffer
 - ◆ Noise may suffer
- In practice on Cellular phone for low quality applications
 - ◆ Ringers
 - ◆ Buzzers

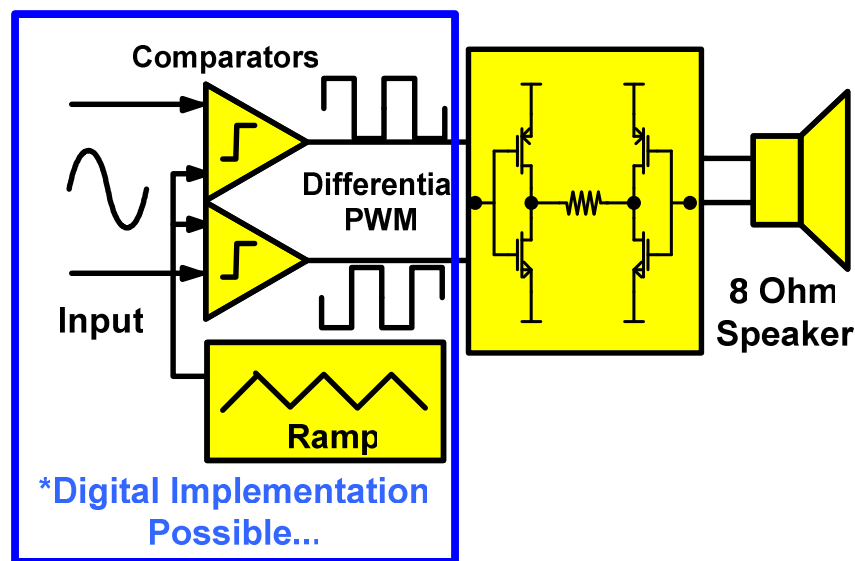




Architectures

→ *Open Loop Bridge with Digital P.S. and Load correction methods*

- Sample power supply with ADC and pre-condition the signal to correct for power supply changes
- Start up calibration loop → measures load and also pre-conditions the signal based upon the pre-existing load
- Stability is major factor
- Digital processing required
 - ◆ Mixer
 - ◆ Programmable Equalizer
 - ◆ Significant area and power increase
- In practice for extreme performance high power applications

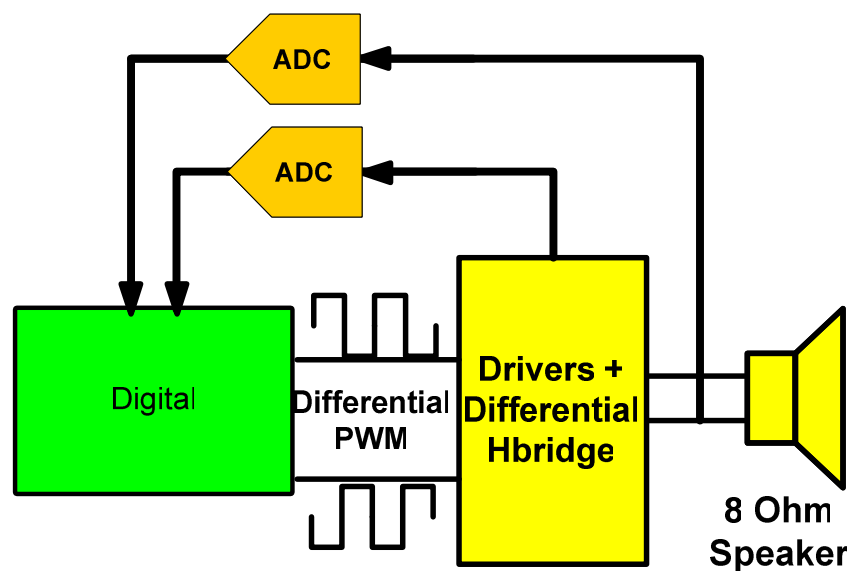




Architectures

→ Closed Loop System

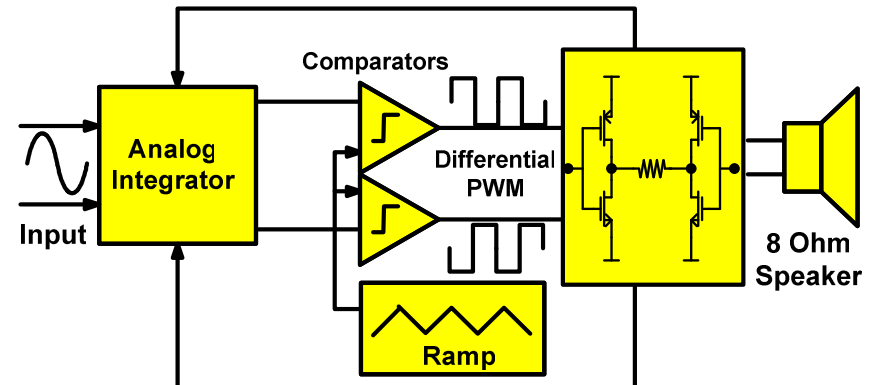- Provides mechanism with corrects for Power Supply noise and Errors
- Fixed Gain
- Load independent Gain
- Area and Efficiency are acceptable for the application
- Feedback system also corrects for other error sources in the system
- Direct replacement for existing continuous time amplifiers
 - ◆ *Competitive to AB in Performance & Area*
 - ◆ *No system changes required*





Architectures Summary

→ *Open Loop Bridge*

- More Efficient
- Smaller Area (Bridge Only)
- Approximately 0 PSRR
- Output Amplitude is proportional to power supply voltage and loading conditions
→ **no gain control**
- No error source correction method as with feedback system
 - ◆ THD may suffer
 - ◆ Noise may suffer
- In practice on Cellular phone for low quality applications
 - ◆ Ringers
 - ◆ Buzzers

→ *Open Loop Bridge with Digital P.S. and Load correction methods*


- Sample power supply with ADC and pre-condition the signal to correct for power supply changes
- Start up calibration loop → measures load and also pre-conditions the signal based upon the pre-existing load
- Stability is major factor
- Digital processing required
 - ◆ Mixer
 - ◆ Programmable Equalizer
 - ◆ Significant area and power increase
- In practice for extreme performance high power applications

→ *Closed Loop System*

- Provides mechanism with corrects for Power Supply noise and Errors
- Fixed Gain
- Load independent Gain
- Area and Efficiency are acceptable for the application
- Feedback system also corrects for other error sources in the system
- Direct replacement for existing continuous time amplifiers
 - ◆ *Competitive to AB in Performance & Area*
 - ◆ *No system changes required*
- *Chosen Architecture*



Audio Channel with Class D

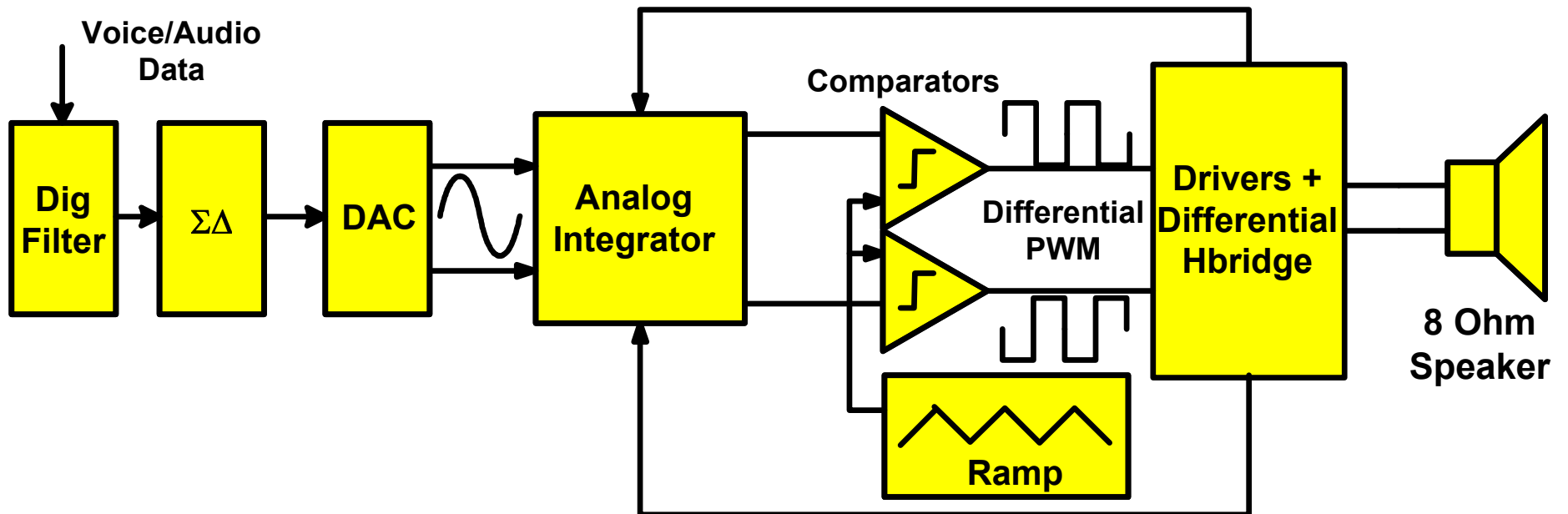

3/14/2005

21



Stability Criteria

- At first glance the system is first order and should therefore be inherently stable
- However, there is a secondary stability criterion which must be met
 - If the slew rate of the integrator exceeds that of the ramp from which the PWM carrier is derived then the system becomes unstable
 - In a system where the average input and output common modes are equal, Equation (1) defines stability
 - Where the input and output common modes are not equal equations (2) & (3) outline the stability criterion


$$F_{INTPole} \leq \frac{F_{Ramp}}{\pi} \quad (1)$$

$$4 * V_{Aramp} * F_{ramp} \geq \frac{1}{C_I} \left(\frac{V_{CMA} \pm V_I}{R_{IN}} + \frac{V_{CMA} \pm V_O \mp V_{CMO}}{R_{FB}} \right) \quad (2)$$

$$V_{CMA} = V_{CMINPUT} + (V_{CMOUT} - V_{CMIN}) * \left(\frac{R_{IN}}{R_{IN} + R_{FB}} \right) \quad (3)$$



Typical Signals

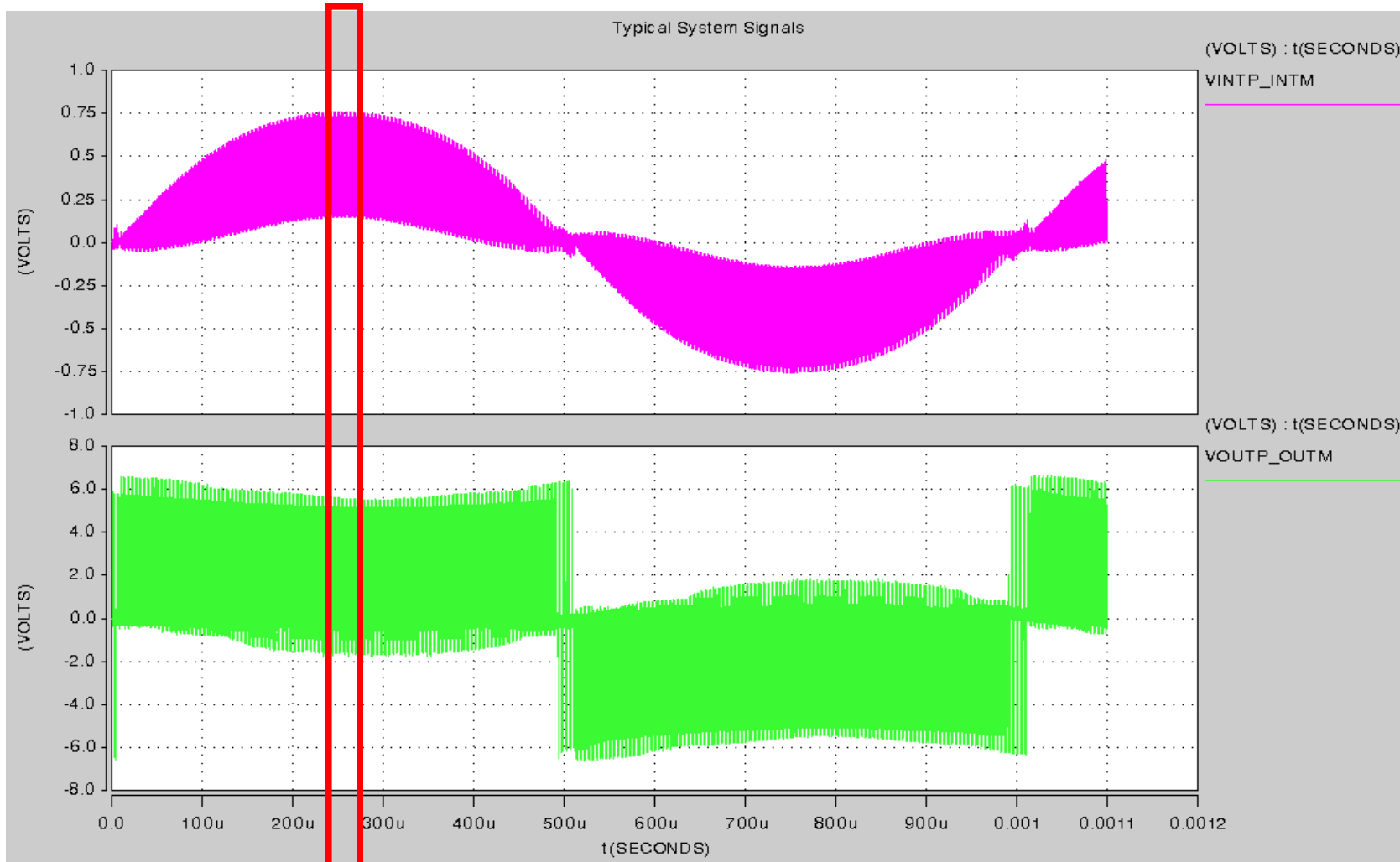


3/14/2005

Continued

23



Typical Signals

 

3/14/2005

24



Integration Advantages in Deep Sub Micron CMOS

- Processing advantages
 - Higher I_{drive} per area
 - Faster devices & sub circuits
 - Reduced area & minimum feature size
 - Direct battery connection at no additional cost
- Embedded solutions
 - System partitioning
 - Flexibility





Design Challenges in Deep Sub Micron Technologies

- We need a direct battery connection: Reliability Issues
 - Maximum Drain to Source voltage
 - Gate Oxide Integrity
- Device leakage currents
 - Channel Leakage
 - Gate Leakage
 - Drain/Source to Body Leakage



Drain Extended Devices

  

Drain Extend PMOS cross section


→ Make High Voltage Design Possible for no extra cost!!!

- Free from processing perspective (no extra masks or steps)
- Using Core or thin gate oxides high voltage design is made possible
- Drain is “extended” away from gate
- Allows the Gate to Drain voltage to be much greater while other terminals still must meet core device reliability standards
- Matching?
- I_{DRIVE} is reduced
- C_{GD} is much greater than core devices
- FT is much less than core devices



Integrator

 
- Input Common Mode Range
- High DC Gain
- Good Common Mode Rejection
- High Linearity
- Low Noise
- Low Power
- Good PSRR
- Low Area
 - Amplifier
 - Passives
- Performance depends mainly upon Amplifier
- Passives must be linear





Integrator Amplifier

- Input Common Mode Range
- High Gain
- High Phase Margin
- High Gain Margin
- Band width at least 10X greater than Modulation frequency
- Low power
- Low area
- Good common mode feedback performance
 - Gain
 - Phase Margin
 - Gain Margin
- Linearity must be a significant margin above overall loop specification
- Noise must be a significant margin above overall loop specification
- Large output swing (compared to V_{LDO})

 


3/14/2005

29



Comparator

 - High Gain
- High speed
 - Rise & Fall time
 - Propagation delay
- Low power
- Low area
- Low Noise
- Rail to rail input range – comparing a large scale ramp signal to the integrator output




3/14/2005

30



Ramp Generator

 
- Provides the triangular wave form required for “Natural Sampling”
- Must be linear for good Signal THD
- Must have large swing range for good stability versus area trade off of overall design
- Should have minimal frequency drift versus process, voltage, and temperature
 - PLL
 - Trim
 - Auto calibration





Half Bridge Circuits

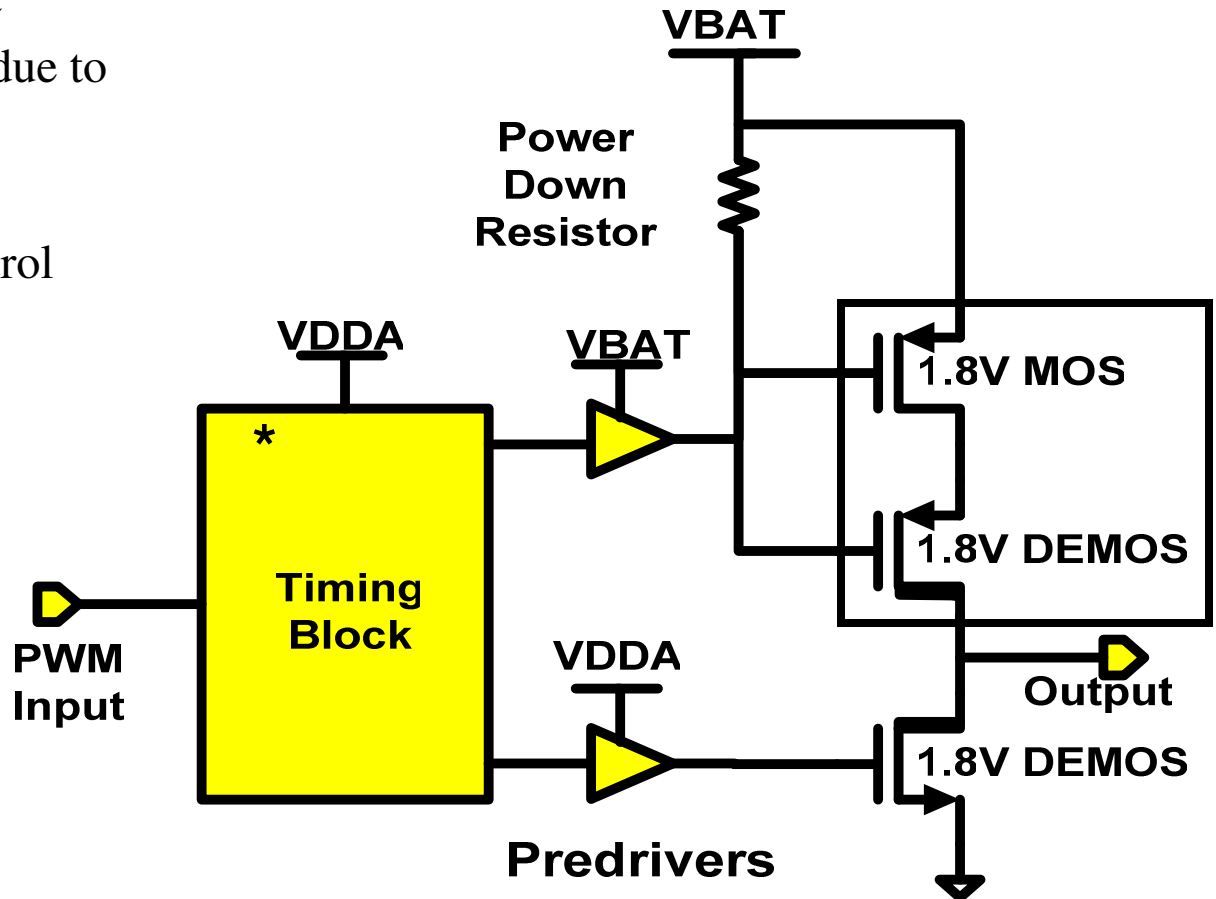- Timing Block
 - Shoot-through current
 - Output node glitches due to parasitic inductances
- Pre-drivers
 - Independent gate control
 - Reliability concerns
- Output Devices
 - Low leakage
 - Low $R_{\text{DS(on)}}$
 - Minimum Area
 - Reliability Concerns




3/14/2005

32



Half Bridge: PMOS Driver

 
- Must Address reliability concerns and protect the gate of the Power PMOS device
- Minimal Propagation Delay
- Minimal Rise and Fall times
- Low Power
- Low Area





Class D System

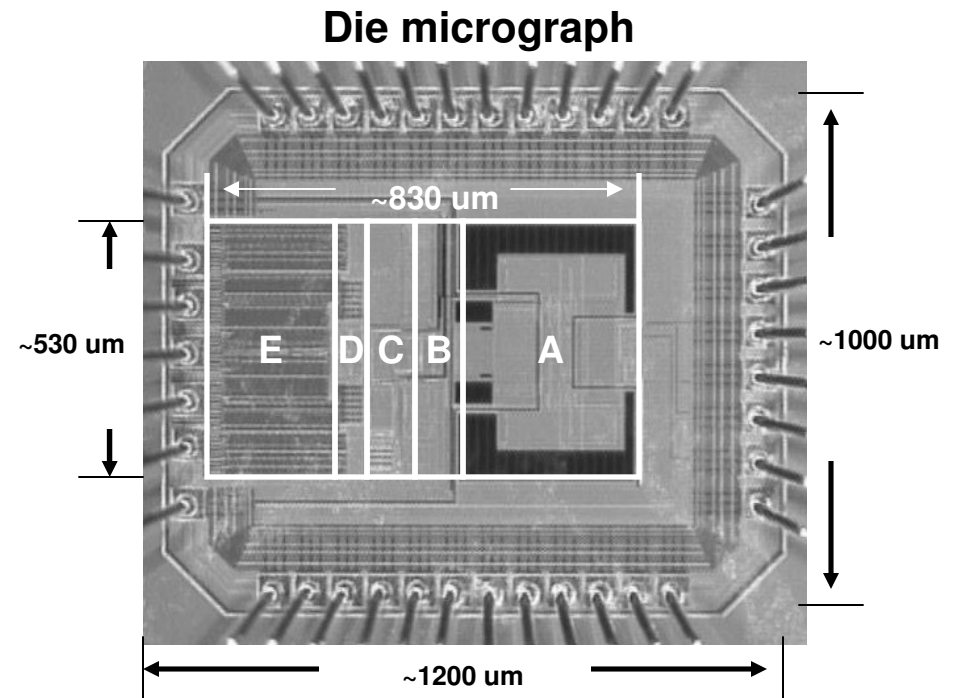- (A) – Loop Filter
- (B) – Comparator
- (C) – Ramp Generator
- (D) – POWER PMOS gate drive circuit
- (E) – Output MOSFET Devices





Block Specifications

→ *Integrator*

- DC Gain (amplifier)
- Bandwidth (amplifier)
- Noise
- CMRR
- THD
- Power & Area

→ *Comparator*

- Input Range
- Gain
- Noise
- Propagation Delay
- Rise & Fall time
- Power & Area

→ *Ramp Generator*

- Linearity
- Noise
- Amplitude
- Frequency
- Power & Area

→ *Bridge*

- R_{DSON}
- Propagation Delay
- Rise & Fall time
- Power & Area



Typical Specifications for Mobile Audio

Function	THD (dB)	SNR (dB)	Power (mW)	PSRR (dB) @217Hz	Load (ohms)
MP3 Audio (stereo)	90	93	32	65	16
			16		32
Polyphonic Ringer	60	76	500	65	8
Handset	60	76	500	65	8
Speaker Phone	60	76	500	65	8
			1000		4!!!

3/14/2005

36




More on Efficiency...

Non Ideal impacts on Class D Efficiency

- Quiescent power
- Power MOSFET R_{DSON}
- Switching Current in the bridge
- Shoot Through current in the bridge
- Current in the MOSFET body diodes during switching due to package and load inductances
- Non-ideal supplies
 - ◆ Output Resistance of source
 - ◆ Board trace route resistance & inductance
- Trapezoidal wave form vs. Square wave
 - ◆ The rise and fall period will reduce the maximum Efficiency
 - ◆ Efficiency loss is proportional to $T_{\text{Rise/Fall}}/T_{\text{Period}}$
 - ◆ Exacerbated by small pulse widths at zero crossings



More on Efficiency (cont)

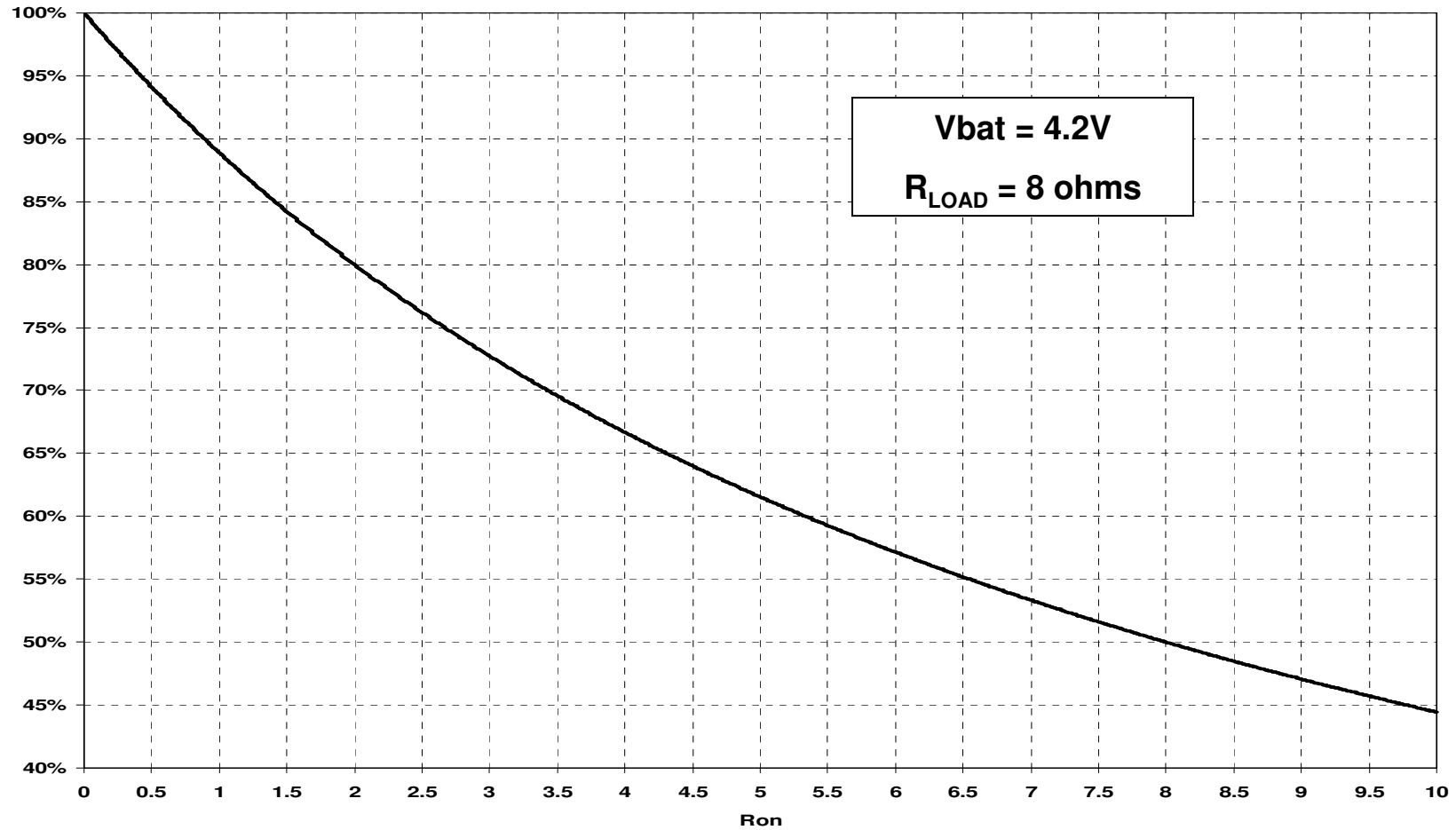


Effect of R_{DSON} on Power Efficiency

3/14/2005

38



Delivered Power

 


Effect of R_{DSON} on Power Delivery capabilities

3/14/2005

39



Testing Methodology

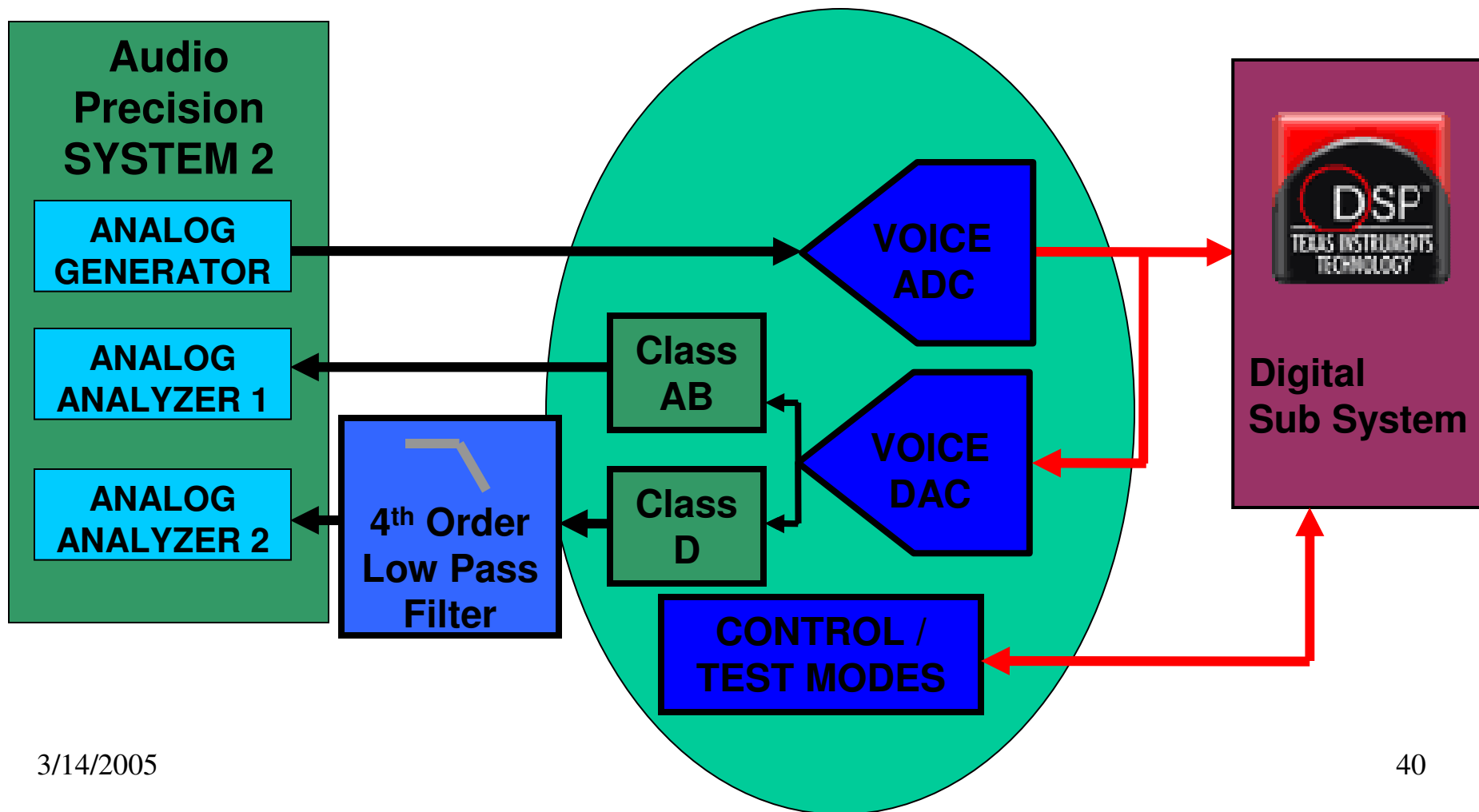

3/14/2005

40



Testing Challenges

- Highly non-linear PWM characteristics create undesired out of band energies
- Provide clean references for device operation within the system
- Measure PSRR with heavy demands on the supply from class D
- Ensuring the Reliability of the devices under lab testing conditions
 - Proper power supply sequencing
 - Special care during debug situations
- Board design with special consideration to the current and power levels required by Class D
- Extra filtering for accurate capture of data compared to continuous time power amplifiers

3/14/2005

41




Measurements

- Greater than 700 mW is delivered to 8 ohms
- THD Performance is better than 75 dB
- SNR Performance measured above 98 dB (referred to 1W)
- 75% Efficiency has been measured
- PSRR @ 217Hz is greater than 70 dB
- Power Supply Intermod of 217 Hz around 1 kHz output tone < -83 dBc
- Area is ~0.44 mm²
- System functional with $2.4 \text{ V} < V_{\text{battery}} < 6 \text{ V}$



THD vs. Power Delivered

 


**Peak performance measured from 20 –20kHz is >75 dB
($< 0.02\%$) at ~300 mW using a 1kHz test tone**

3/14/2005

43



Full Power Spectrum

 


3/14/2005

44



Efficiency vs. Power

 Efficiency of 75.5% is measured at ~380 mW using a 1kHz test tone*




3/14/2005

45



SNR vs. Frequency

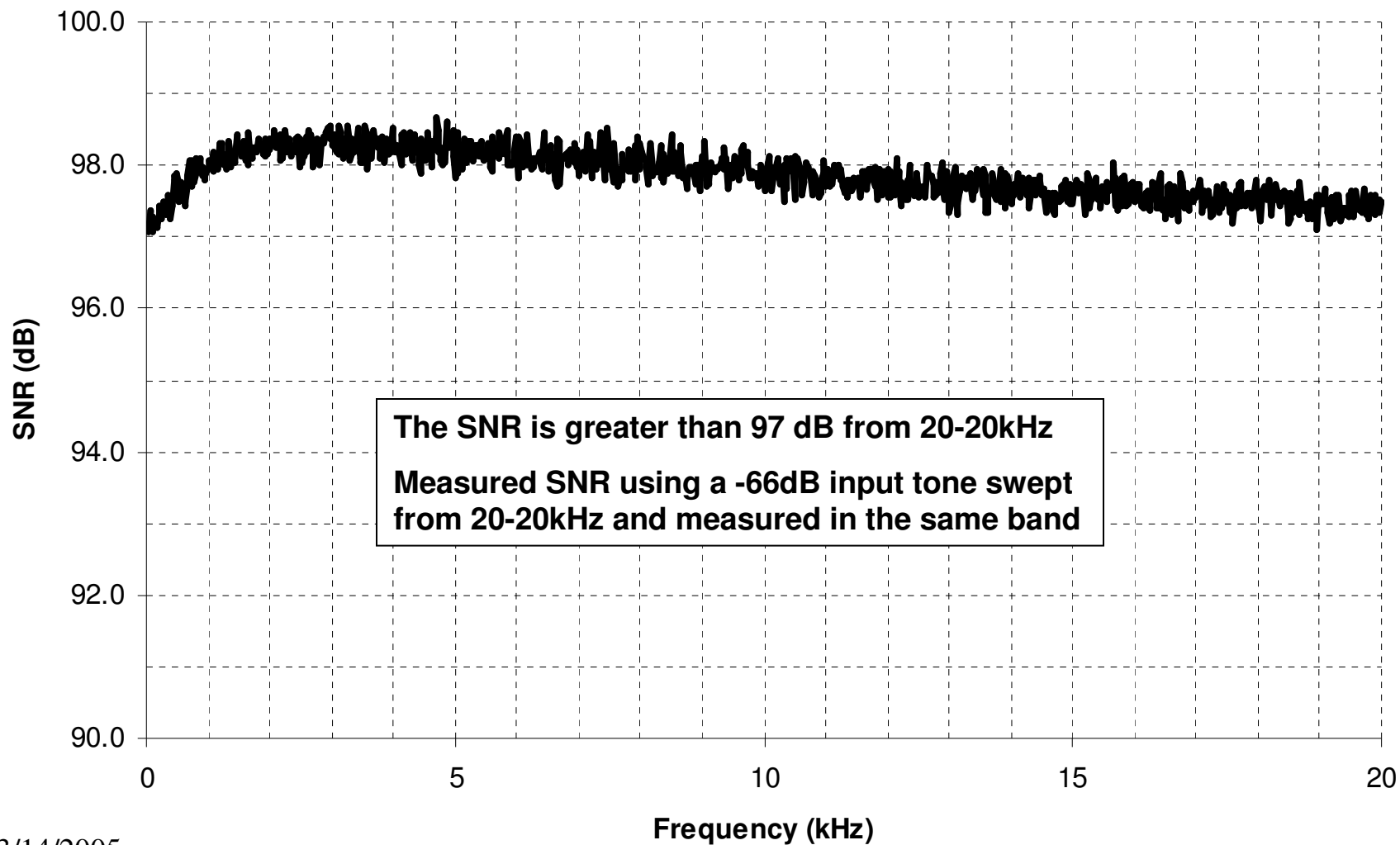


3/14/2005

46



PSRR vs. Frequency

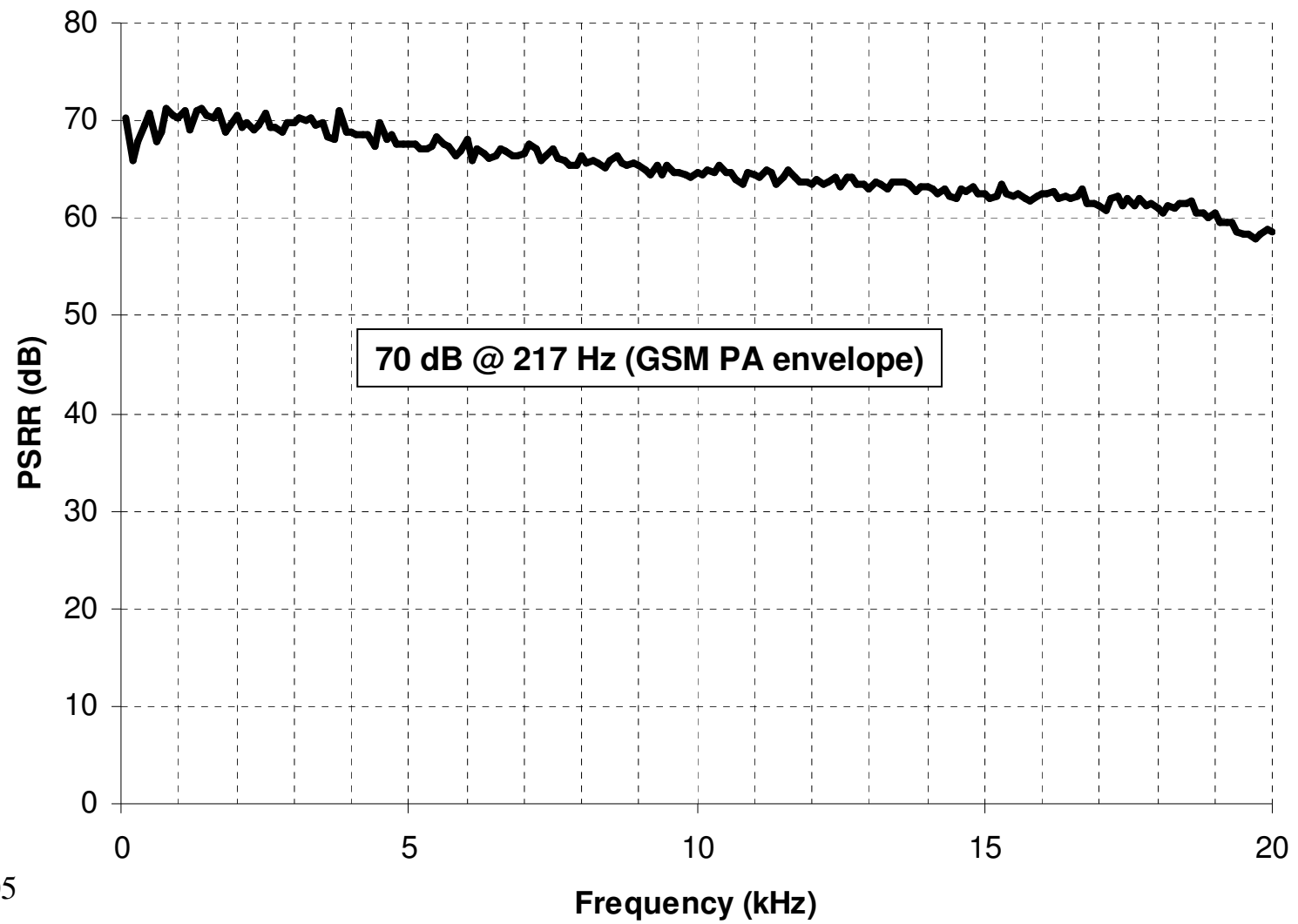


3/14/2005

47



PS Inter-modulation Test Spectrum

 


3/14/2005

48



PS Intermod Spectrum (No Disturbance)

 

3/14/2005

49



Conclusion

- ➔ High Efficiency power amplifiers are essential to the future of Audio Enabled Mobile devices
- ➔ Integration of Audio Power Amplifiers provides cost efficient and flexible system partitioning options
- ➔ High efficiency & power Audio performance Class D amplifier has been demonstrated in 90 nm digital CMOS technology
 - 73 dB THD
 - 70 dB PSRR @ 217 Hz
 - 83 dB Power Supply Inter-modulation Rejection around Carrier
 - 93 dB SNR (referred to 330 mW)
 - 75% Efficiency
 - > 700 mW output
 - 0.44 mm²



Acknowledgements

I would like to acknowledge the help of all those at TI who have made this design and presentation possible

- *Vijay Rentala – Design*
- *Jose Arteaga – Characterization & Test*
- *Srinath Ramaswamy – Design*
- *Francisco Ledesma – Design*
- *Jagadeesh Krishnan – Design*
- *Patti Menefee – Layout*
- *Abdelaziz Ketani – Layout*
- *Jimmy Tran – Layout*
- *Clif Jones – Consultation*
- *Paras Dagli – Consultation*
- *Wayne Chen – Consultation*
- *Lars Ribo – Consultation*
- *Gangadhar Burra – Management*
- *Baher Haroun – Management*