

Mixed-Signal Measurement Circuits For Embedded Test Access

**Gordon W. Roberts
McGill University**


(Presently on leave with DFT MicroSystems)

October 26, 2003


Outline

- ➔ Introduction
 - On-Chip Instruments
 - Signal Generators
 - Sampling Oscilloscopes
 - Coherent Sampling Test System
 - Time Domain Reflectometry & Transmission
 - Timing Analyzers
 - Conclusions

System On-A-Chip / In-A-Package

 


Component-Based Design

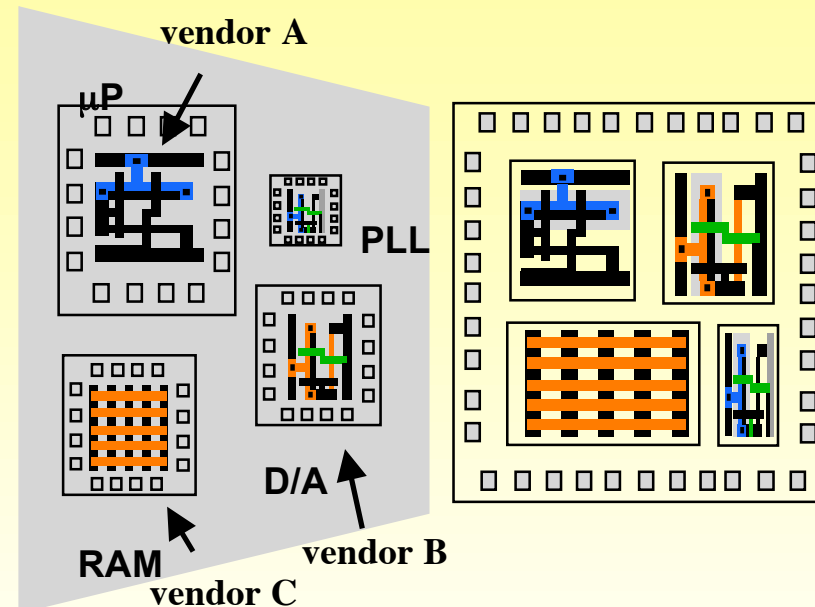


Core-Based Design

- **More and more components are being integrated into smaller and smaller devices/packages.**
 - **Gaining test access to ALL components is becoming increasingly more difficult.**

Embedded Test Capability

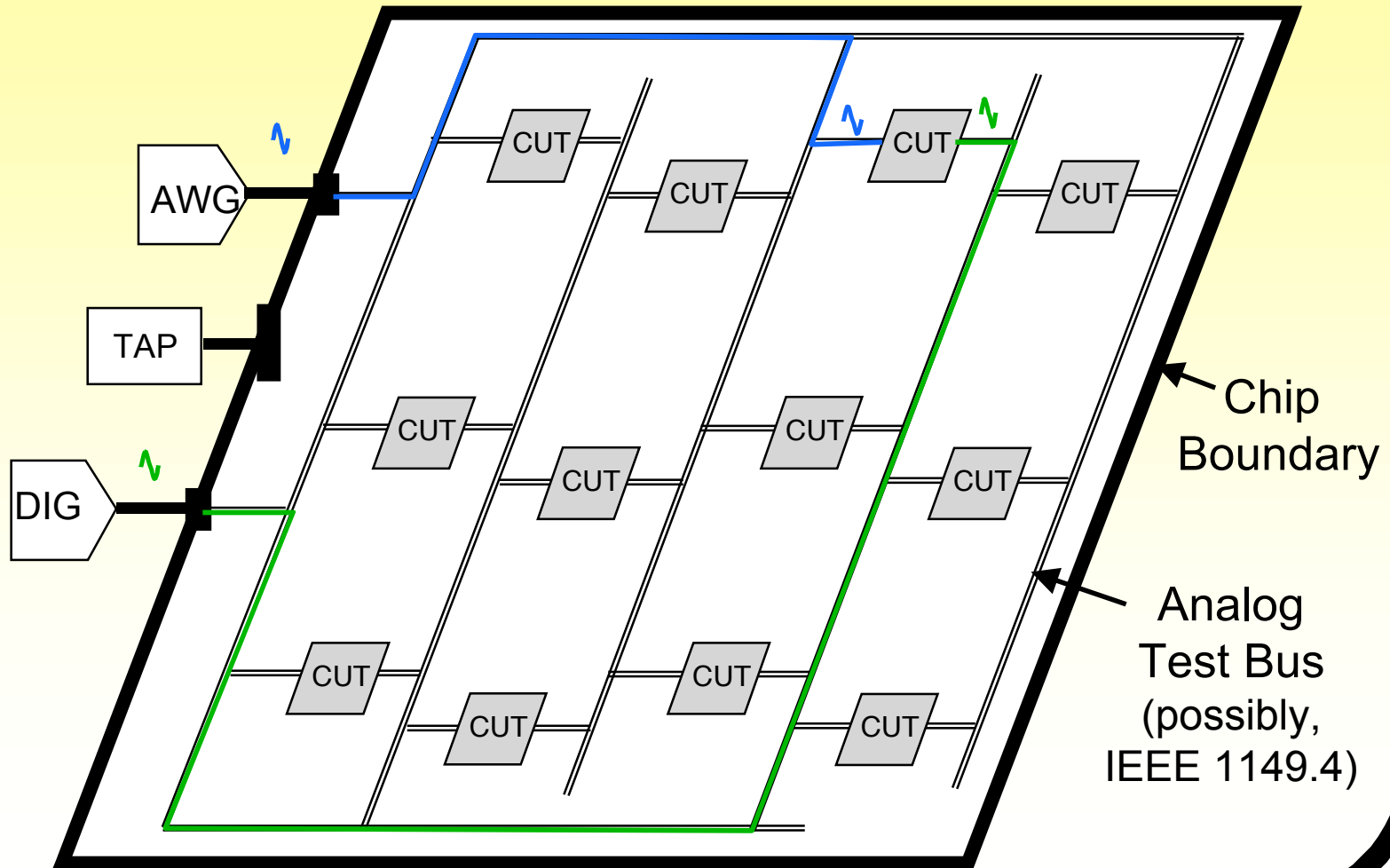


Test Bus / Test Ports

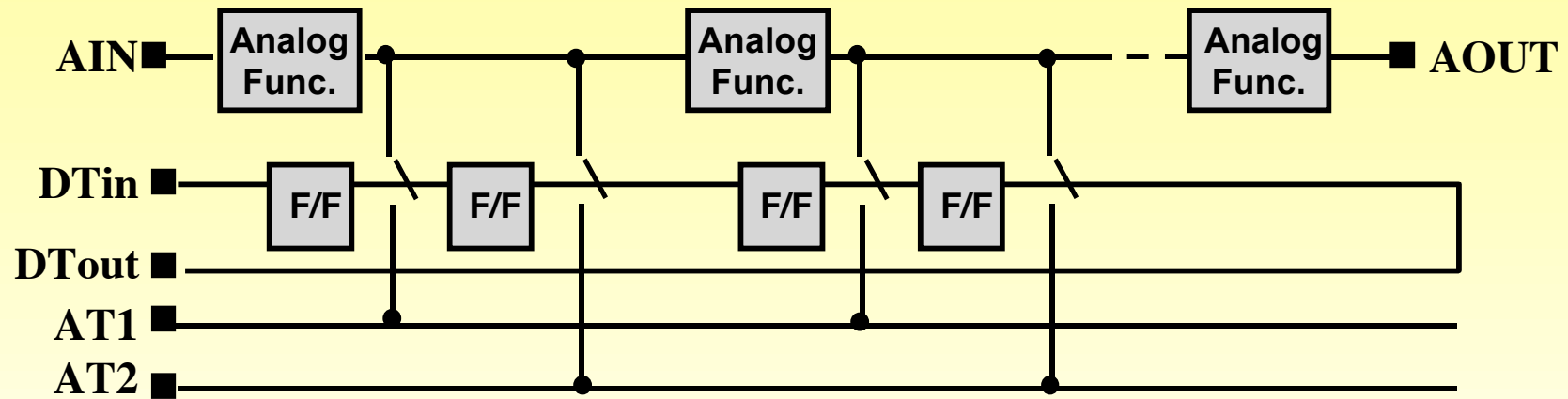


- A test bus provides **observability** and/or **controllability** of internal nodes on an IC/board/system.
- Standardizing the pins of the test port facilitates test set-up and program re-use.
 - IEEE industrial standard (IEEE 1149.4).
- Good analog switches are difficult to realize in advanced CMOS.

Moving Test Instruments Directly On-Chip

 

Move the test equipment to the signals-under-test rather than the signals to the test equipment!


Improving Diagnostic Capability

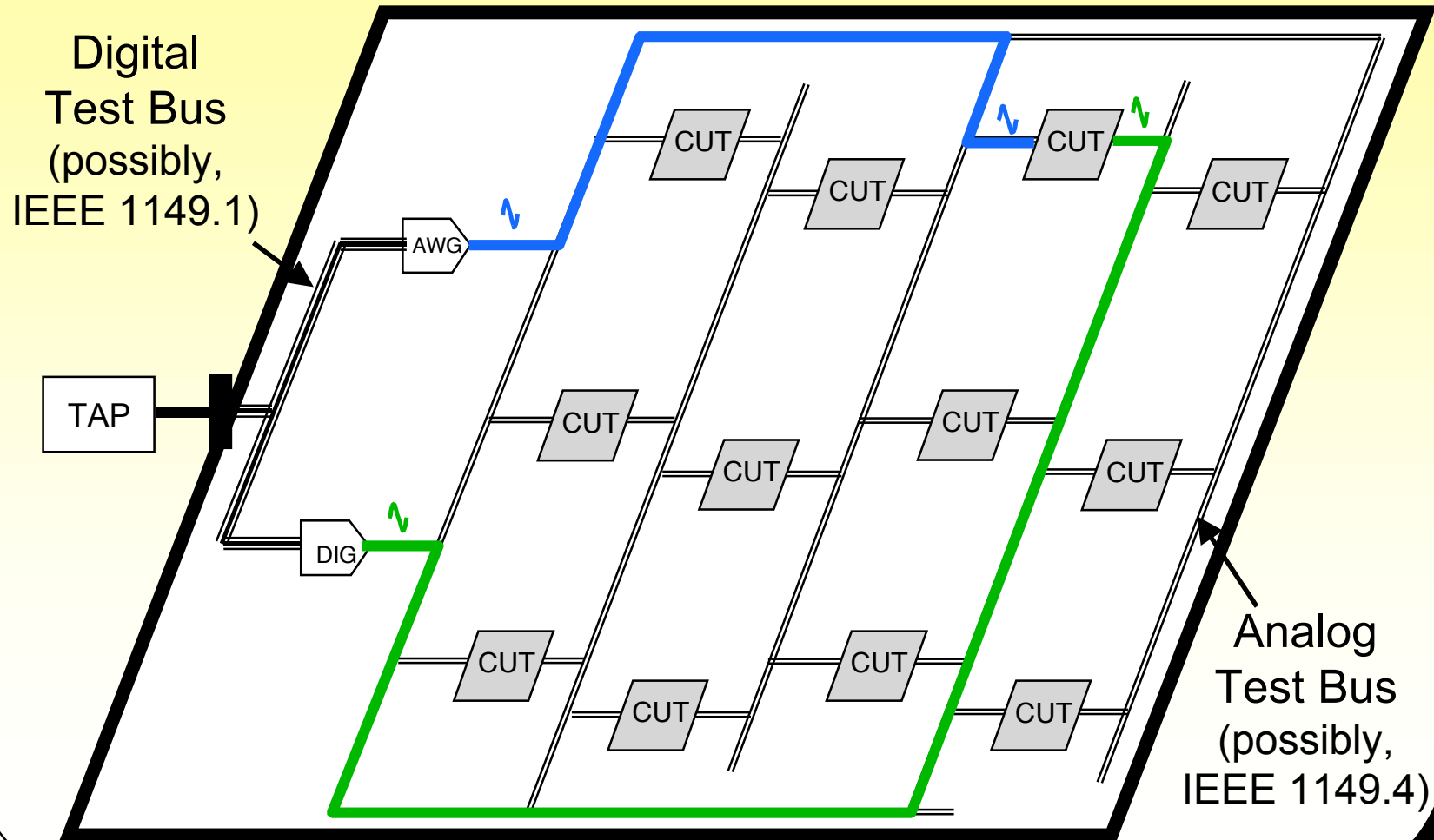


Improving SOC Test Times

Digital Test Bus
(possibly, IEEE 1149.1)

TAP

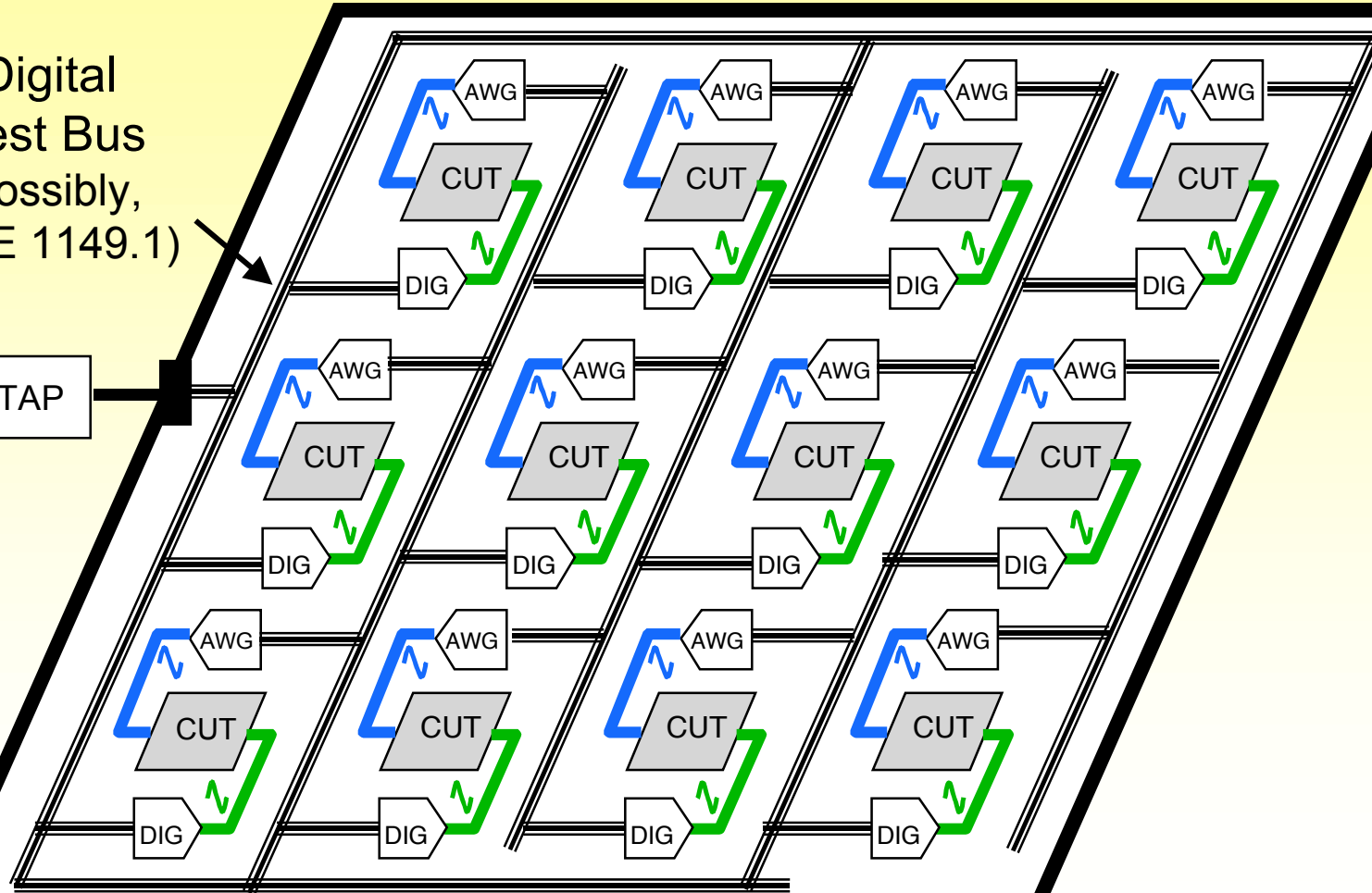

Design For Manufacturability

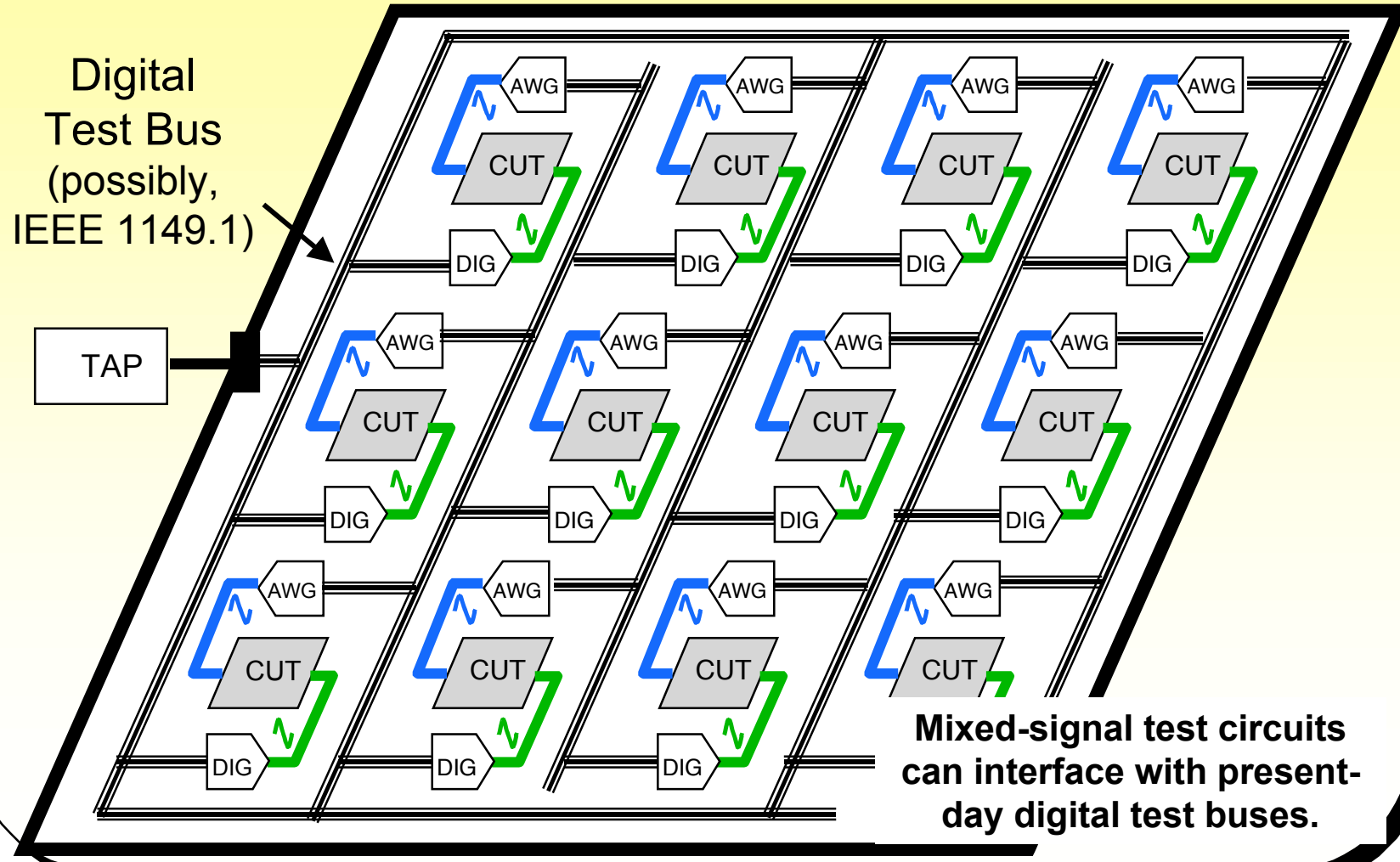

Mixed-signal test circuits can interface with present-day digital test buses.


Outline

- Introduction
- ➔ On-Chip Instruments
 - Signal Generators
 - Sampling Oscilloscopes
 - Coherent Sampling Test System
 - Time Domain Reflectometry & Transmission
 - Timing Analyzers
- Conclusions

Analog Signal Generation

Conventional Analog Signal Generation:

 - Tuned oscillator circuits
- Relaxation oscillator circuits




Problem for On-Chip Solution:

- Low-Q operation unless using crystals.
- Difficult to control amplitude, frequency and multi-tone signals.
- Frequency and amplitude sensitive to absolute value of components.



Analog Signal Generation

Using Direct Digital Frequency Synthesis

 

- A digital signal is numerically created and converted to analog form using a D/A circuit.
- Advantages:
 - Largely digital, stable signal generation and fully programmable (both amplitude and frequency).
 - Frequency set by system or external clock.
 - Coherent measurement system - fastest measurement
- Disadvantages:
 - Large silicon area requirement.

  
Data Conversion Using Delta-Sigma Modulation



- Delta-sigma modulation converts multi-bit precision signals into a single-bit digital pattern
- Pulse Density Modulation, PDM


Single-Bit Generation

 - Record a portion of a $\Sigma\Delta$ output
- Reproduce it periodically
 - Easily implemented
 - High speed
- Desired Tone, same Frequency and Amplitude as input





Scan-Chain Generator

Analog & Digital Signals

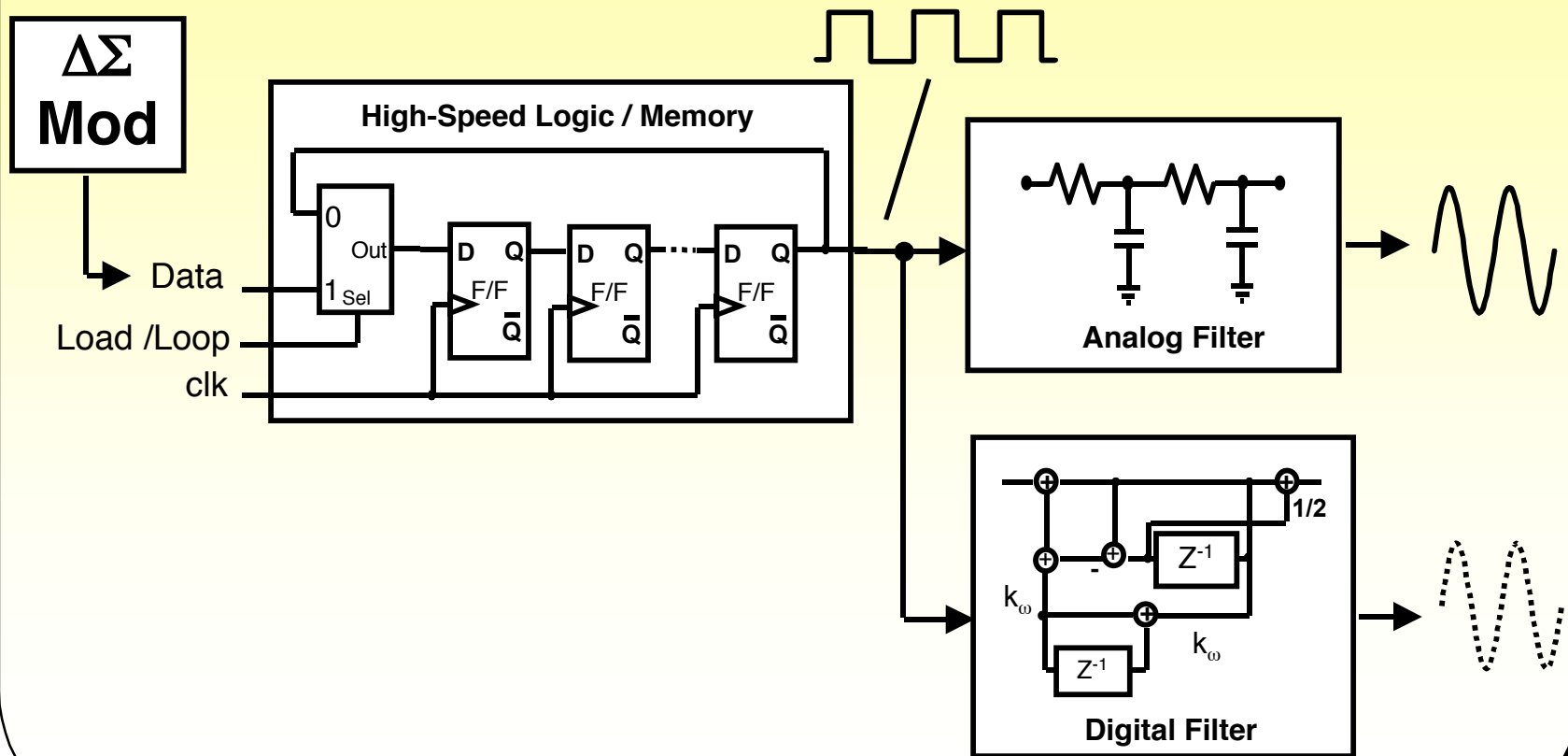


Signal Generation Equations

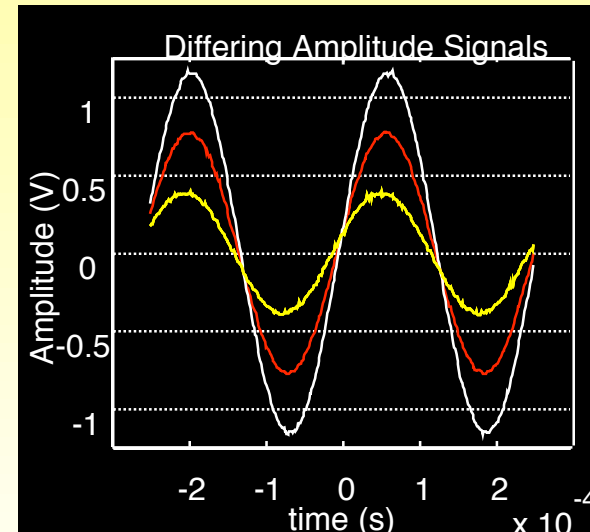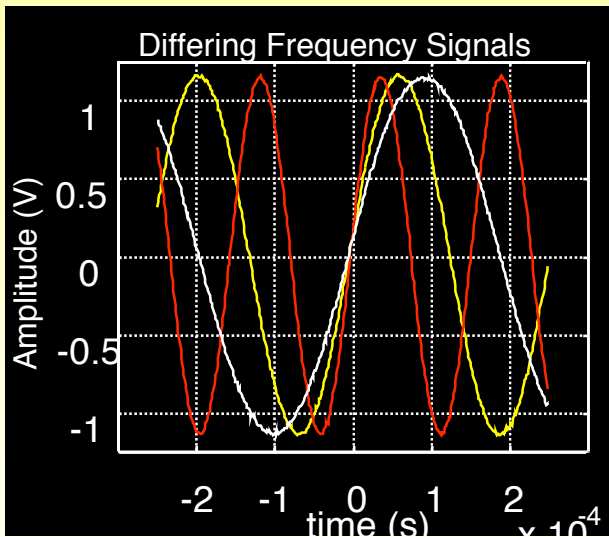


- Both frequency and amplitude of test signal can be controlled by changing the density of 1's and 0's in the digital pattern.

392-Bit Sine Wave

 

Power Density Spectrum

 


Oscilloscope Trace


- Go to web-site <http://www.macs.ece.mcgill.ca/~roberts/> to download other examples

Multi-Tone Waveform

Two-Tone Frequency Spectrum

 


Two-Tone Oscilloscope Trace

 


- example of a reconstructed two-tone signal

Sawtooth Waveform

Frequency Spectrum of Sawtooth

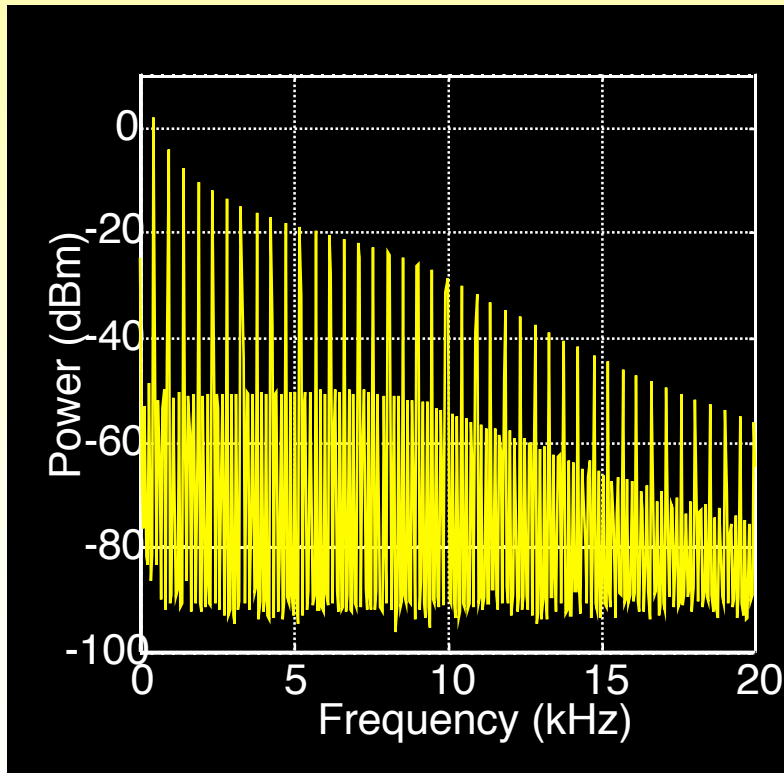

Scope Trace of Sawtooth

 


- 476 Hz sawtooth (infinite-tone) reconstruction

Outline


- Introduction
- On-Chip Instruments
 - Signal Generators
 - ➔ Sampling Oscilloscopes
 - Coherent Sampling Test System
 - Time Domain Reflectometry & Transmission
 - Timing Analyzers
- Conclusions

Test Bus With On-Chip Buffers

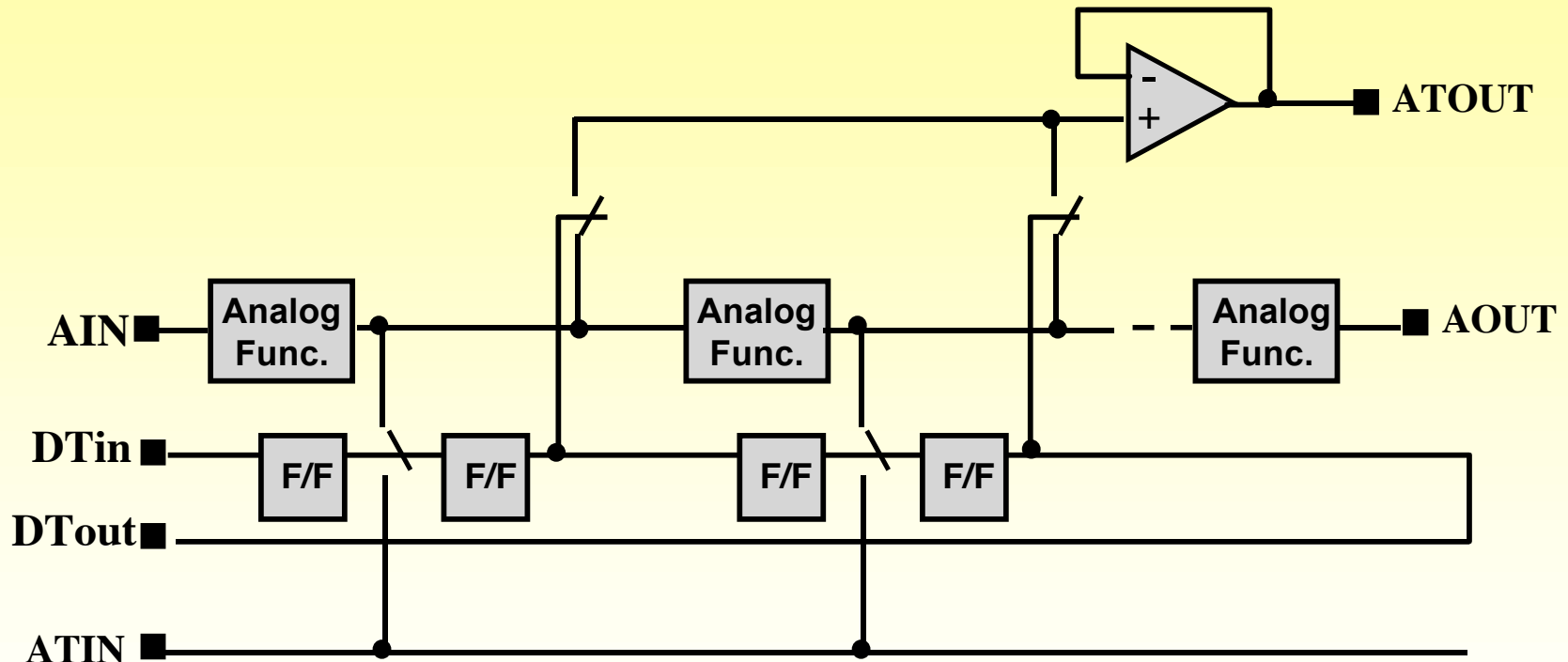


- A test bus often has an on-chip voltage buffer to drive off-chip loads.

Test Bus With On-Chip Comparator

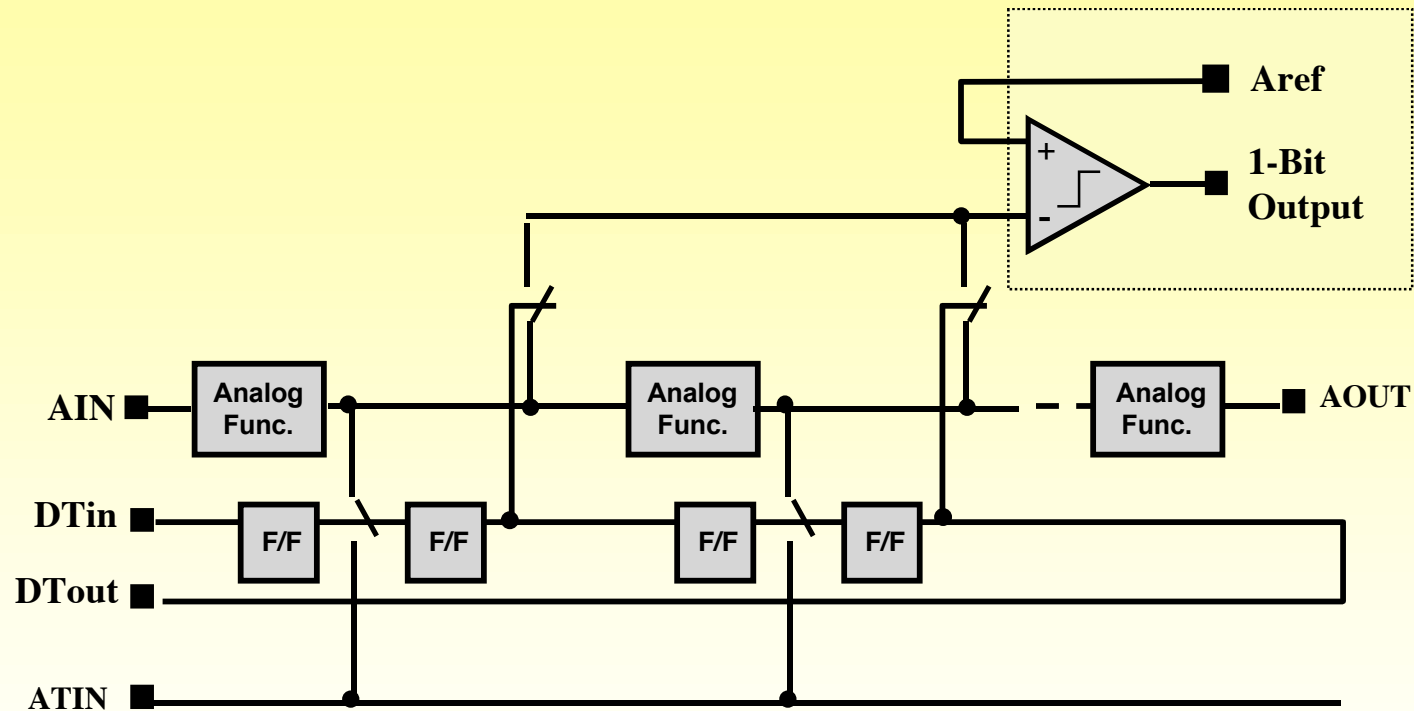

- A test bus can be turned into a sampling oscilloscope by replacing the voltage buffer with a 1-bit comparator.
 - Only digital signals are moved across the chip boundary.

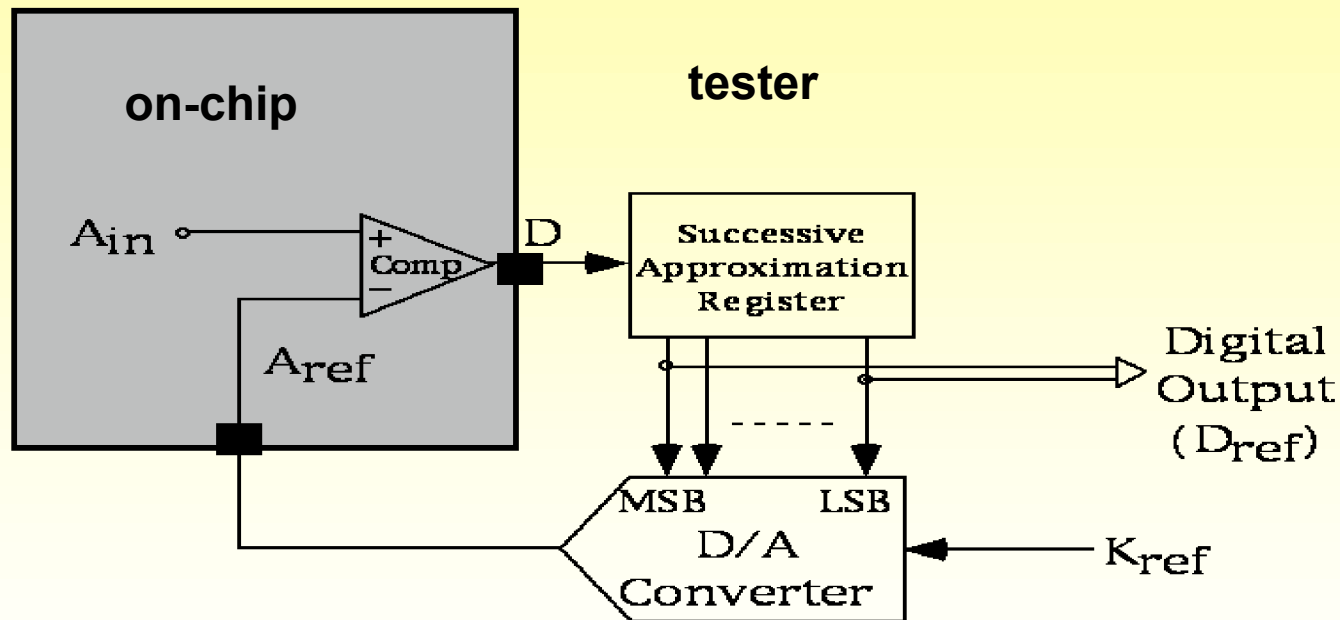
A/D Conversion Algorithm (successive-approximation process)



$$A_{in} = K_{ref} \left(\frac{b_1}{2^1} + \frac{b_2}{2^2} + \frac{b_3}{2^3} + \dots + \frac{b_N}{2^N} \right)$$

On-Chip Oscilloscope

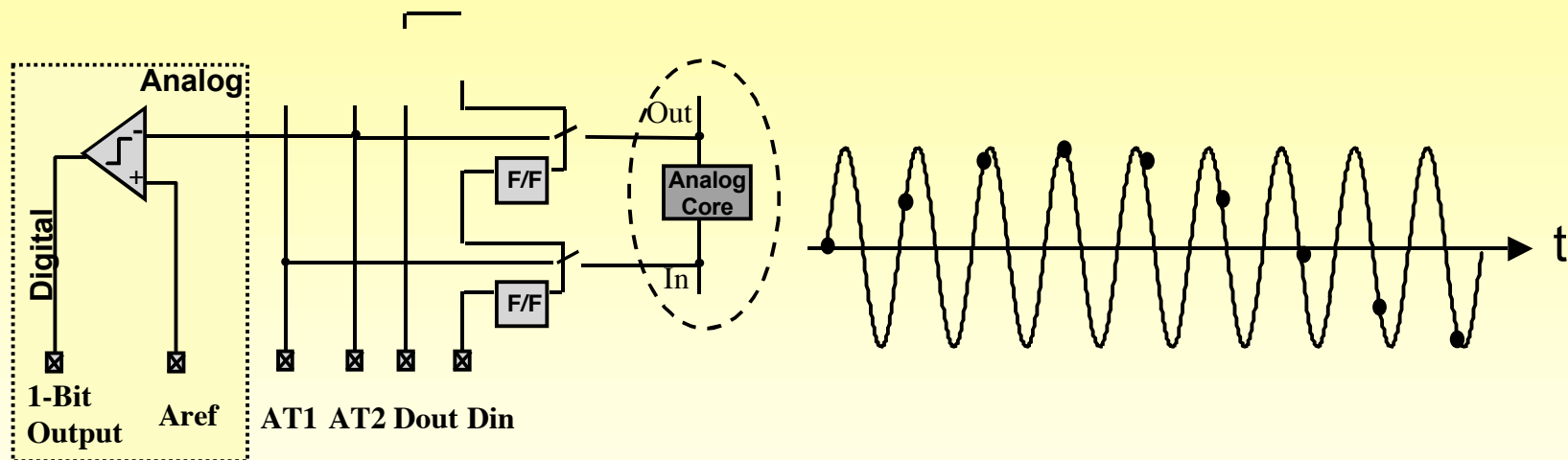(High-Speed Signals Observed Using Subsampling)



Chip Configured for
IEEE1149.1/1149.4 Test Bus


Subsampling Principle

- K. Loström, "Early capture for boundary scan timing measurements," Proc. of the International Test Conference, pp. 417-422, Oct. 1996.
- A. Hajjar and G. W. Roberts, International Test Conference, 1998.

Outline

- Introduction
- On-Chip Instruments
 - Signal Generators
 - Sampling Oscilloscopes
 - ➔ Coherent Sampling Test System
 - Time Domain Reflectometry & Transmission
 - Timing Analyzers
- Conclusions

Coherent Test System

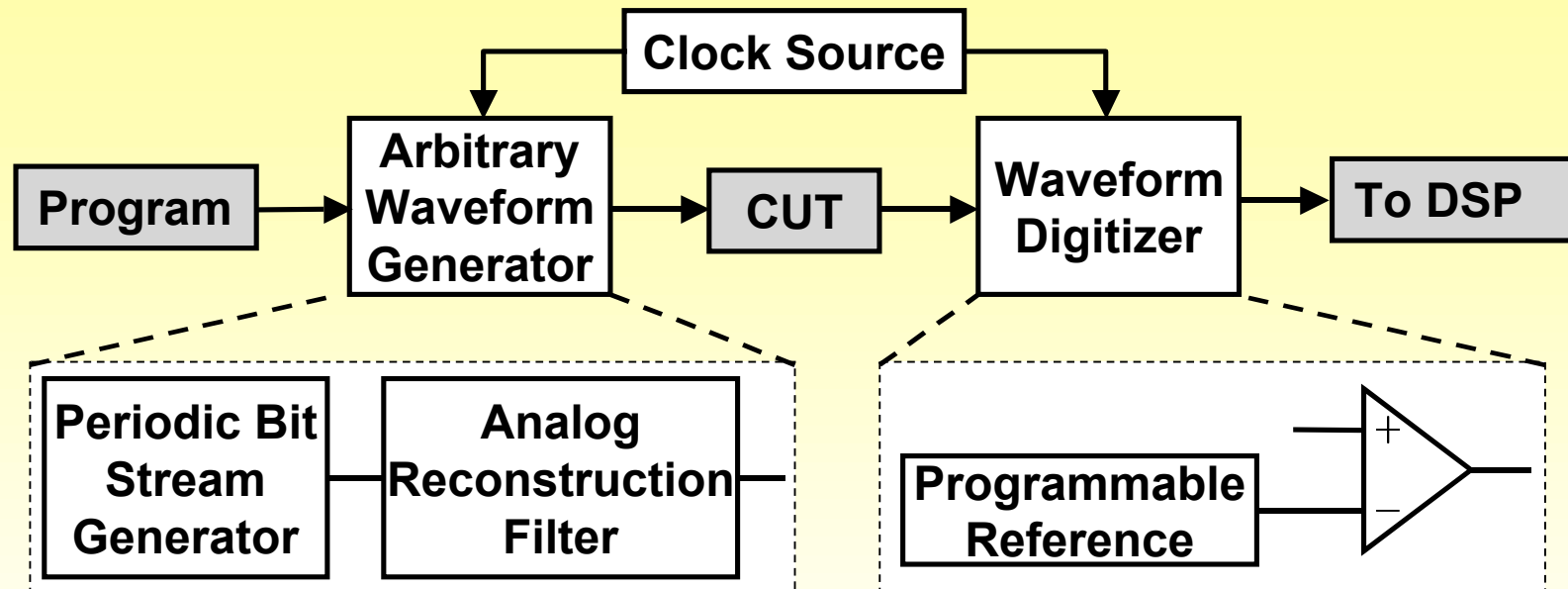


- Functional diagram identical to that of a generic DSP-based test system
- Unified clock guarantees coherence between the generation and measurement subsystems

* M. Hafed, N. Abaskharoun and G. W. Roberts, "A 4 GHz Effective Sample-Rate Integrated Test Core for Analog and Mixed-Signal Circuits," IEEE Journal of Solid-State Circuits, Vol. 37, No. 4, pp. 499-514, April 2002.


Signal Generation

Periodic $\Delta\Sigma$ Bit Stream Approach

 - Output of $\Delta\Sigma$ modulator is approximated using a short repetitious sequence of bits
- Very short sequences demonstrate high spectral purity analog signals




Waveform Digitizer Implementation

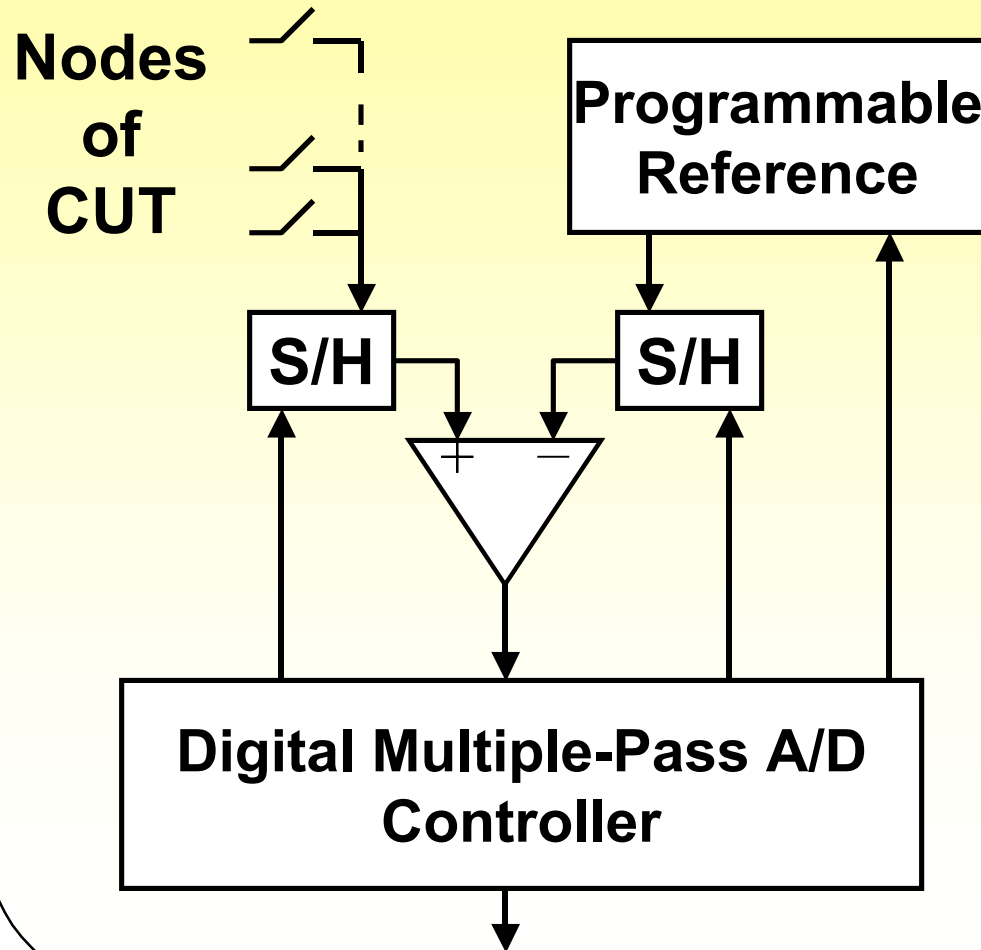

- No Specific requirements on comparator
- S/H decouples sampling rate from comparator conversion rate
- M. Hafed & G. Roberts ITC'2000

Programmable Reference Generator

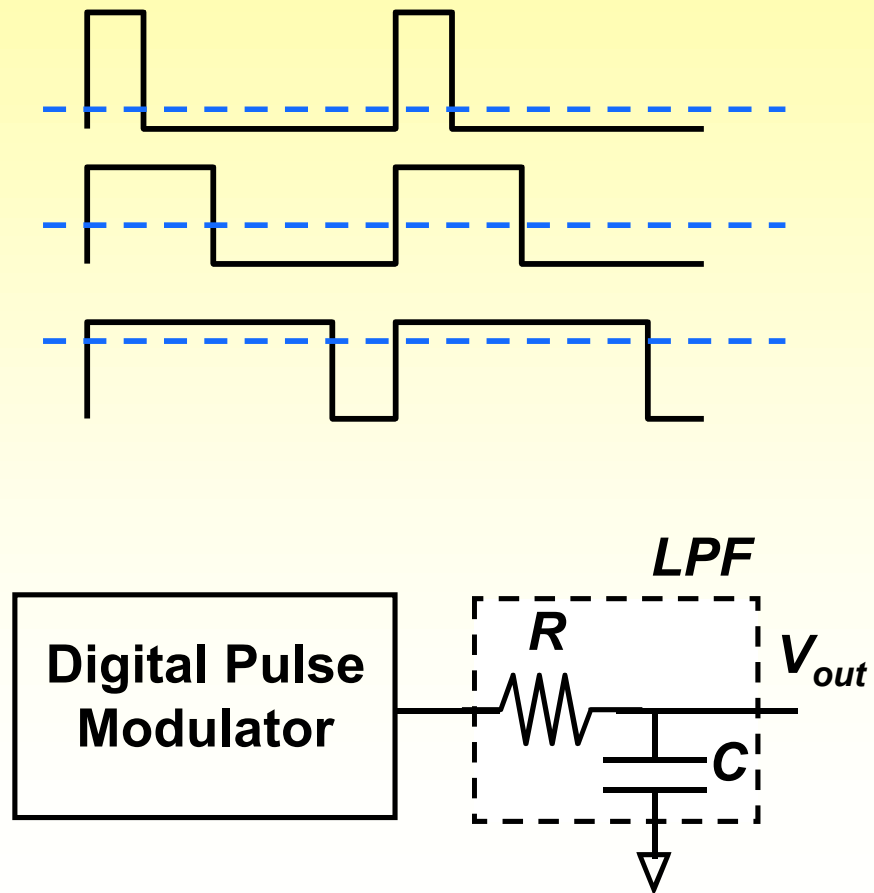- DC level is encoded in the average of a finite-length periodic digital bit sequence
- Passive on-chip filter achieves area efficiency, simplicity, and robustness




Passive Filtering


- Passive RC does not alter DC component regardless of the values of R and C:

$$|H(f)| = \frac{1}{\sqrt{1 + (2 \cdot \pi \cdot f \cdot R \cdot C)^2}}$$

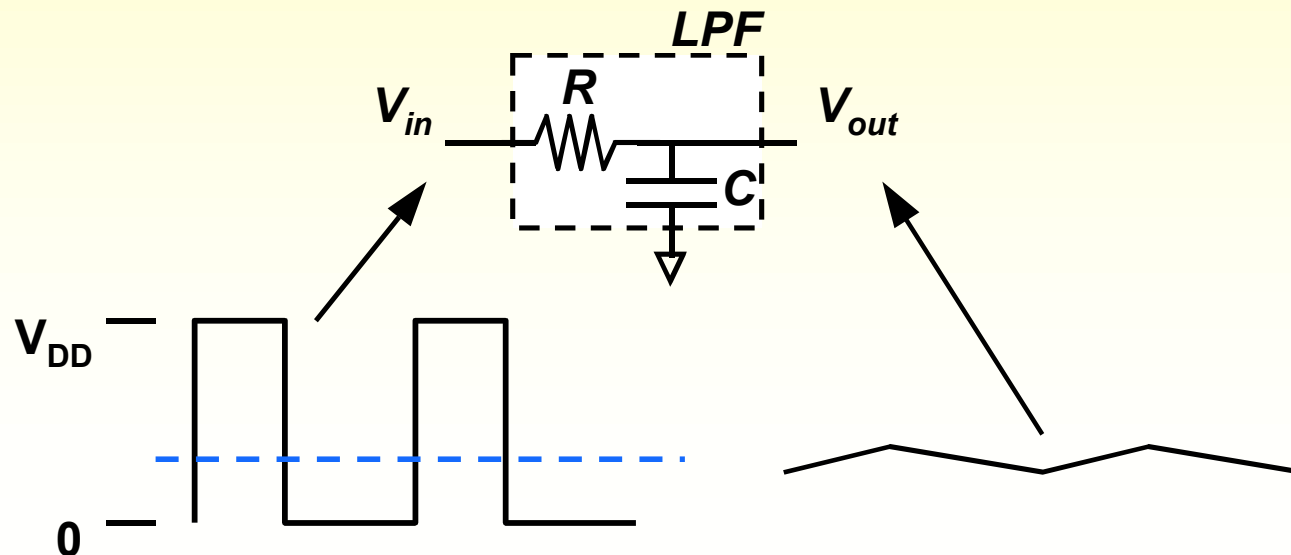- Filter trades off amplitude resolution (allowable ripple) versus speed (settling time)




PWM Frequency Domain Description

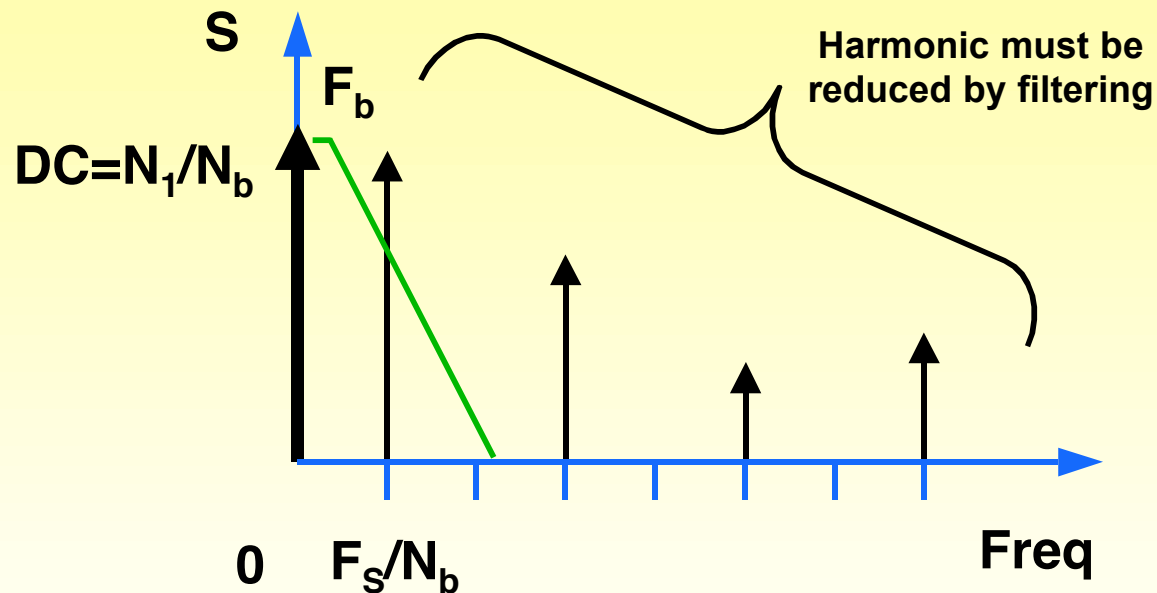

- The DC tone has a magnitude which is dependent on the ratio of 1's (N_1) to the total number of bits in the digital periodic sequence (N_b).
- The magnitude and distribution of the AC harmonics depend on the sequence of 1's and 0's in the bitstream.



PDM Frequency Domain Description

 

- Using Pulse Density Modulation (PDM) has the effect of pushing most of the harmonic power higher in frequency therefore alleviating the filter requirements.
- DC Patterns can be generated in the exact same way as for the AC signals.


Digitization Using On-Chip Comparators

  - A_{ref} is successively modified until the quantization level of the sample-under-test is determined




- Inherent sub-sampling operation means high effective sampling rate

Multipass Method

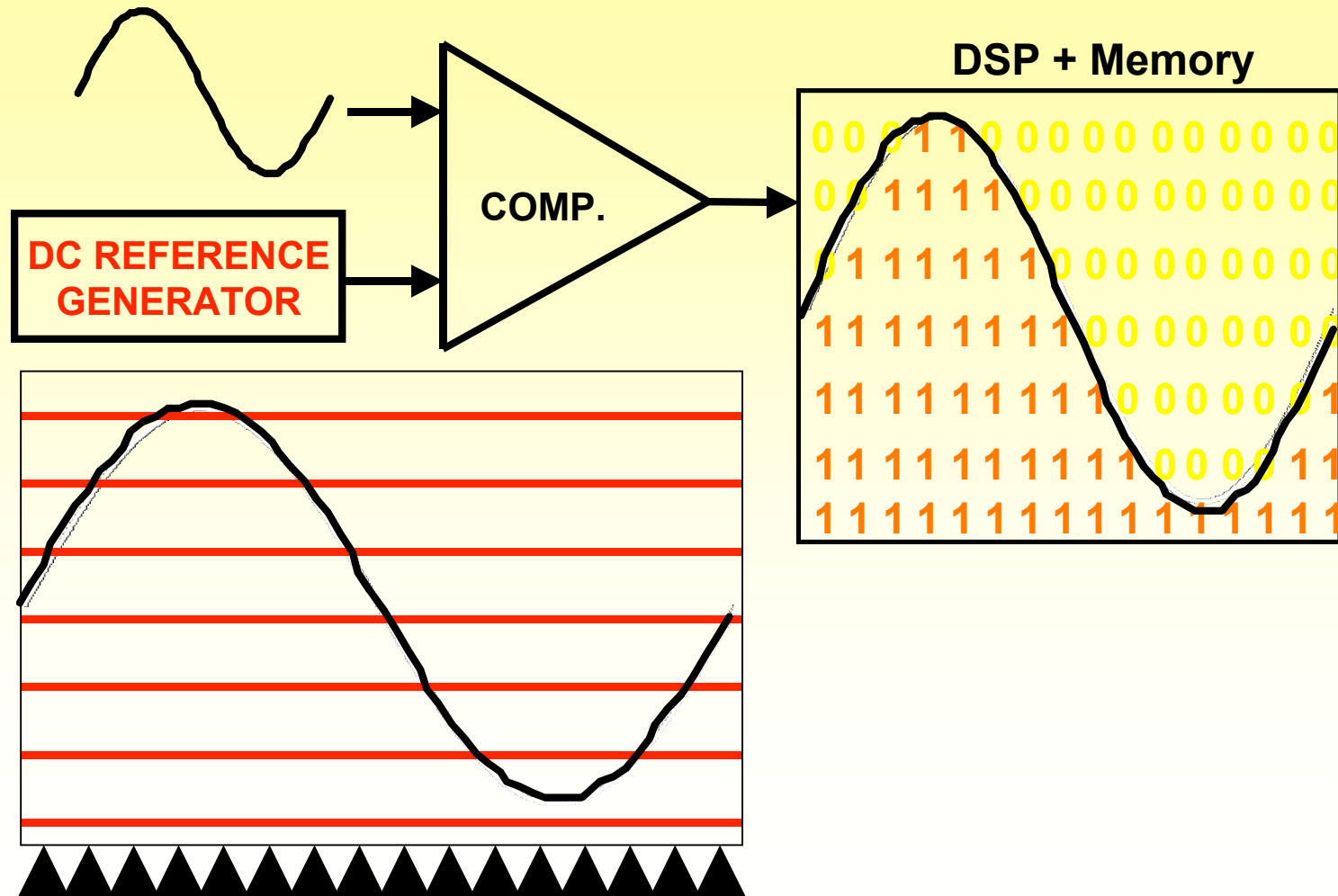

Almost All-Memory Implementation

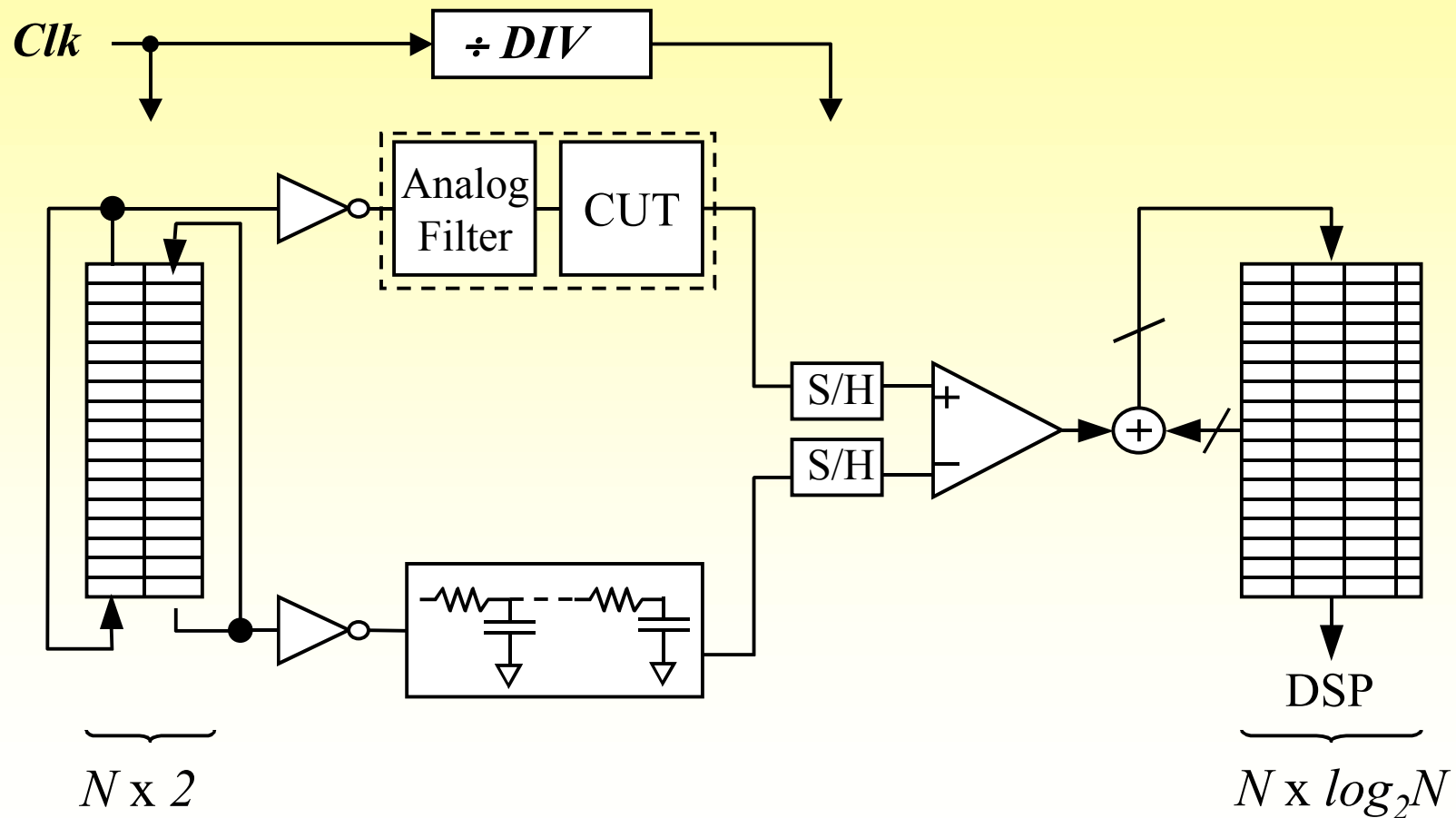

US & Canada Patent Pending

8-Bit, 4 GHz AWG & Digitizer

M. Hafed & G. Roberts CICC'2000, JSCC April 2002


Chip Details

- Technology: 0.35 μm , 3.3 V CMOS
- Amplitude Resolution: 8 bits
- Effective Sampling Rate: 4 GHz
- Time resolution (off-chip): 200 ps
- SFDR: 65 dB @ 500 kHz
40 dB @ 500 MHz

Periodic Bit
Stream
Generator

Programmable
Reference

S/H, Comparator,
A/D Controller

 

10-Bit, 4 GHz AWG & Digitizer

M. Hafed & G. Roberts / Wireless Test Workshop 2001


Chip Details

- Technology: 0.35 μm , 3.3 V CMOS
- Amplitude Resolution: 10 bits
- Effective Sampling Rate: 4 GHz
- Time resolution (on-chip): 200 ps
- SFDR: 65 dB @ 500 kHz
40 dB @ 500 MHz


Periodic Bit
Stream
Generators

Digitizer


Timing Module

 

 Measured Performance Curve-Tracer Functionality




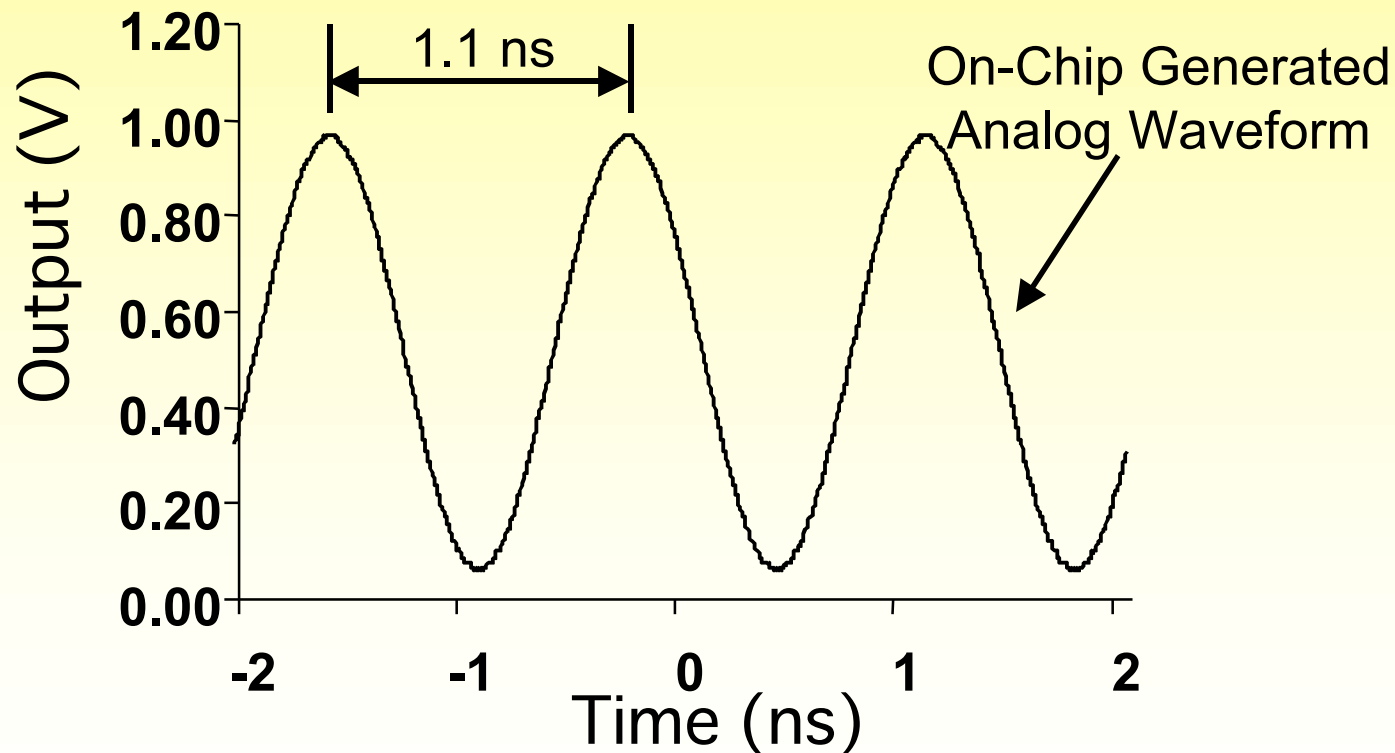Measured Performance Oscilloscope-Like Functionality




Maximum harmonic error: < 0.01%

Waveform Digitizer Measured Performance

 


Measurement Capability

Spectrum Analyzer-Like Functionality

 


- On-chip measurement result compared to actual measurement on a HP3588 Spectrum Analyzer

Interfacing With Off-Chip Eqmt

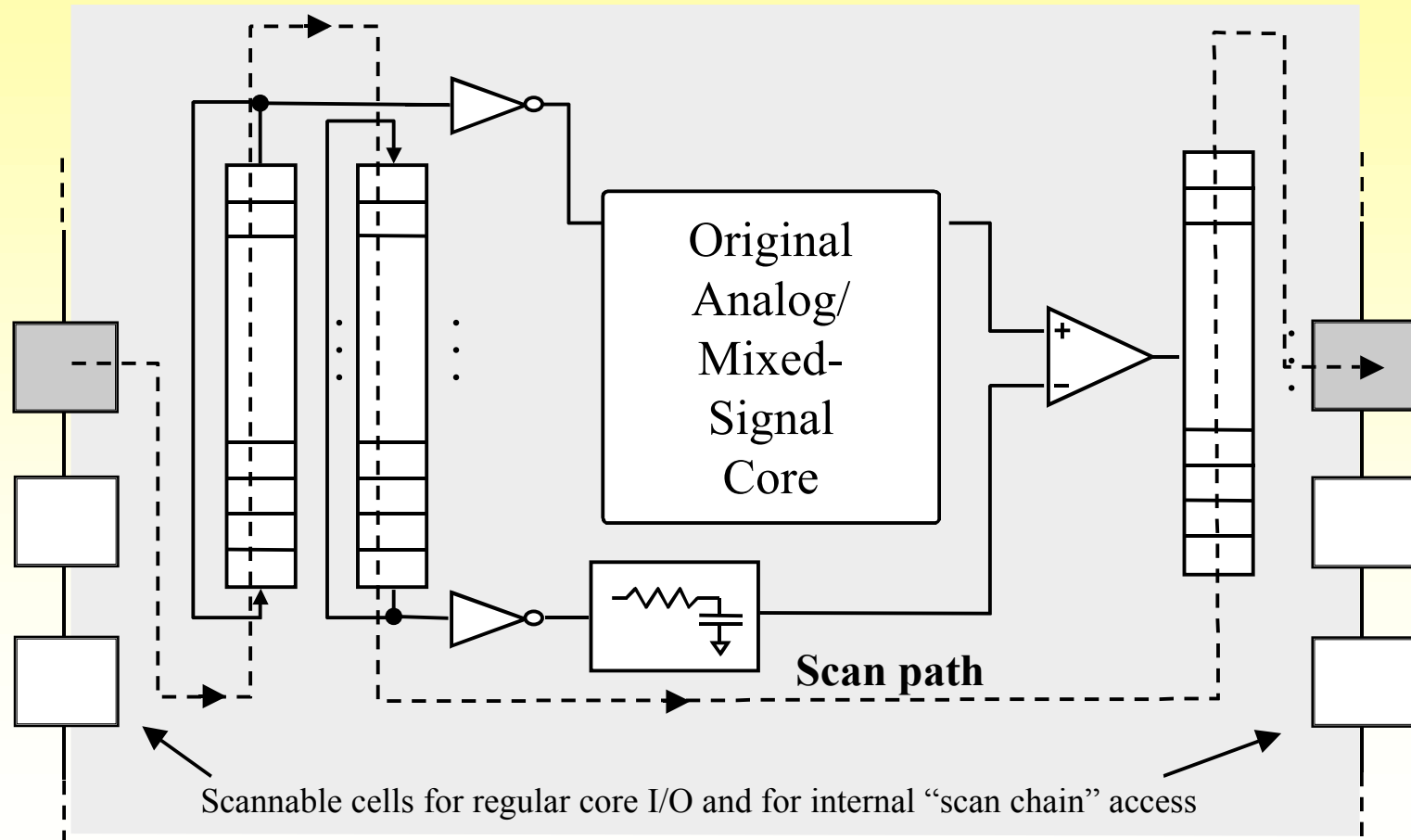


Moving Scan Chains Off Chip

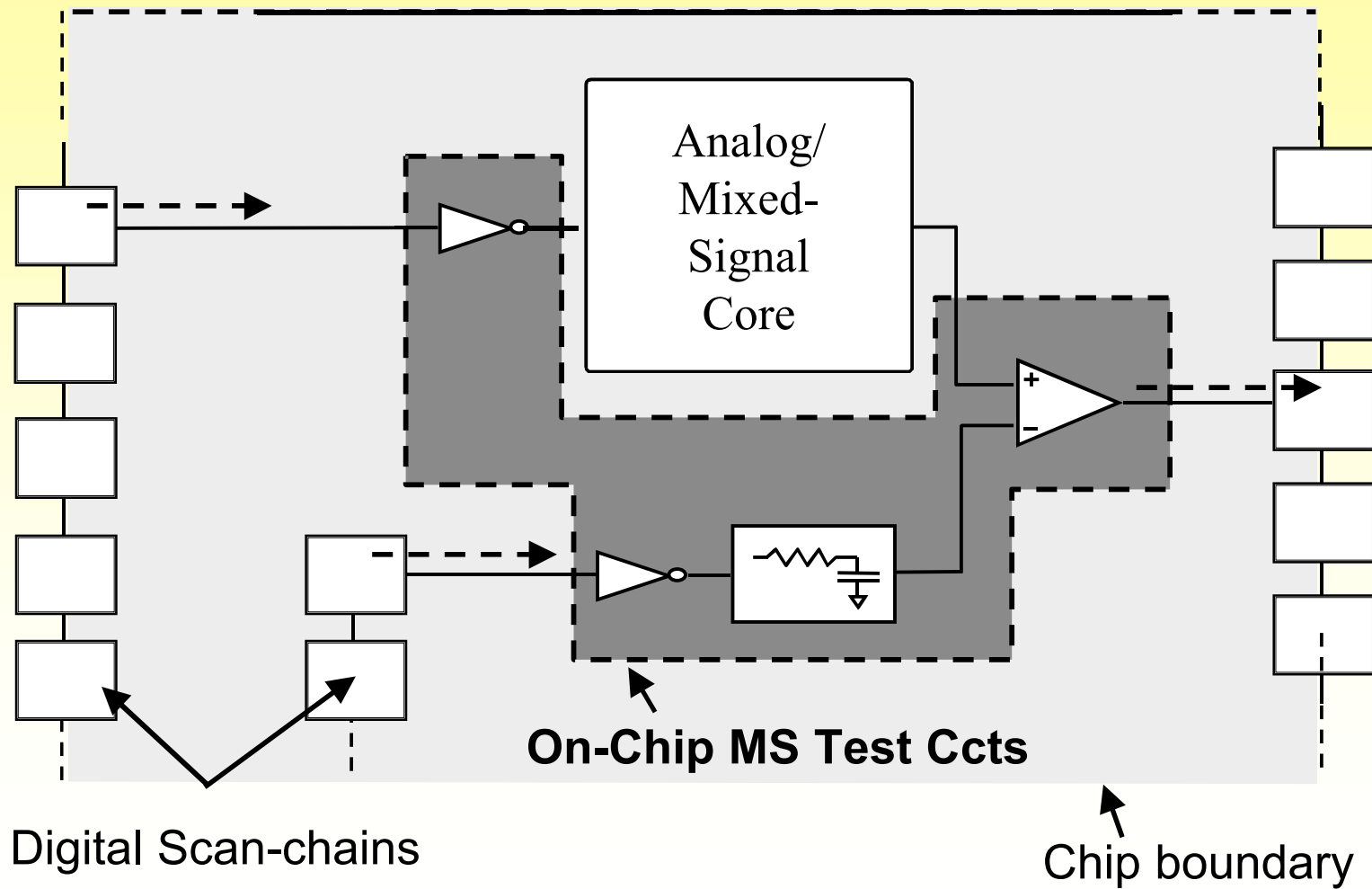

Outline

- Introduction
- On-Chip Instruments
 - Signal Generators
 - Sampling Oscilloscopes
 - Coherent Sampling Test System
 - ➔ Time Domain Reflectometry & Transmission
 - Timing Analyzers
- Conclusions



Board Testing: Time Domain Reflectometry

 


- Board-level interconnect
- 8-bit resolution
- 4-GHz sample rate

Board-Level TDR at 4 GSample/s

  - Board-level interconnect
- 8-bit resolution
- 4-GHz sample rate




Crosstalk Characterization

 

- Investigating on-chip crosstalk effects is often performed with a multi-conductor structure using different forms of signal excitation.
 - On-chip behavior is often difficult to obtain due to package parasitics and equipment loading effects.

10 GHz Sampling Scope Prototype


(M. Hafed & G. Roberts CICC 2003)

 


Area per DIG: 0.044 mm² (8-Bit Sampler)

10-GHz TDT Experimental Results

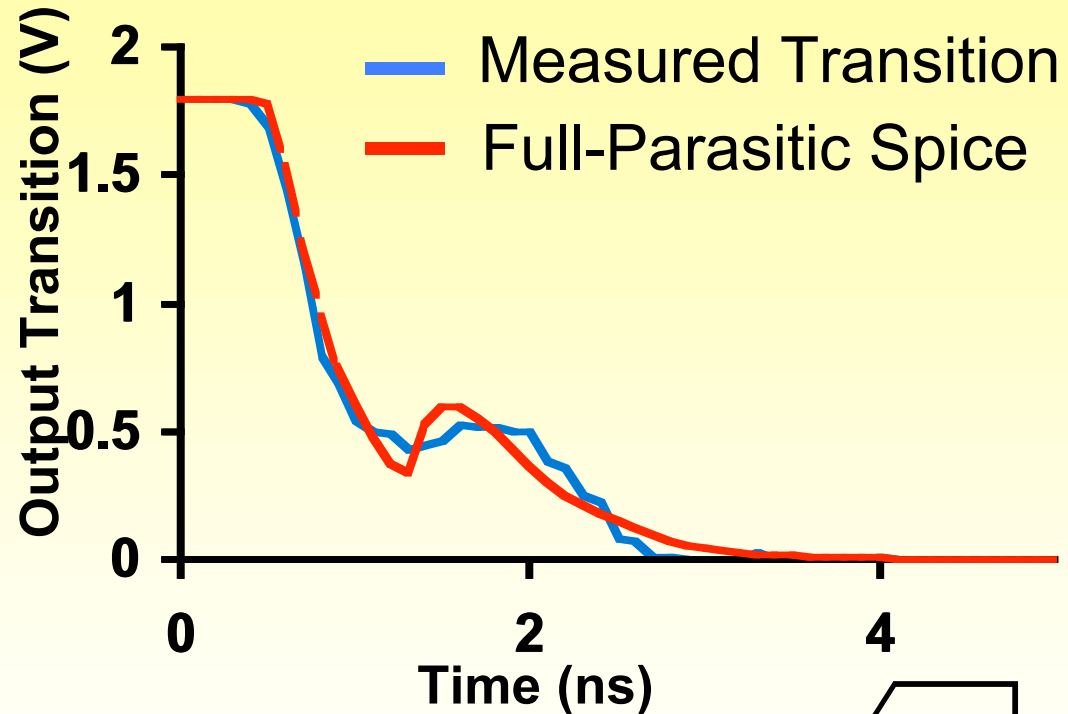
- Complete in situ digitization
- 6-bit resolution
- 10 GHz sample rate
- Other signal-integrity tests demonstrated




Substrate Noise

 

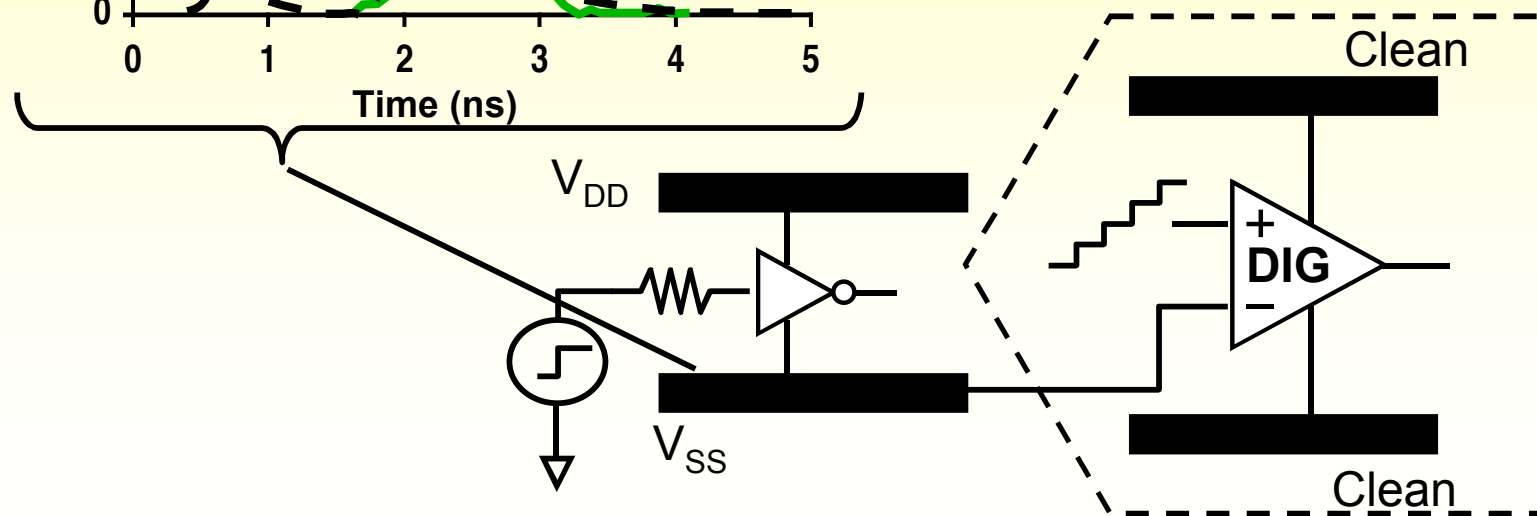
- Example of bounce on high resistance ground path
- Need to investigate improved sampling techniques




Power Supply Noise

 

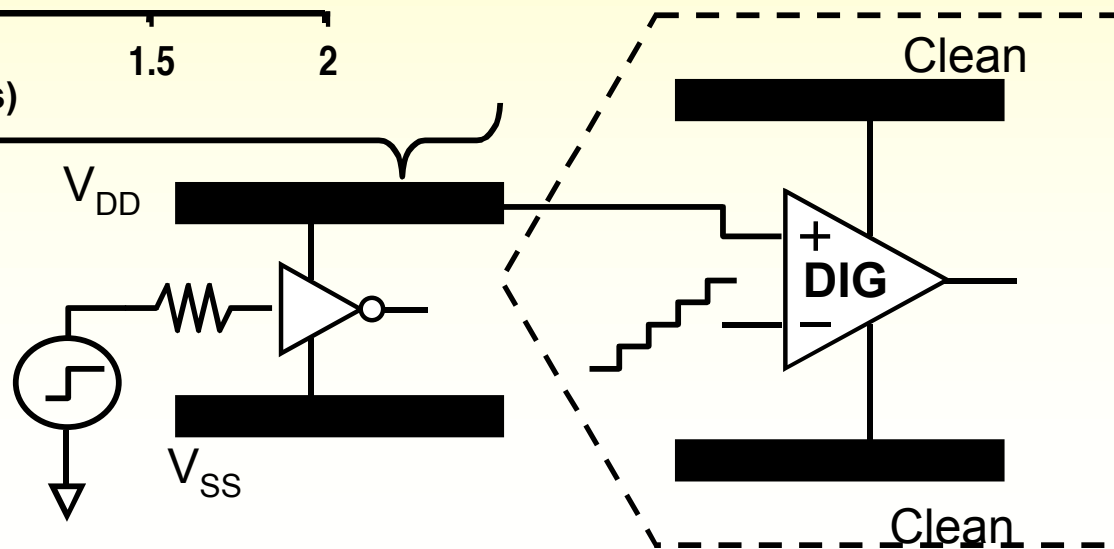- Other integrity issues successfully demonstrated
- Translation into frequency domain possible because of digitization




High-Frequency Tuned Amplifier

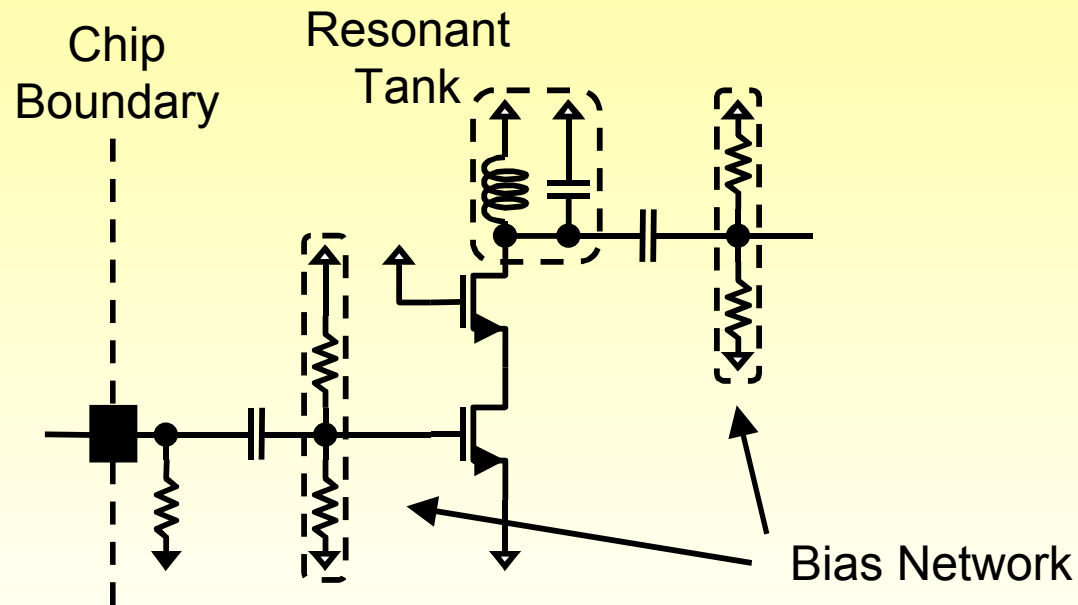


- Simple circuit for illustration purposes. Similar to a LNA, although not optimized for noise considerations
- **Output Signal not expected to be driven off-chip in “mission” environment**
- Conventional measurement requires buffer insertion

Buffer Insertion for Probe Test

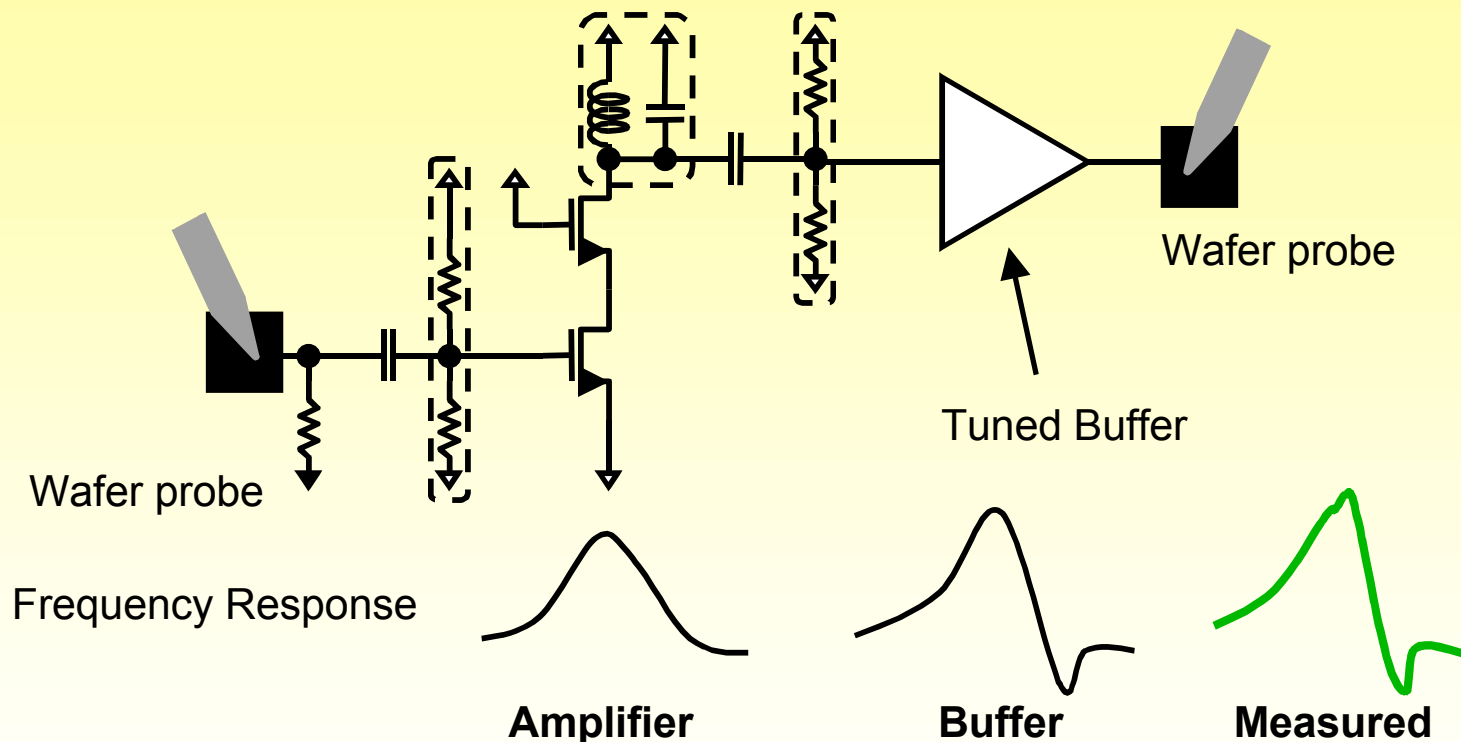

- Even wafer probing presents too large a load
- Inserted buffer is typically also tuned in frequency (depending on termination)
- Measured spectrum influenced by buffer characteristics


Proposed Test Vehicle

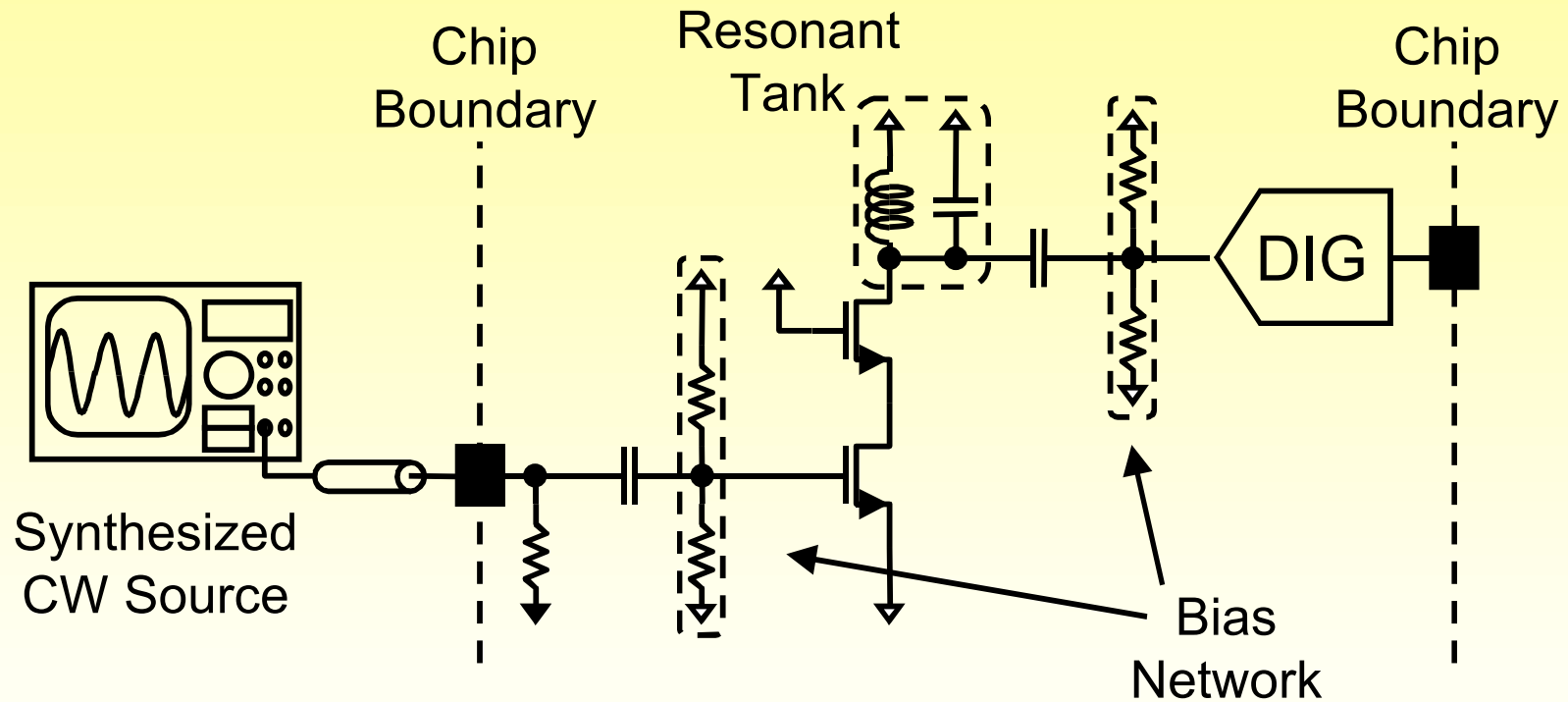


- Amplifier output directly sampled on-chip
- Flat response of DIG ensures proper extraction of spectral characteristics
- Offset/gain errors, and noise need to be investigated

Experimental Results

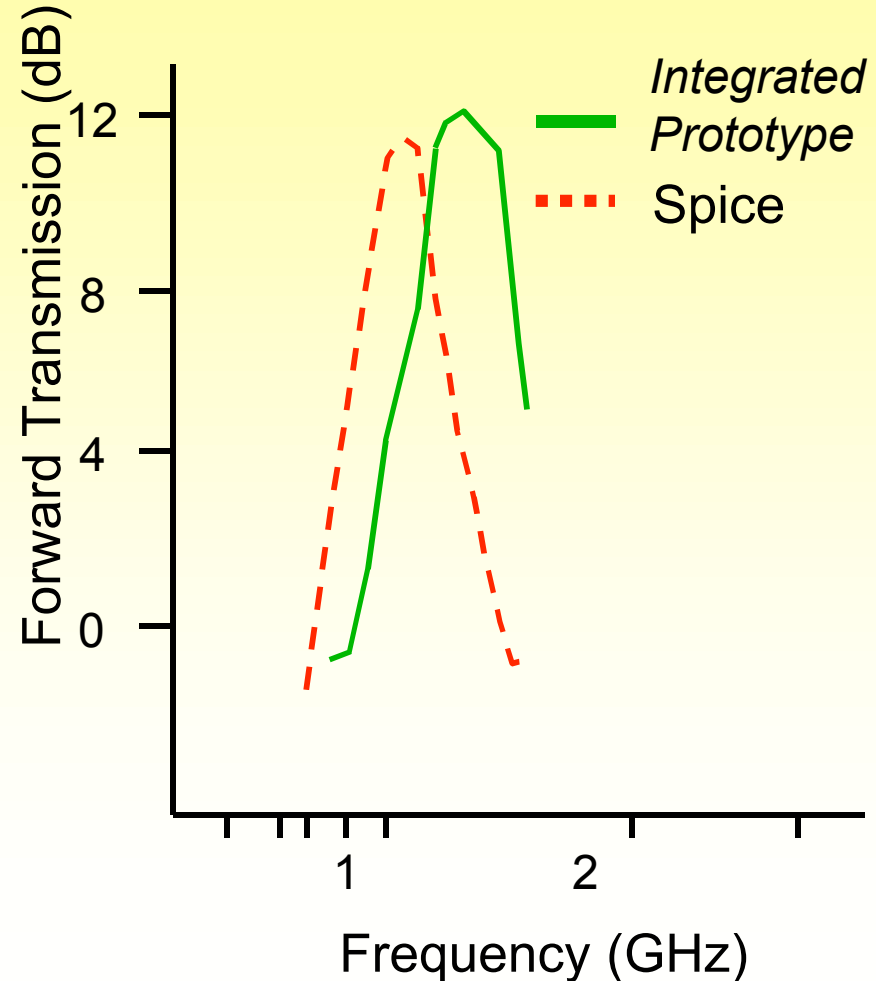
- *Embedded test* technology used to implement same DSP-based solution
- LNA resonance frequency slightly offset from simulation
- Investigate correlation with simulation




Outline

- Introduction
- On-Chip Instruments
 - Signal Generators
 - Sampling Oscilloscopes
 - Coherent Sampling Test System
 - Time Domain Reflectometry & Transmission
-  Timing Analyzers
- Conclusions


Measuring Jitter

 


Edge Density (Jitter CDF)

 


Edge Histogram (Jitter PDF)

 


RMS-Jitter Measurement

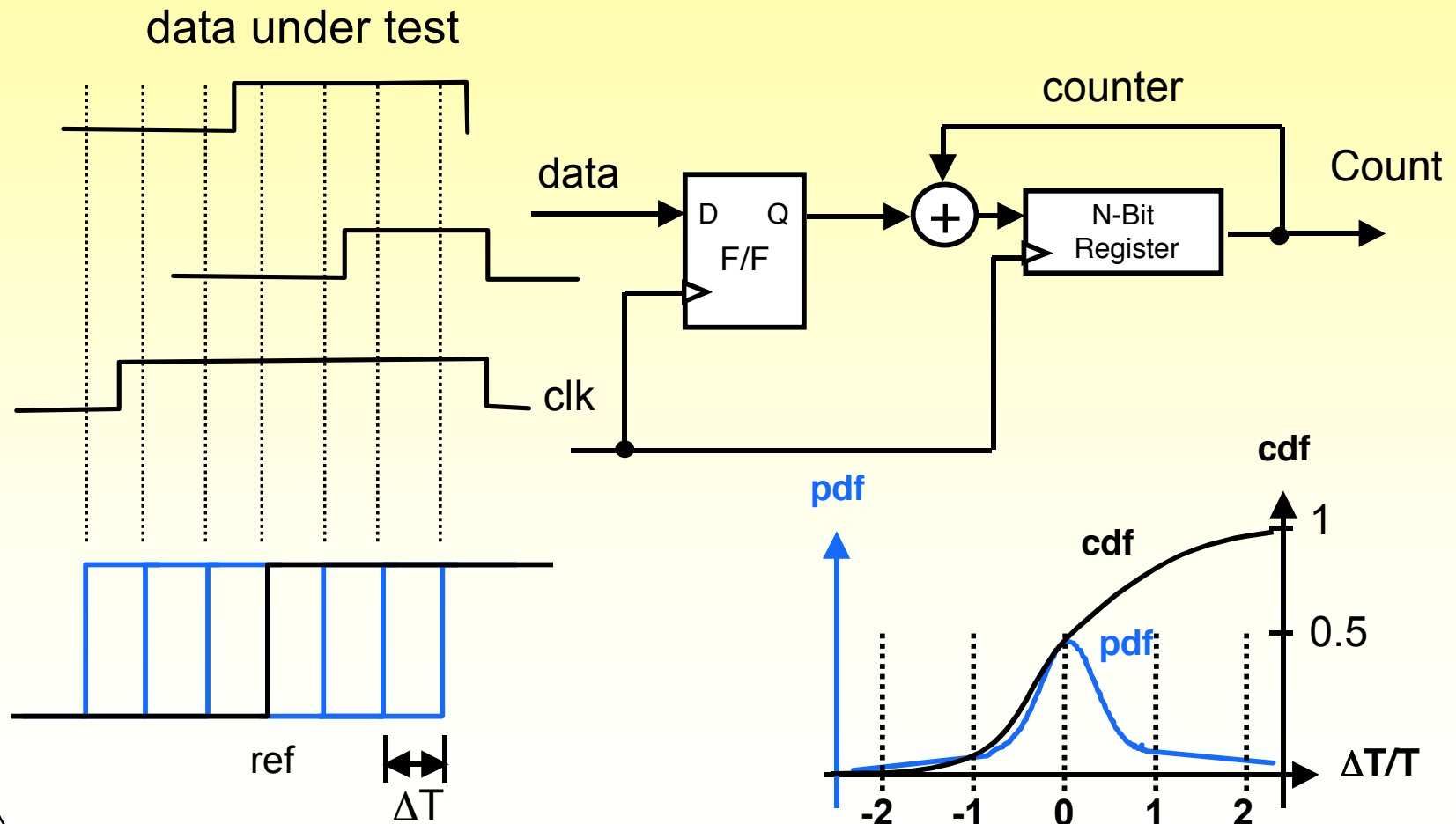

RMS-Jitter Measurement

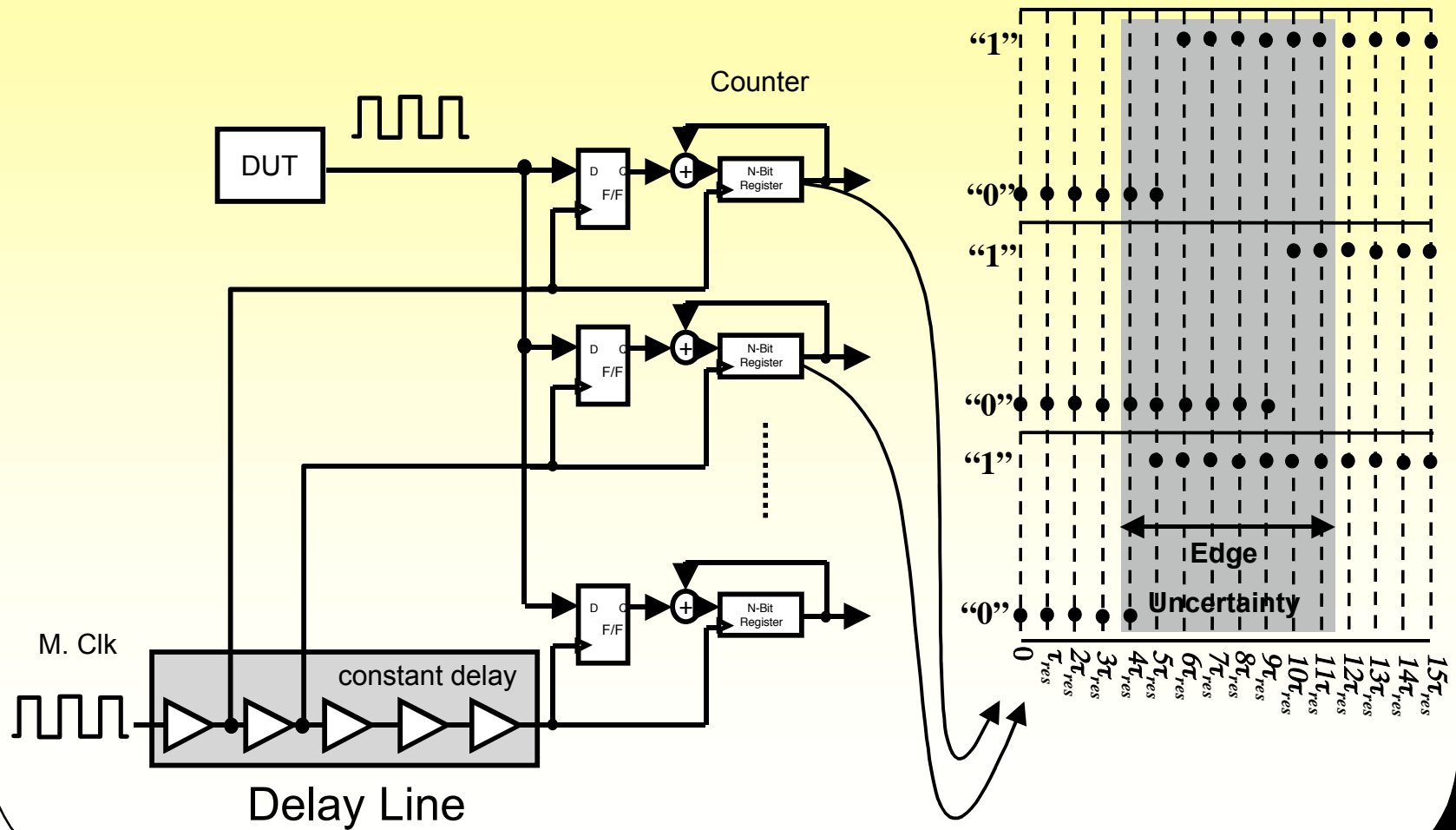

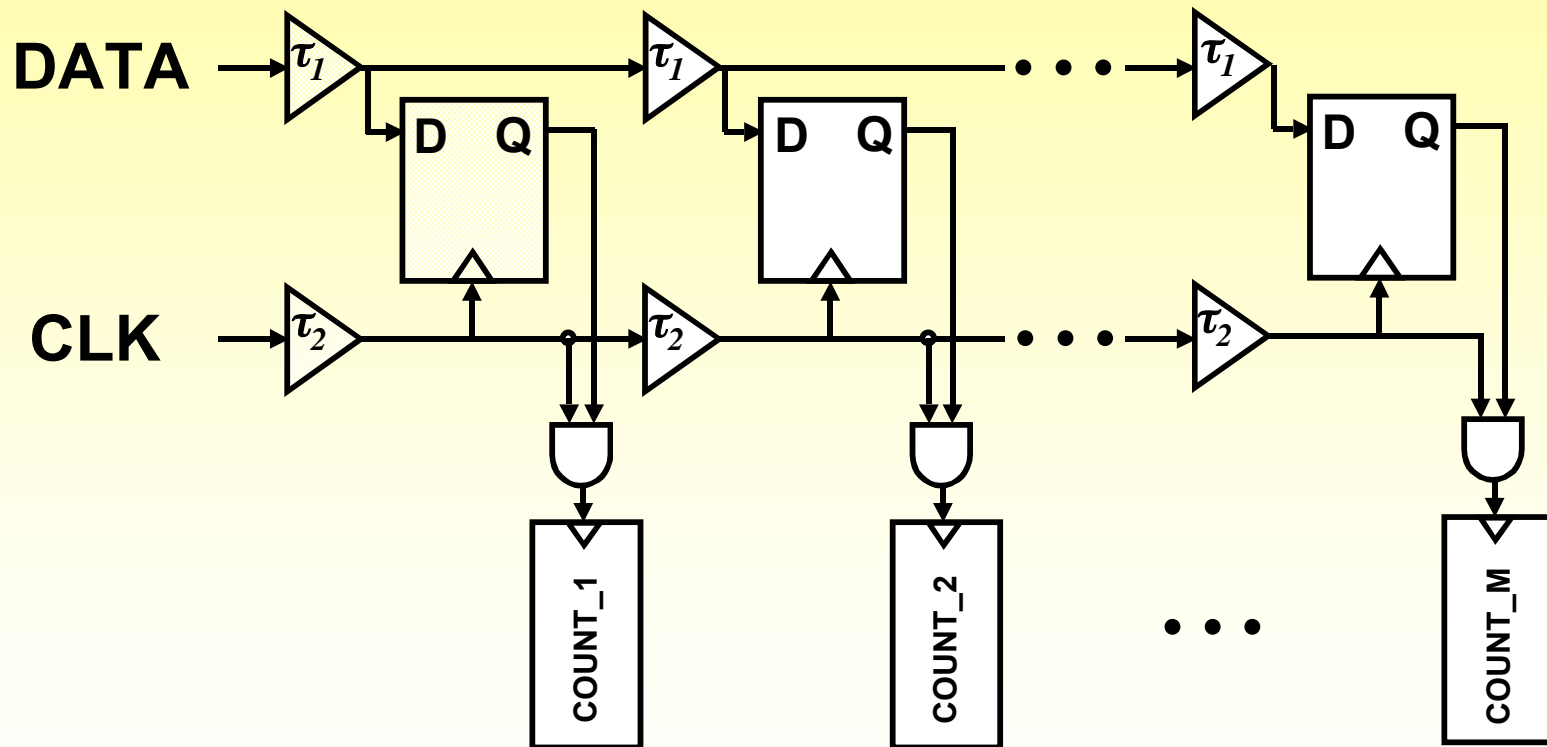Jitter Measurement Device Using A Venier Delay Line




- Sub-gate delays can be realized using a VDL structure:
$$\tau_2 > \tau_1, \tau_{res} = \tau_2 - \tau_1$$

Chip Micrograph

N. Abaskharoun & G. Roberts CICC'2001


 
- 101 Stage VDL in a 0.35 μ m CMOS
- VDL: 2.4 mm²
- Counters: 3.1 mm²
- BIG Circuit!!



Jitter Measurement



Guassian and Sinusoidal Distributions

Pk-Pk = 310 ps
RMS = 30.41 ps

  

Pk-Pk = 324 ps
RMS = 27.61 ps

Pk-Pk = 644 ps
RMS = 230.4 ps

 
 


Pk-Pk = 666 ps
RMS = 220.2 ps

$\tau_{res} = 18$ ps


Vernier Delay Line (VDL)

Overcome Drawbacks

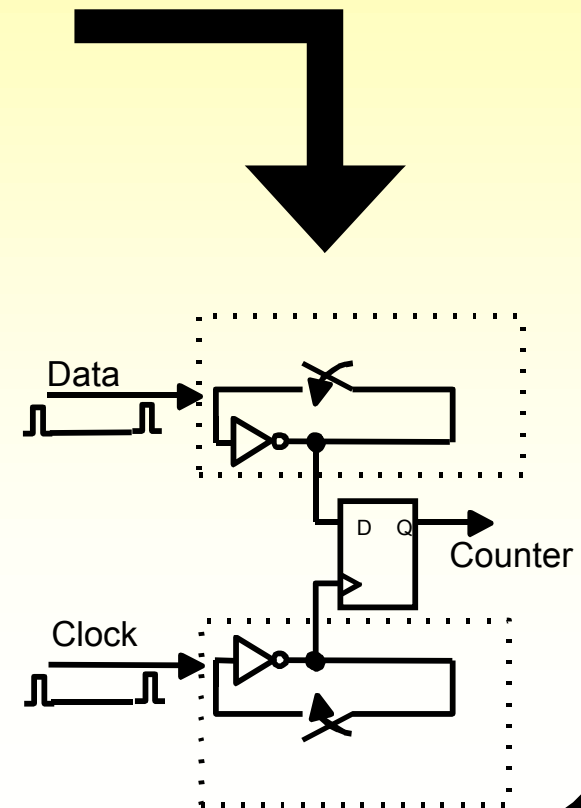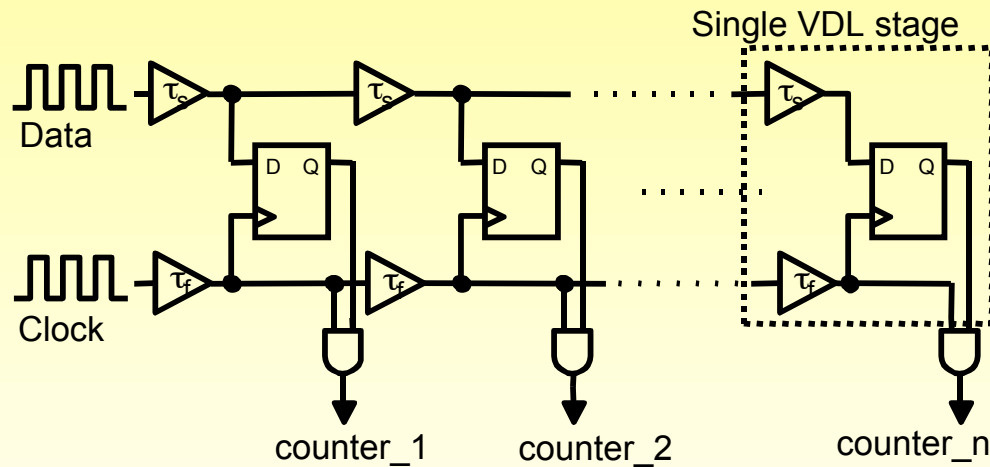

Component-Invariant VDL

Complete Circuit

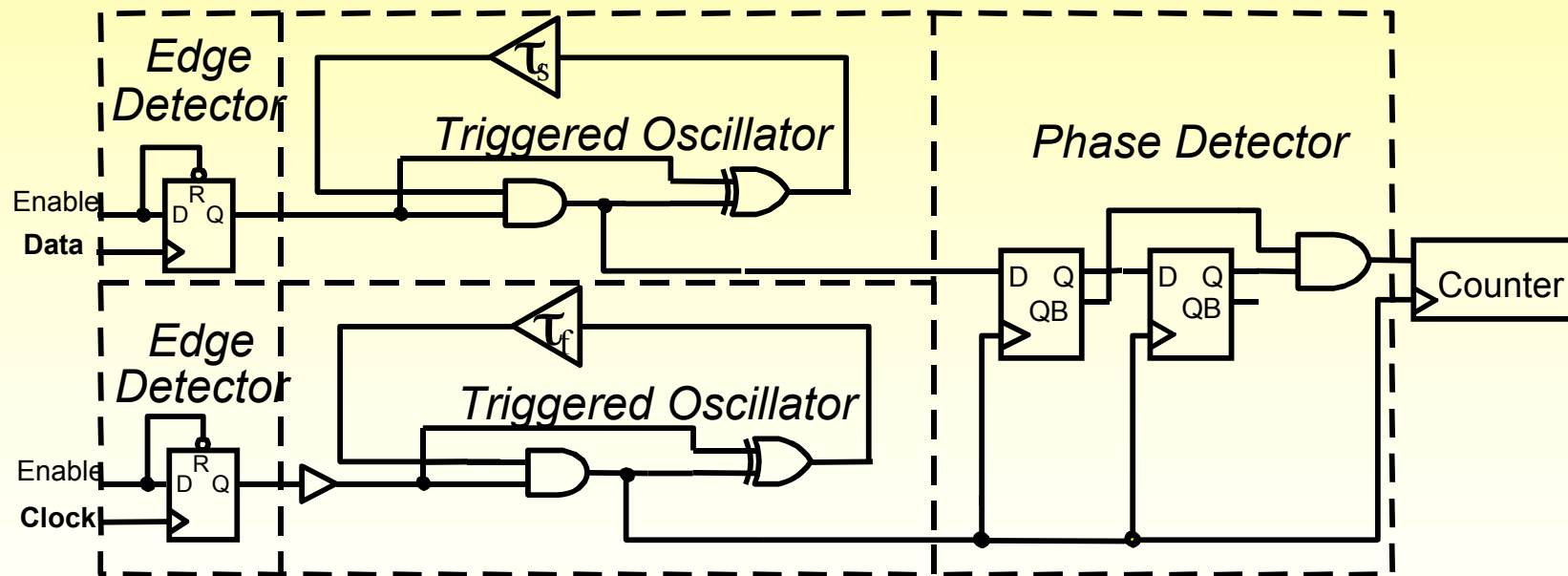


US & Canada Patent Pending

55 ps (19 ps) Timing Analyzer

A. Chan & G. W. Roberts, CICC'2002


 
- 0.18 μm TSMC CMOS process
- 0.12 mm^2 per component-invariant VDL
- Expected resolution: ~ 10 ps
- Measured resolution: 19 ps
- Highest clock input frequency: 5 GHz
- Test time: ~ 150 ns/sample (6.66 MHz sampling rate)



Experimental Results

IC Implementation – Pseudo Gaussian Distribution

VDL Timing resolution = 19 ps

 
 


	VDL	Wavecrest
RMS Jitter	21.1 ps	18.68 ps
Peak to peak Jitter	158.2 ps	124.5 ps

Experimental Results

IC Implementation – Pseudo Sinusoidal Distribution


VDL Timing resolution = 19 ps

  

	VDL	Wavecrest
RMS Jitter	32.5 ps	41.94 ps
Peak to peak Jitter	234.5 ps	197.8 ps

Experimental Results

 Mean Value of VDL Jitter Distribution Vs. Wavecrest



Conclusions

- Present and future SOC will require some form of Design-For-Test (DFT) to aid the test process.
 - Embedded cores can be accessed externally with an analog test bus and ATE
 - On-chip digitizer is essential for high-speed and low noise measurements.
 - Signal generator + digitizer provides full tester capability on chip.
- Numerous test instruments have been fabricated directly on-chip and can serve as a foundation for the engineering laboratory of the future.