



Troubleshooting and Lessons Learned Using Protective Relay Event Analysis

GE Digital Energy Multilin

Seminar Presenter

Terrence Smith
Terrence.Smith@GE.com
423-304-0843

Seminar Agenda

- Overhead distribution ground fault inside industrial facility causes a generator stator fault
- Incorrect current transformer wiring causes bus fault during power transformer energization
- Fault on distribution system causes unusual transformer high side currents
- Incorrect current transformer wiring causes motor thermal overload trip
- Generator loss of excitation and reverse power trips
- Overcurrent trip on paralleling switchgear
- Synchronous motor trip on power factor
- Substation heat pumps drops bus voltage by 1kV causes capacitor bank trip

Review Of Symmetrical Components




imagination at work

Symmetrical and Non-Symmetrical Systems:


Symmetrical System:

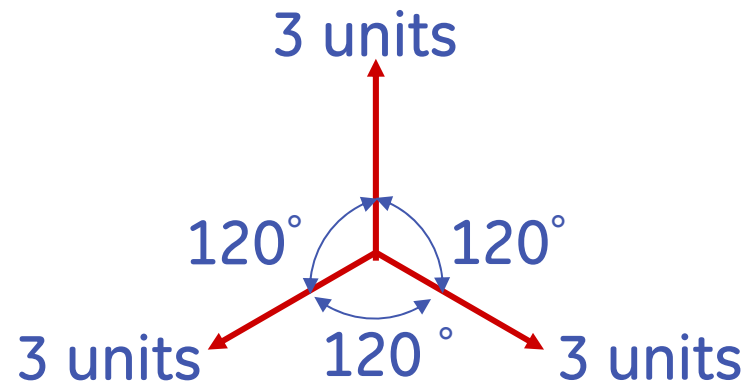- Counter-clockwise rotation
- All current vectors have equal amplitude
- All voltage phase vectors have equal amplitude
- All current and voltage vectors have 120 degrees phase shifts **and a sum of 0v**.




Non-Symmetrical System:

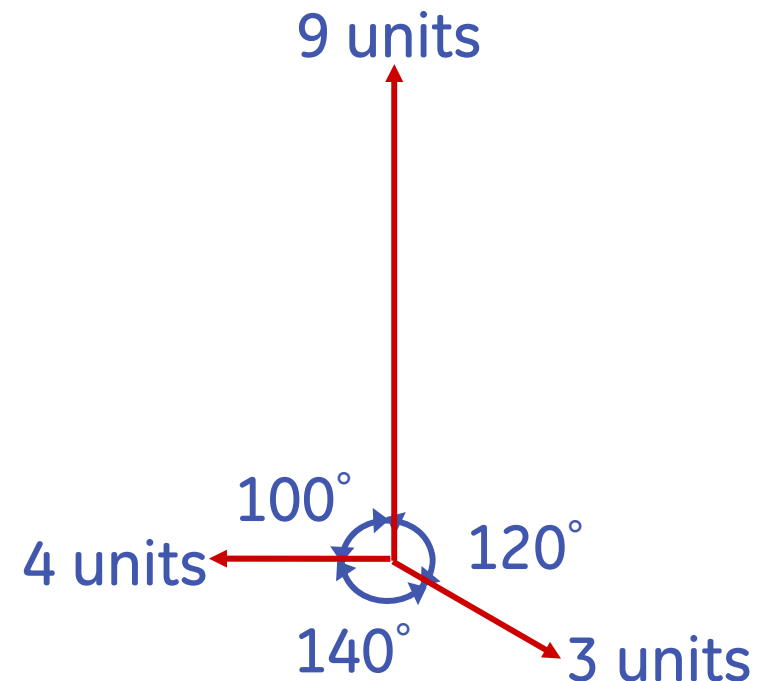- Fault or Unbalanced condition
- If one or more of the symmetrical system conditions is not met




Symmetrical Components:

Positive Sequence (Always Present)

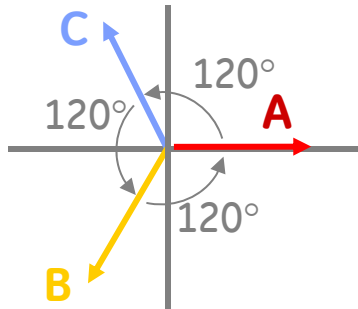


- **A-B-C Counter-clockwise** phase rotation
- All phasors with equal magnitude
- All phasors displaced 120 degrees apart

Zero Sequence

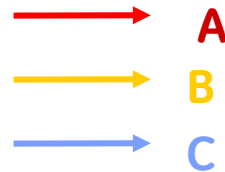

- No Rotation Sequence
- All phasors with equal magnitude
- All phasors are in phase

Negative Sequence

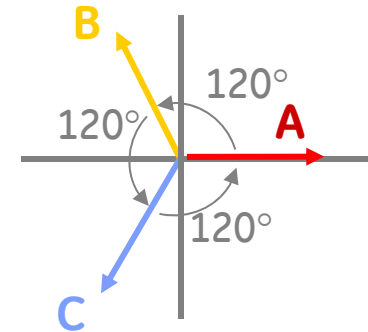

- **A-C-B counter-clockwise** phase rotation
- All phasors with equal magnitude
- All phasors displaced 120 degrees apart

Symmetrical Components:

Positive

Sequence
Component:

$$I_1 = \frac{1}{3} (I_a + \alpha I_b + \alpha^2 I_c) \quad V_1 = \frac{1}{3} (V_a + \alpha V_b + \alpha^2 V_c)$$



Negative

Sequence
Component:

$$I_2 = \frac{1}{3} (I_a + \alpha^2 I_b + \alpha I_c) \quad V_2 = \frac{1}{3} (V_a + \alpha^2 V_b + \alpha V_c)$$

Zero Sequence
Component:
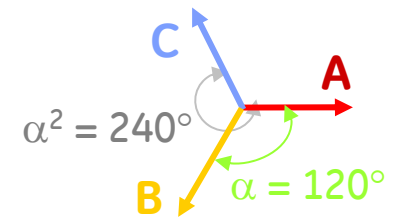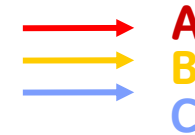
$$I_0 = \frac{1}{3} (I_a + I_b + I_c) \quad V_0 = \frac{1}{3} (V_a + V_b + V_c)$$



Unbalanced Line-to-Neutral Phasors:

$$I_a = I_1 + I_2 + I_0$$

$$V_a = V_1 + V_2 + V_0$$

$$I_b = \alpha^2 I_1 + \alpha I_2 + I_0$$

$$V_b = \alpha^2 V_1 + \alpha V_2 + V_0$$



$$I_c = \alpha I_1 + \alpha^2 I_2 + I_0$$

$$V_c = \alpha V_1 + \alpha^2 V_2 + V_0$$

α = Phasor @ +120°

α^2 = Phasor @ 240°

Calculating Symmetrical Components:

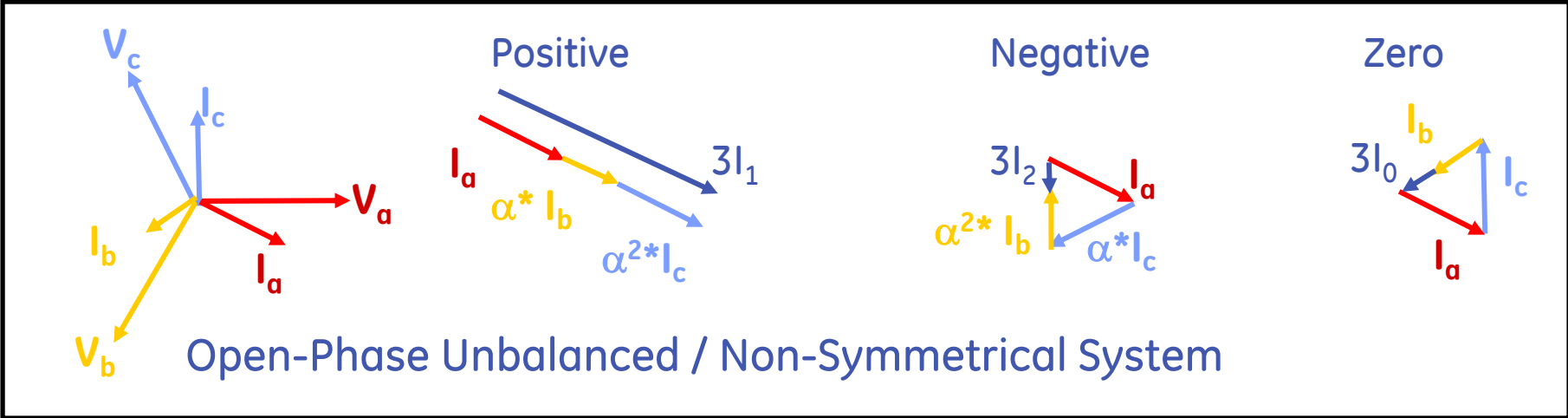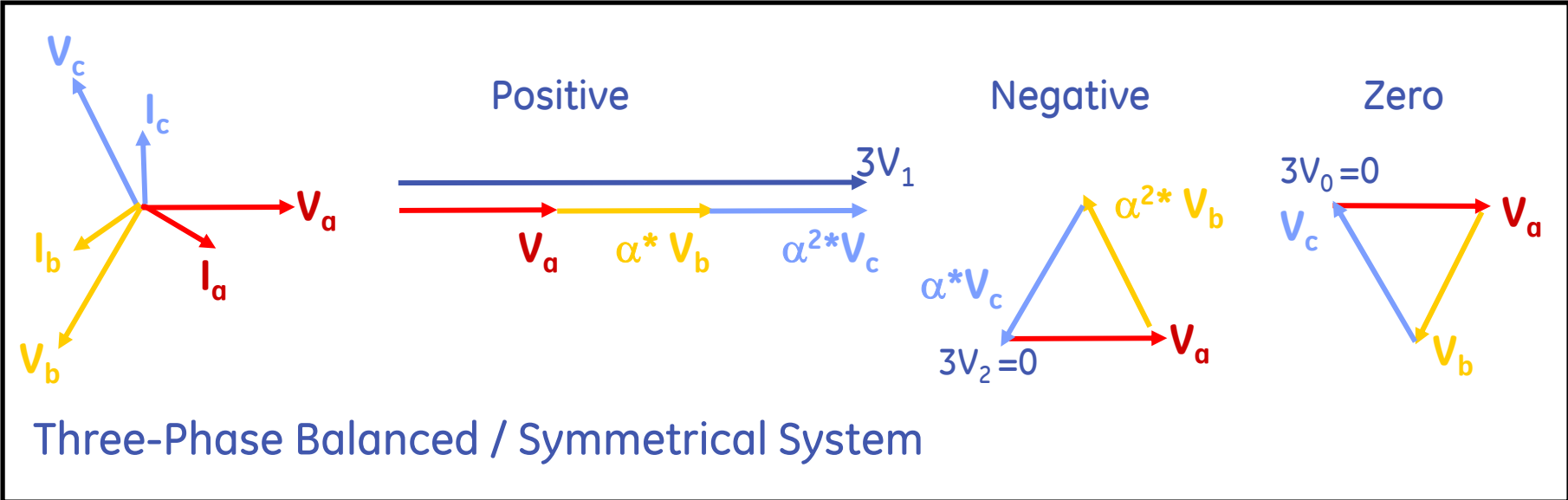

Symmetrical Components

Example: Perfectly Balanced & ABC Rotation

$$I_0 = 1/3(I_a + I_b + I_c)$$

$$V_0 = 1/3(V_a + V_b + V_c)$$

$$I_1 = 1/3(I_a + aI_b + a^2I_c)$$



$$V_1 = 1/3(V_a + aV_b + a^2V_c)$$

$$I_2 = 1/3(I_a + a^2I_b + aI_c)$$

$$V_2 = 1/3(V_a + a^2V_b + aV_c)$$

$$a = 1 \angle 120^\circ$$

$$a^2 = 1 \angle 240^\circ$$

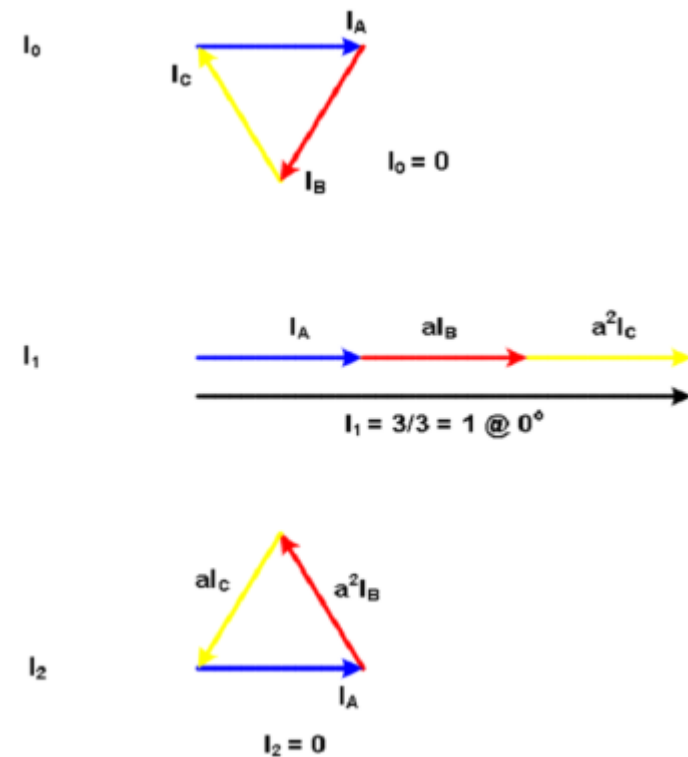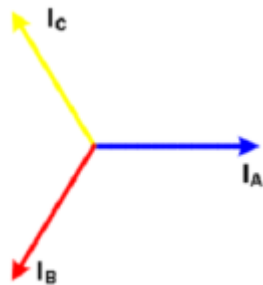

Symmetrical Components

Example: B-Phase Rolled & ABC Rotation

$$I_0 = 1/3(I_a + I_b + I_c)$$

$$V_0 = 1/3(V_a + V_b + V_c)$$

$$I_1 = 1/3(I_a + aI_b + a^2I_c)$$





$$V_1 = 1/3(V_a + aV_b + a^2V_c)$$

$$I_2 = 1/3(I_a + a^2I_b + aI_c)$$

$$V_2 = 1/3(V_a + a^2V_b + aV_c)$$

$$a = 1 \angle 120^\circ$$

$$a^2 = 1 \angle 240^\circ$$

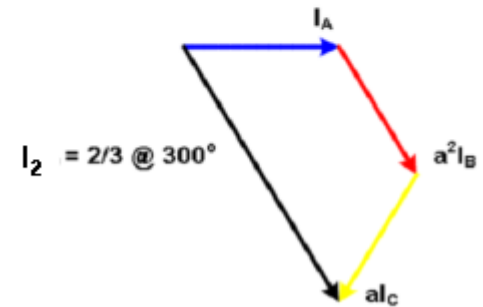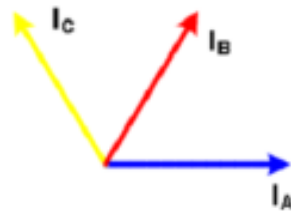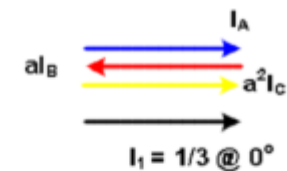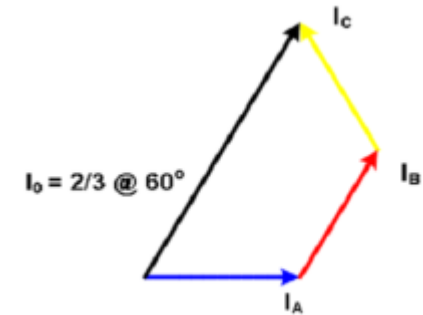

Symmetrical Components

Example: B-Phase & C-Phase Rolled & ABC Rotation

$$I_0 = 1/3(I_a + I_b + I_c)$$

$$V_0 = 1/3(V_a + V_b + V_c)$$

$$I_1 = 1/3(I_a + aI_b + a^2I_c)$$





$$V_1 = 1/3(V_a + aV_b + a^2V_c)$$

$$I_2 = 1/3(I_a + a^2I_b + aI_c)$$

$$V_2 = 1/3(V_a + a^2V_b + aV_c)$$

$$a = 1 \angle 120^\circ$$



$$a^2 = 1 \angle 240^\circ$$

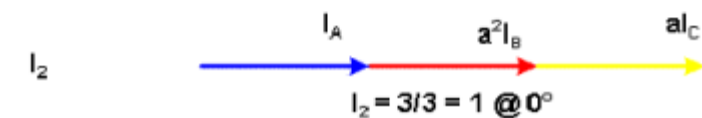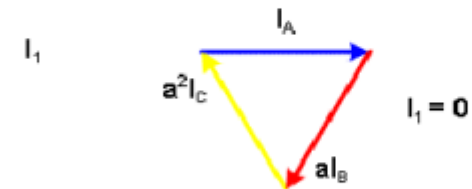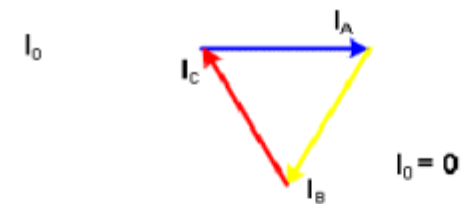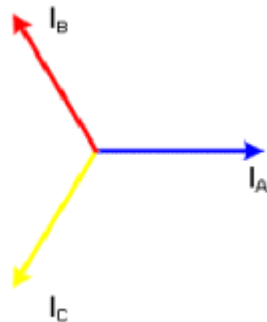

Result: 100% I2 (Negative Sequence Component)


Summary of Symmetrical Components:

- Under a no-fault condition, the power system is considered to be essentially symmetrical therefore, only positive sequence currents and voltages exist.
- At the time of a fault, positive, negative and possibly zero sequence currents and voltages exist.
 - All positive, negative and zero sequence currents can be calculated using real world phase voltages and currents along with Fortescue's formulas.
 - $I_n = I_a + I_b + I_c = 3 I_0$

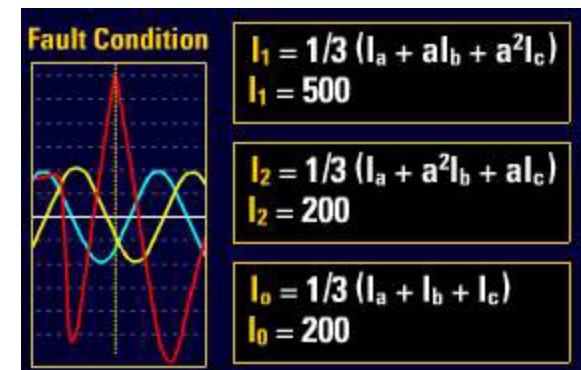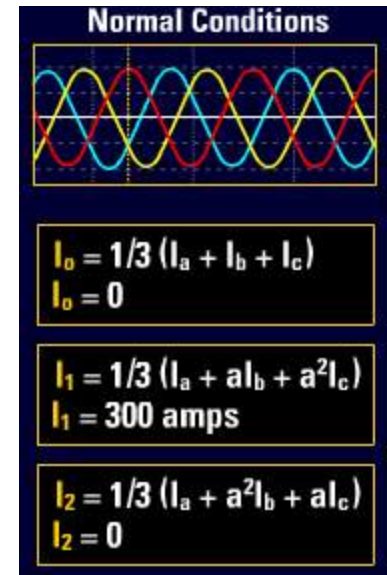

Power System Faults

Fault Analysis

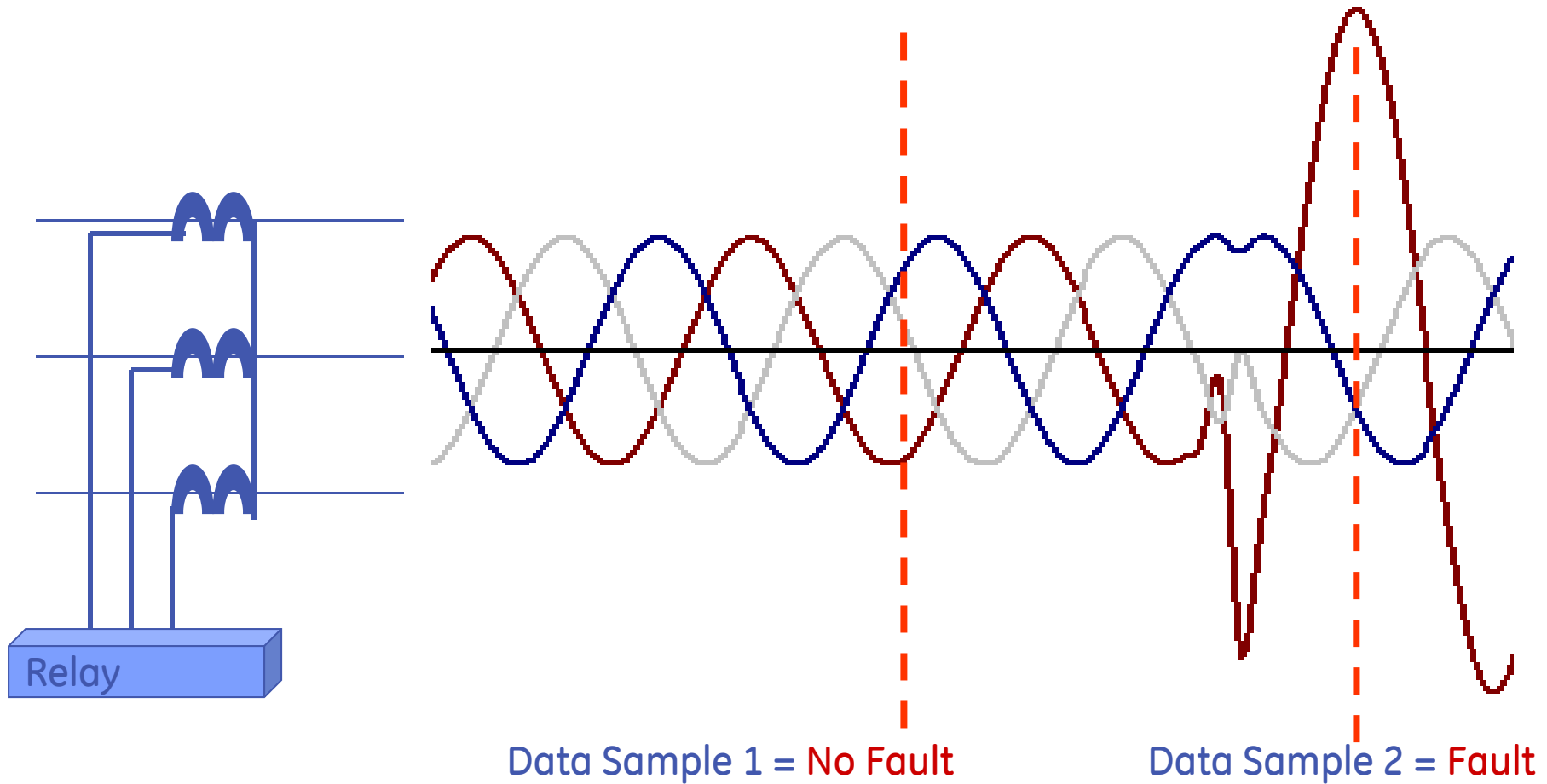


Power System Faults


Fault Analysis

For Normal Conditions:

Data Sample 1
Phasor Diagram:

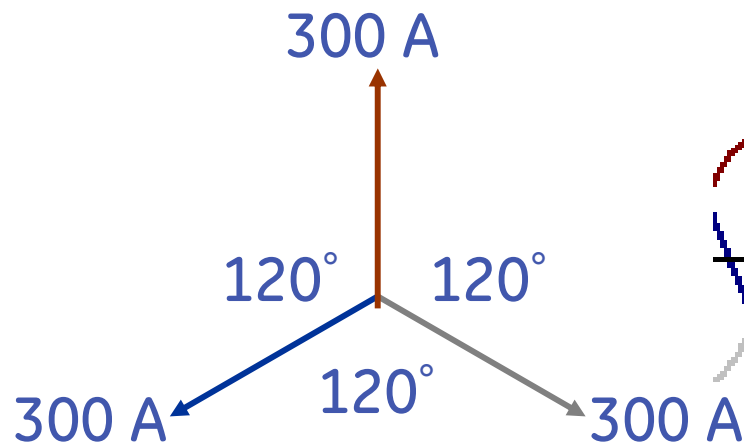

Waveform Capture:

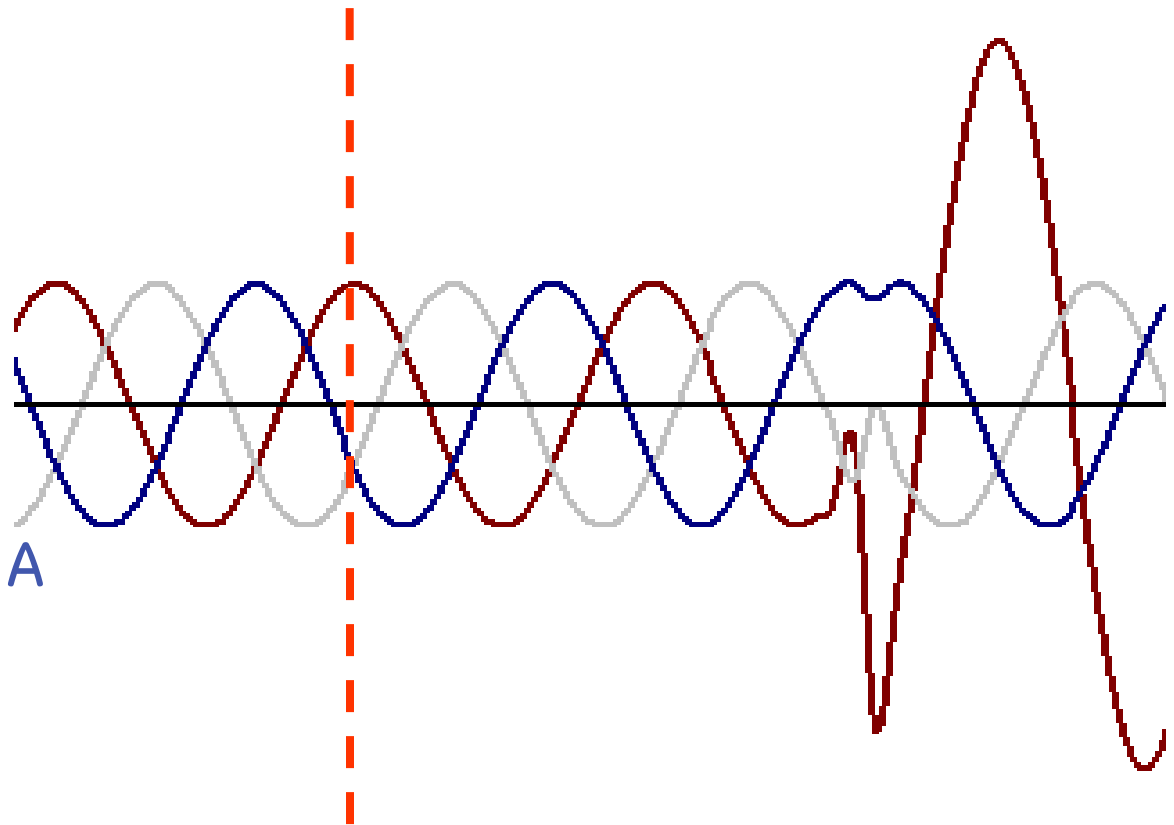

Data Sample 1 = No Fault

Power System Faults


Fault Analysis - Example

For Fault Condition:

Negative Sequence Component, I_2 :

$$I_2 = \frac{1}{3}(I_a + \alpha^2 I_b + \alpha I_c)$$
$$= \frac{1}{3}(600 \text{ A})$$

$$I_2 = 200 \text{ Amps}$$

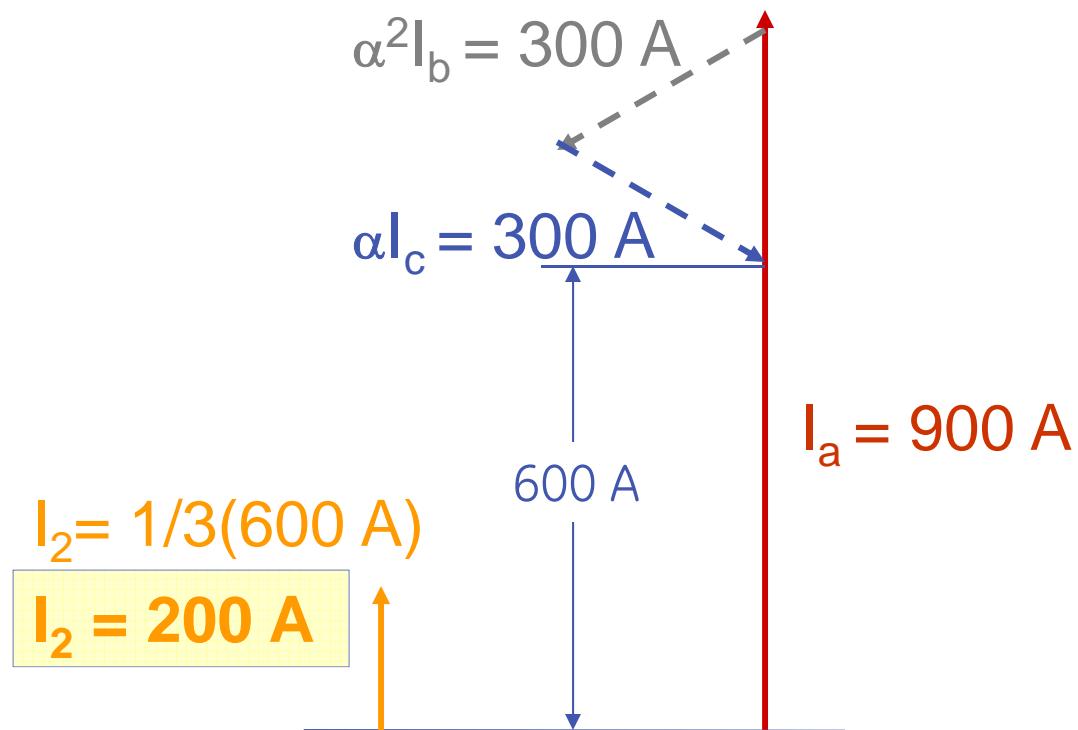


Power System Faults

Fault Analysis - Example

For Fault Condition:

Zero Sequence Component, I_0 :

$$I_0 = \frac{1}{3}(I_a + I_b + I_c)$$

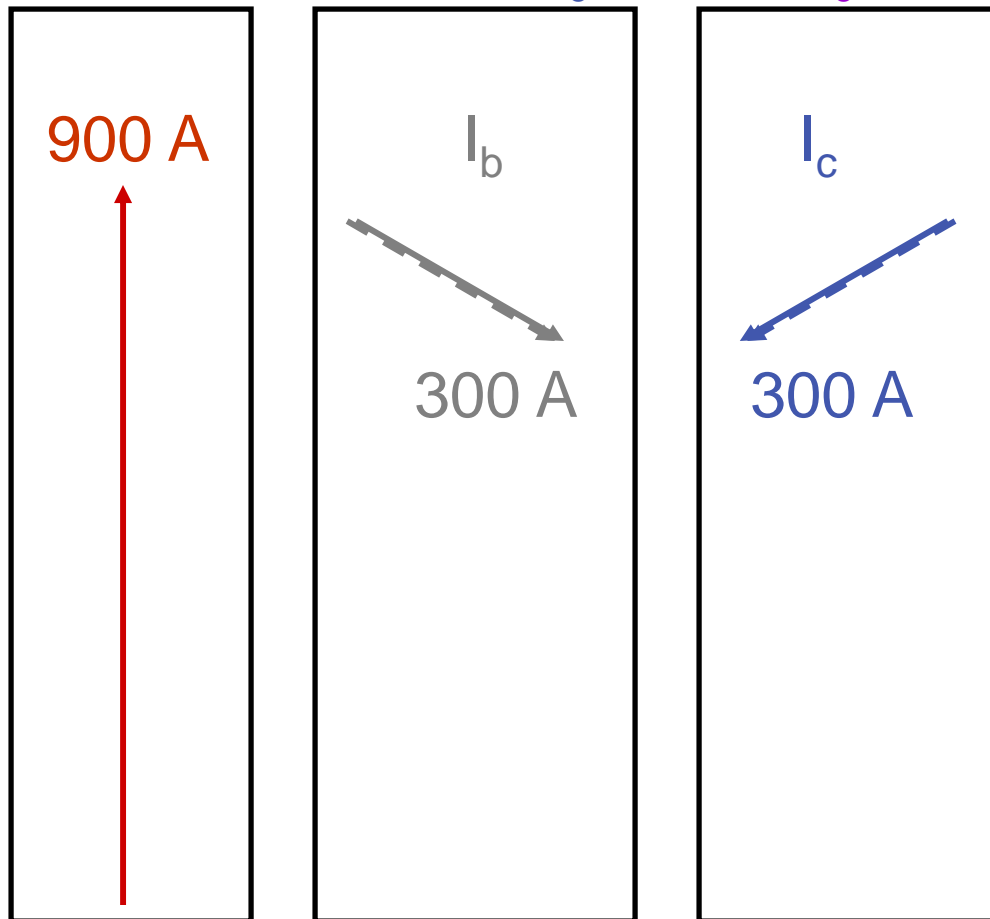

Power System Faults


Fault Analysis - Example

For Fault Condition:

Zero Sequence Component, I_0 :

$$I_0 = \frac{1}{3}(I_a + I_b + I_c)$$
$$= \frac{1}{3}(600 \text{ A})$$

$$I_0 = 200 \text{ Amps}$$

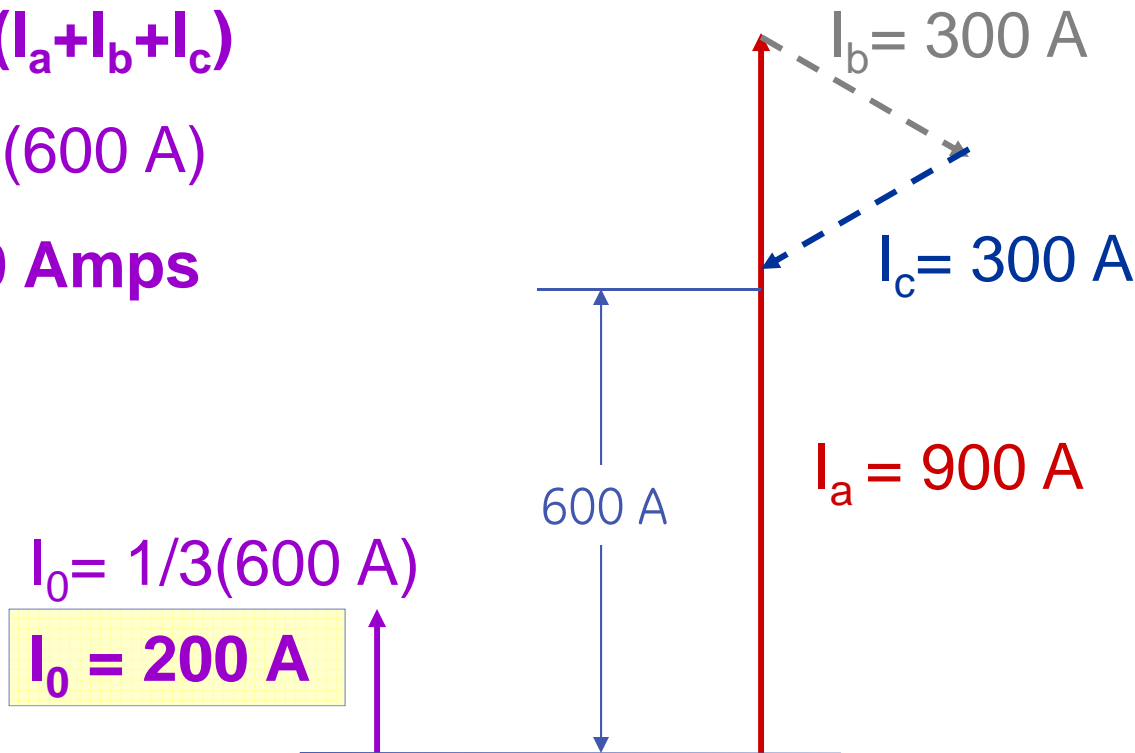

Power System Faults

Fault Analysis - Example

For Fault Condition:


Verifying Fault Current on Phase A:

$$I_a = I_1 + I_2 + I_0$$

$$= 500 \text{ A} + 200 \text{ A} + 200 \text{ A}$$

$$I_a = \mathbf{900 \text{ Amps}}$$

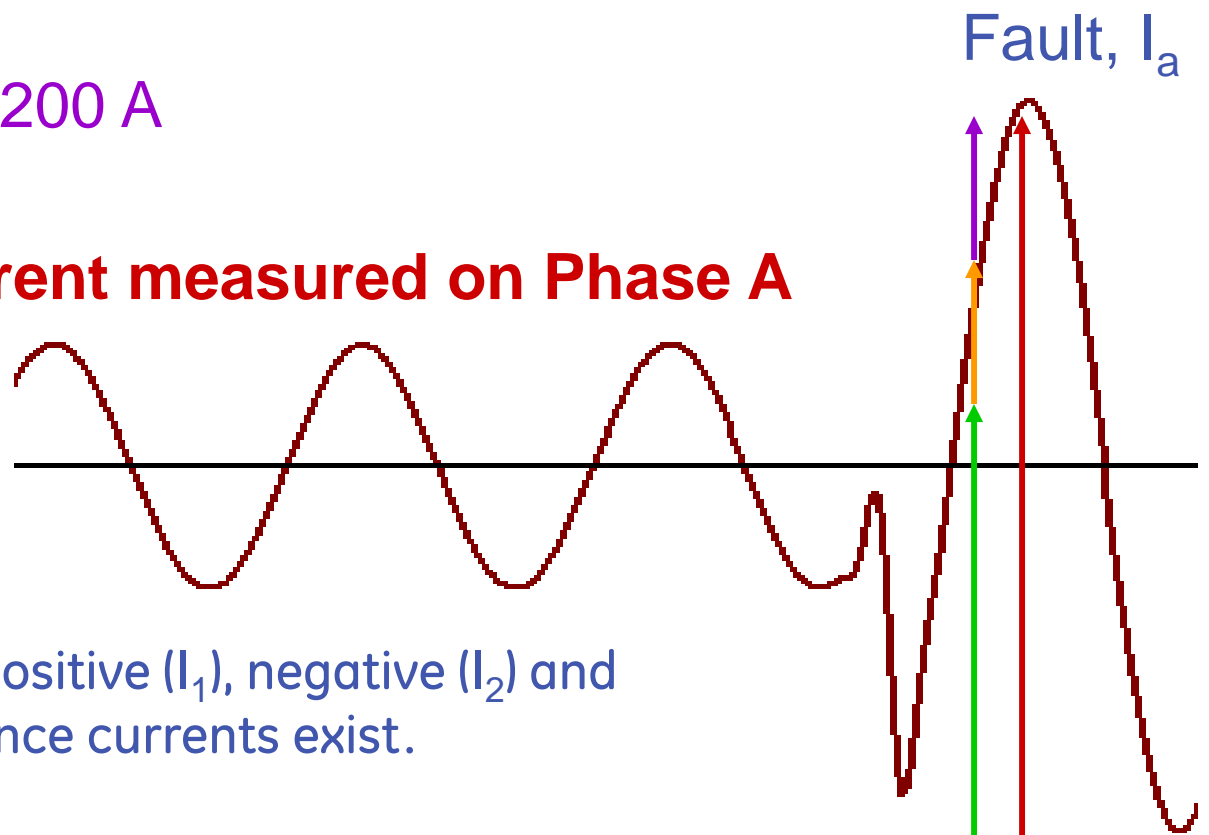
= actual fault current measured on Phase A



At the time of a fault, positive (I_1), negative (I_2) and possibly zero (I_0) sequence currents exist.


Sequence Networks

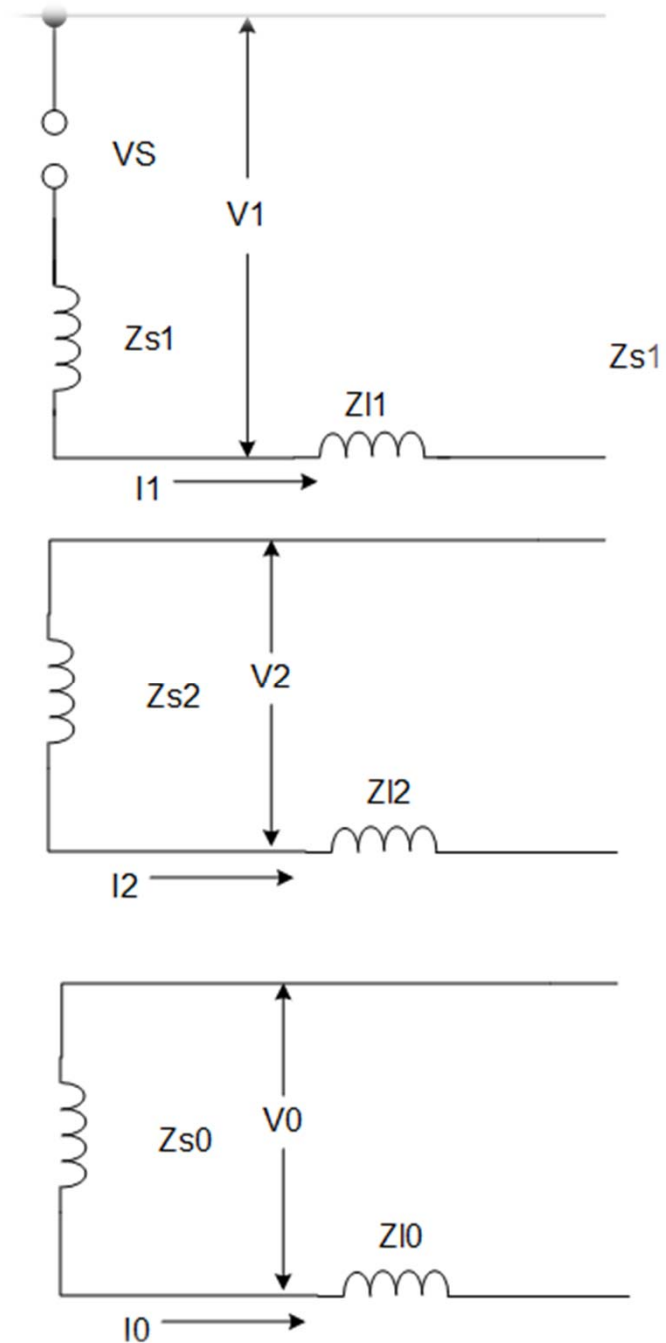- Where is sequence voltage highest?
- What generates negative and zero sequence currents?




How do we connect so that $I_1=I_2=I_0$?

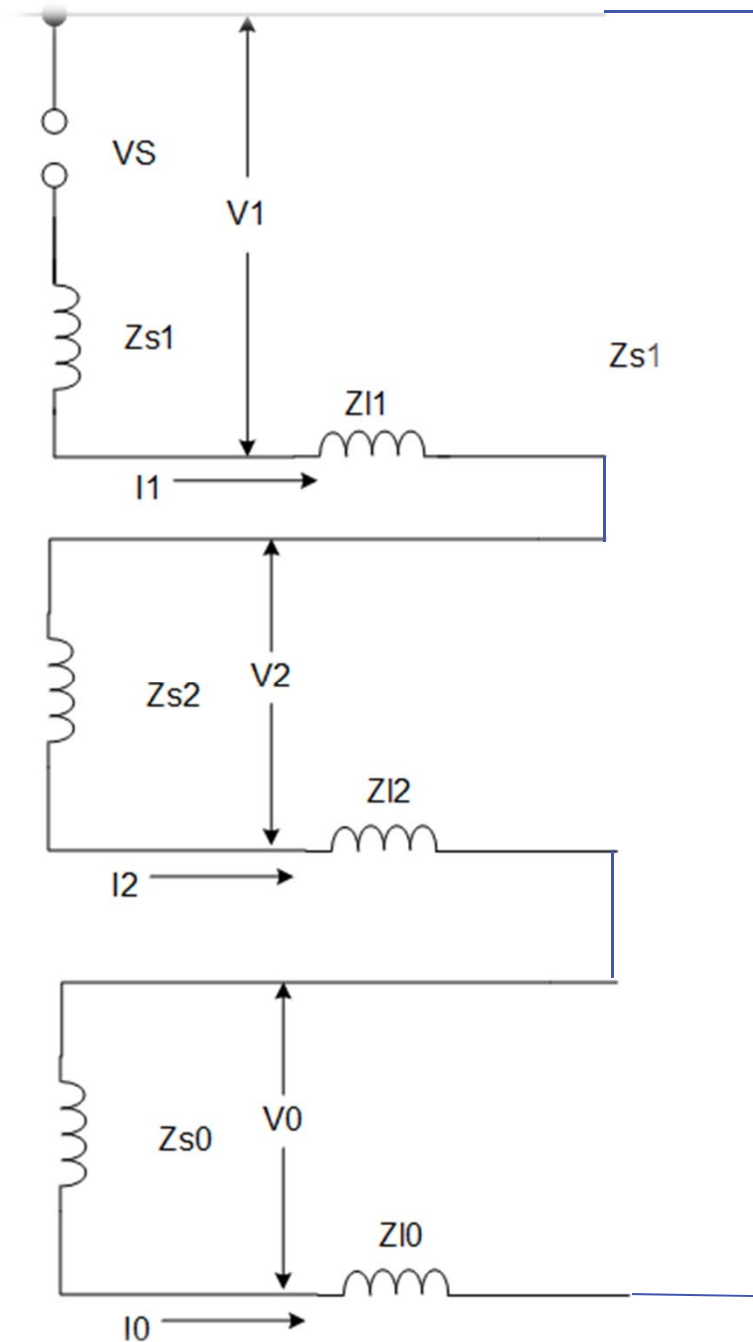- The sequence networks have to be in series for a phase to ground fault on a solidly grounded system.




Common Fault Types:

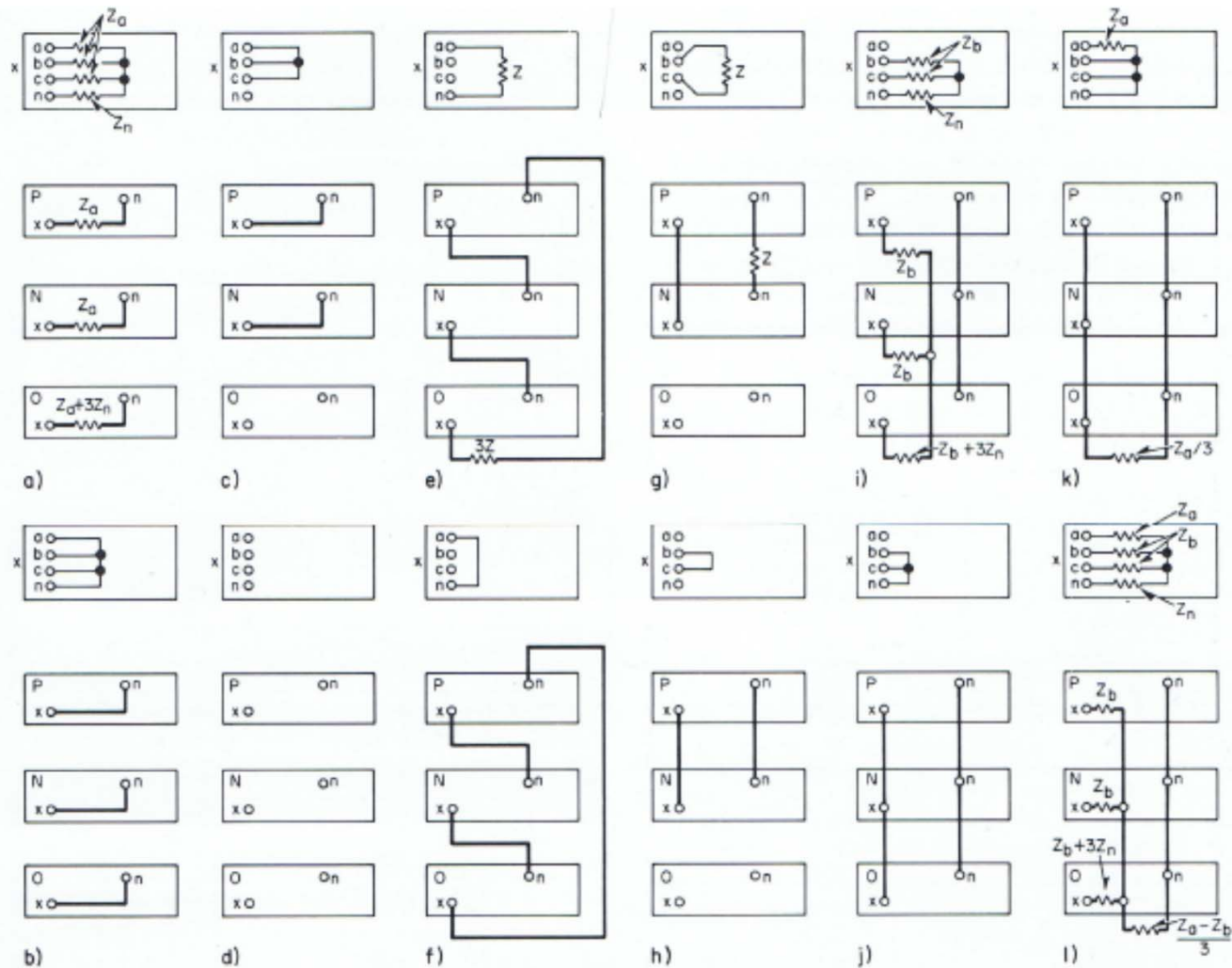

Note:

- a) Balanced load or three-line-to-ground fault with impedances.
- b) A three-line-to-ground fault.
- c) A three-phase fault.
- d) A shunt circuit open.
- e) A line-to-ground fault through an impedance.
- f) A line-to-ground fault.
- g) A line-to-line fault through impedance.
- h) A line-to-line fault.
- i) A two-line-to-ground fault with impedance.
- j) A two-line-to-ground fault.
- k) A three-line-to-ground fault with impedance in phase a.
- l) Unbalanced load or three-line-to-ground fault with impedance.

Transformer Interconnections:

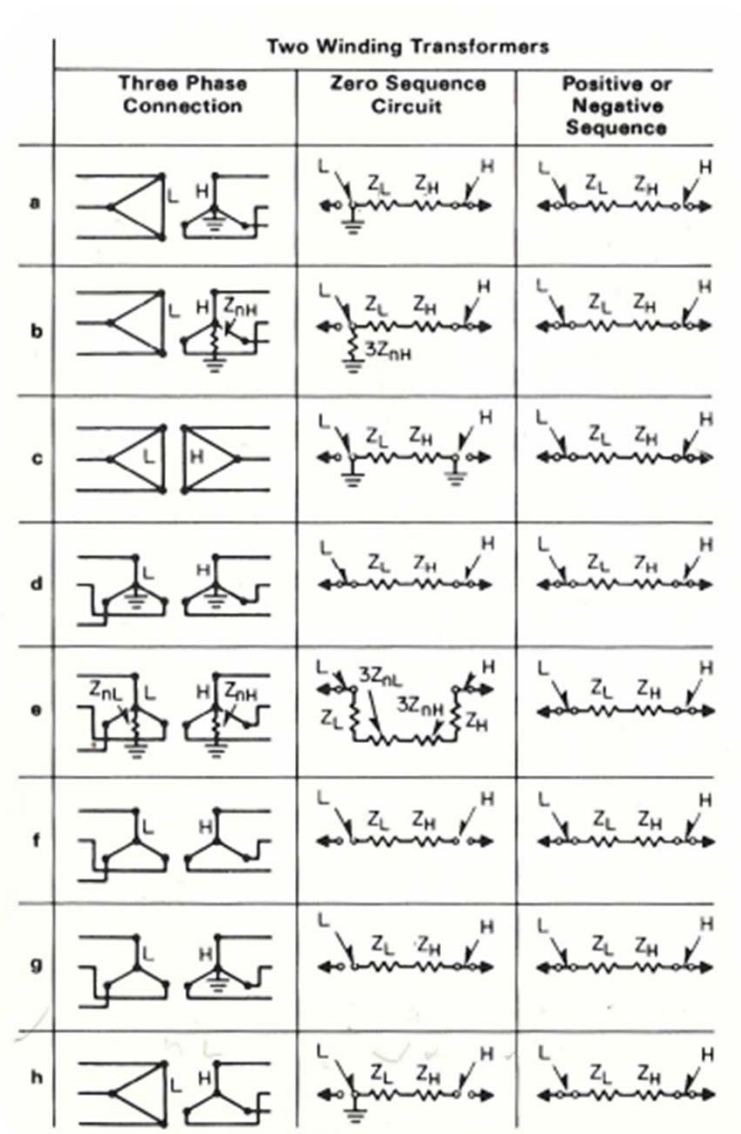


Analysis of Interesting Events Using Waveforms





imagination at work

Snake Causes a Distribution Fault

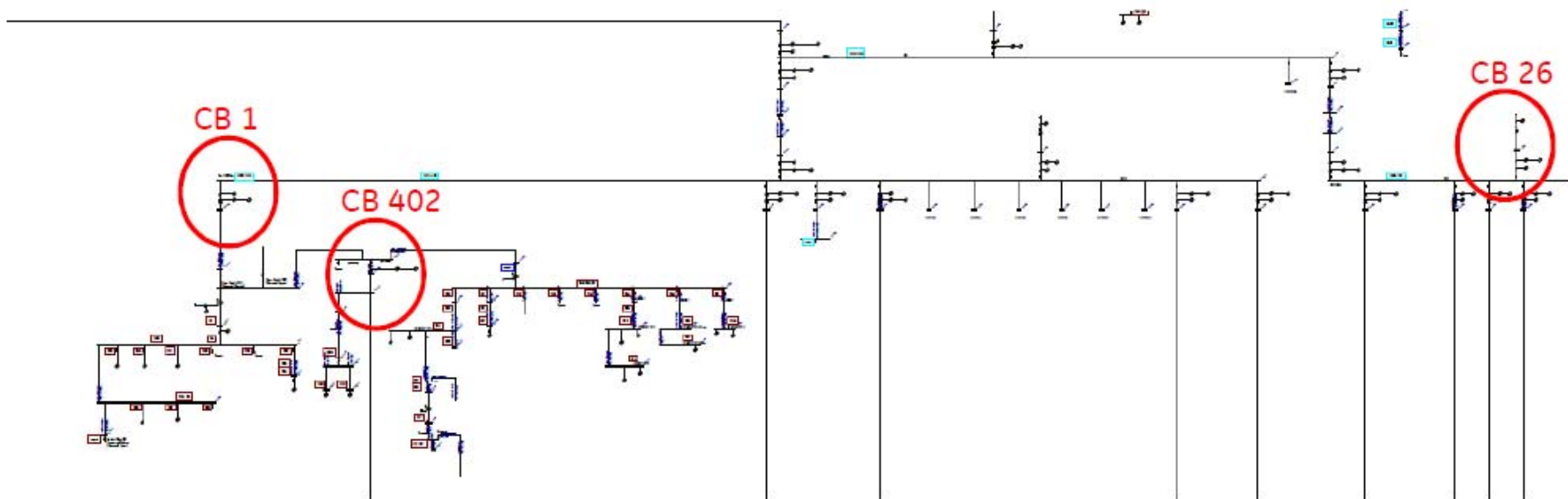

tion Fault

| Event | Date | Time | Cause of Event |
|-------|------------|--------------|--|
| 48 | 03/20/2014 | 22:20:49.968 | Dropout: Phase Instantaneous OC 1 |
| 47 | 03/20/2014 | 22:20:49.954 | Alarm: Phase B - Arcing Current |
| 46 | 03/20/2014 | 22:20:49.953 | Dropout: Neutral Time OC 1 |
| 45 | 03/20/2014 | 22:20:49.953 | Dropout: Ground Time OC |
| 44 | 03/20/2014 | 22:20:49.945 | Input(C) ON-Block Neutral Time OC 1 |
| 43 | 03/20/2014 | 22:20:49.945 | Input(C) ON-Block Ground Time OC |
| 42 | 03/20/2014 | 22:20:49.945 | Input(C) ON-User Input D / ABB 50D Blk |
| 41 | 03/20/2014 | 22:20:49.937 | Pickup: Negative Sequence Overvoltage |
| 40 | 03/20/2014 | 22:20:49.921 | Pickup: Phase B - Phase Time OC 2 |
| 39 | 03/20/2014 | 22:20:49.921 | Pickup: Negative Sequence Time OC |

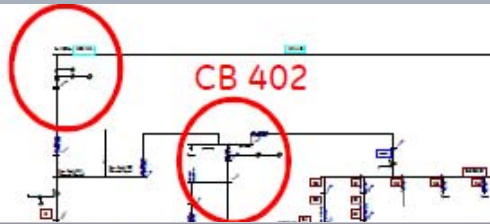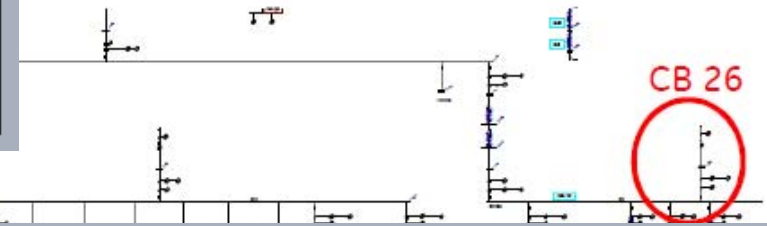


| Event | Date | Time | Cause of Event |
|-------|------------|-------------|---------------------|
| 46 | 03/22/2014 | 22:20:10.05 | Differential Trip |
| 45 | 03/22/2014 | 21:13:33.34 | Differential Trip |
| 44 | 03/22/2014 | 20:50:10.92 | Differential Trip |
| 43 | 03/21/2014 | 11:33:29.68 | Differential Trip |
| 42 | 03/21/2014 | 09:14:34.50 | Differential Trip |
| 41 | 03/21/2014 | 08:47:18.56 | Differential Trip |
| 40 | 03/20/2014 | 23:20:33.15 | Differential Trip |
| 39 | 02/11/2014 | 08:38:36.53 | Cont. Power Applied |
| 38 | 02/11/2014 | 08:38:35.74 | Control Power Lost |
| 37 | 02/11/2014 | 08:31:11.56 | Cont. Power Applied |

| Event | Date | Time | Cause of Event |
|-------|------------|--------------|-----------------------------------|
| 374 | 03/20/2014 | 22:00:48.232 | Pickup: Ground Insta |
| 373 | 03/20/2014 | 22:00:48.232 | Pickup: Ground |
| 372 | 03/20/2014 | 22:00:48.232 | Trip: Phase C - Phase Ins |
| 371 | 03/20/2014 | 22:00:48.232 | Pickup: Phase C - Phase In |
| 370 | 03/20/2014 | 22:00:48.232 | Trigger Trace I |
| 369 | 03/20/2014 | 22:00:48.232 | Trip: Phase C - Phase Ins |
| 368 | 03/20/2014 | 22:00:48.232 | Pickup: Phase C - Phase In |
| 367 | 03/20/2014 | 22:00:48.231 | Trigger Data Logger |
| 366 | 03/20/2014 | 22:00:48.231 | Pickup: Phase C - Phase Time OC 1 |
| 365 | 02/11/2014 | 07:37:38.182 | Trigger Data Logger |

Relays at all three locations tripped. All three had different times. Are these events related???




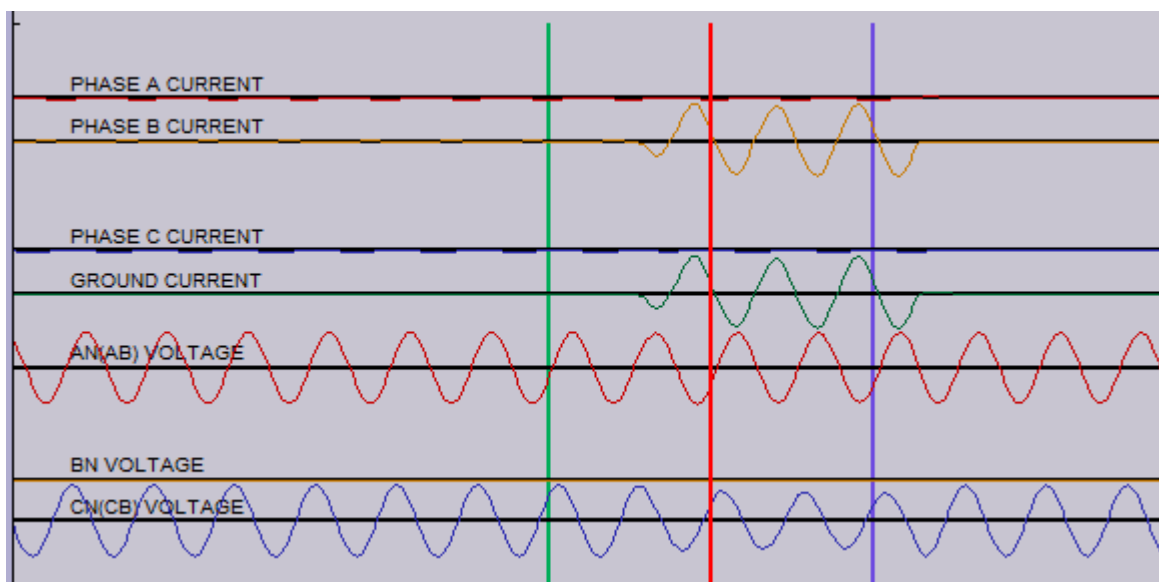Relays at all three locations tripped. All three had different times. Are these events related???




Why B phase on one and C on the other?
CB01

CB402

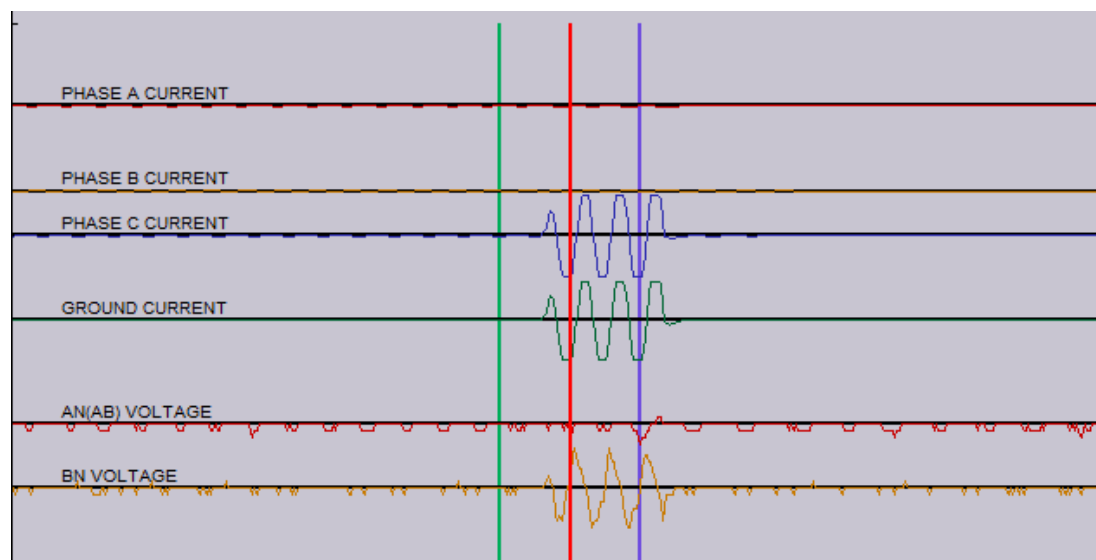


What about the Generator???

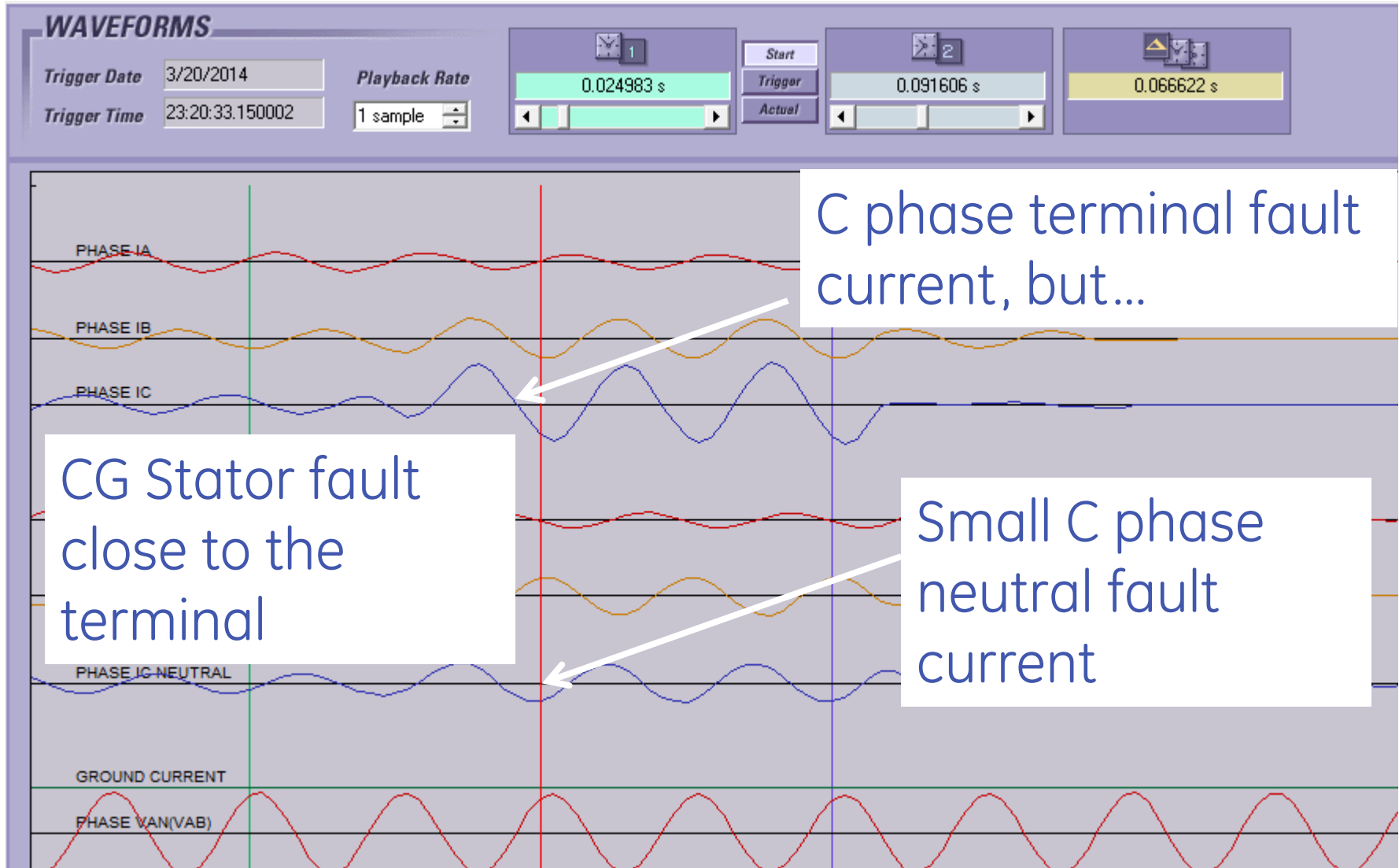

What happened here??


- C phase to ground fault because of the snake
- Zone interlocking scheme failed because of a settings error
- Generator failed due to the extra stress caused by the fault.
- Biggest Challenge was synchronizing the time differences in the relays.

Challenges to Time Synchron

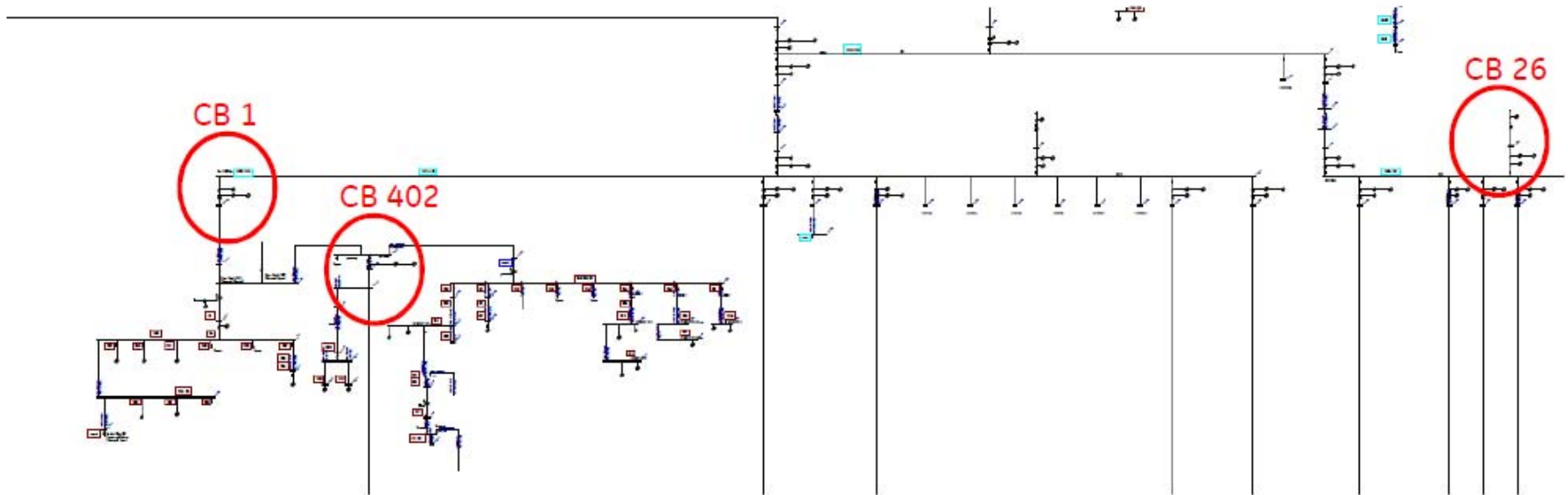




Modern Time Synchronization

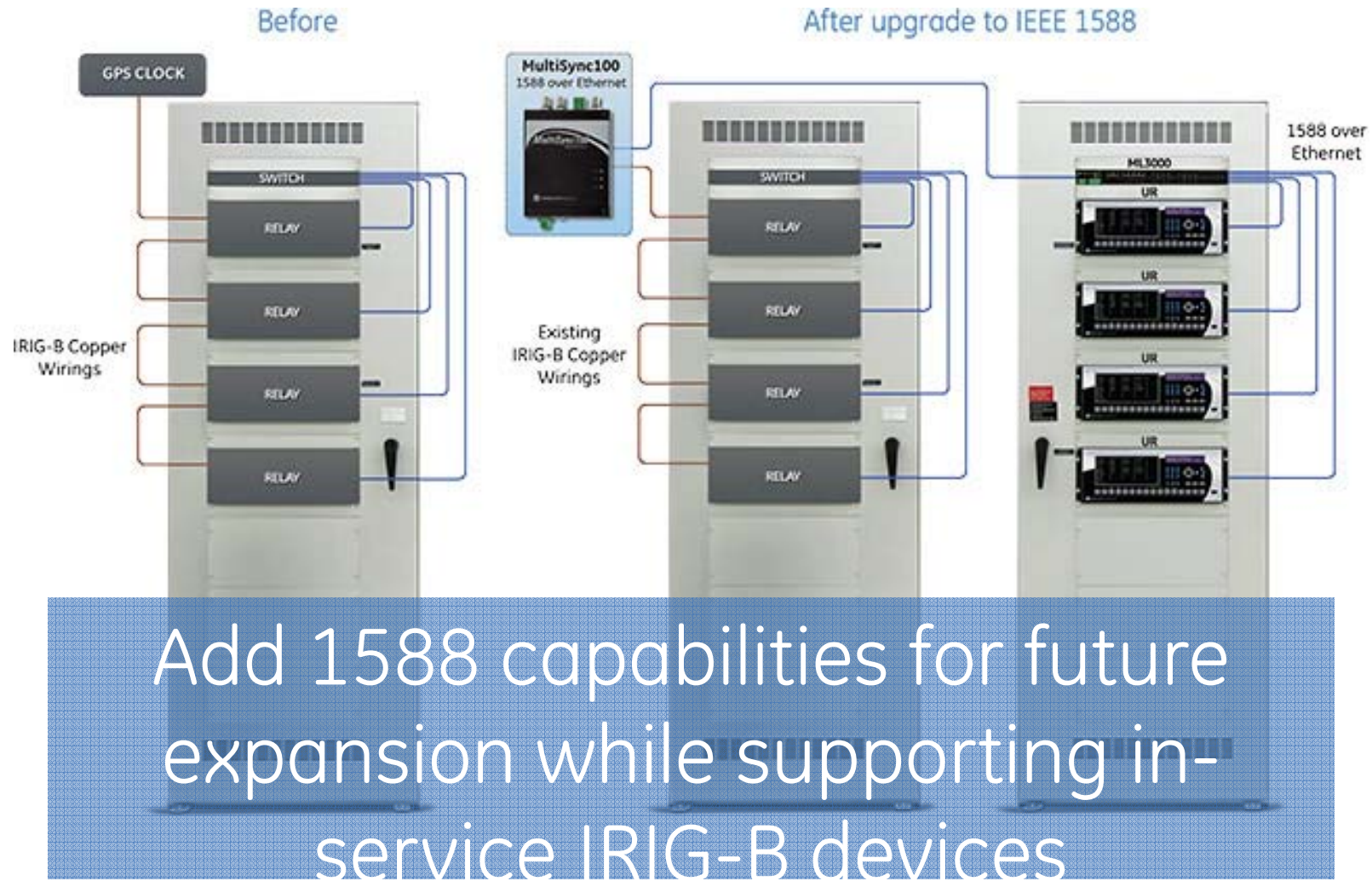



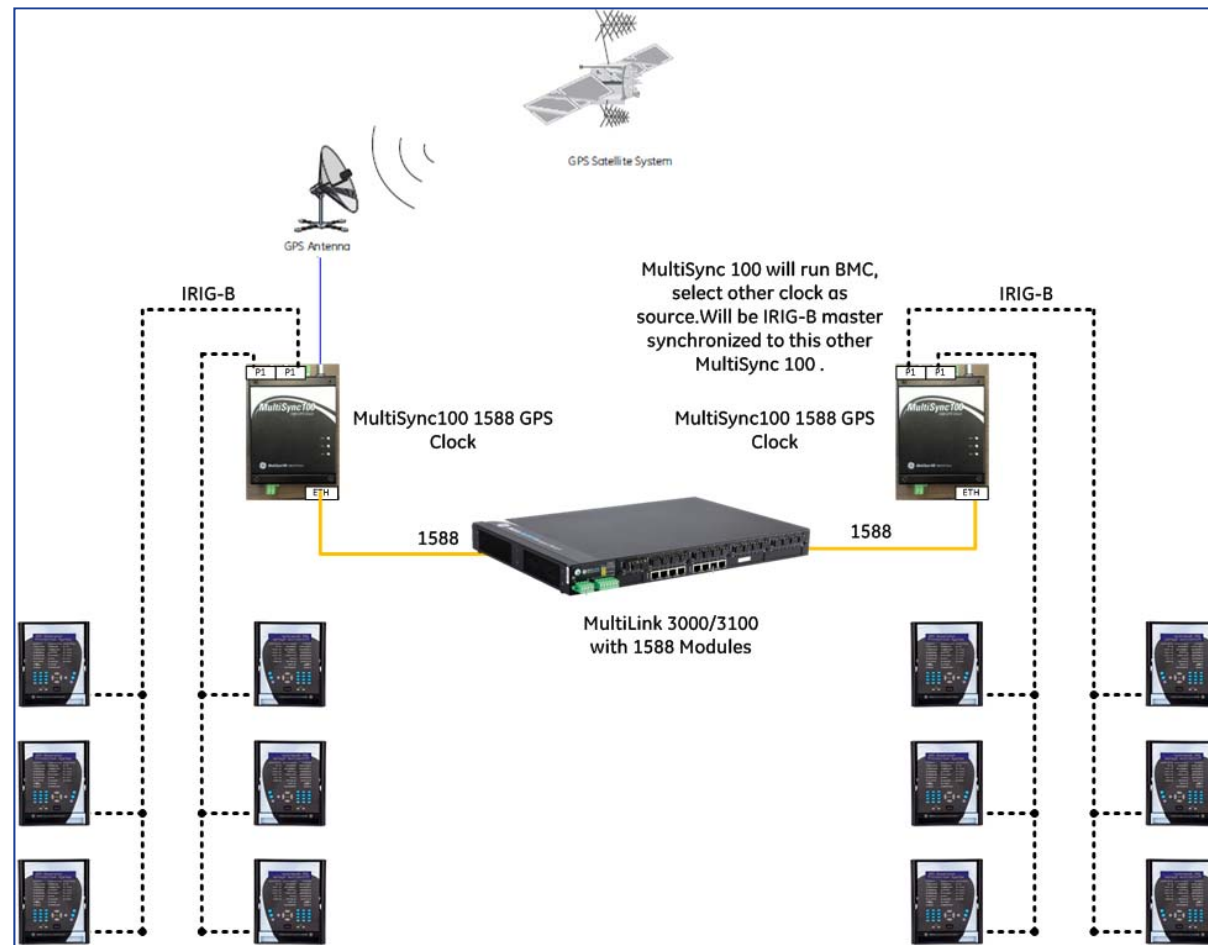
1588 Protocol over a wide area with legacy devices




Generator Relay Failure to Trip on Loss of Excitation

The Story

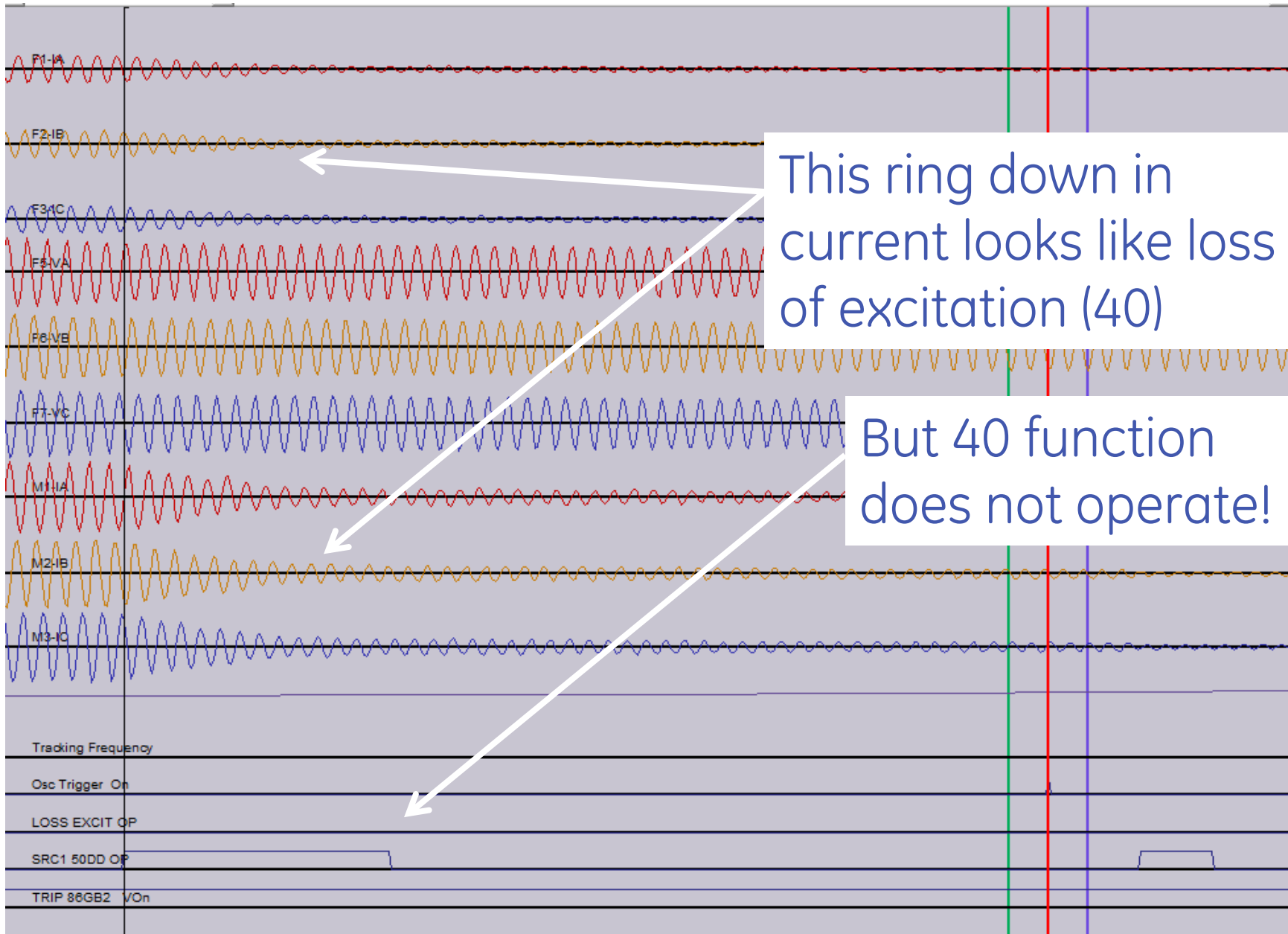- We lost the exciter
- The relay failed to trip on loss of excitaton




Let's look at the phasors

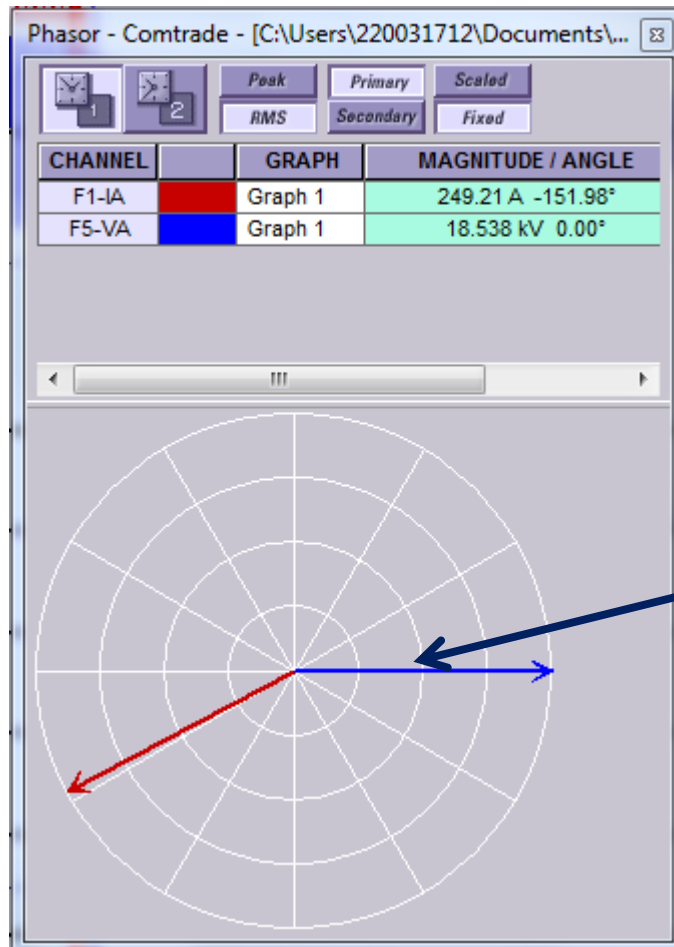


Why is current in opposite direction from voltage?

Machine limits

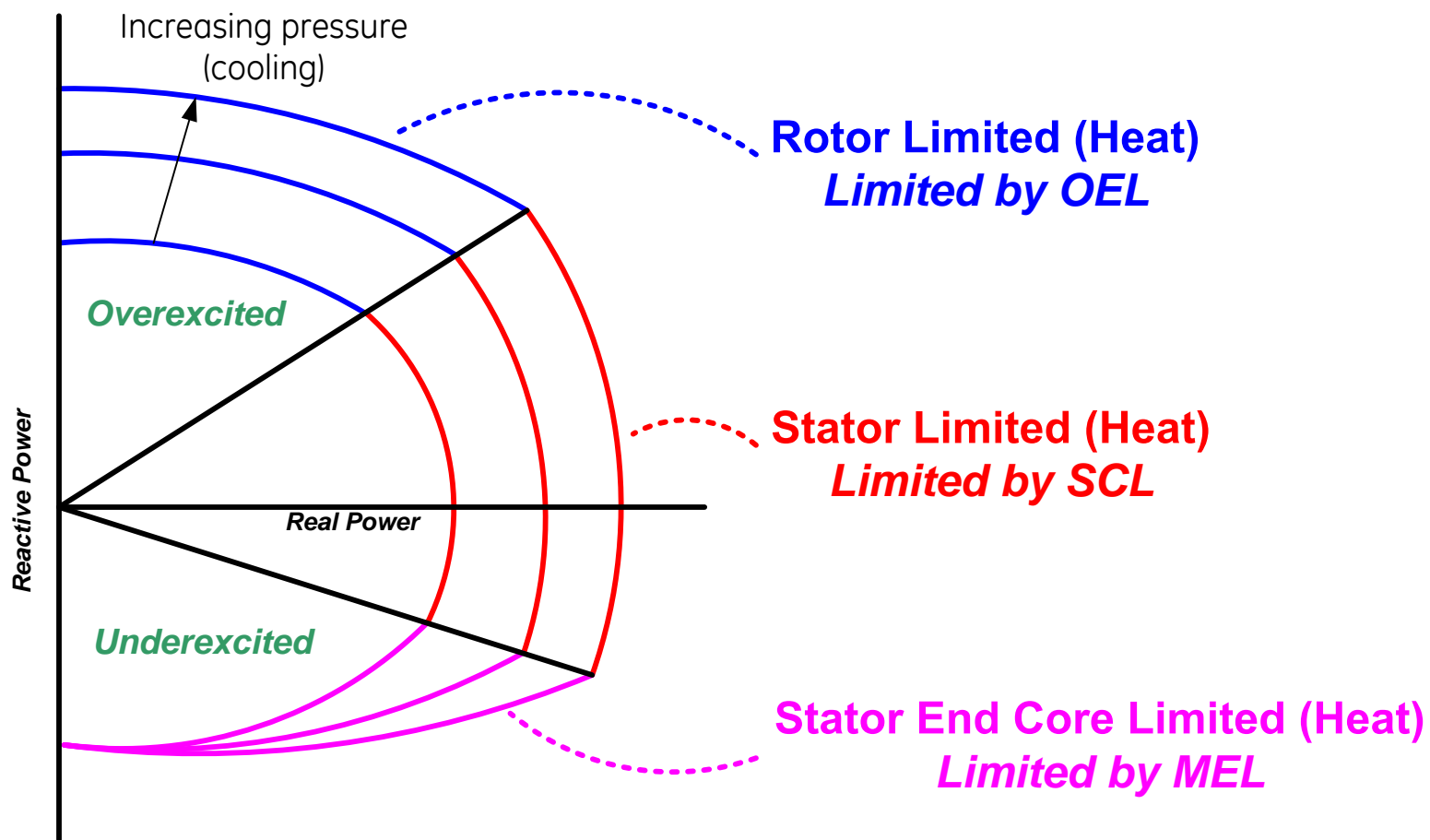

Loss of field

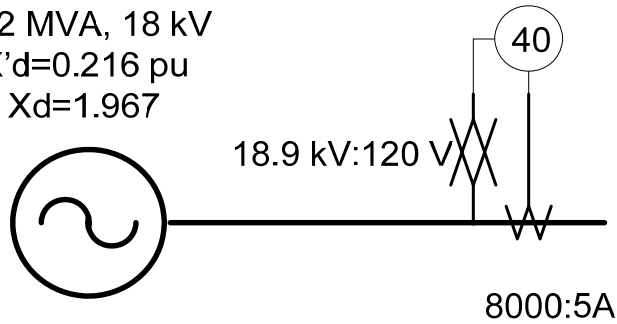212 MVA, 18 kV
 $X'd=0.216$ pu
 $X_d=1.967$




$$VT = \frac{18900}{120} = 157.5$$

$$CT = \frac{8000}{5} = 1600$$

$$Z_{base} \text{ (sec)} = \frac{\text{base } kV^2}{\text{base MVA}} \cdot \frac{CTR}{VTR} = \frac{(18kV)^2}{211MVA} \cdot \frac{1600}{157.5} = 15.54\Omega$$

$$X'_d \text{ (sec)} = X'_d \cdot Z_{base} \text{ (sec)} = 0.216 \cdot 15.54 = 3.36\Omega$$

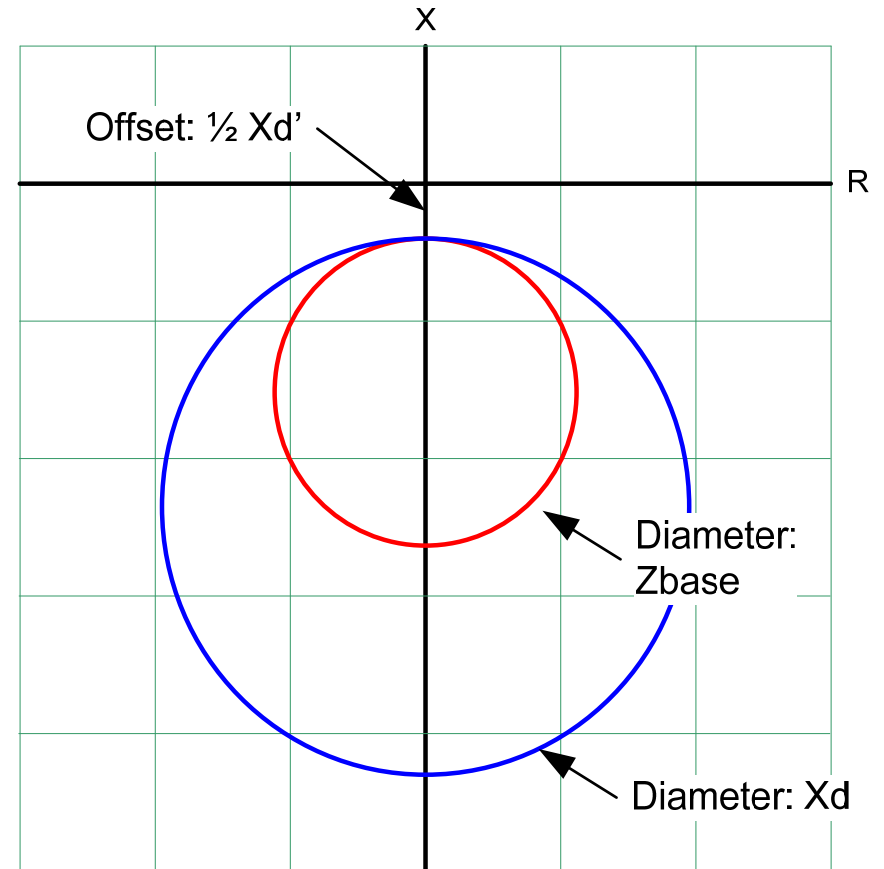
$$X_d \text{ (sec)} = X_d \cdot Z_{base} \text{ (sec)} = 1.967 \cdot 15.54 = 30.57\Omega$$




**Something with your current
is not right !**

**Ok, then why don't I trip on
Differential?**

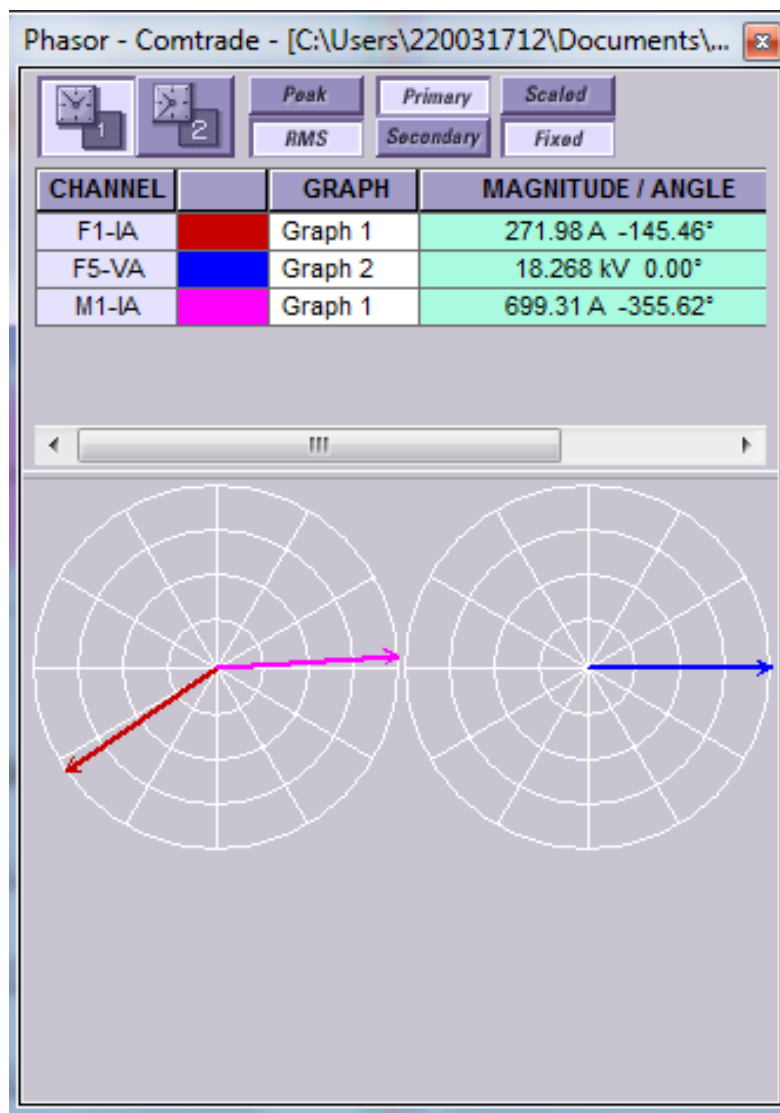Once I account for transformer, currents sum to zero



So what's wrong with 40 function?

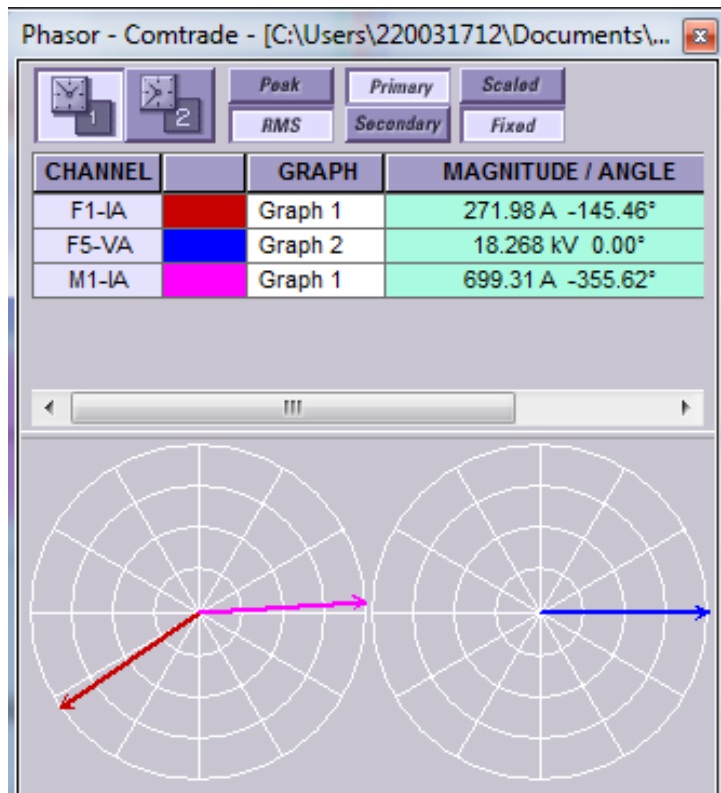

Loss Of Excitation // CCGG30_5_1_10.urs : C:\User...

Save Restore Default Reset VIEW ALL

| SETTING | PARAMETER |
|-------------------------|----------------------|
| Function | Enabled |
| Source | GEN (SRC 1) |
| Center 1 | 2.50 ohm |
| Radius 1 | 2.03 ohm |
| UV Supervision Enable 1 | Enabled |
| Pickup Delay 1 | 0.050 s |
| Center 2 | 3.83 ohm |
| Radius 2 | 3.41 ohm |
| UV Supervision Enable 2 | Enabled |
| Pickup Delay 2 | 0.500 s |
| UV Supervision | 0.700 pu |
| Block | SRC1 VT FUSE FAIL OP |
| Target | Latched |
| Events | Enabled |

CCGG30_5_1_10.urs Grouped Elements: Group 1 Screen ID: 19

Signal Sources // CCGG30_5_1_10.urs : C:\Users\220031712\Documents\Documents\Events\G30 Trip _did not trip on loss of excit...

Save Restore Default Reset VIEW ALL mode

| PARAMETER | SOURCE 1 | SOURCE 2 | SOURCE 3 | SOU |
|-----------|----------|----------|----------|-----|
| Name | GEN | G DIFF | SYNC | SF |
| Phase CT | F1 | M1 | None | Noi |
| Ground CT | M1 | M1 | None | Noi |
| Phase VT | F5 | None | M5 | Noi |
| Aux VT | None | M5 | None | Noi |

CCGG30_5_1_10.urs System Setup Screen ID: 162

Fault on Distribution System Causes Unusual Transformer High Side Currents



imagination at work

The Story


- Distribution transformer feeding medium voltage overhead distribution.
- In oscillography, we see two phases of fault current on the high side of the transformer for a single phase to ground fault on the low side

WAVEFORMS


Trigger Date 1/7/2009
Trigger Time 09:33:38.774539
Playback Rate 1 sample



Control panel for waveform analysis:

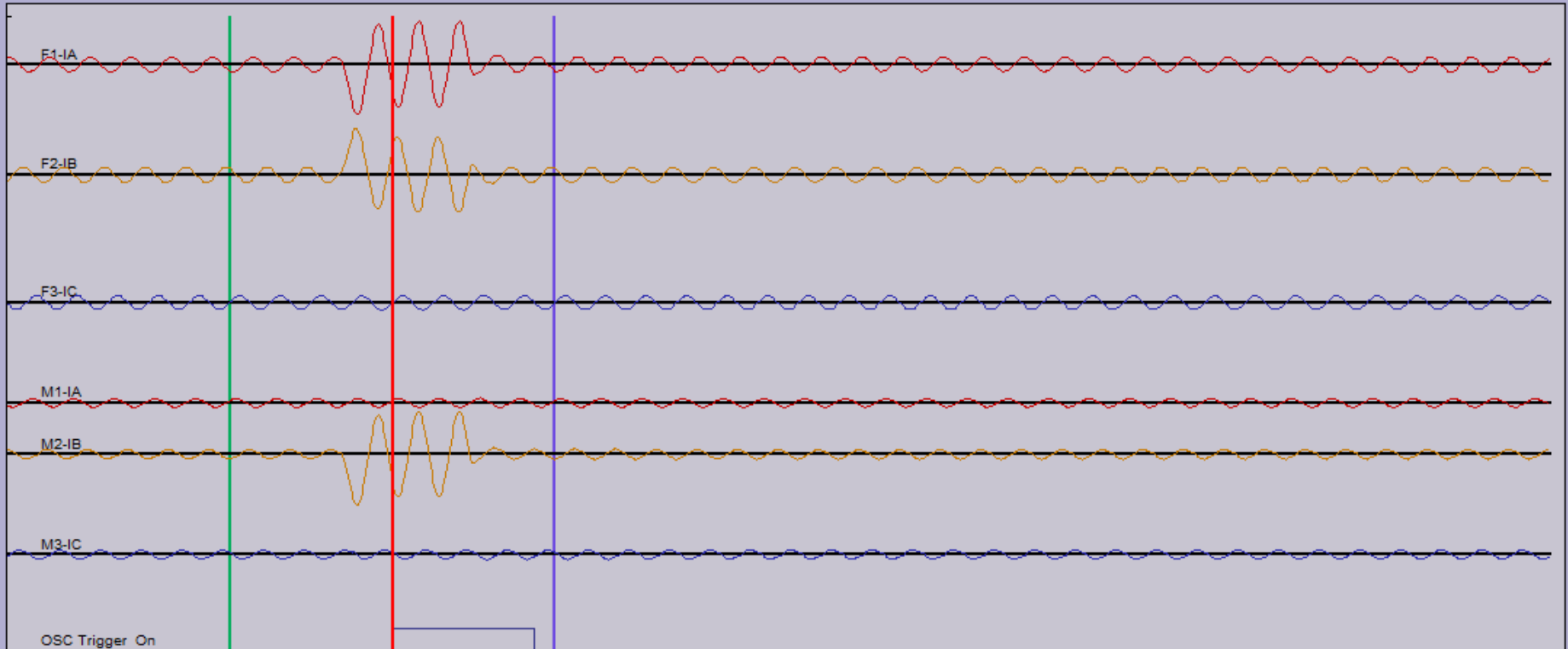- Channel 1: 0.091696 s
- Channel 2: 0.225072 s
- Channel 3: 0.133376 s
- Buttons: Start, Trigger, Actual




Delta-Wye

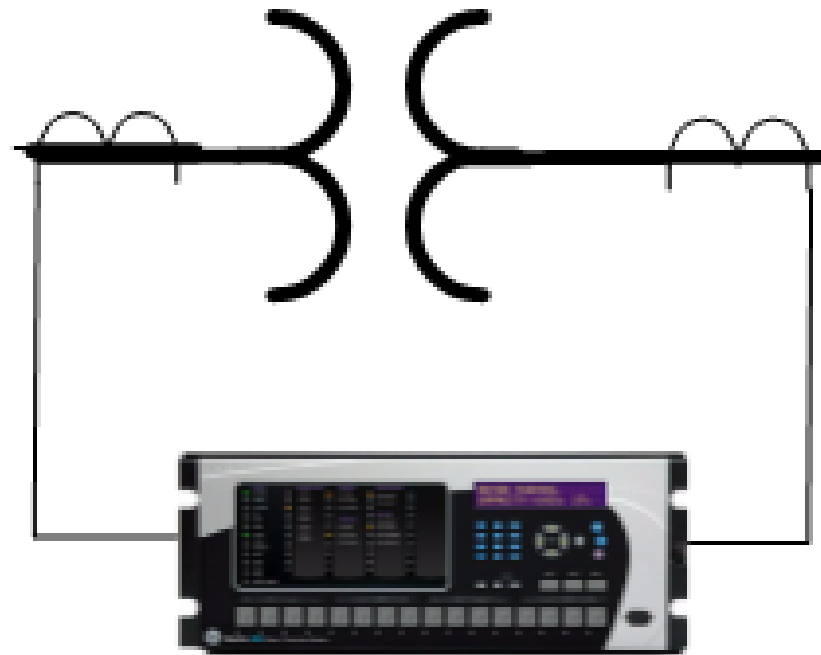

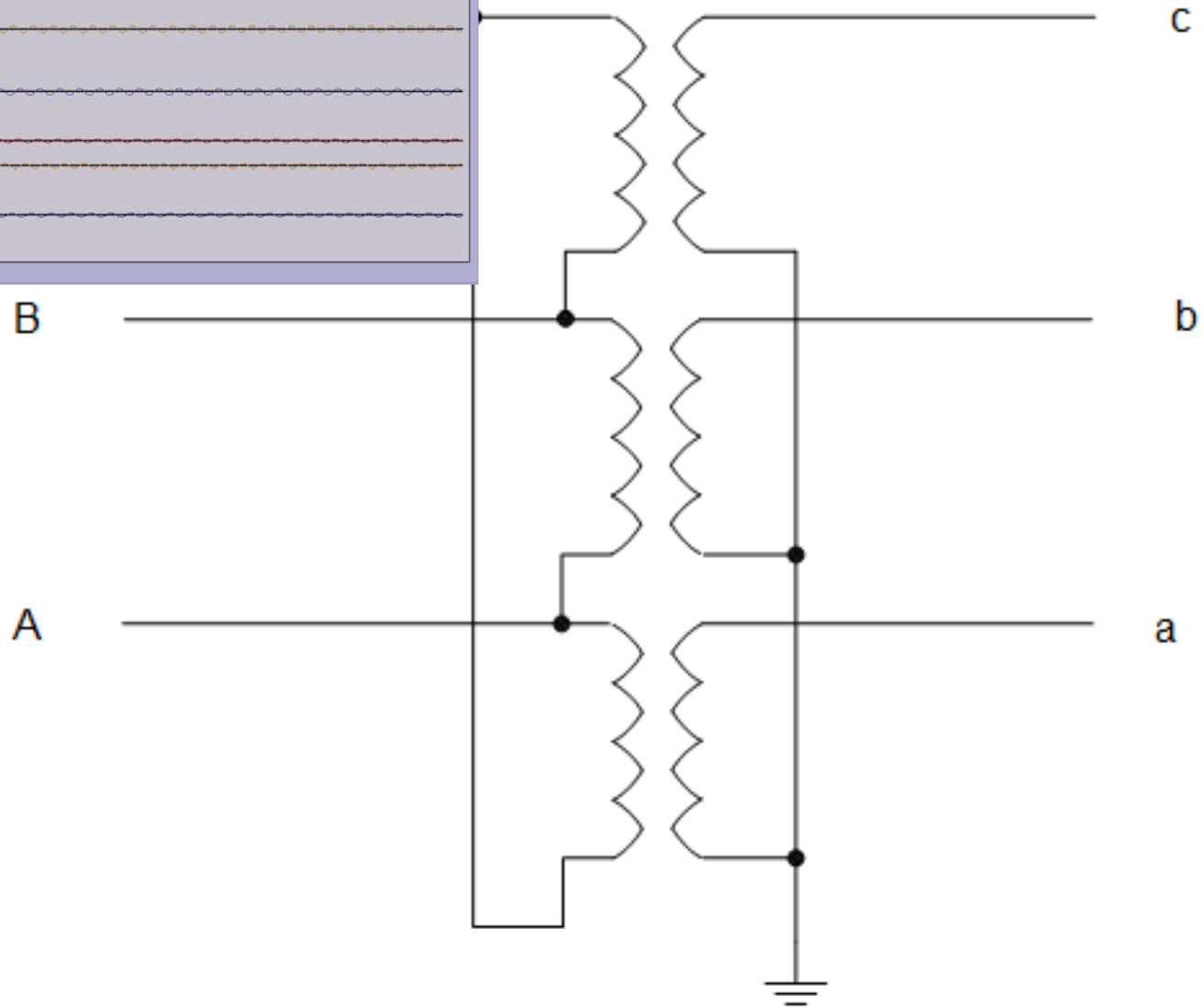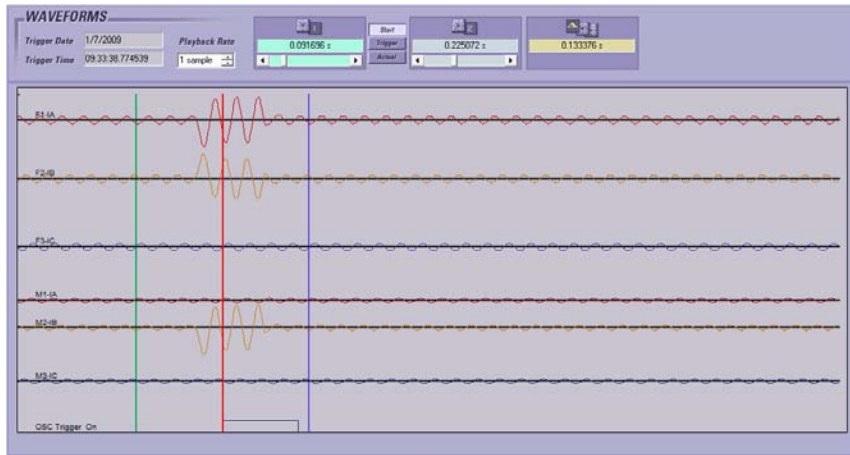


Pre-Fault Values


F1 Symmetrical components

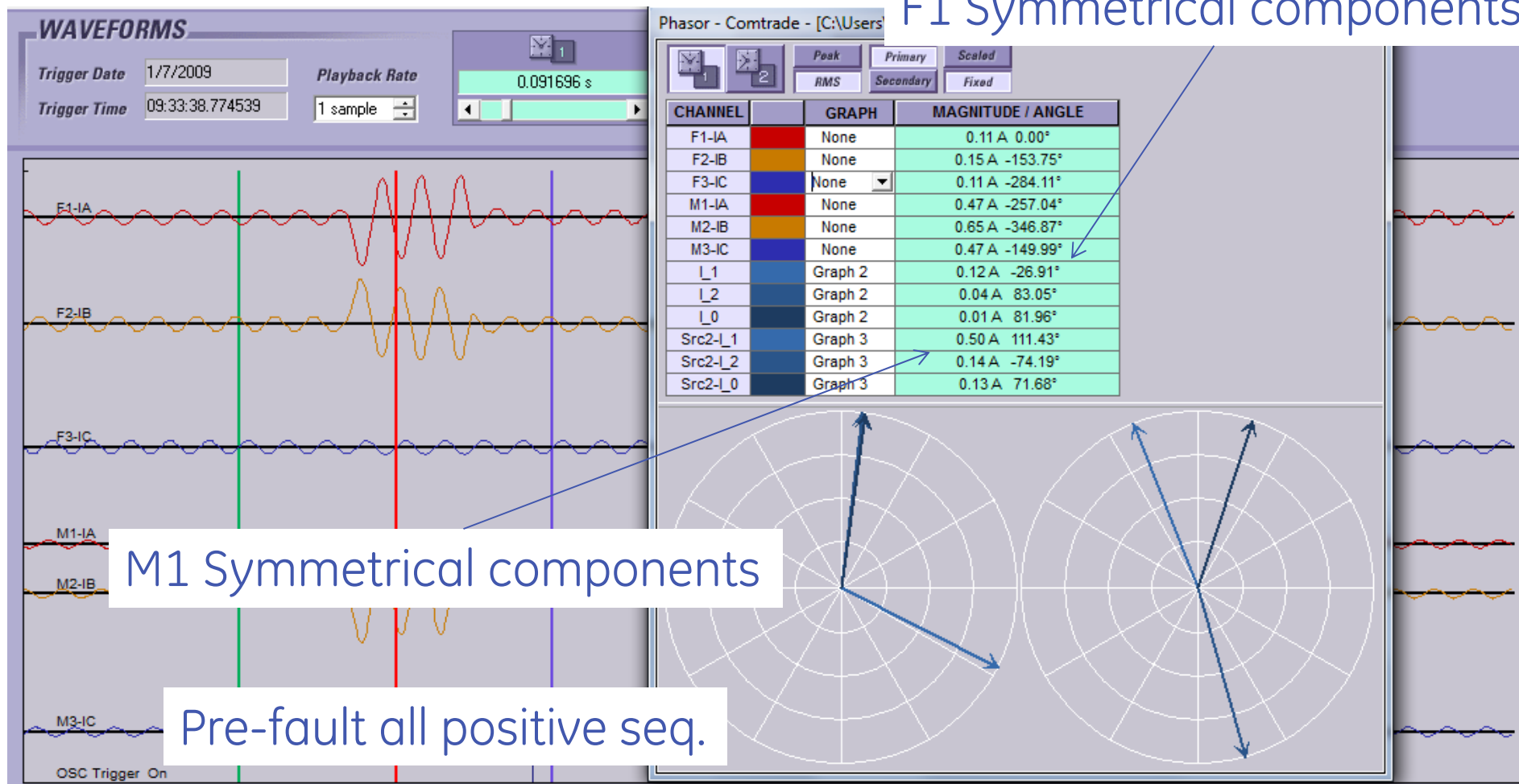

Fault Values

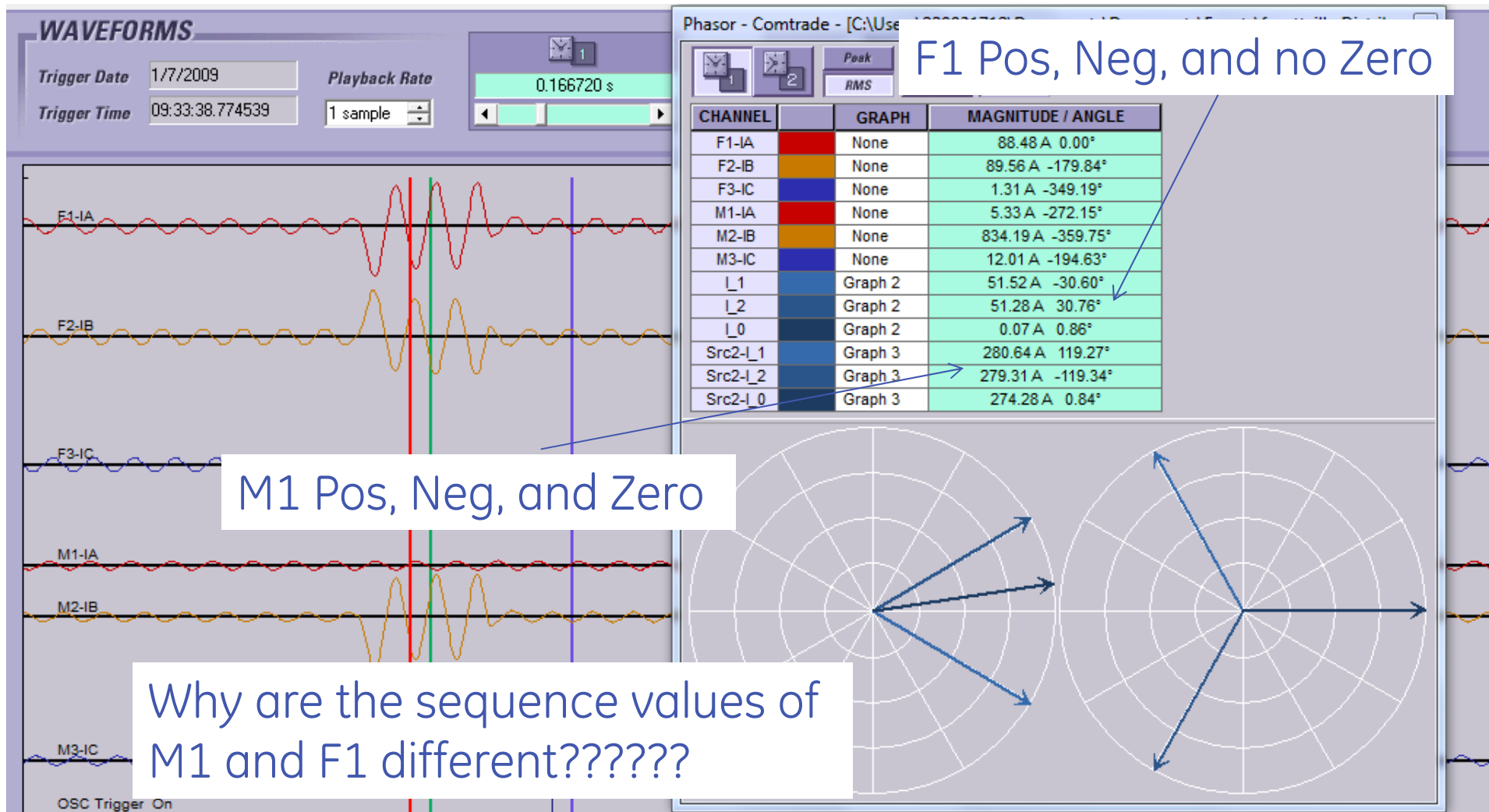


The Fault Network as Seen From F1

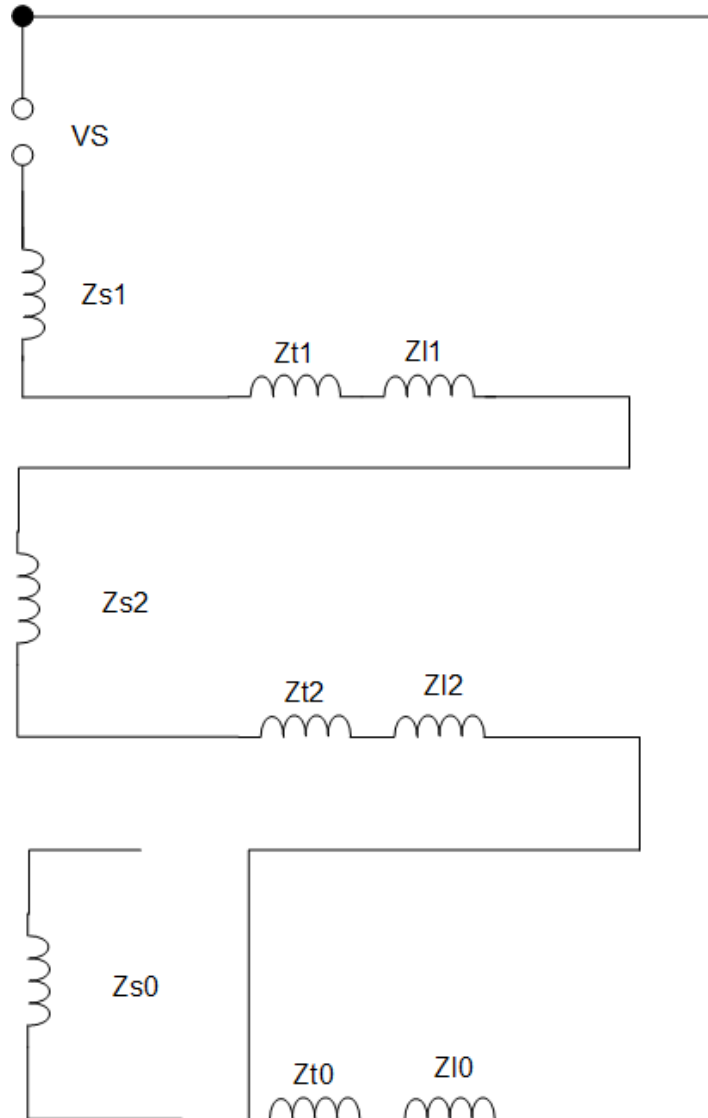


| | | | |
|----------|--|---------|-------------------|
| Src2-I_1 | | Graph 3 | 280.64 A 119.27° |
| Src2-I_2 | | Graph 3 | 279.31 A -119.34° |
| Src2-I_0 | | Graph 3 | 274.28 A 0.84° |

The Fault Network as Seen From M1

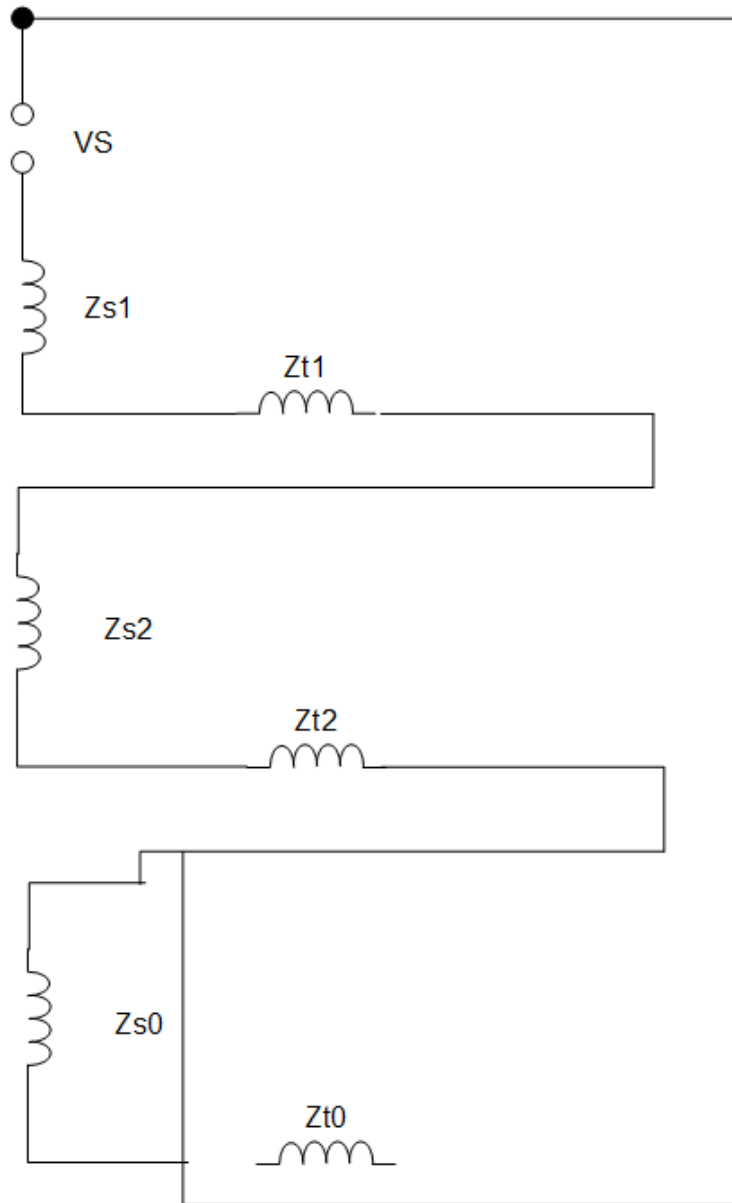


| | | | |
|----------|--|---------|------------------------|
| I_{L1} | | Graph 2 | 51.52 A -30.60° |
| I_{L2} | | Graph 2 | 51.28 A 30.76° |
| I_{L0} | | Graph 2 | 0.07 A 0.86° |

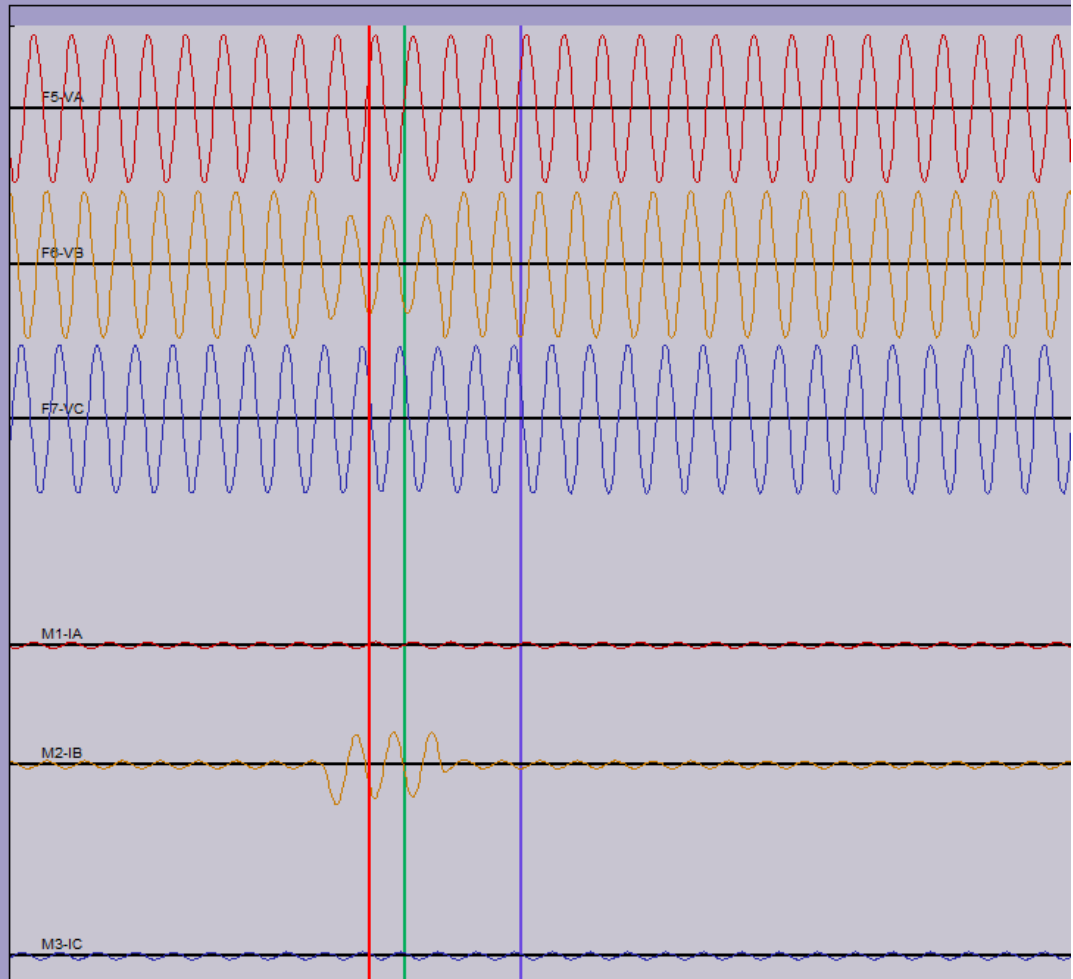What Effect Does this Fault Have on Voltage?



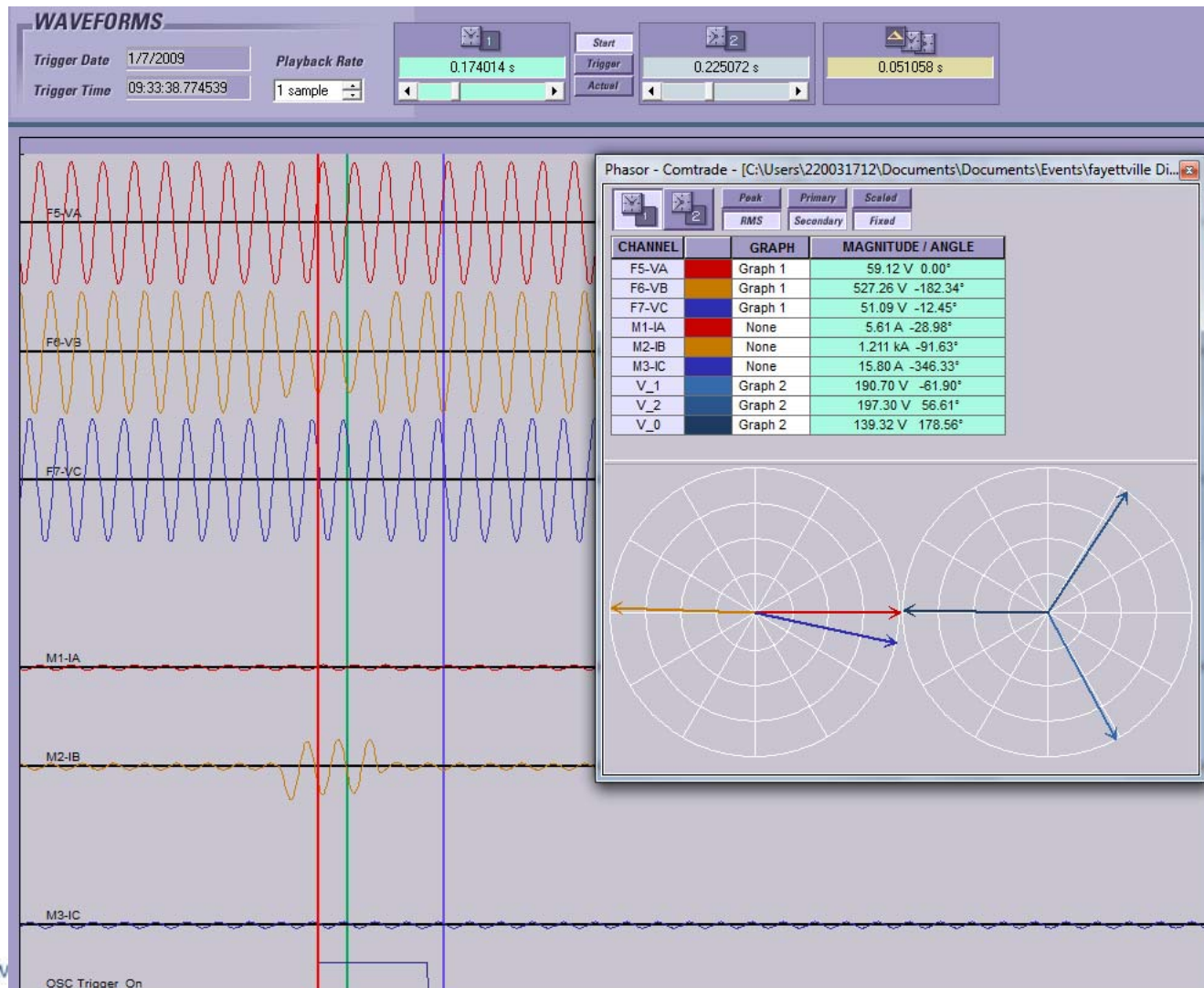What Effect Does this Fault Have on Voltage?



Incorrect current
transformer wiring causes
bus fault during power
transformer energization




imagination at work

The Story

- I have energized the transformer
- As soon as I pickup load, I get a transformer differential.

Oscillography

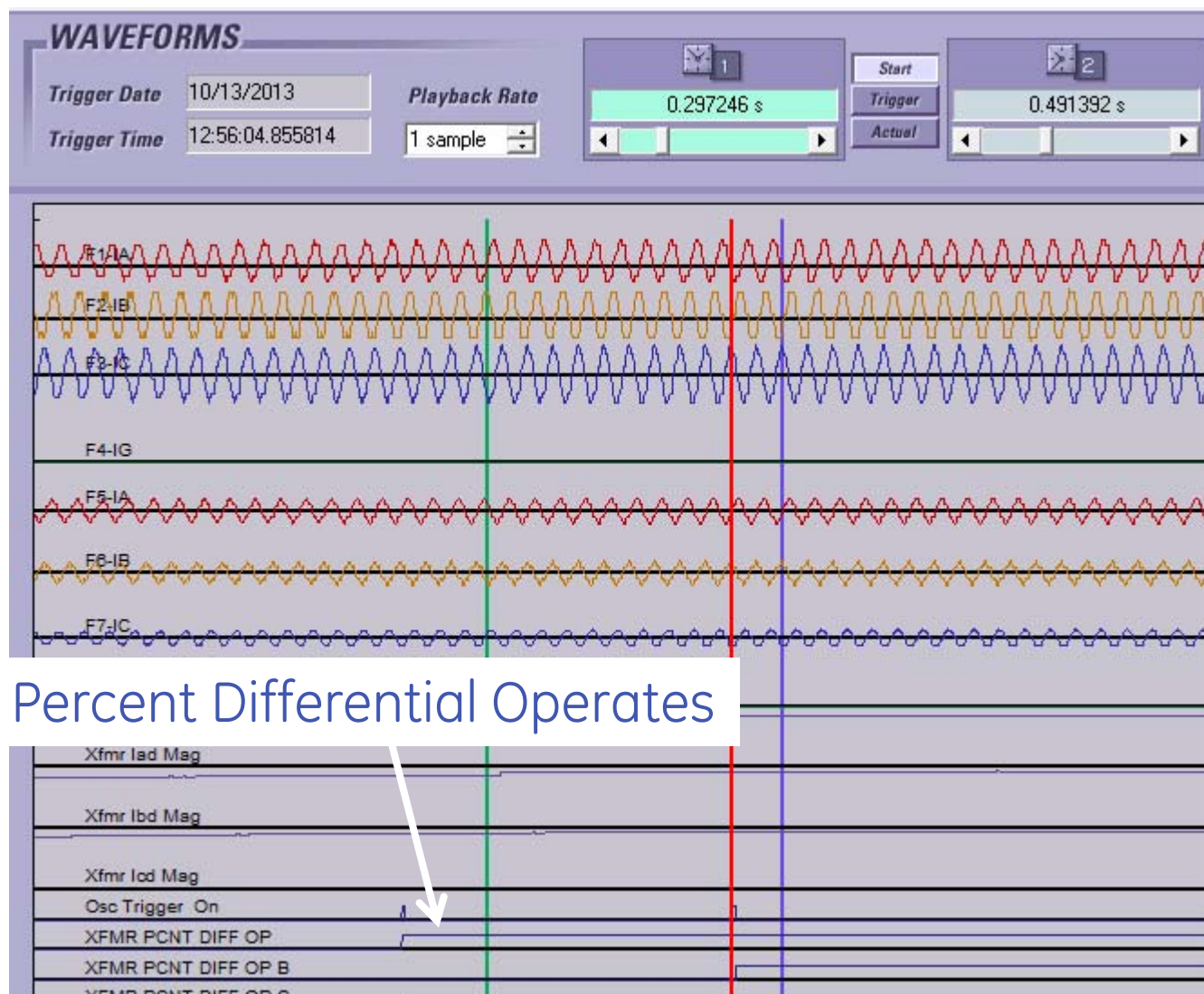


Percent Differential Operates




imagination at work


Oscillography

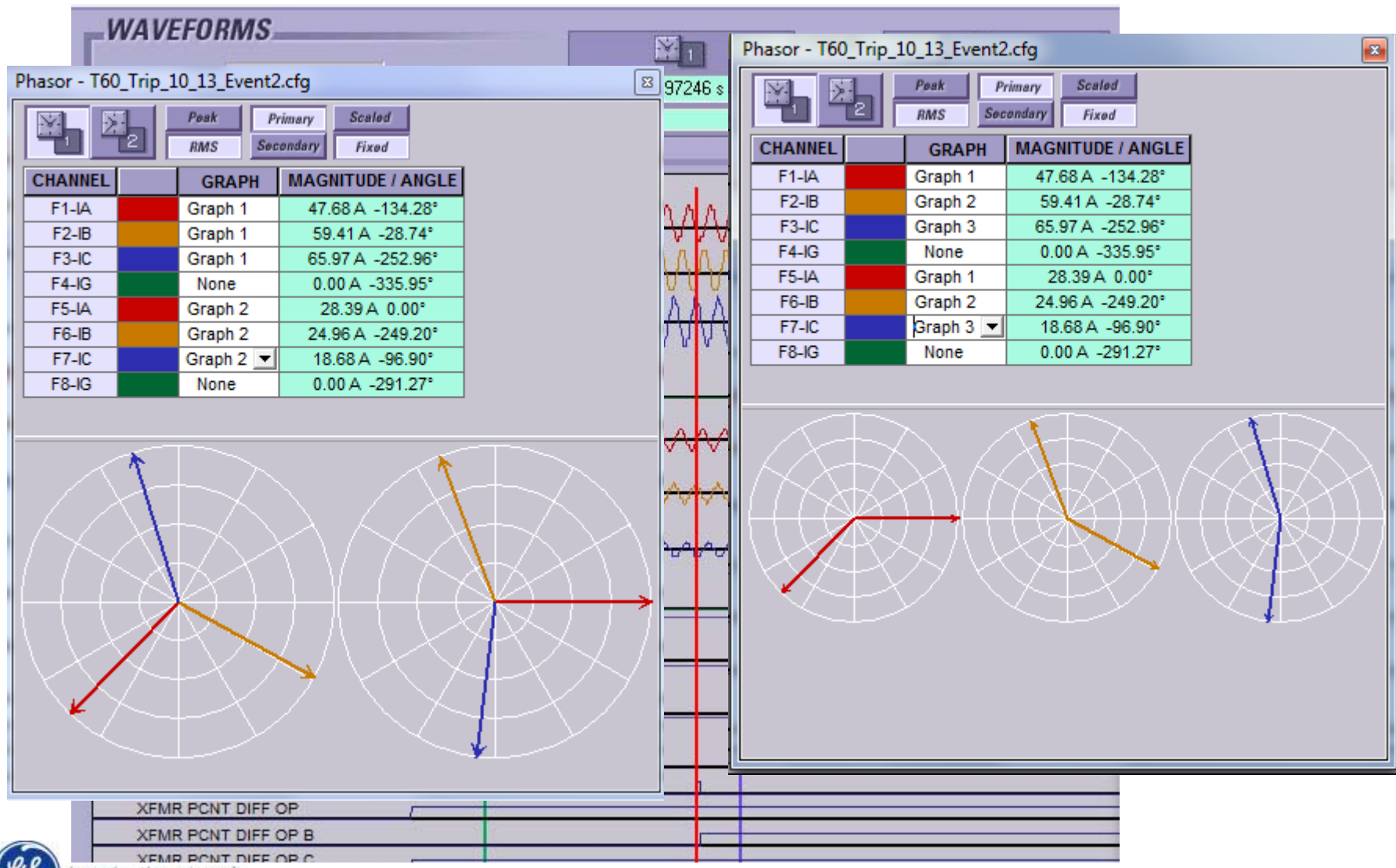


What I expect to see for ABC rotation:

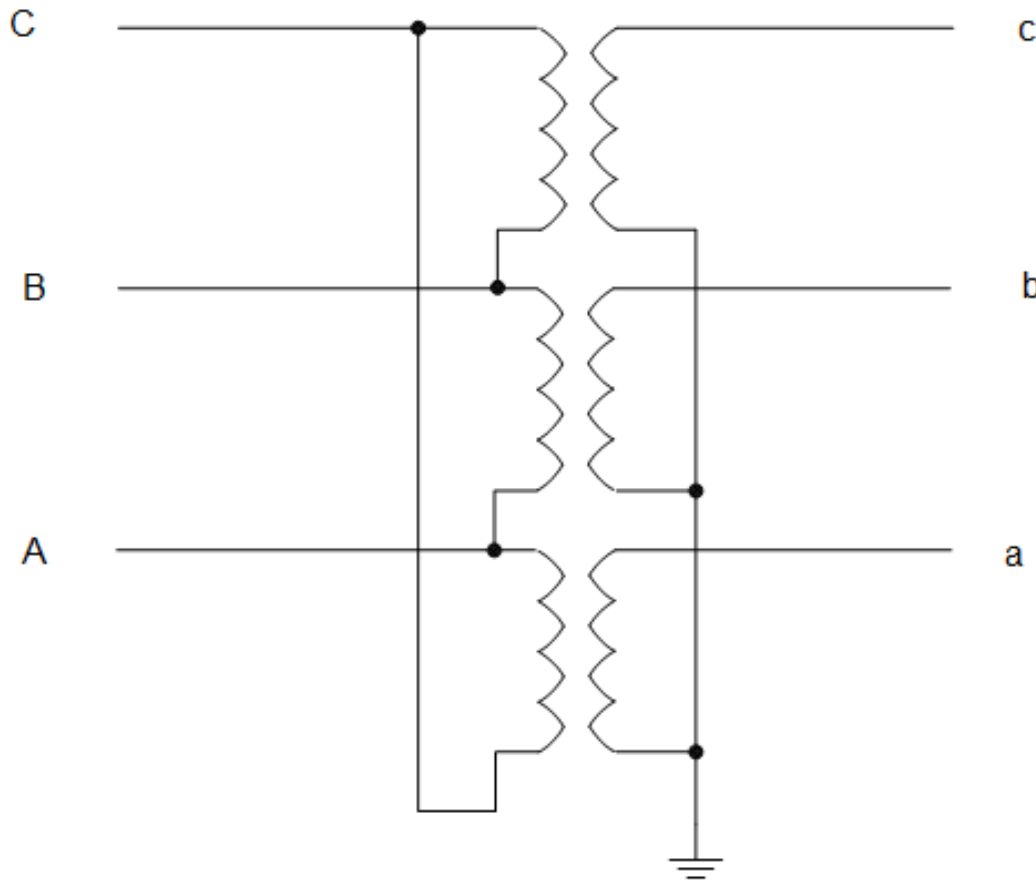

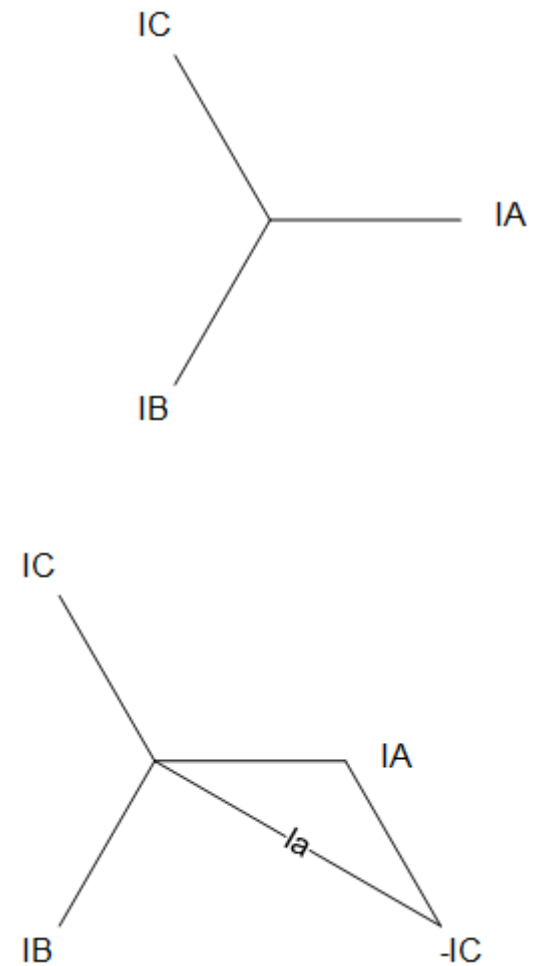Typically H Winding leads X winding by 30 degrees



What I expect to see for ABC rotation:


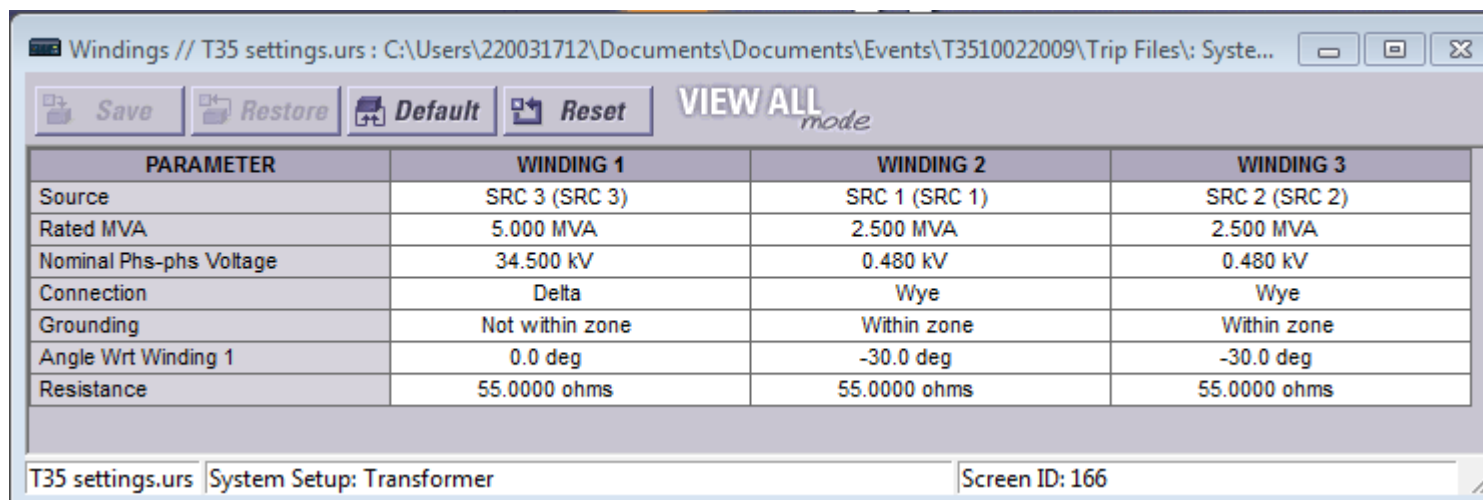


| PARAMETER | WINDING 1 | WINDING 2 | WINDING 3 |
|-------------------------|-----------------|---------------|---------------|
| Source | SRC 3 (SRC 3) | SRC 1 (SRC 1) | SRC 2 (SRC 2) |
| Rated MVA | 5.000 MVA | 2.500 MVA | 2.500 MVA |
| Nominal Phs-phs Voltage | 34.500 kV | 0.480 kV | 0.480 kV |
| Connection | Delta | Wye | Wye |
| Grounding | Not within zone | Within zone | Within zone |
| Angle Wrt Winding 1 | 0.0 deg | -30.0 deg | -30.0 deg |
| Resistance | 55.0000 ohms | 55.0000 ohms | 55.0000 ohms |


We compensate the measured currents with settings

Typically H Winding leads X winding by 30 degrees


What I expect to see for ABC rotation:

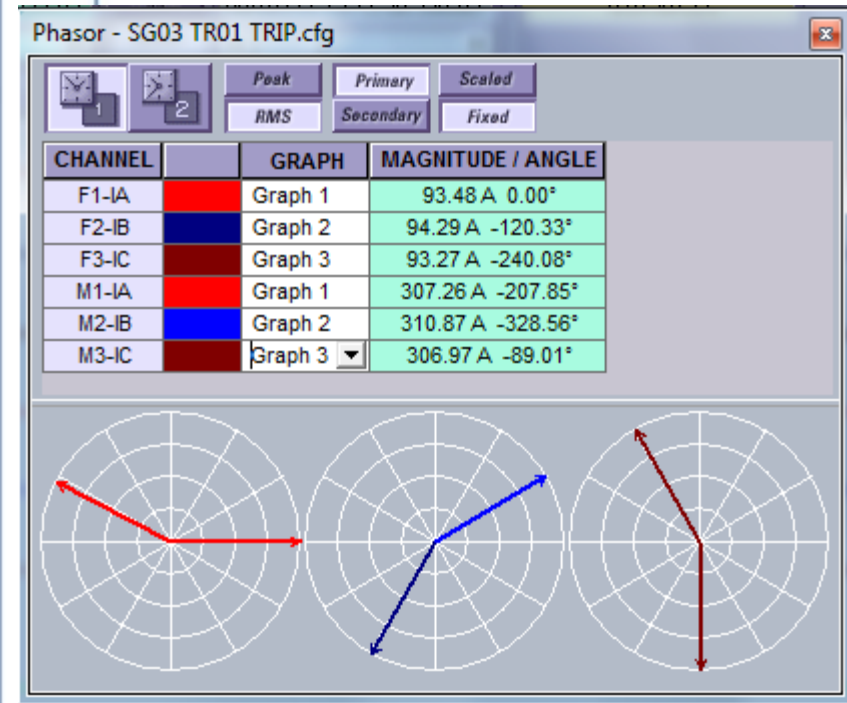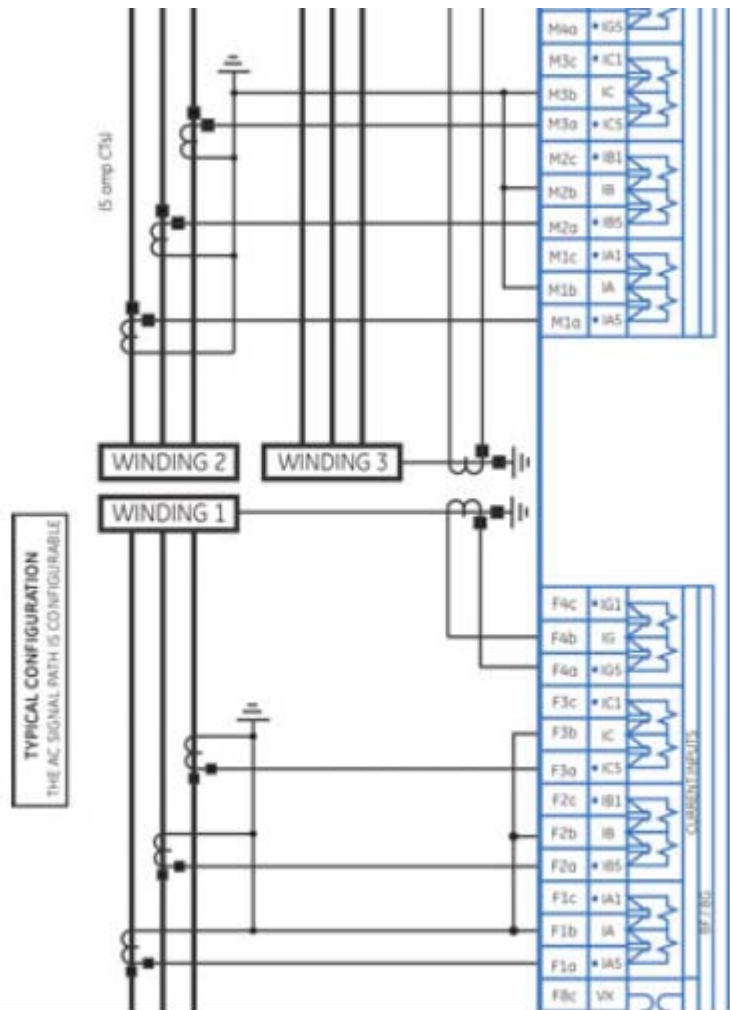


But this isn't ABC rotation:

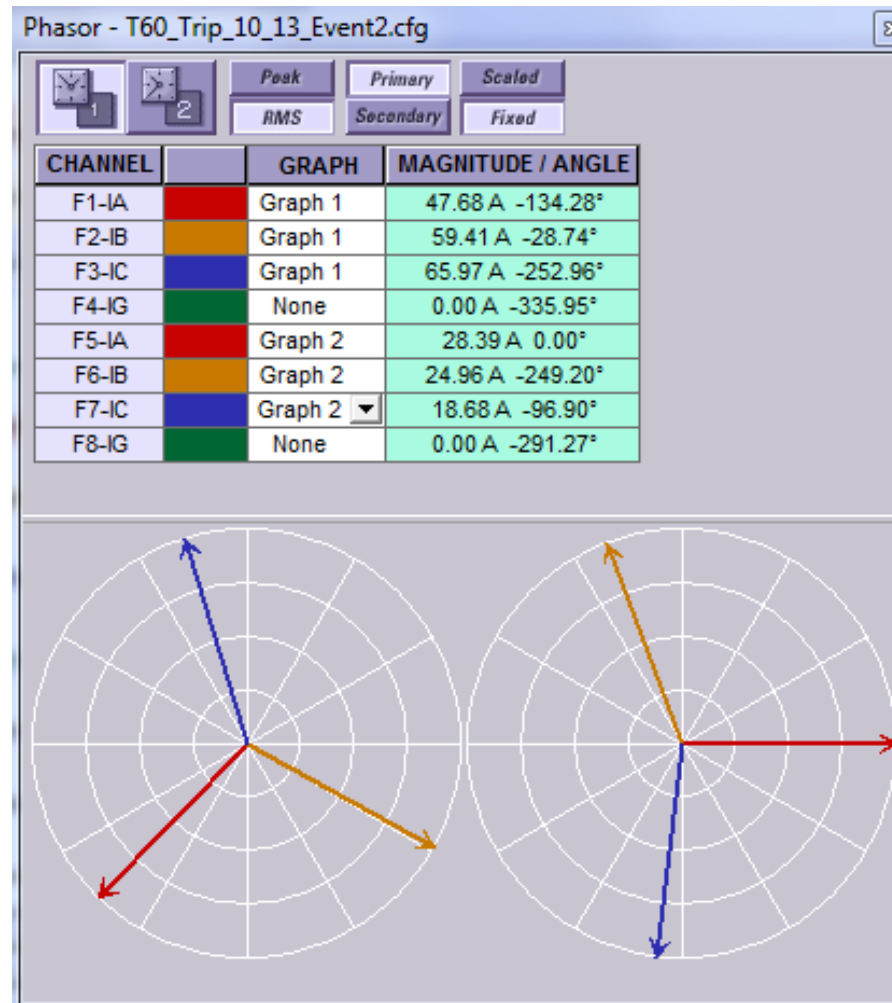

But this isn't ABC rotation:

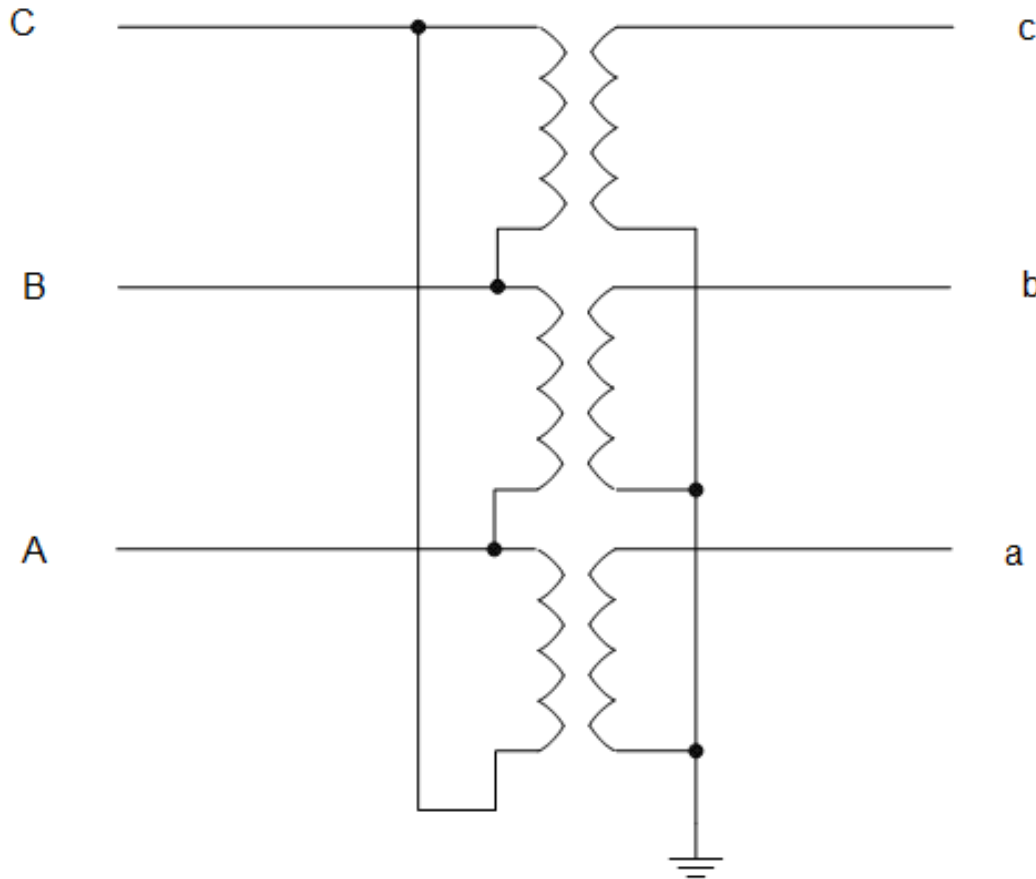

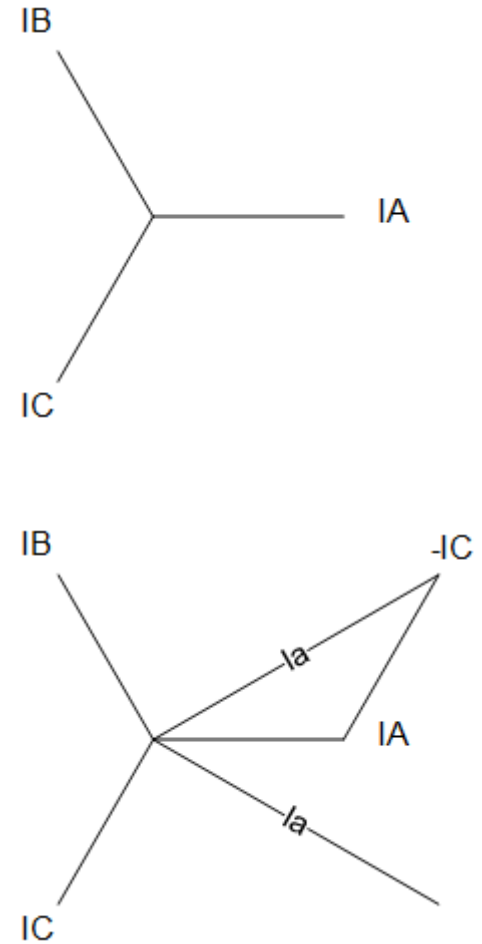Typically H Winding lags X winding by 30 degrees on ACB rotation




Trip occurred because of setting

Windings // T35 settings.urs : C:\Users\220031712\Documents\Documents\Events\T351002

Save Restore Default Reset VIEW ALL mode



| PARAMETER | WINDING 1 | WINDING 2 |
|-------------------------|-----------------|---------------|
| Source | SRC 3 (SRC 3) | SRC 1 (SRC 1) |
| Rated MVA | 5.000 MVA | 2.500 MVA |
| Nominal Phs-phs Voltage | 34.500 kV | 0.480 kV |
| Connection | Delta | Wye |
| Grounding | Not within zone | Within zone |
| Angle Wrt Winding 1 | 0.0 deg | -30.0 deg |
| Resistance | 55.0000 ohms | 55.0000 ohms |

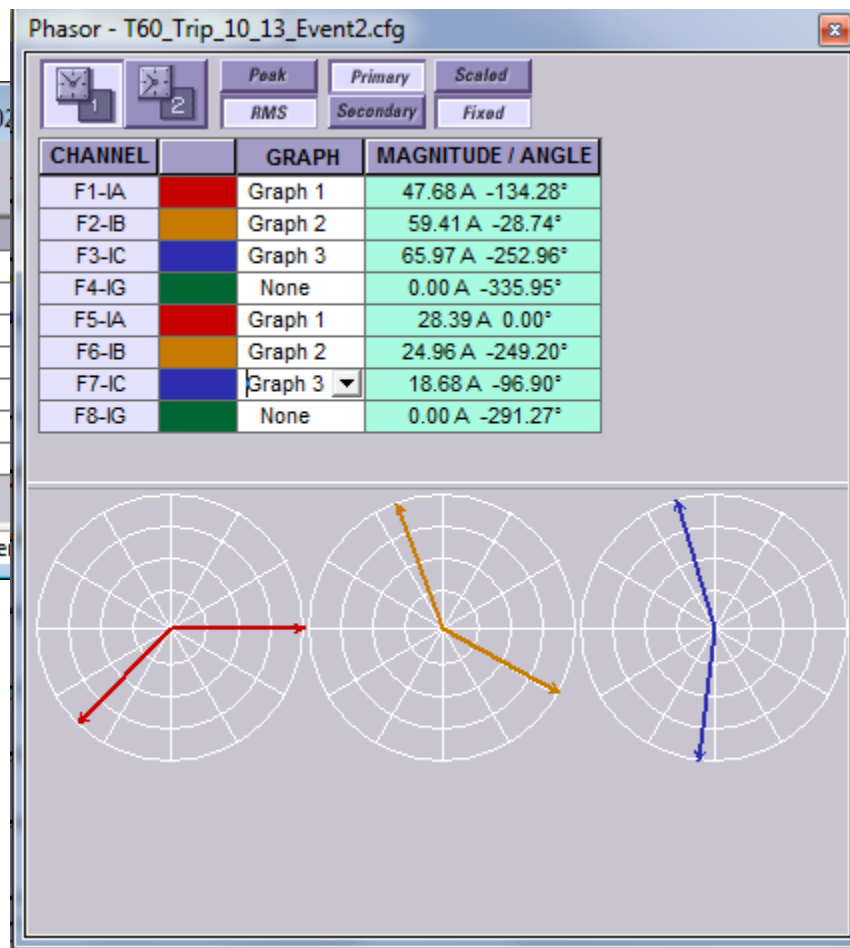T35 settings.urs System Setup: Transformer Screen



Typically H Winding lags X winding by 30 degrees on ACB rotation

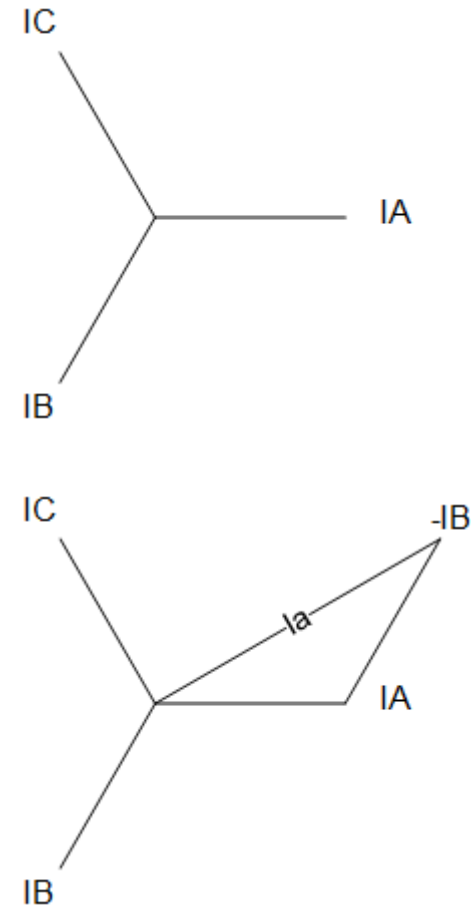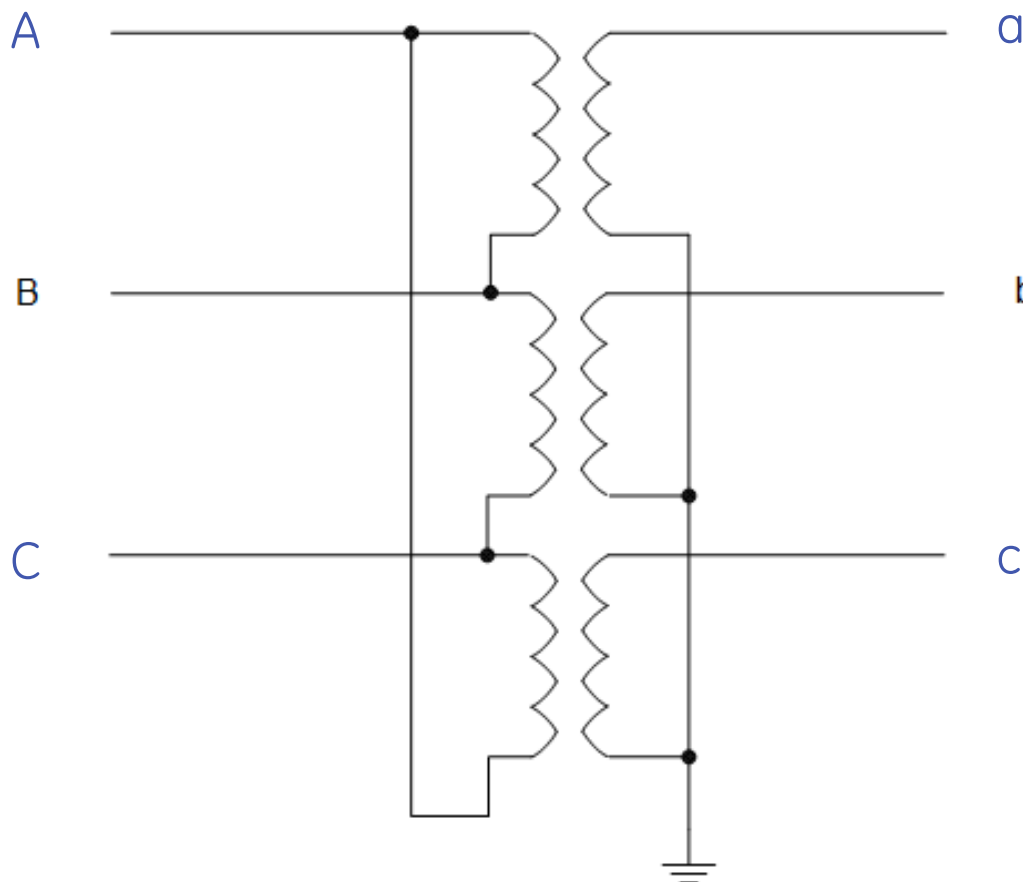What happens if I swap phases on my H winding:




Swapping phases on the High side changes my transformer from 30 lag to 30 lead

Reversed Phase Causes Motor Thermal Overload Trip

The Story


- New switchgear feeding motor
- When we start the motor, it trips after about 10 minutes.

Waveforms

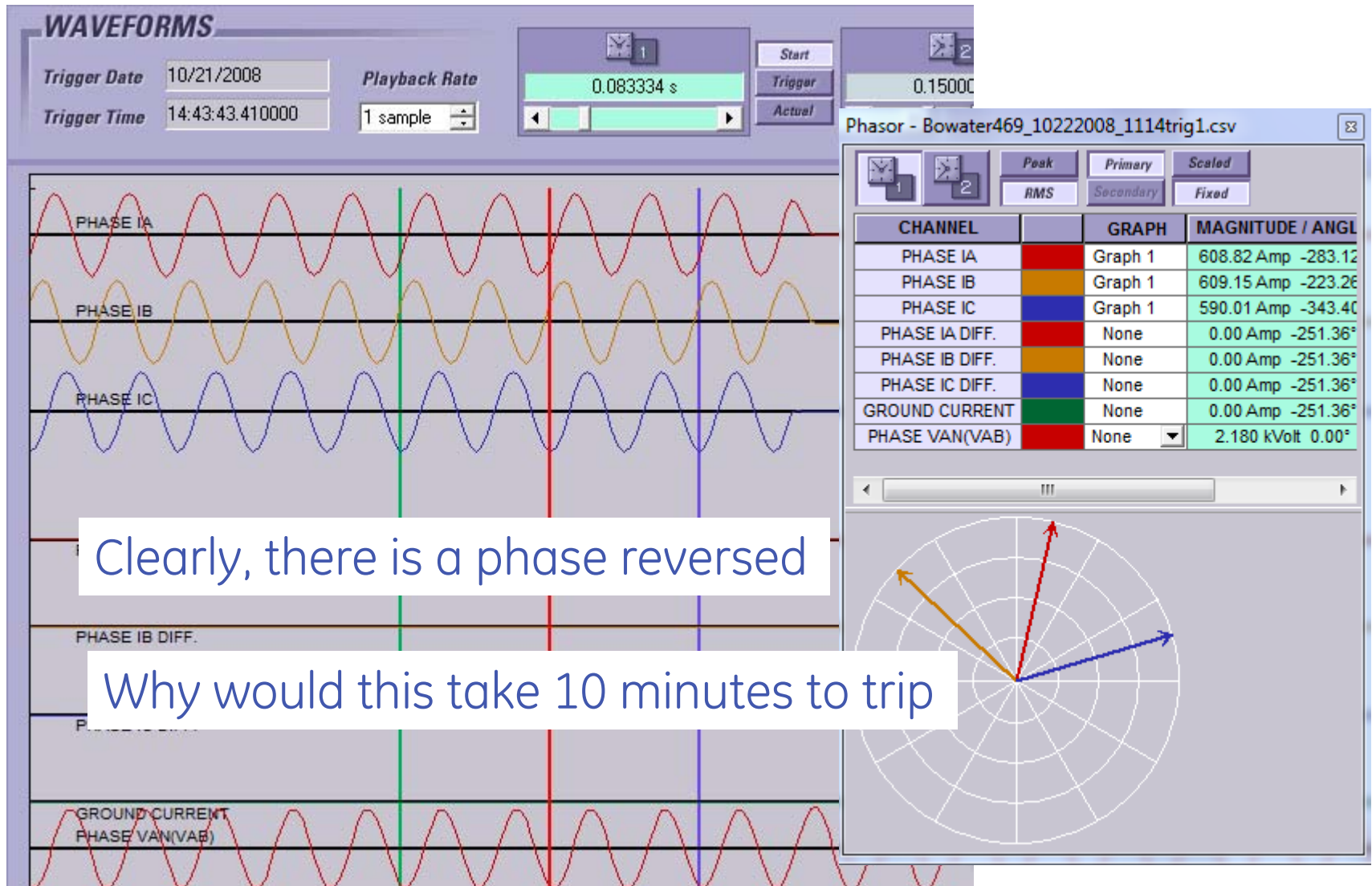



Thermal Model – Thermal Capacity Used

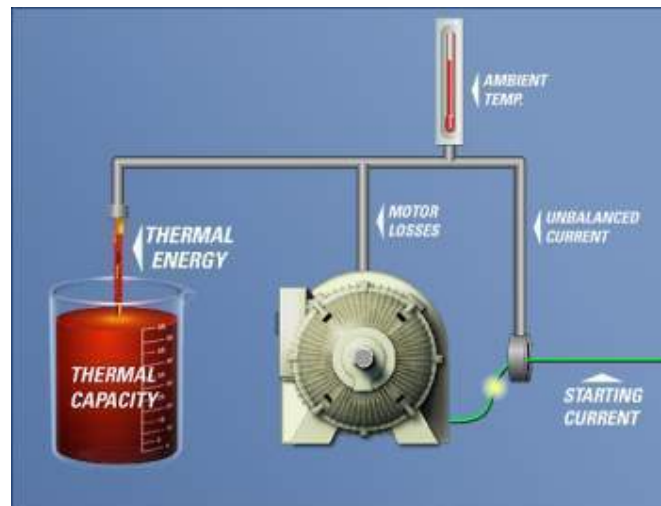- Thermal Capacity Used (TCU) is a criterion selected in thermal model to evaluate thermal condition of the motor.
- TCU is defined as percentage of motor thermal limit utilized during motor operation.
- A running motor will have some level of thermal capacity used due to Motor Losses.
- Thermal Trip when Thermal Capacity Used equals 100%




Thermal Model - Current Unbalance Bias

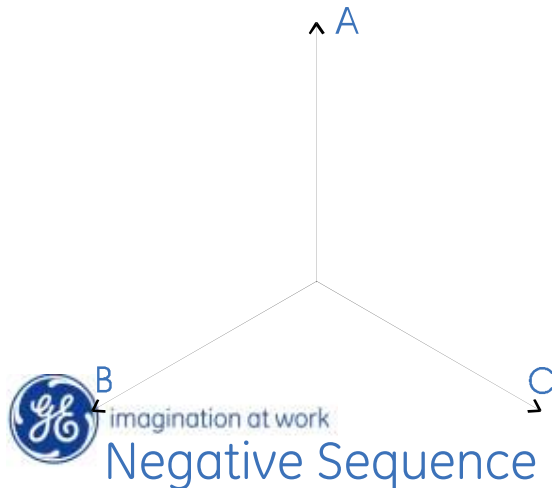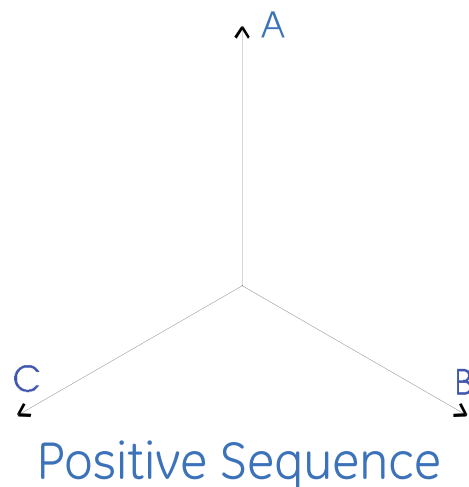Negative sequence currents (or unbalanced phase currents) will cause additional rotor heating that will be accounted for in Thermal Model.



- Main causes of current unbalance

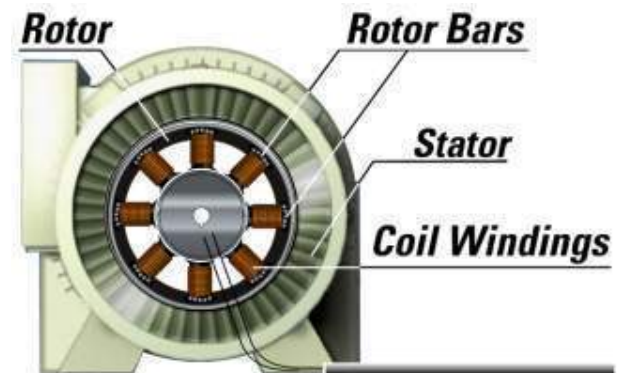- Blown fuses
- Loose connections
- Stator turn-to-turn faults
- System voltage distortion and unbalance
- Faults



Thermal Model - Current Unbalance Bias


- **Equivalent heating motor current** is employed to bias thermal model in response to current unbalance.

$$I_{EQ} = \sqrt{I_M^2 \times (1 + K \times (I_2/I_1)^2)}$$


- I_m - real motor current; K - unbalance bias factor; I_1 & I_2 - positive and negative sequence components of motor current.
- K factor reflects the degree of extra heating caused by the negative sequence component of the motor current.
- IEEE guidelines for typical and conservative estimates of K .

$K = 175/I_{LRC}^2$ TYPICAL

$K = 230/I_{LRC}^2$ CONSERVATIVE

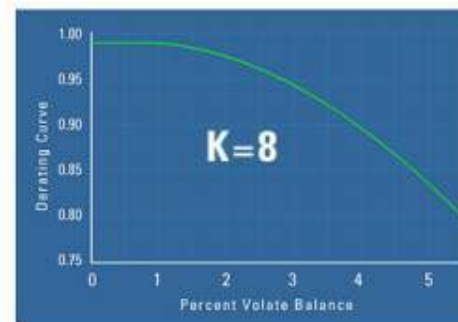


NEMA

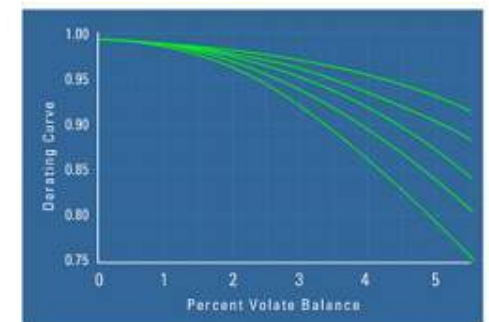


Multilin

Motor Derating Curves

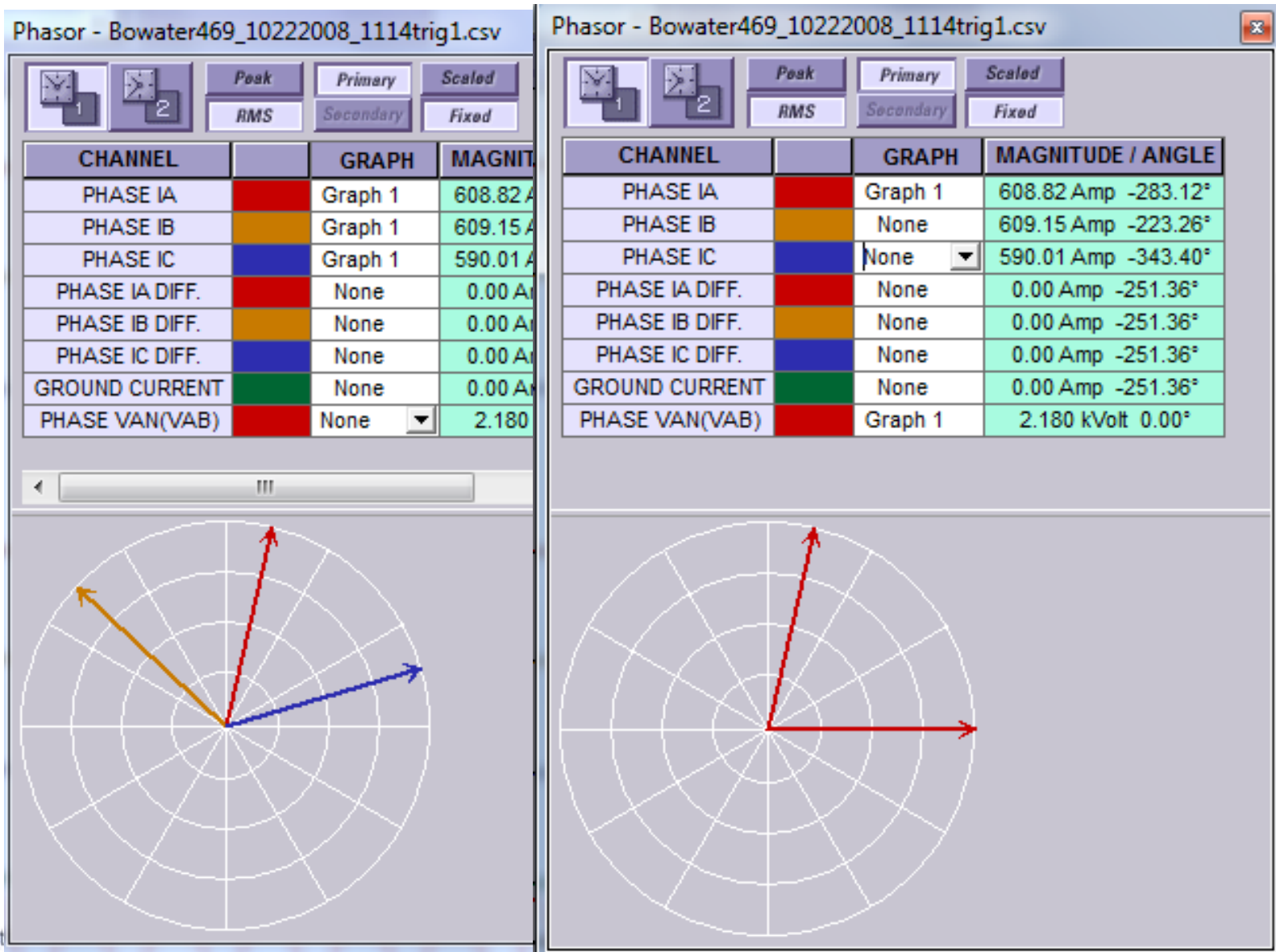
Is the reversed phase the only error here?



VAB voltage relative to VAG


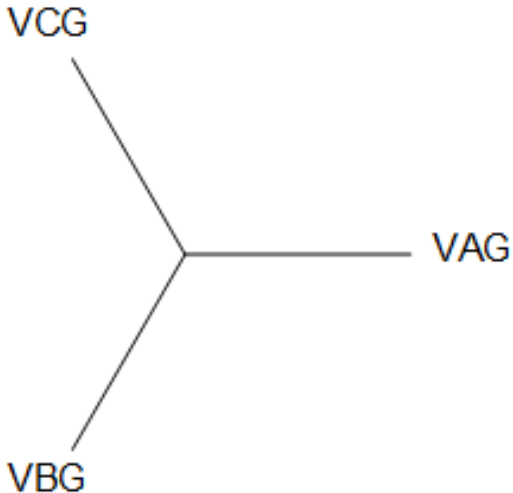


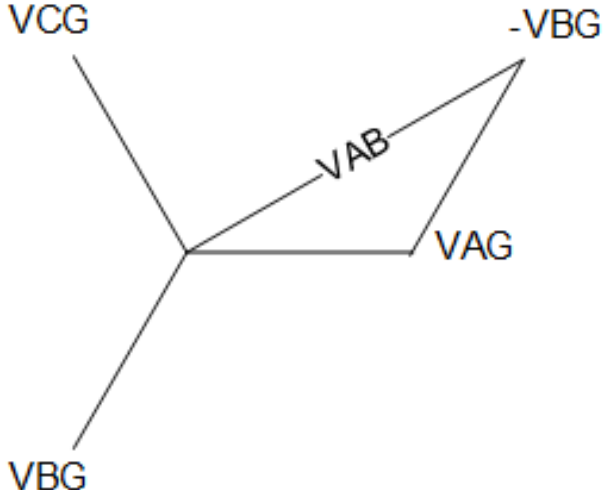For an ABC rotation, VAG lags VAB by 30 degrees





Is the reversed phase the only error here?

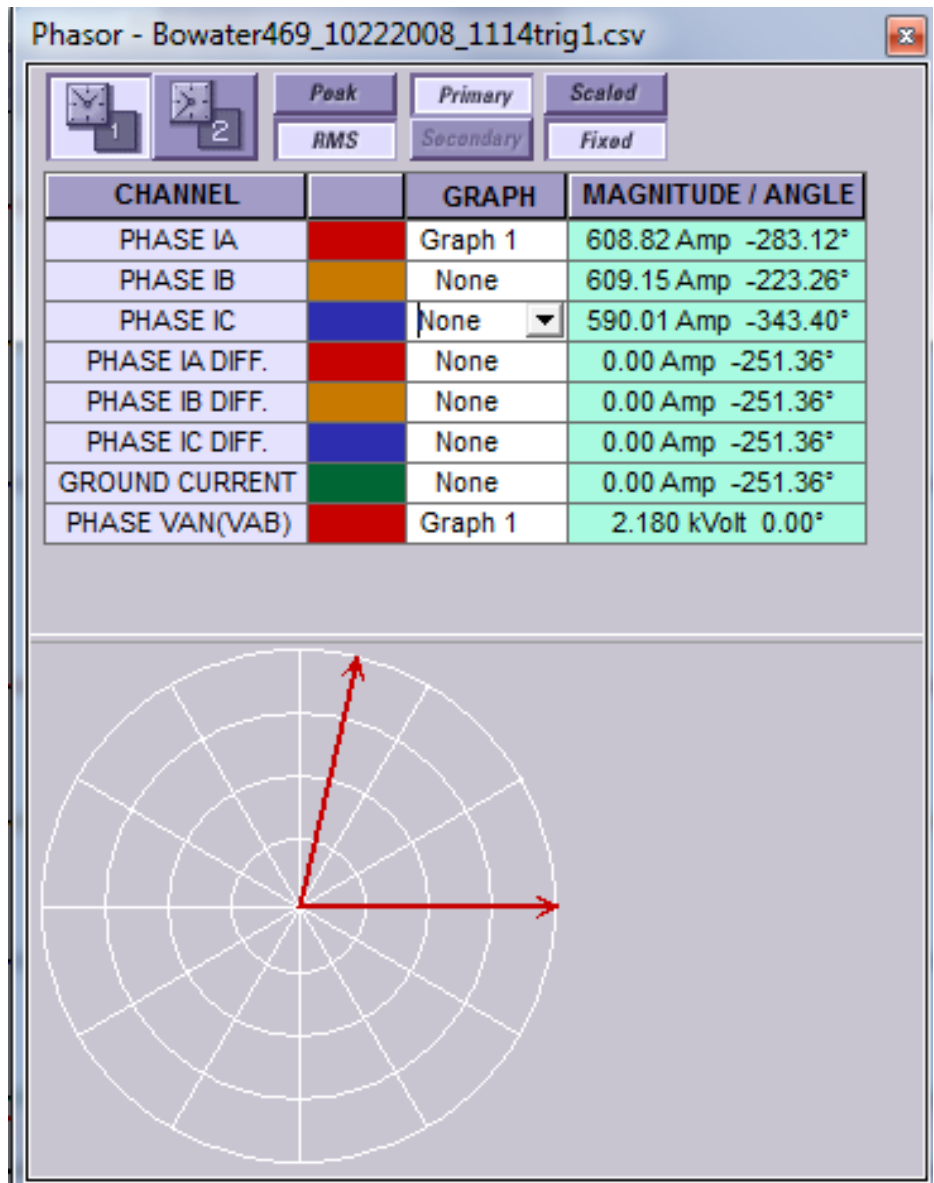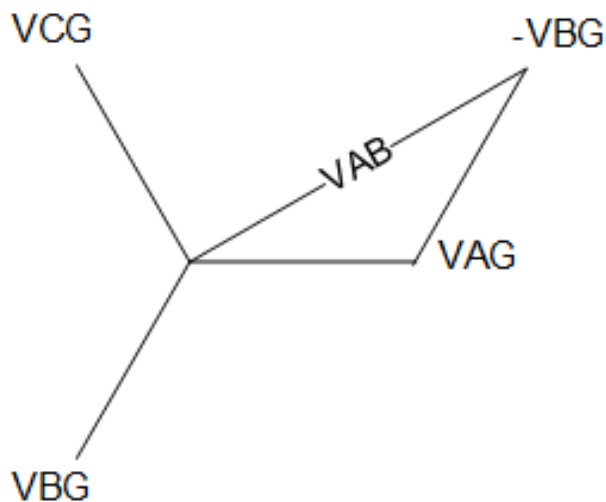For an ABC rotation, VAG lags VAB by 30 degrees




How to fix

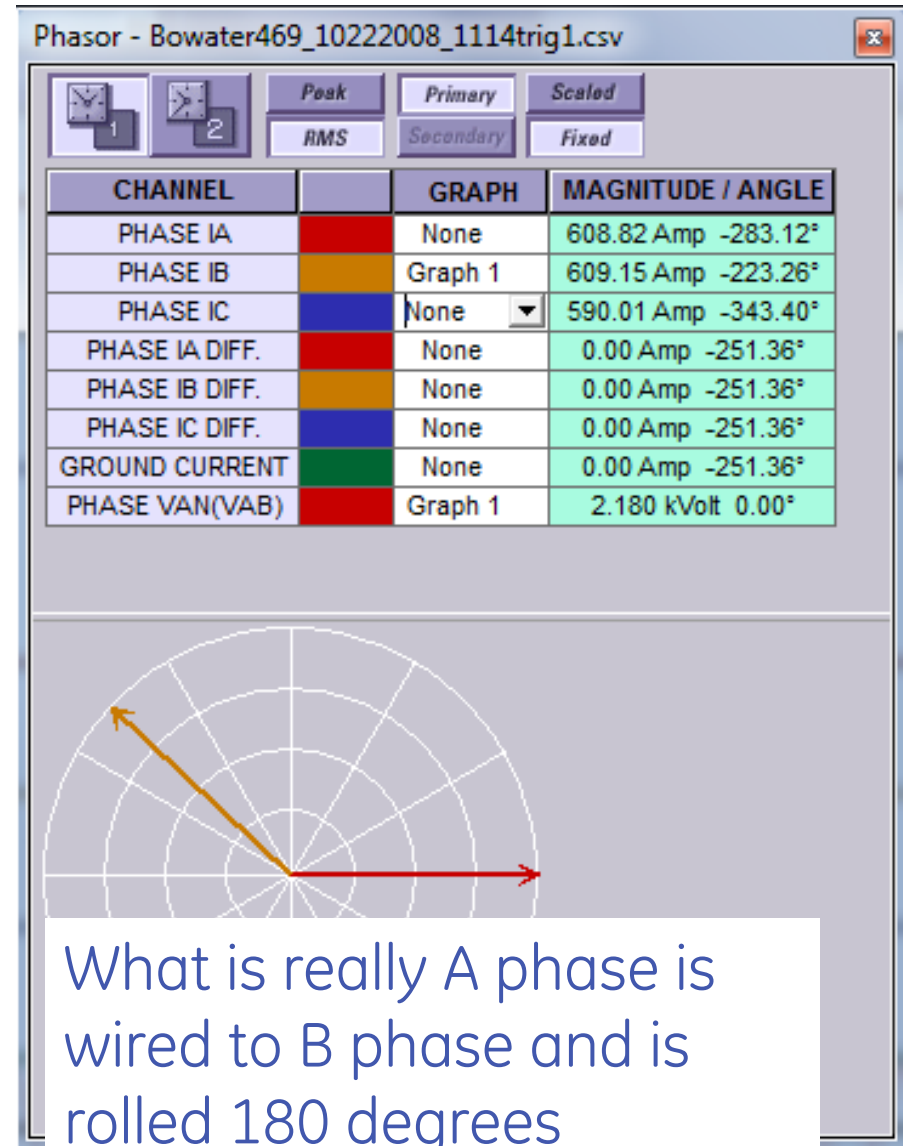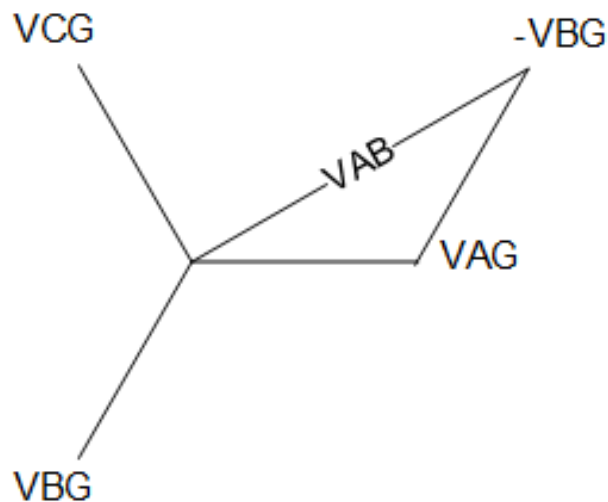For an ABC rotation, VAG lags VAB by 30 degrees



How to fix

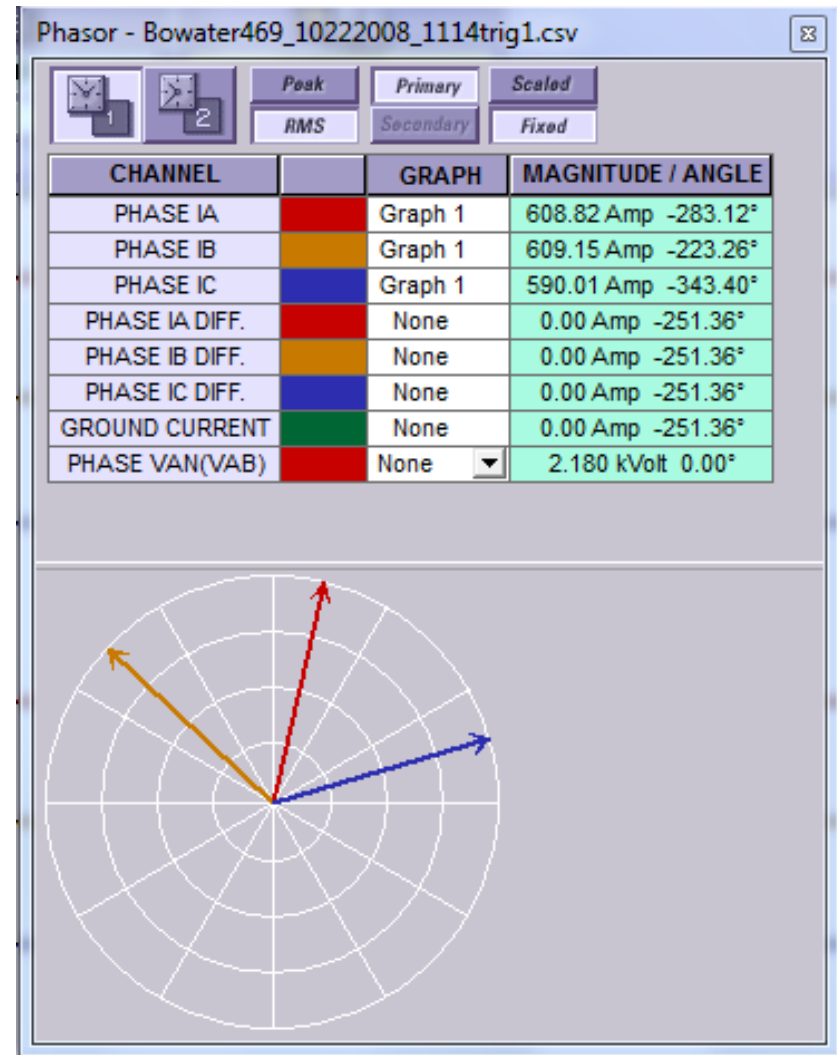- Move wire from B to A and roll 180 degrees
- Move wire from C to B and roll 180 degrees
- Move wire from A to C and don't roll.




Lessons Learned

- This relay had a rolled phase, but also a lot of other issues
- During start up, verify metered values
 - Negative sequence voltage and current should be small relative to positive sequence quantities
 - Power factor should be as expected 80-90% lagging for induction machines and loads.
 - Phase relationships should be as expected (across transformers)

Low Impedance Bus Differential Trip When the Second Breaker is Closed on the Bus

The Story

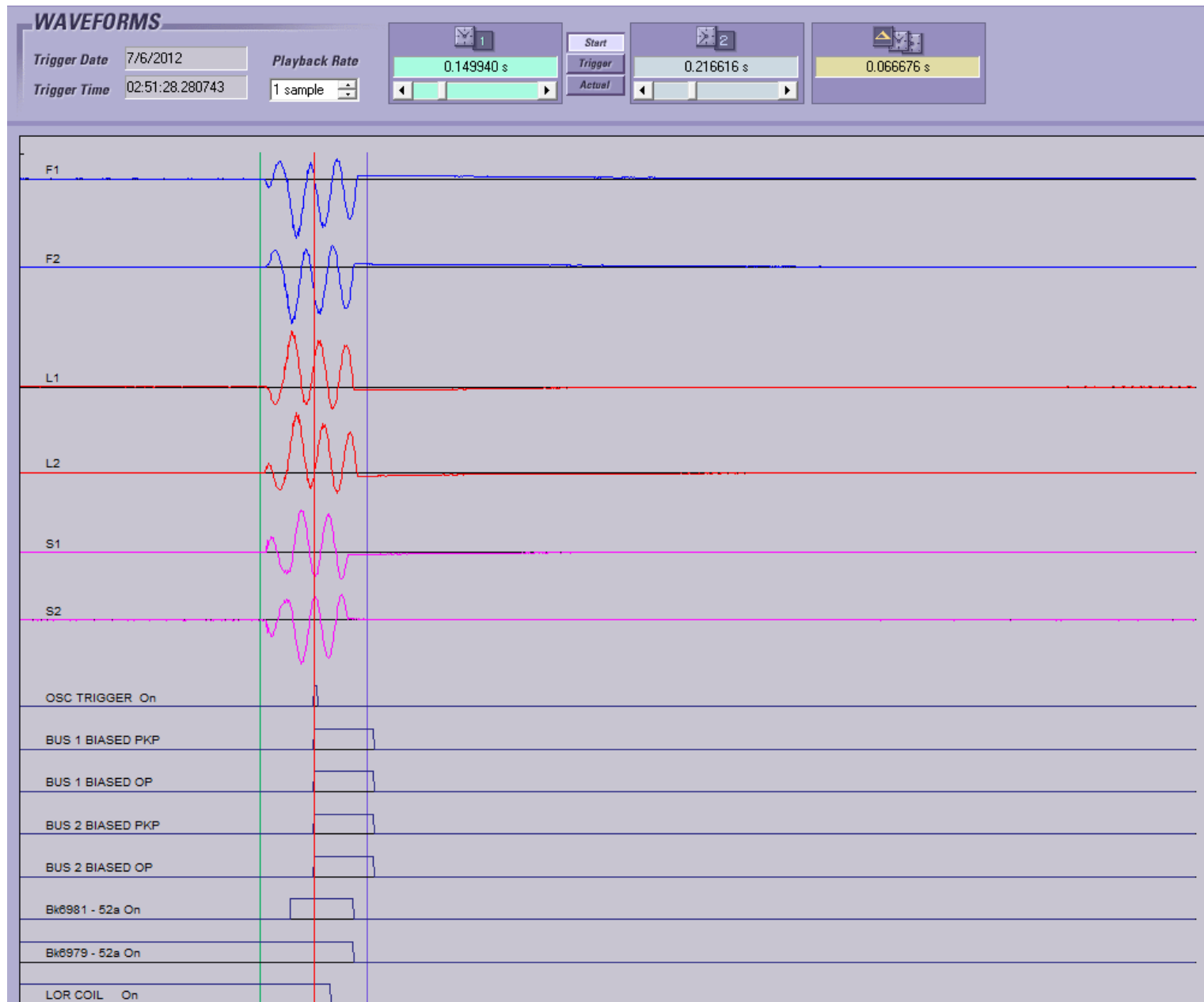
- We are installing a bus differential
- When we pick up load, we trip



87B Bus Differential Configuration



| Save Restore Default Reset VIEW ALL <i>mode</i> | | | |
|--|------------|------------|------------|
| PARAMETER | BUS ZONE 1 | BUS ZONE 2 | BUS ZONE 3 |
| Bus Zone CT A | F1 | L1 | S1 |
| Bus Zone Direction A | IN | IN | IN |
| Bus Zone Status A | ON | ON | ON |
| Bus Zone CT B | F2 | L2 | S2 |
| Bus Zone Direction B | IN | IN | IN |
| Bus Zone Status B | ON | ON | ON |
| Bus Zone CT C | F3 | L3 | S3 |
| Bus Zone Direction C | IN | IN | IN |
| Bus Zone Status C | ON | ON | ON |
| Bus Zone CT D | F4 | L4 | S4 |
| Bus Zone Direction D | IN | IN | IN |
| Bus Zone Status D | OFF | OFF | OFF |
| Bus Zone CT E | F5 | L5 | S5 |
| Bus Zone Direction E | IN | IN | IN |
| Bus Zone Status E | OFF | OFF | OFF |
| Bus Zone CT F | F6 | L6 | S6 |
| Bus Zone Direction F | IN | IN | IN |
| Bus Zone Status F | OFF | OFF | OFF |
| Bus Zone CT G | F7 | L7 | S7 |
| Bus Zone Direction G | IN | IN | IN |
| Bus Zone Status G | OFF | OFF | OFF |
| Bus Zone CT H | F8 | L8 | S8 |
| Bus Zone Direction H | IN | IN | IN |
| Bus Zone Status H | OFF | OFF | OFF |

Let's look at the phasors

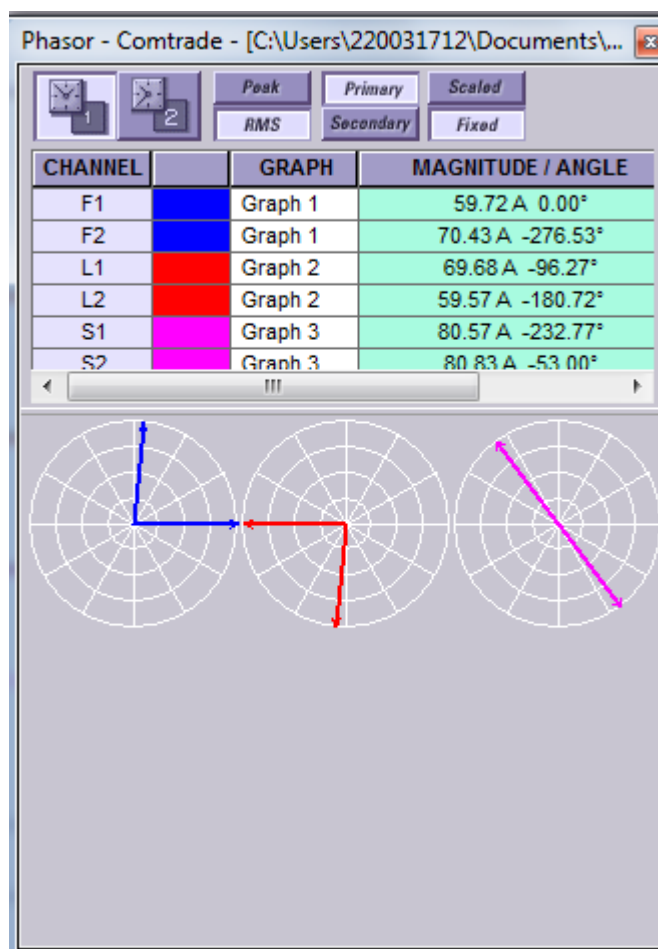

How do we fix this monstrosity?

Corrective action required

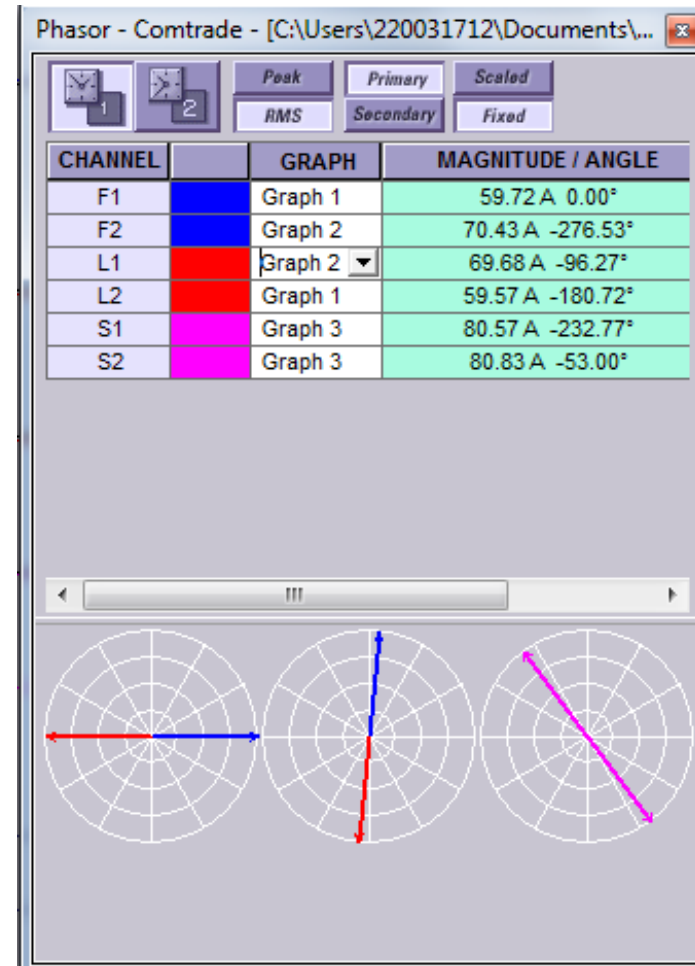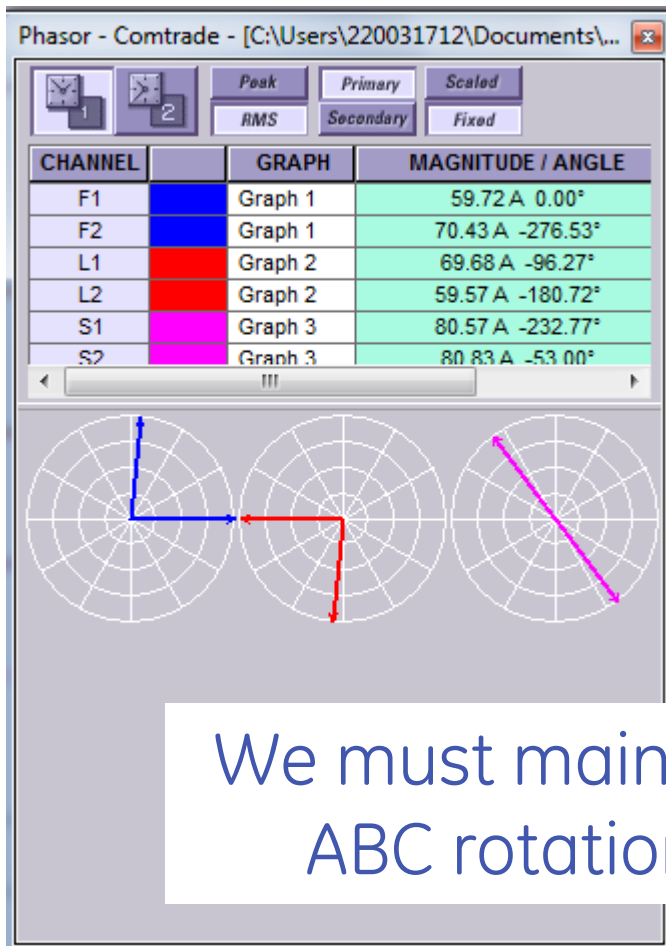

Paralleling Switchgear Trip



imagination at work

The Story

- This relay trips every time I close the breaker
- It is tripping on Overcurrent.
- You need to send me a new relay because this one is obviously bad.

Events

| Event | Date | Time | Cause of Event |
|-------|------------|--------------|-----------------------------------|
| 19 | 12/17/2009 | 15:53:35.475 | Trigger Data Logger |
| 18 | 12/17/2009 | 15:53:35.475 | Trigger Trace Memory |
| 17 | 12/17/2009 | 15:53:35.475 | Trip: Phase ABC - Phase Time OC 1 |
| 14 | 12/10/2009 | 17:53:30.495 | Trigger Data Logger |
| 13 | 12/10/2009 | 17:53:30.494 | Trigger Trace Memory |
| 12 | 12/10/2009 | 17:53:30.494 | Trip: Phase ABC - Phase Time OC 1 |

Select Events


17

| Event Parameter | Value |
|---------------------------------|-----------------------------------|
| Date of Event | 12/17/2009 |
| Time of Event | 15:53:35.475 |
| Cause of Event | Trip: Phase ABC - Phase Time OC 1 |
| Phase A Current Magnitude(A) | 2470 Amp |
| Phase A Current Angle(Lag) | 209 ° Lag |
| Phase B Current Magnitude(A) | 2520 Amp |
| Phase B Current Angle(Lag) | 330 ° Lag |
| Phase C Current Magnitude(A) | 2456 Amp |
| Phase C Current Angle(Lag) | 91 ° Lag |
| Ground Current Magnitude(A) | 0 Amp |
| Ground Current Angle(Lag) | 0 ° Lag |
| A-N (A-B) Voltage Magnitude(kV) | 6.98 kV |
| A-N (A-B) Voltage Angle(Lag) | 0 ° Lag |
| B-N (B-C) Voltage Magnitude(kV) | 7.02 kV |
| B-N (B-C) Voltage Angle(Lag) | 120 ° Lag |



imagination at work

Waveforms

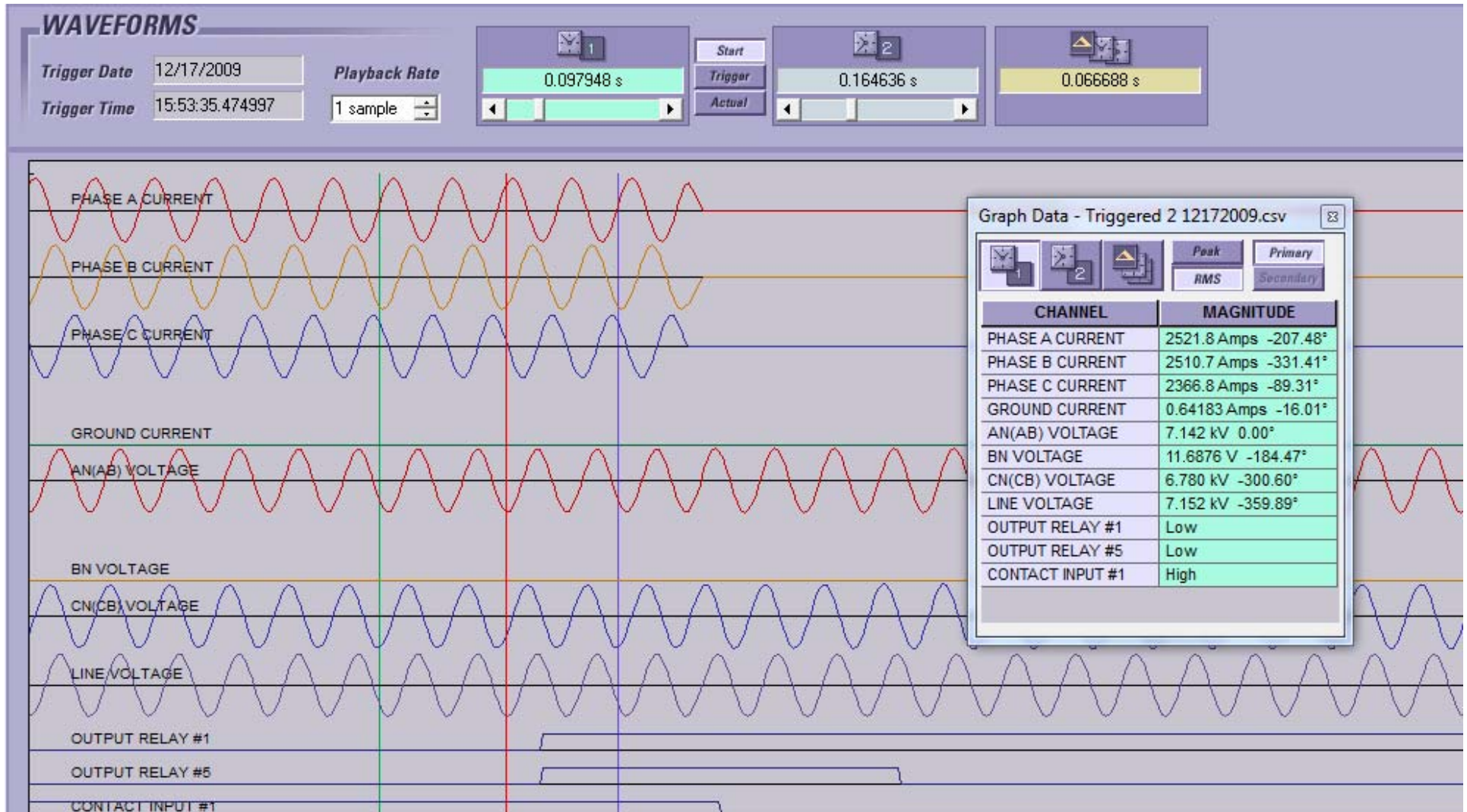


How Microprocessor Relays Fail


- Power Supplies – Failures there most likely mean the relay is dead with no lights.
- Processor failures – Failures there cause an alarm which takes the relay out of service and illuminates an alarm LED.
- DSP failures – Failures there are rare, would typically raise an alarm and would show distorted metering values.
- Safe to say, this relay has NO problems, it is doing what it is suppose to do.

Where is this relay and when is it tripping?


So what are you actually paralleling?

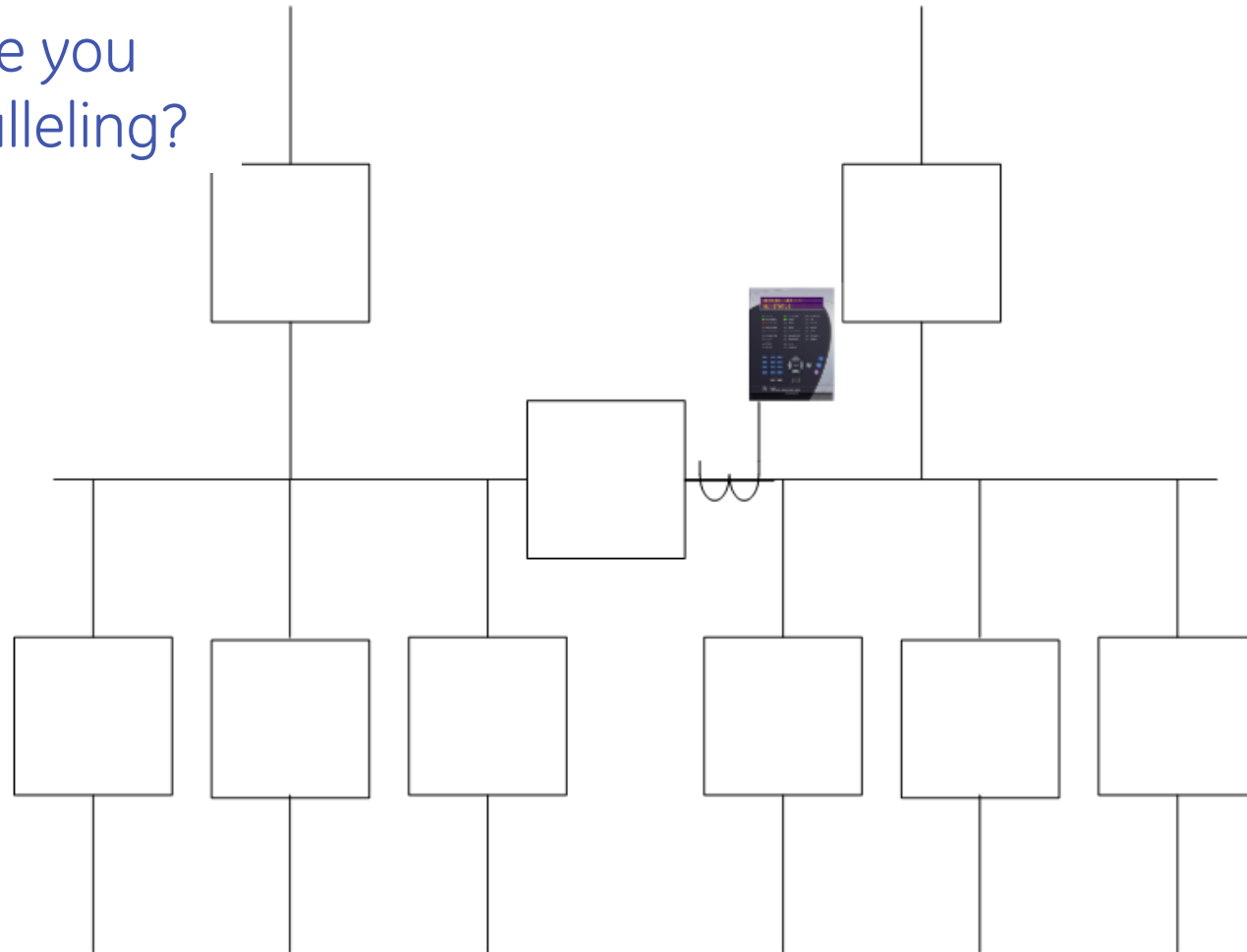

So what are you actually paralleling?

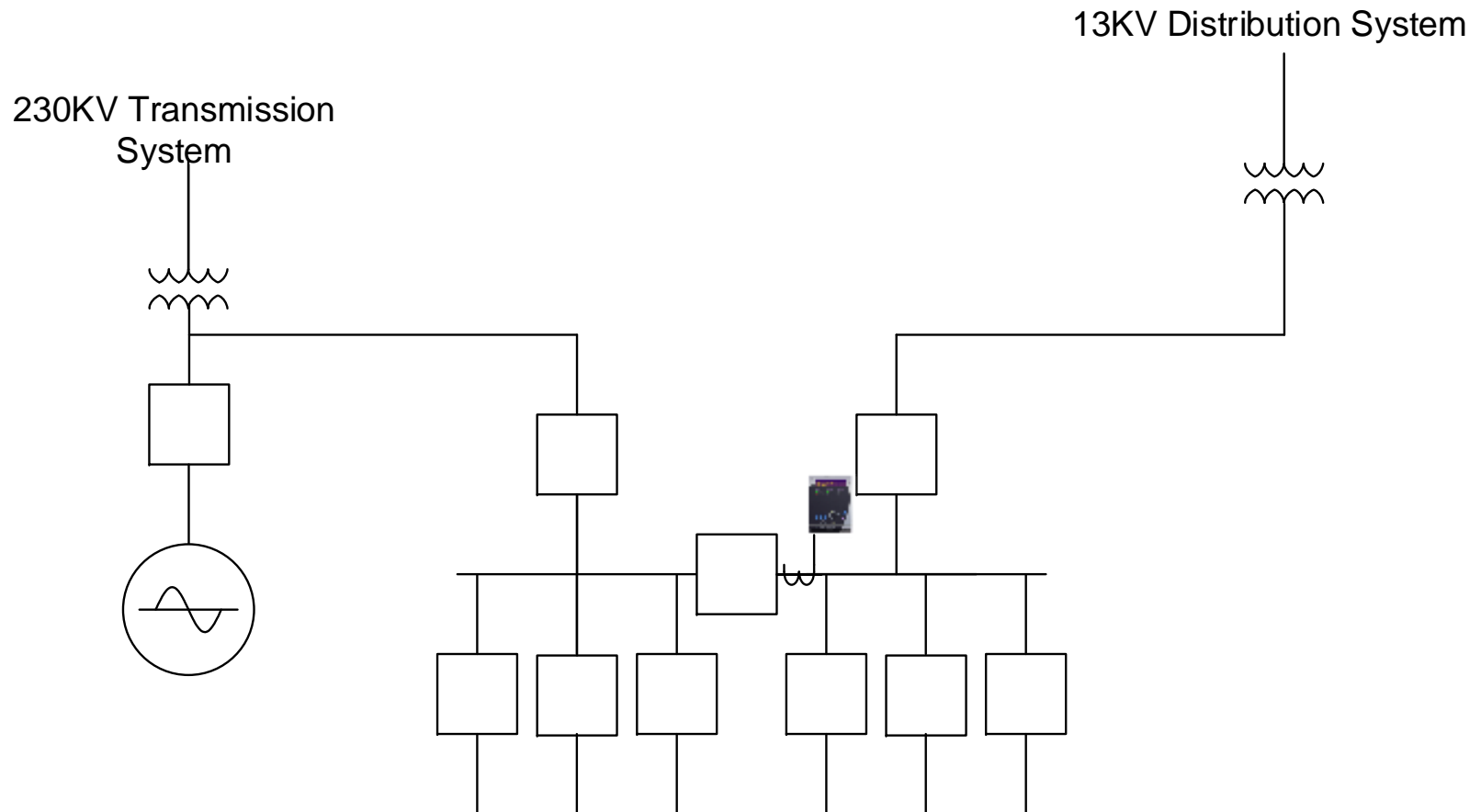

Equivalent Circuit

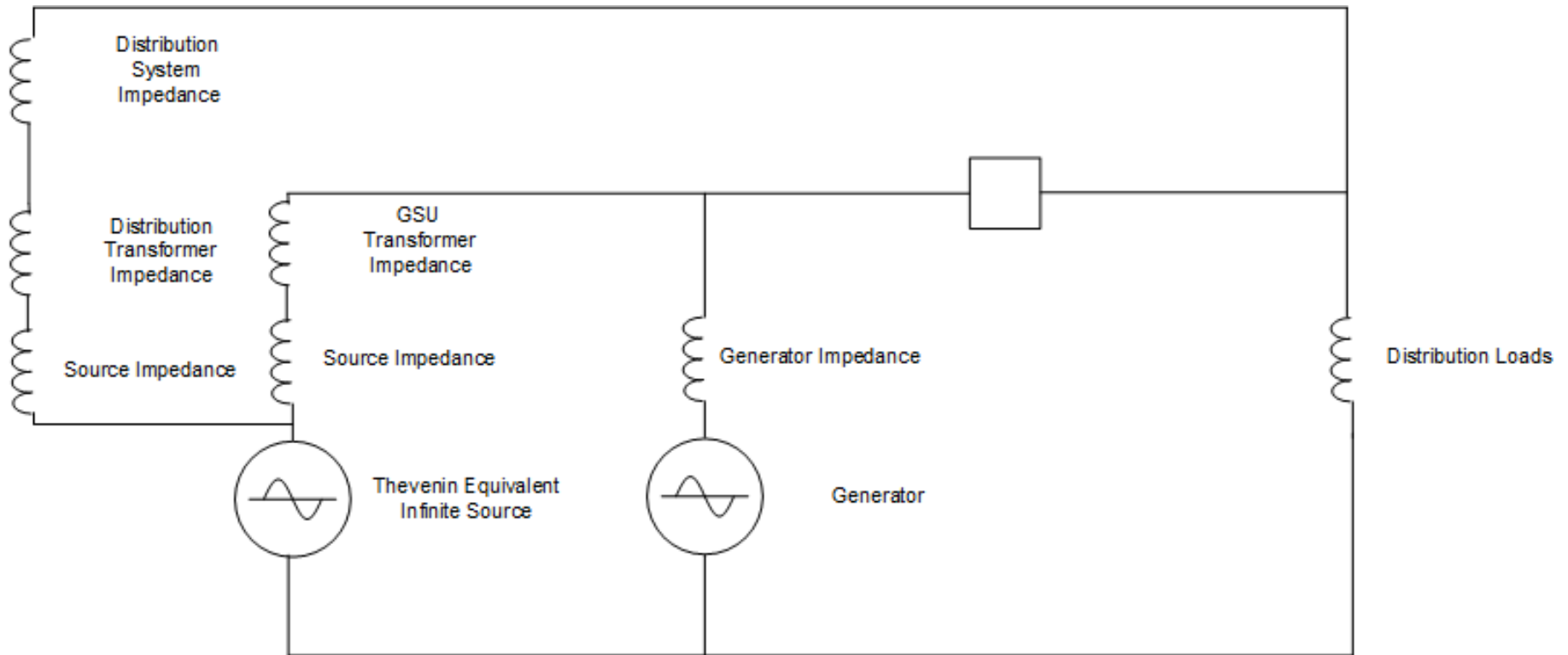

Since Parallel:

$$Z_{dist} I_{dist} = Z_{tran} I_{tran}$$

$$Z_{dist} / Z_{tran} = I_{tran} / I_{dist}$$

If $Z_{dist} \gg Z_{tran}$

Then $I_{tran} \gg I_{dist}$

Possible Solutions


- Can't really raise the TOC pickup setting on the tie breaker 750 and can't really make the time delay longer
- Could add controls to trip a selected breaker after all three are closed.
- Never parallel these two sources. Add mechanical interlocks to prevent parallel of all three sources.

Synchronous Motor Trip on Power Factor


The Story

- Synchronous motor is tripping on power factor pull-out
- Four of these compressors at the facility and is only happening to this compressor
- Started happening after we had the motor rebuilt.

Synchronous Motor Theory

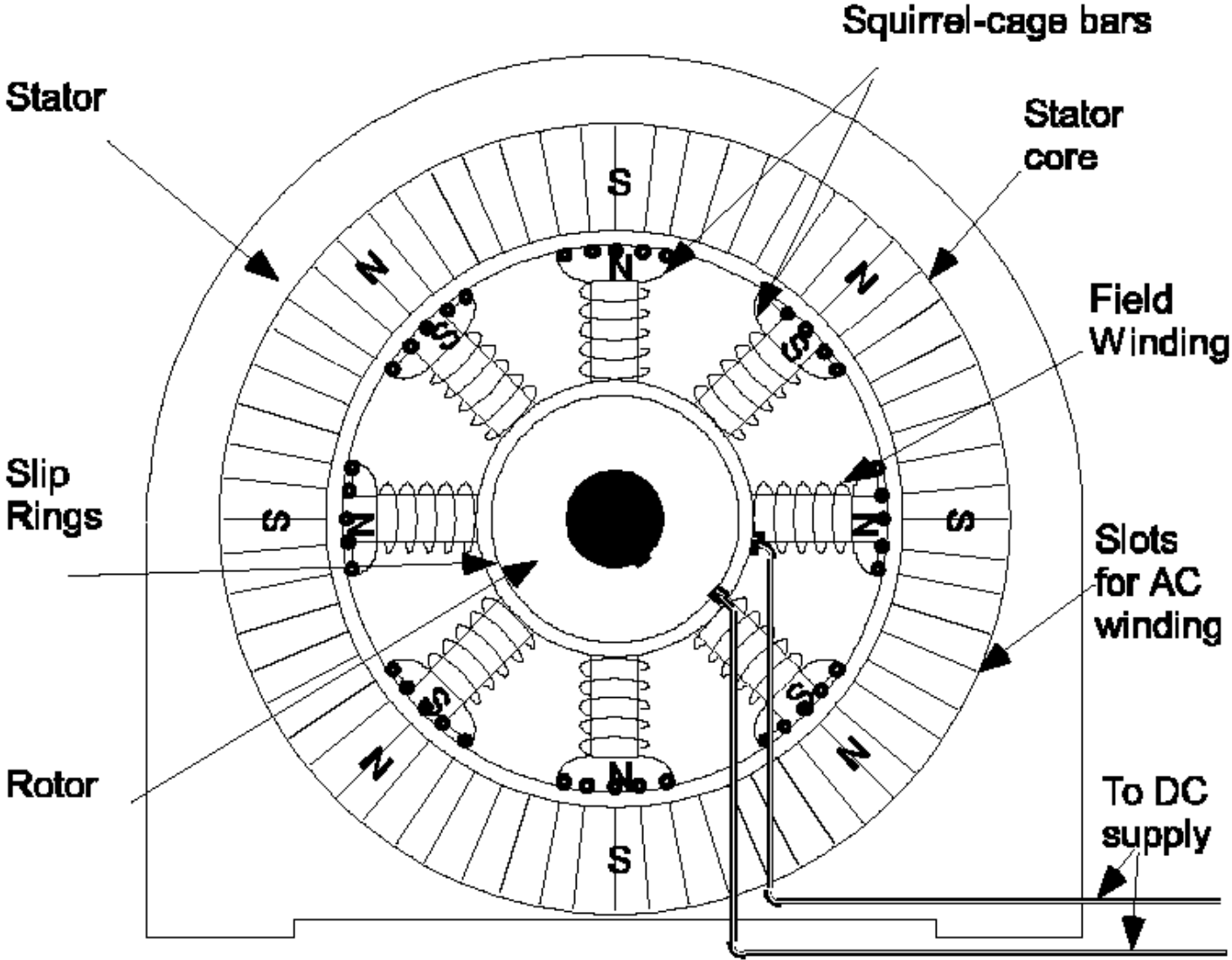


Machine Excitation

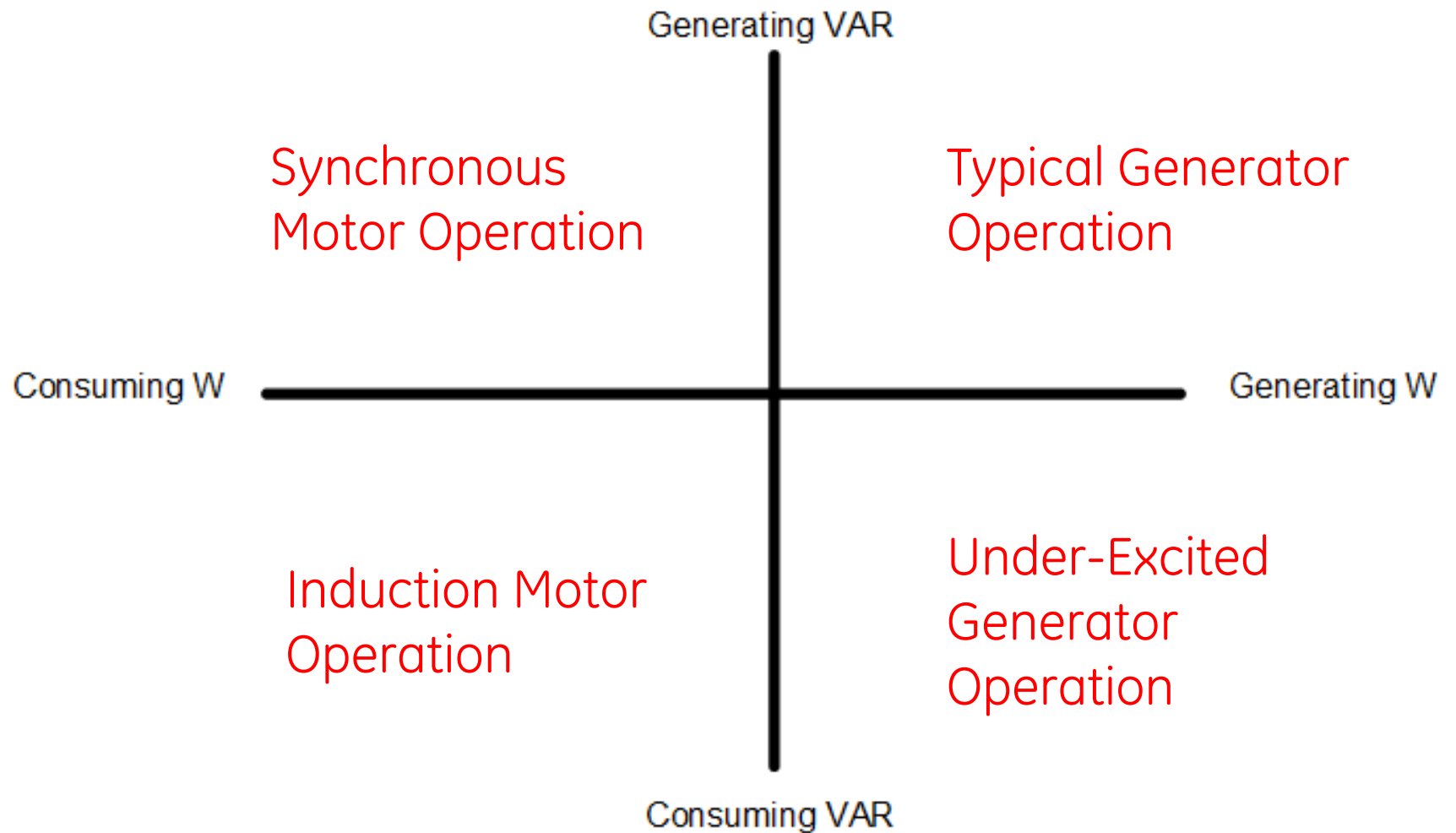


Synchronous Machines

- In an induction motor, the more load you have, the larger your slip.
- In a synchronous motor, $\text{slip}=0$. The more load you have (without increasing excitation) the greater your (negative) power factor.
- To prevent slipping a pole (pull-out protection) you use power factor protection to trip when your load changes beyond what your exciter can keep up with.


Reciprocal Compressors

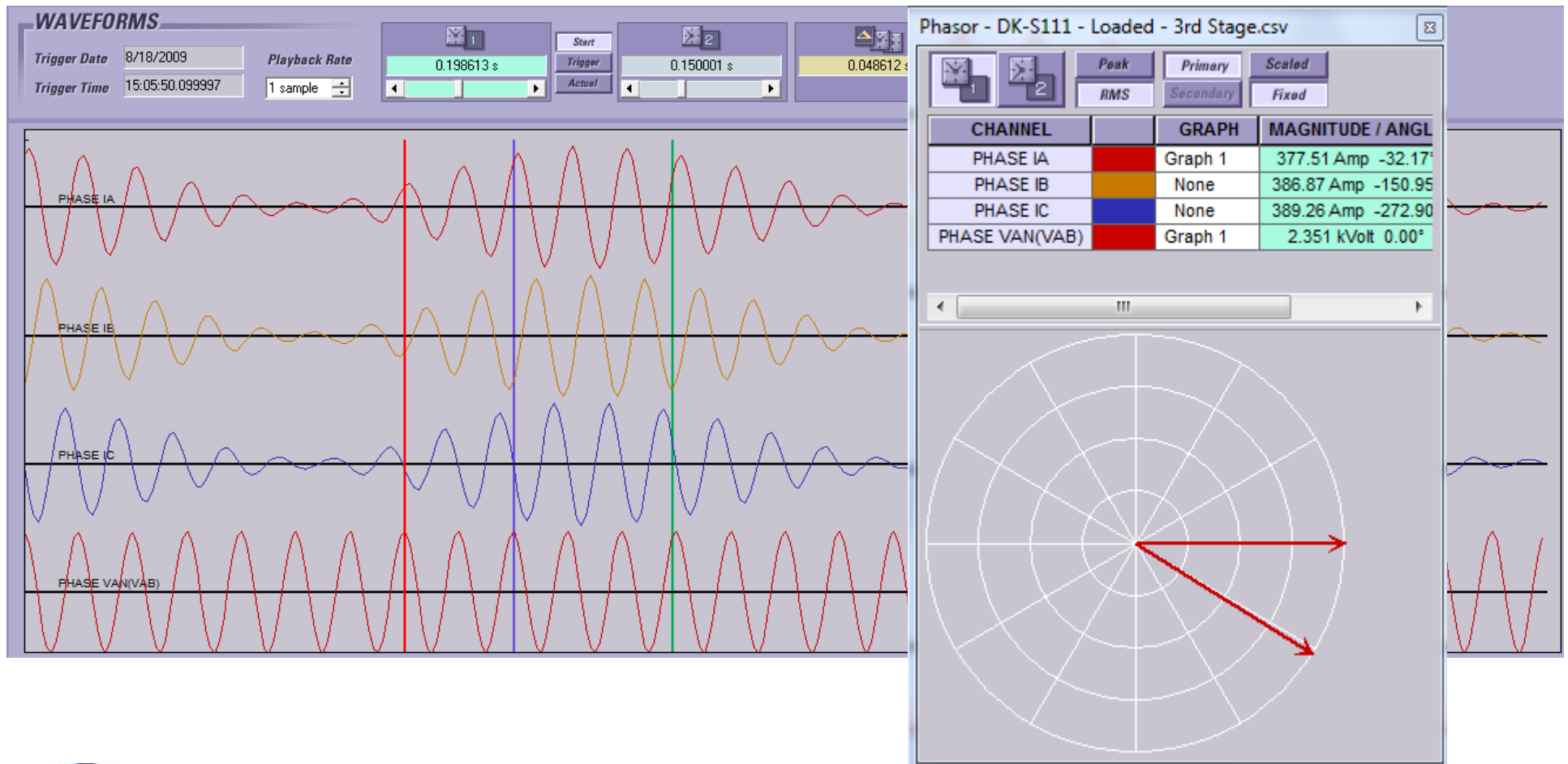


Reciprocal Compressors

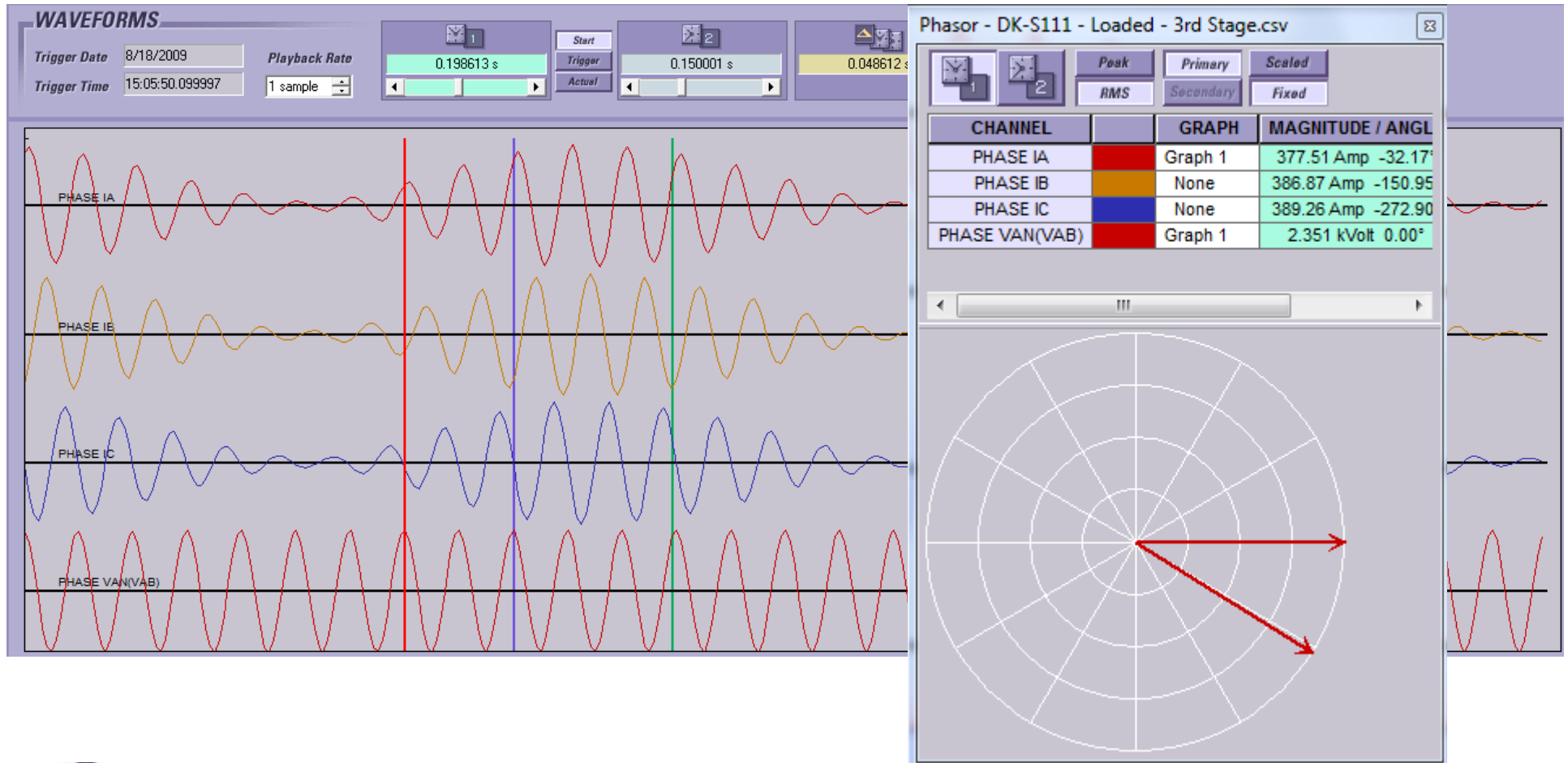

The Problem Compressor – Loaded Cycle

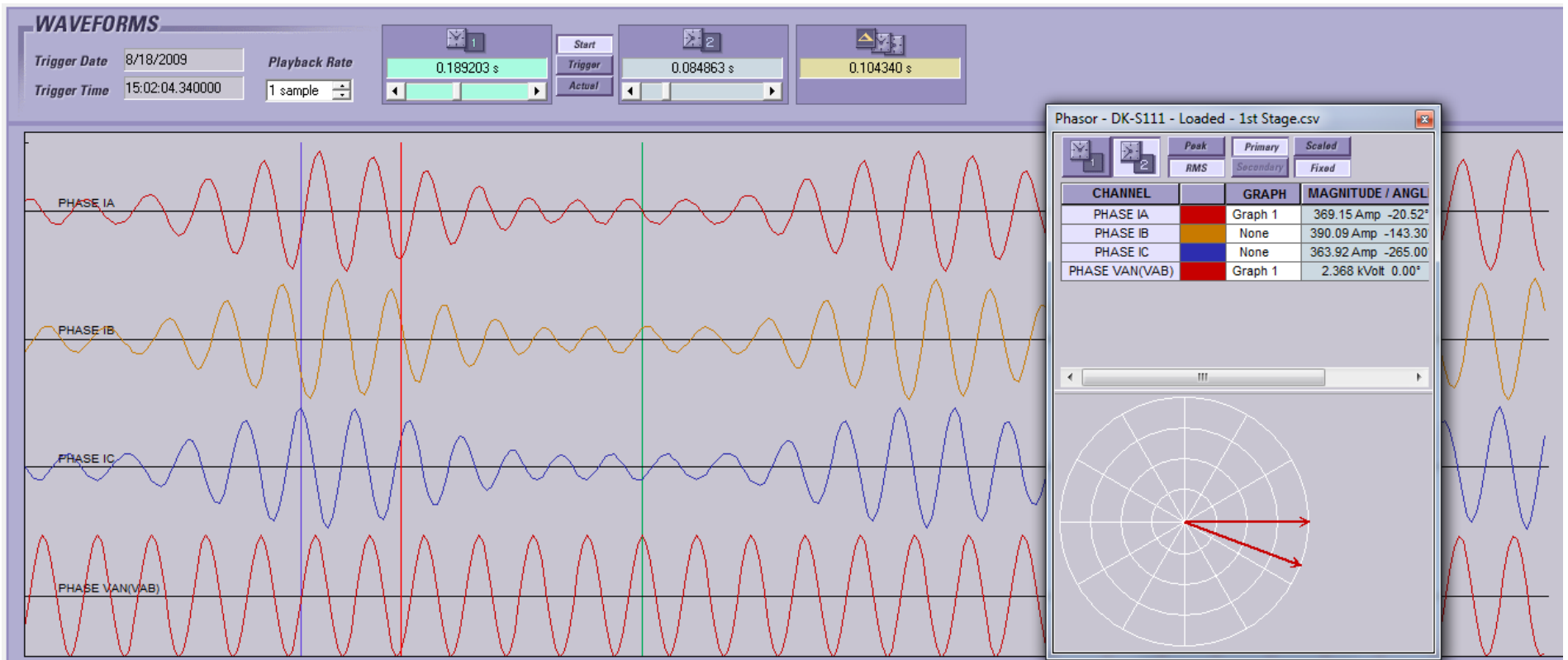

The Problem Compressor – Un-Loaded Cycle

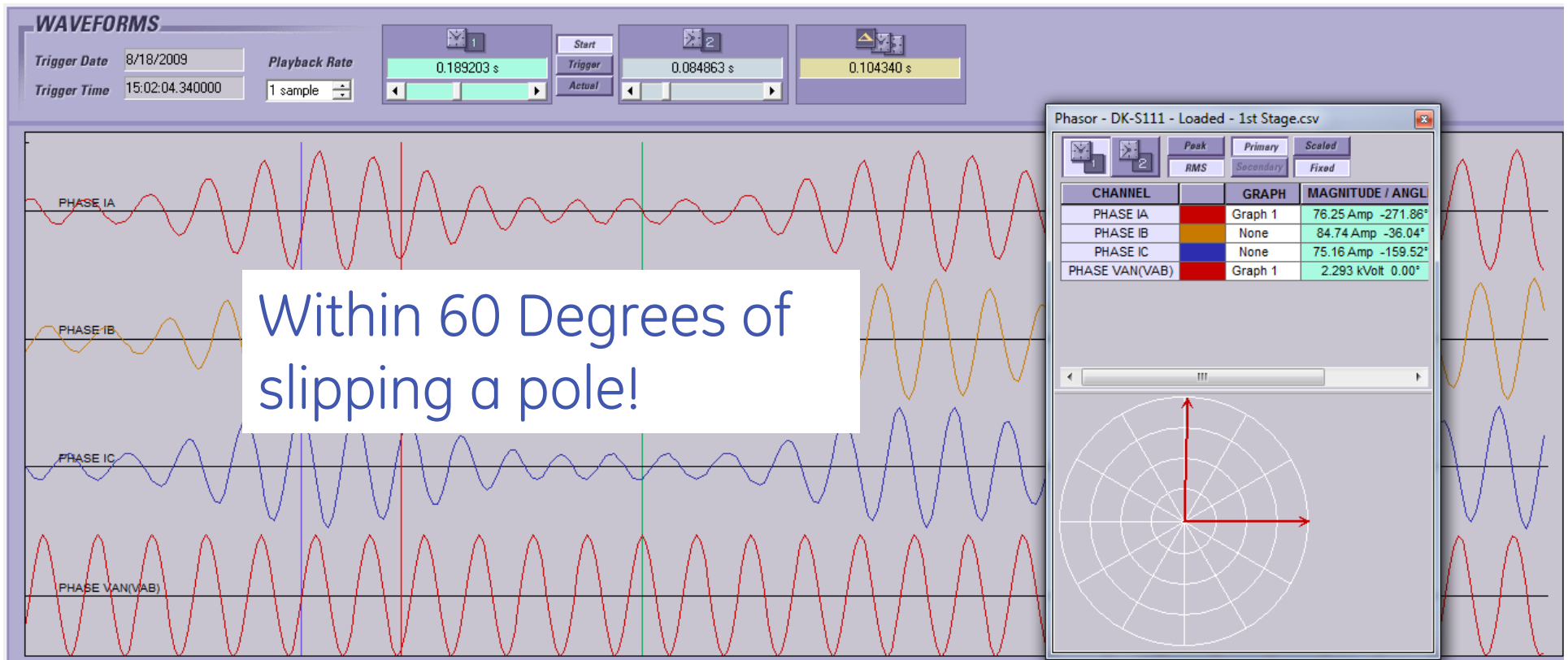

Problem

- This cannot be fixed with relay settings.
- Must talk to motor manufacture about why this compressor behaves this way.
- A mechanical problem was causing the issue.

Substation heat pumps drops
bus voltage by 1kV causes
capacitor bank trip




imagination at work


The Story

- This relay is tripping on B phase voltage differential.
- Two relays in the station and they are both tripping on B phase voltage differential.
- The redundant relays are not tripping.


Six Capacitor Banks – 2 Relays

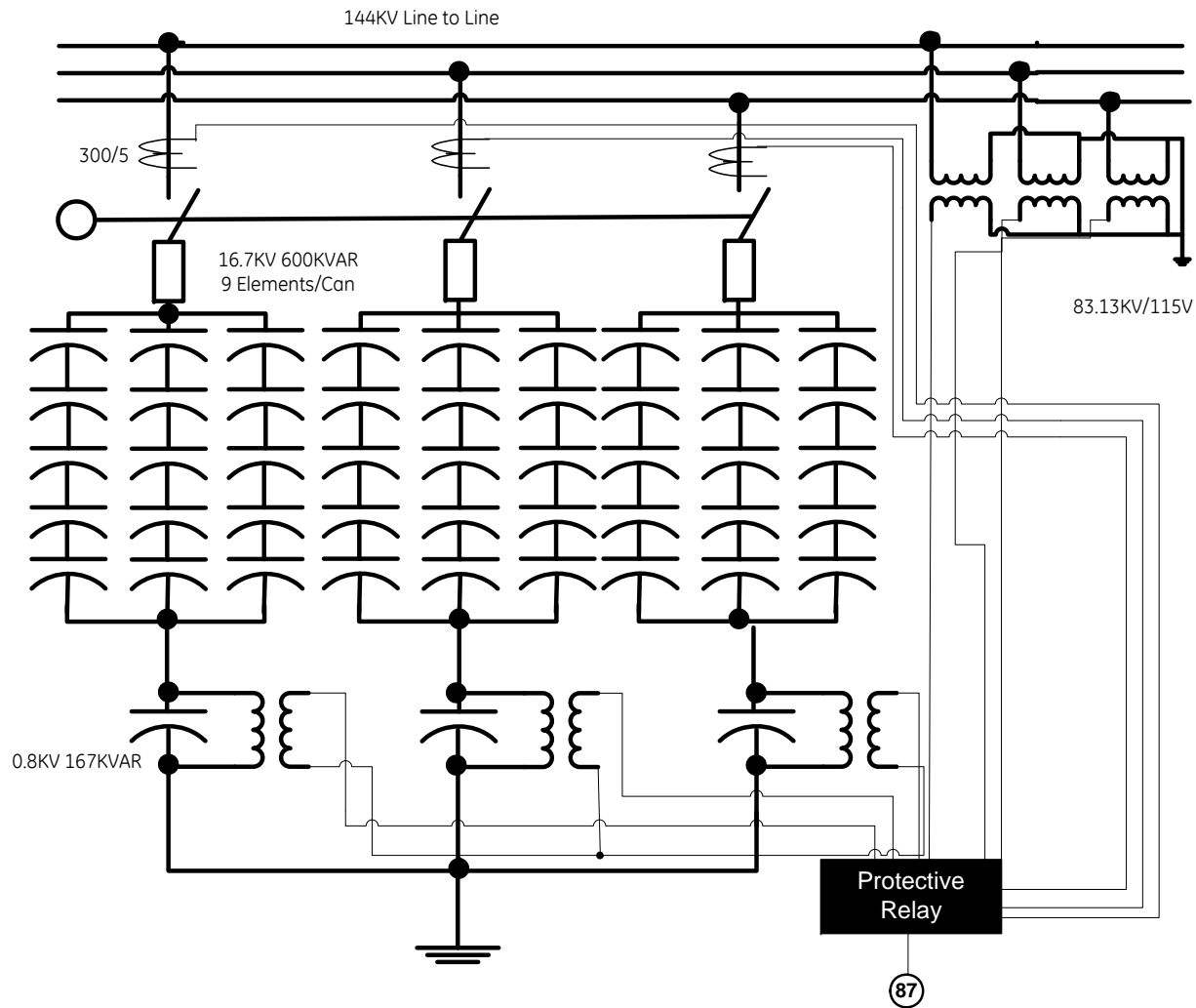


Pre-Fault Values of the Trip

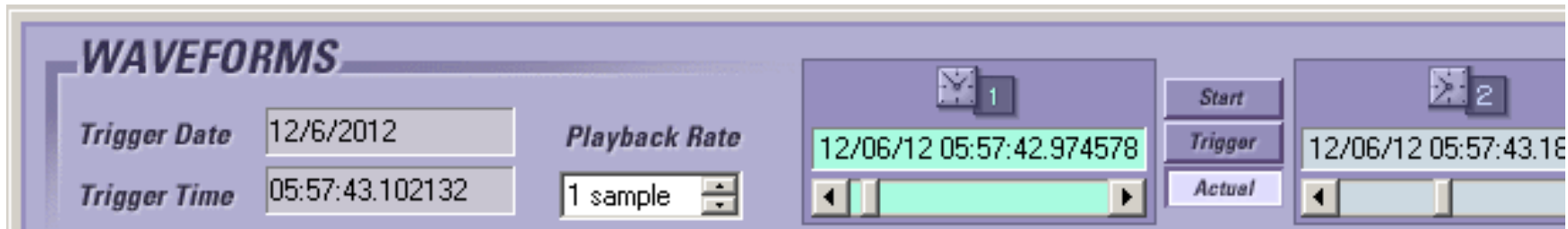
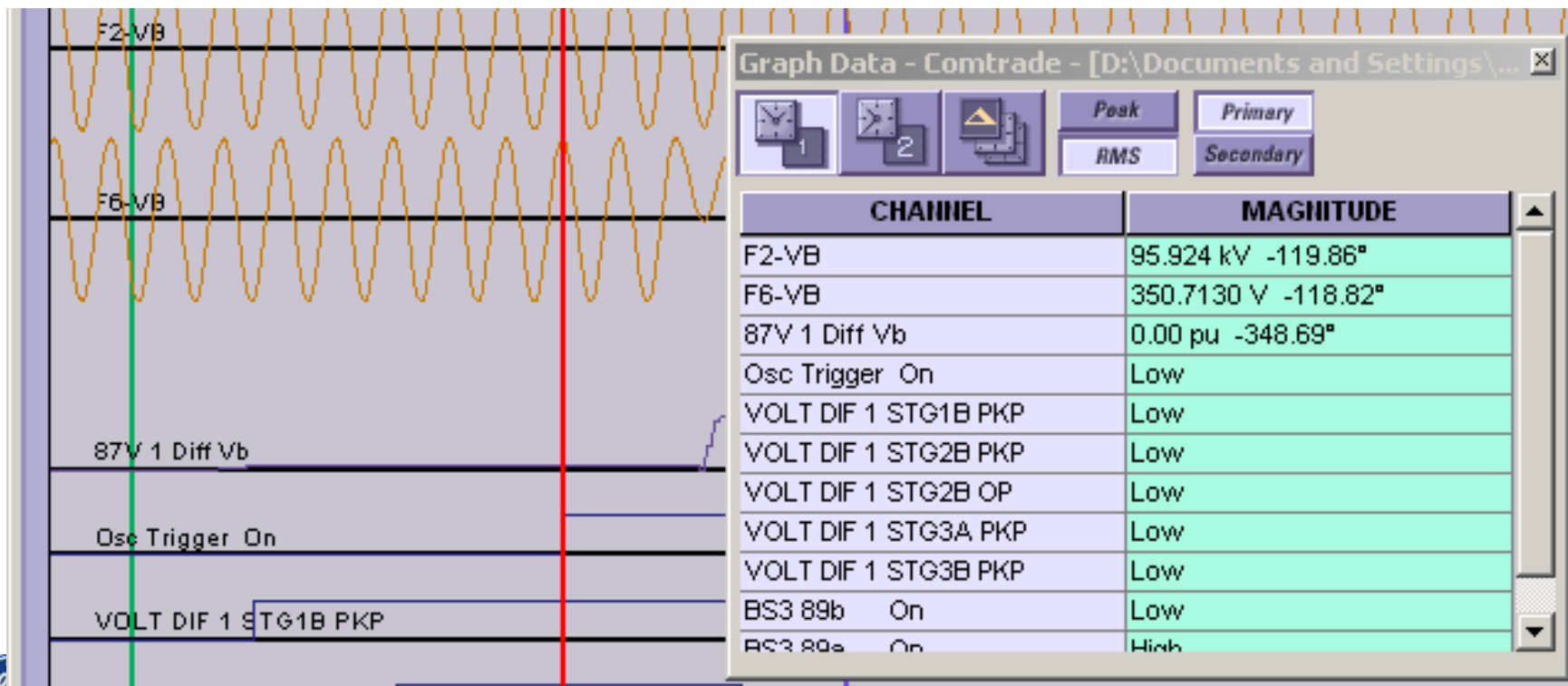
$$95,924 - 274(350.7130) = 171 = 0.002 \text{ pu}$$




Fault Values of the Trip

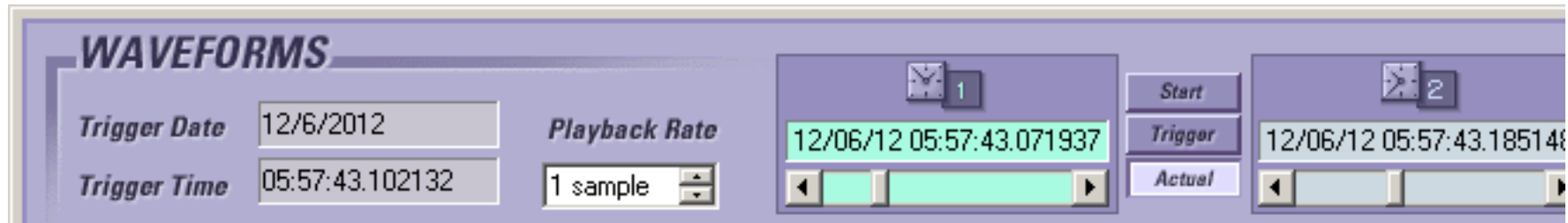

$$94047 - 274(350.6185) = 2022 = 0.022$$



Trip is set to 0.02 with a 50ms Delay

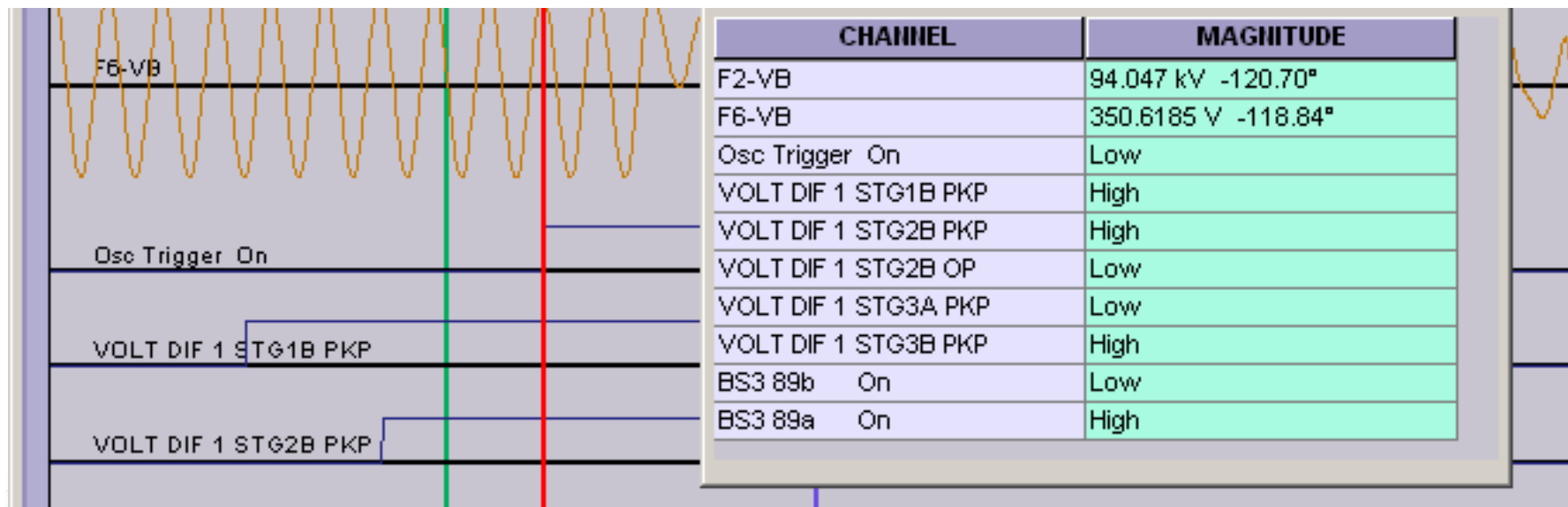

Event Records

| Event Number | Date/Time | Cause | Data |
|--------------|------------------------------------|-----------------------------|------|
| 14869 | Dec 06 2012 09:39:10.059863 | VOLT DIF 1 STG1B PKP | |
| 14868 | Dec 06 2012 09:39:10.057780 | VOLT DIF 1 STG3B PKP | |
| 14867 | Dec 06 2012 09:34:42.158641 | VOLT DIF 1 DPO | |
| 14866 | Dec 06 2012 09:34:41.939957 | VOLT DIF 1 STG1B PKP | |
| 14865 | Dec 06 2012 09:34:41.937874 | VOLT DIF 1 STG3B PKP | |
| 14864 | Dec 06 2012 09:09:40.170983 | VOLT DIF 1 DPO | |
| 14863 | Dec 06 2012 09:09:39.941888 | VOLT DIF 1 STG1B PKP | |
| 14862 | Dec 06 2012 09:09:39.937723 | VOLT DIF 1 STG3B PKP | |
| 14861 | Dec 06 2012 09:04:47.548600 | VOLT DIF 1 DPO | |
| 14860 | Dec 06 2012 09:04:47.340254 | VOLT DIF 1 STG1B PKP | |
| 14859 | Dec 06 2012 09:04:47.334000 | VOLT DIF 1 STG3B PKP | |
| 14858 | Dec 06 2012 08:30:45.022783 | VOLT DIF 1 DPO | |
| 14857 | Dec 06 2012 08:30:44.824911 | VOLT DIF 1 STG1B PKP | |
| 14856 | Dec 06 2012 08:30:44.818661 | VOLT DIF 1 STG3B PKP | |
| 14855 | Dec 06 2012 08:25:36.661146 | VOLT DIF 1 DPO | |
| 14854 | Dec 06 2012 08:25:36.409093 | VOLT DIF 1 STG1B PKP | |
| 14853 | Dec 06 2012 08:25:36.402841 | VOLT DIF 1 STG3B PKP | |
| 14852 | Dec 06 2012 08:10:57.612625 | VOLT DIF 1 DPO | |
| 14851 | Dec 06 2012 08:10:57.441826 | VOLT DIF 1 STG1B PKP | |
| 14850 | Dec 06 2012 08:10:57.435578 | VOLT DIF 1 STG3B PKP | |
| 14849 | Dec 06 2012 08:07:05.098656 | VOLT DIF 1 DPO | |
| 14848 | Dec 06 2012 08:07:04.861241 | VOLT DIF 1 STG1B PKP | |
| 14847 | Dec 06 2012 08:07:04.854994 | VOLT DIF 1 STG3B PKP | |
| 14846 | Dec 06 2012 07:46:07.766480 | VOLT DIF 1 DPO | |
| 14845 | Dec 06 2012 07:46:07.581104 | VOLT DIF 1 STG1B PKP | |
| 14844 | Dec 06 2012 07:46:07.574854 | VOLT DIF 1 STG3B PKP | |
| 14843 | Dec 06 2012 06:36:56.390804 | VOLT DIF 1 DPO | |
| 14842 | Dec 06 2012 06:36:56.147116 | VOLT DIF 1 STG1B PKP | |
| 14841 | Dec 06 2012 06:36:56.140867 | VOLT DIF 1 STG3B PKP | |
| 14840 | Dec 06 2012 06:30:17.260222 | VOLT DIF 1 DPO | |
| 14839 | Dec 06 2012 06:30:17.064404 | VOLT DIF 1 STG1B PKP | |
| 14838 | Dec 06 2012 06:30:17.058150 | VOLT DIF 1 STG3B PKP | |




Event Records

| | | | |
|-------|-----------------------------|----------------------|--|
| 14846 | Dec 06 2012 07:46:07.766480 | VOLT DIF 1 DPO | |
| 14845 | Dec 06 2012 07:46:07.581104 | VOLT DIF 1 STG1B PKP | |
| 14844 | Dec 06 2012 07:46:07.574854 | VOLT DIF 1 STG3B PKP | |
| 14843 | Dec 06 2012 06:36:56.390804 | VOLT DIF 1 DPO | |
| 14842 | Dec 06 2012 06:36:56.147116 | VOLT DIF 1 STG1B PKP | |
| 14841 | Dec 06 2012 06:36:56.140867 | VOLT DIF 1 STG3B PKP | |
| 14840 | Dec 06 2012 06:30:17.260222 | VOLT DIF 1 DPO | |
| 14839 | Dec 06 2012 06:30:17.064404 | VOLT DIF 1 STG1B PKP | |
| 14838 | Dec 06 2012 06:30:17.058150 | VOLT DIF 1 STG3B PKP | |

| | | | |
|-----|-----------------------------|----------------------|--|
| 407 | Dec 06 2012 07:46:07.766474 | VOLT DIF 1 DPO | |
| 406 | Dec 06 2012 07:46:07.581100 | VOLT DIF 1 STG1B PKP | |
| 405 | Dec 06 2012 07:46:07.579020 | VOLT DIF 1 STG3B PKP | |
| 404 | Dec 06 2012 06:36:56.386634 | VOLT DIF 1 DPO | |
| 403 | Dec 06 2012 06:36:56.149212 | VOLT DIF 1 STG1B PKP | |
| 402 | Dec 06 2012 06:36:56.142947 | VOLT DIF 1 STG3B PKP | |
| 401 | Dec 06 2012 06:30:17.253968 | VOLT DIF 1 DPO | |
| 400 | Dec 06 2012 06:30:17.070645 | VOLT DIF 1 STG1B PKP | |
| 399 | Dec 06 2012 06:30:17.064396 | VOLT DIF 1 STG3B PKP | |

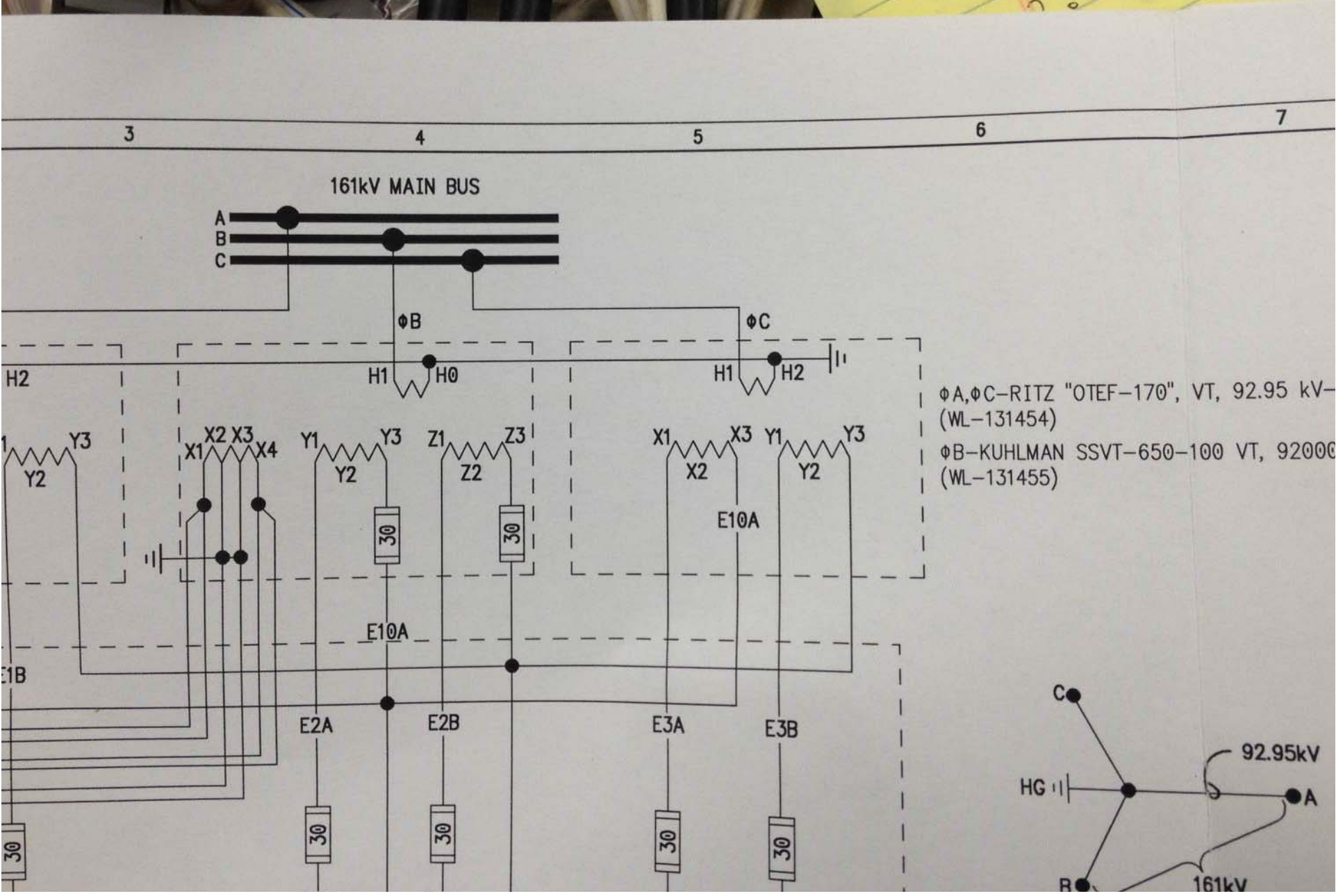One of these things isn't like the others!





WAVEFORMS


Trigger Date 12/11/2012
Trigger Time 10:32:22.000000

1
12/11/12 10:33:35.499832

Start
Trigger
Actual

2
12/11/12 10:33:35.893577

0.393745 s

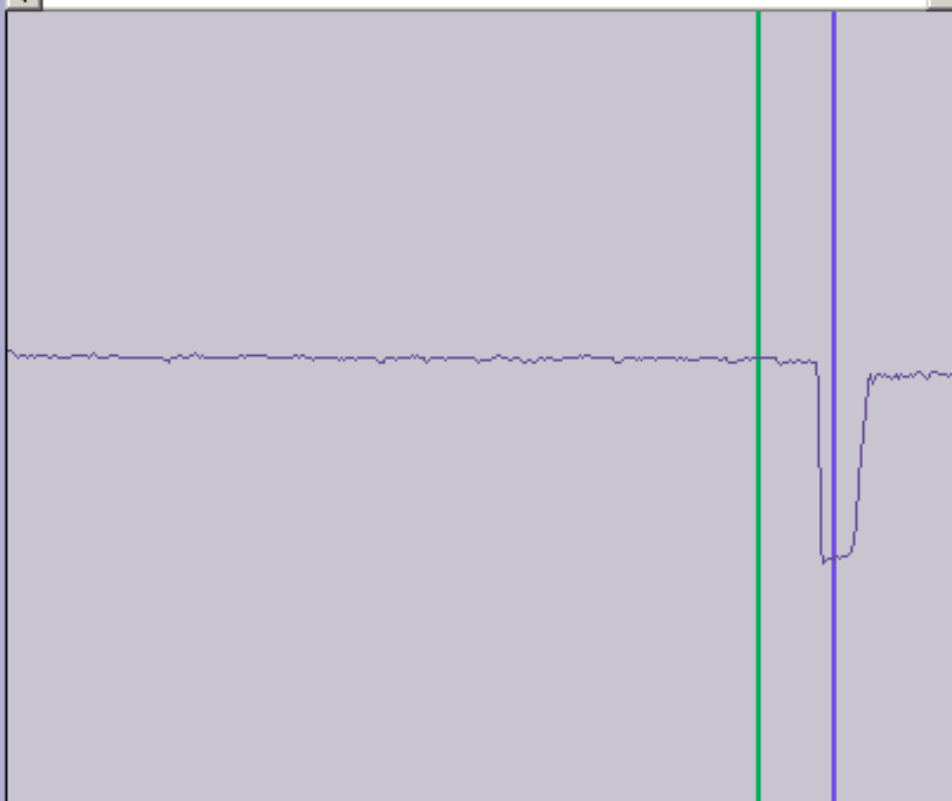

Graph Data - Comtrade - [D:\Documents and Settings\All Users\Doc

| CHANNEL | MAGNITUDE |
|--------------|-----------|
| 1004 Vbg RMS | 91.721 kV |

| | | | | | | | |
|-----------------------|------------|---------|----|---|-----|-----|-------|
| () W48H1-A00 | WMCB-08A | 230/208 | 60 | 1 | 58 | 60 | N/A |
| () W48H1-A02 | EHWH04-A04 | 230/208 | 60 | 1 | 63 | 70 | 37/26 |
| () W48H1-A04 | EHWH42-A05 | 230/208 | 60 | 1 | 89 | 90 | 37/51 |
| () W48H1-A05 | EHWH42-A10 | 230/208 | 60 | 1 | 89 | 90 | 37/51 |
| (X) W48H1-A10BPXXXE | EHWH42-A15 | 230/208 | 60 | 1 | 111 | 125 | 59/51 |
| () W48H1-A15 | EHWH04-A20 | 230/208 | 60 | 1 | | | |
| () W48H1-A20 | | | | | | | |

SHORT-CIRCUIT CURRENT: 5KA RMS SYMMETRICAL
 BRANCH CIRCUIT SELECT CURRENT 23.1 OPERATING VOLTAGE RANGE: 197 VAC MIN. 253 VAC MA

SERIAL NUMBER 343D122899483-02

SUITABLE FOR OUTDOOR USE ALL MOTORS ARE THERMALLY PROTECTED

| | VAC | HZ | ELECTRICAL RATINGS | | | LRA | RLA |
|----------------|---------|----|--------------------|----------|-----------|------------|-----------|
| | | | PH | HP | FLA | | |
| COMPRESSOR | 230/208 | 60 | 1 | | | 131/131 | 19.5/21.2 |
| OUTDOOR MOTOR | 230/208 | 60 | 1 | 1/3 | 2.5 | | |
| INDOOR MOTOR | 230/208 | 60 | 1 | 1/2 | 3.3 | | |
| WERV-A5A | 230/208 | 60 | 1 | | 2.2 | (OPTIONAL) | |
| HEATER PACKAGE | | | | KW | FLA | | |
| EHWH04-A04 | 240/208 | 60 | 1 | 4/3 | 16.7/14.4 | | |
| EHWH42-A05 | 240/208 | 60 | 1 | 5/3.75 | 20.8/18.1 | | |
| EHWH42-A10 | 240/208 | 60 | 1 | 10/7.5 | 41.6/36.2 | | |
| EHWH42-A15 | 240/208 | 60 | 1 | 15/11.25 | 62.5/54.1 | | |
| EHWH04-A20 | 240/208 | 60 | 1 | 20/15 | 83.2/72.1 | | |

-- FACTORY REFRIGERANT --
 FACTORY CHARGED R410A: 144 OZ. DESIGN PRESSURE PSIG 449 HIGH 238 LOW

-- CLEARANCES --


UNIT CASING SUITABLE FOR 0 INCH CLEARANCE.

OUTLET DUCT CLEARANCE 1/4 INCH MINIMUM FOR AT LEAST FIRST 3 FEET OF DUCT. REFER TO INSTALLATION INSTRUCTIONS FOR ADDITIONAL CLEARANCE INFORMATION. MAXIMUM OUTLET AIR TEMPERATURE: 200
 THIS MODEL HAS BEEN TESTED AT STATIC PRESSURES FROM 0 TO .5 IN. WATER COLUMN. CONSULT INSTALLATION INSTRUCTIONS FOR MAXIMUM PERMITTED STATIC PRESSURE FOR SPECIFIC EQUIPMENT APPL

INSTALLER: WHEN INSTALLING OPTIONAL BARD HEATER PACKAGE: PERMANENTLY MARK THIS SERIAL PLATE TO SHOW THE INSTALLED HEATER PACKAGE.

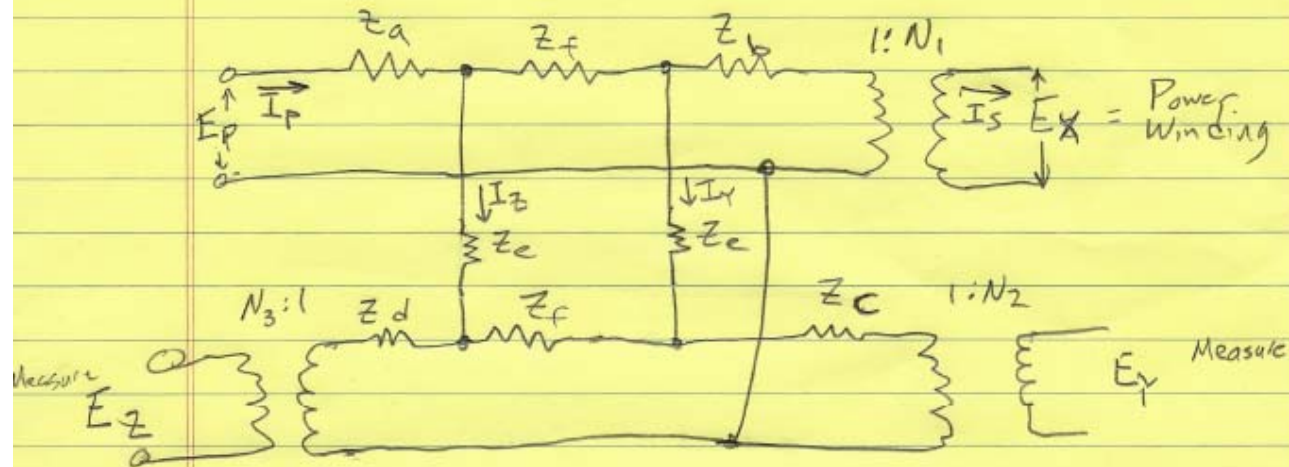(1) ONLY BARD HEATER PACKAGES LISTED ABOVE ARE SUITABLE FOR USE WITH THIS UNIT. USE OF ANOTHER HEATER PACKAGE voids warranty and could cause safety hazards.

Four Winding Xfmr equivalent circuit
(comes from section 55 of Westinghouse T&D Reference Book)



Assume I_z and I_y are magnetizing only
(since they are measurement windings) $I_z = I_y \rightarrow 0$

$$E_z = \frac{E_p - Z_a I_p - \overset{0}{I_z}(Z_d + Z_e)}{N_3} = \frac{E_p - Z_a I_p}{N_3}$$

$$E_y = \frac{E_p - Z_a I_p - Z_b(I_p - \overset{0}{I_z}) - \overset{0}{I_y}(Z_c + Z_e)}{N_2} = \frac{E_p - Z_a I_p - Z_b I_p}{N_2}$$

if $I_z = I_y \rightarrow 0$ then $I_s = I_p N_1$ or $I_p = I_s / N_1$
if I_s increases, so does I_p
Therefore E_z and E_y decrease as I_s increases.

What can I do to prevent nuisance trips when the heat pump kicks on?

- Capacitor Bank Protection is set very sensitive. In this case at 2%.
- Can interlock the heat pump contactor with an 89B contact (humor intended)
- Can add a standard VT to provide voltages for protection.

How would this effect other relaying

- Phase and Ground Distance Protection:
 - Could cause an element to over-reach if a fault occurred at the same instance of a heat pump start.
 - Probably wouldn't affect steady state conditions unless extremely heavily loaded line.

How would this effect other relaying

- Bus Under-voltage:
 - Probably would be unaffected because of the duration.

Lessons Learned

- Capacitor Bank Protection requires very sensitive settings.
- VT error can influence those setting.
- We still spend most of our time talking about instrument transformers.

Questions ?



imagination at work



Thank You For the Time

