

VCO-Based Quantizers – Has Their Time Arrived?

***IEEE Distinguished Lecture
Austin, TX***

**Michael H. Perrott
October 2012**

**Copyright © 2012 by Michael H. Perrott
All rights reserved.**



Why Should We Consider VCO-Based Quantizers?

- **Advanced CMOS processes improve digital circuits**
 - **Faster speed, higher density**

- ***But*, analog circuits suffer**
 - **Reduced intrinsic device gain ($g_m r_o$)**
 - **Reduced supply voltages**

- **VCO-based quantizers utilize *time* as the signal**
 - **Take advantage of digital improvements**
 - **Offer a simple design that is high speed, multi-bit**

 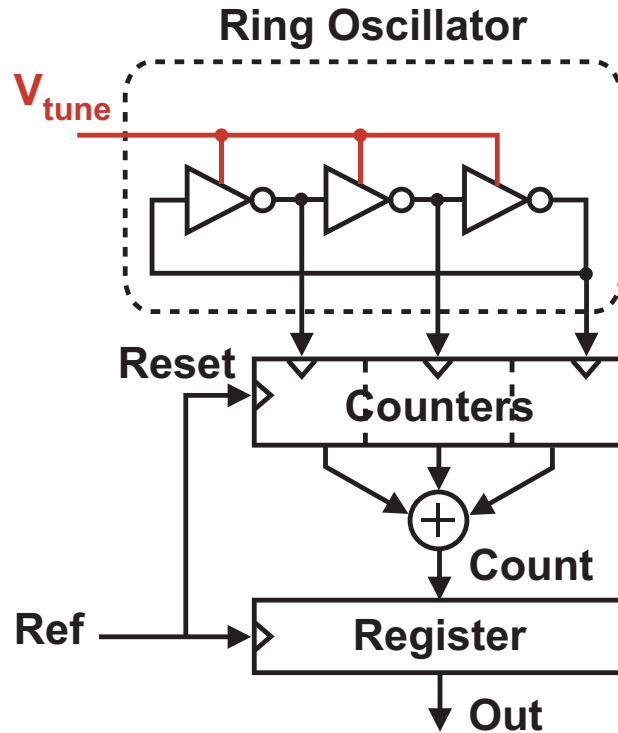
Using a Voltage Controlled Oscillator as an ADC



Wismar, ESSCIRC 2006
Kim, ISCAS 2006
Alon, JSSC 2005

- **Input:** analog tuning of ring oscillator frequency
- **Output:** count of oscillator cycles per Ref clock period

 
Phase Sampling Can Be More Efficient than Counting




- V_{tune} controls delay of cells
 - Alters the number of transitions per ref clock period
- Digital circuits compute transition count at each sample

VCO-Based Quantizer Shapes Delay Mismatch


Measurement 1

 


Measurement 2

 

Measurement 3

 


Measurement 4

 

- Barrel shifting through delay elements
 - Mismatch between delay elements is first order shaped


Advantages of VCO-based Quantization

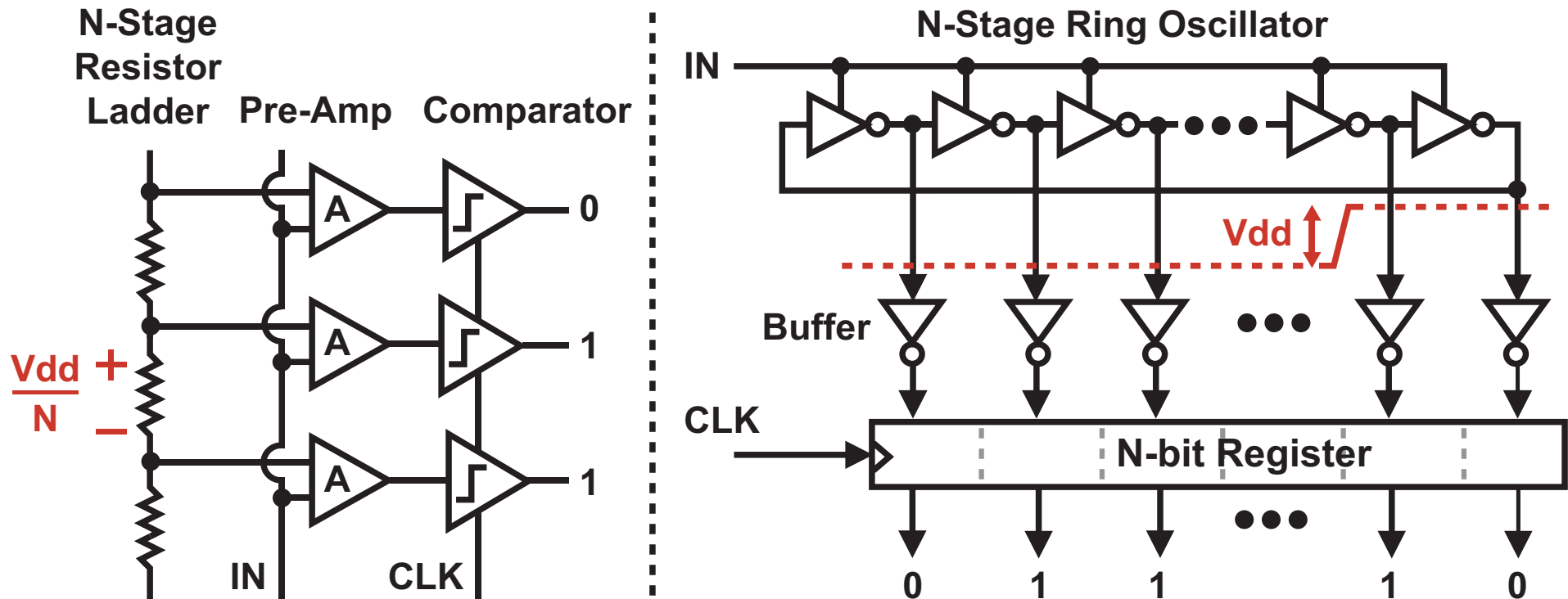

- Highly digital implementation
- Offset and mismatch is not of critical concern
- Metastability behavior is potentially improved
- SNR improves due to quantization noise shaping

Implementation is high speed, low power, low area


Modeling a VCO-Based Quantizer

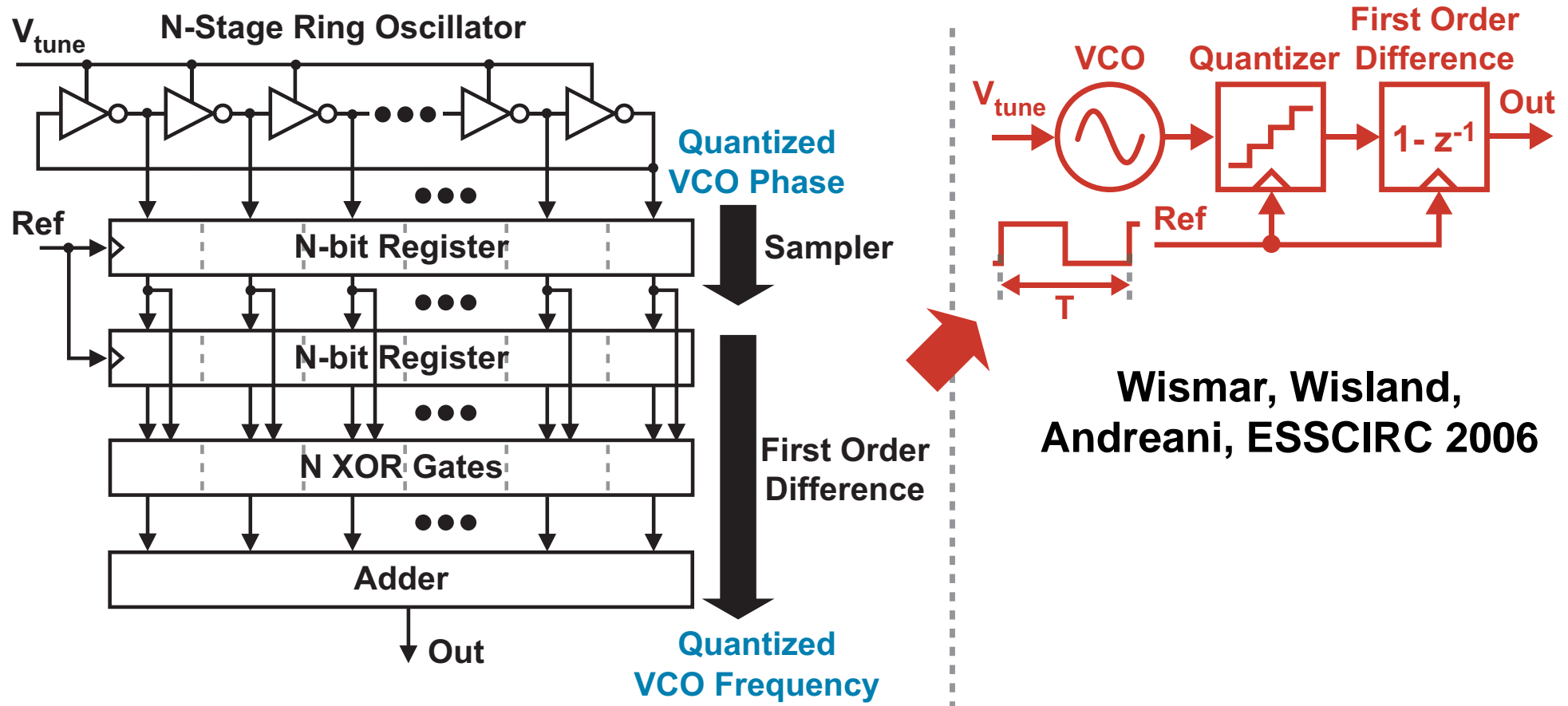


- **VCO provides quantization, register provides sampling**
 - Model as separate blocks for convenience
- **XOR operation yields first order difference operation**
 - Extracts VCO frequency from sampled VCO phase

Corresponding Frequency Domain Model

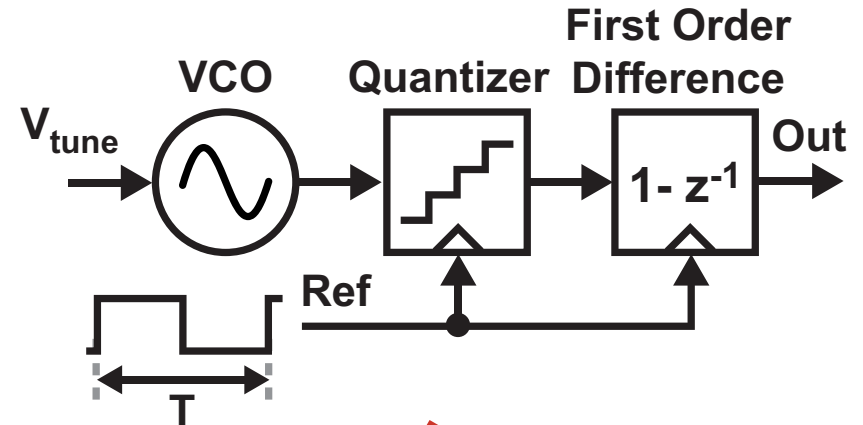- VCO: nonlinear integrator
- Phase sampler: scale by $1/T$
- Quantizer: adds noise
- First order diff: shapes noise




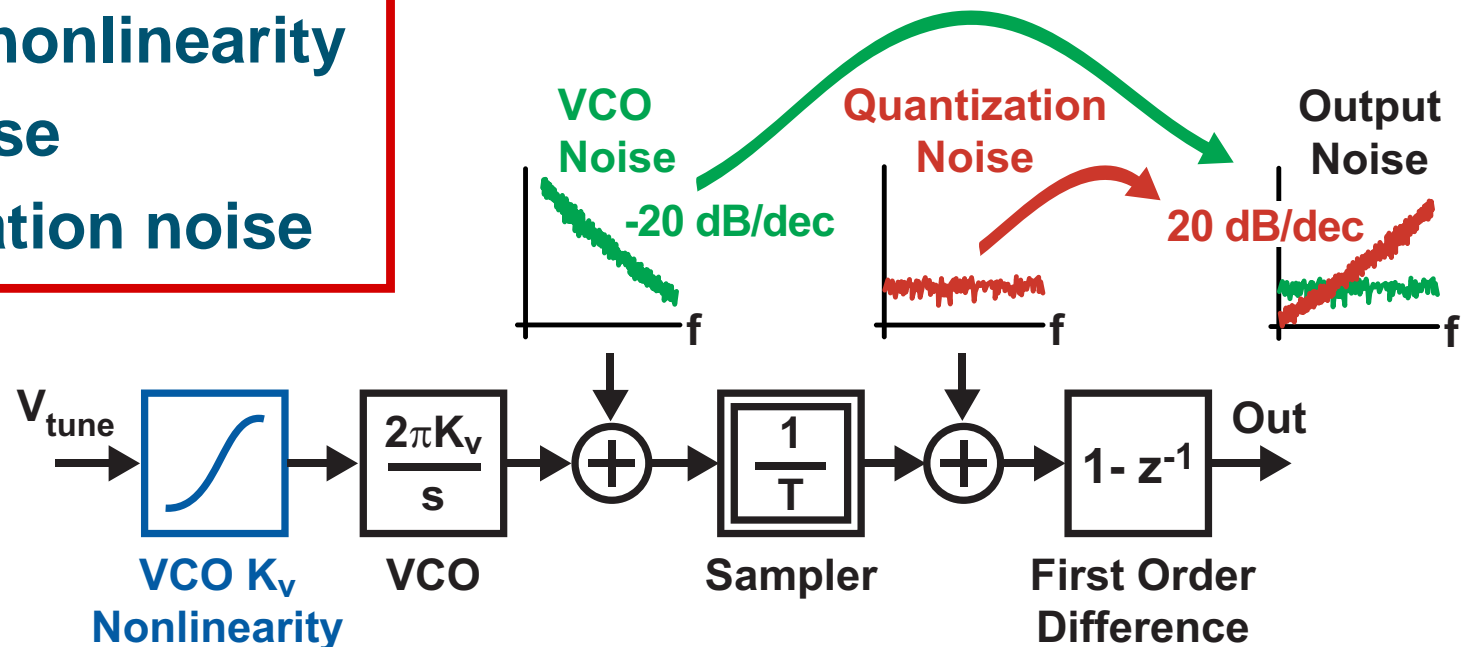- Key non-idealities:
 - VCO K_V nonlinearity
 - VCO noise
 - Quantization noise



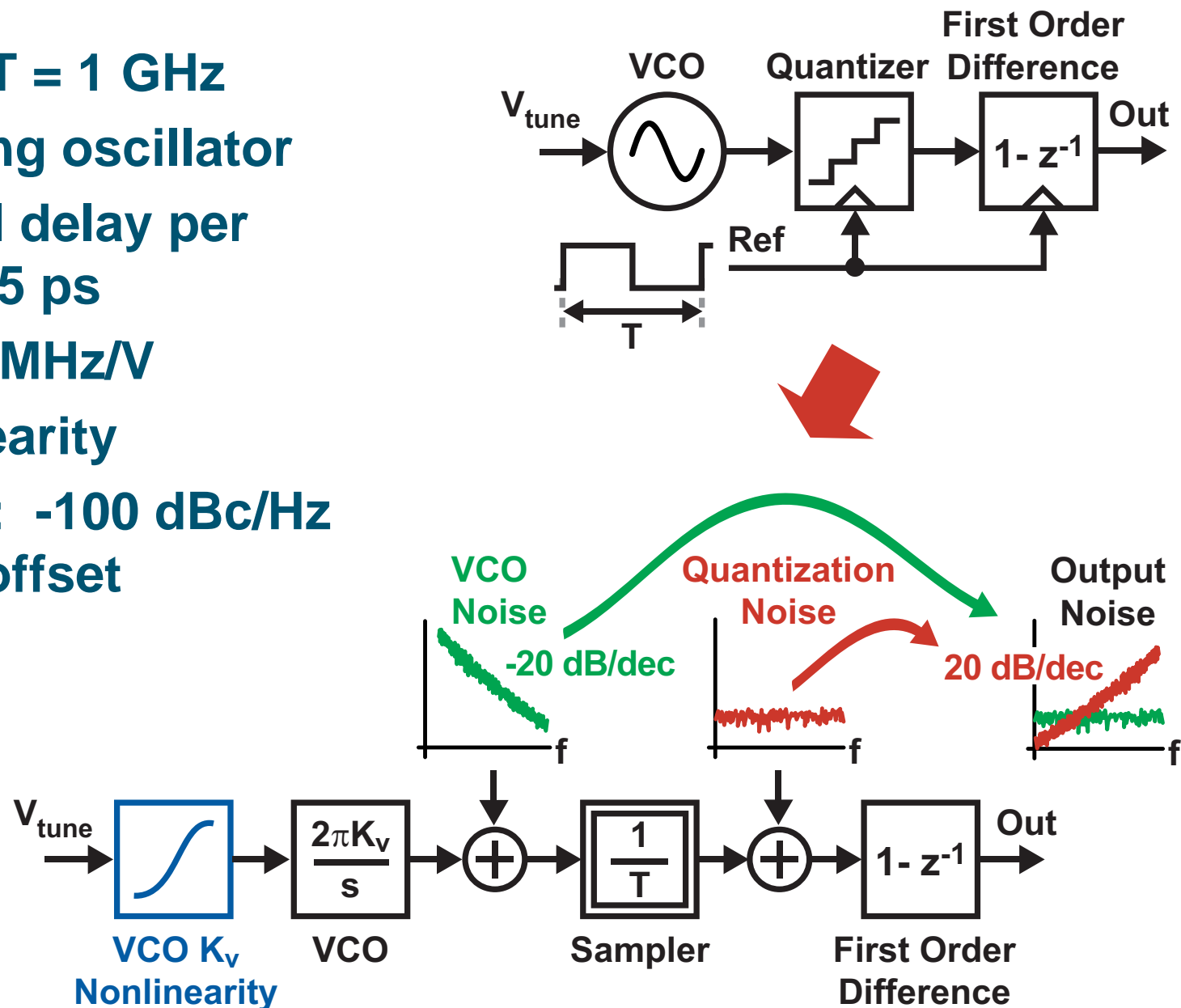
Example Design Point for Illustration

- Ref clk: $1/T = 1 \text{ GHz}$
- 31 stage ring oscillator
 - Nominal delay per stage: 65 ps
- $K_{\text{VCO}} = 500 \text{ MHz/V}$
 - $\pm 5\%$ linearity
- VCO noise: -100 dBc/Hz at 10 MHz offset




Example SNDR with 20 MHz BW (1 GHz Sample Rate)

Simulated ADC Output Spectrum

 


Conditions	SNDR
Ideal	68.2 dB
VCO Thermal Noise	65.4 dB
VCO Thermal + Nonlinearity	32.2 dB

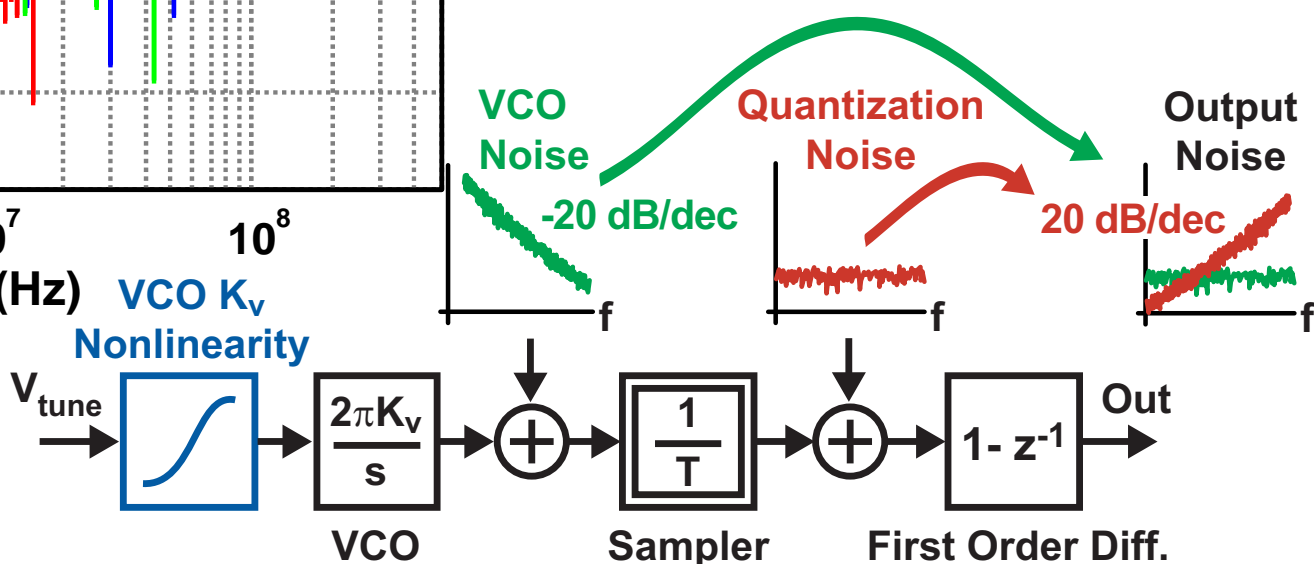


Key Issues: Nonlinearity and VCO Phase Noise

- **VCO K_v nonlinearity**
 - Limits SNDR with distortion
 - Linear K_v oscillator difficult
- **VCO phase noise**
 - Degrades SNR and SNDR
 - Improves with area/power

Conditions	SNDR
Ideal	68.2 dB
VCO Thermal Noise	65.4 dB
VCO Thermal + Nonlinearity	32.2 dB

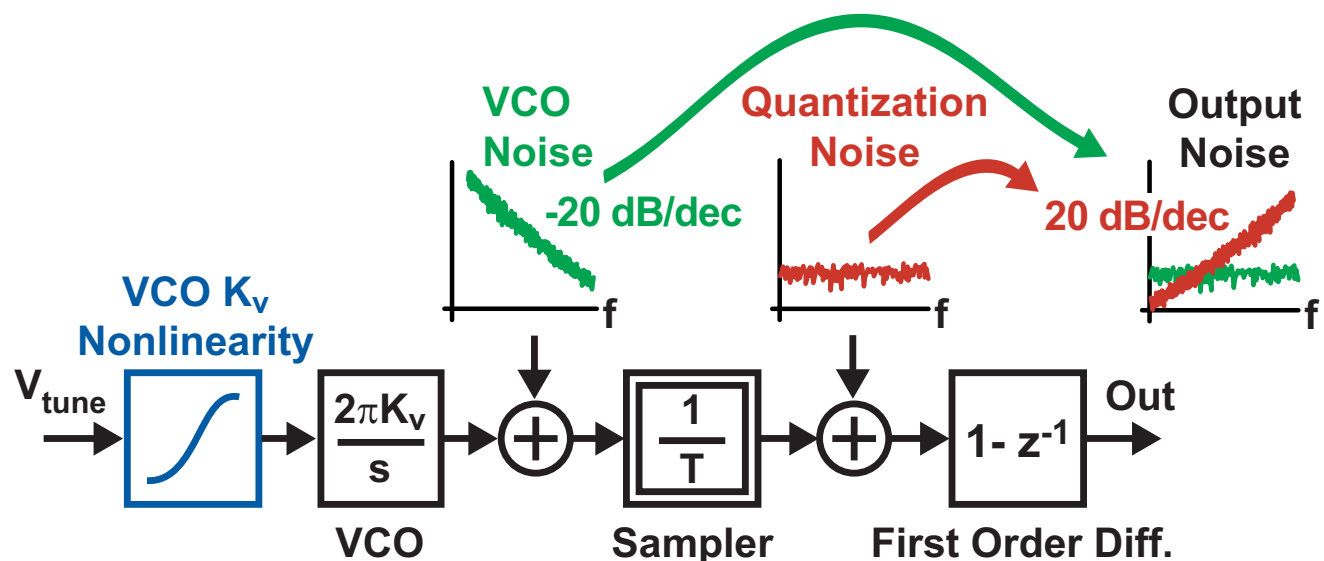


Pseudo-Differential Implementation

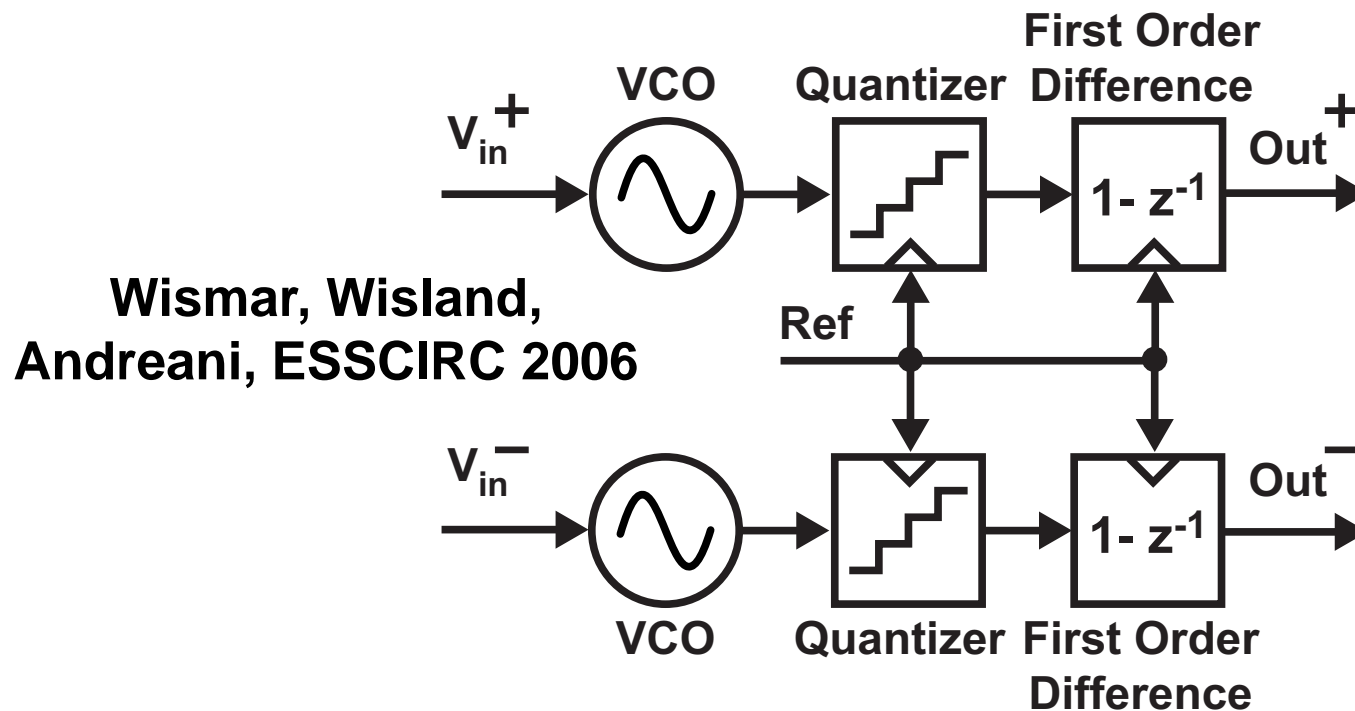


- Even order nonlinearity reduced
- VCO phase noise reduced 3dB (double area/power)
- Benchmark: 44 dB SNDR with 20 kHz BW
 - Impressive 0.2V supply, 440 nW power in 90nm CMOS

Digital Correction of Nonlinearity

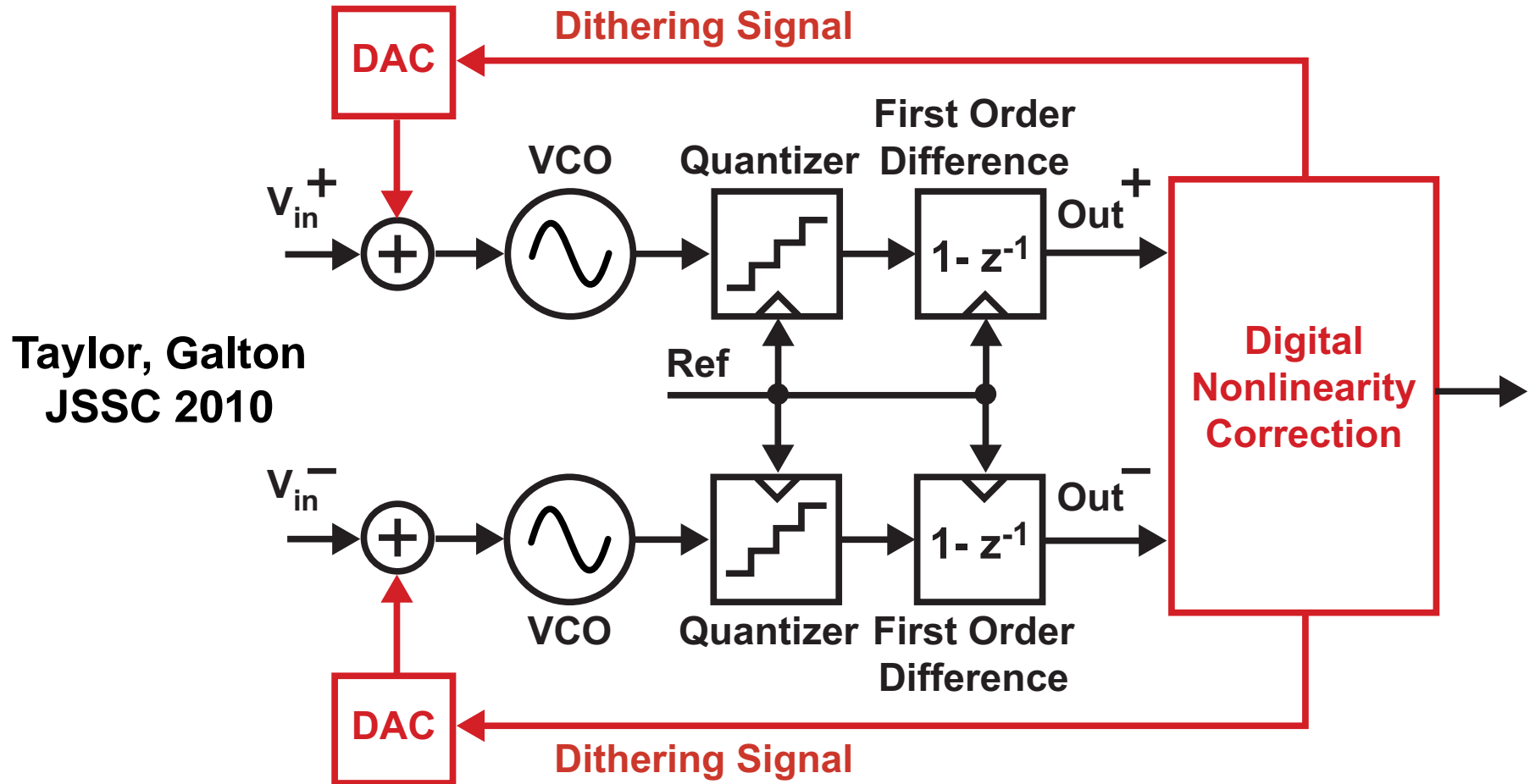


- **Highly digital implementation (65nm CMOS)**
 - ~70/78 dB SNDR at 18/4.5MHz BW (FOM: 297fJ/conv)
- **Issues: calibration time, only first order noise shaping**

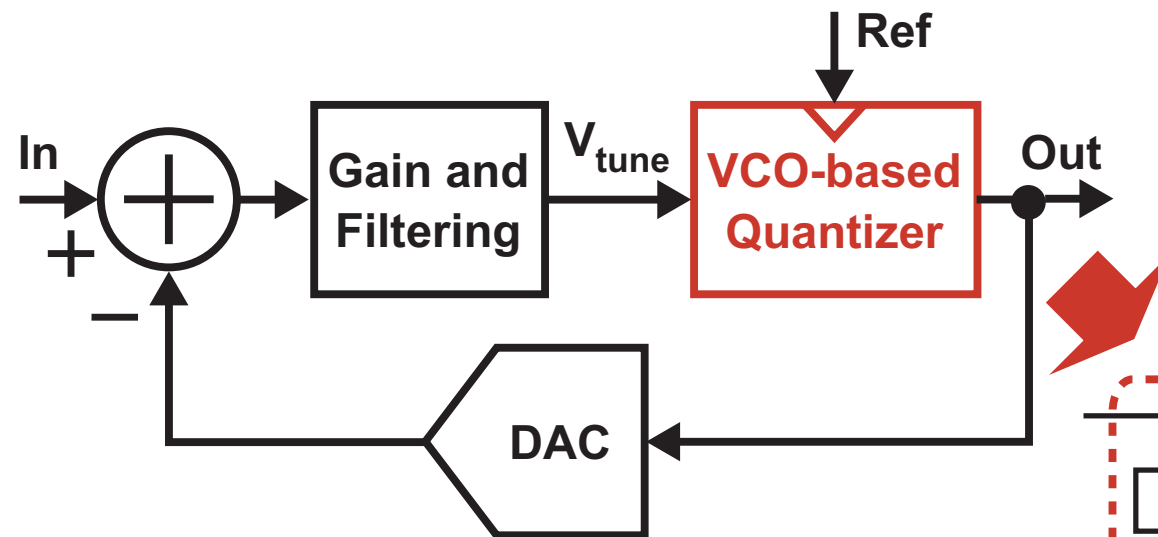Reducing the Impact of Nonlinearity using Feedback




Iwata, Sakimura,
TCAS II, 1999
Naiknaware, Tang,
Fiez, TCAS II, 2000

 - **Continuous-time Δ - Σ ADC**
 - VCO-based quantizer provides multi-bit implementation with first order noise shaping
- **Gain before VCO quantizer**
 - Suppresses VCO nonlinearity
 - Suppresses VCO phase noise



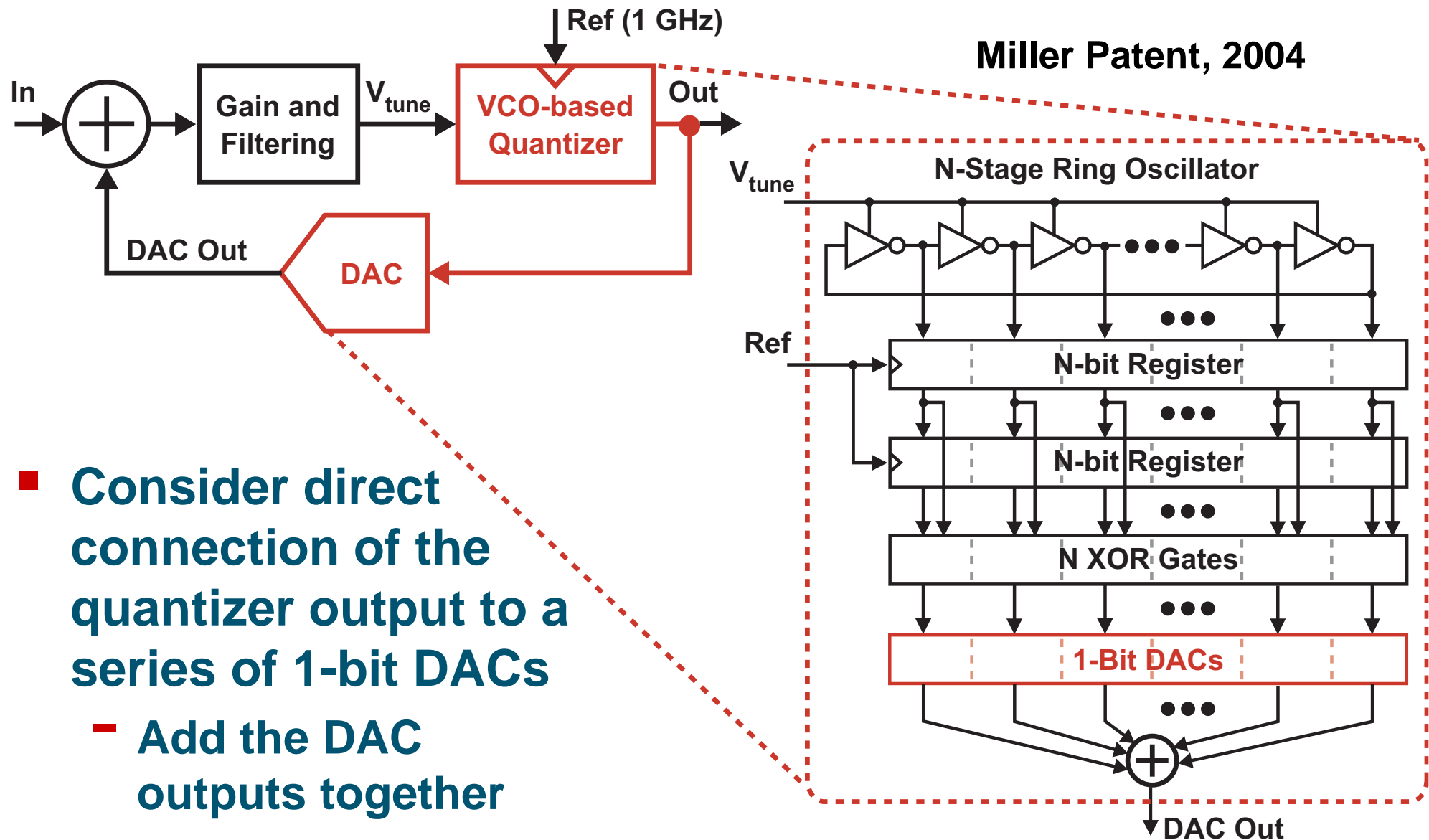
Leveraging Barrel Shifting in the Quantizer




- Consider direct connection of the quantizer output to a series of 1-bit DACs
 - Add the DAC outputs together

Intrinsic barrel shifting of the DAC elements is achieved!

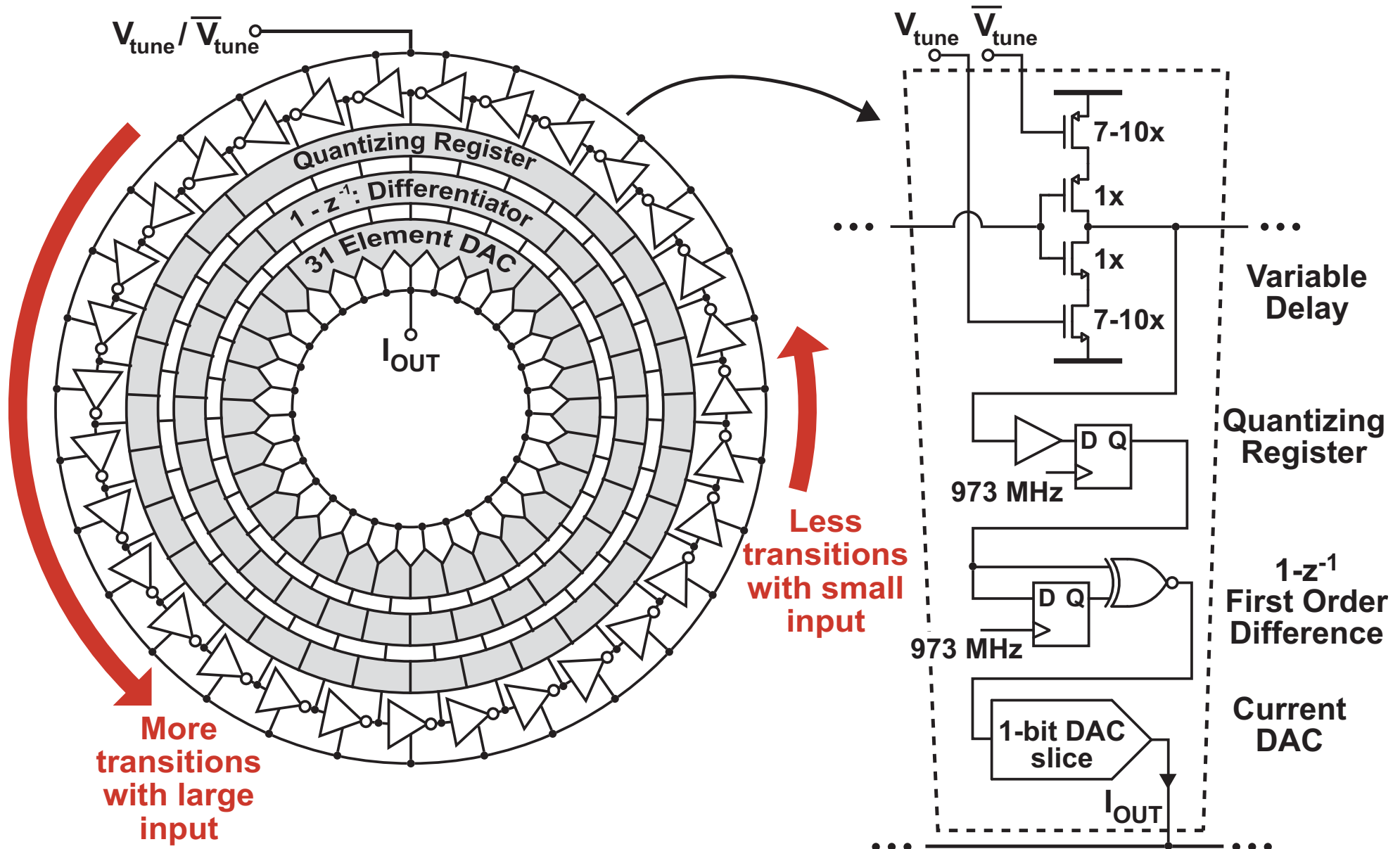A Geometric View of the VCO Quantizer/DEM and DAC




 A Second Order Continuous-Time Delta-Sigma ADC





- **Second order dynamics** achieved with only *one* op-amp
 - Op-amp forms one integrator
 - I_{dac1} and passive network form another (lossy) integrator
 - Minor loop feedback compensates for quantizer delay
- **Third order noise shaping** due to VCO-based quantizer

Custom IC Implementing the Prototype

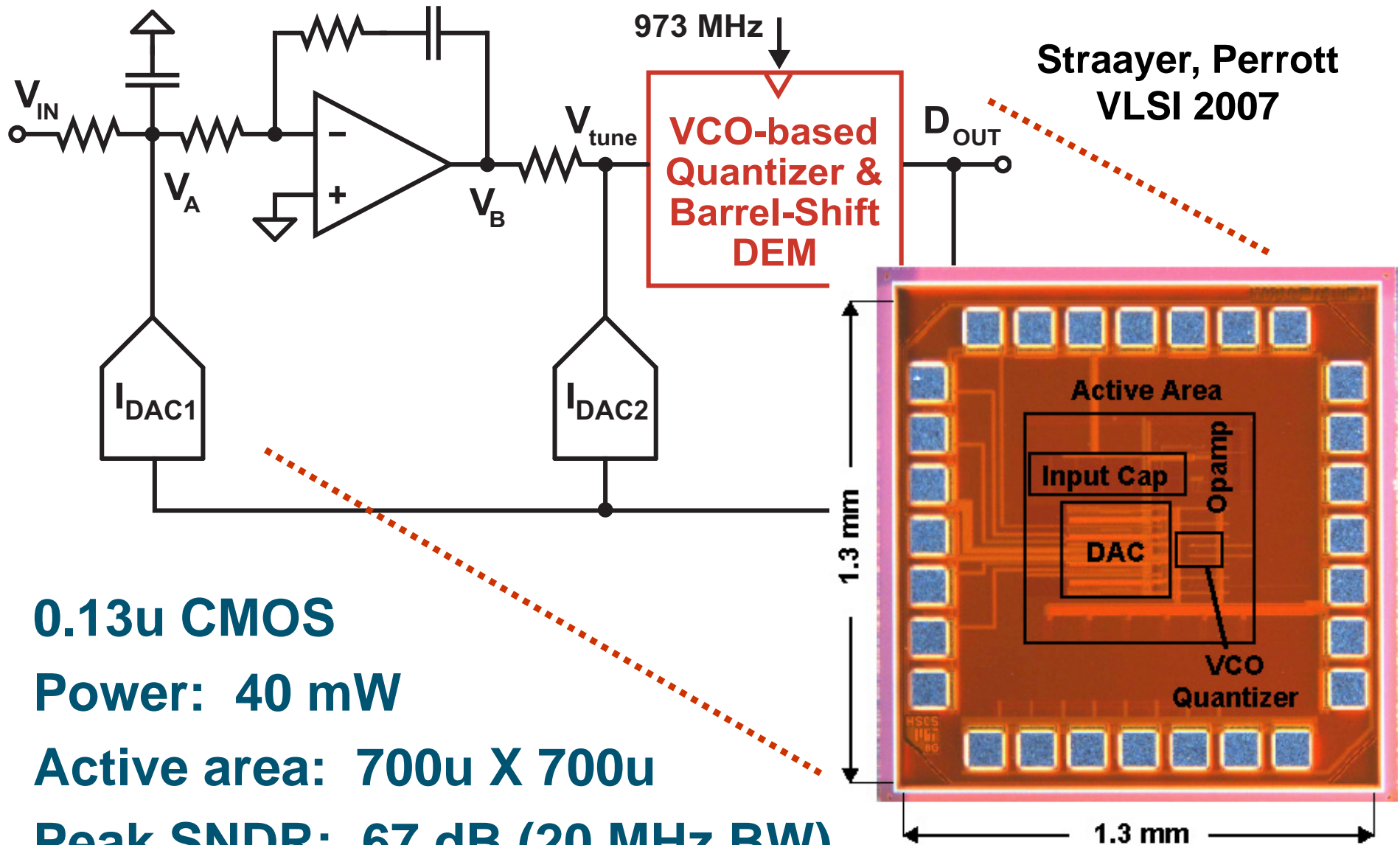


- 0.13u CMOS
- Power: 40 mW
- Active area: 700u X 700u
- Peak SNDR: 67 dB (20 MHz BW)
- Efficiency: 0.5 pJ/conv. step

Design of the VCO Core Inverter Cell

  

- 31 stages
- Fast for good resolution (< 100 psec / stage)
- Large K_{VCO} (600-700 MHz) with good dynamic range
- 2 bits of coarse tuning for process variations
- < 8 mW for 1 GSPS 5-bit quantizer / DEM


Opamp Design is Straightforward

 

Simulated Performance:


- $A_v = 55$ dB
- $GBW = 2$ GHz
- $P_{DISS} = 15$ mW

 High SNR of
VCO-based
quantizer allows
reduced
opamp gain (A_v)




Primary Feedback DAC Schematic

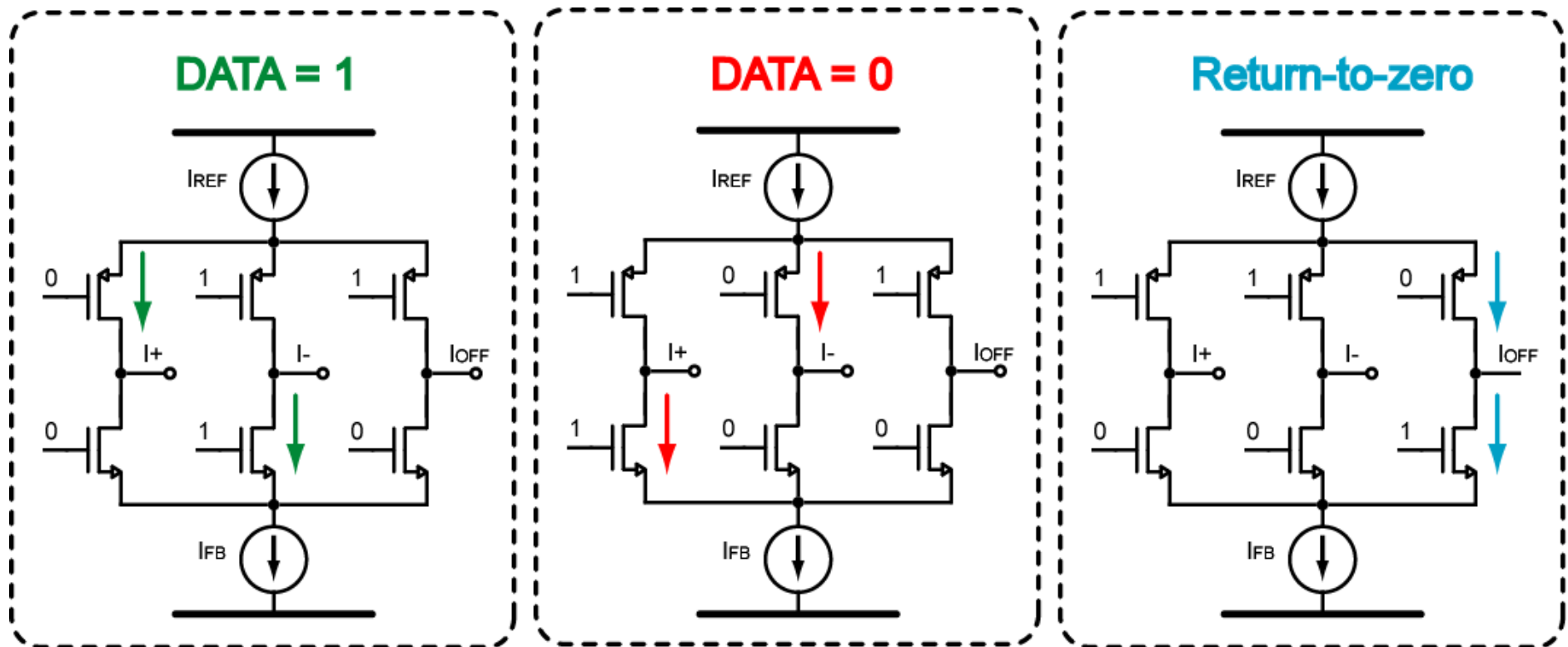
- Fully differential RZ pulses
- Triple-source current steering
- I_{OFF} is terminated off-chip



Measured Spectrum From Prototype

 


 Measured SNR/SNDR Vs. Input Amplitude (20 MHz BW)




How Do We Overcome K_v Nonlinearity to Improve SNDR?

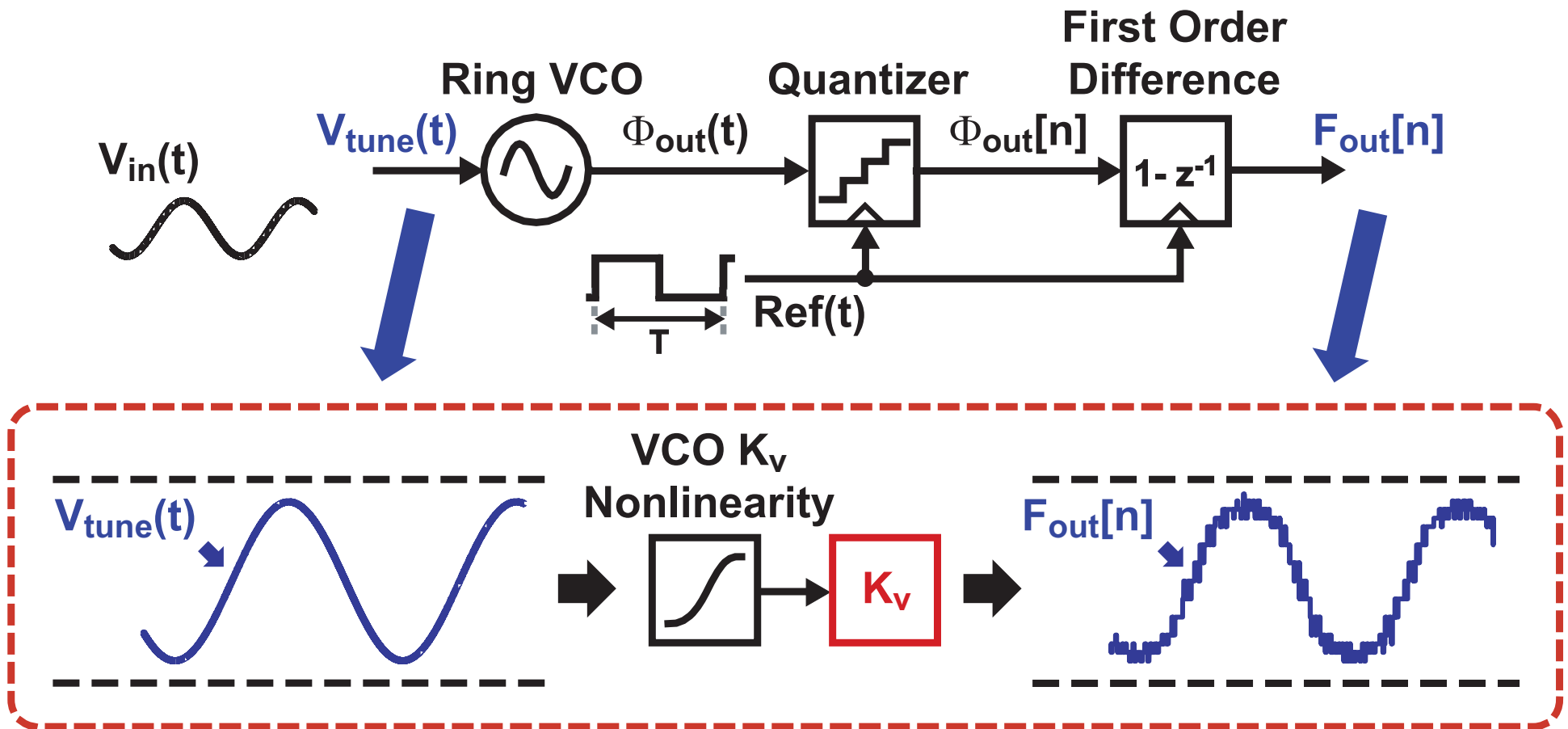Voltage-to-Frequency VCO-based ADC (1st Order Δ - Σ)




- Typically, VCO frequency is desired output variable
 - ▀ Input uses full voltage-to-frequency (K_v) characteristic
 - ▀ Strong distortion at extreme ends of the K_v curve

 Voltage-to-Phase Approach (1st Order Δ - Σ)




- VCO output *phase* is now the output variable
 - Small perturbation on V_{tune} allows large VCO phase shift
 - VCO acts as a CT integrator with *infinite* DC gain

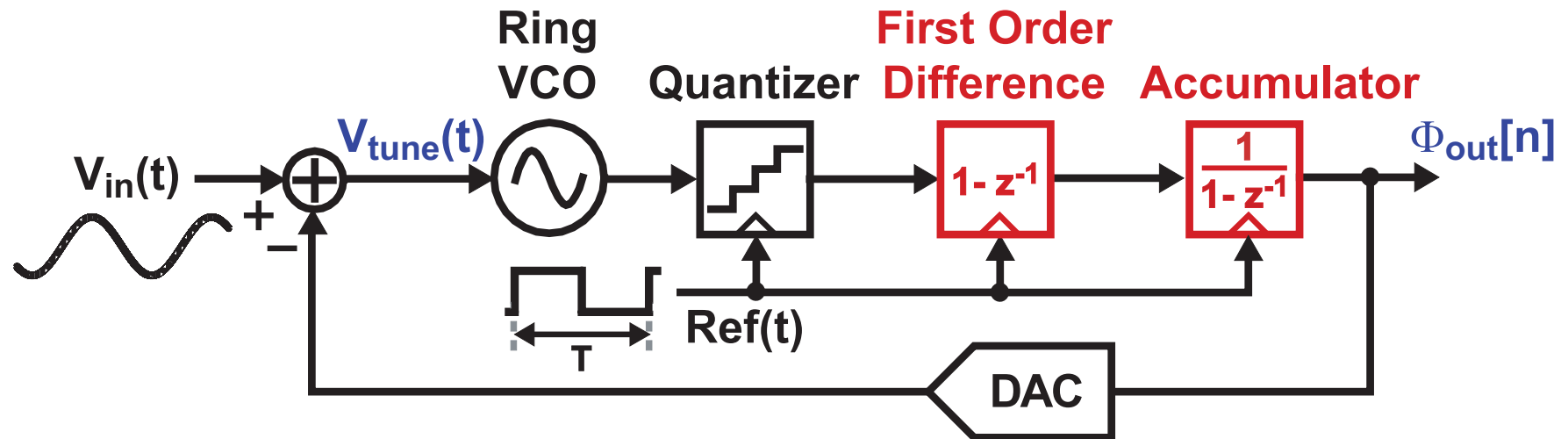High Speed Implementation of Phase-Based ADC




Park, Perrott
JSSC 2009

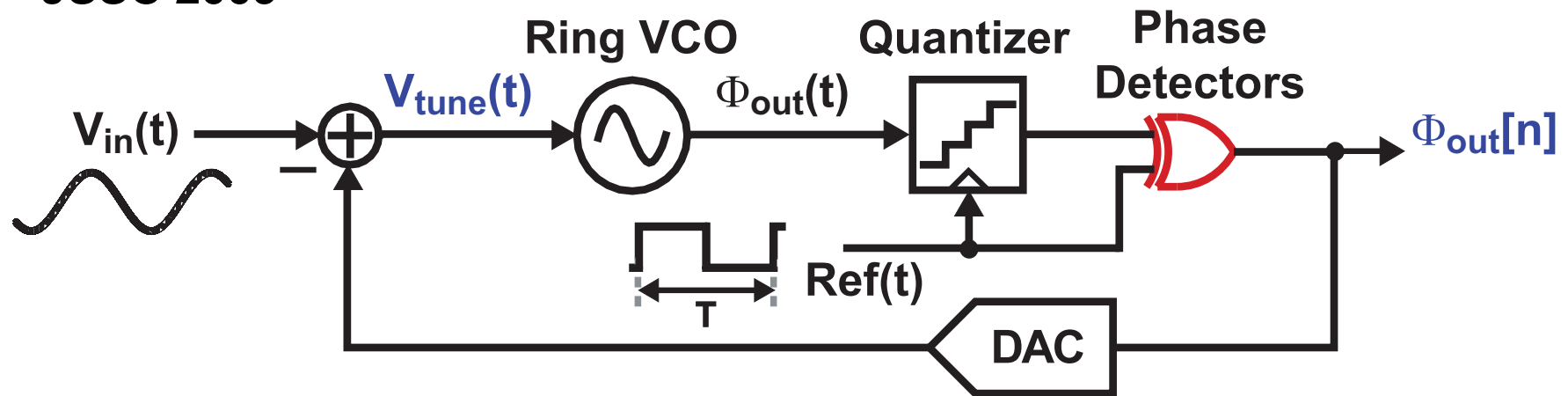


High SNDR requires higher order $\Delta-\Sigma$...

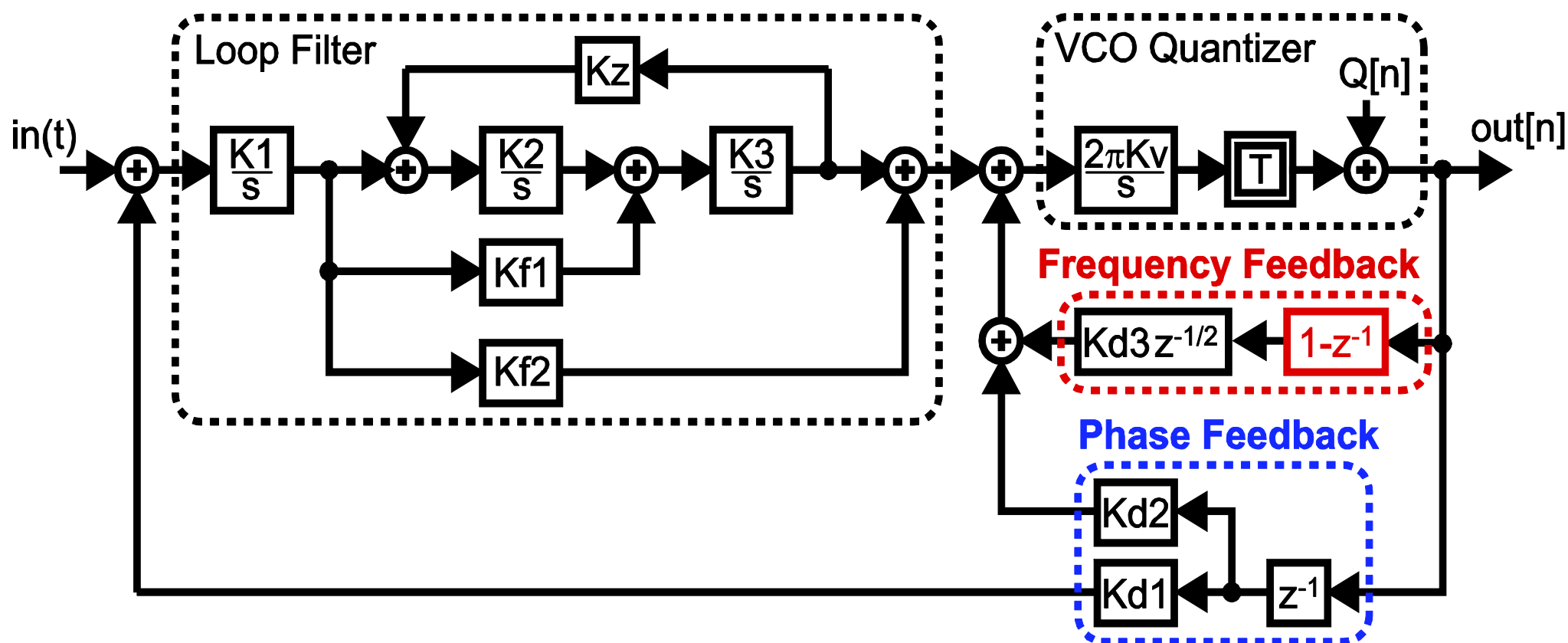Proposed 4th Order Architecture for Improved SNDR




- **Goal: ~80 dB SNDR with 20 MHz bandwidth**
 - Use 4th order loop filter, 4-bit VCO-based quantizer
 - 4-bit quantizer: tradeoff resolution versus DEM overhead
- **Combined frequency/phase feedback for stability/SNDR**

Schematic of Proposed Architecture

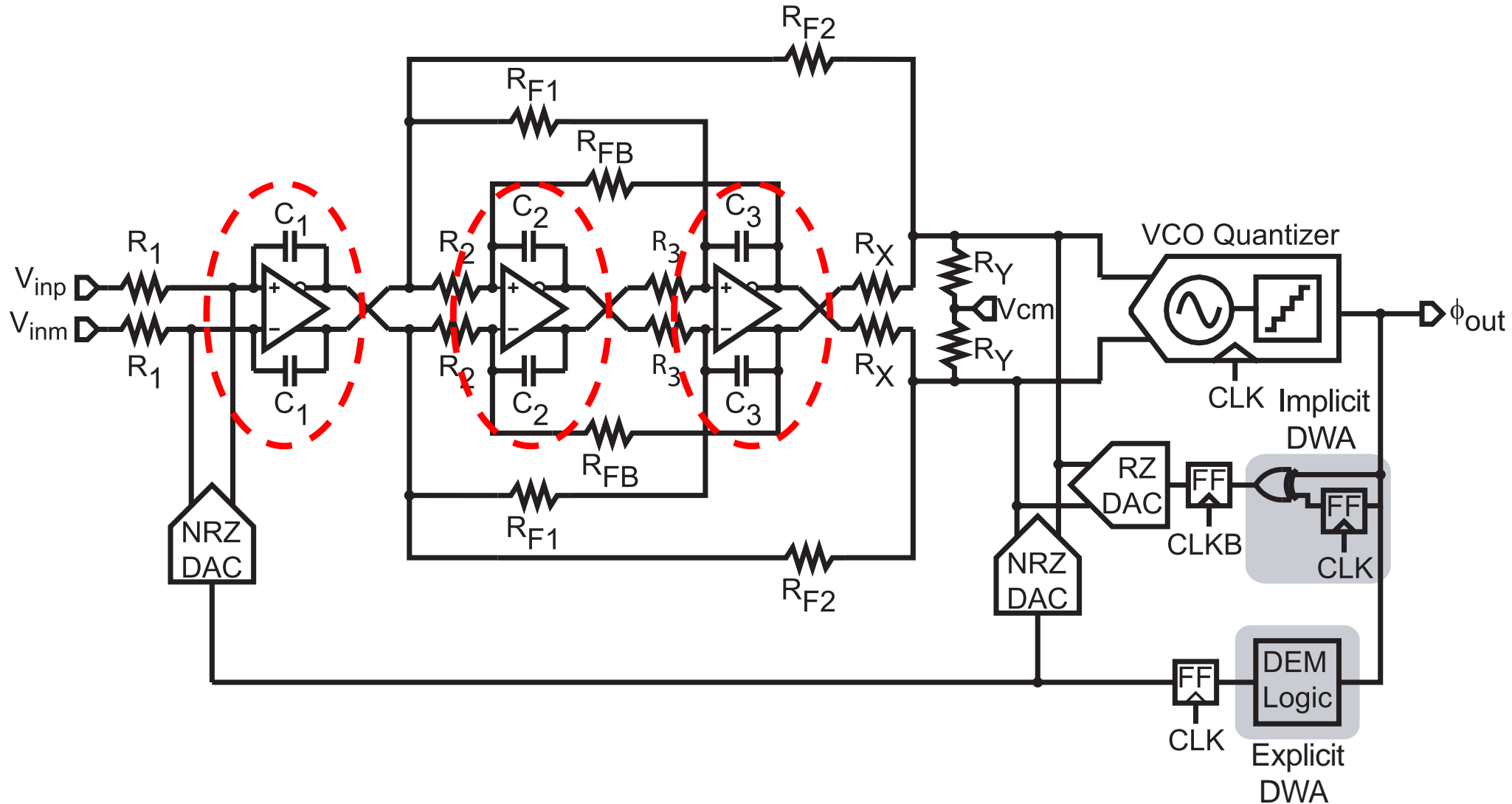


- Opamp-RC integrators
 - Better linearity than Gm-C, though higher power

Schematic of Proposed Architecture

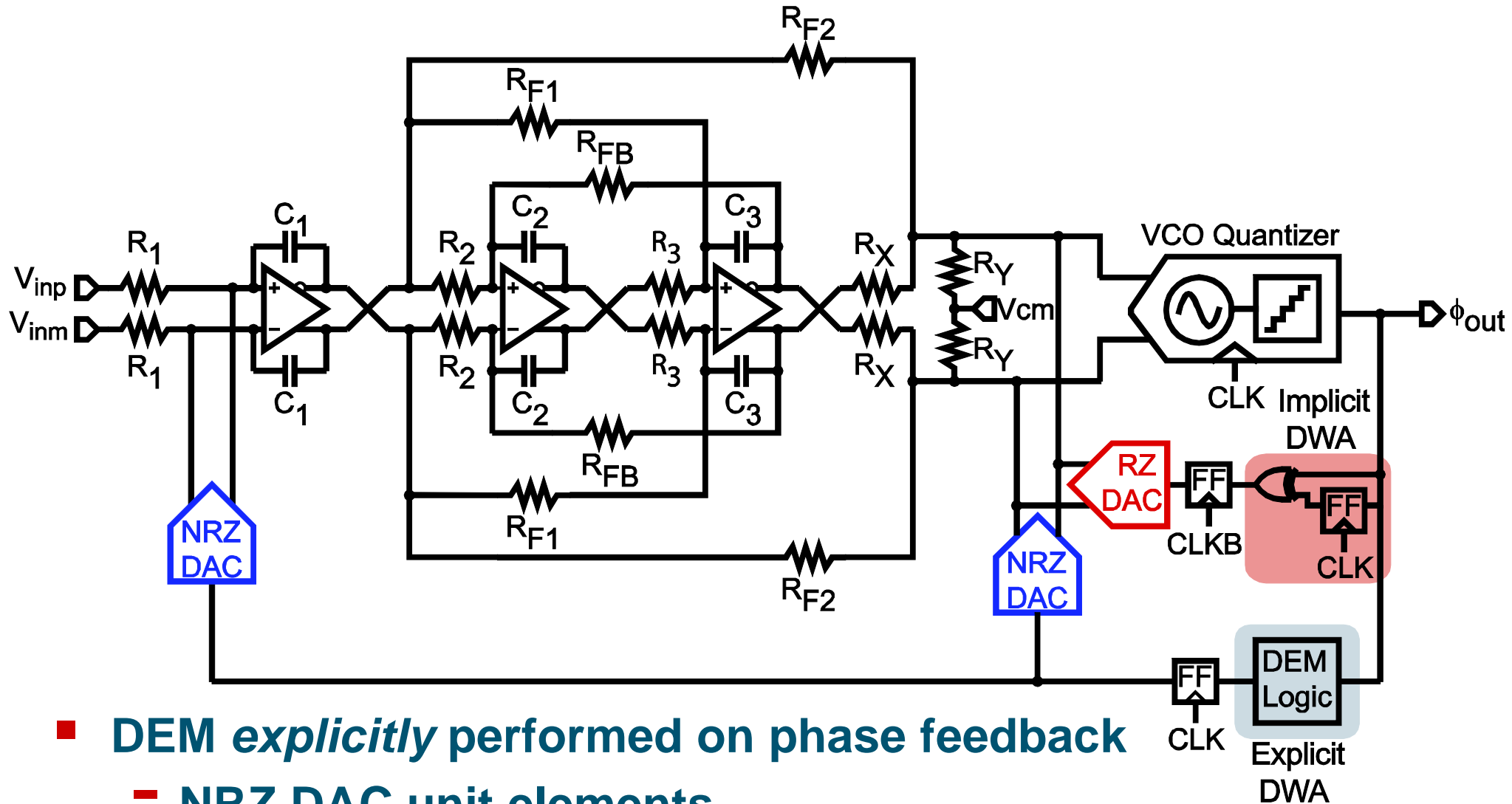

- **DEM explicitly performed on phase feedback**
 - NRZ DAC unit elements
- **DEM implicitly performed on frequency feedback (Miller)**
 - RZ DAC unit elements

 Behavioral Simulation (available at www.cppsim.com)



Key Nonidealities

- VCO Kv non-linearity
- Device noise
- Amplifier finite gain, finite BW
- DAC and VCO unit element mismatch




85 dB SNDR!

VCO nonlinearity is *not* the bottleneck for achievable SNDR!


Circuit Details

VCO Integrator Schematic

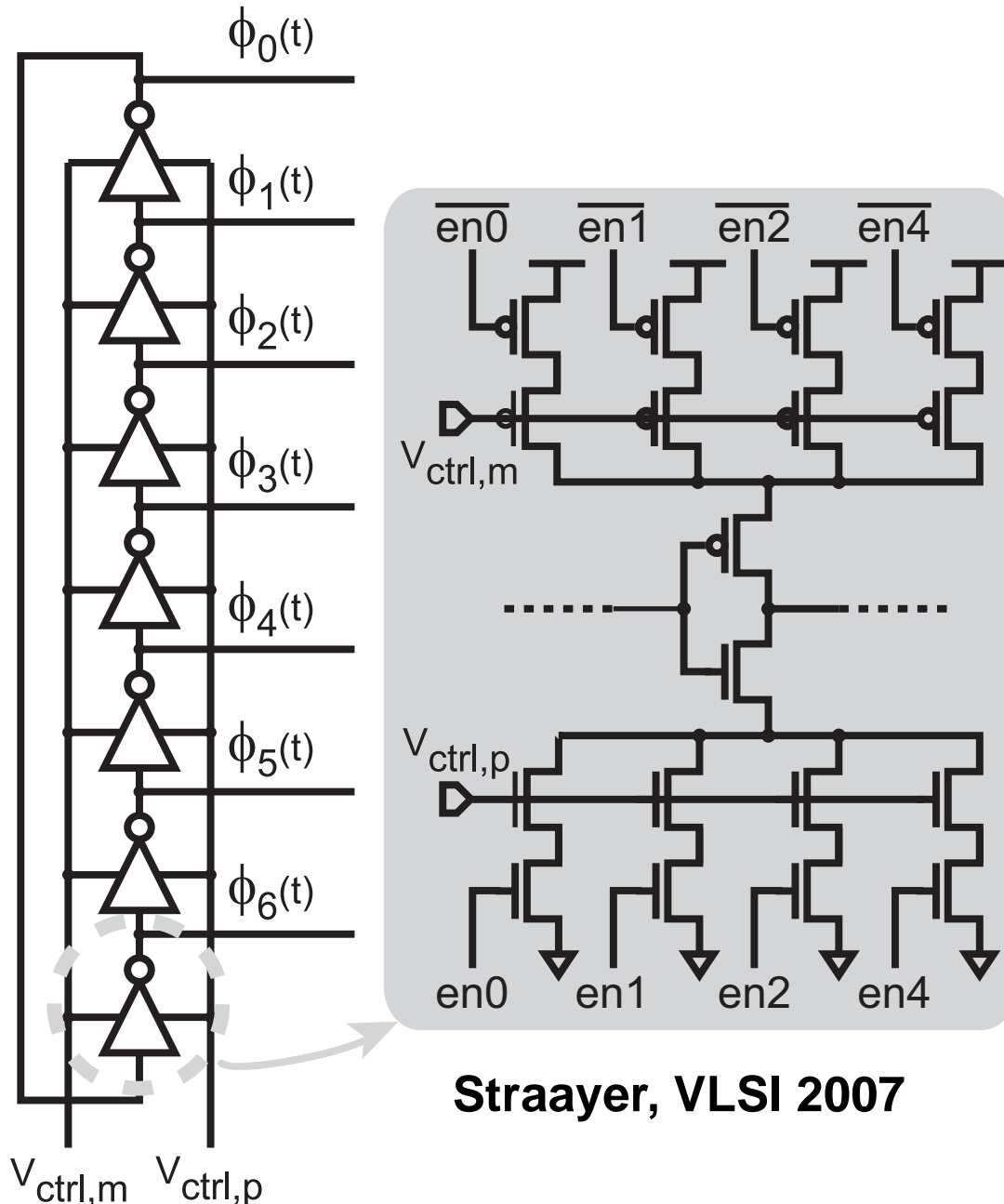

- **15 stage current starved ring-VCO**
 - 7 stage ring-VCO shown for simplicity
 - Pseudo differential control
 - PVT variation accommodated by enable switches on PMOS/NMOS
- **Rail-to-rail VCO output phase signals (VDD to GND)**


VCO Quantizer Schematic

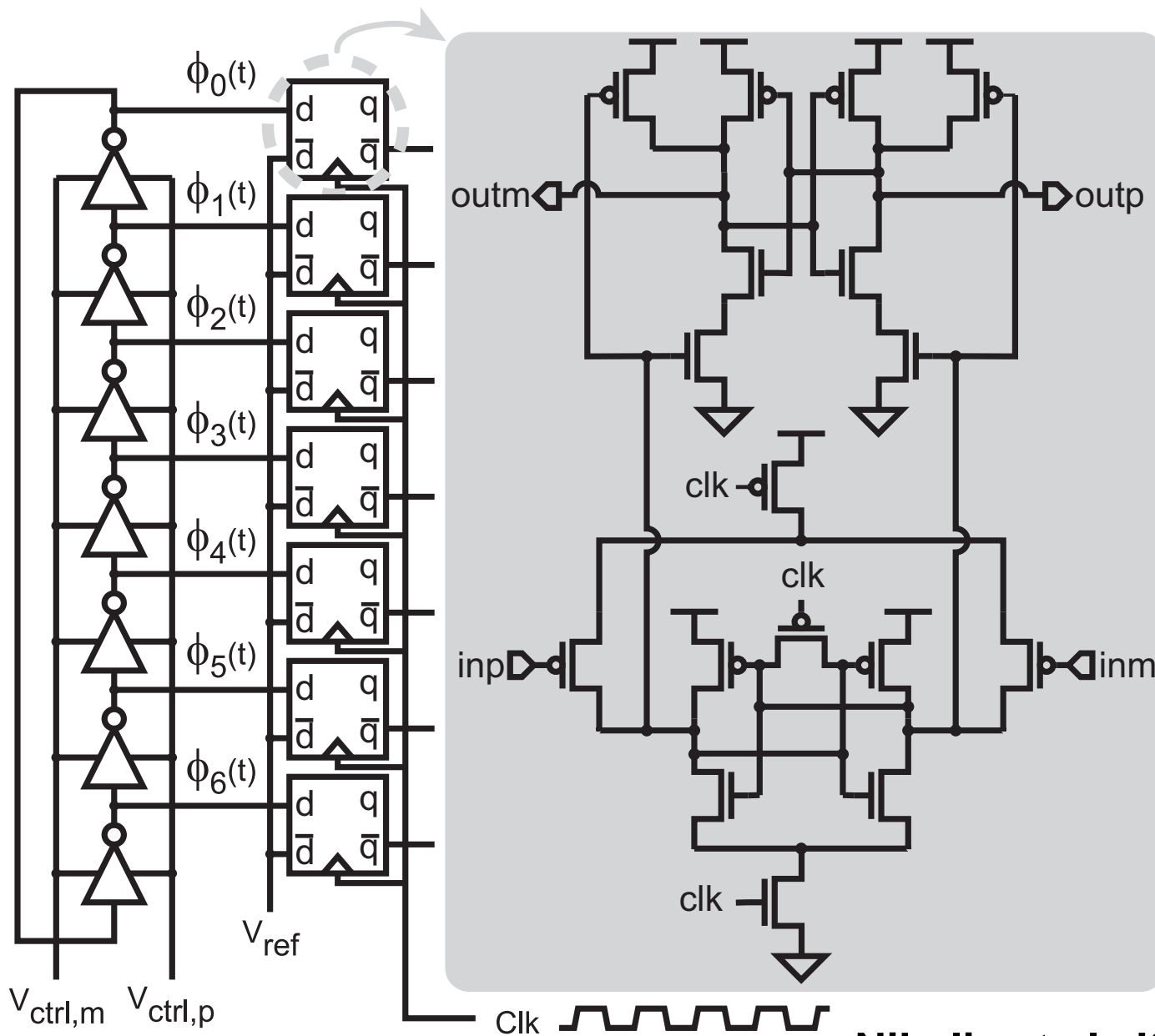

- Phase quantization with sense-amp flip-flop
 - Single phase clocking
- Rail-to-rail quantizer output signals (VDD to GND)

Nikolic et al, JSSC 2000

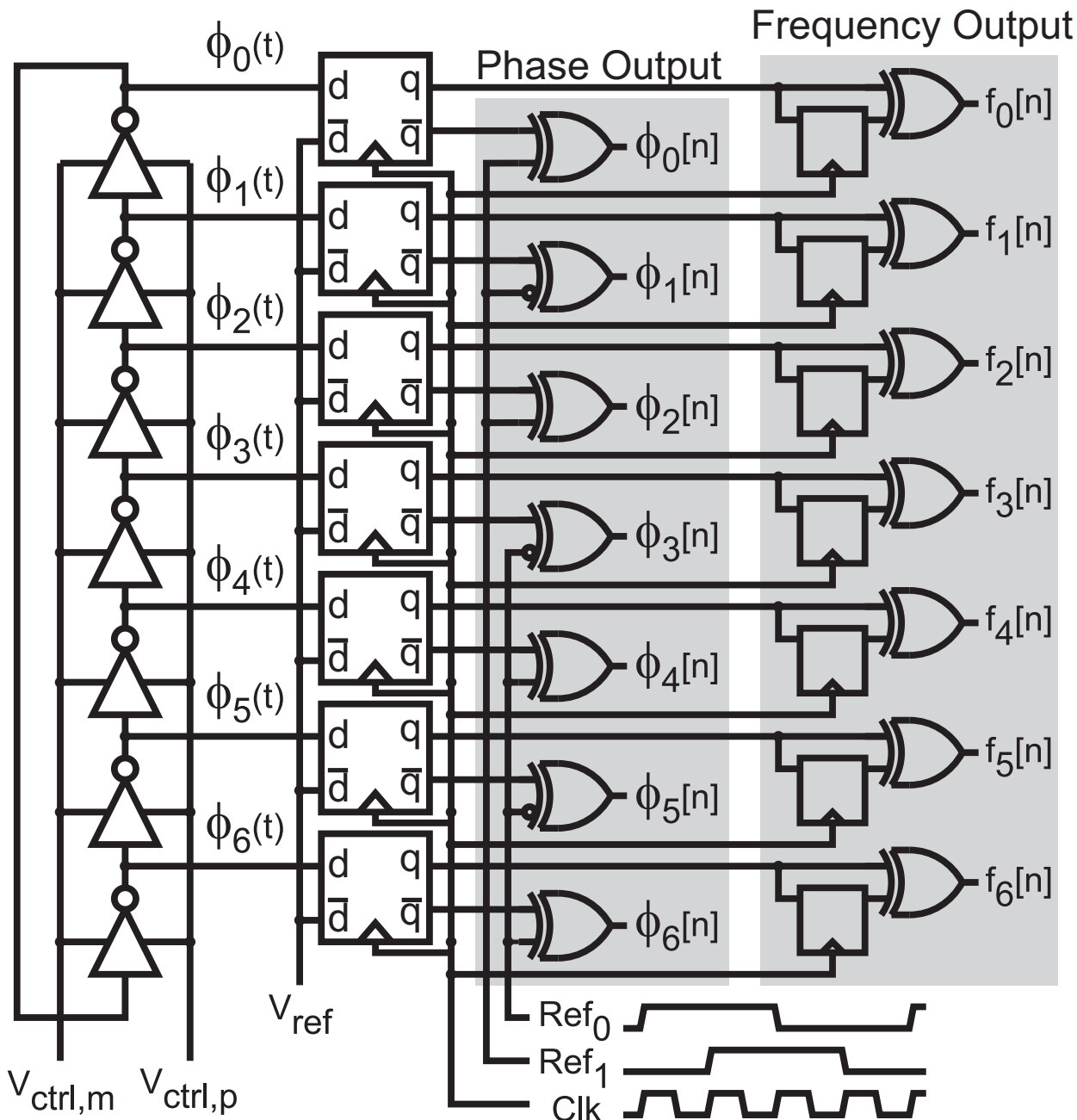
Phase Quantizer, Phase and Frequency Detector



- **Highly digital implementation**
 - Phase sampled & quantized by SAFF
 - XOR phase and frequency detection with FF and XOR
- **Automatic DWA for frequency detector output code**
 - Must explicitly perform DWA on phase detector output code

Main Feedback DAC Schematic

(same cell for V_{inm})

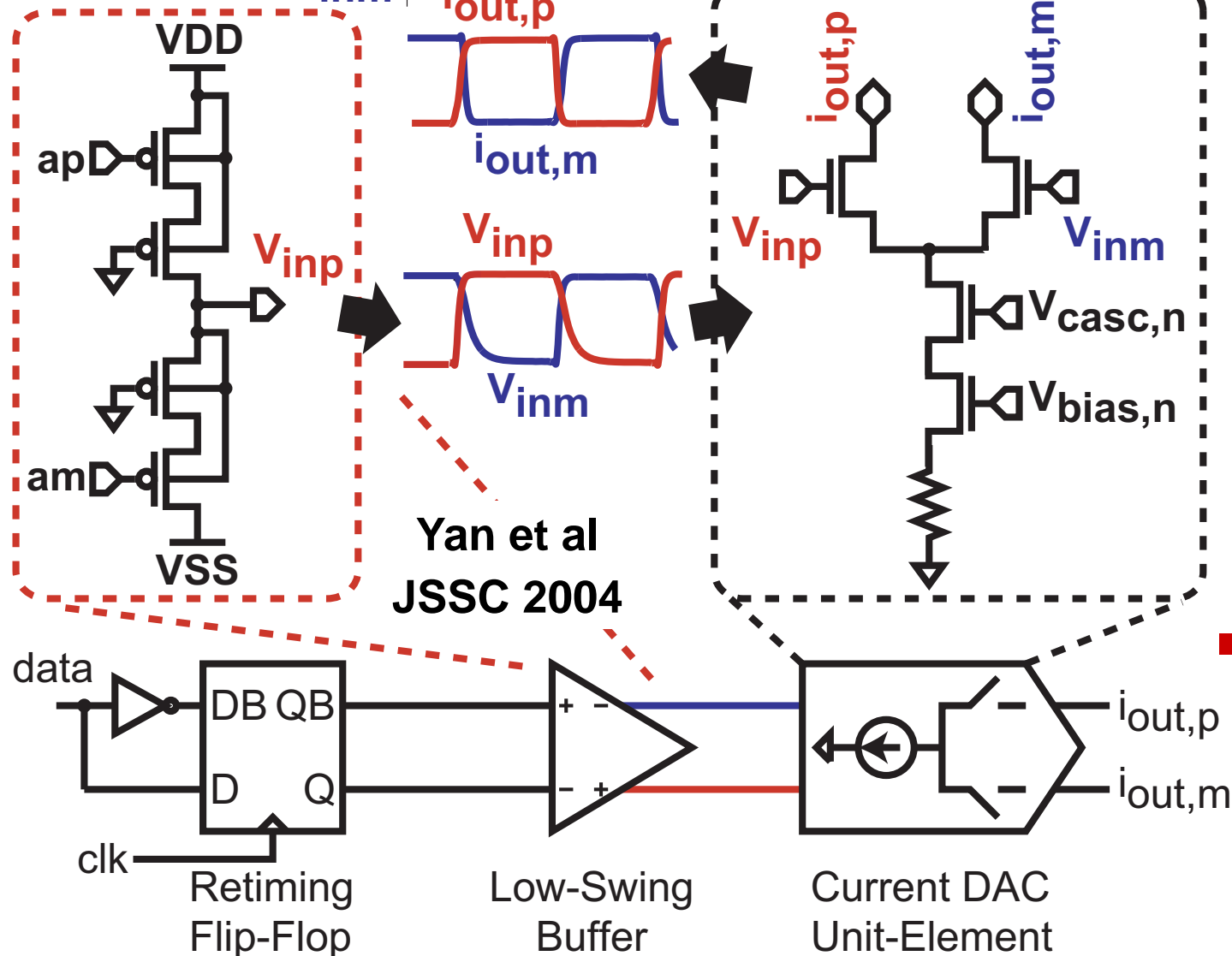


Low-swing buffers

- Keeps switch devices in saturation
- Fast “on”/Slow “off” reduces glitches at DAC output
- Uses external V_{dd}/V_{ss}


Resistor degeneration minimizes $1/f$ noise

Bit-Slice of Minor Loop RZ DAC

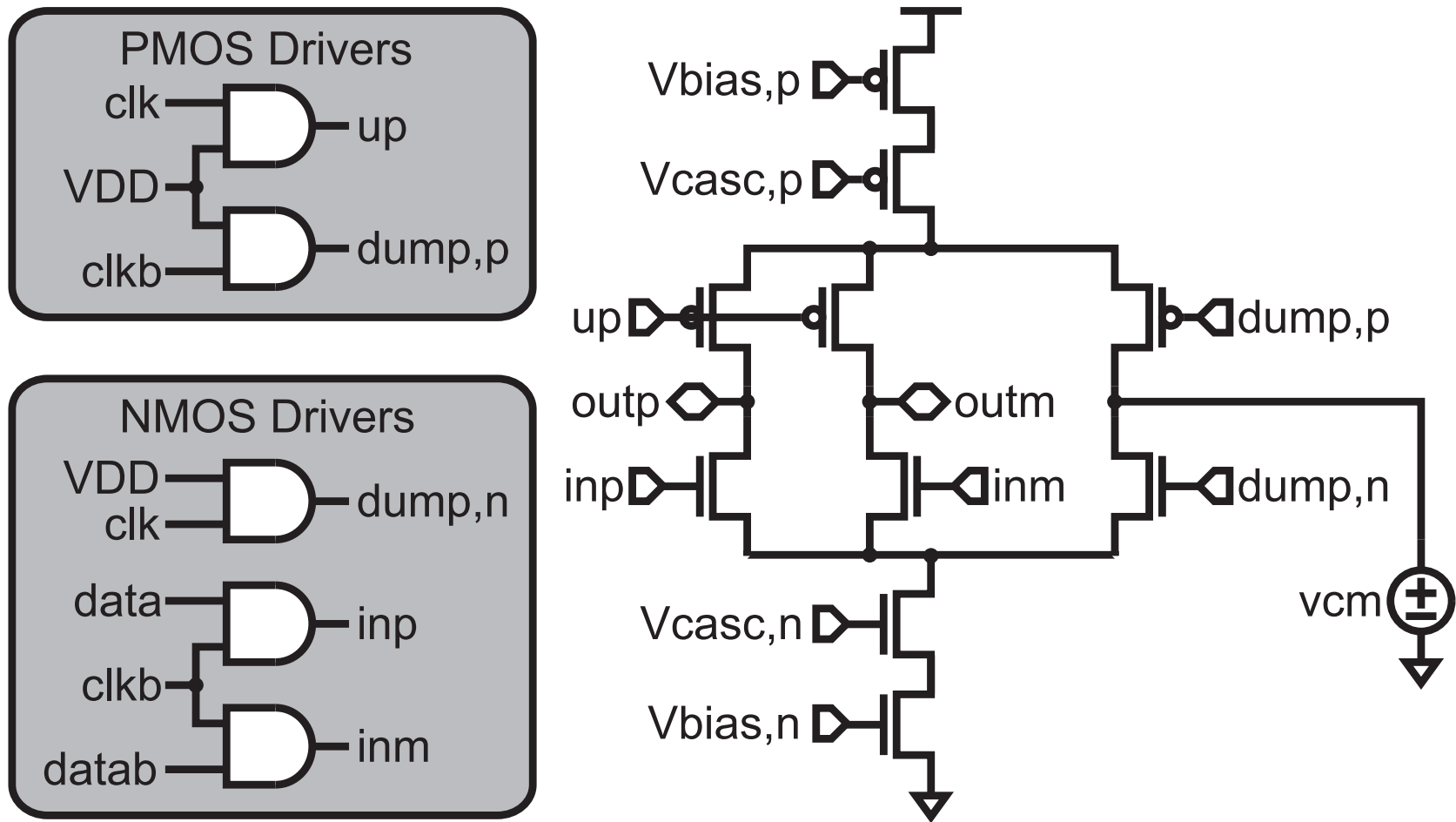

- **RZ DAC unit elements transition every sample period**
 - Breaks code-dependency of transient mismatch (ISI)
 - Uses full-swing logic signals for switching


Opamp Schematic

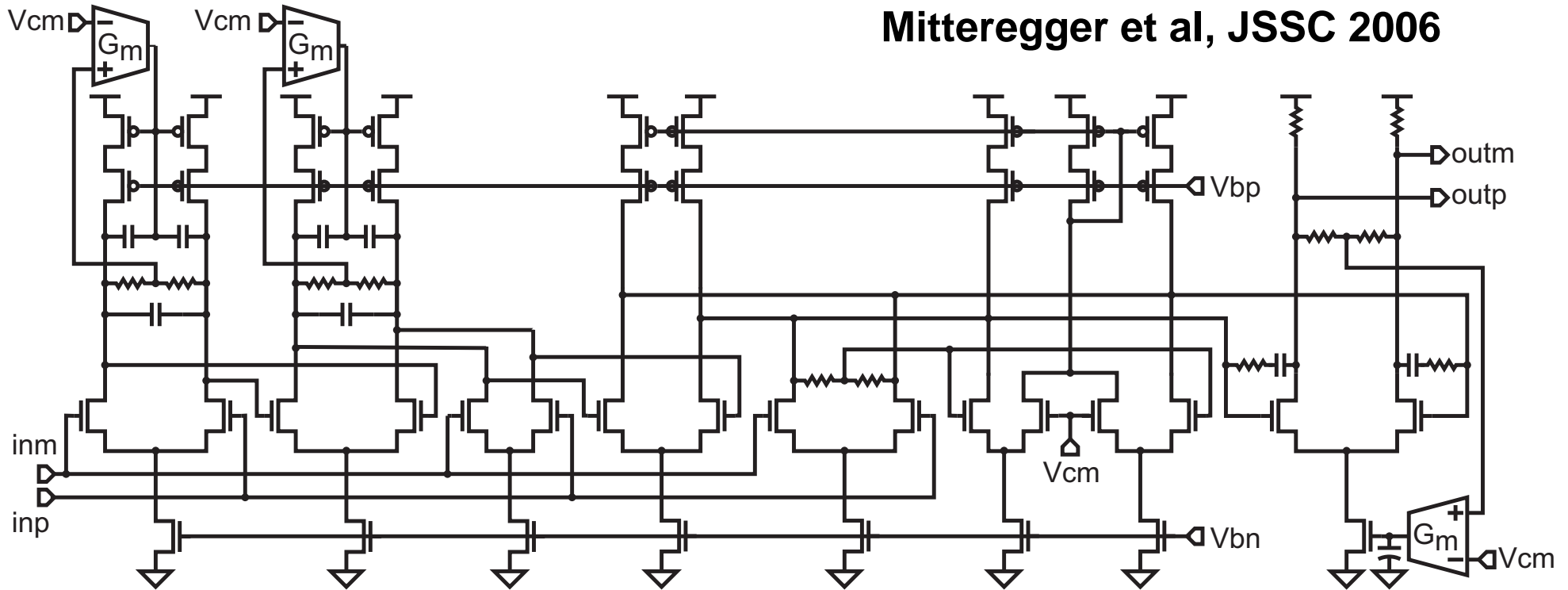

Parameter	Value
DC Gain	63 dB
Unity-Gain Frequency	4.0 GHz
Phase Margin	55°
Input Referred Noise Power (20 MHz BW)	11 μ V (rms)
Power ($V_{DD} = 1.5$ V)	22.5 mW

- **Modified nested Miller opamp**
 - 4 cascaded gain stages, 2 feedforward stages
 - Behaves as 2-stage Miller near cross-over frequencies
 - Opamp 1 power is 2X of opamps 2 and 3 (for low noise)


DEM Architecture (3-bit example)

 

- Achieves low-delay to allow 4-bit DEM at 900 MHz
 - ─ Delay is half a sample period


Die Photo (0.13u CMOS)

Die photo courtesy of Annie Wang (MTL)

 

- **Active area**
 - 0.45 mm²
- **Sampling Freq**
 - 900 MHz
- **Input BW**
 - 20 MHz
- **Supply Voltage**
 - 1.5 V
- **Analog Power**
 - 69 mW
- **Digital Power**
 - 18 mW


Measured Results

 

- **78 dB Peak SNDR performance in 20 MHz**
 - Bottleneck: transient mismatch from main feedback DAC
- **Architecture robust to VCO K_v non-linearity**

Figure of Merit: 330 fJ/Conv with 78 dB SNDR

 
Behavioral Model Reveals Key Performance Issue




- Amplifier nonlinearity degrades SNDR to 81 dB
- DAC transient mismatch degrades SNDR to 78 dB
 - DEM does not help this
 - Could be improved with dual RZ structure

Transient DAC mismatch is likely the key bottleneck

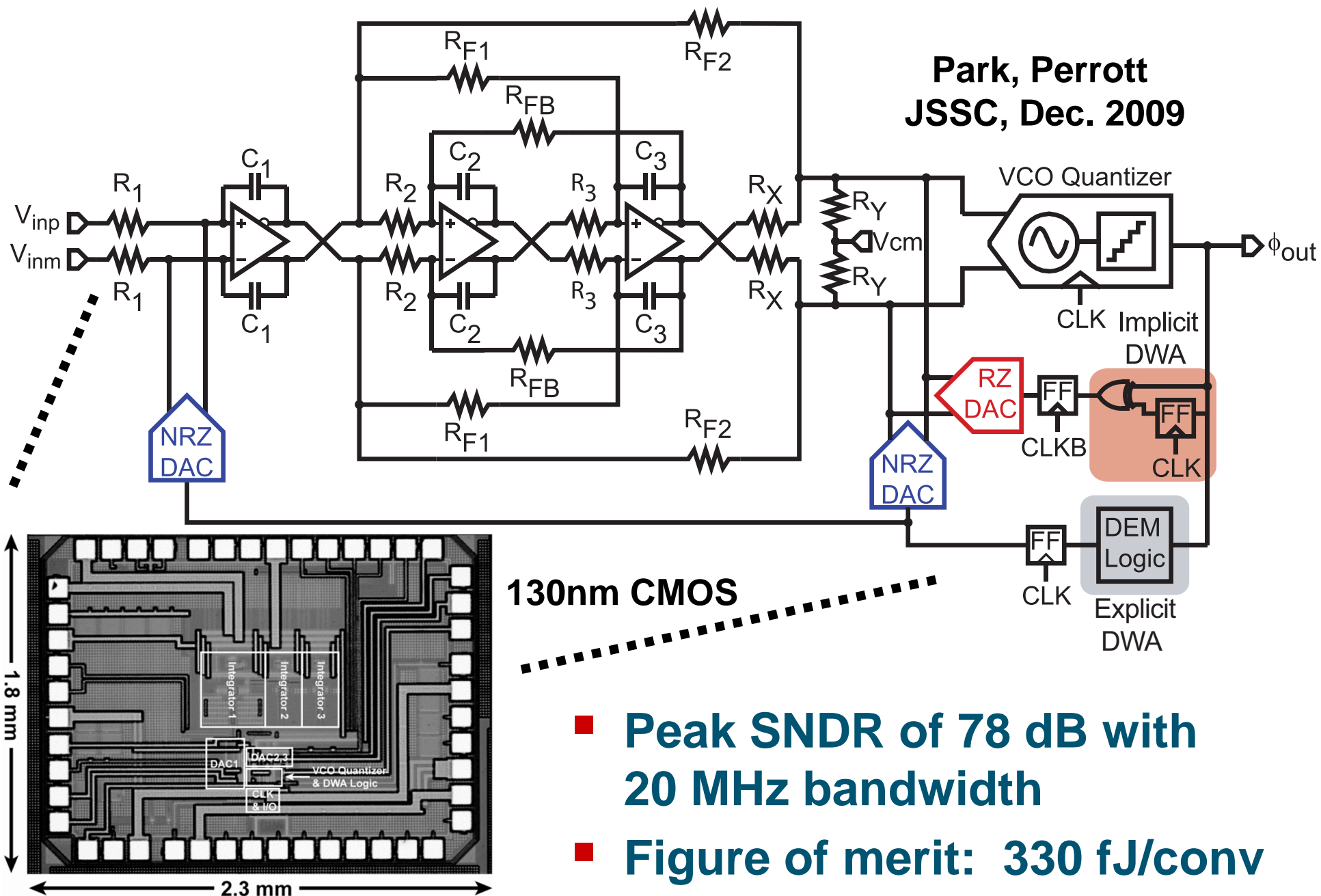Summary of Fourth Order CT Delta-Sigma ADC




Consider Time-to-Digital Conversion

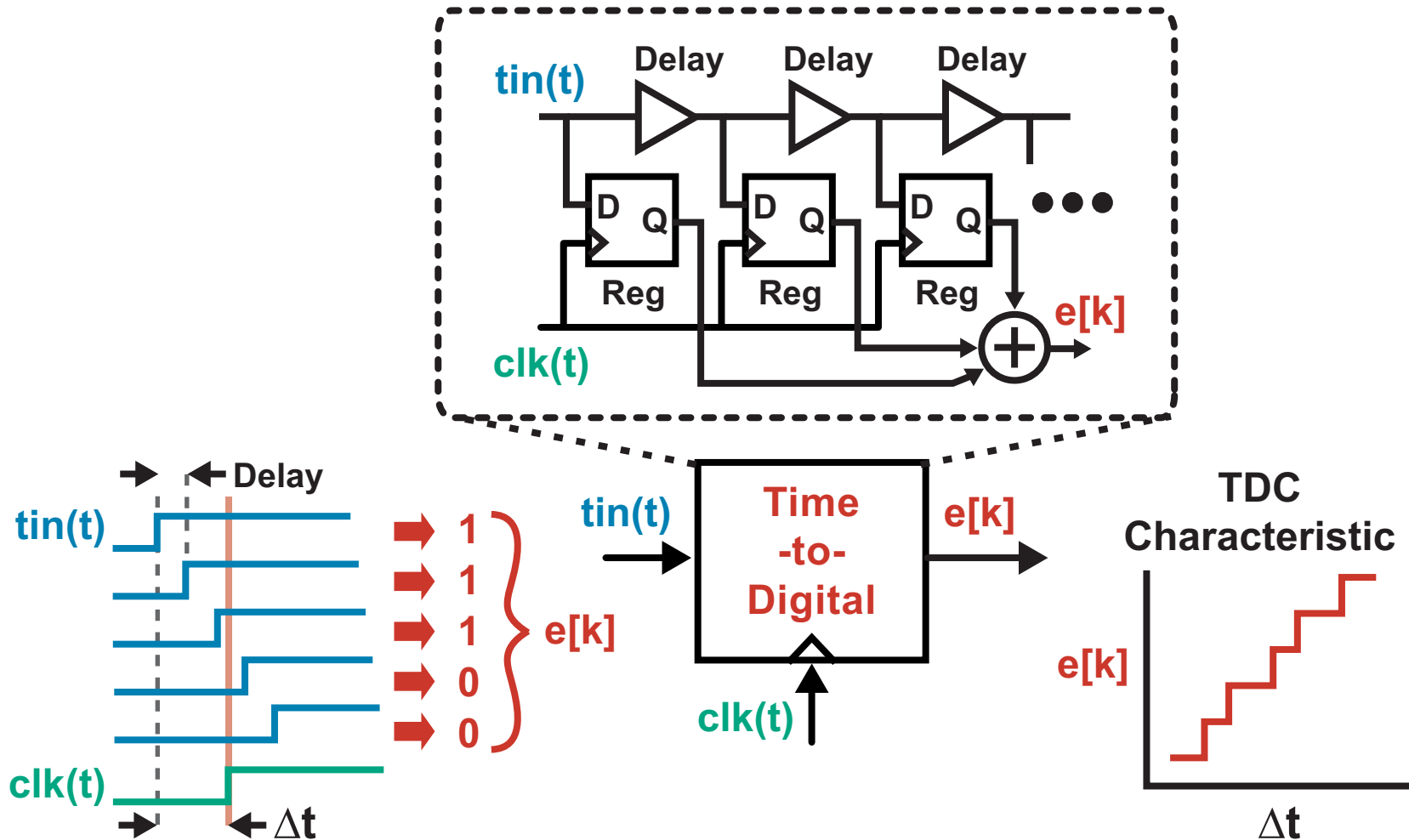

- Quantization in time achieved with purely digital gates
 - Easy implementation, resolution improving with Moore's law

How can we leverage this for quantizing an analog voltage?

Adding Voltage-to-Time Conversion

 


Naraghi, Courcy, Flynn, ISSCC 2009

- **Analog voltage is converted into edge times**
 - Time-to-digital converter then turns the edge times into digitized values
- **Key issues**
 - Non-uniform sampling
 - Noise, nonlinearity

Is there a simple implementation for the Voltage-to-Time Converter?





A Highly Digital Implementation

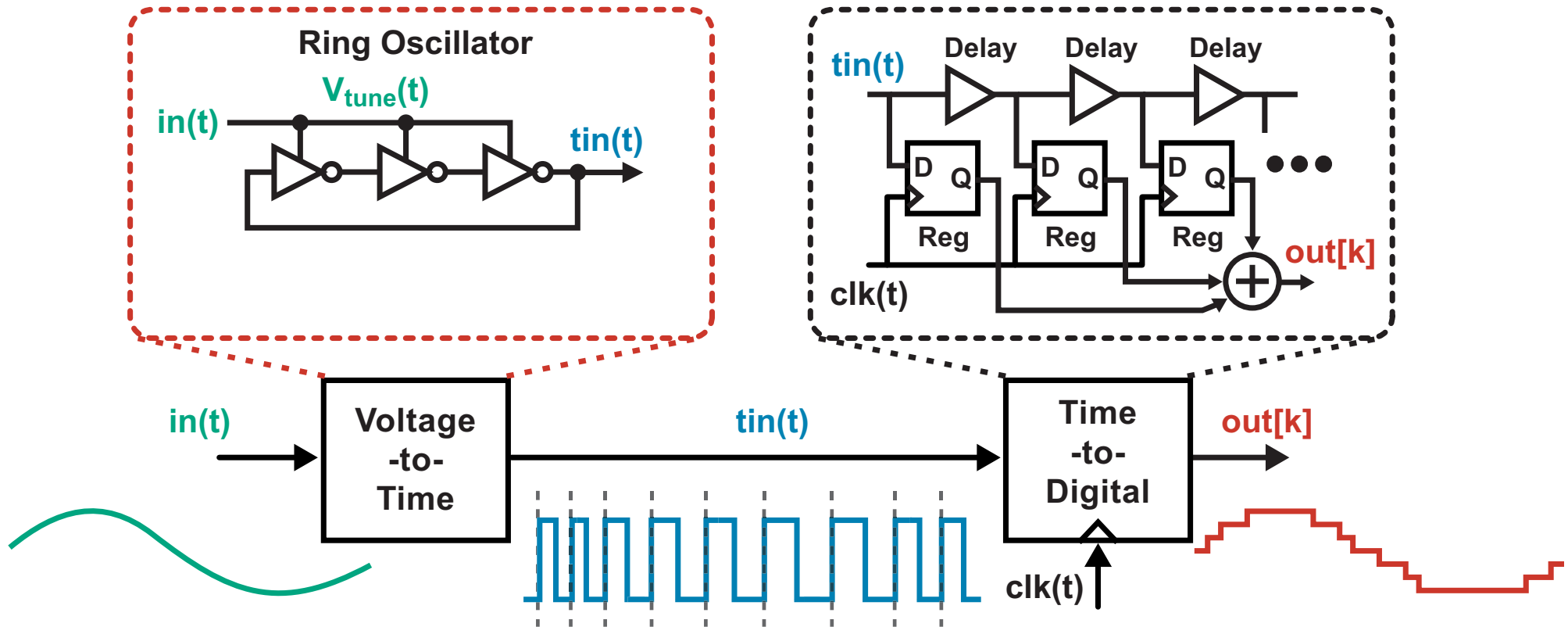

- A voltage-controlled ring oscillator offers a simple voltage-to-time structure
 - Non-uniform sampling is still an issue


We can further simplify this implementation and lower the impact of non-uniform sampling

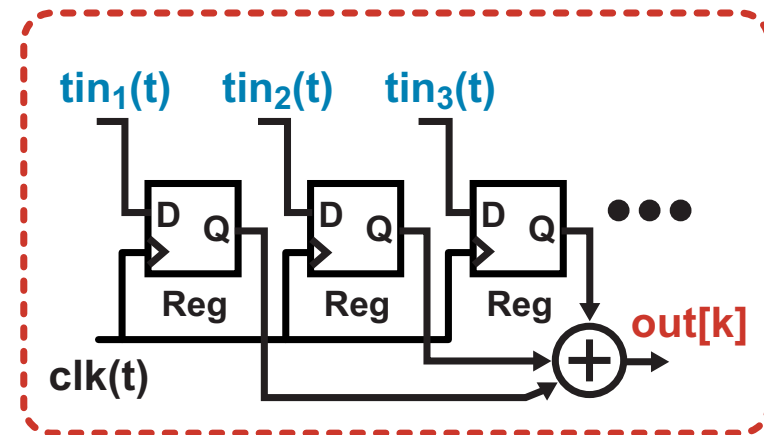   Making Use of the Ring Oscillator Delay Cells



- Utilize all ring oscillator outputs and remove TDC delays
 - Simpler implementation
- TDC output now samples/quantizes phase state of oscillator


Improved Non-Uniform Sampling Behavior

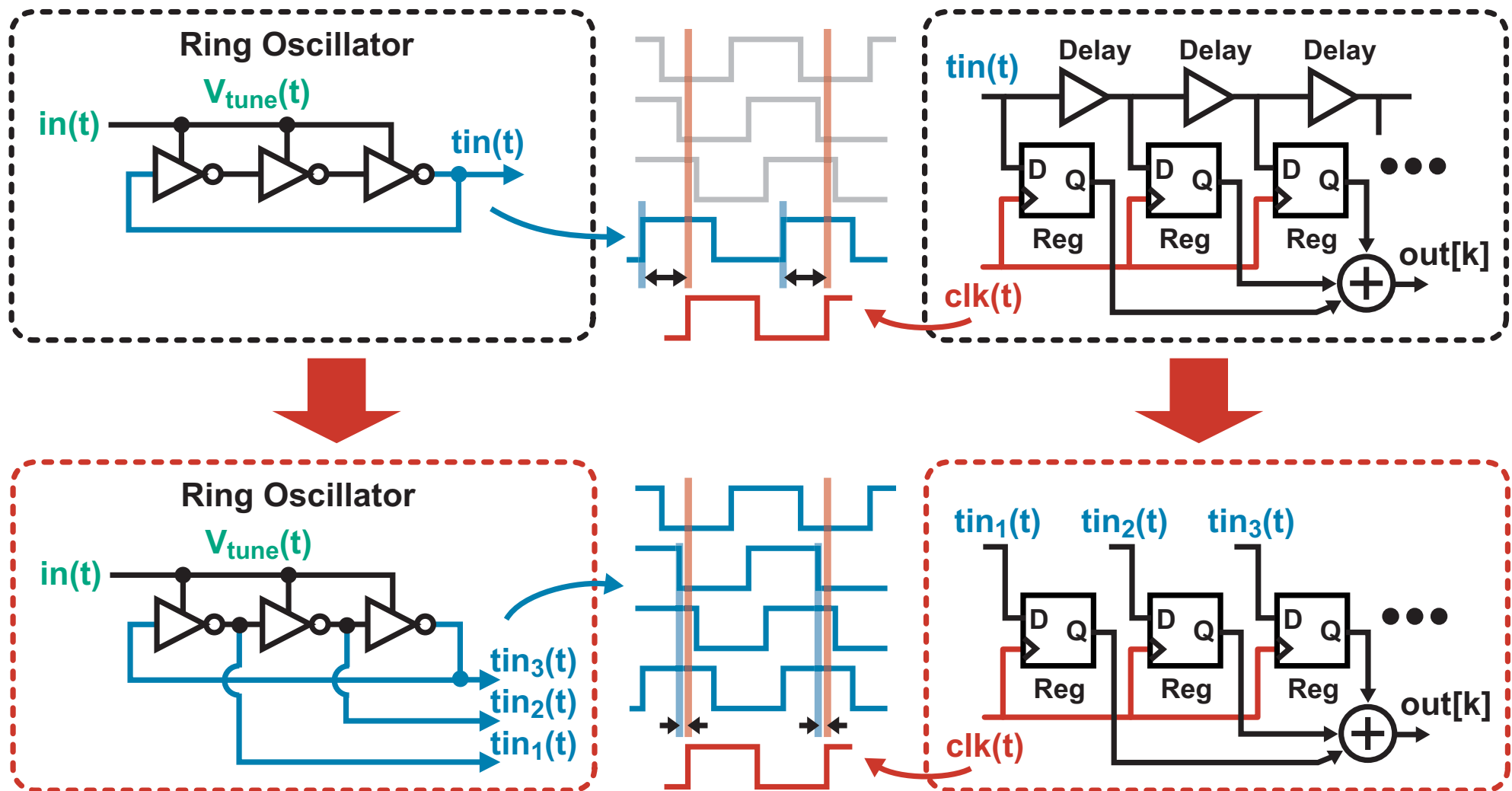

- Oscillator edges correspond to a sample window of the input
- Sampling the oscillator phase state yields sample windows that are much more closely aligned to the TDC clk


Key Observation

 - The VCO-Based ADC provides an excellent vehicle for using a conventional TDC for analog-to-digital conversion
 - Efficiently combines voltage-to-time and time-to-digital conversion
 - Minimizes issue of non-uniform sampling



VCO-based ADCs are very efficient “time-based” circuits


Some Other VCO-based ADC Approaches

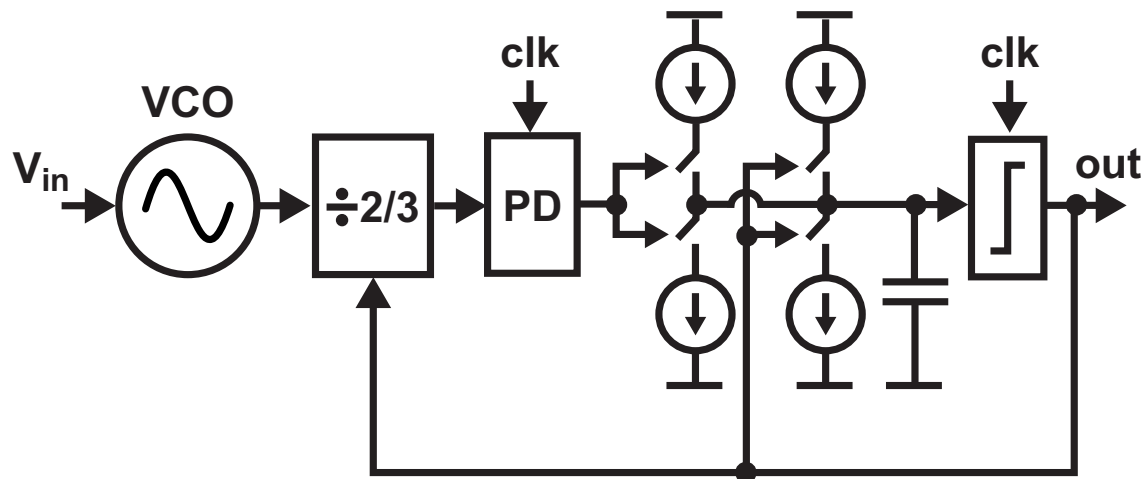


Park, Perrott
ISCAS 2009

Yoon, Kim, Jang, Cho
TCAS1 Dec 2008

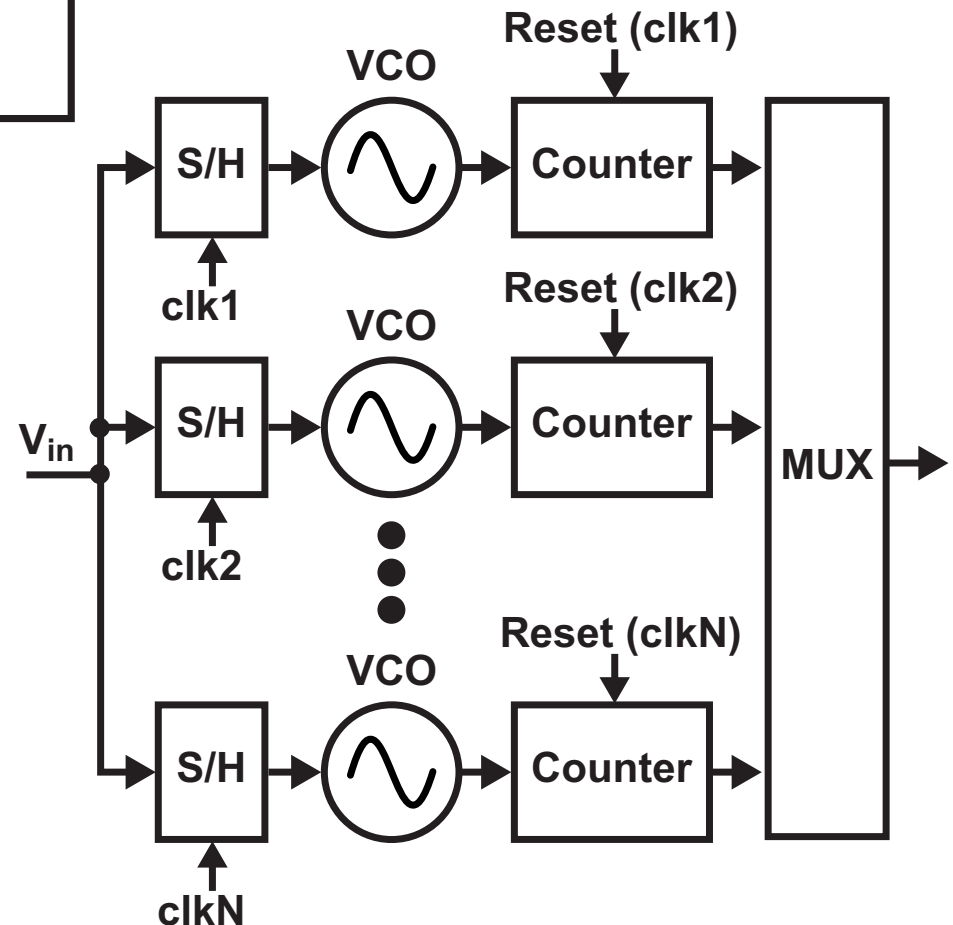- Increase noise shaping to second order by adding frequency divider and charge pumps
- Use interleaved VCO quantizers to create bandpass ADC




Recent Performance of VCO-Based ADCs

 

Approaching 100fJ/conv-step at 78dB SNDR

A Simple Interface Between Analog and Digital

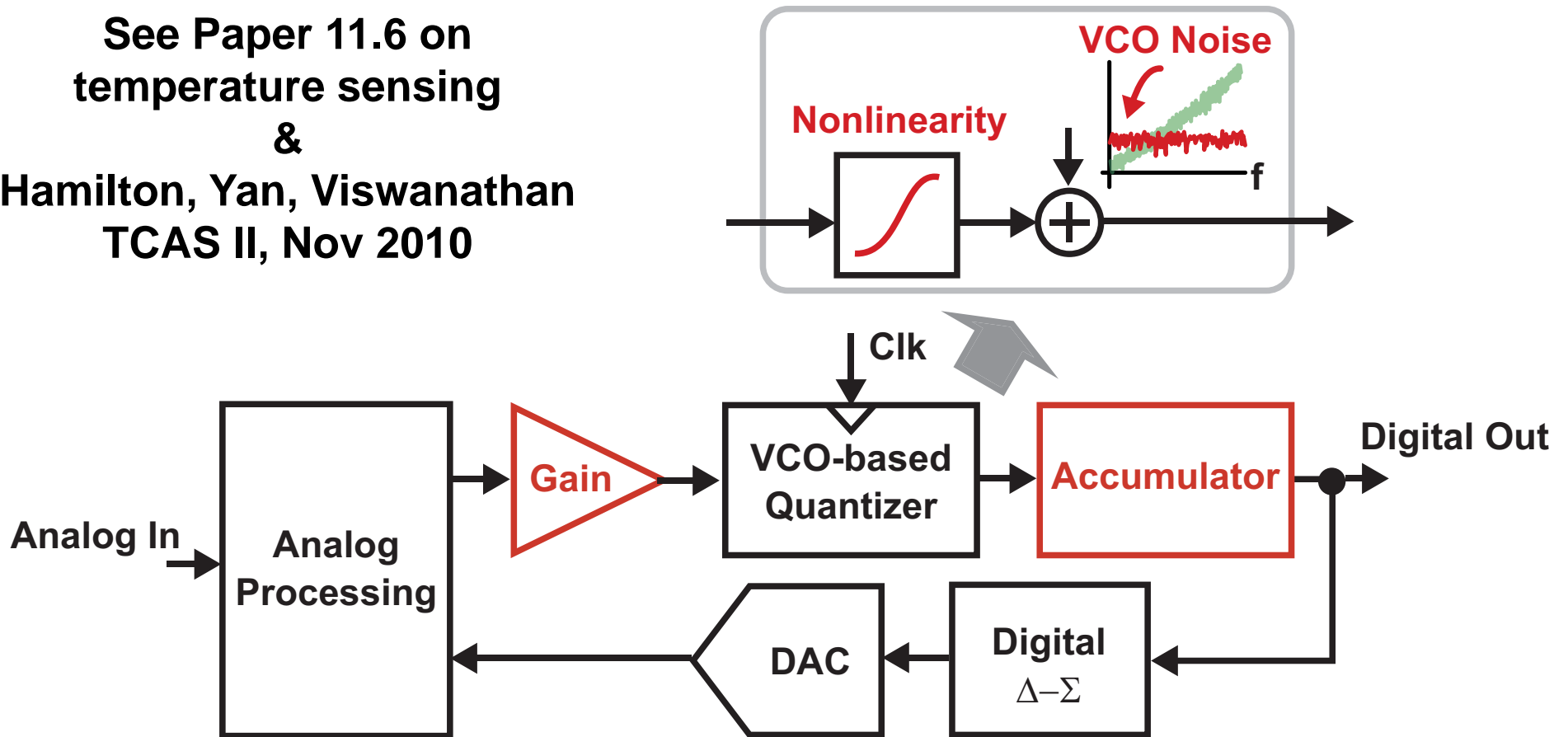See Paper 11.6 on
temperature sensing
&
Hamilton, Yan, Viswanathan
TCAS II, Nov 2010



- Accumulator reduces impact of nonlinearity
- Gain reduces impact of VCO phase noise

Plays well to the strengths and weaknesses of
VCO-based quantizers

Conclusion on VCO-Based Quantizers

- **Leverage Moore's law**
 - Consist of ring oscillator(s) and digital logic
 - Improved speed, power, area with advanced CMOS
- **Are relatively easy to design**
 - First order shaping of quantization noise and mismatch
 - Infinite DC gain when used as an integrator
- **Have shortcomings that can be overcome**
 - Nonlinearity: utilize calibration or feedback
 - VCO phase noise: utilize feedback

**Performance is now at state of the art at 78dB SNDR
and improving steadily**