

# Non-Foster Reactances for Electrically- Small Antennas, High-Impedance Surfaces, and Engineered Materials

James T. Aberle

Associate Professor of Electrical Engineering  
School of Electrical, Computer and Energy Engineering  
Arizona State University

# Outline of Presentation

- What Does “Non-Foster” Mean?
- Possible Applications of Non-Foster Reactances
  - Electrically Small Antennas
  - High-Impedance Surfaces
  - Artificial High-Permeability Materials
- Realization of Non-Foster Reactances

# Outline of Presentation

- **What Does “Non-Foster” Mean?**
- Possible Applications of Non-Foster Reactances
  - Electrically Small Antennas
  - High-Impedance Surfaces
  - Artificial High-Permeability Materials
- Realization of Non-Foster Reactances




# Foster's Reactance Theorem

- The theorem is a consequence of conservation of energy.
- The slope of the input reactance (susceptance) of a lossless passive one-port is always positive.
- All zeros and poles of the impedance (admittance) function are simple, and a zero must lie between any two poles, and a pole between any two zeros.




# Consequences of Foster's Reactance Theorem

- Impedances (admittances) of passive one-port networks rotate clockwise on the Smith Chart as frequency increases.
- There is no such thing as a negative capacitor or a negative inductor (for passive circuits).

# Foster Network

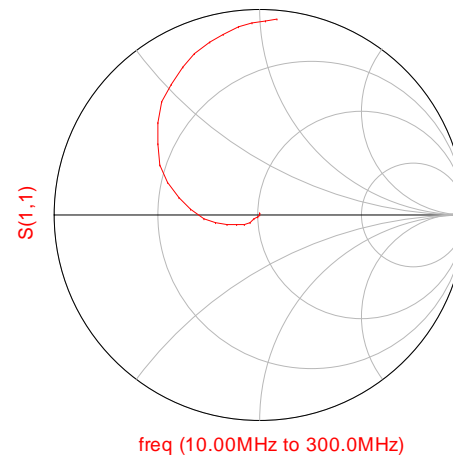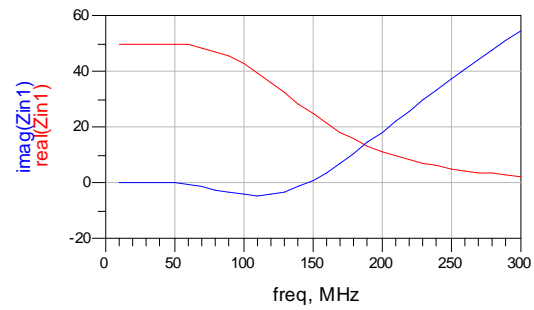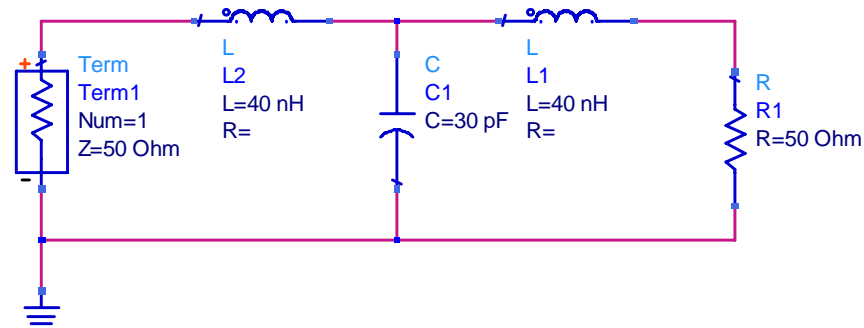

# Non-Foster Network

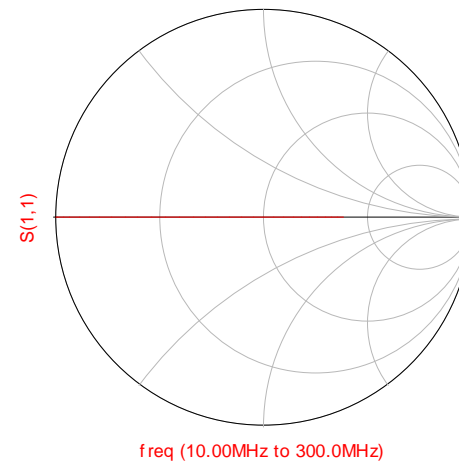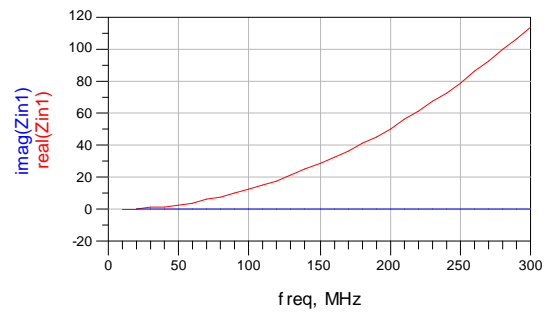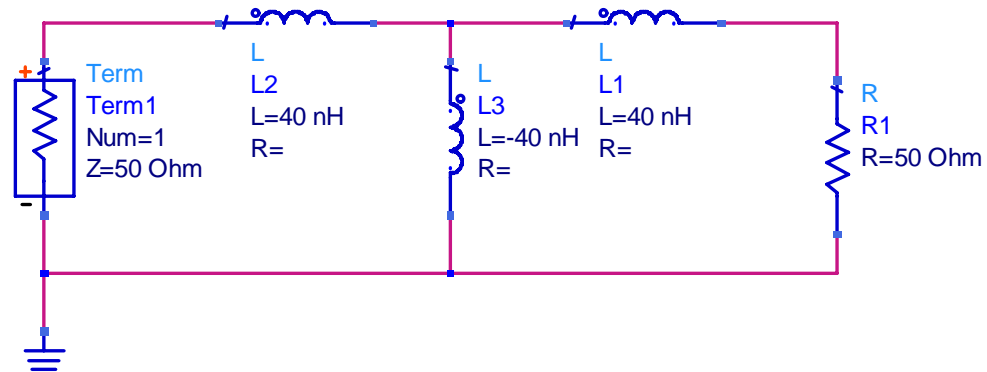


# Outline of Presentation

- What Does “Non-Foster” Mean?
- Possible Applications of Non-Foster Reactances
  - **Electrically Small Antennas**
  - High-Impedance Surfaces
  - Artificial High-Permeability Materials
- Realization of Non-Foster Reactances





# VHF Whip: A Canonical ESA

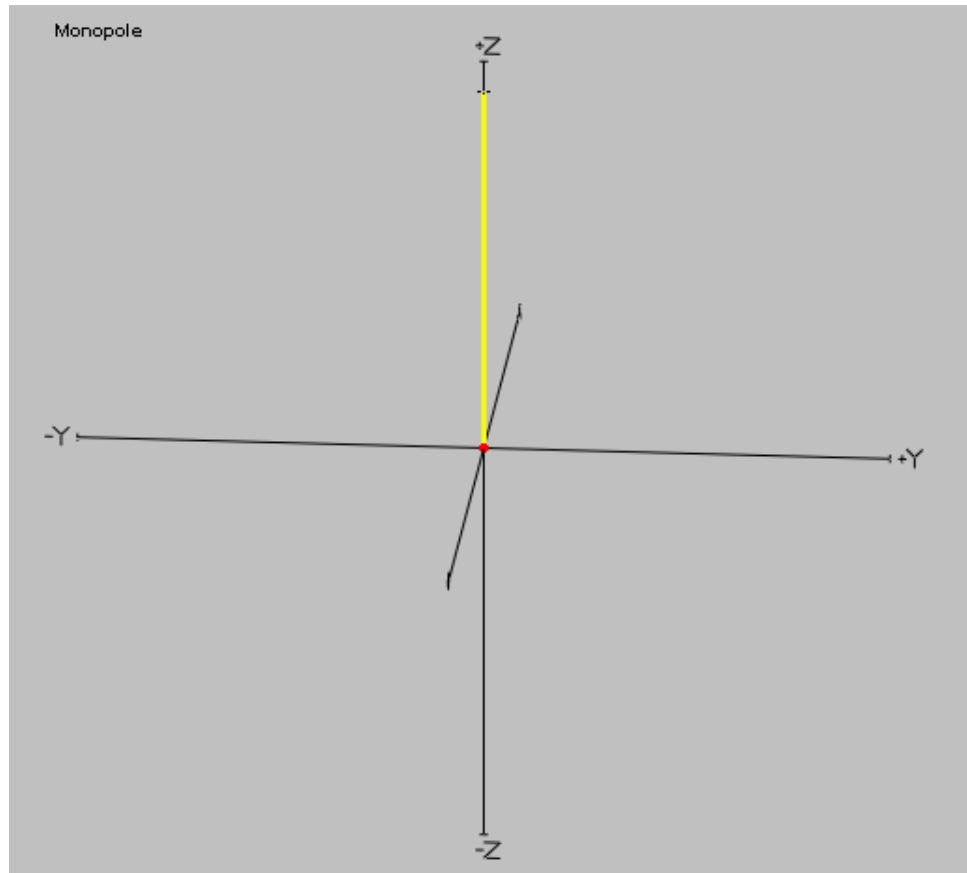

- Geometry of monopole antenna as modeled in **Antenna Model** software. The monopole is a copper cylinder 0.6 meters in length and 0.010 meters in diameter, mounted on an infinite perfect ground plane.
- Frequency range is 30 to 90 MHz.

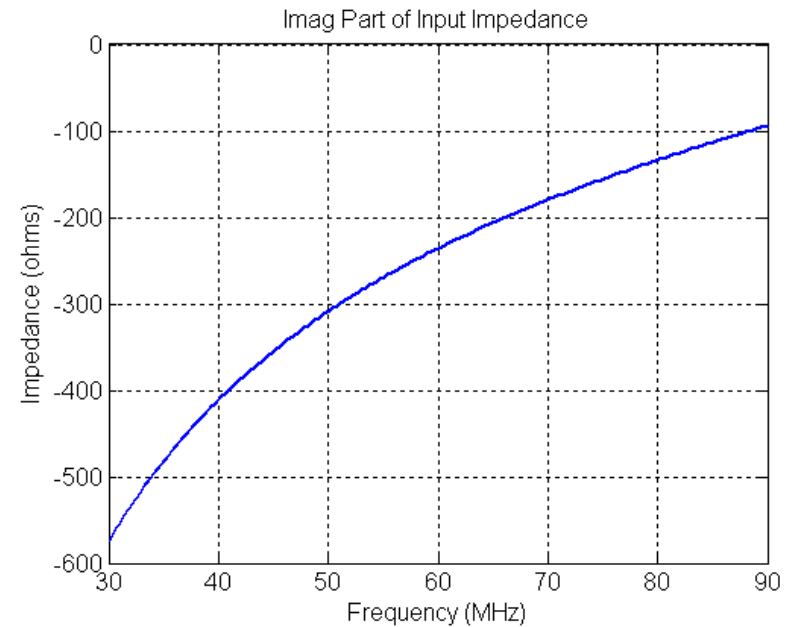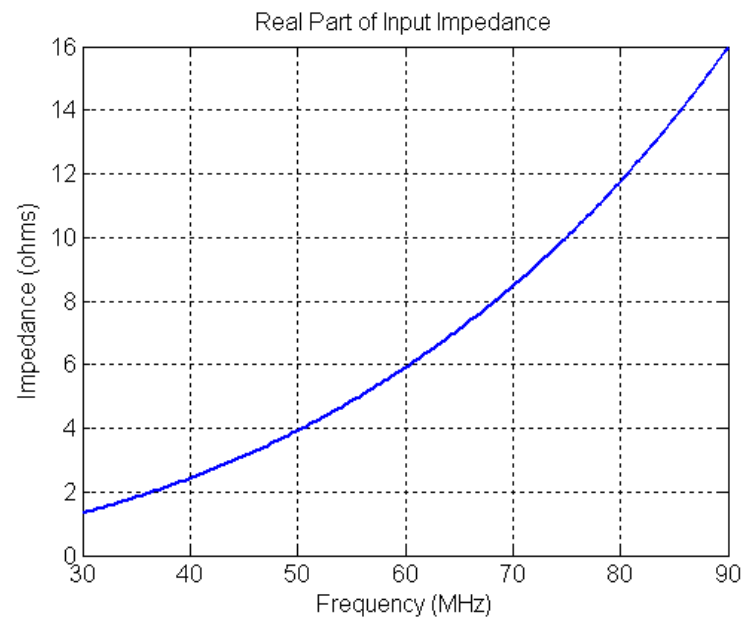
# Input Impedance of VHF Whip From Simulation



# Two Tools to Help With Analysis

- Exact *two-port* representation of antenna in frequency domain in terms of s-parameters.
- Approximate lumped equivalent circuit model of antenna over frequency range of interest.

# Two-Port Representation of Antenna

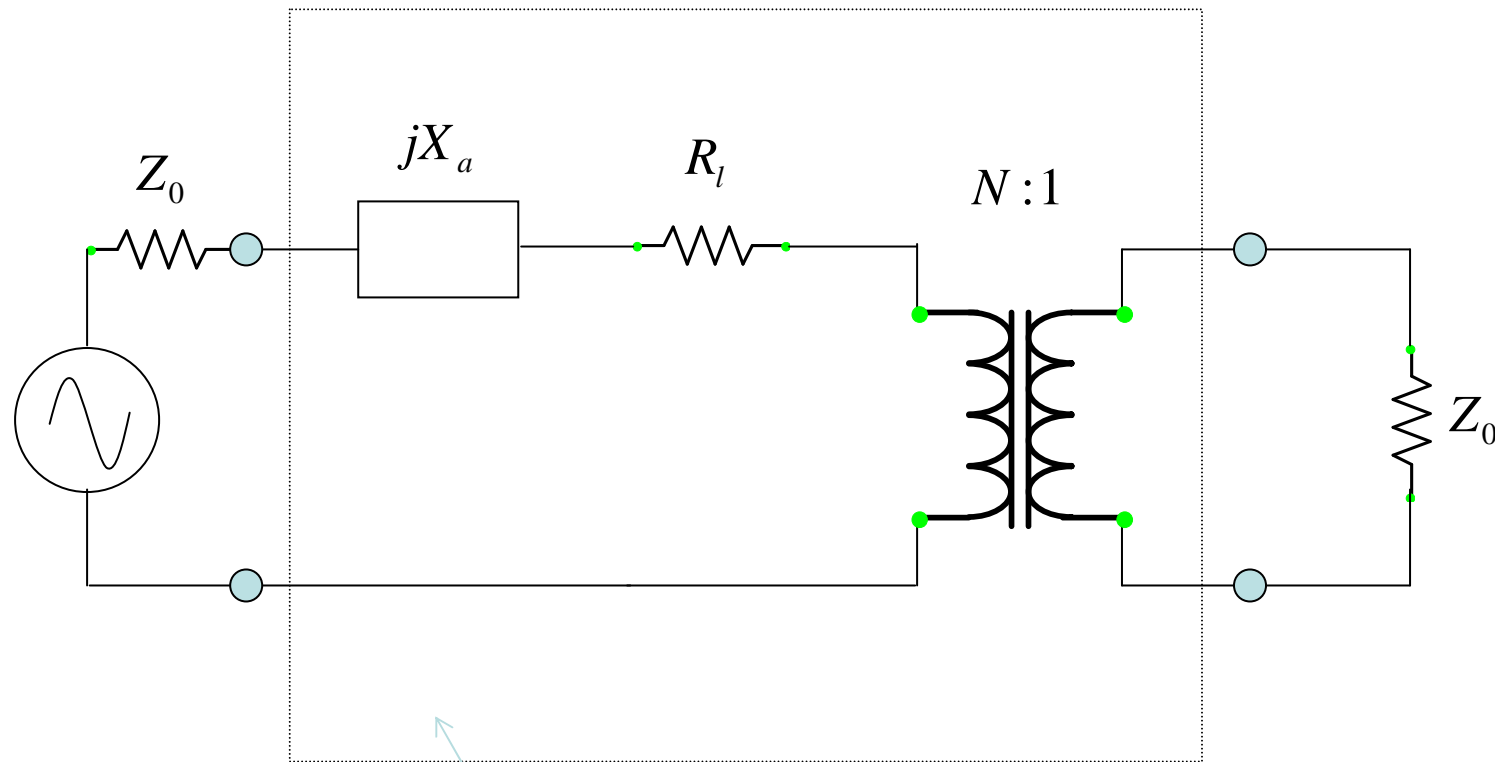

The quantities in this box are re-evaluated at every frequency for which we have data.

# Two-Port Representation of Antenna

$$Z_a = R_a + jX_a = R_r + R_l + jX_a$$

$$R_r = e_{cd} R_a = \text{radiation resistance}$$

$$R_l = (1 - e_{cd}) R_a = \text{dissipative loss resistance}$$

$$X_a = \text{antenna reactance}$$

$$N = \sqrt{\frac{R_r}{Z_0}}$$

# Two-Port Representation of Antenna

- Antenna impedance and radiation efficiency are used to produce a Touchstone \*.s2p file for use in circuit simulation – the exact two-port representation of the antenna at each frequency for which we have data.
- Allows concepts like transducer power gain and stability measures to be applied to antennas. The latter being particularly important for considering the use of non-Foster reactances in antenna matching networks.

## Approximate Equivalent Circuit of the Antenna

- To model the antenna, we assume that the real part of the antenna impedance varies as the square of frequency, and the imaginary part behaves as a series LC.

$$\bar{Z}_a = R_0 \left( \frac{\omega}{\omega_0} \right)^2 + j \left( \omega L_a - \frac{1}{\omega C_a} \right)$$

Impedance produced by equivalent circuit

## Approximate Equivalent Circuit of the Antenna

- Evaluation of the model parameters ( $R_0$ ,  $L_a$  and  $C_a$ ):

$$R_0 = \Re\{Z_a(\omega_0)\}$$

$$\begin{bmatrix} \omega_1 & \frac{-1}{\omega_1} \\ \omega_2 & \frac{-1}{\omega_2} \end{bmatrix} \begin{Bmatrix} L_a \\ \frac{1}{C_a} \end{Bmatrix} = \begin{Bmatrix} \Im\{Z_a(\omega_1)\} \\ \Im\{Z_a(\omega_2)\} \end{Bmatrix}$$






# Approximate Equivalent Circuit of the Antenna


$$R_0 = 4.30 \Omega$$

$$L_a = 194 \text{ nH}$$

$$C_a = 8.69 \text{ pF}$$

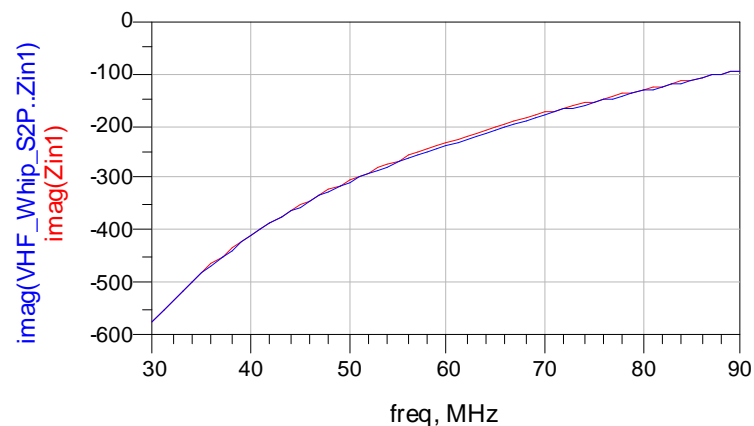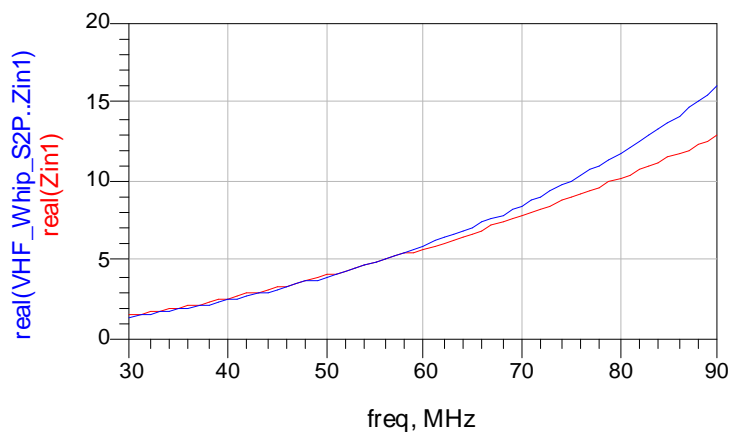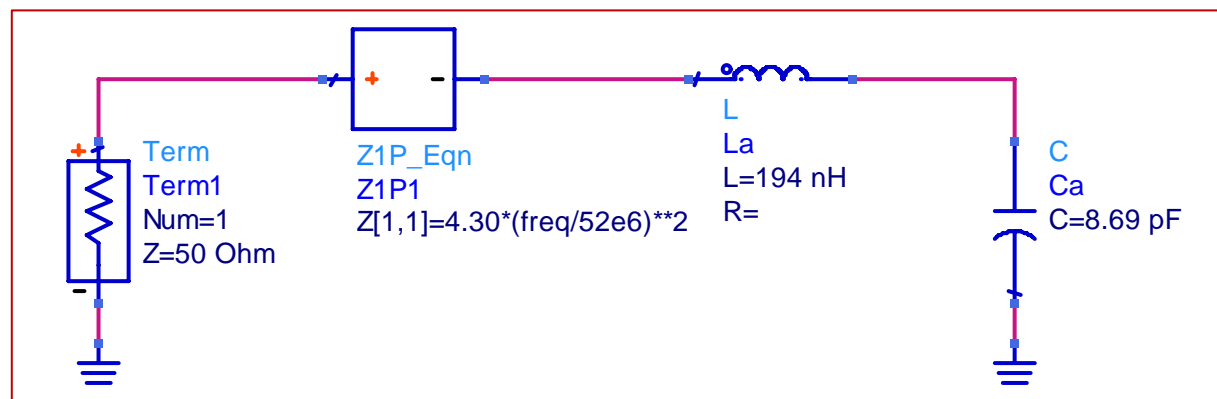

# Matching Network Concept

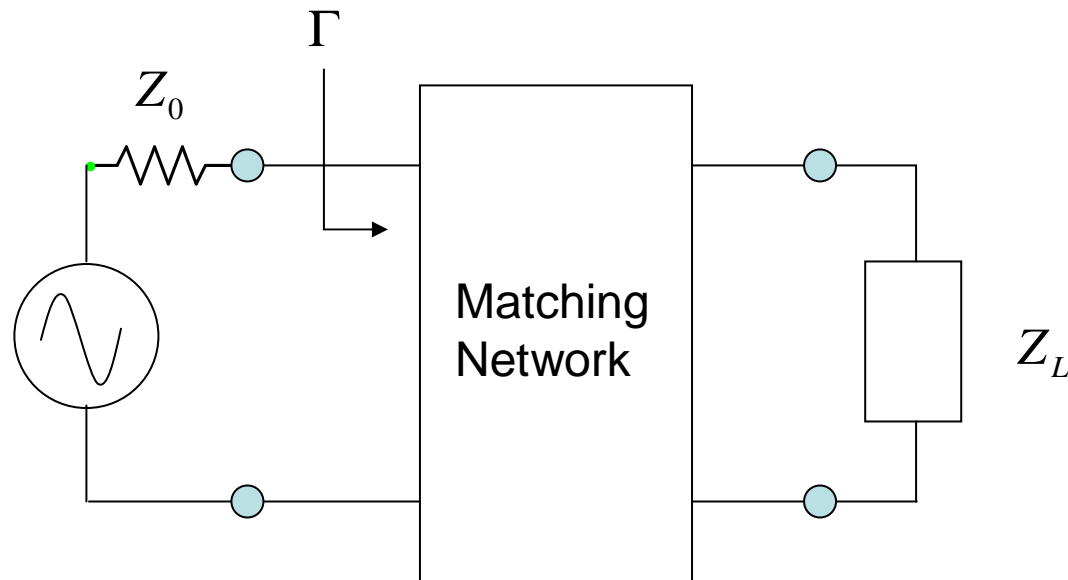

# Points to Consider

- A real passive matching network can only approach and never exceed the performance predicted by the Bode-Fano criterion.
- The matchable bandwidth is limited by the  $Q$  of the load.
- The matchable bandwidth can only be increased by de-Qing the load – that is by intentional introduction of dissipative losses into the matching network – and concomitant reduction in radiation efficiency.

# Bode-Fano Criterion

$$\frac{\Delta f}{f_0} \leq \frac{\pi}{Q \cdot \ln\left(\frac{1}{\Gamma_m}\right)}$$


Maximum allowable reflection coefficient

$Q$  of the load

Maximum value of fractional bandwidth that can be achieved with any passive, lossless matching network.


$$Q = 81.9, \Gamma_m = \frac{1}{3} \Rightarrow \frac{\Delta f}{f_0} \leq 0.035$$

# Single-Tuned Mid-band Match

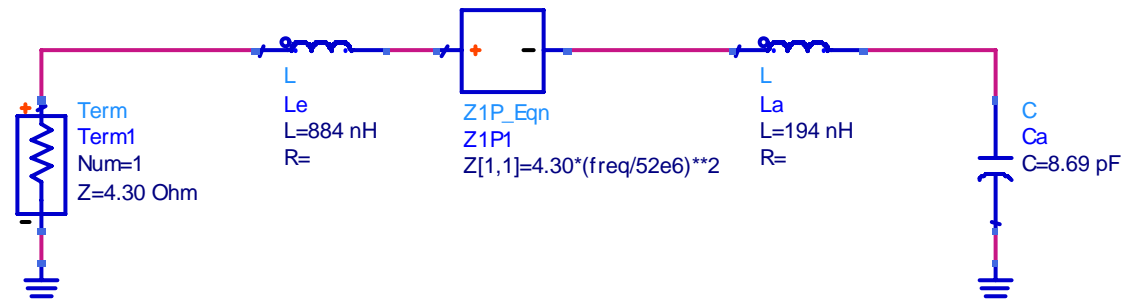

m1  
freq=51.80MHz  
S(1,1)=-10.409 / -73.141  
impedance = Z0 \* (0.992 - j0.630)

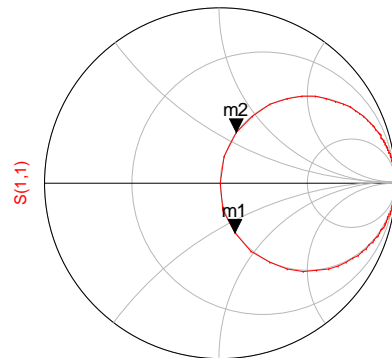m2  
freq=52.20MHz  
S(1,1)=-10.477 / 71.883  
impedance = Z0 \* (1.008 + j0.630)




freq (30.00MHz to 90.00MHz)

$$\frac{\Delta f}{f_0} \approx \frac{52.2 - 51.8}{52} = 0.008$$


Analytical:  $\frac{\Delta f}{f_0} = \frac{1}{\sqrt{2Q}} = 0.009$

# Wheeler-Lopez Double-Tuned Matching

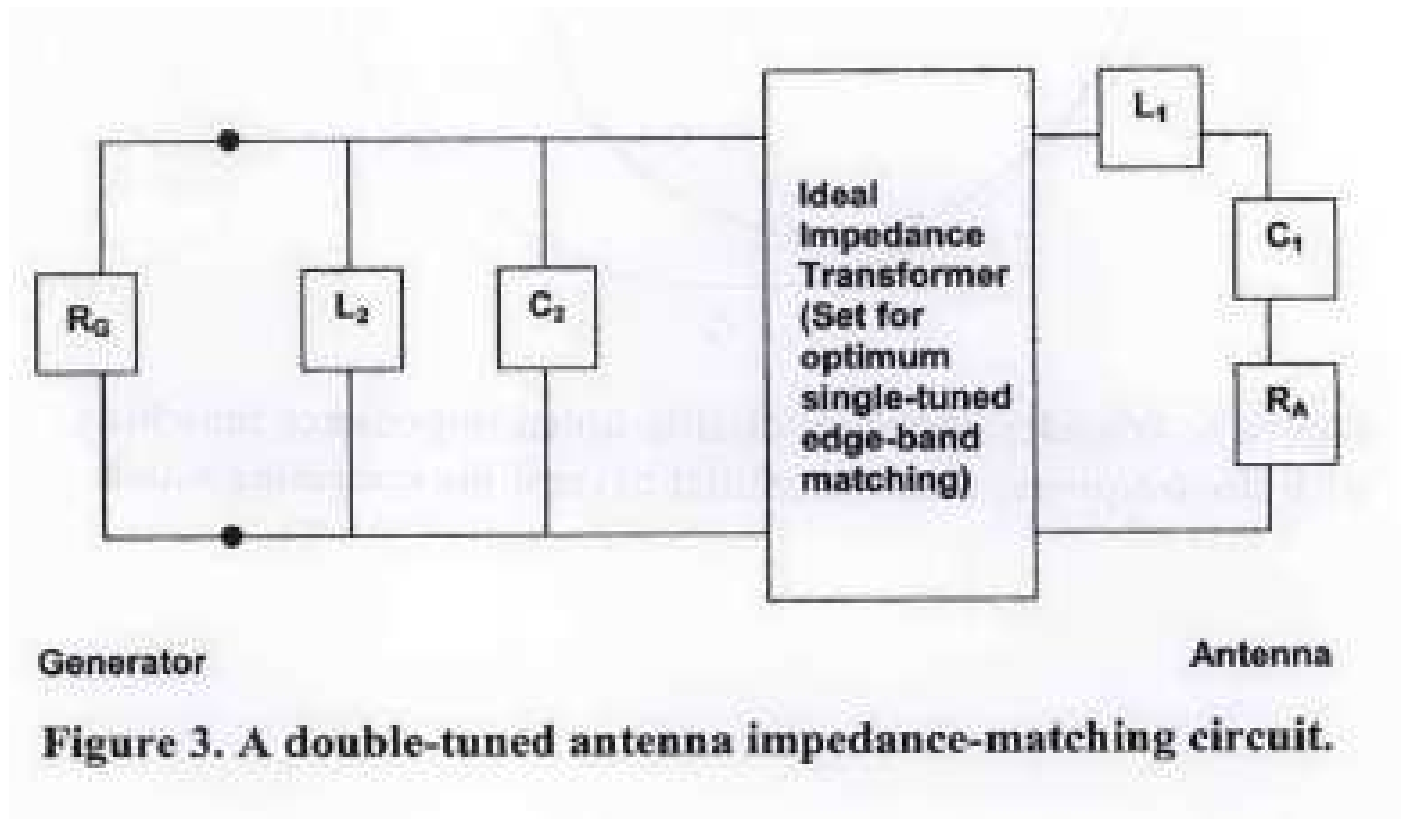



A.R. Lopez, "Wheeler and Fano Impedance Matching", *IEEE Antennas and Propagation Magazine*, Vol. 49, No. 4, August 2007

# Wheeler-Lopez Double-Tuned Matching


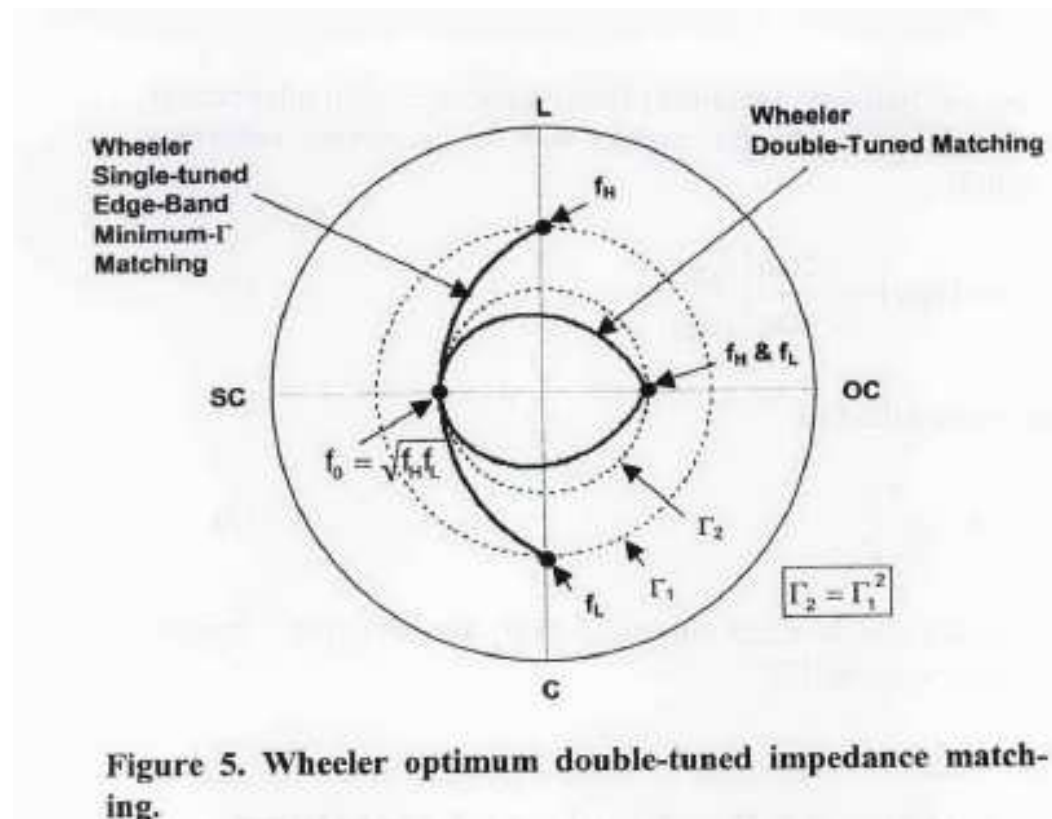


A.R. Lopez, "Wheeler and Fano Impedance Matching", *IEEE Antennas and Propagation Magazine*, Vol. 49, No. 4, August 2007
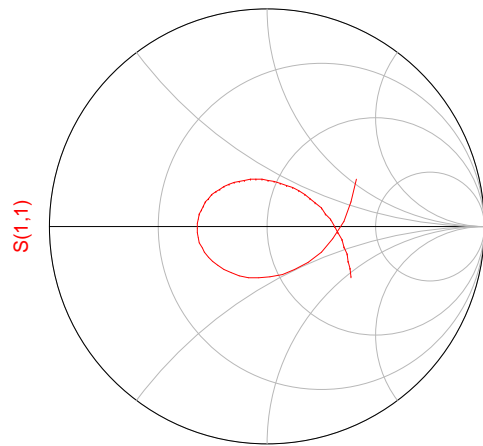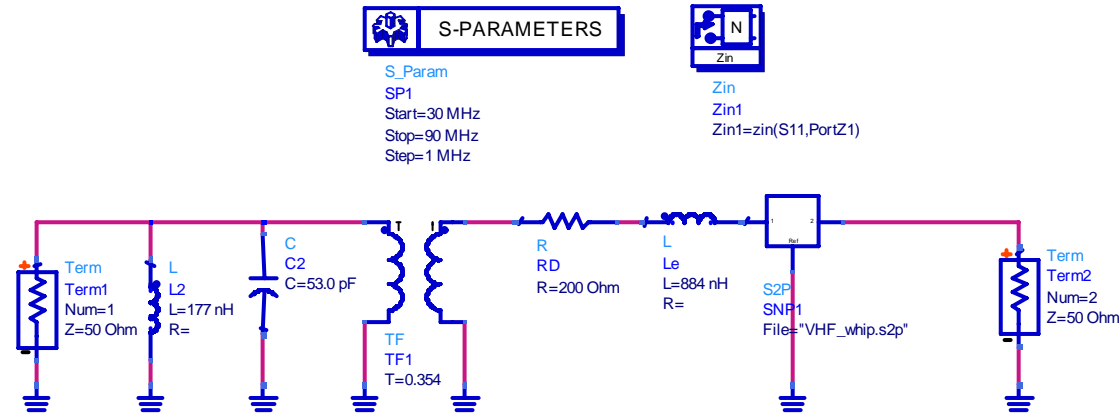
# Wheeler-Lopez Double-Tuned Matching with Antenna De-Qing




freq (30.00MHz to 90.00MHz)

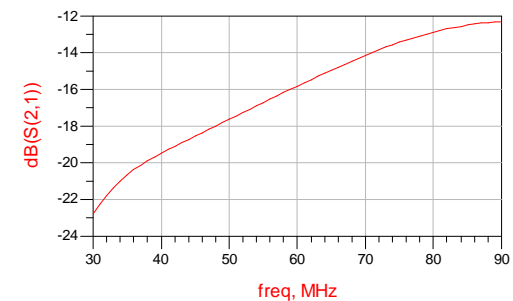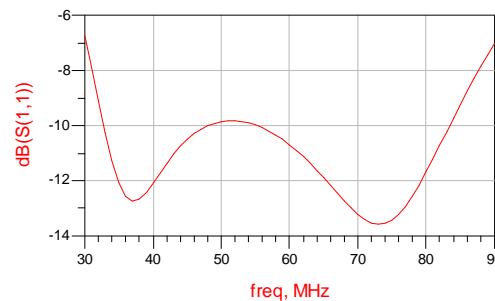

Decent match, poor efficiency


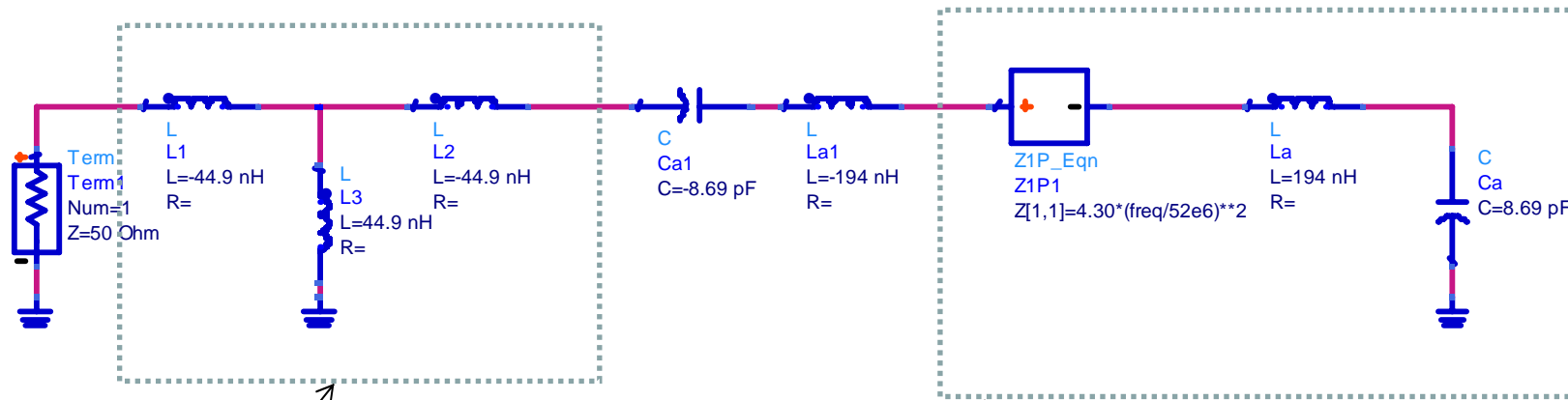
# Matching Network with Non-Foster Reactances




Dualizer


Antenna

*Cancel frequency squared dependence of radiation resistance.*





Van Der Pol, Proc, IRE, Feb. 1930

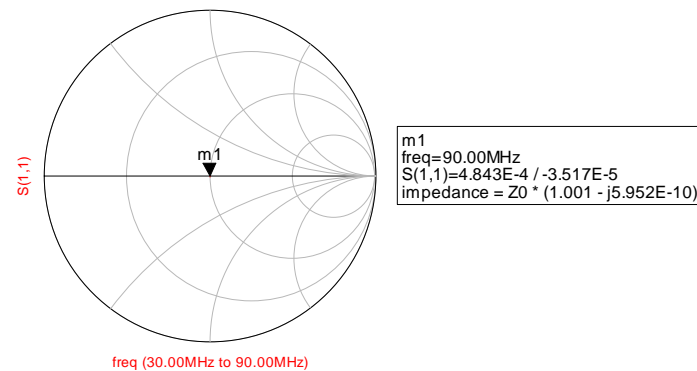
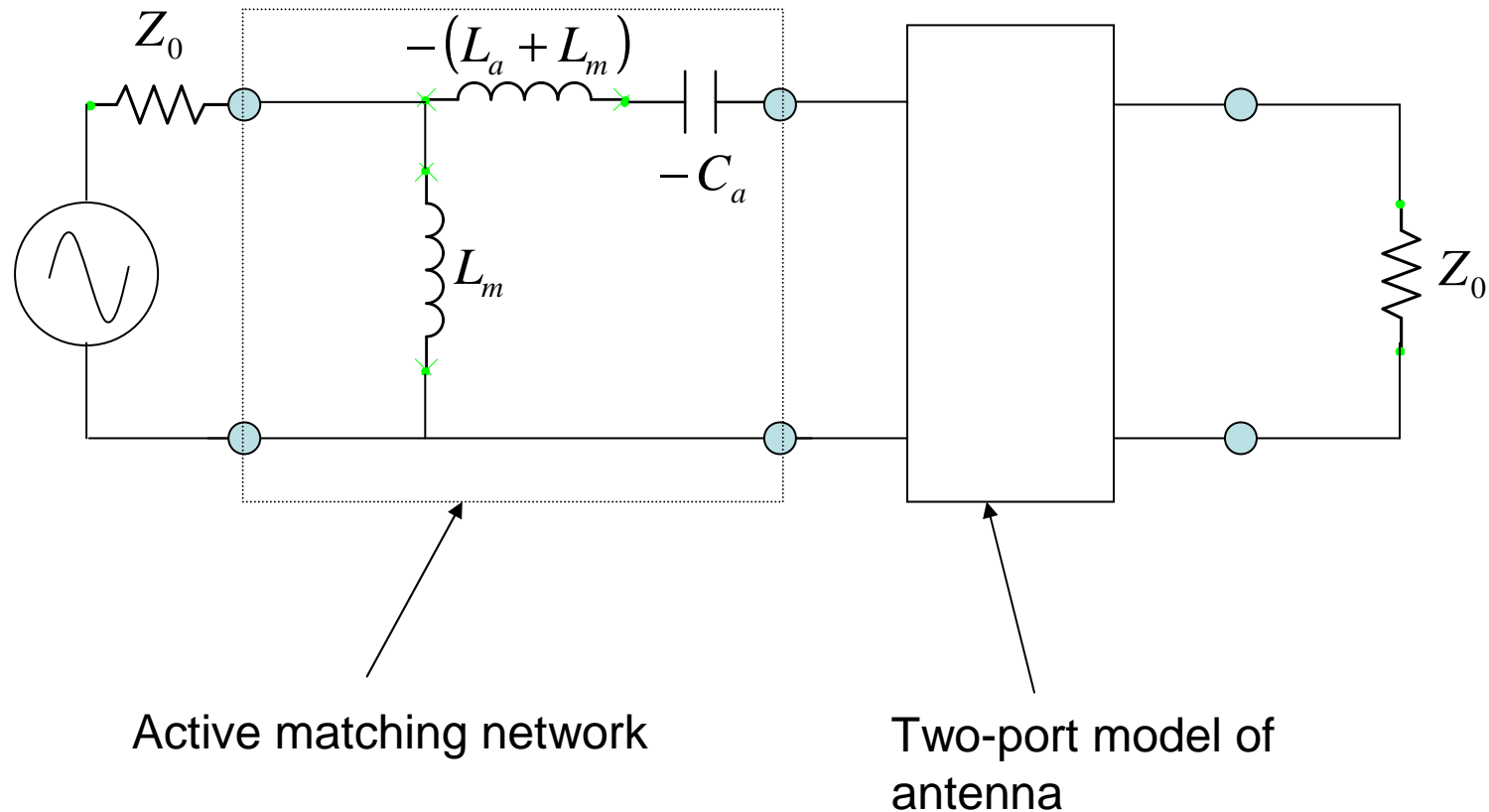
# Antenna with More Practical Matching Network using Non-Foster Reactances.






# Optimized Non-Foster Matching Network

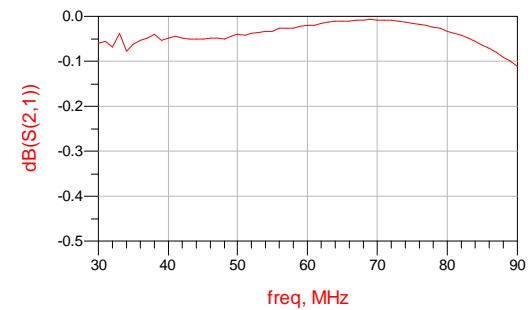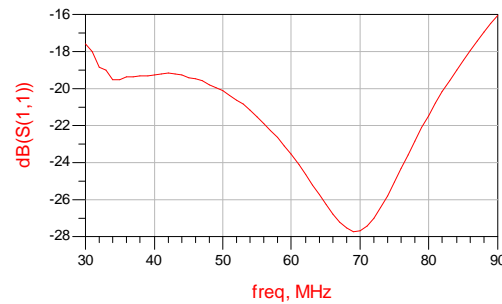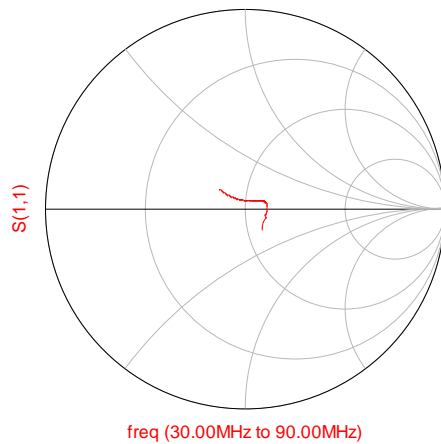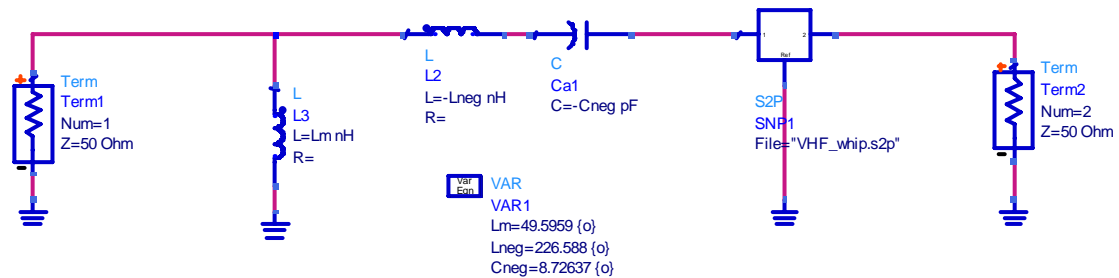

# Outline of Presentation

- What Does “Non-Foster” Mean?
- Possible Applications of Non-Foster Reactances
  - Electrically Small Antennas
  - **High-Impedance Surfaces**
  - Artificial High-Permeability Materials
- Realization of Non-Foster Reactances

# High-Impedance Ground Plane

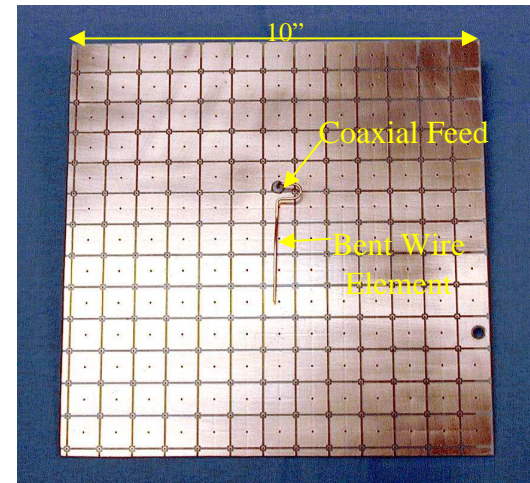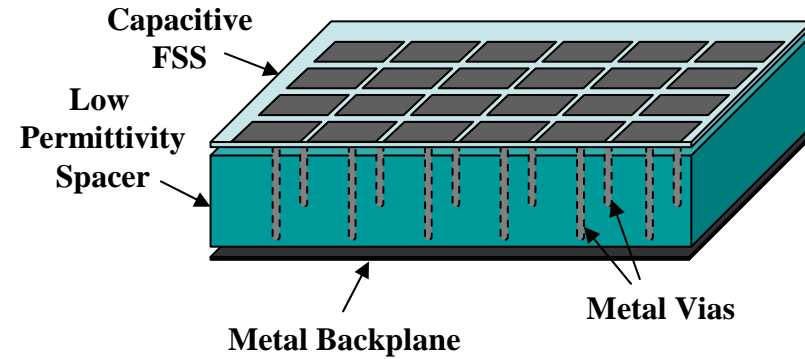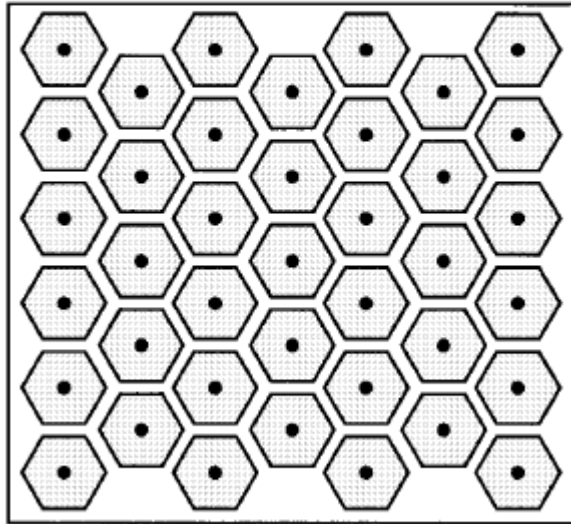


Sievenpiper, et. al, IEEE Trans. MTT, Nov. 1999



# EM Properties of the Sievenpiper High-Impedance Ground Plane

- Surface impedance is (ideally) an open-circuit (emulating a PMC rather than a PEC like a conventional ground plane).
- Propagation of TM and TE surface waves is not supported (thus can be called an electromagnetic bandgap structure).

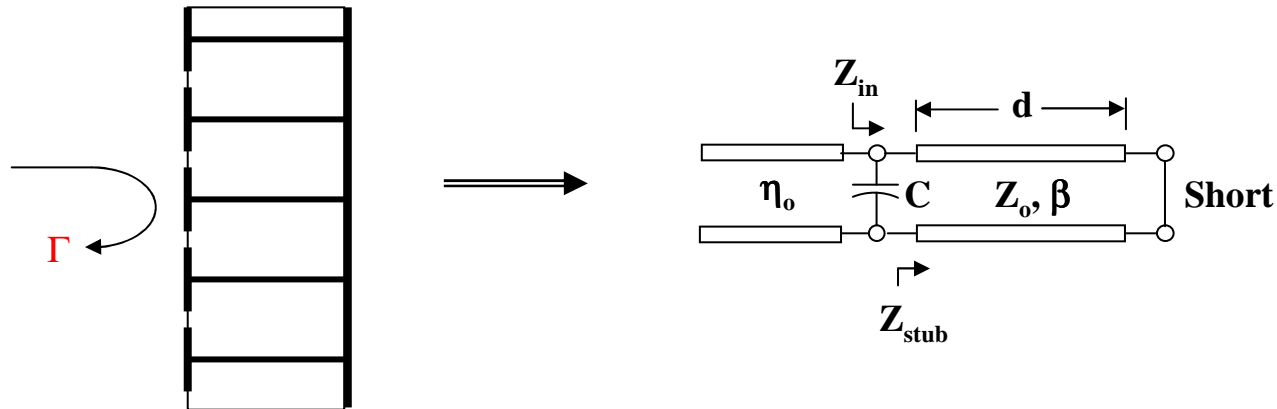
# Model for Surface Impedance of Sievenpiper HIS



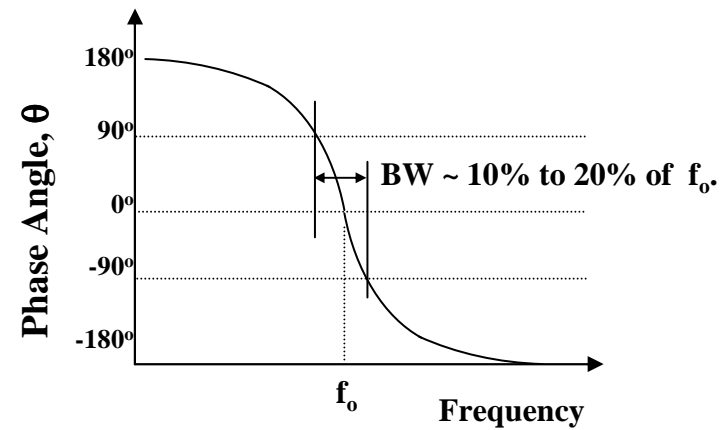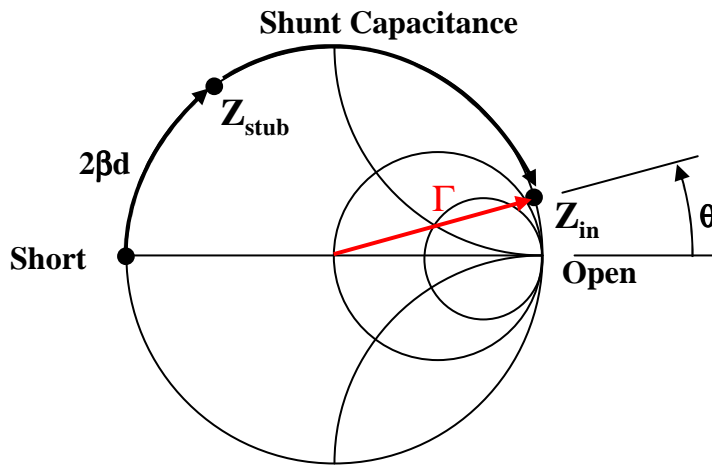For plane waves at normal incidence, the substrate may be understood as an electrically short length of shorted transmission line in parallel with a shunt capacitance at the reference plane of the outer surface.


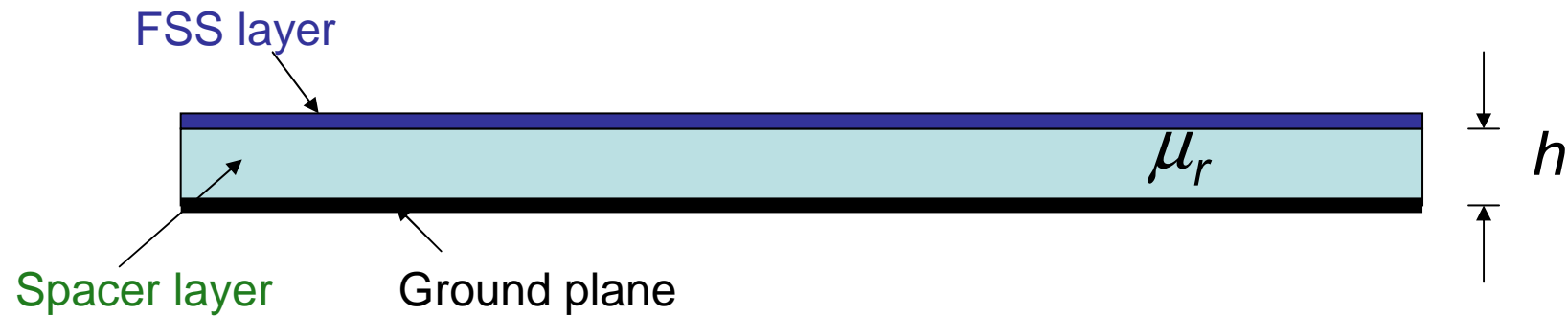
# Reflection Phase Bandwidth of Sievenpiper HIS




$$\frac{\Delta\omega}{\omega_0} = 2\pi\mu_r \frac{h}{\lambda_0}$$




# Electrically-Thin Broadband High-Impedance Surface

- In principle, one could realize an electrically-thin broadband HIS by using a high-permeability spacer layer.
- A high-permeability meta-material can be realized using artificial magnetic molecules (AMMs) implement with negative inductance circuits.
- Unfortunately, AMM performance is very sensitive to component tolerances.
- But, there is a better way ...
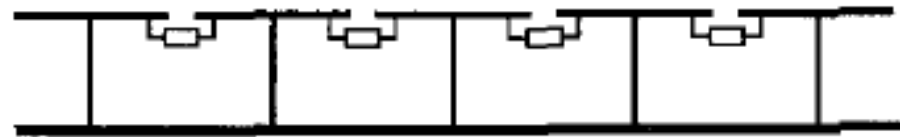
# Electrically-Thin Broadband High-Impedance Surface




(a)

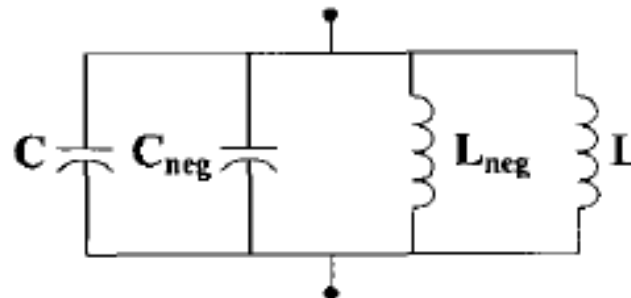

(b)


Kern, Werner, Wilhelm, APS 2003

# Electrically-Thin Conventional HIS

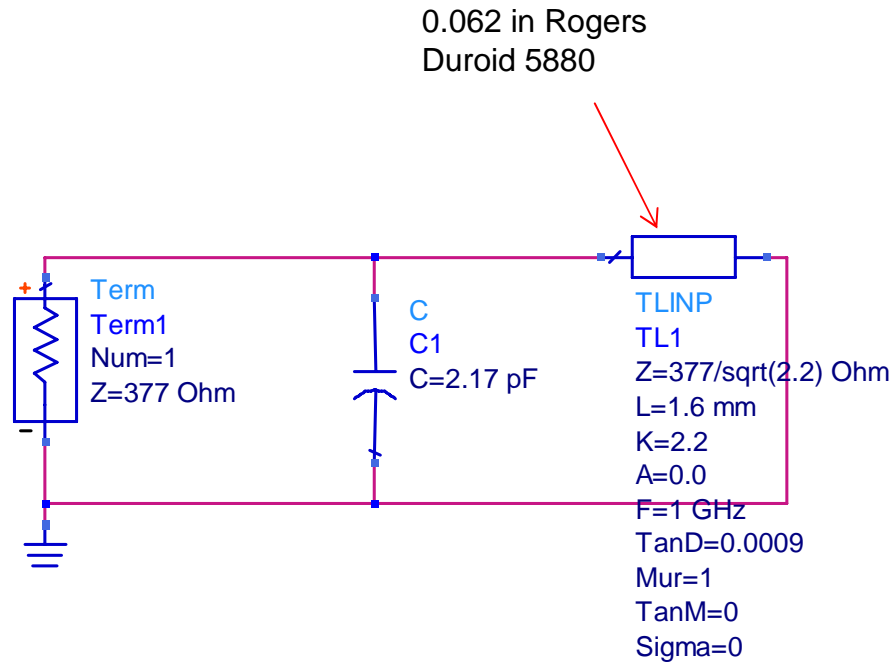



m1 freq=2.308GHz phase(S(1,1))=90.015	m2 freq=2.502GHz phase(S(1,1))=-90.204
---	--

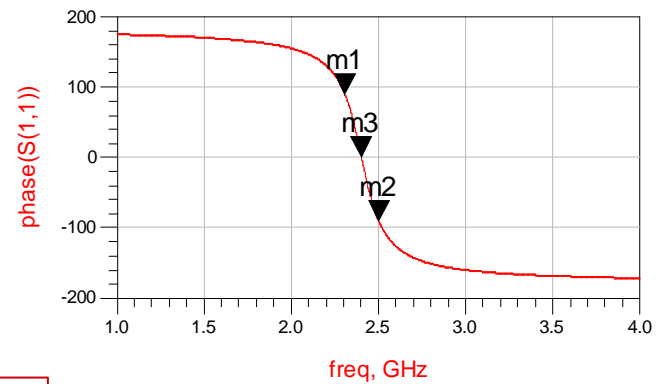m3 freq=2.403GHz phase(S(1,1))=-0.139
---




$$\frac{\Delta f}{f_0} = 8\%$$

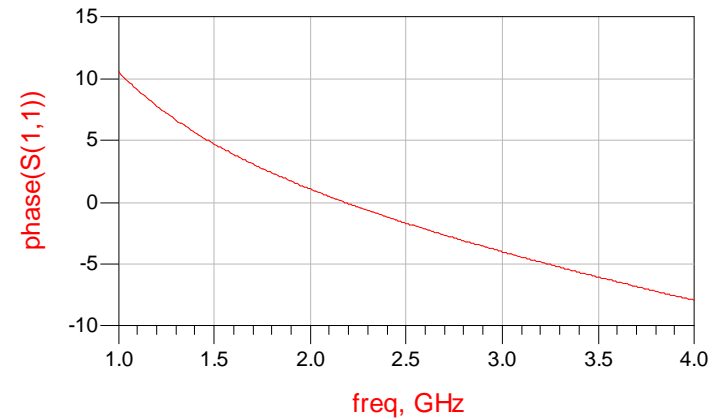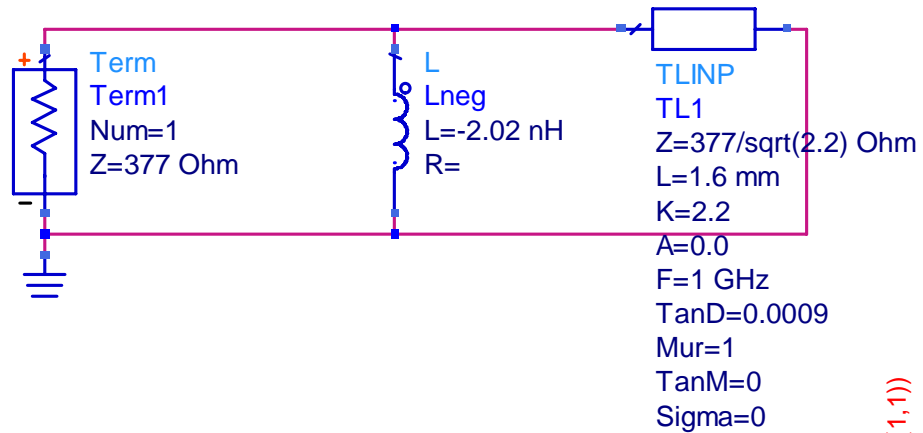
# Electrically-Thin HIS with Negative Inductance




# Unit Cell of Sievenpiper HIGP

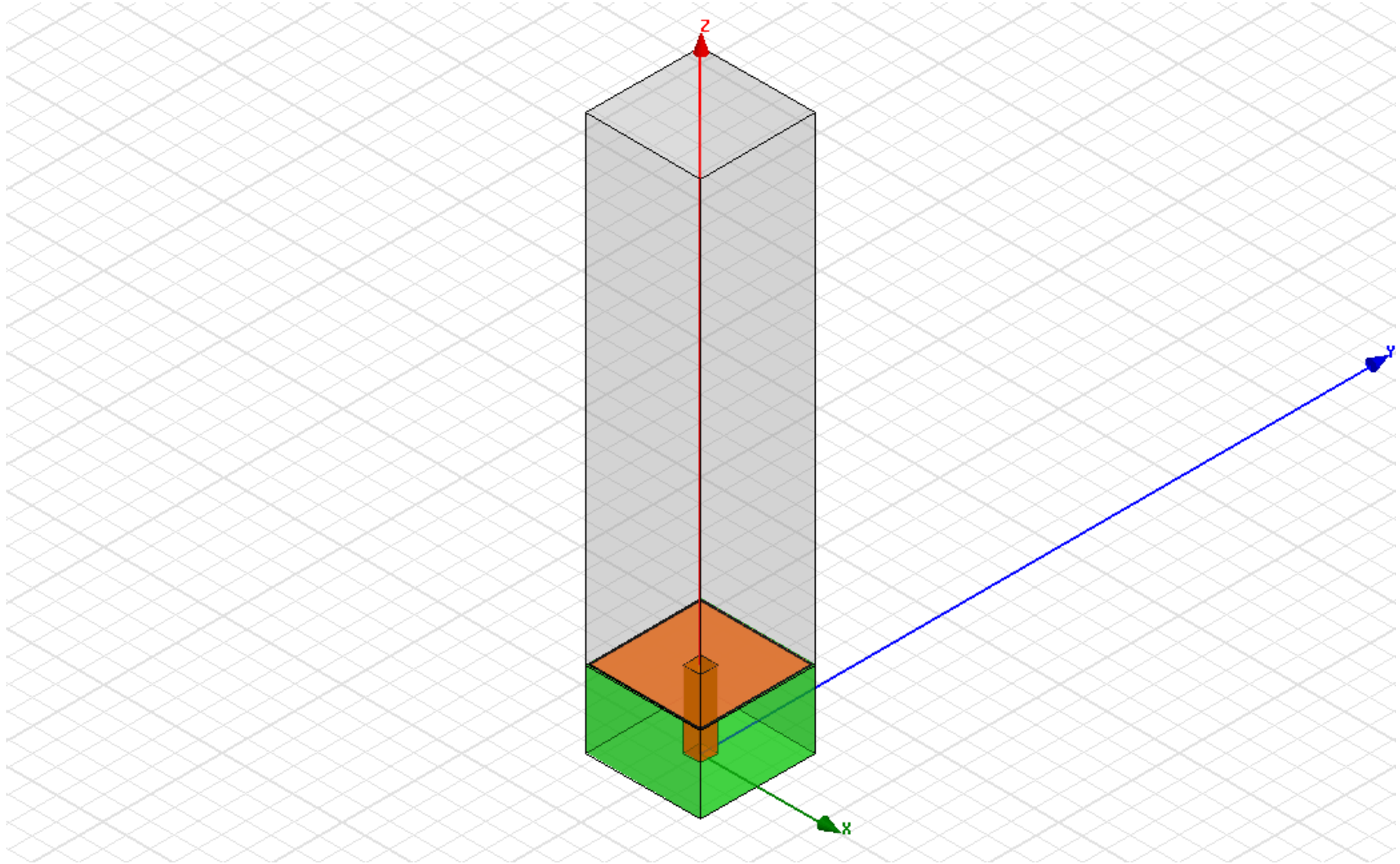

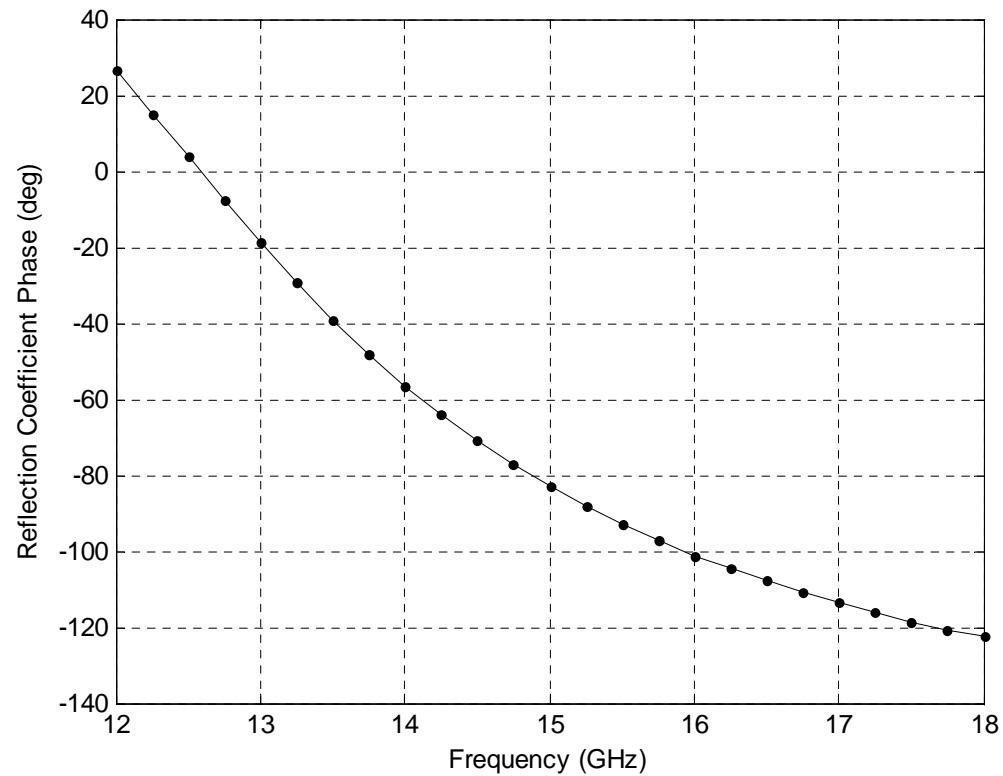
# Reflection Phase Response of Sievenpiper HIGP


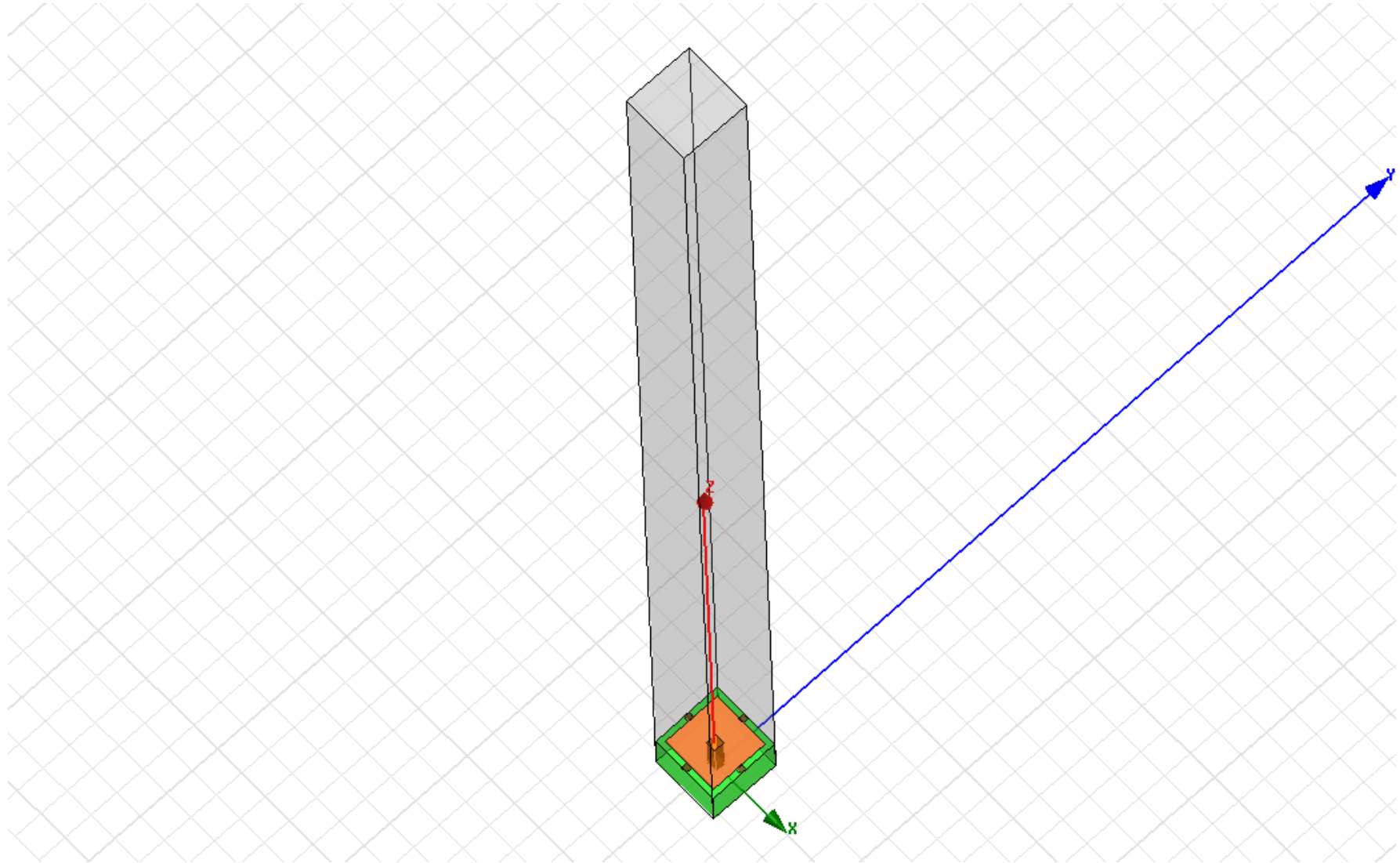
# Unit Cell of Sievenpiper HIGP with Reactive Loading



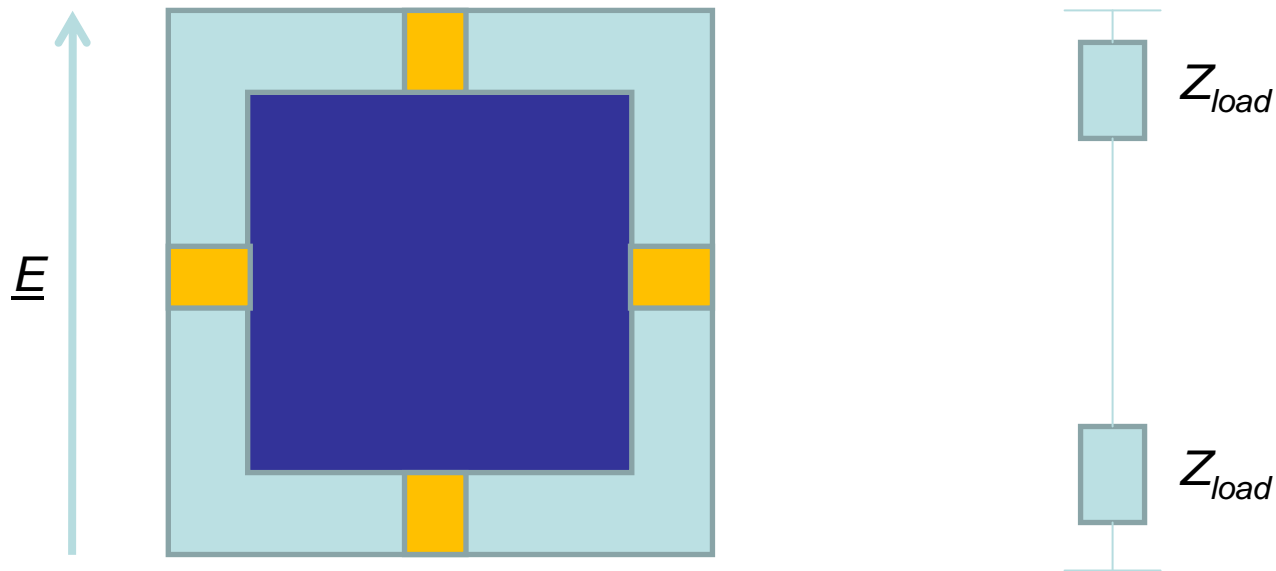
# Equivalent Circuit of Loaded HIGP for Normally Incident Plane Wave





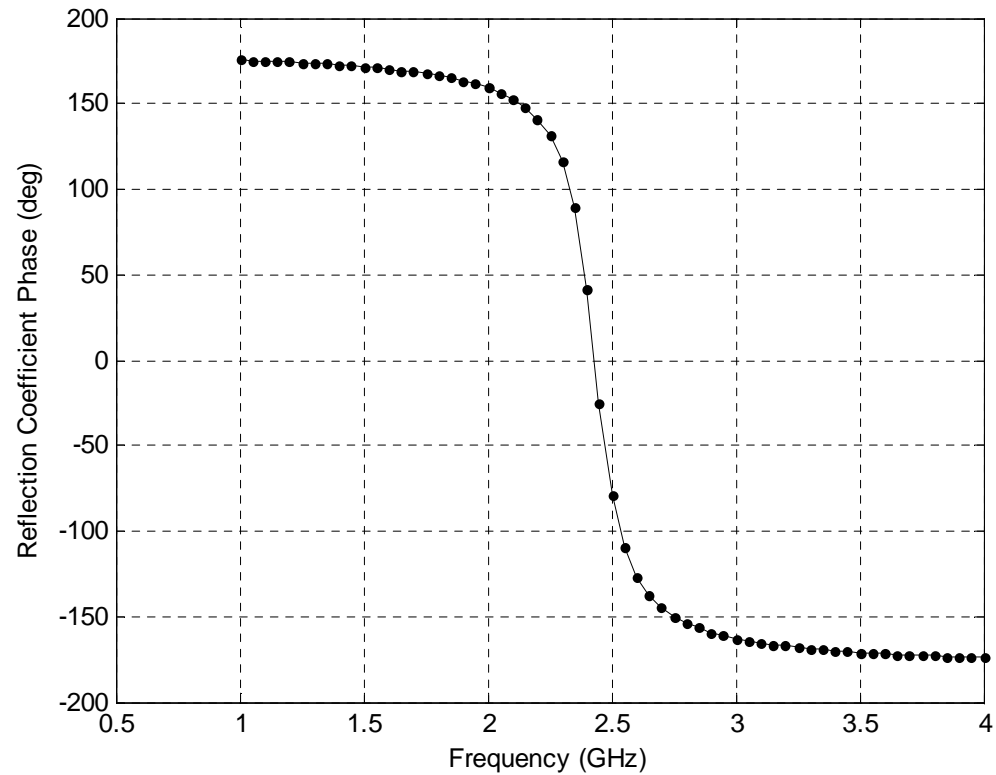
# Reflection Phase of Capacitively Loaded HIGP


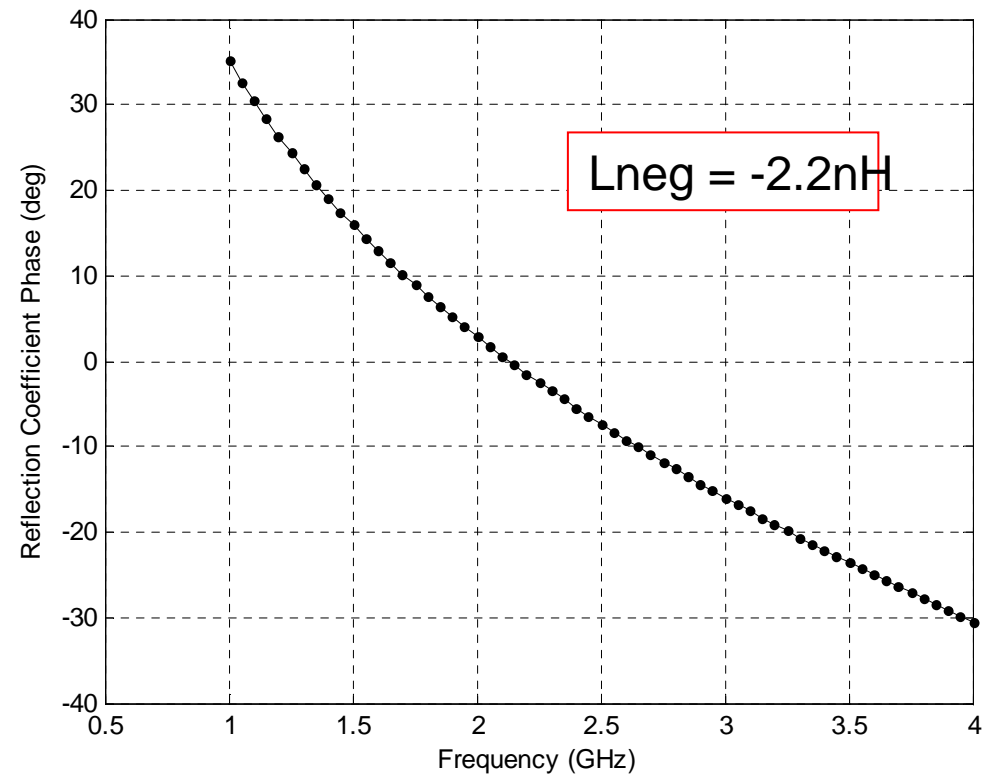
# Reflection Phase of Negative-Inductor Loaded HIGP



# Outline of Presentation

- What Does “Non-Foster” Mean?
- Possible Applications of Non-Foster Reactances
  - Electrically Small Antennas
  - High-Impedance Surfaces
  - **Artificial High-Permeability Materials**
- Realization of Non-Foster Reactances

# What is an Artificial Material?


- An artificial material is a large-scale emulation of an actual material, obtained by embedding a large number of electrically small inclusions (“artificial molecules”) within a host medium.
- Like natural molecules, the electrically small inclusions exhibit electric and/or magnetic dipole moments.
- As a result of these dipole moments, the macroscopic electromagnetic constitutive parameters ( $\epsilon_r$  and  $\mu_r$ ) are altered with respect to the host medium.

$$\underline{D} = \overset{=}{\epsilon} \bullet \epsilon_0 \underline{E}$$
$$\underline{B} = \overset{=}{\mu} \bullet \mu_0 \underline{H}$$

# Why Create an Artificial Magnetic Material?


- “Naturally” occurring magnetic materials (ferrites) are heavy, fragile and expensive, and they also exhibit relatively high magnetic losses and dielectric constant.
- Available ferrite materials provide a limited selection of relative permeabilities.
- The permeability tensor of the ferrite is controlled by applying a static magnetic field – permanent magnets and/or electromagnets are required.

# Artificial Magnetic Metamaterial

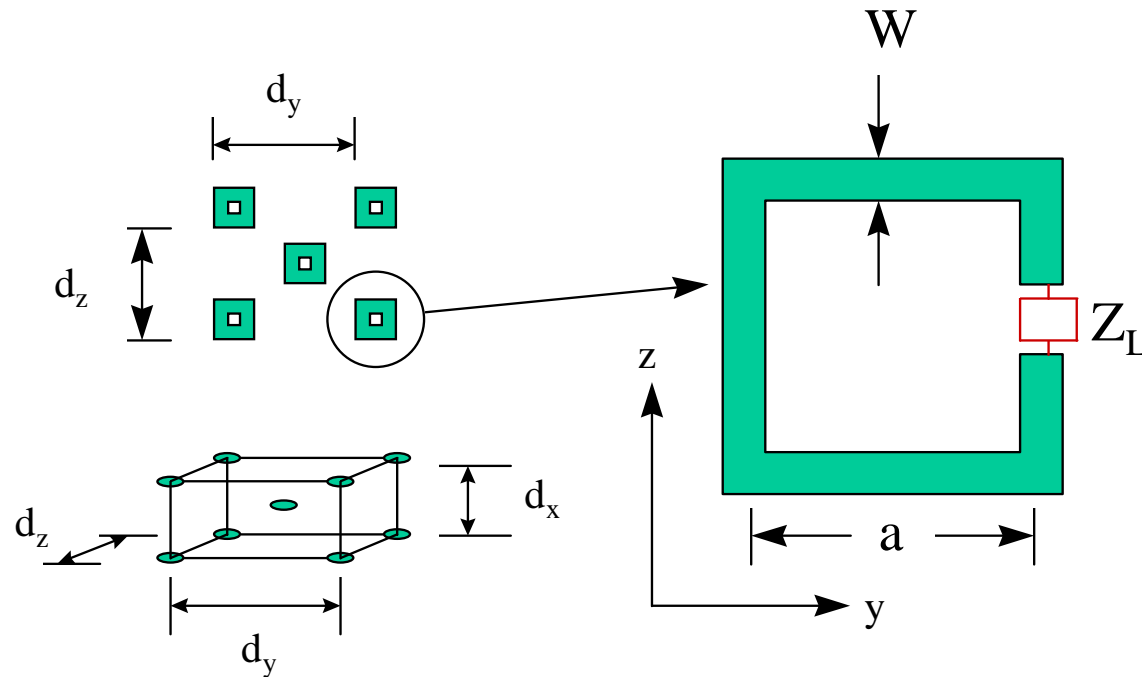


- A 3-dimensional lattice of artificial molecules.
- Electrically small loop with a load impedance
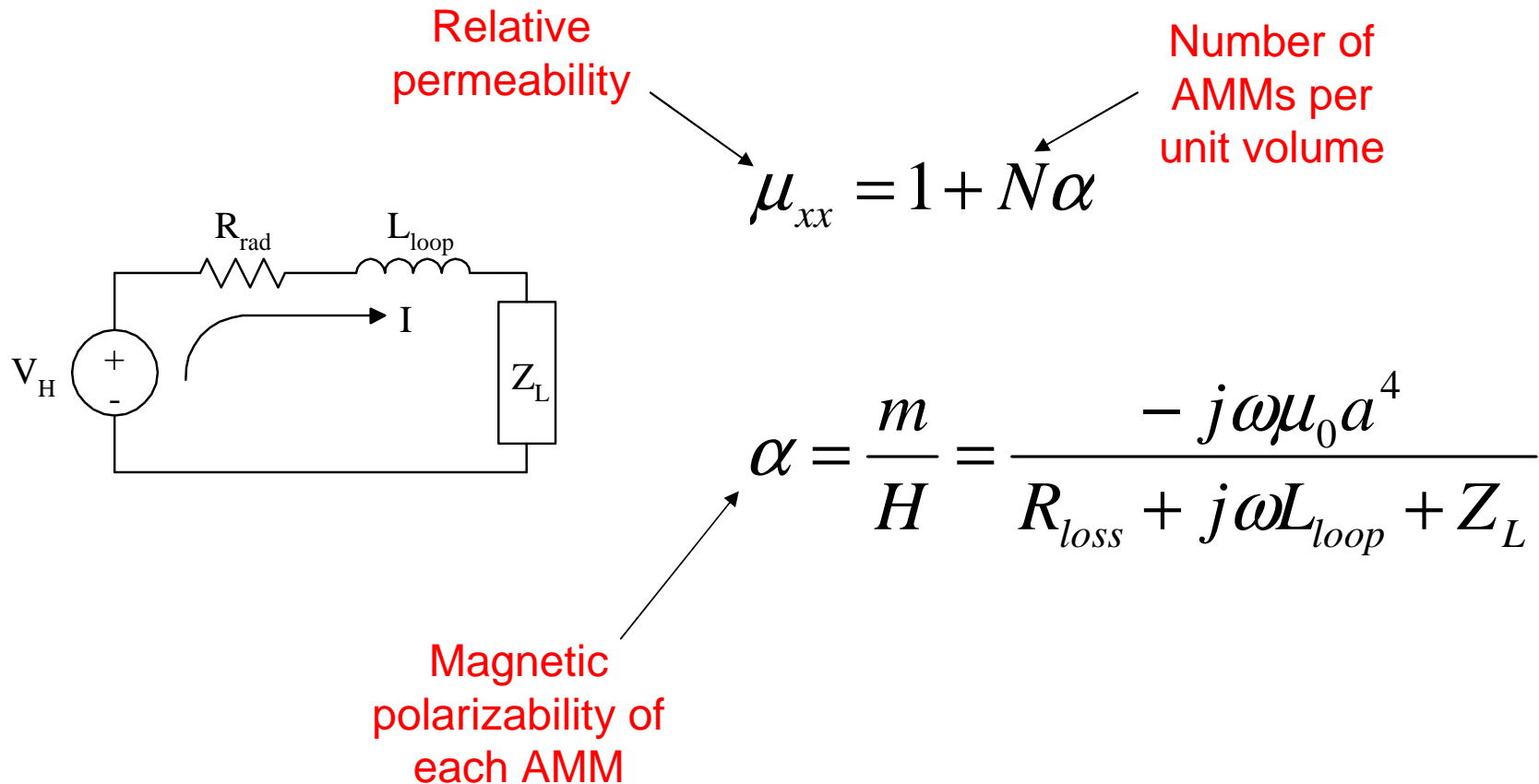
## Simple Circuit Model for Artificial Magnetic Molecule (AMM)



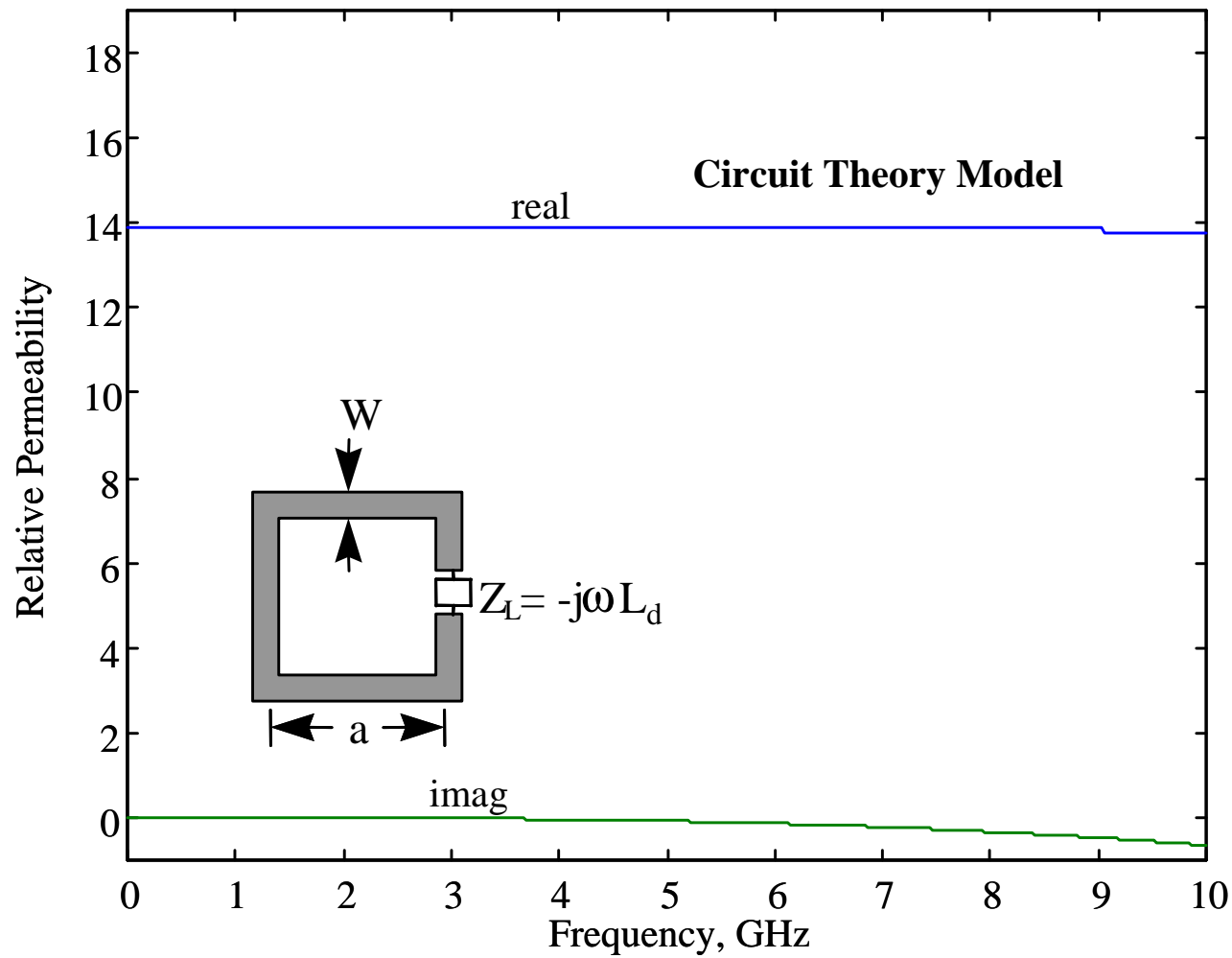
# Broadband, High Permeability Requires Negative Inductance




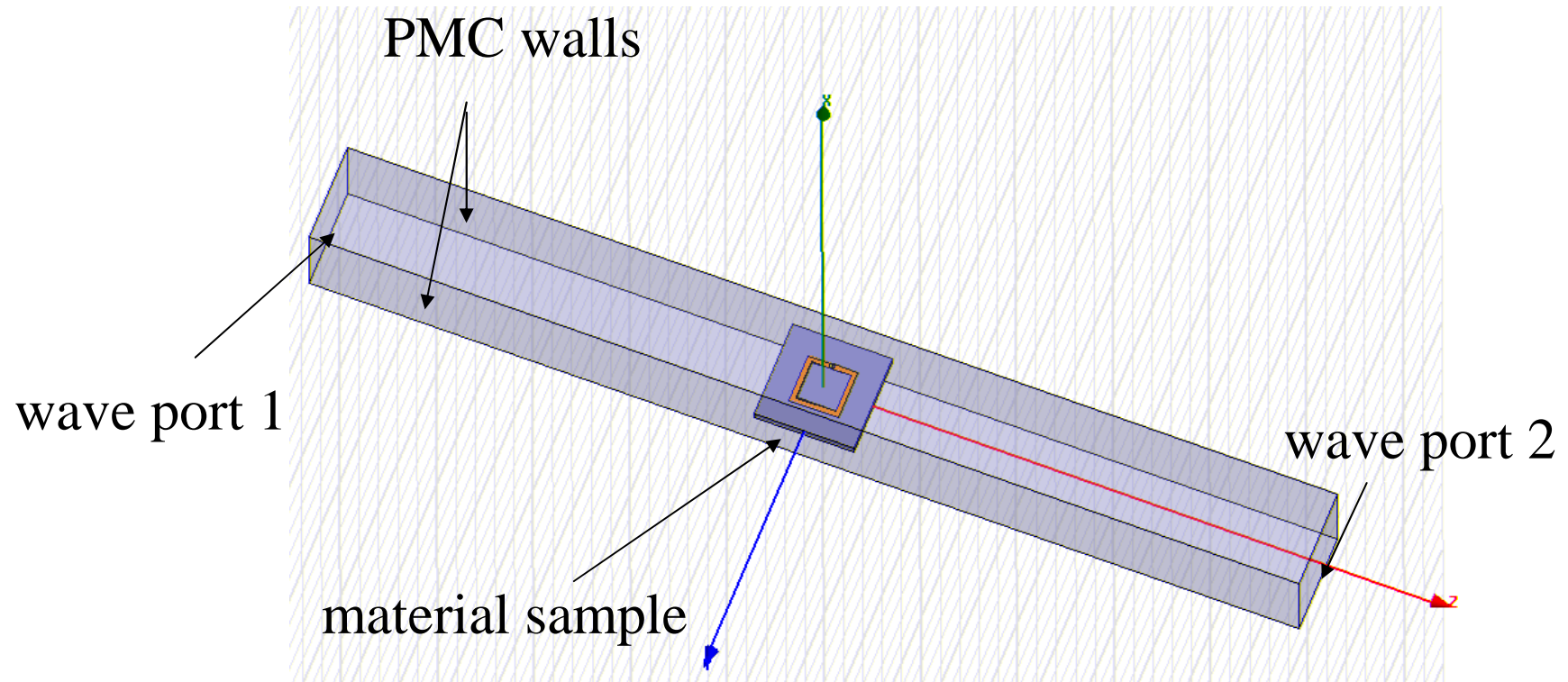
# How to Extract Material Properties

(TEM waveguide containing material sample)




# How to Extract Material Properties

- HFSS
  - Two port S parameters calculation of TEM waveguide containing material sample.
- MATLAB
  - Shifting of the reference planes.
  - Conversion of S-parameters to ABCD parameters.
  - Calculation of propagation constant and characteristic impedance of equivalent transmission line.
  - Evaluation of the material properties.

# How to Extract Material Properties

(Loop Configuration)

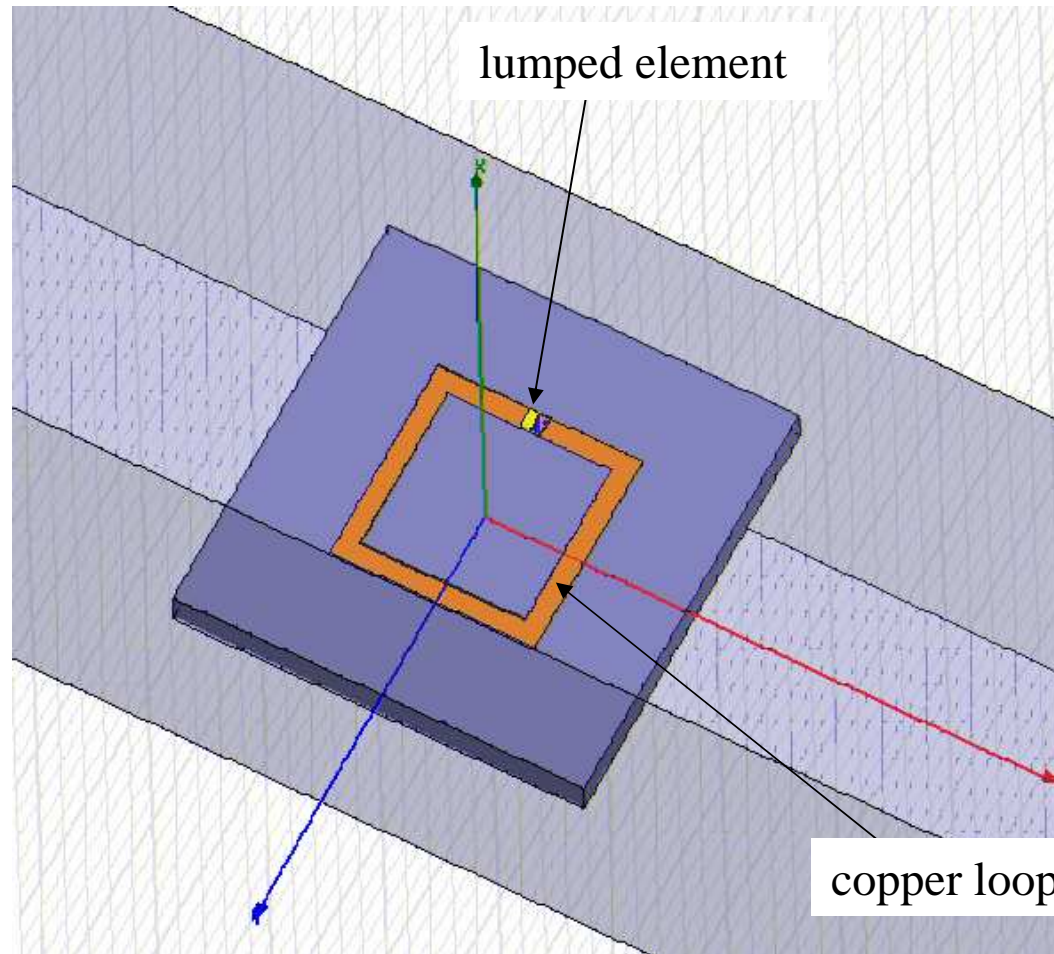

## Negative Inductance is Modeled as a Frequency-Dependent Capacitance

$$C_{equiv} = \frac{1}{(2\pi f)^2 |L_{neg}|}$$

**Lumped RLC Boundary**

General | Defaults

Name: LumpRLC1

Parallel R, L, C Values

Resistance: 1 Ohm

Inductance: 0 nH


Capacitance: 1/((2\*pi\*Freq)^2\*Lneg)

Current Flow Line: Defined

Use Defaults


OK Cancel
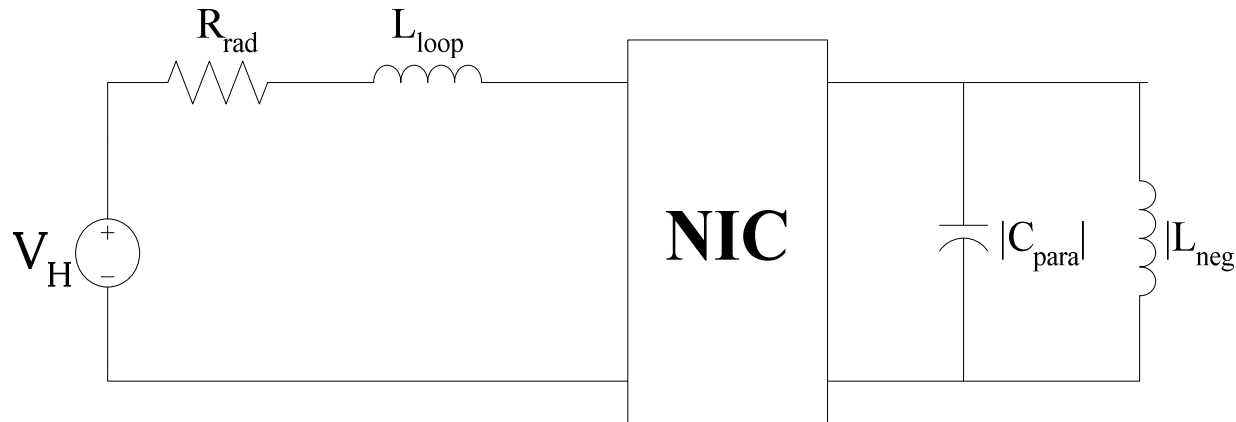
# Cancellation of Parasitic Capacitance Using NIC



To remove the resonance, the parasitic capacitance of the loop should be compensated by a negative capacitance.
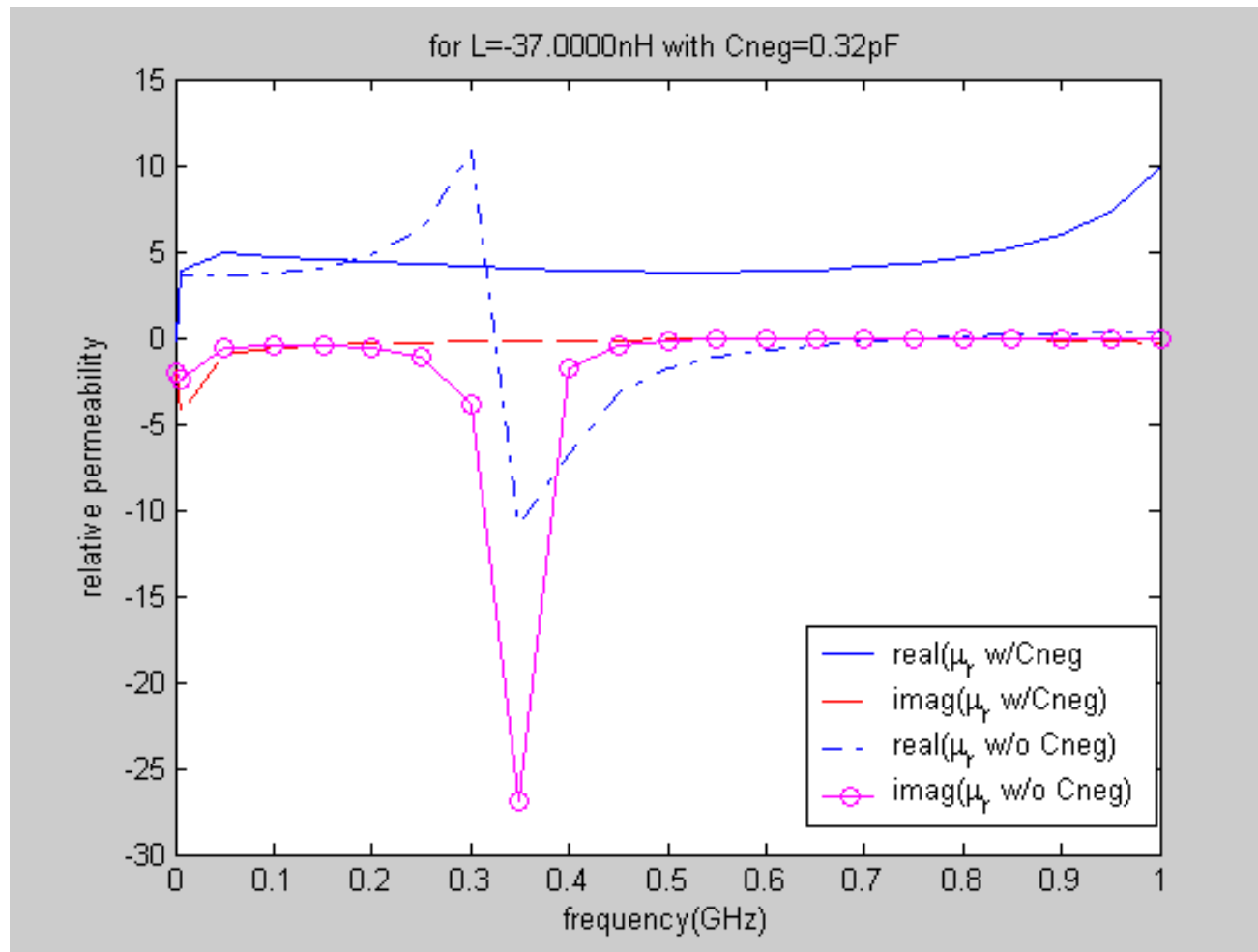
## Remedy for Snoek-Like Phenomenon: Add Negative Capacitance in Shunt with Negative Inductance




# Outline of Presentation

- What Does “Non-Foster” Mean?
- Possible Applications of Non-Foster Reactances
  - Electrically Small Antennas
  - High-Impedance Surfaces
  - Artificial High-Permeability Materials
- **Realization of Non-Foster Reactances**

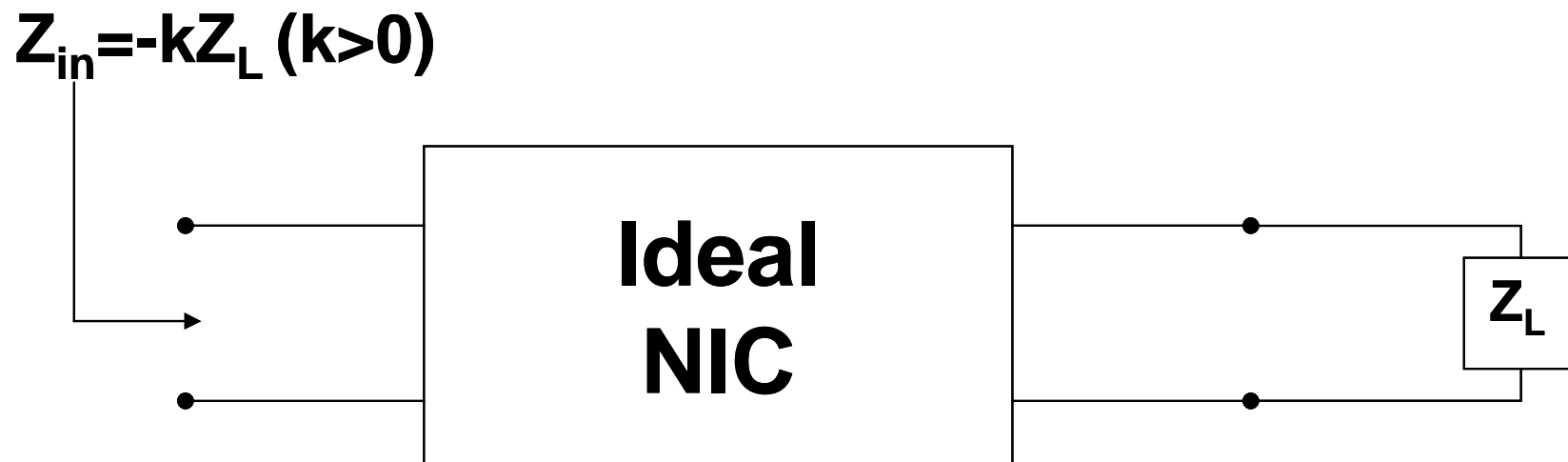
# Negative Impedance Converter (NIC)

- An ideal NIC is a two-port network such that when a load impedance is attached to the output terminal, the input impedance is the (possibly scaled) negative value of the load impedance.






# Canonical NIC

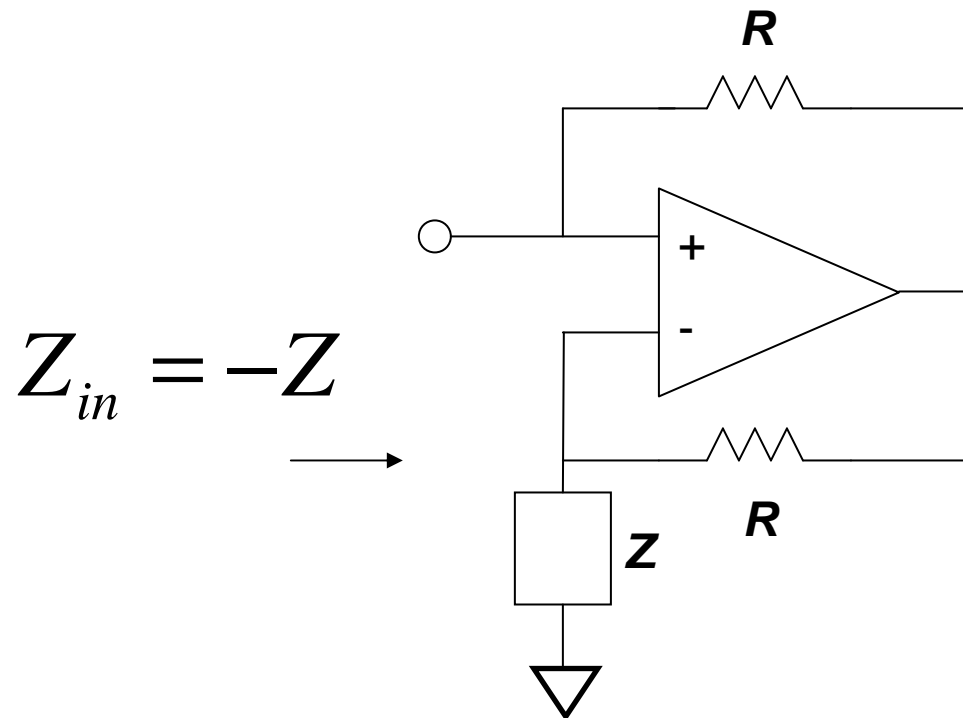


# Simple Op-Amp Test Circuit

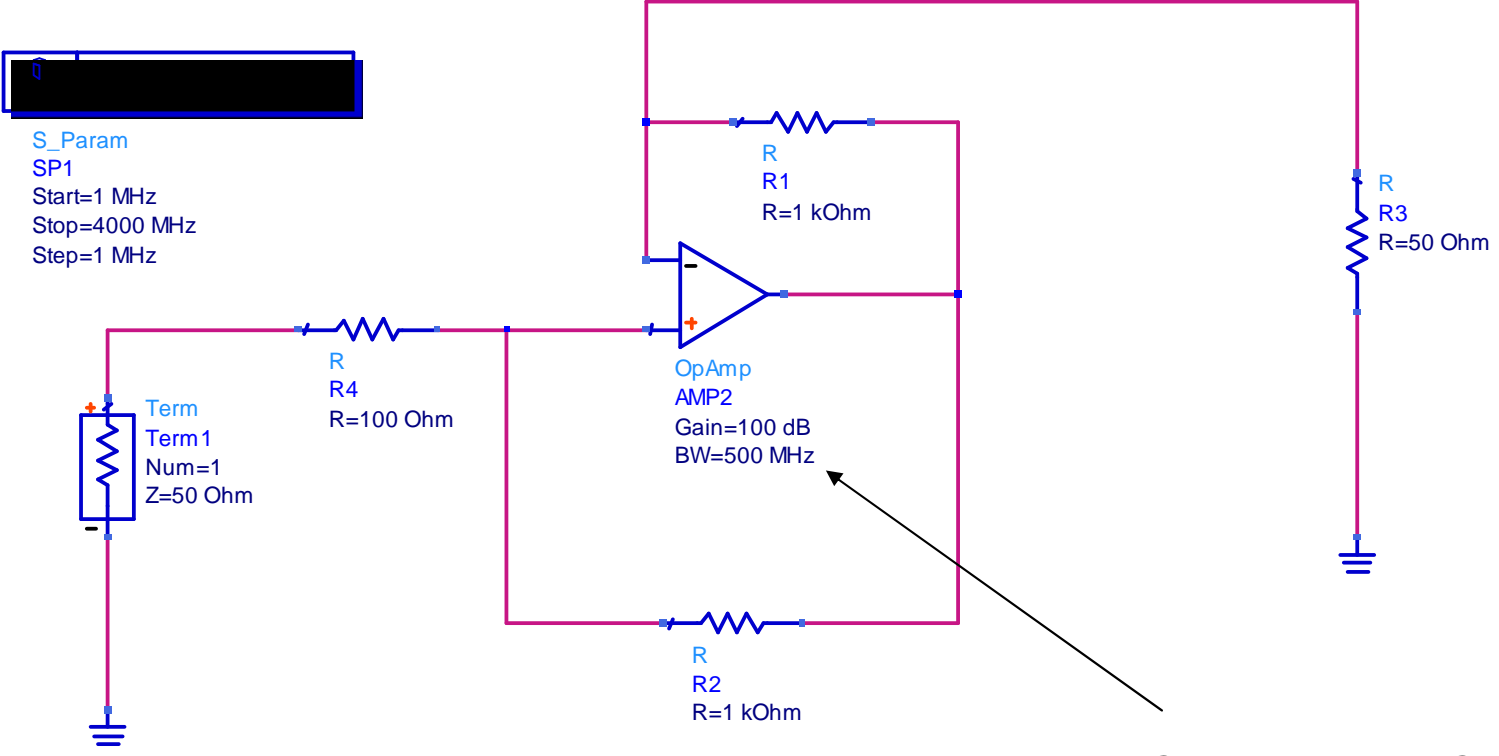


FOM:  $RL > 15$  dB

Can specify DC gain and unity gain BW.


Unity-gain BW = 500 MHz

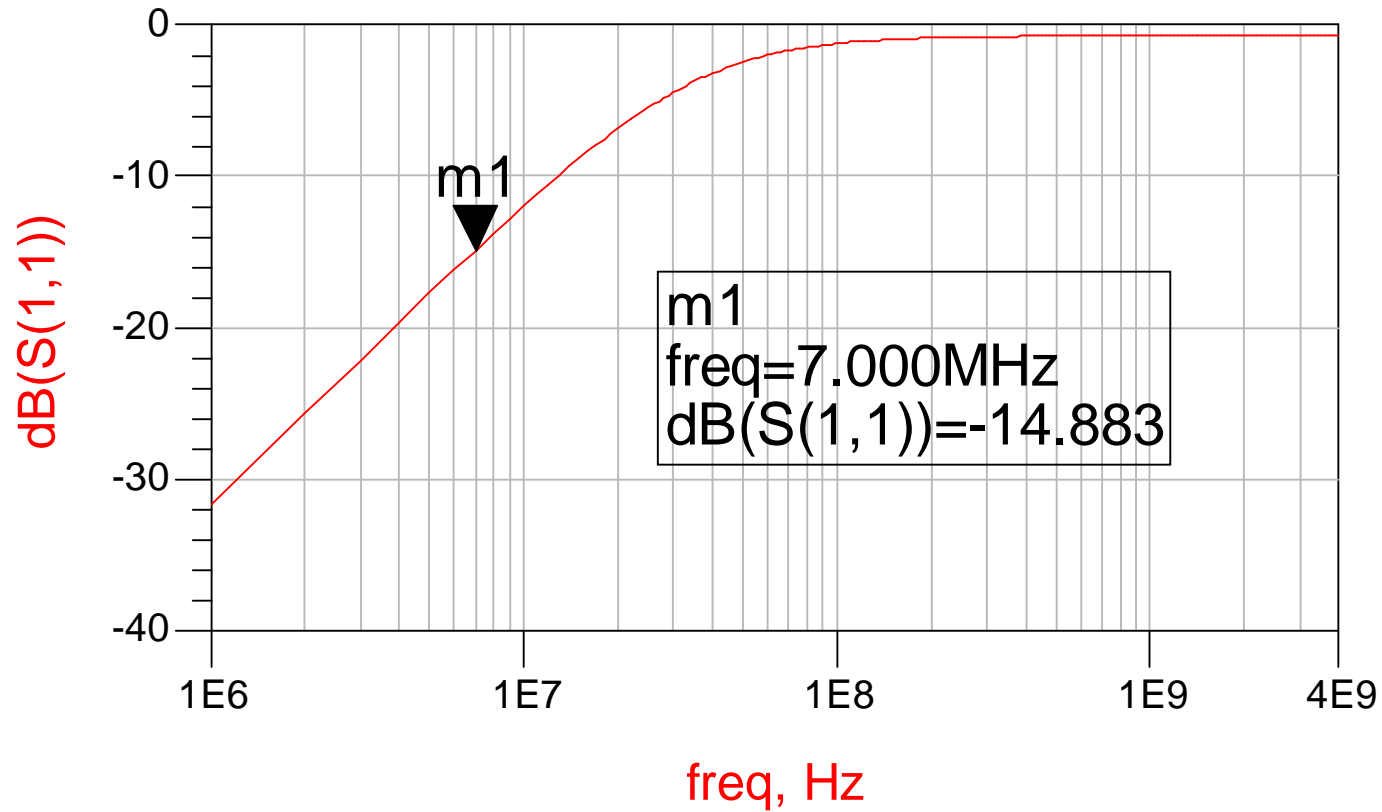

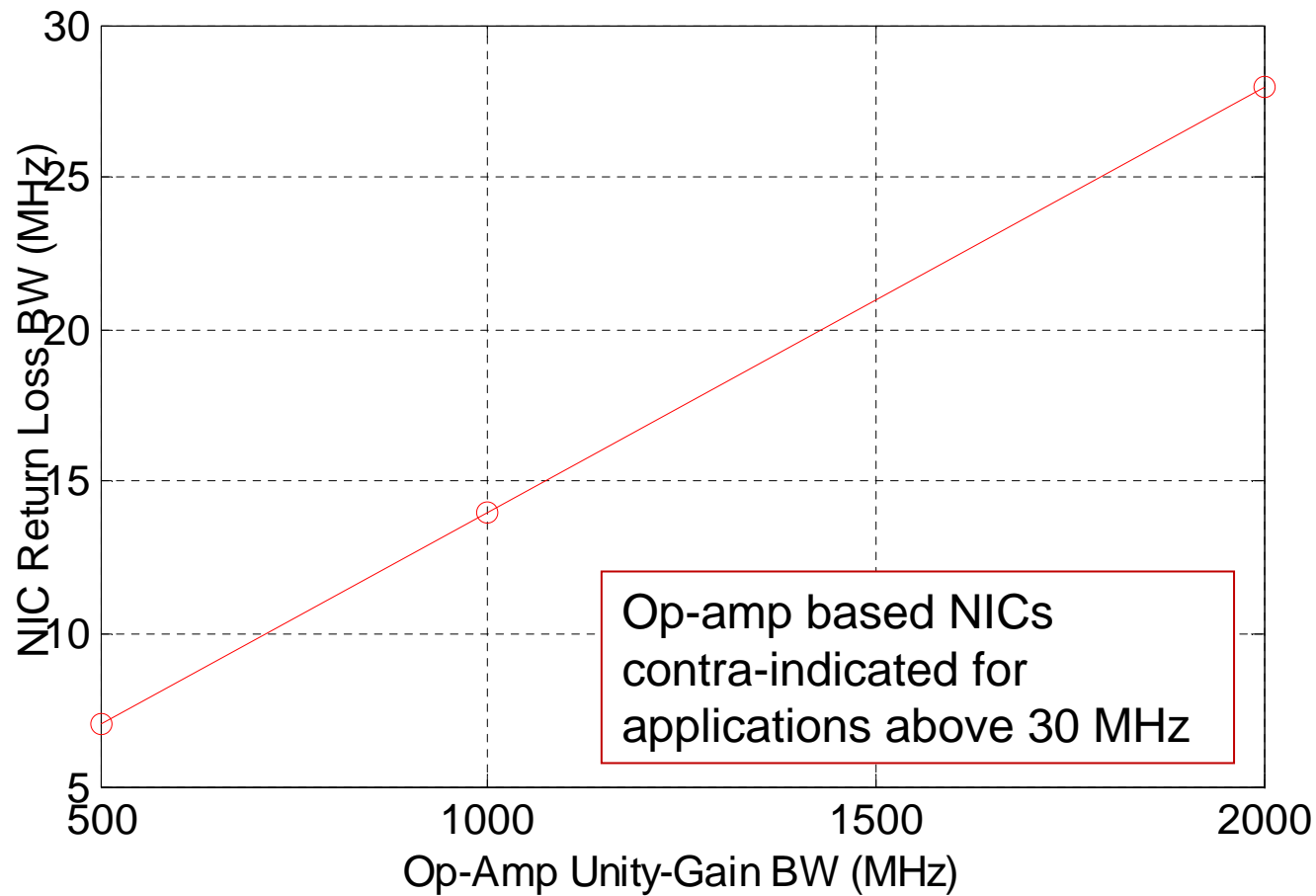
# NIC Return Loss BW vs. Op-Amp Unity Gain BW



# Fabricated OPA690 NIC Evaluation Board

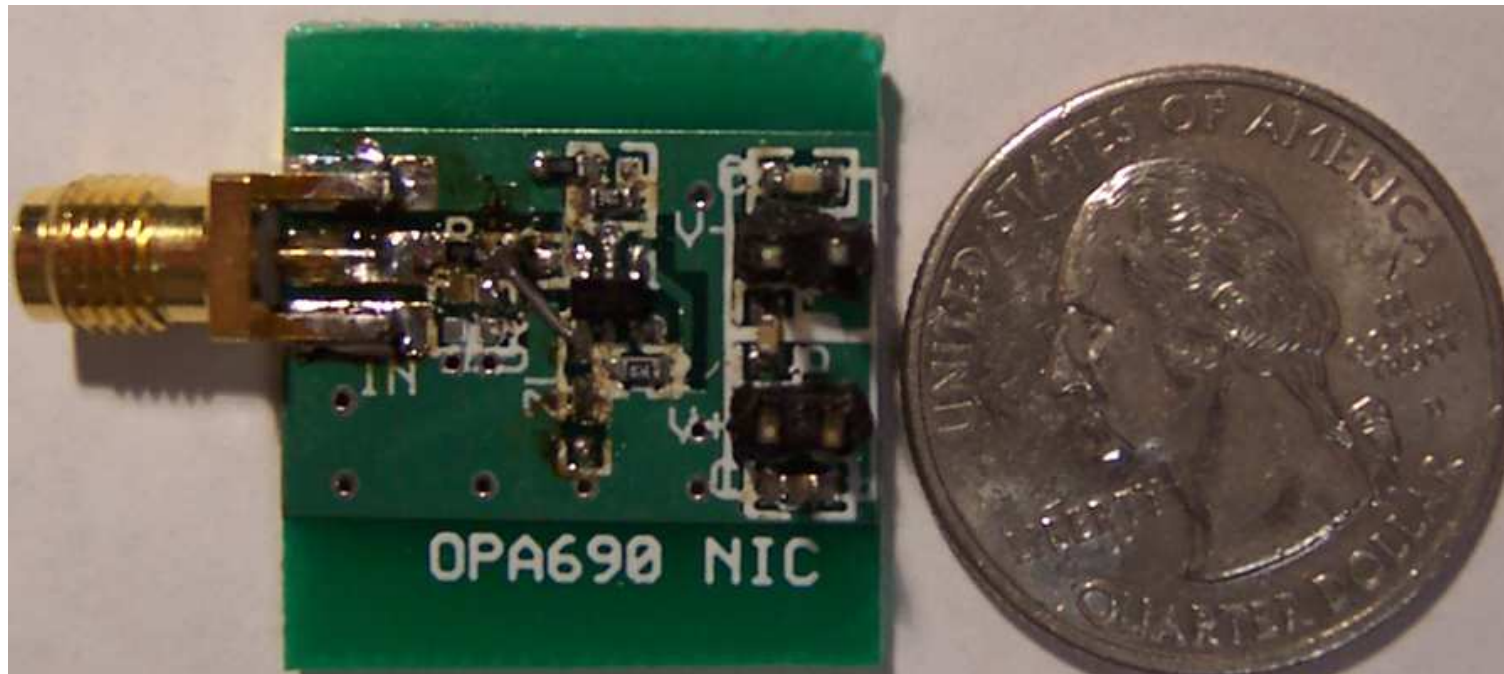

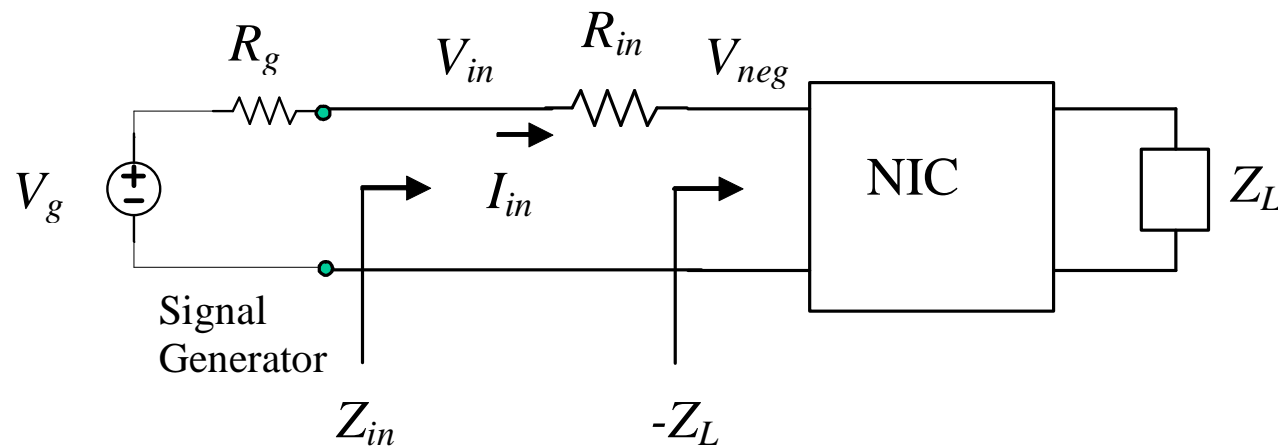
# Circuit for evaluating the performance of a grounded negative impedance




Stability requires that

$$R_{in} > |Z_L|$$
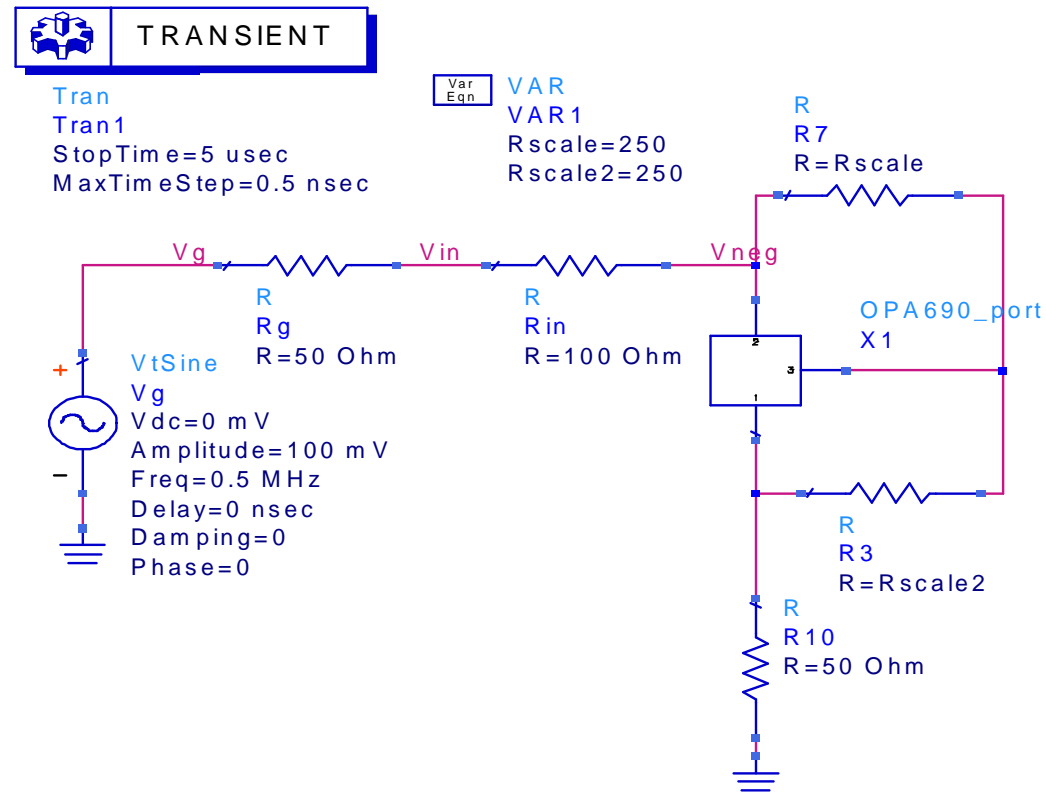
# Schematic captured from Agilent **ADS** of the circuit for evaluating the performance of the OPA690 NIC



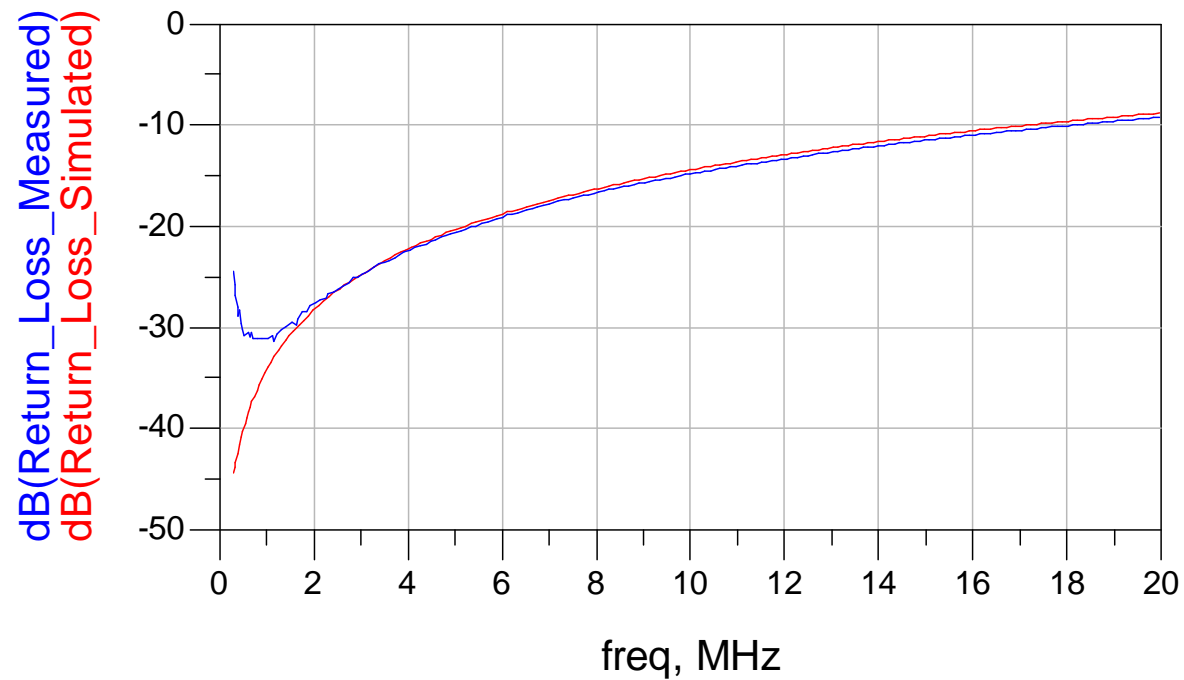
# Simulated and measured return loss for the OPA690 NIC evaluation circuit





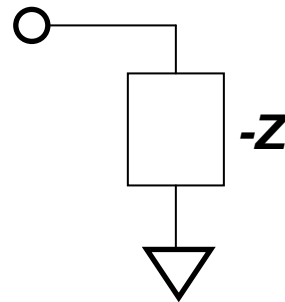
# Ground Negative Impedance Versus Floating Negative Impedance


- Canonical NIC and most other NIC circuits in the literature produce **grounded negative impedance**



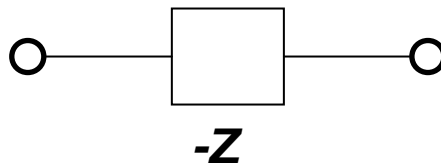- But for the applications we are considering here, we need **floating negative impedance**


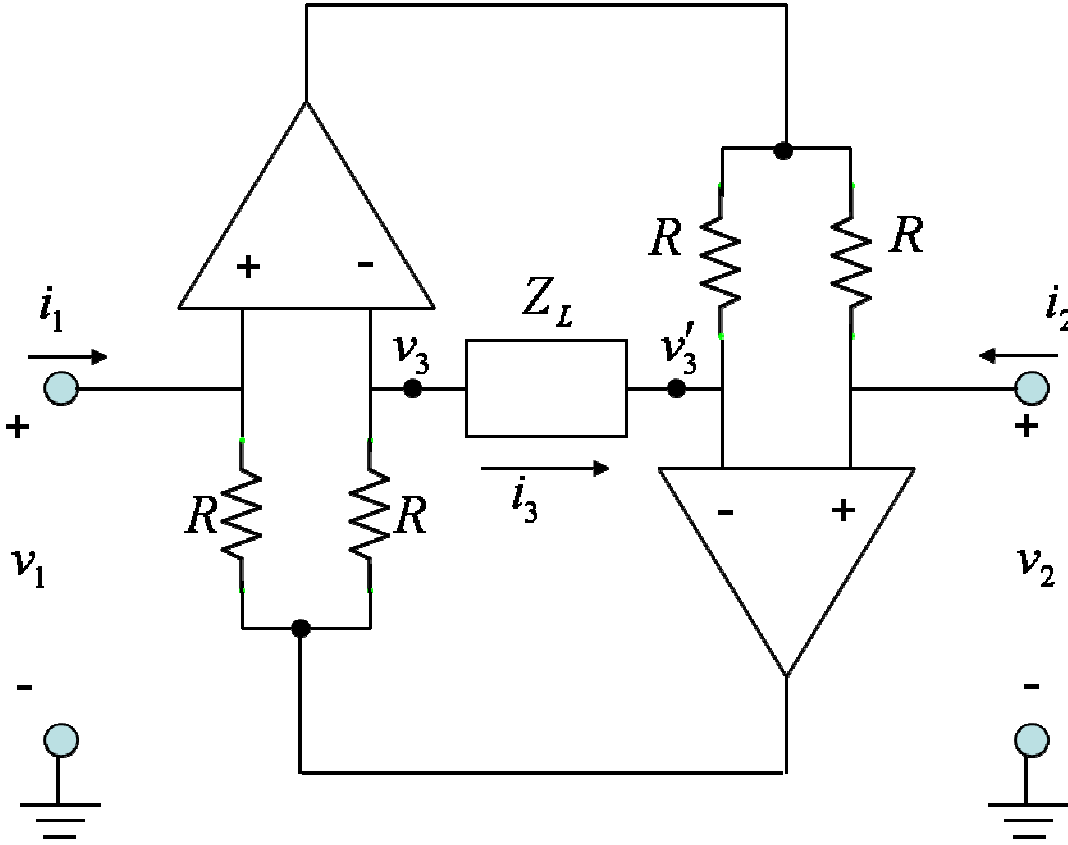
# Floating NIC Realized Using Two Op-Amps



# Op-Amp FNIC Test Circuit

**S-PARAMETERS**


S\_Param  
 SP1  
 Start=0.1 MHz  
 Stop=100 MHz  
 Step=0.1 MHz

**Mu**




Mu  
 Mu1  
 Mu1=mu(S)

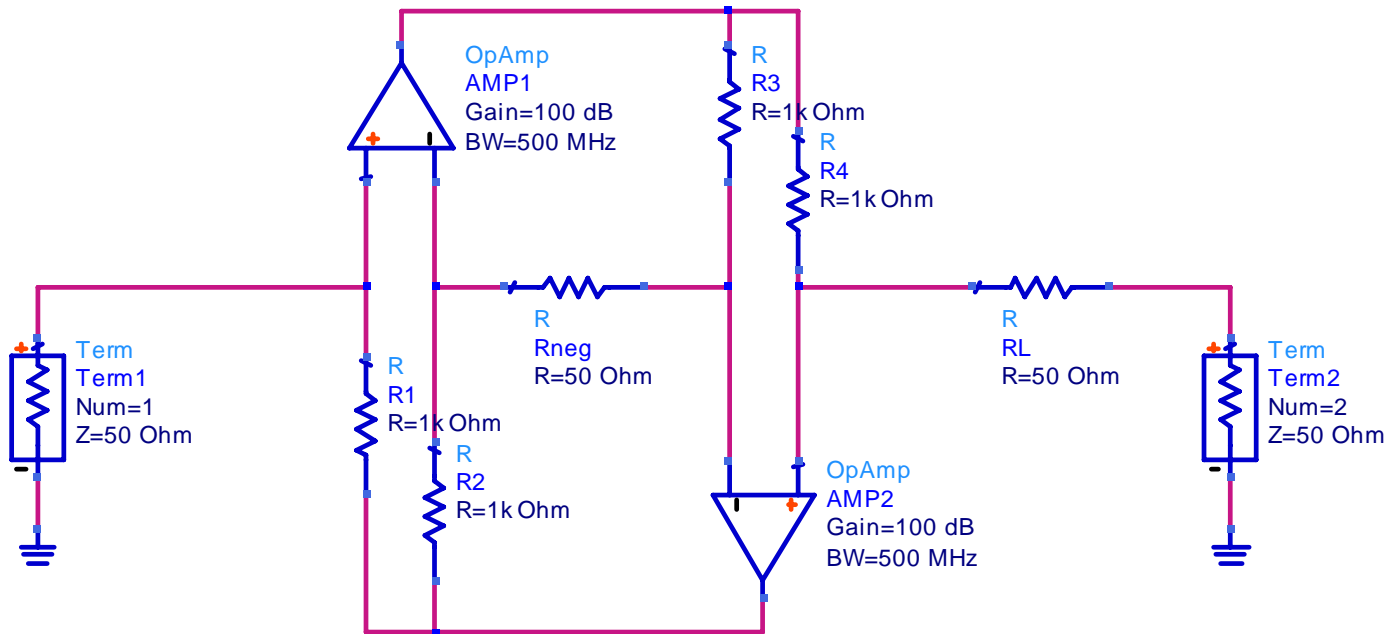**MuPrime**

MuPrime  
 MuPrime1  
 MuPrime1=mu\_prime(S)




Unity-gain BW = 500 MHz

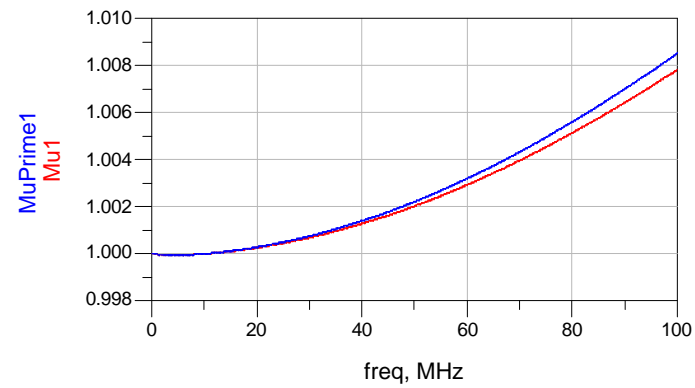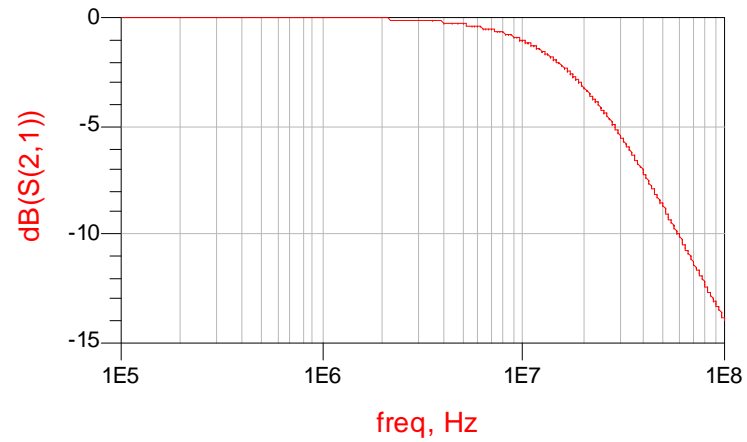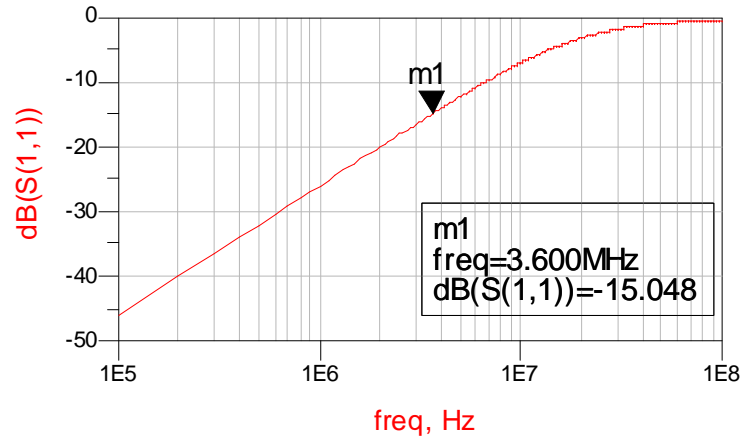


# NIC Return Loss BW vs. Op-Amp Unity Gain BW

Op Amp BW	15 dB RL NIC BW
500 MHz	3.6 MHz
1000 MHz	7.2 MHz
2000 MHz	14.5 MHz

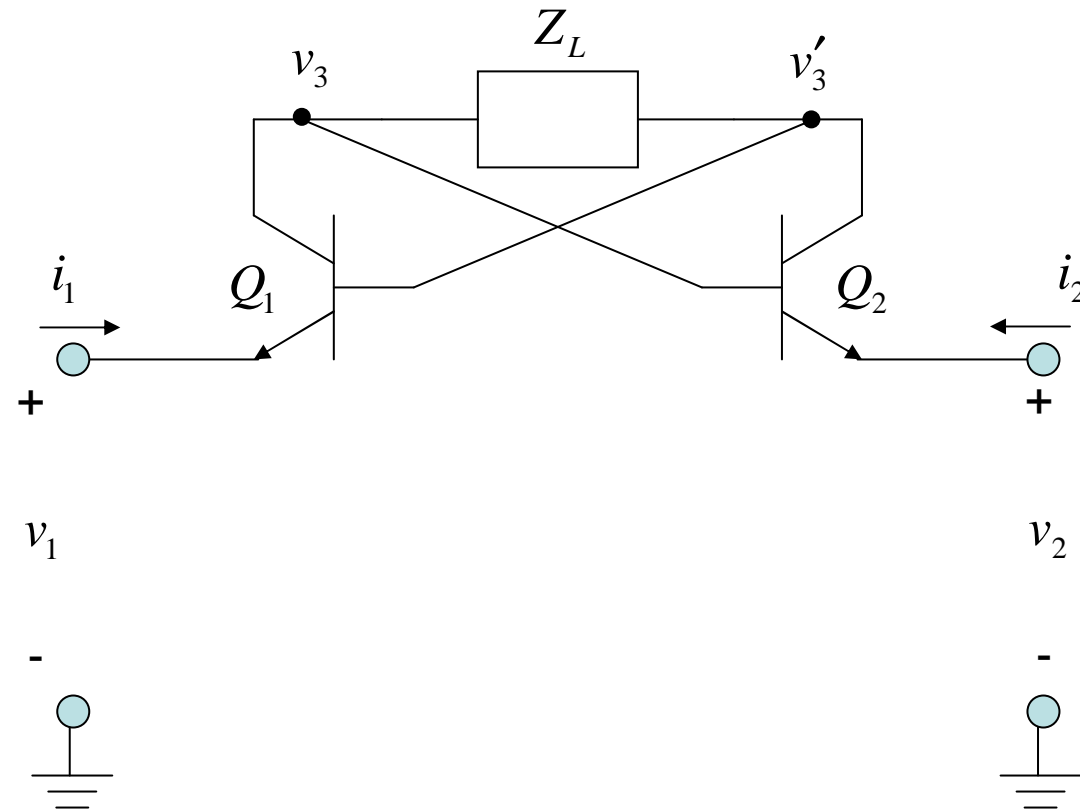
# Floating NIC Circuit Using Two Transistors



# NIC “All-Pass” Test Circuit


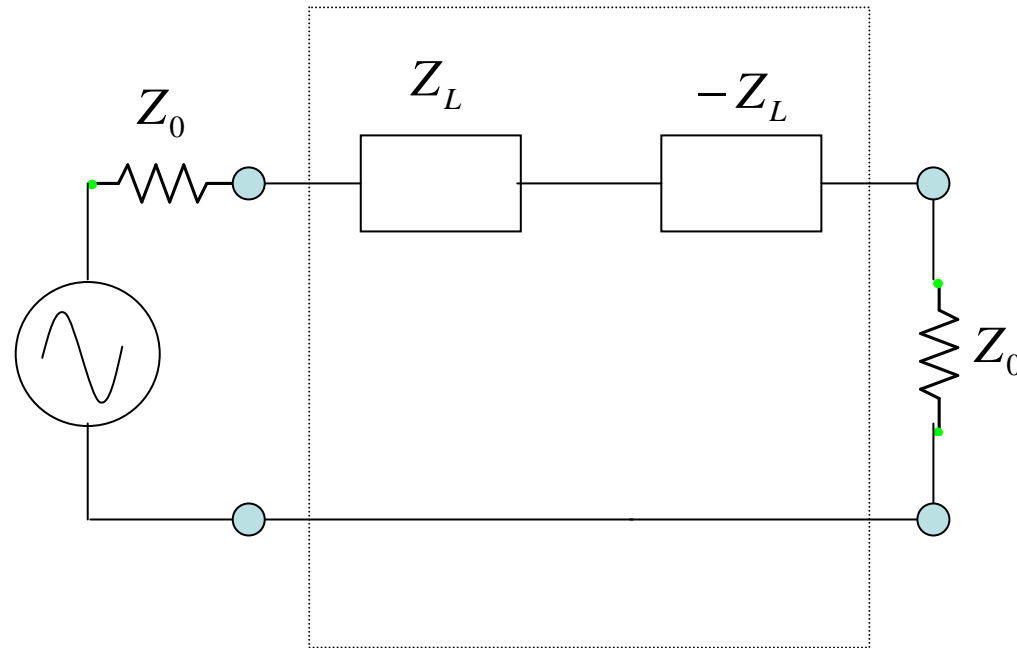


# High-Frequency BJT Device Model

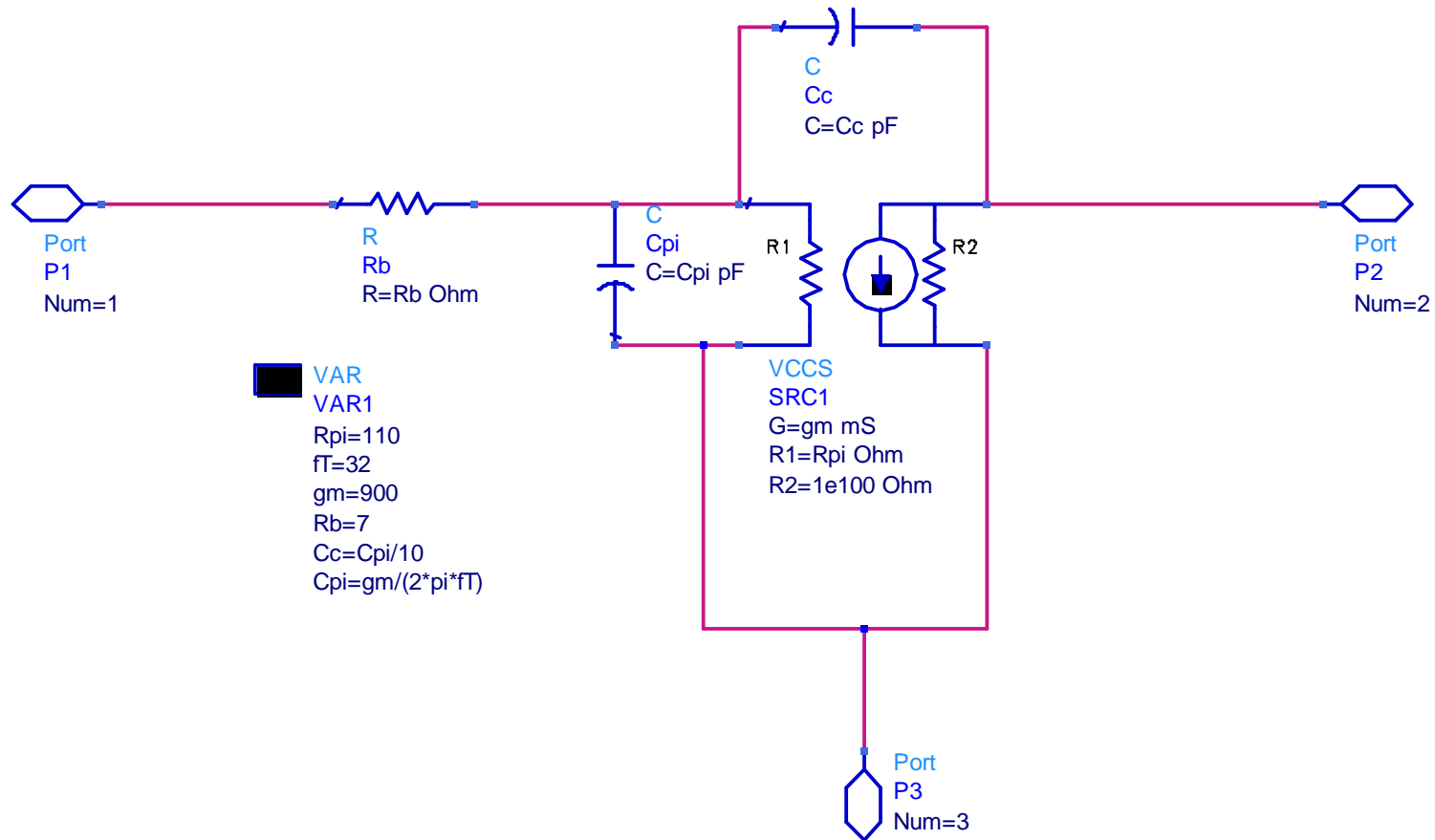





# Test Circuit Results ( $f_T = 32$ GHz)

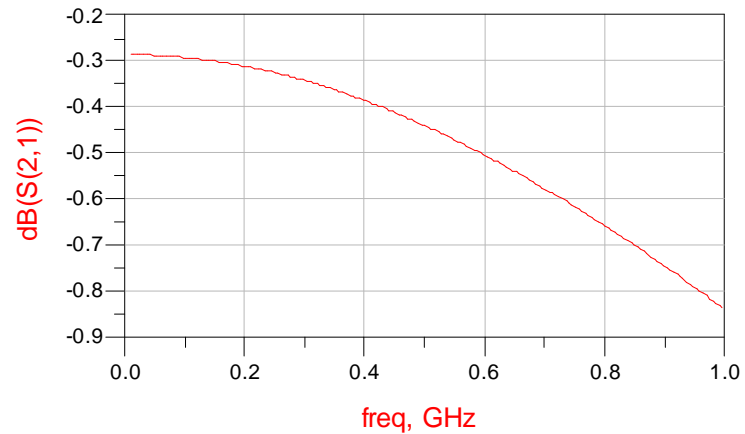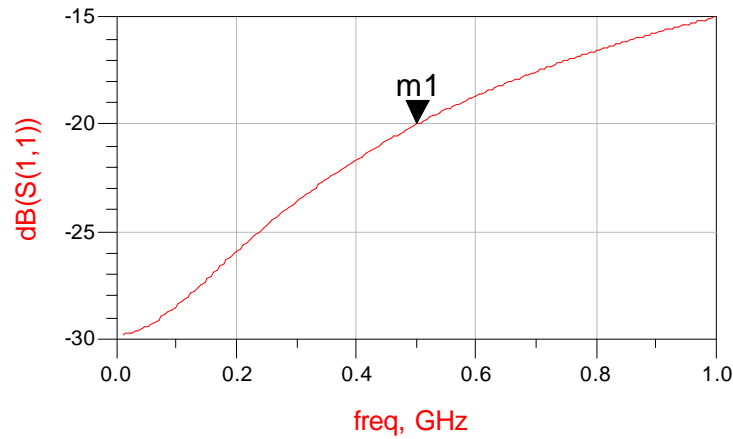



m1  
freq=502.0MHz  
dB(S(1,1))=-19.995

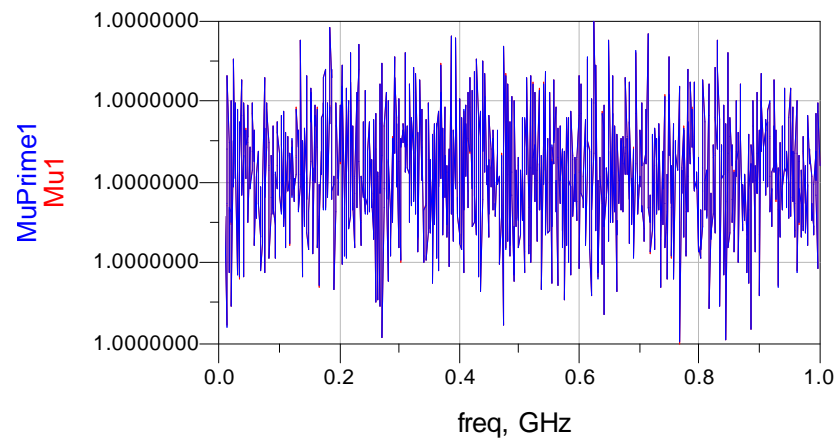


# All-Pass -20 dB RL BW v. $f_T$

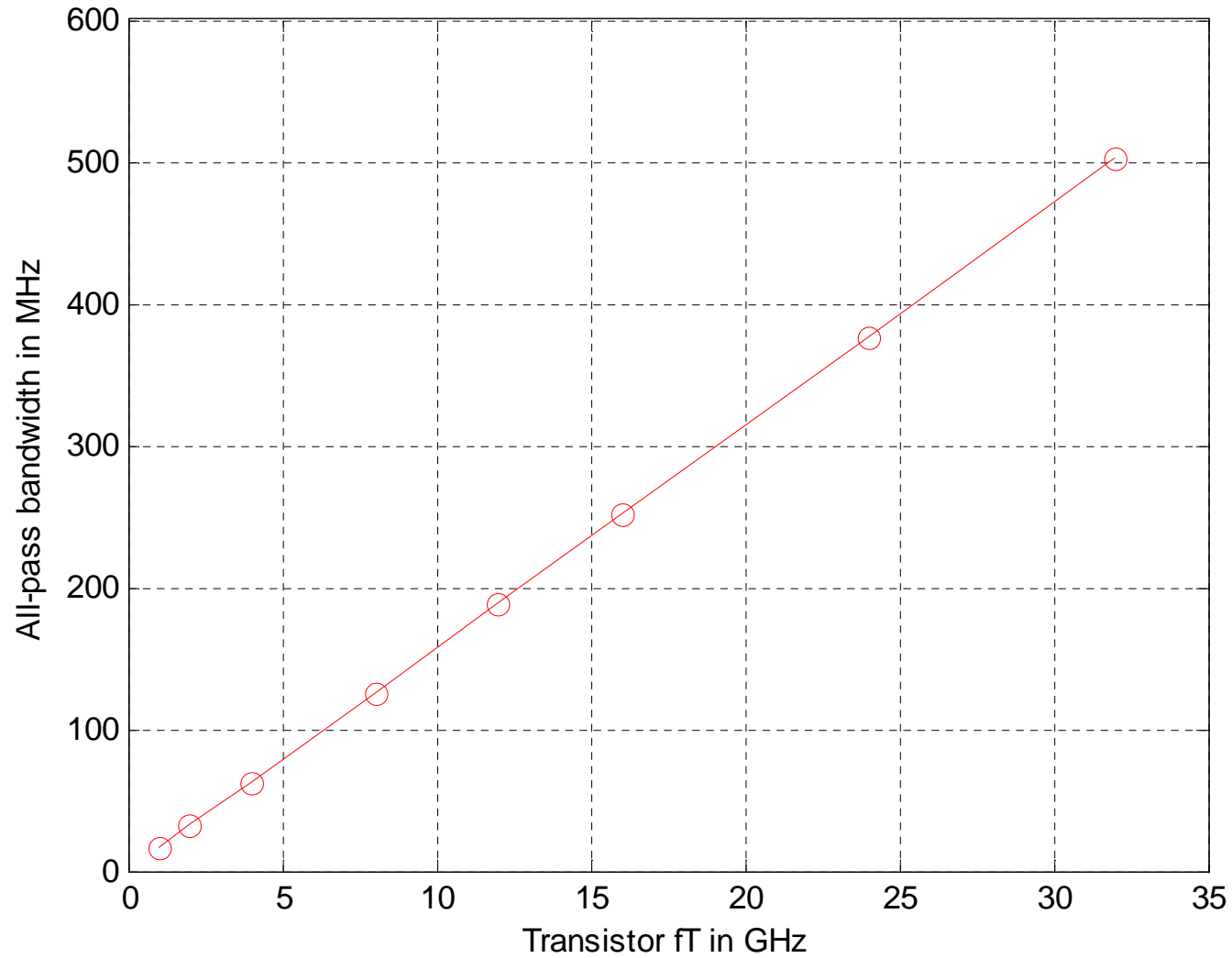
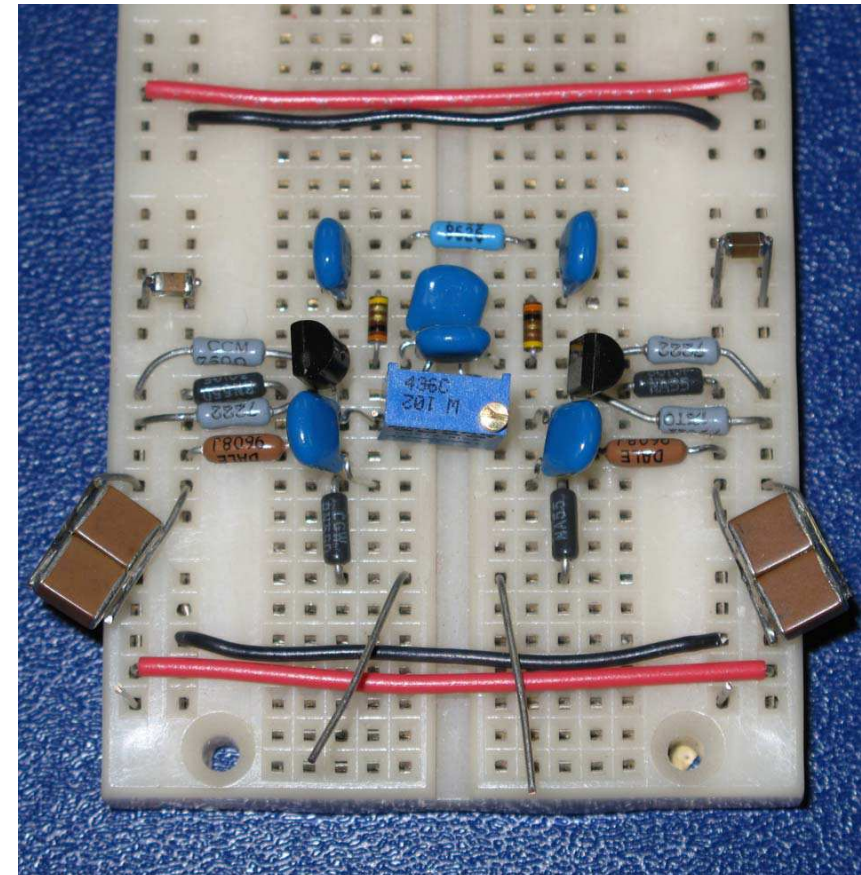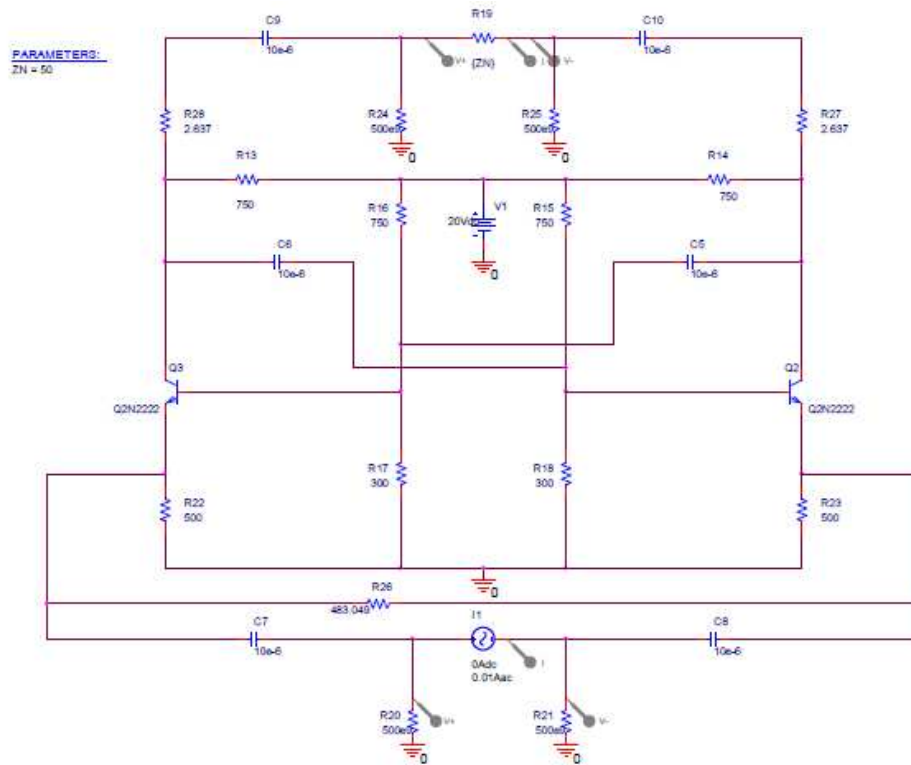
# Fabricated Two Transistor Floating NIC Using 2N2222 Devices


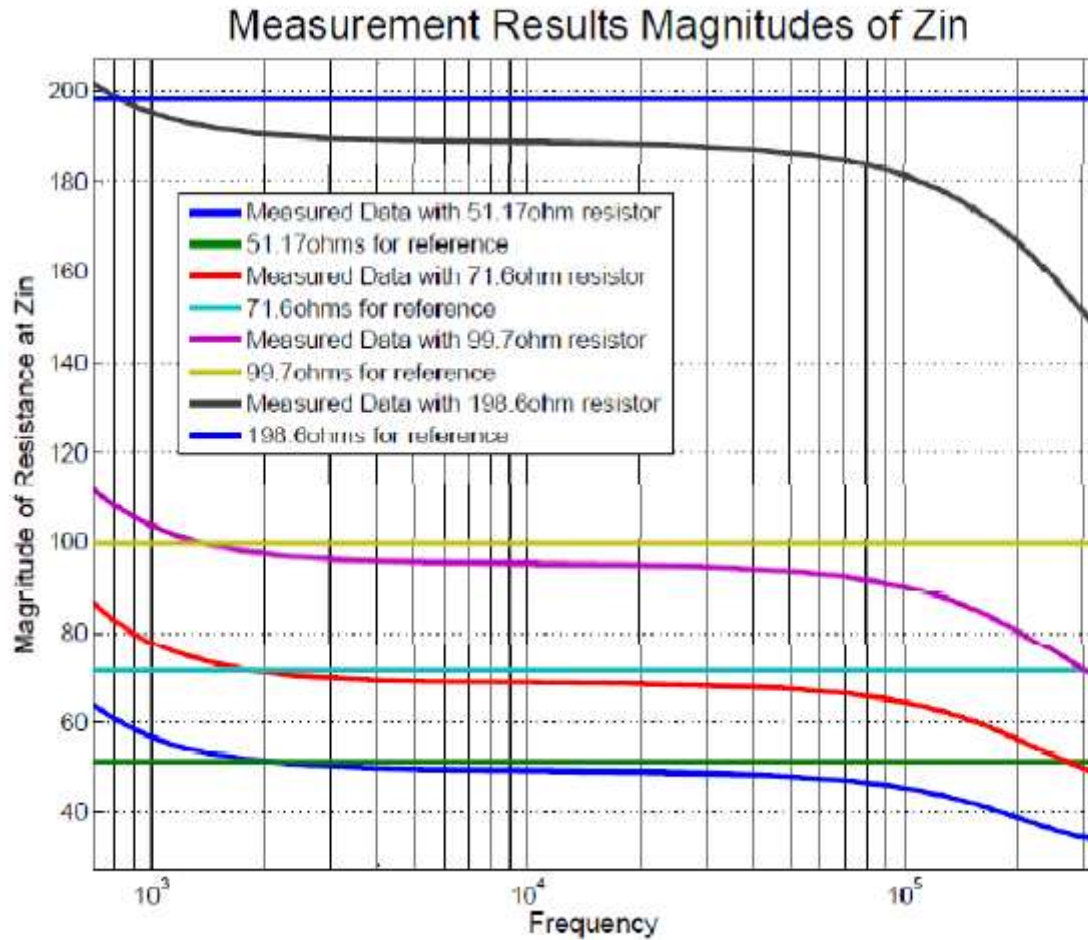
# Measured Results for Two Transistor FNIC




# Summary of NIC Developments

- We've had some successes in fabricating NICs that work up to about 50 MHz.
- We have had many more failures.
- The main issue concerns stability – small and large signal stability.
- We are making progress, albeit very slowly ...
- Someday, someone will make a reliable FNIC that works into the 100s of MHz range.

# How Best to Use a NIC to Make a Non-Foster Reactance?

- Direct negation:

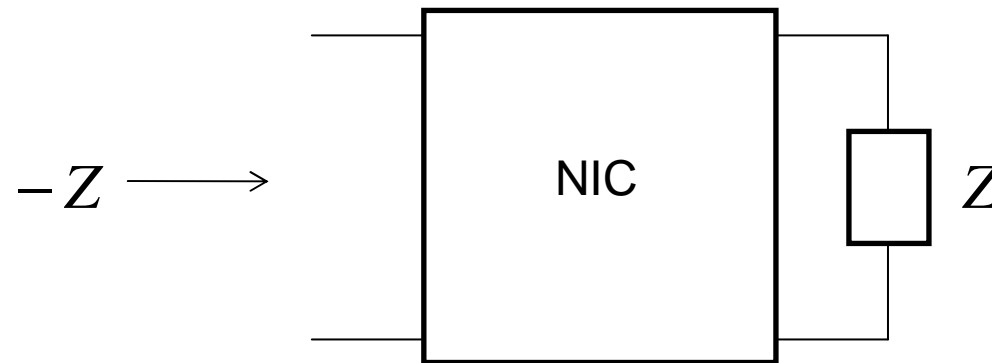

# How Best to Use a NIC to Make a Non-Foster Reactance?

- Using a certain transformation:

Verman, Proc. IRE, Apr. 1931

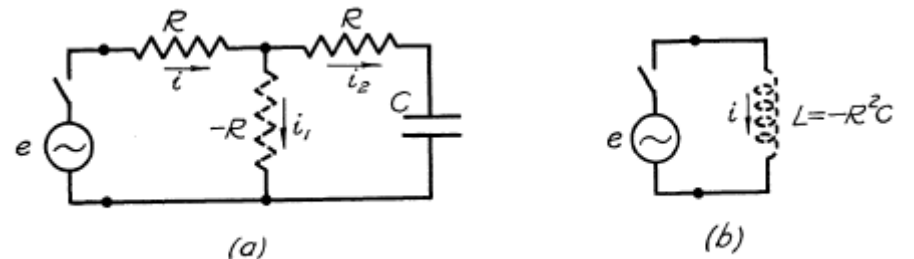


Fig. 1



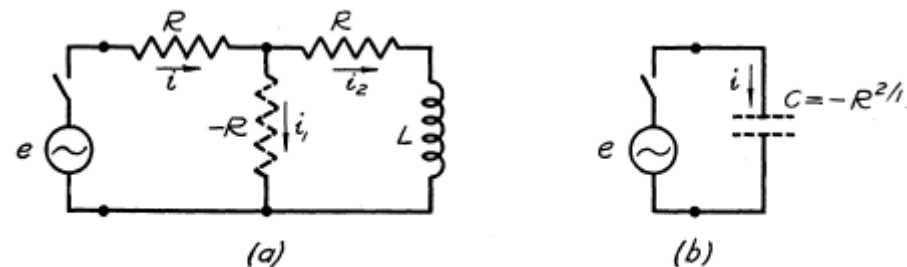


Fig. 2

# Negative Impedance Transformation

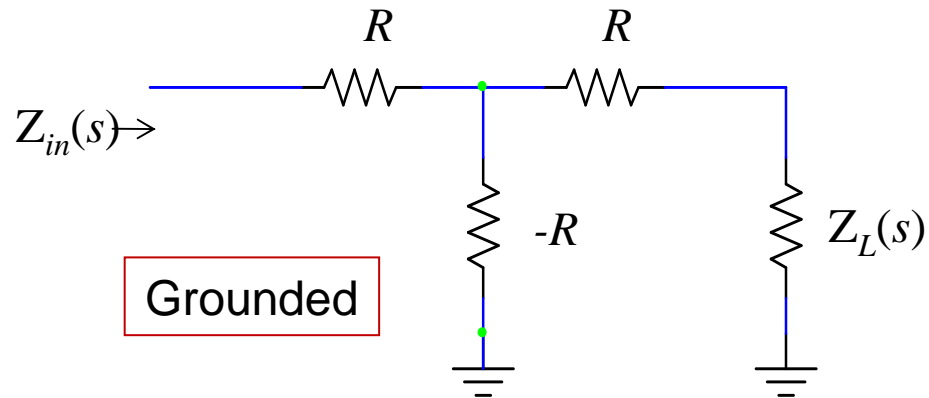

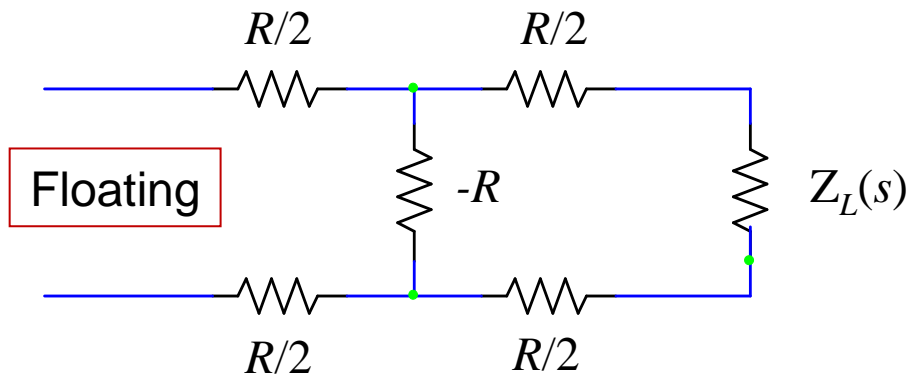- Can develop an NIC that needs to work for only one value of real impedance
- Also suggests the possibility of using negative resistance diodes (Tunnel, Gunn, etc.) for NIC realization



$$Z_{in}(s) = \frac{(R + Z_L(s))(-R)}{Z_L(s)} + R = \frac{-R^2}{Z_L(s)}$$




# Negative Impedance Transformation

$Z_L(s)$	$Z_{in}(s)$
$sL$	$\frac{-1}{sC_{neg}}$
$\frac{1}{sC}$	$-sL_{neg}$
$sL + \frac{1}{sC}$	$\frac{1}{-sC_{neg} - \frac{1}{sL_{neg}}}$
$\frac{1}{sC + \frac{1}{sL}}$	$-sL_{neg} - \frac{1}{sC_{neg}}$


$$L_{neg} = R^2 C$$

$$C_{neg} = \frac{L}{R^2}$$

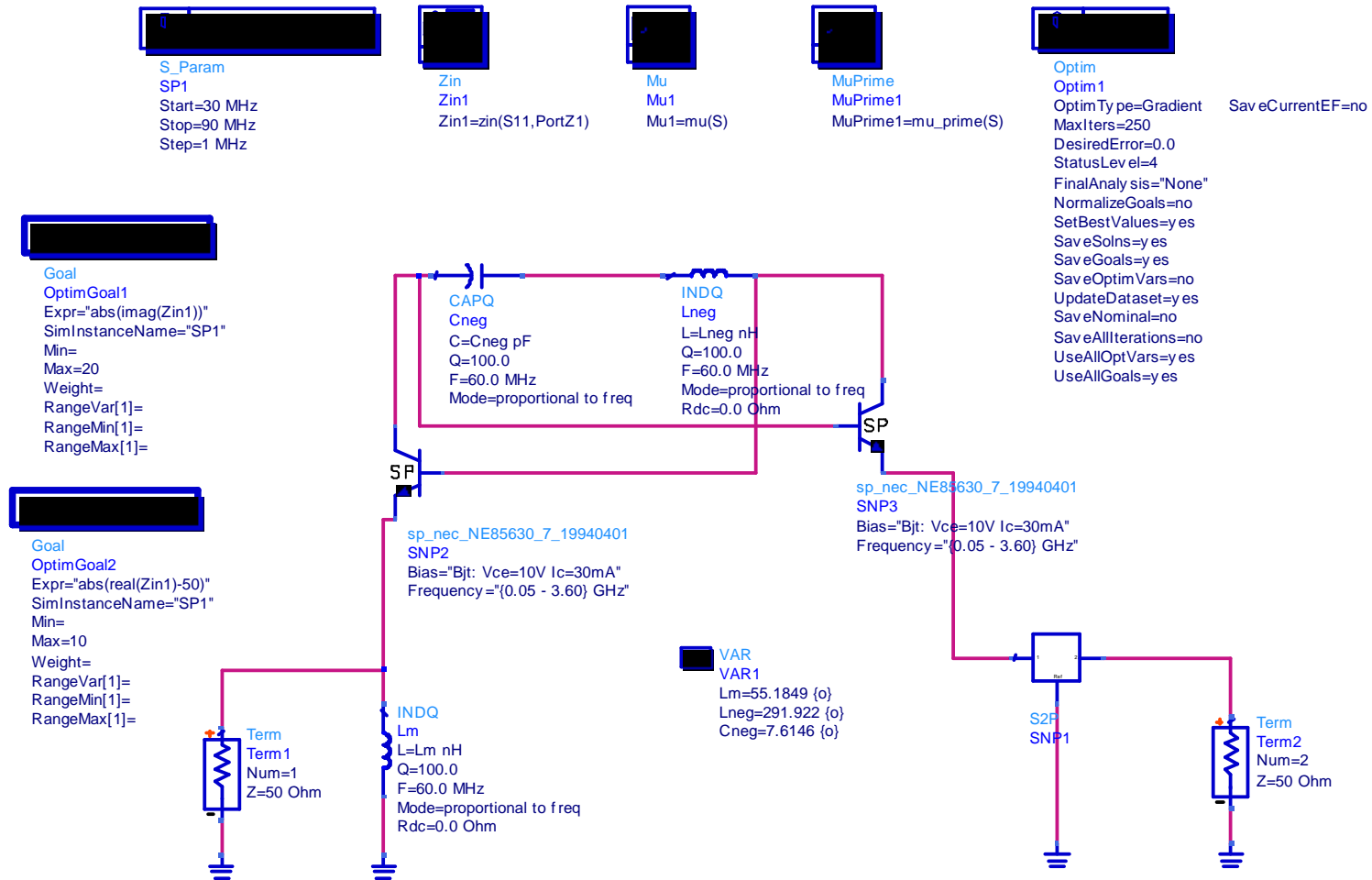
# Schematic captured from Agilent ADS of VHF monopole with active matching network



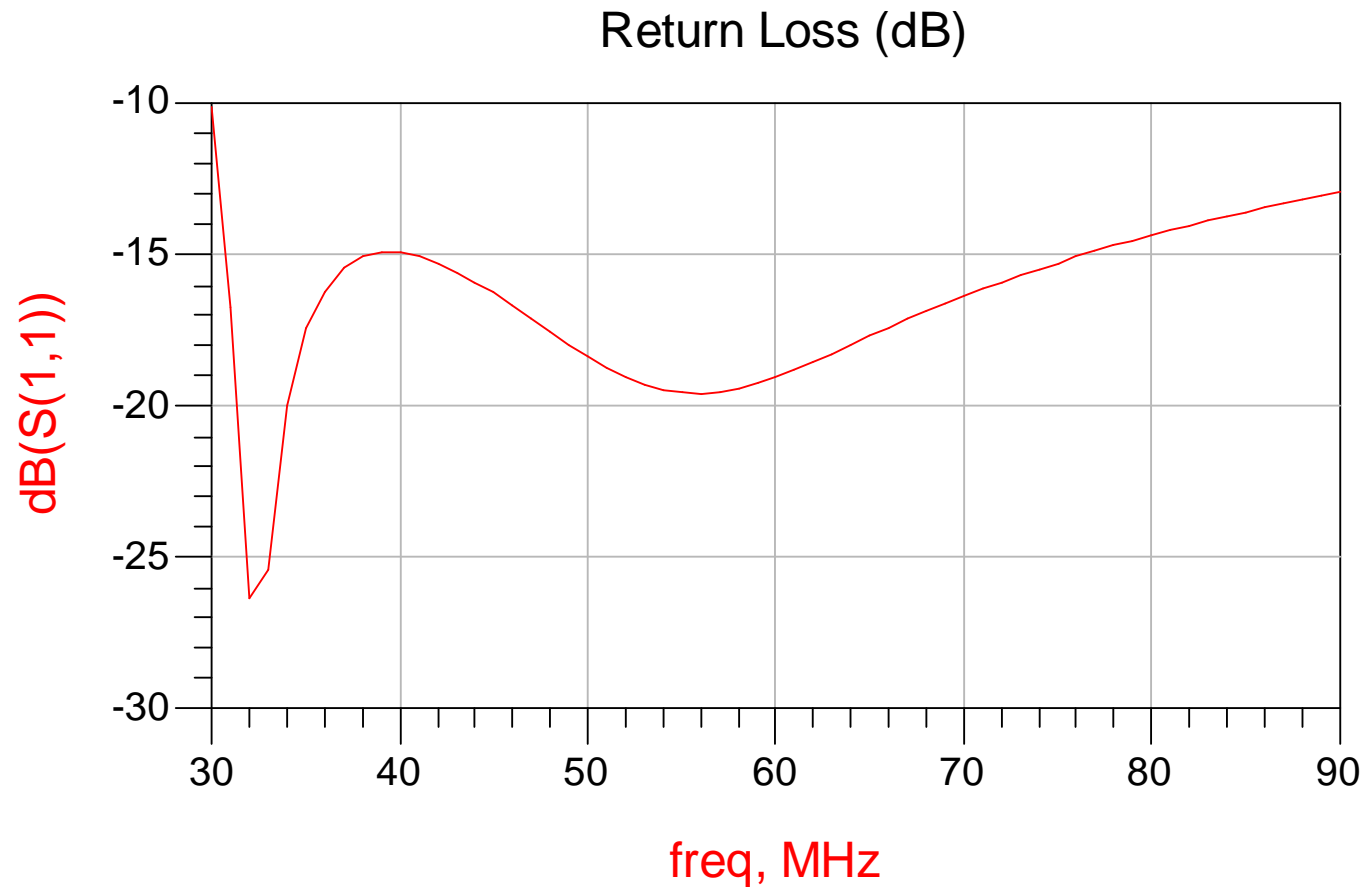
# Simulated return loss at input of optimized active matching network and antenna


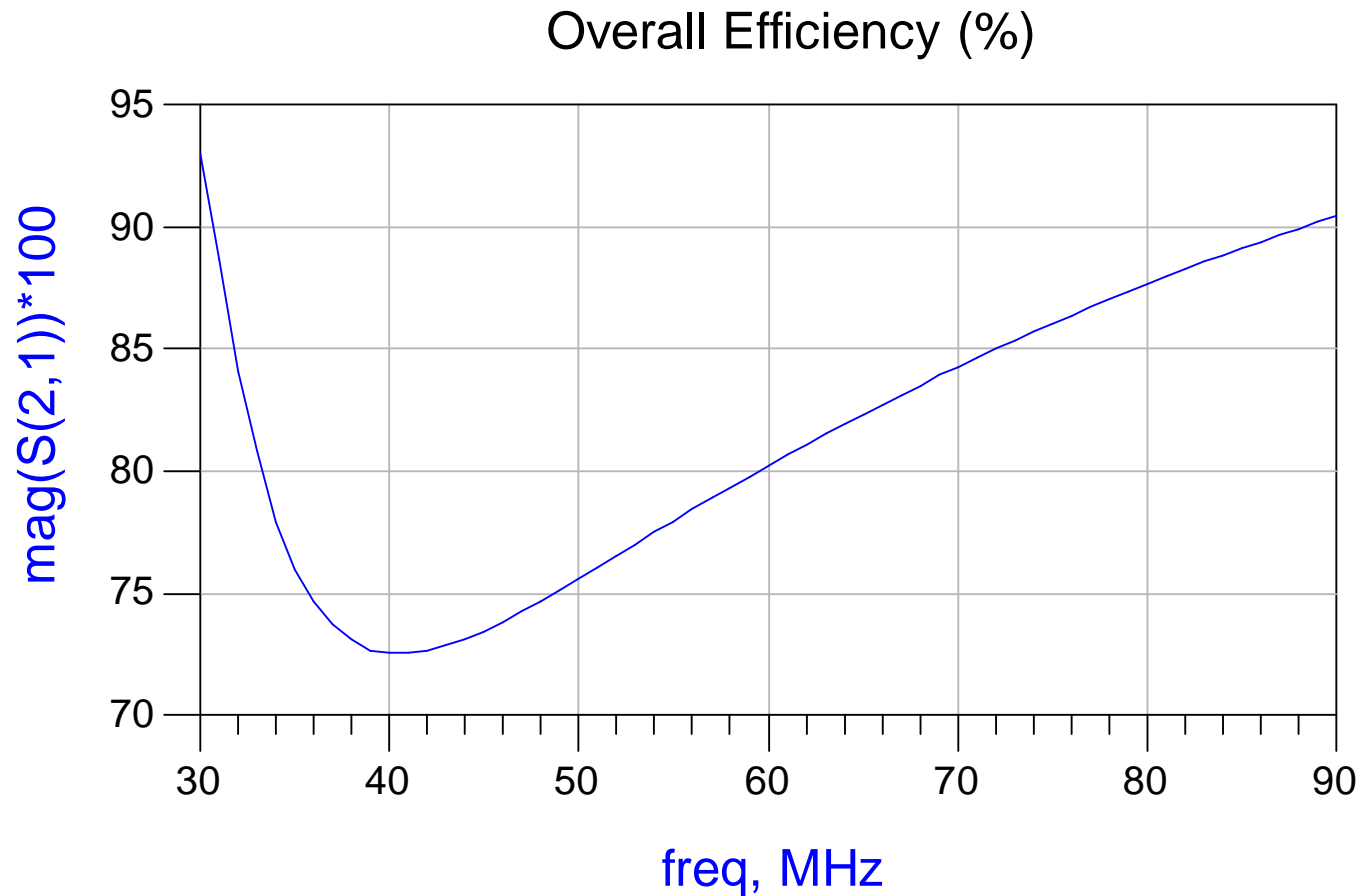
# Overall efficiency (in percent) of optimized active matching network and antenna


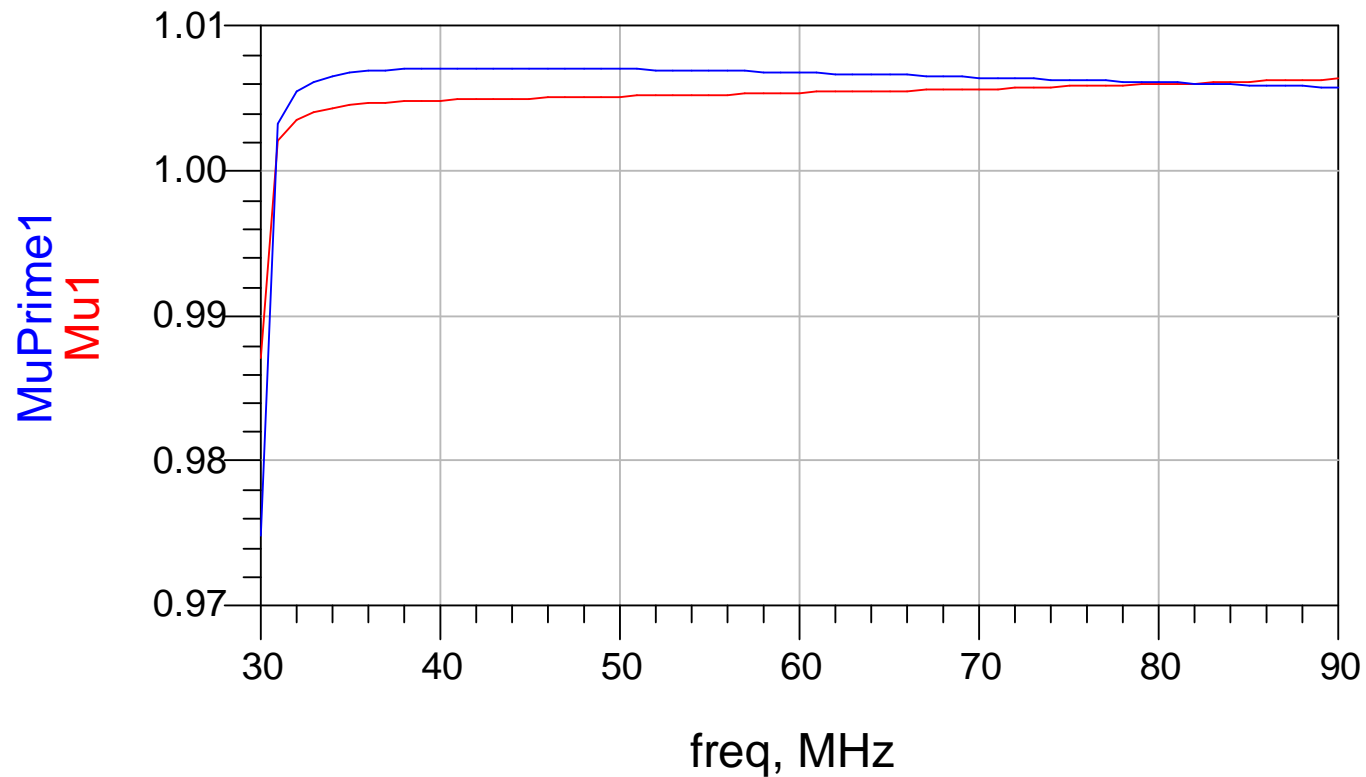
# Small-signal geometrically-derived stability factor for the optimized active matching network and antenna



# Outline of Presentation

- What Does “Non-Foster” Mean?
- Possible Applications of Non-Foster Reactances
  - Electrically Small Antennas
  - High-Impedance Surfaces
  - Artificial High-Permeability Materials
- Realization of Non-Foster Reactances

# Summary

- The use of non-Foster reactances could improve the performance of ESAs and HIGPs dramatically.
- Some hard-won successes have been achieved in the development of the requisite NICs.
- But an interdisciplinary team with expertise in circuits as well as field theory and sufficient funding is needed to realize reliable high frequency non-Foster reactances and to integrate them into electromagnetic devices.