

Design Techniques for Scalable, Sub-pJ/b Serial I/O Transceivers



Samuel Palermo

spalermo@tamu.edu

Analog & Mixed-Signal Center

Texas A&M University

Outline

- Motivation
- Power-Scalable I/O Techniques
- Low-Power Clocking
- Low-Power Equalizers
- Conclusion

More and More Data ...

Human-driven traffic growth



Hi definition video conference



facebook


amazon.com



Google



You Tube

 

Source: Cisco Global Cloud Index, 2014 - 2019




Machine-driven traffic growth



Cloud service, big data, IoT



Enterprise service

  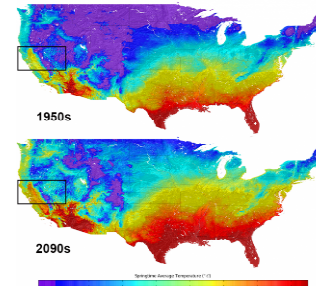


Supercomputer


High-Speed Serial I/O

- Found in applications ranging from high-end computing systems to smart mobile devices
- Typical processor platform
 - Processor-to-memory: DDR3
 - Processor-to-peripheral: PCIe & USB
 - Storage: SATA
 - Network: LAN
- Mobile systems
 - DSI : Display Serial Interface
 - CSI : Camera Serial Interface
 - UniPRO : MIPI Universal Protocol

Intel IvyBridge w/ Chipset

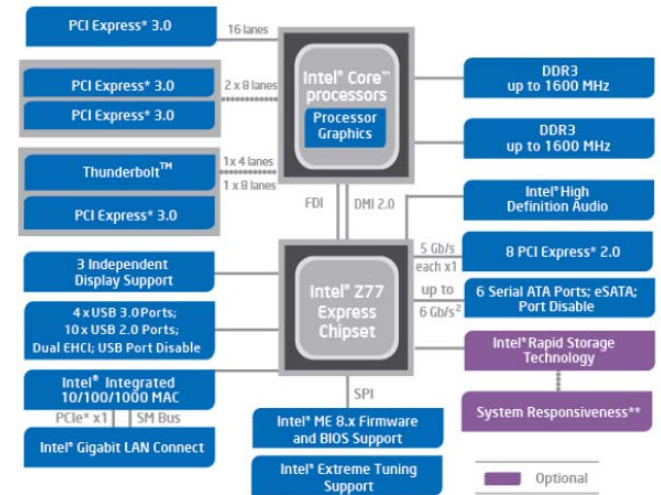


High-Speed Electrical Link System

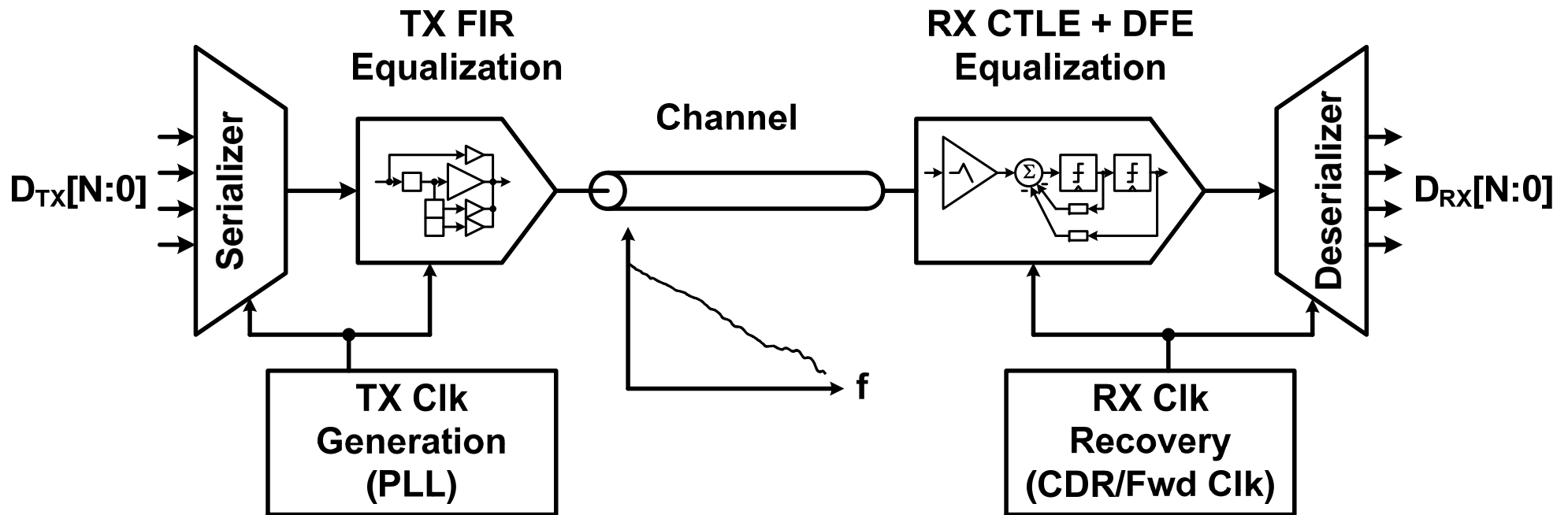

- Data serialization required due to limited I/O channel count
- Future systems demand efficient high-speed drivers, receivers, and clock generation/recovery circuitry
- Equalization circuitry compensates for high frequency channel loss

I/O Energy Efficiency is Paramount

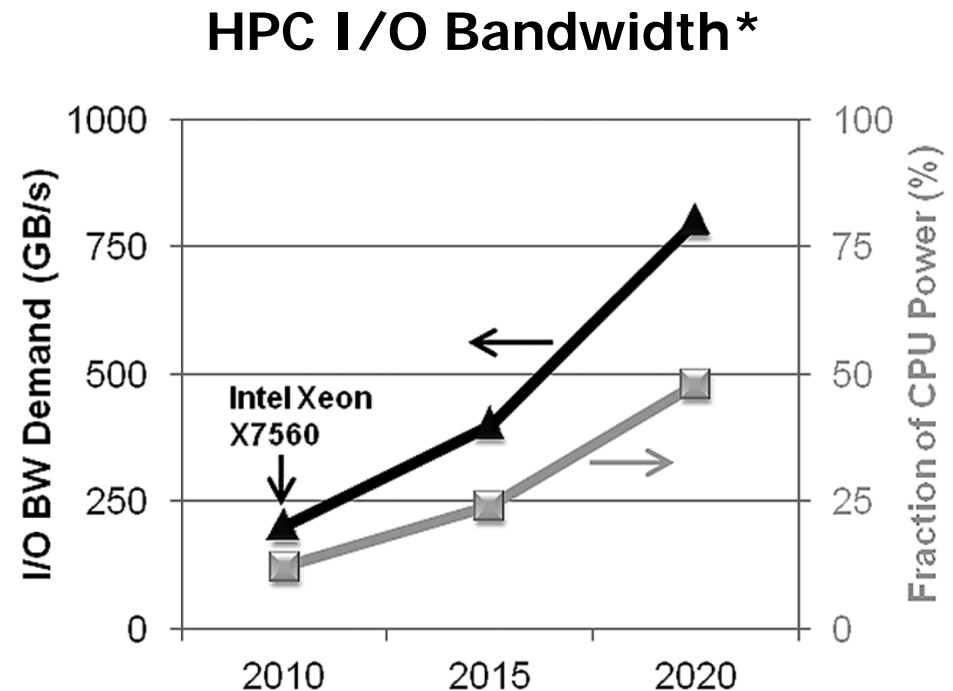- High-performance processor aggregate I/O bandwidth demands will soon approach 1TB/s
- Typical I/O power budgets are 10W or less
- Energy efficiencies near 1mW/Gbps are necessary





*M. Mansuri *et al*, "A Scalable 0.128–1 Tb/s, 0.8–2.6 pJ/bit, 64-Lane Parallel I/O in 32-nm CMOS," *IEEE JSSC*, Dec. 2013.

Outline

- Motivation
- Power-Scalable I/O Techniques
- Low-Power Clocking
- Low-Power Equalizers
- Conclusion


Scaling Supply with Data Rate

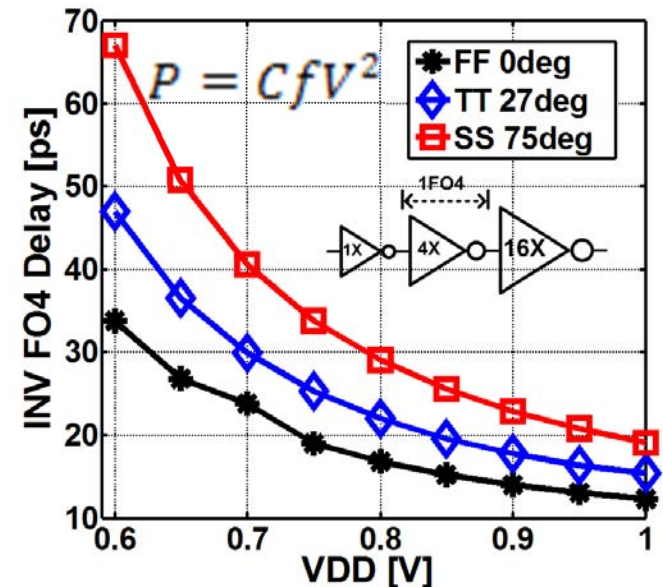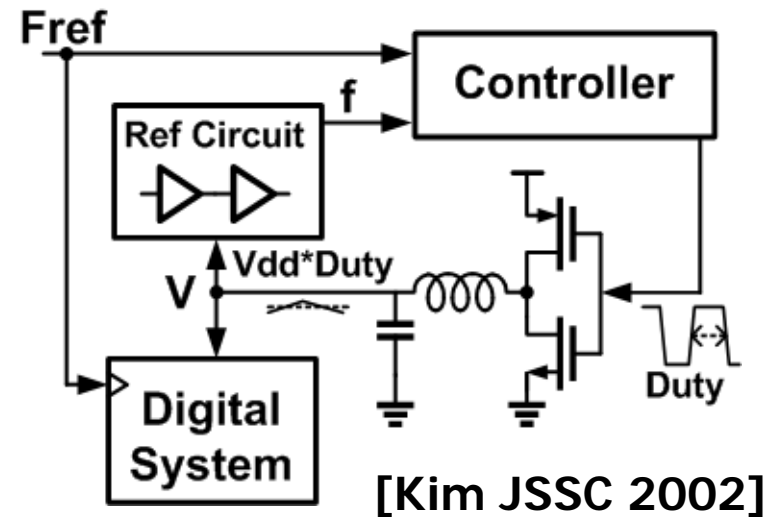- Adaptive power supply regulation allows the minimum voltage required for a given data rate
- Efficient DC-DC converters driven by a frequency controller generate the supply voltage for the I/O clocking and serialization
- Dramatic energy efficiency improvements possible, particularly as data rates scale down based on I/O bandwidth demand



* GP 65nm CMOS Technology


Increasing Data Rate with Parallelism

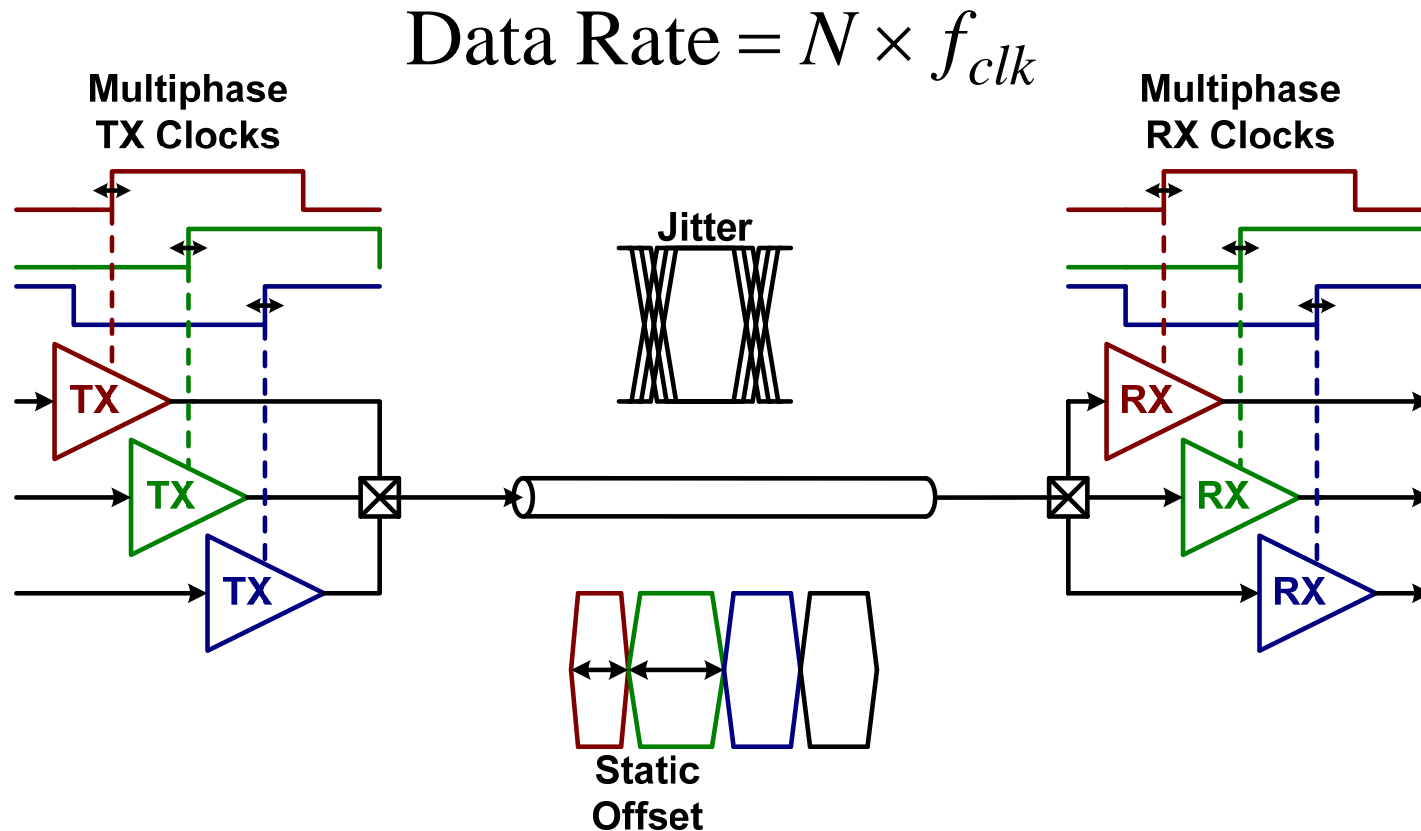

- Utilizing large mux/demux factors allows parallel segments to operate at low clock frequencies and low supply voltages
- Important to minimize jitter and static phase offset of multiple clock phases


Fast Power-State Transitioning

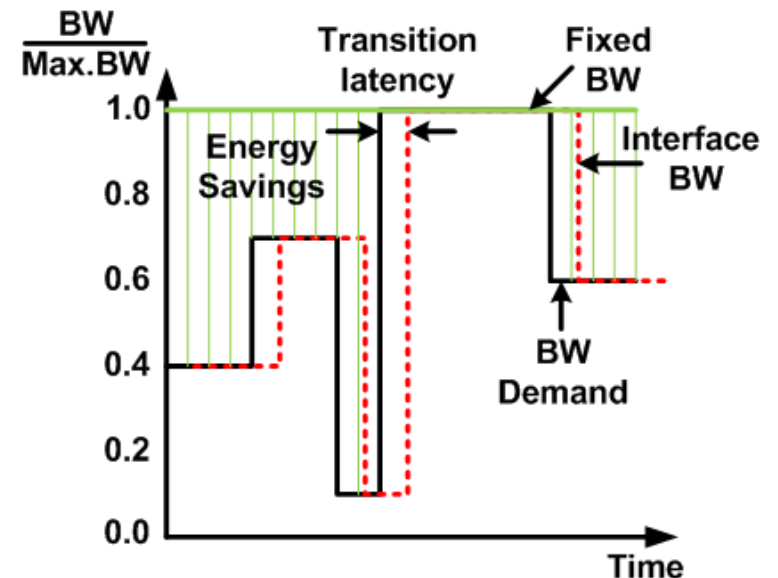- Efficient system operation demands minimal latency when adjusting the I/O per-channel data rates
- Certain applications, such as memory interfaces, have bursts of data traffic which necessitate rapidly achieving maximum I/O bandwidth
- Techniques must be developed to enable fast power-state transitioning of key I/O circuits




[O'Mahony VLSI-DAT 2009]

Low-Swing TX Driver Comparison

 

Current-Mode Driver (CM)

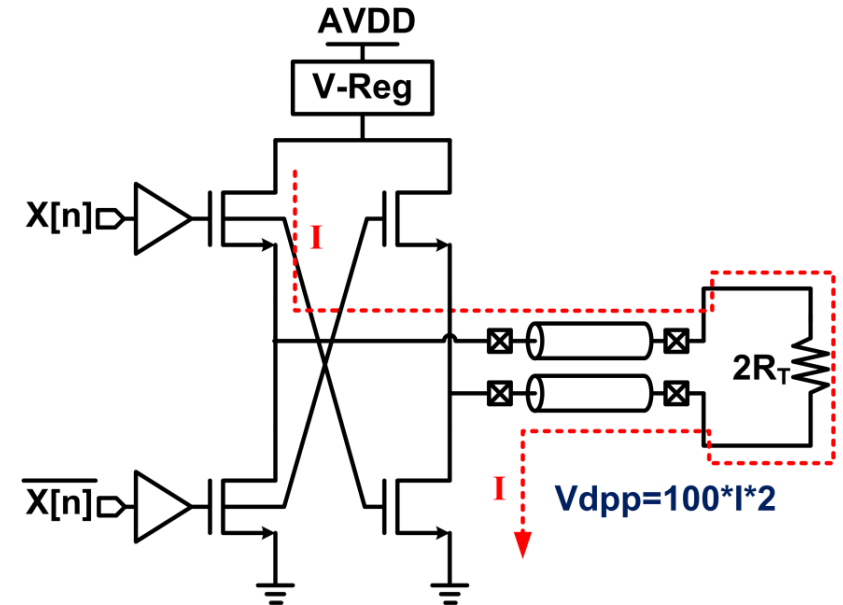- ☺ Norton-equivalent parallel termination
- ☺ High PSRR
- ☺ Low pre-driver complexity
- ☹ High signaling power




Voltage-Mode Driver (VM)

- ☹ Thevenin-equivalent series termination
- ☹ Voltage-regulator is required
- ☺ $\frac{1}{4}$ signaling power of CM


VM driver uses 4X less current than CM driver

Low-Voltage Serial I/O Transceiver

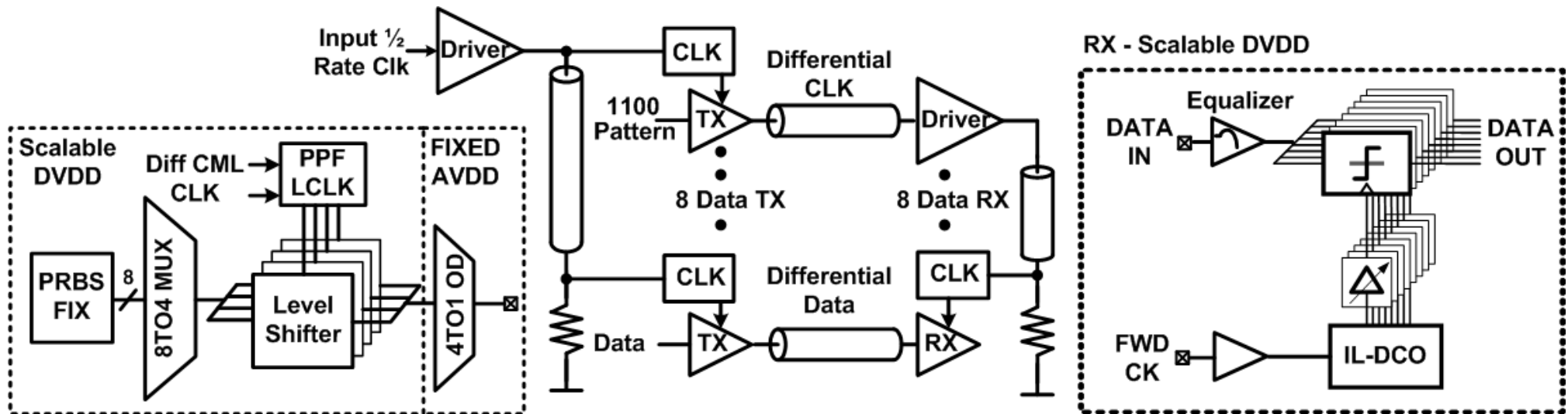


- Utilizes a high TX output multiplexing (4:1) and RX input multiplexing (1:8) factor for low-voltage operation

4:1 Output Multiplexing Voltage-Mode TX

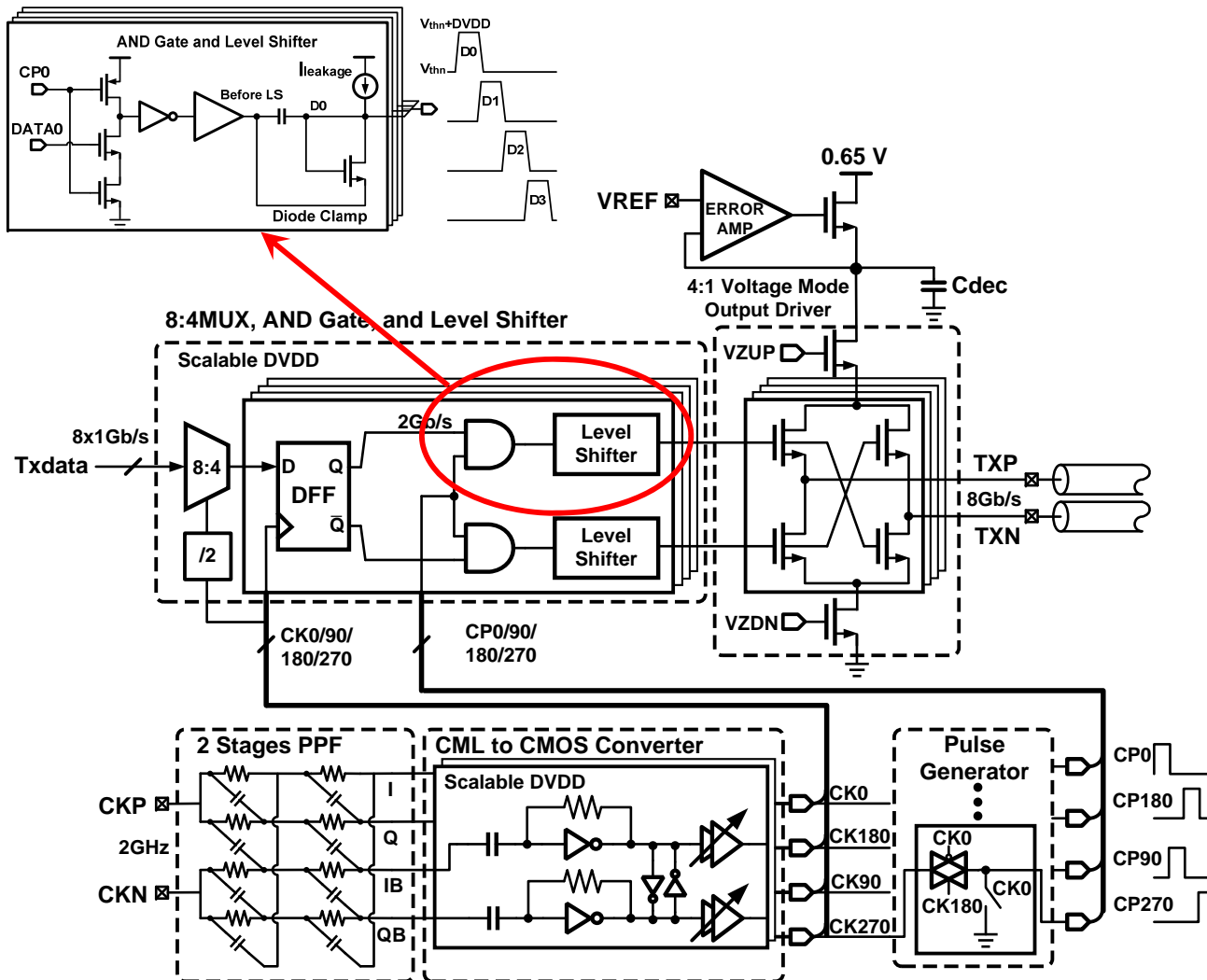



- 4 parallel voltage-mode output segments perform output multiplexing
- Efficient quadrature clock generation with 2-stage poly-phase filter
- Level-shifting pre-driver allows for smaller output transistors

1:8 Input De-Multiplexing RX


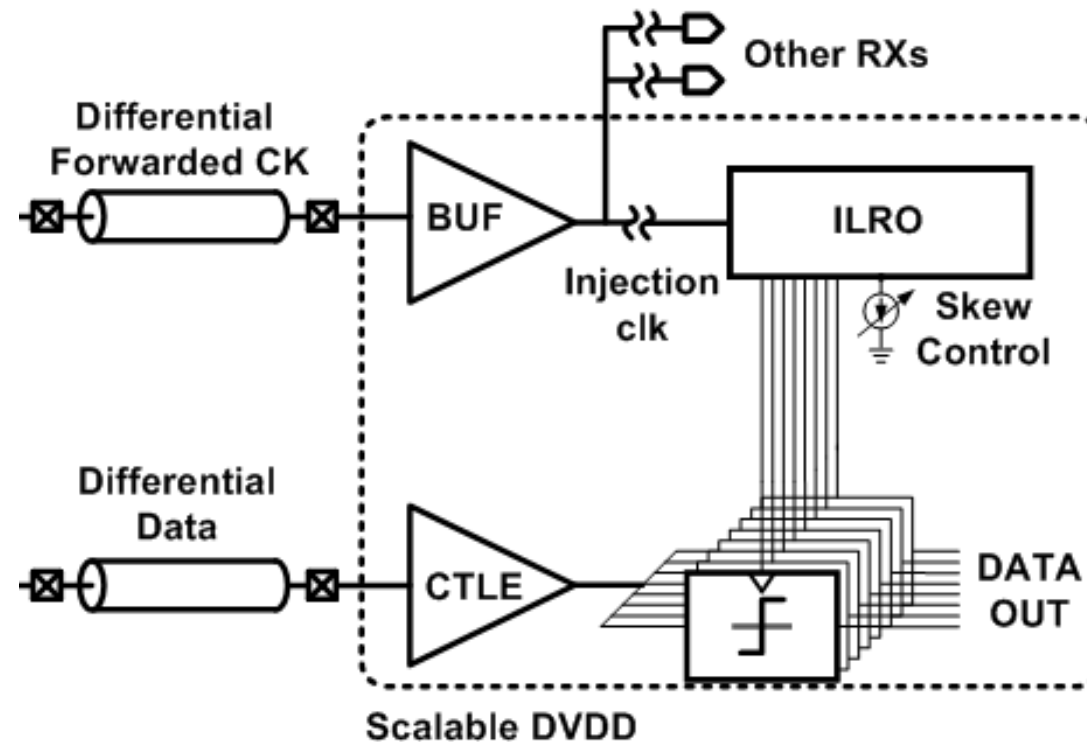


- 1:8 input de-multiplexing allows input comparators to operate at low voltages
- Injection-locked-oscillator is used for efficient multi-phase clock generation and de-skew

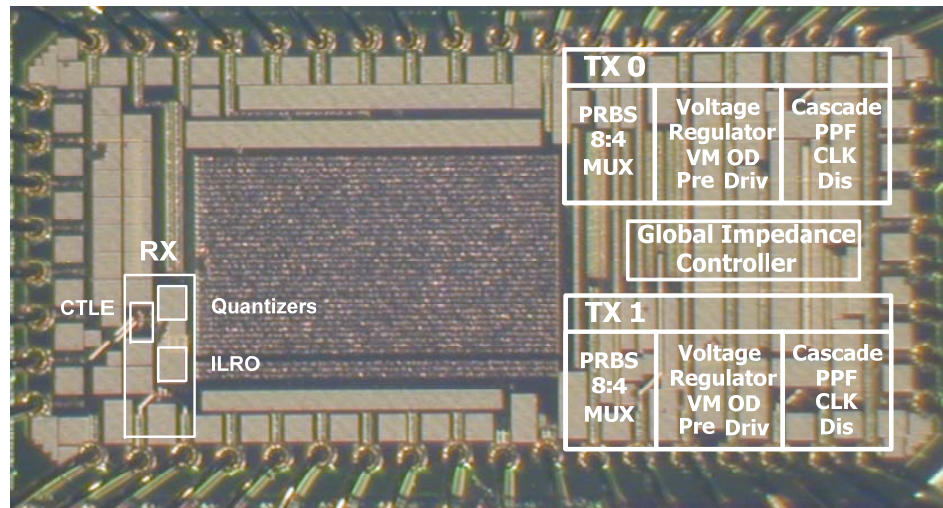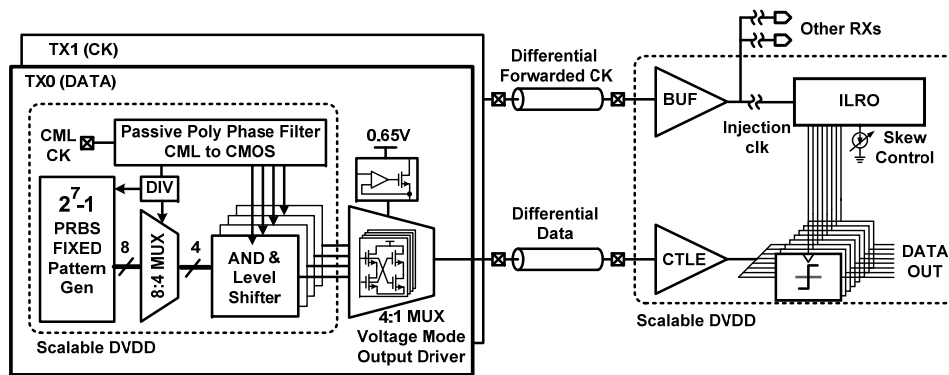0.47-0.66pJ/bit, 4.8-8Gb/s GP 65nm CMOS Prototype



Testing with 20cm FR-4 Channel

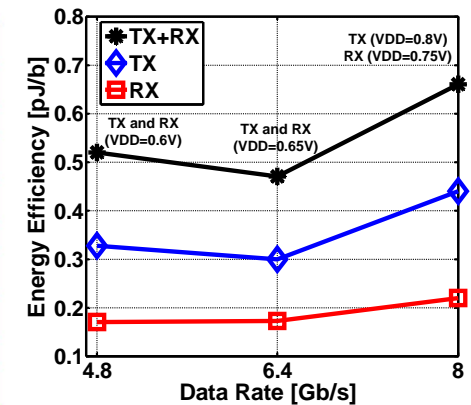 

TX Power Breakdown (6.4Gb/s at 0.65V)	
LDO & Output Driver (150mV _{ppd})	793uW
Serializer, Pre-drivers, Clocking	933uW
Global Impedance Control (amortized across 9 TX)	193uW
TX Energy Efficiency	0.3pJ/b
RX Power Breakdown (6.4Gb/s at 0.65V)	
CTLE, Quantizers, ILRO	1.07mW
Clock Distribution	38uW
RX Energy Efficiency	0.17pJ/b
Total Energy Efficiency	0.47pJ/b


- Optimal 0.47pJ/b energy efficiency achieved at 6.4Gb/s
 - At low data rates, less amortization of static current
 - At high data rates, higher voltage required for serialization timing

Outline


- Motivation
- Power-Scalable I/O Techniques
- **Low-Power Clocking**
- Low-Power Equalizers
- Conclusion

Low-Power Transmitter Clocking

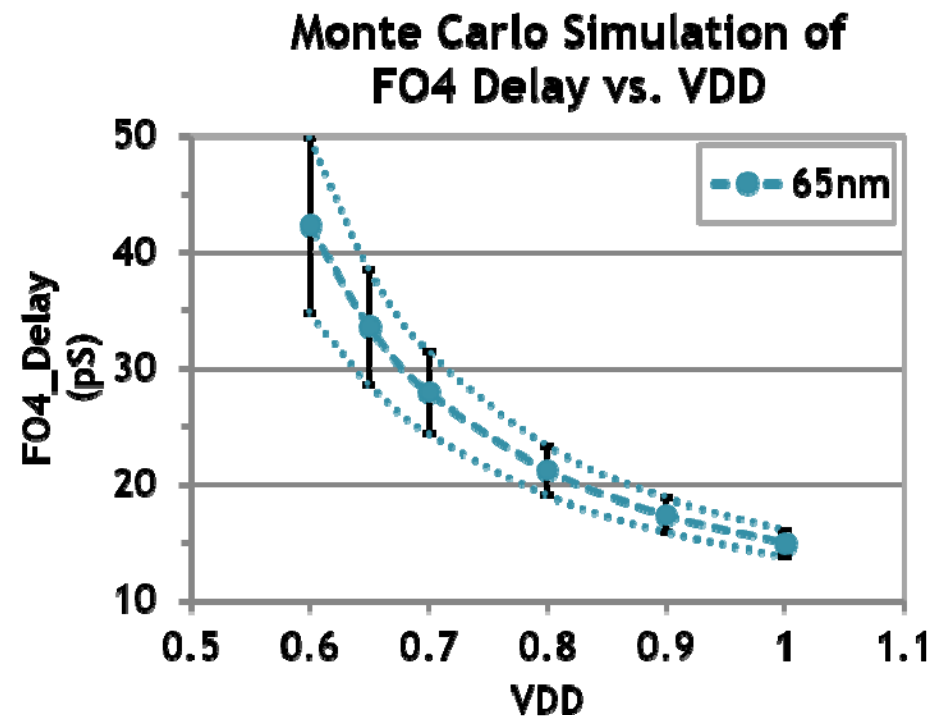
- Transmitters which utilize voltage-scaling to save power require efficient generation of multi-phase clocks
- Key issue is the extreme phase variations faced with low-voltage operation



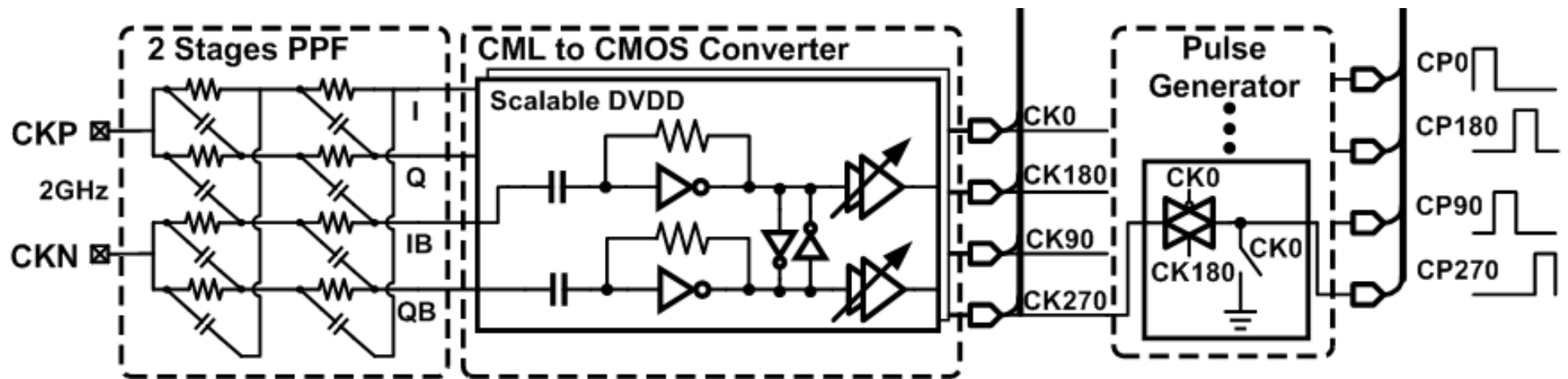Passive Poly-Phase Filter Clock Generation





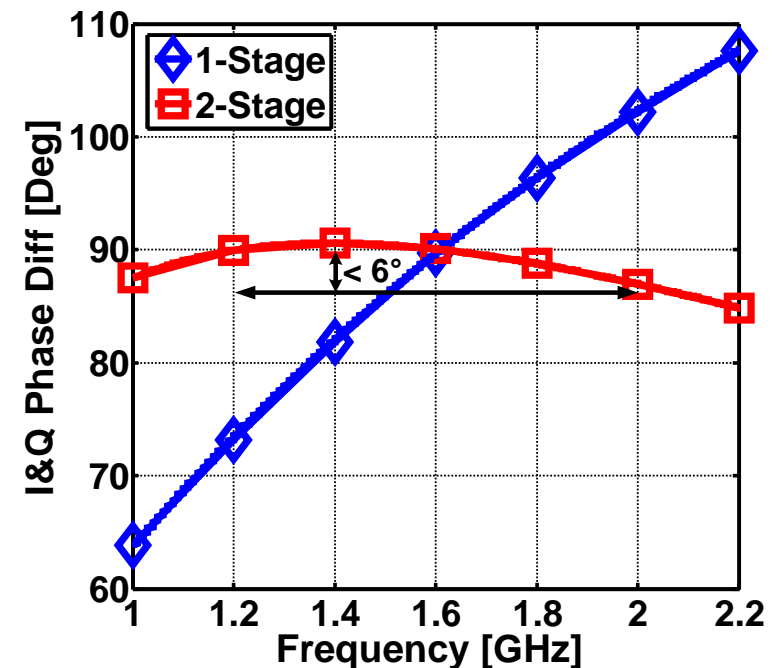- 2-stage passive poly-phase filter generates 4 clock phases for output multiplexing from low-swing global TX $\frac{1}{4}$ -rate differential clocks
- Requires subsequent CML2CMOS converter to generate TX clocks



Injection-Locked Oscillator (ILO) Clock Generation


Diff. ¼-Rate CLK

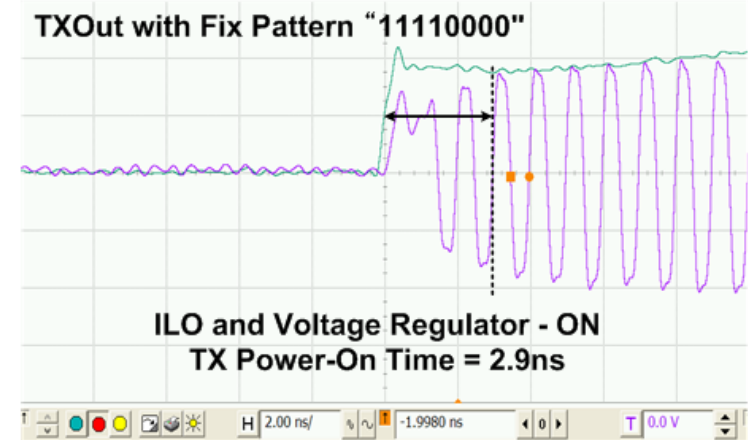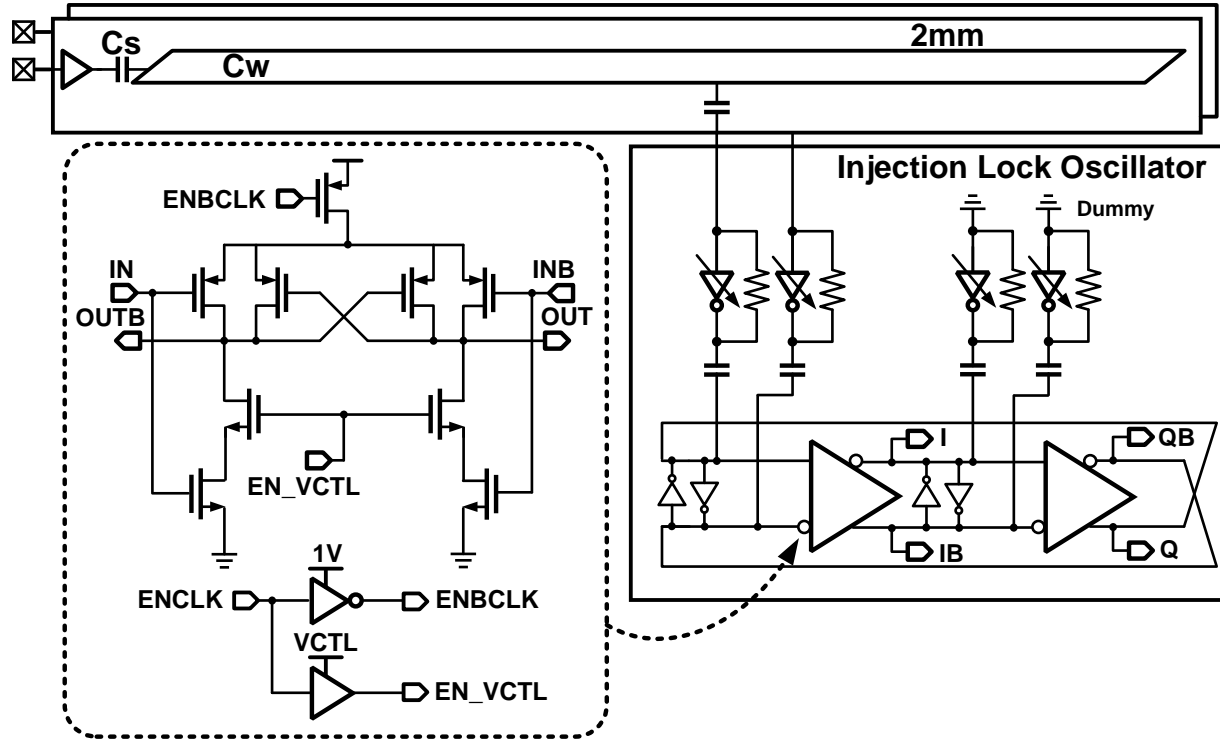


- 4-phase CLK generation by ILO
 - Eliminates CML2CMOS convertor
 - Fine frequency control by EN_VCTL also enables fast power state transition

Async. Sampling Based Phase Calibration

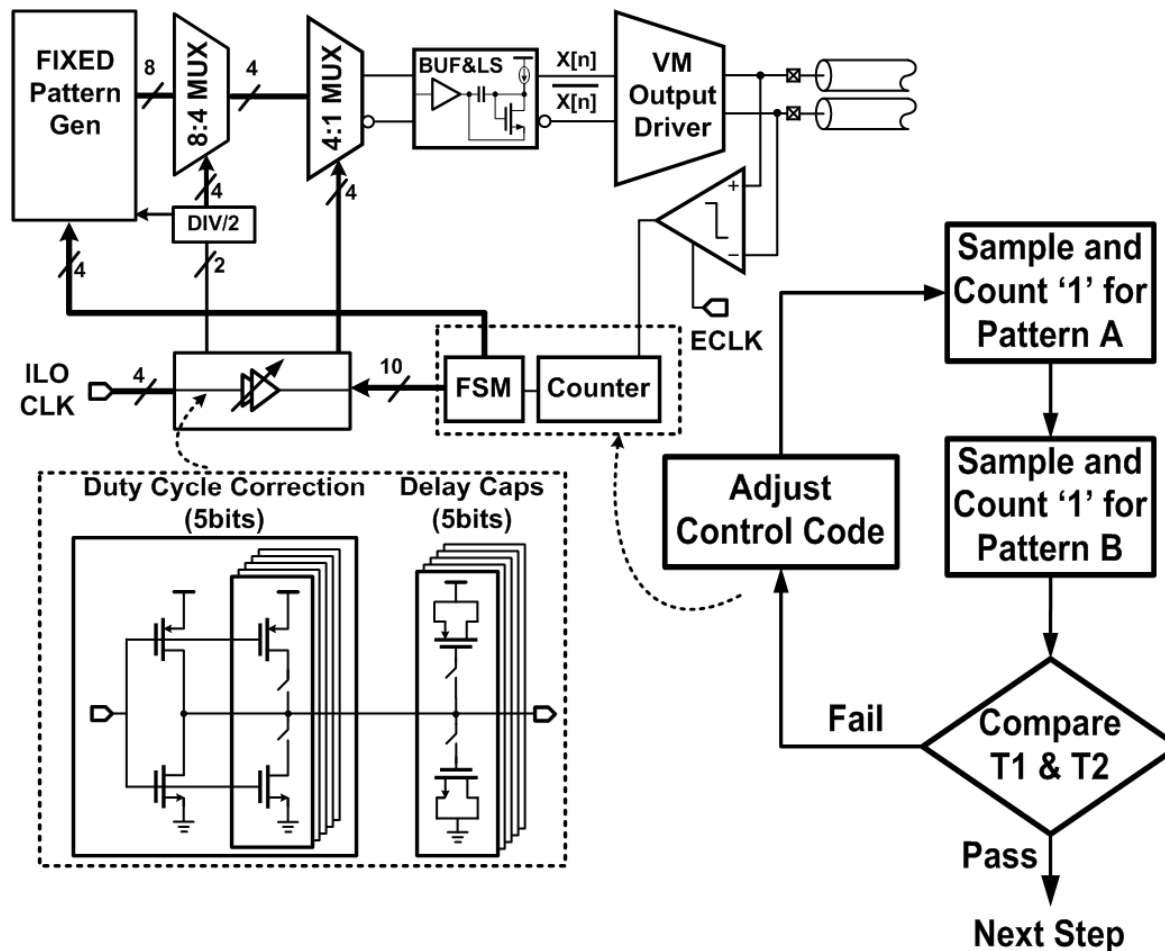
- Compensates for deterministic jitter (DJ) due to duty-cycle distortion (DCD) and phase mismatches of quadrature clocks



Step 1 : Duty Cycle Correction

 

Step 2 : Quadrature Correction

 


Automatic Phase Correction

- Eye diagrams without and with phase calibration




8Gb/s

16Gb/s

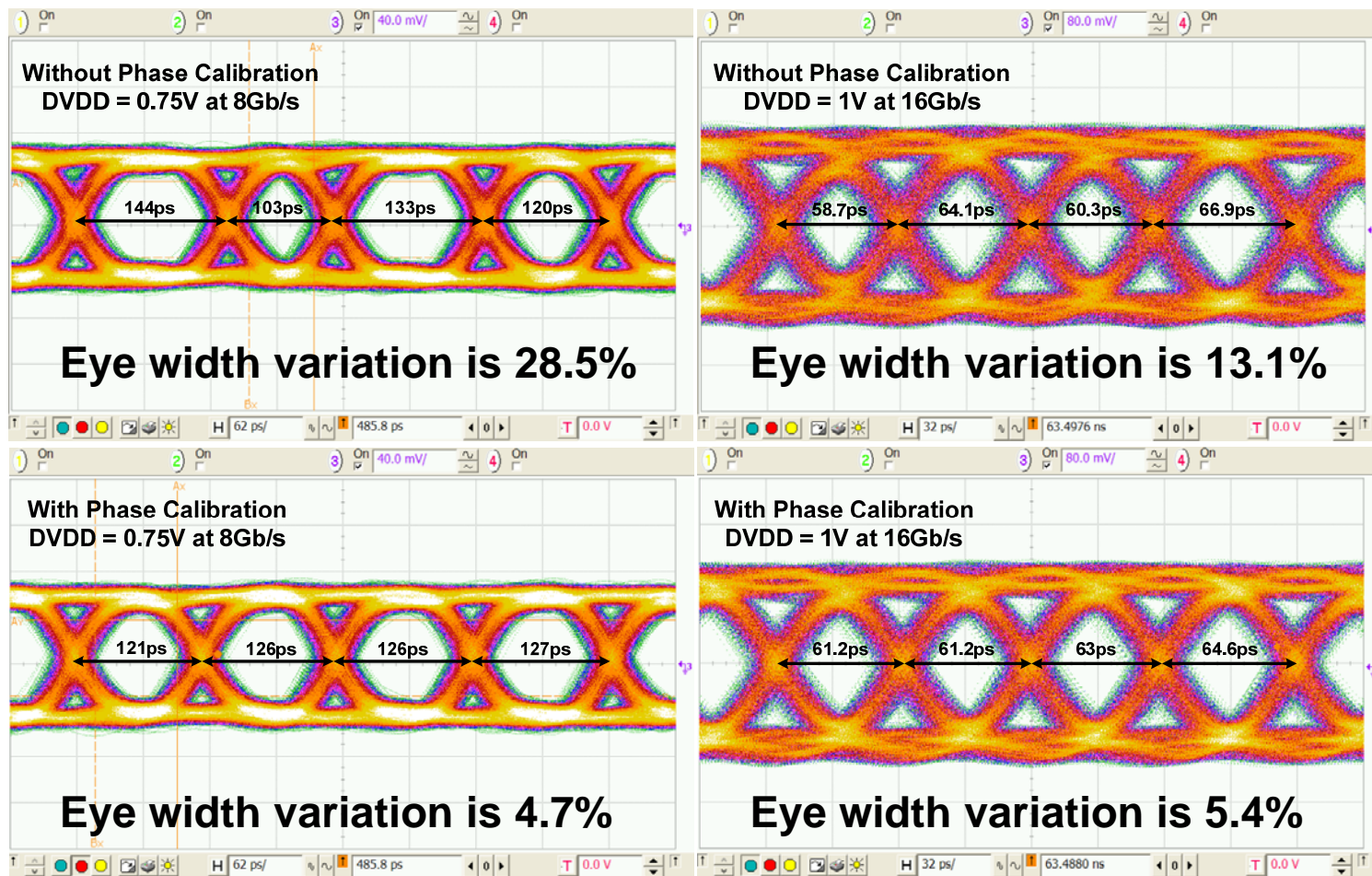

RX-Forwarded Clock I/O De-Skew

  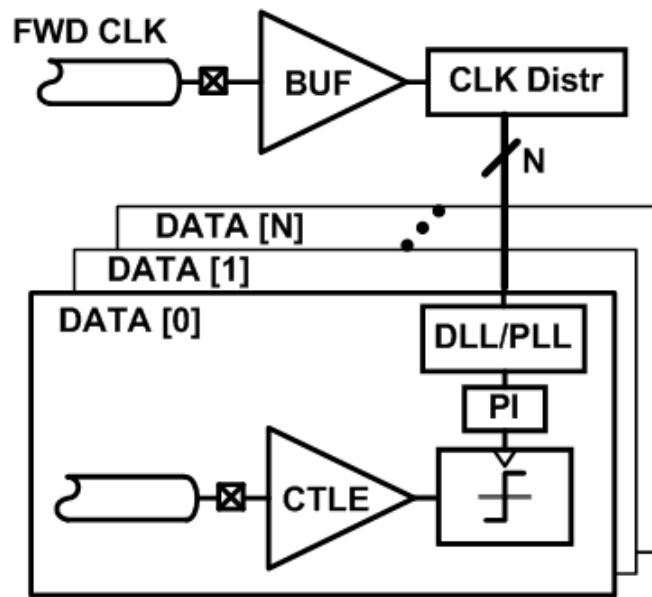- “Coherent” clocking allows jitter tracking, but still need to employ per-channel de-skew to maximize timing margins





DLL/PLL + Phase Interpolator (PI)

- DLL can have jitter amplification, while PLL can have jitter accumulation
- Both circuits can occupy significant area

Injection-Locked Oscillator (ILO)


- Compact low-power implementation
- High jitter tracking bandwidth

ILO-Based De-Skew

 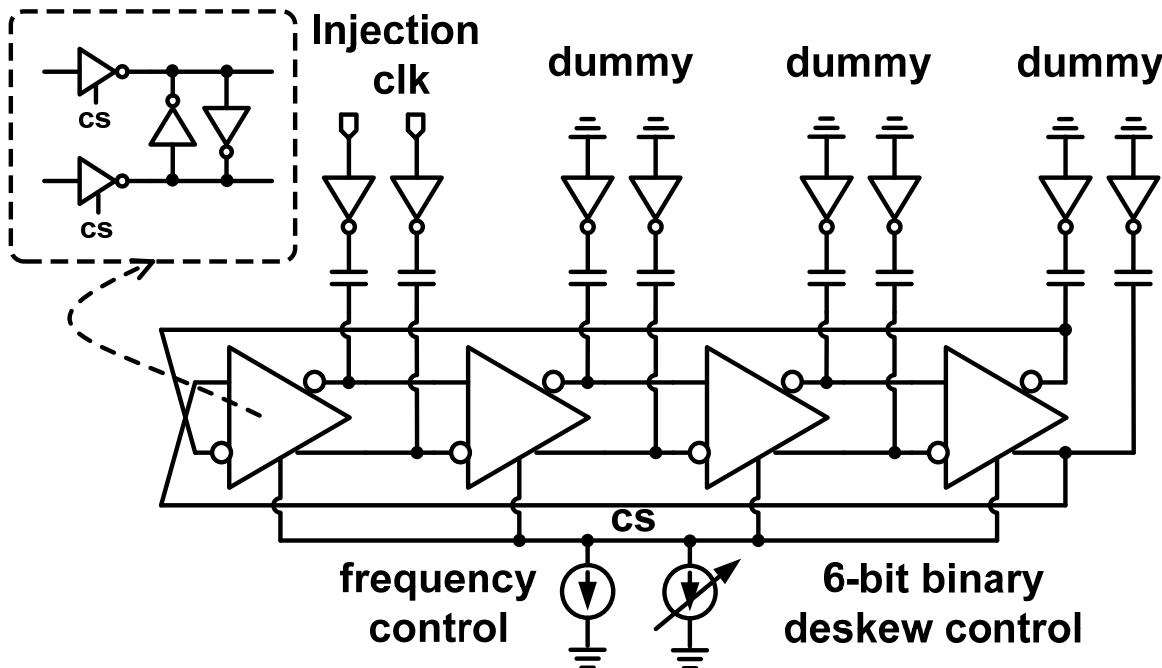


- Current-starved inverter-based ILO produces the multiple clock phases necessary for the receiver samplers
- Fine de-skew control by 6-bit binary current mirror which changes ILO free-running frequency

Phase Drifts with ILO-Based Clocking

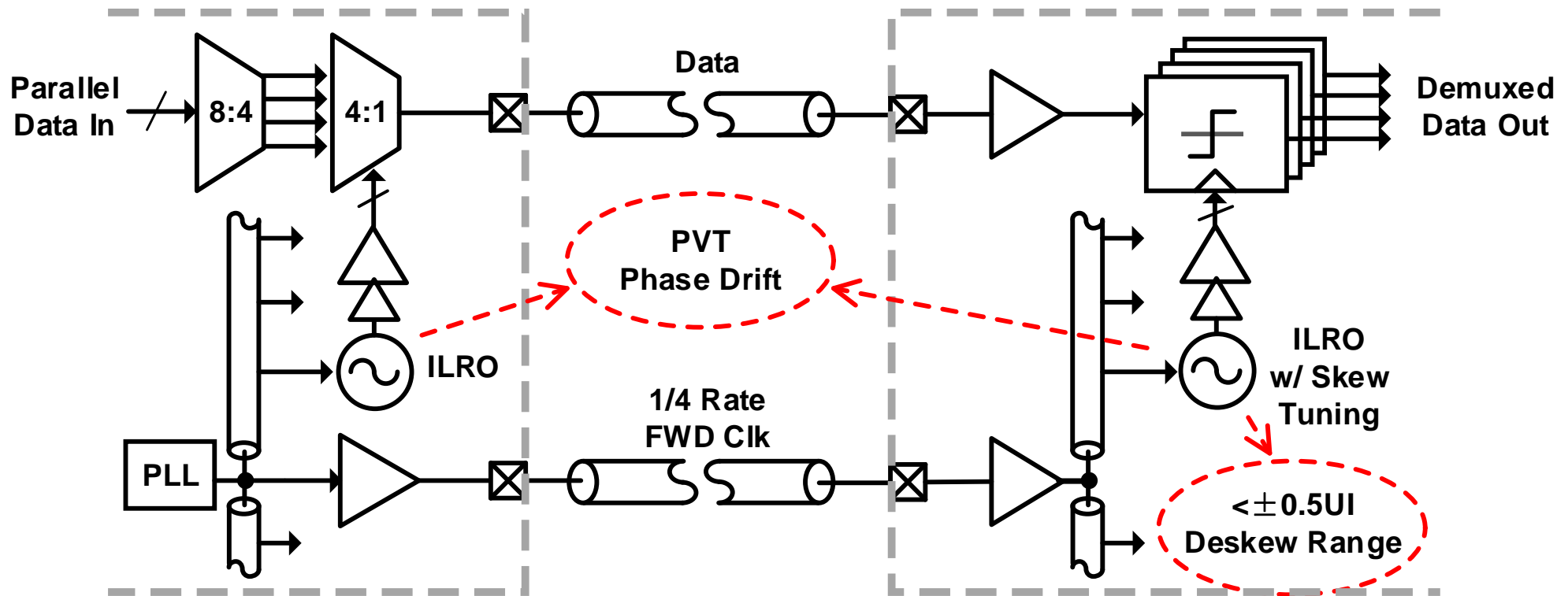



- Voltage and temperature variations can cause the TX/RX ILOs' free running frequency to change, and thus the phase relationship can drift with time

Low-Overhead CDR w/ ILO-Based De-Skew

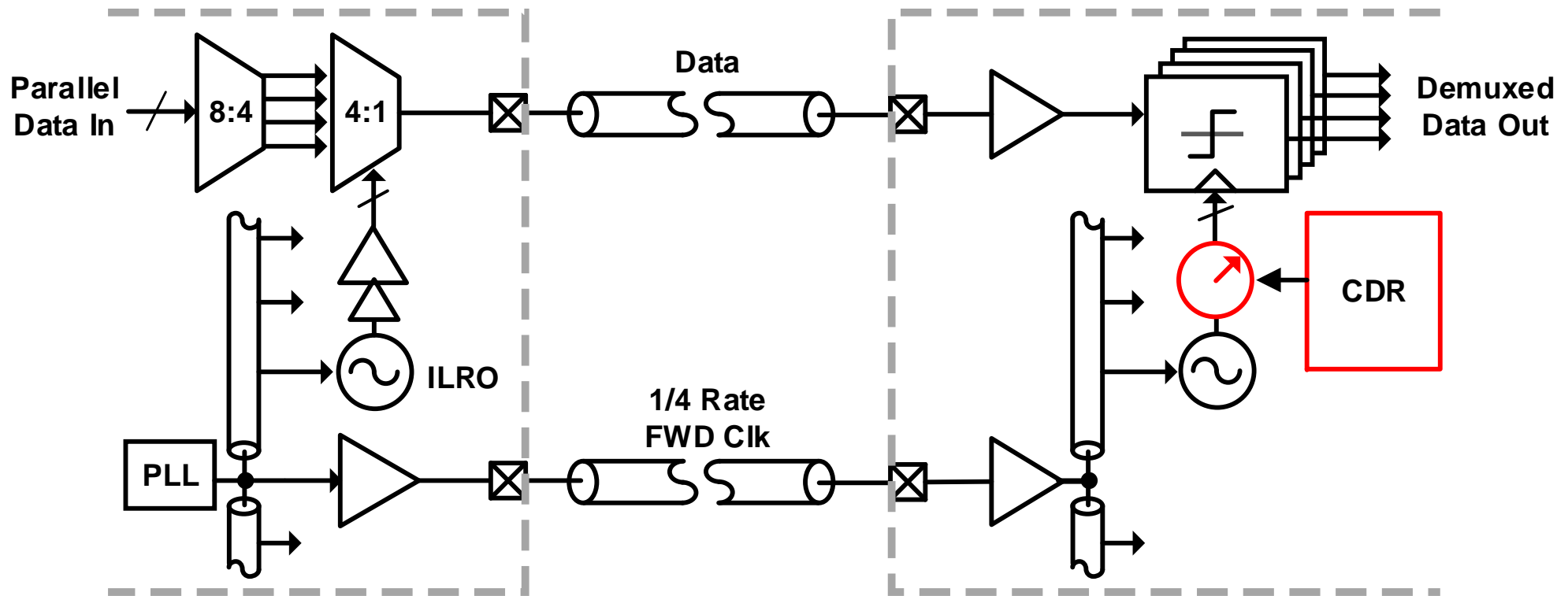


- Introducing a low-overhead CDR into a forwarded-clock system allows tracking of low-frequency phase drifts, while maintaining correlated jitter tracking

Multi-Phase Errors at Low VDD

 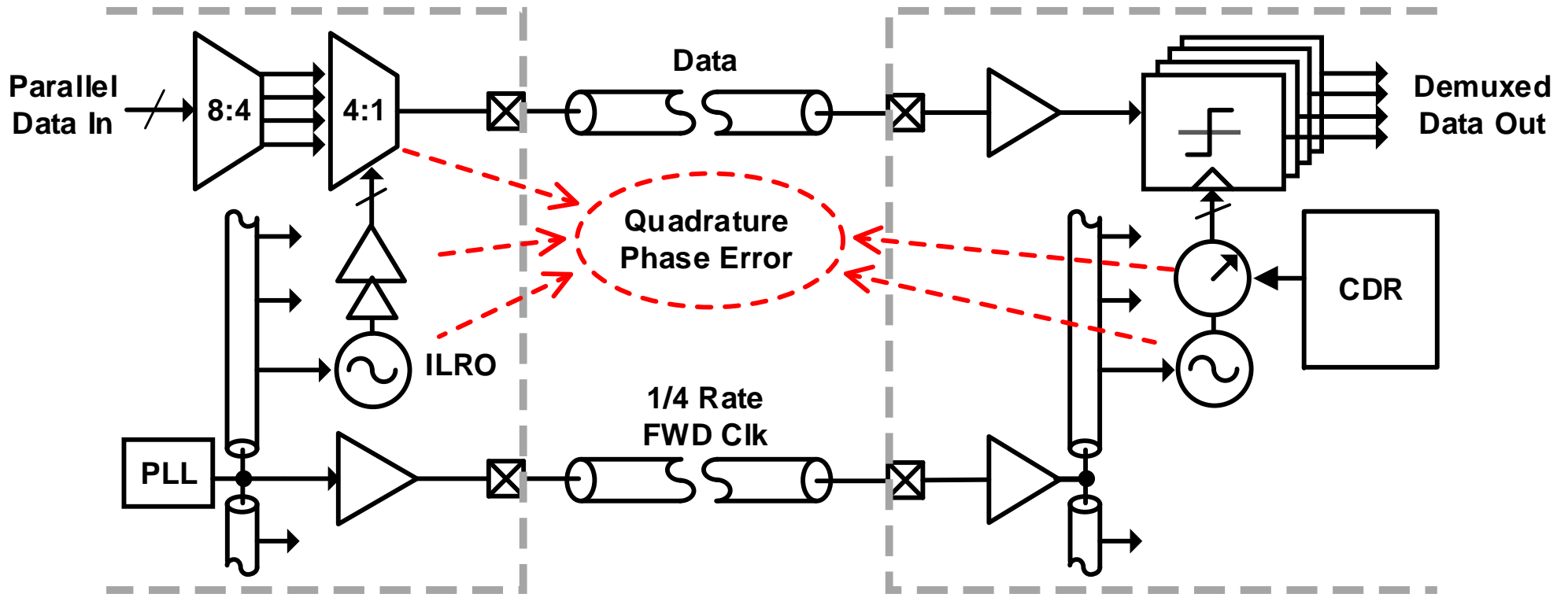




Edge-Rotating 5/4X Sub-Rate CDR

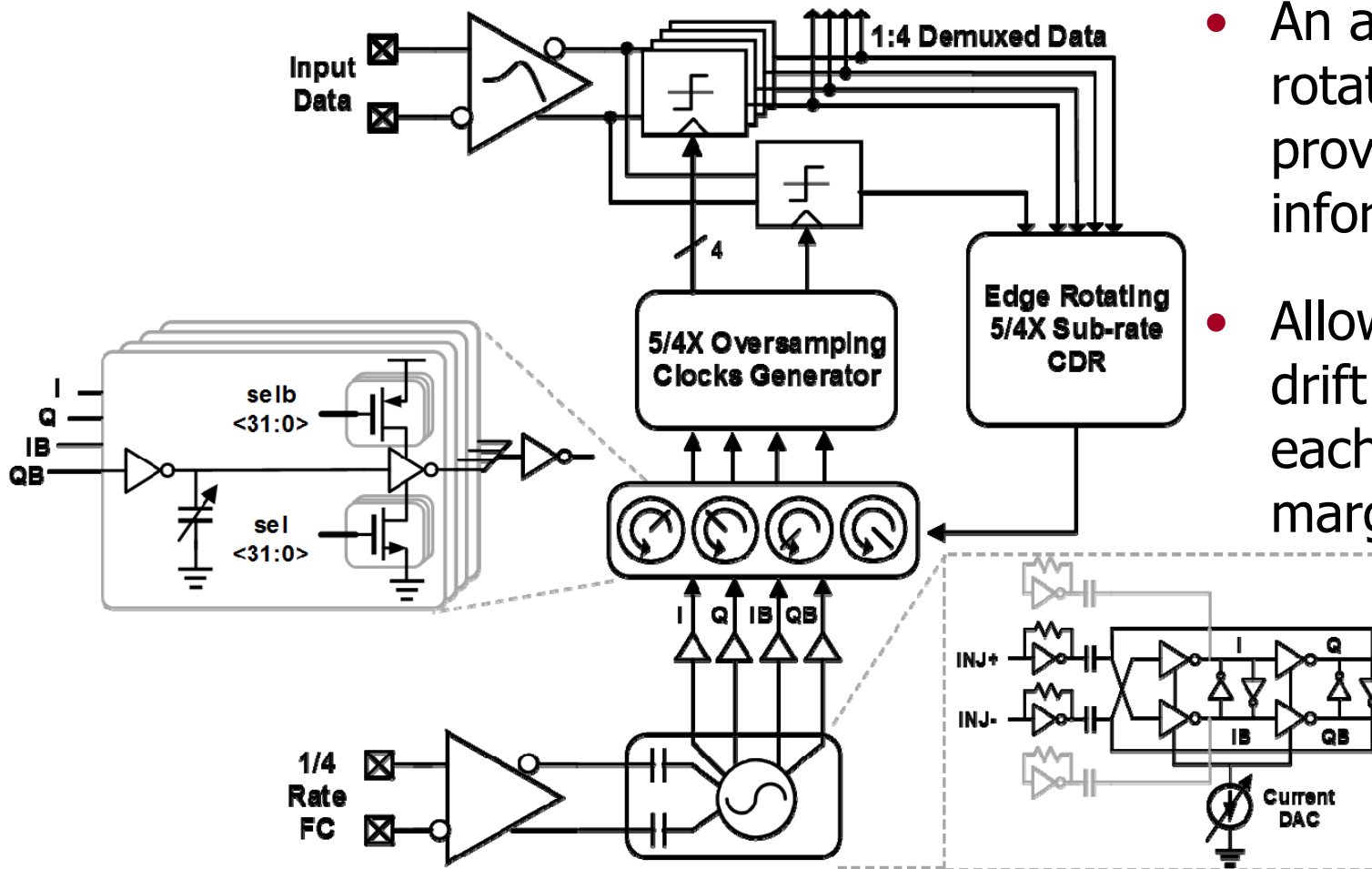

- An additional periodically rotating edge sampler provides the 4-eye phase information to CDR logic
- Allows tracking of phase drift and optimization of each sampler timing margin


14Gb/s GP 65nm CMOS Prototype

  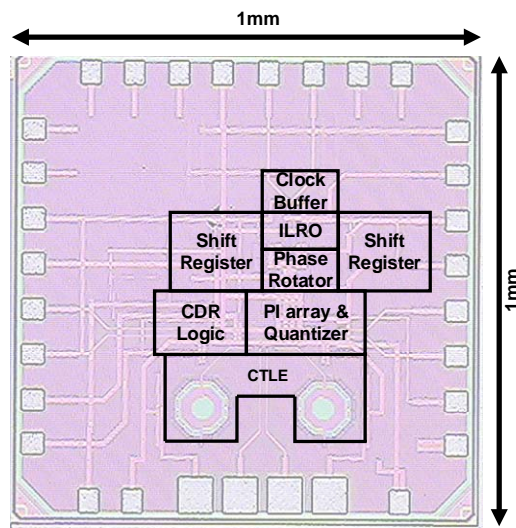Tracking Non-Uniform Eyes Correlated Jitter Tolerance



Uncorrelated Jitter Tolerance

	[2]	[3]	[4]	This Work
V_{DD} , Process	1.0V/65nm	1.25V/90nm	1.08V/32nm	0.8V/65nm
Data Rate	6.4Gb/s	8Gb/s	16Gb/s	14Gb/s
Clock Rate	3.2GHz	2GHz	4GHz	3.5GHz
Clock Arch.	FC	Embedded	FC	FC
Multi-phase Gen.	PLL/PI	DLL	ILO/PI	ILO/PI
RX FOM				
* (Excludes PLL)	3.9pJ/bit*	1.59pJ/bit*	1.02pJ/bit	0.56pJ/bit

 


H. Li, S. Chen, L. Yang, R. Bai, W. Hu, F. Zhong, S. Palermo, and P. Chiang, "A 0.8V, 560fJ/bit, 14Gb/s Injection-Locked Receiver with Input Duty-Cycle Distortion Tolerable Edge-Rotating 5/4X Sub-Rate CDR in 65nm CMOS," VLSI Symp., June 2014.

Outline


- Motivation
- Power-Scalable I/O Techniques
- Low-Power Clocking
- Low-Power Equalizers
- Conclusion

Link with Equalization

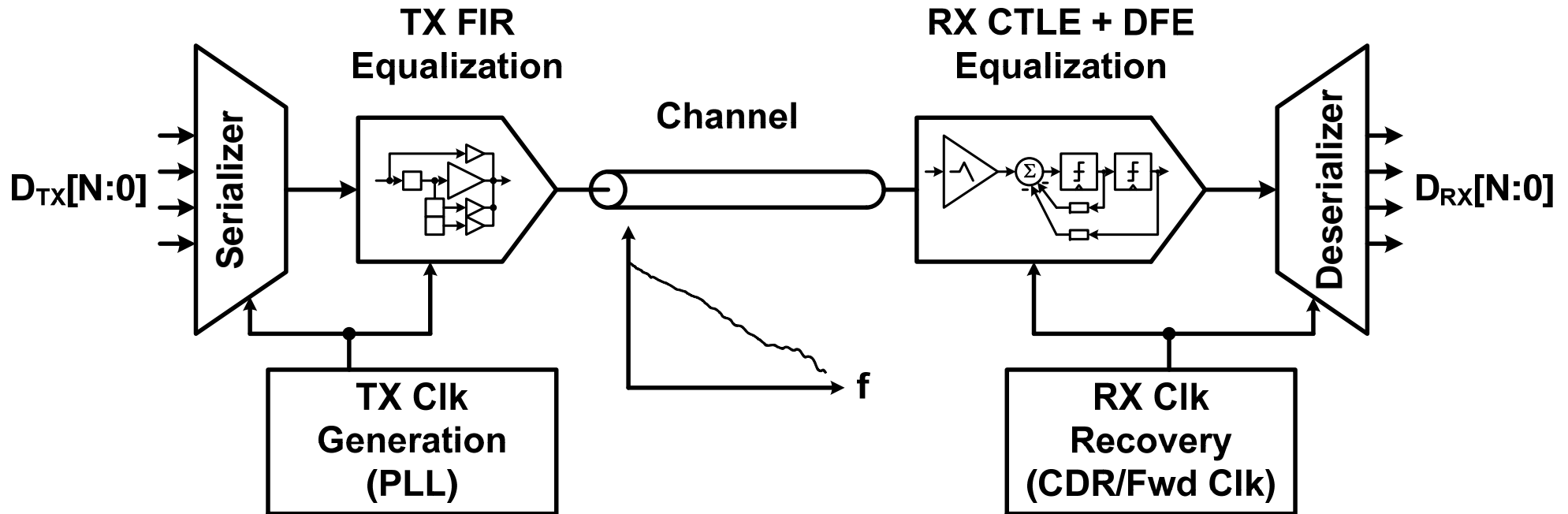


- Equalization goal is to flatten the frequency response out to the Nyquist frequency and remove time-domain ISI

TX-FIR Equalizer Comparisons

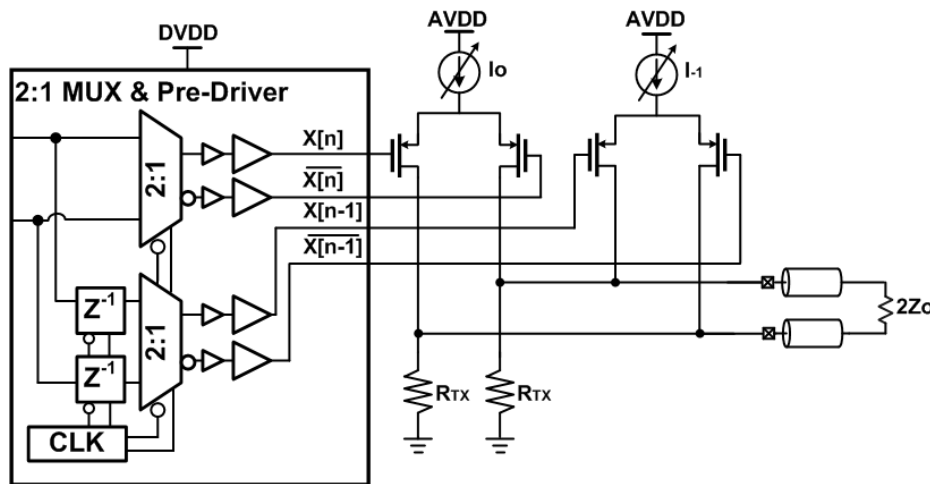

Current-Mode Driver (CM)



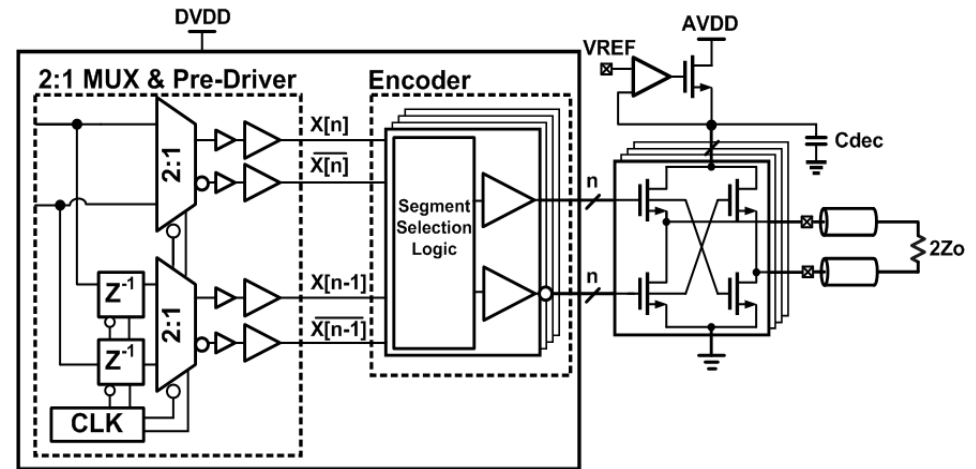


Voltage-Mode Driver (VM)

- FIR equalization can easily be implemented in a current-mode driver by summing tap currents on the termination resistors
- More difficult to implement in voltage-mode drivers due to the series impedance

VM Equalization w/ Shunt Voltage Divider (1)

[Wong JSSC 2004]

 
 
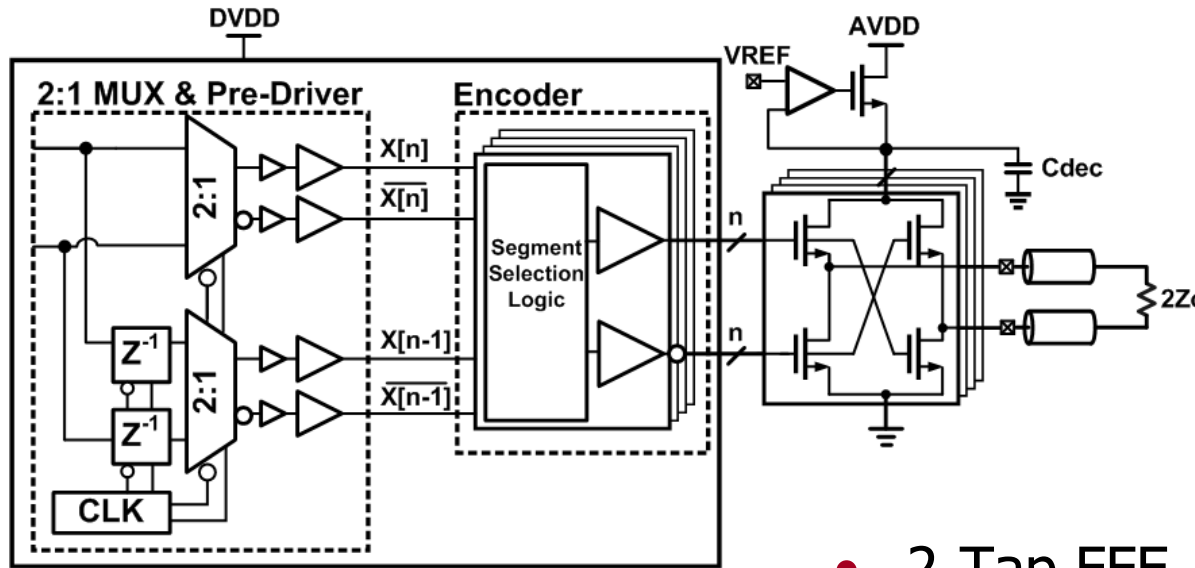


- 2-Tap FFE
 - Parallel combination $\left(R_P = \frac{Z_o}{1-\alpha}, R_N = \frac{Z_o}{\alpha} \right)$
- Z-termination
 - $Z_o = R_P \parallel R_N$
- More current for de-emp. voltage swing

$$I_{sig} = \frac{V_{ref}}{R_T} \left[\frac{1}{2} - \left(\frac{V_{de-em}}{V_{ref}} \right)^2 \right]$$

VM Equalization w/ Added Parallel Path (2)



[Dettloff ISSCC 2010]

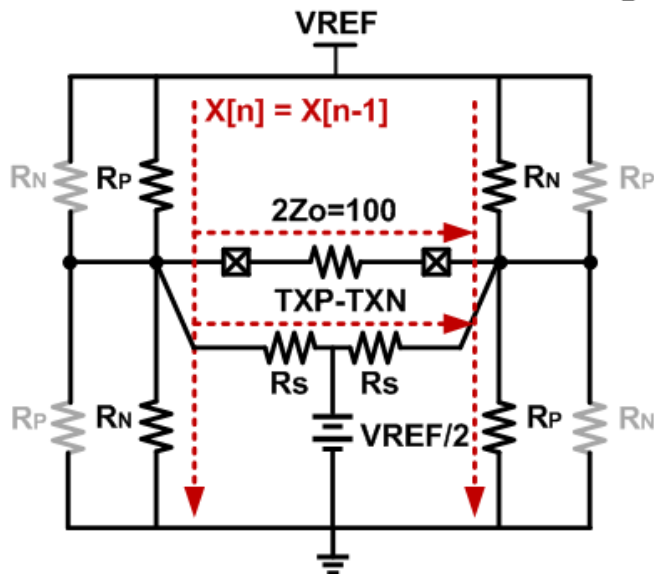  

- 2-Tap FFE
 - Extra series-connected path
 - Constant current path
- Z-termination ($Z_O = R_P \parallel R_N \parallel R_S$)
- Constant signaling power for all V_{SW}
- Non-linear impedance mapping
 - Decoding/pre-driver complexity

VM Equalization w/ Impedance Modulation (3)

[Sredojevic JSSC 2011]

 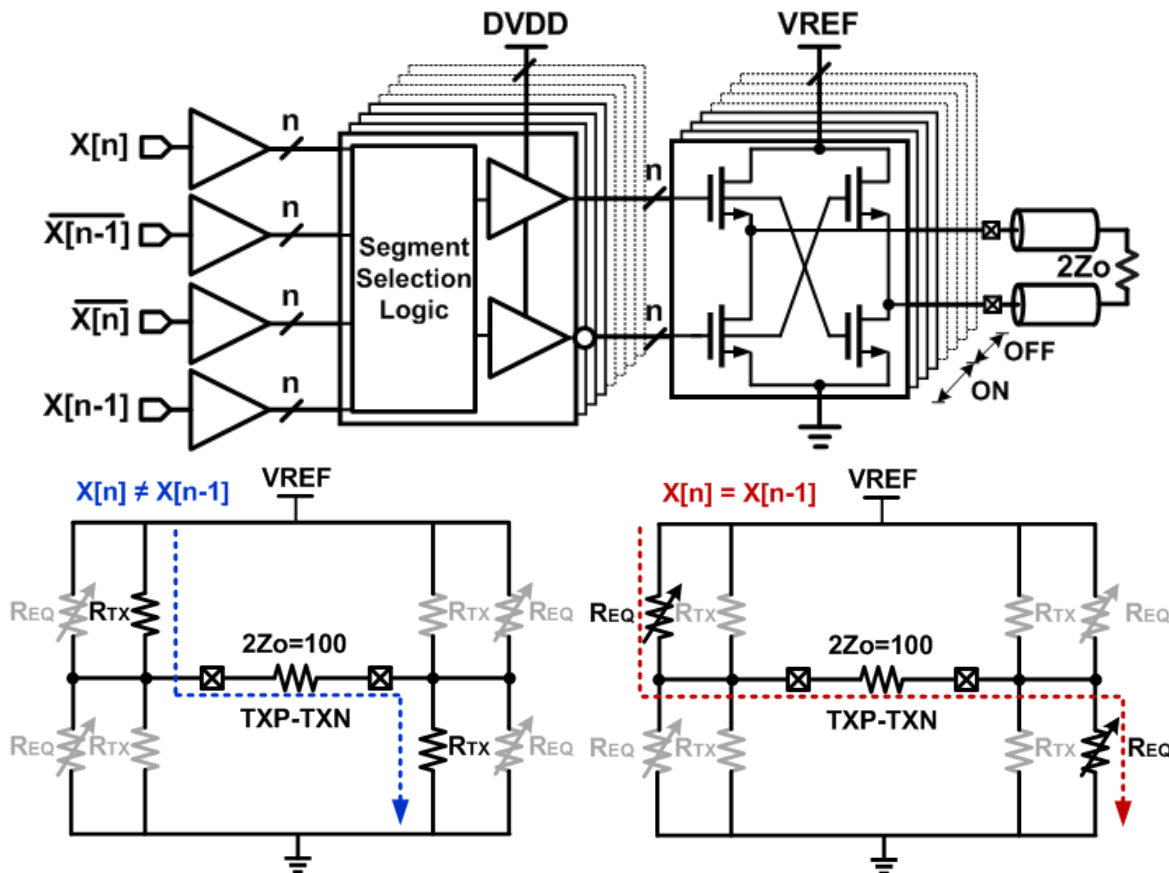


$$I_{sig} = \frac{V_{ppd,max}}{4R_T} (1 - 2\alpha)$$

$$R_{TX} = Z_O, R_{EQ} = \frac{1 + 2\alpha}{1 - 2\alpha} R_{TX}$$


- 2-Tap FFE: Z-modulation (For de-emphasis, higher TX impedance)
- Signaling power $\propto V_{ppd,min} / V_{dd,max}$
- Sacrificing the output termination
- High digital power

VM Equalization w/ Analog Impedance Modulation

Digitally-Controlled Segmented Output

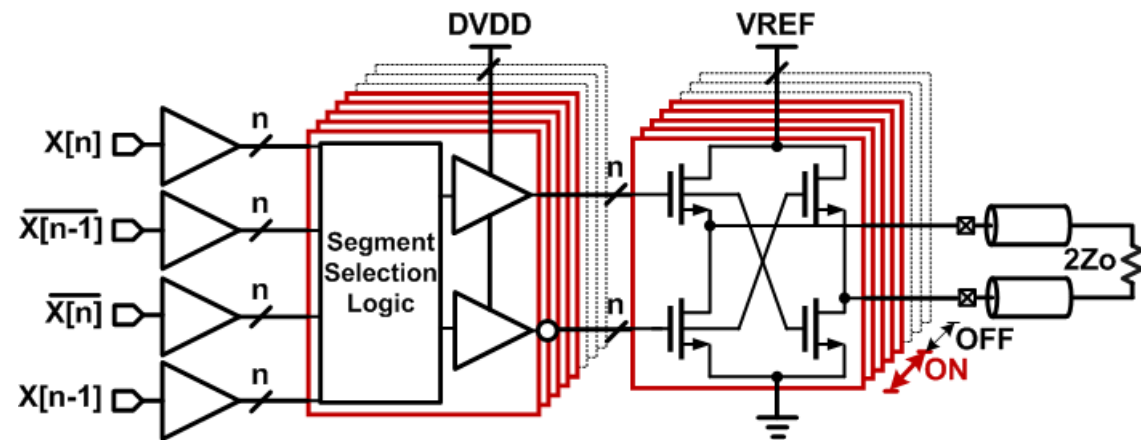


Analog-Controlled Non-Segmented Output

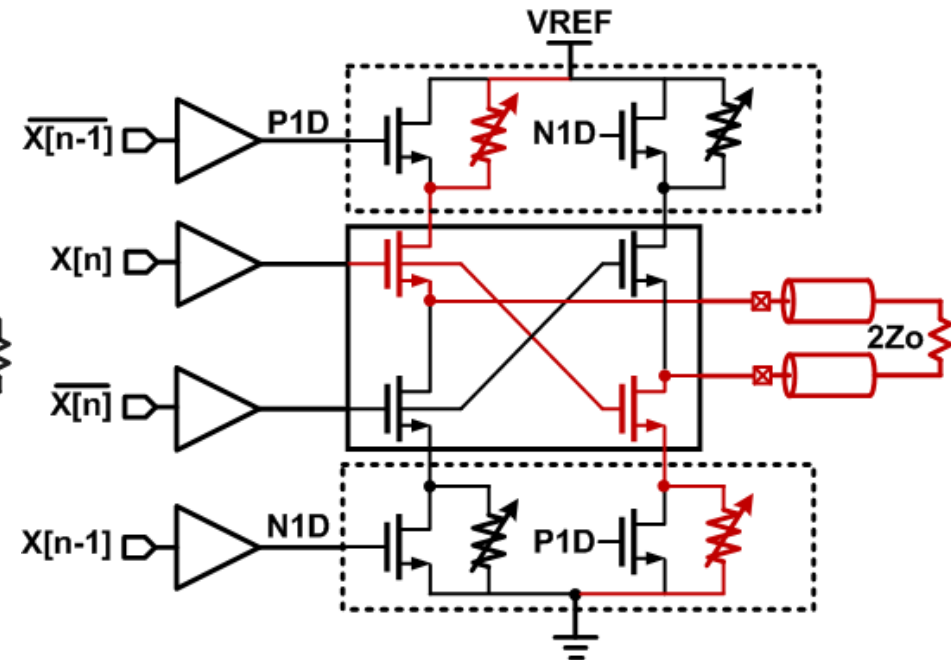

- Segmented pre-driver and output driver significantly increases dynamic power consumption with increased equalization resolution
- Analog tap control obviates output stage segmentation



VM Equalization w/ Analog Impedance Modulation

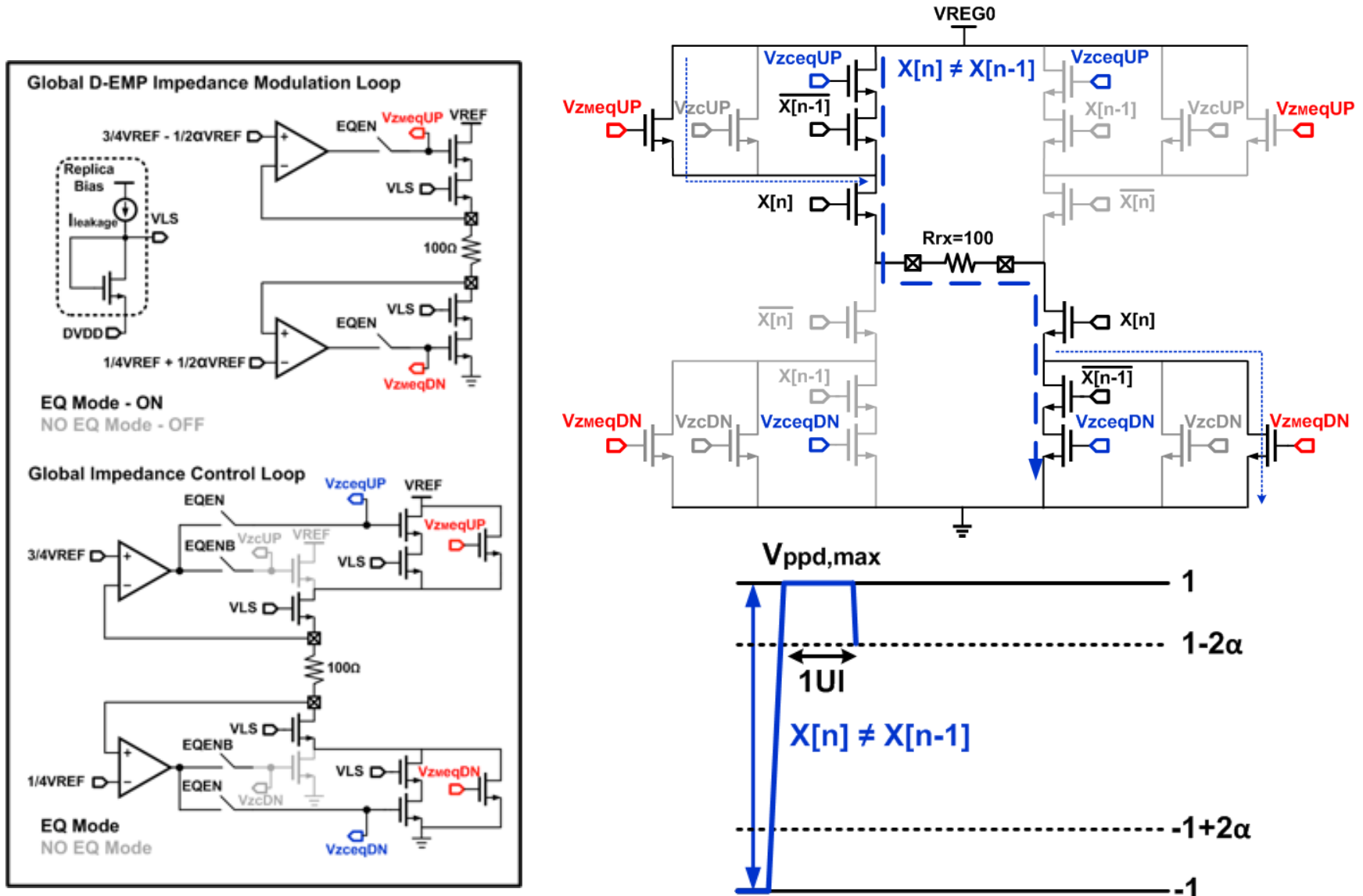- Maximum transmitter output swing during a transition bit






VM Equalization w/ Analog Impedance Modulation

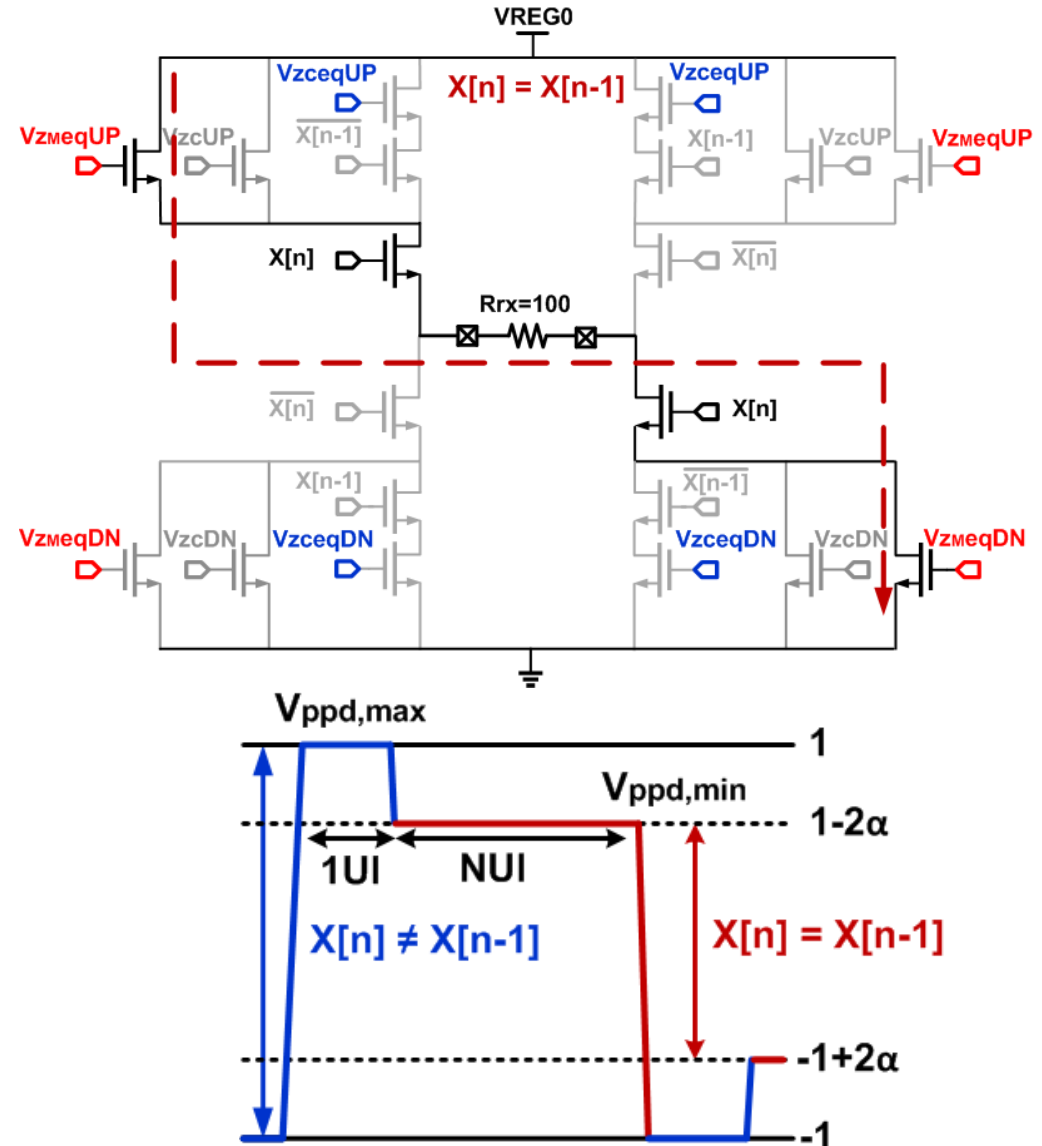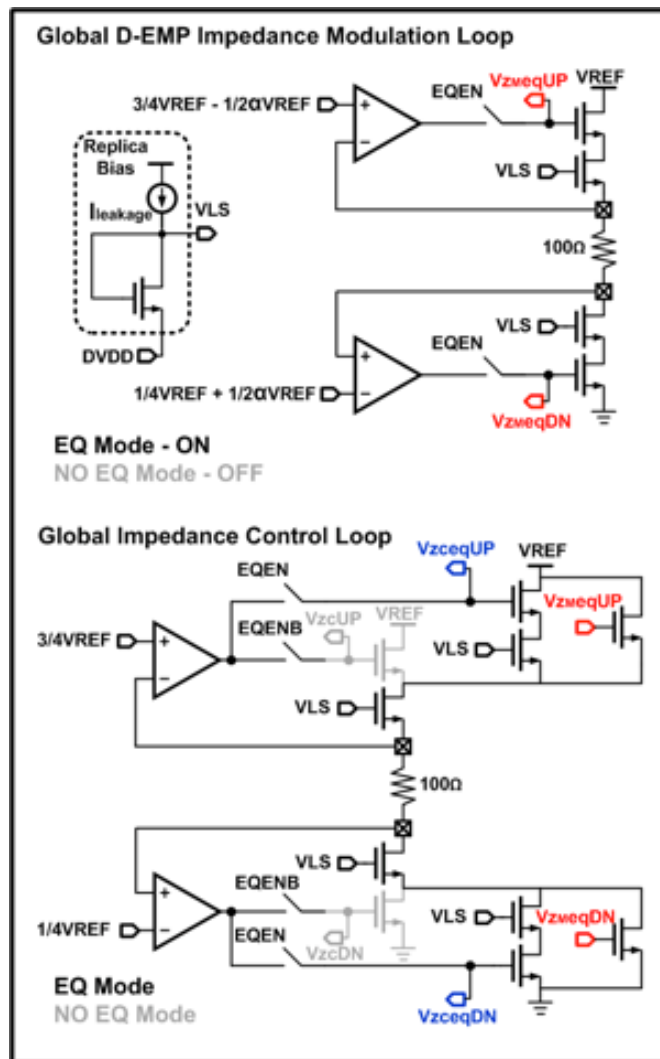- De-emphasis transmitter output swing for run-length > 1





16Gb/s Operation

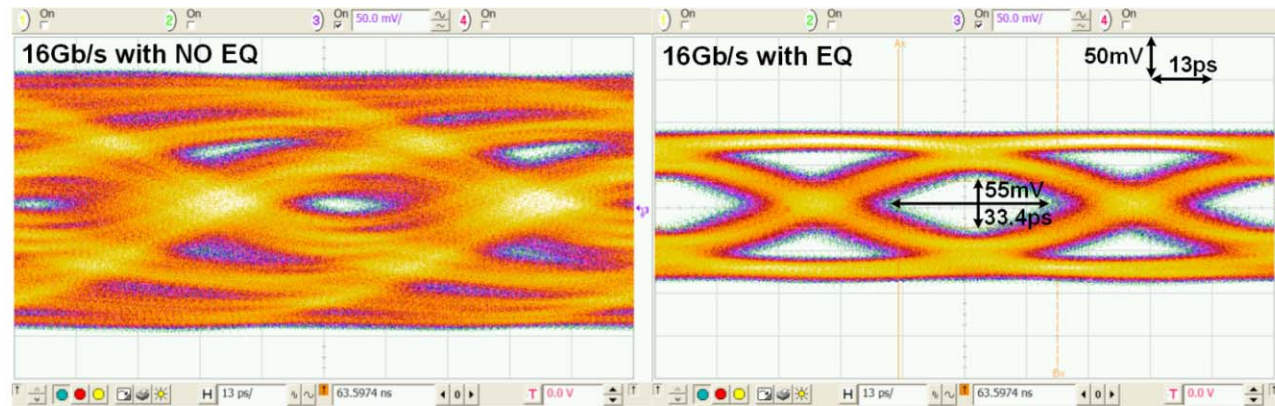  - 5.8 inch FR4 + 0.6m SMA cable -15.5dB loss at 8GHz







Low-Voltage DFE w/ Charge-Based Latches

  




- First stage has small aperture time
- Second stage has small delay to quantized output

16Gb/s Operation

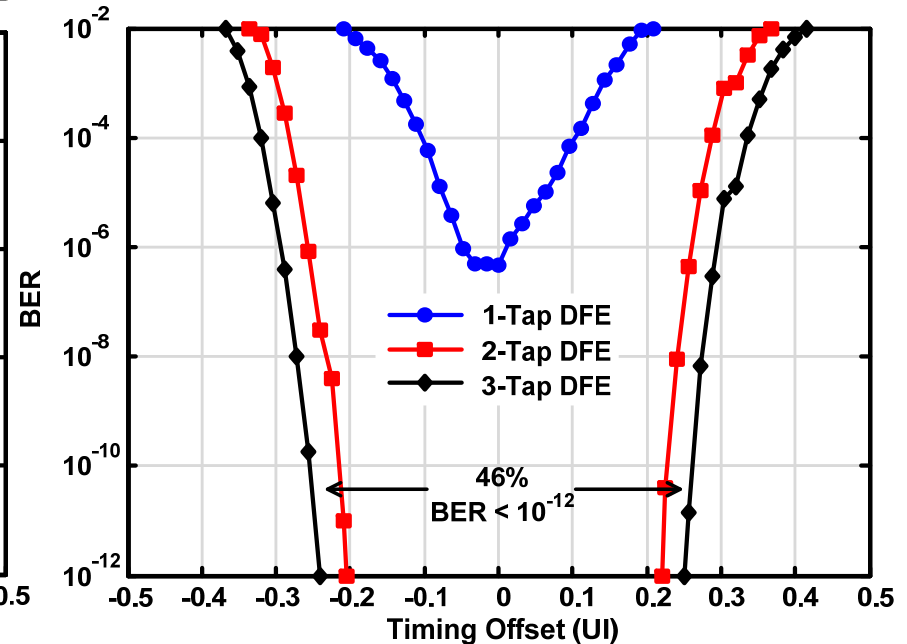 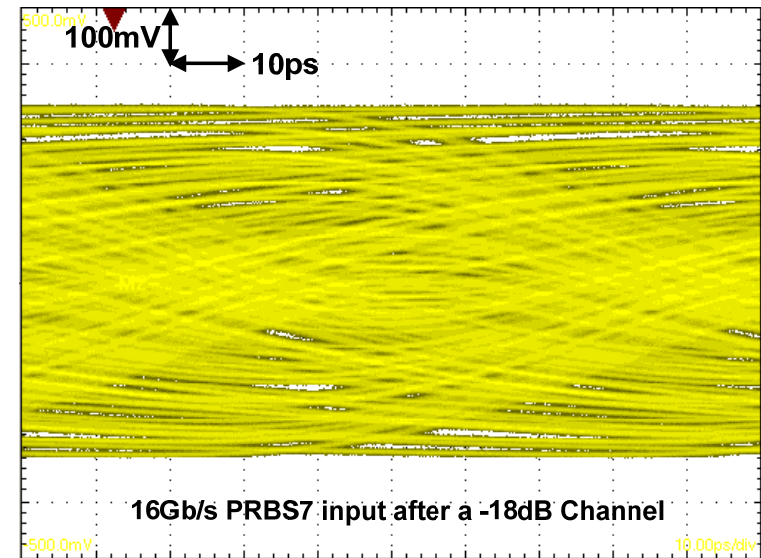 


DFE with Feedback FIR Filter Issues

  
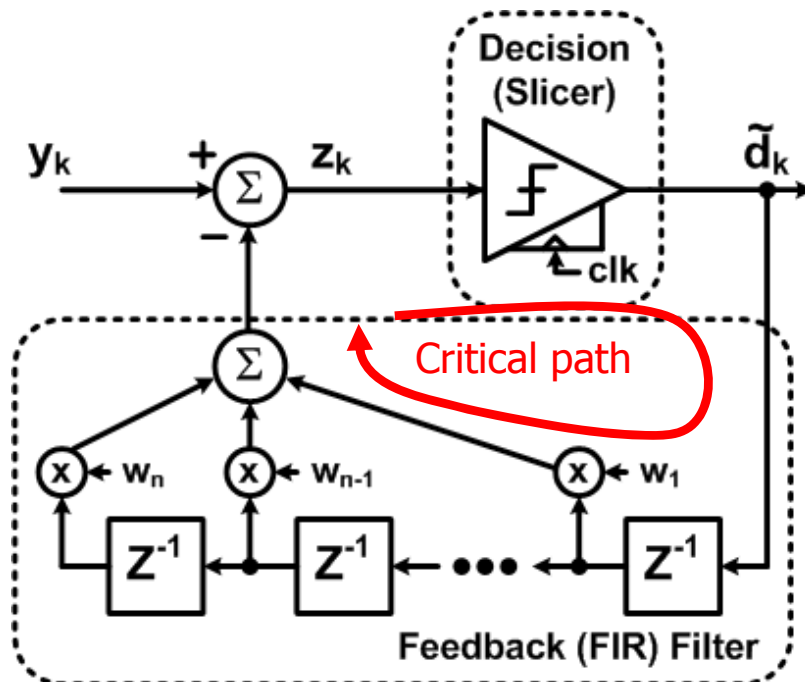
- DFE critical path timing \rightarrow speed/power trade-off
- High-loss channels require large number of DFE taps
 - Increases area and power
 - Increases loading \rightarrow limits speed





DFE with Feedback IIR Filter

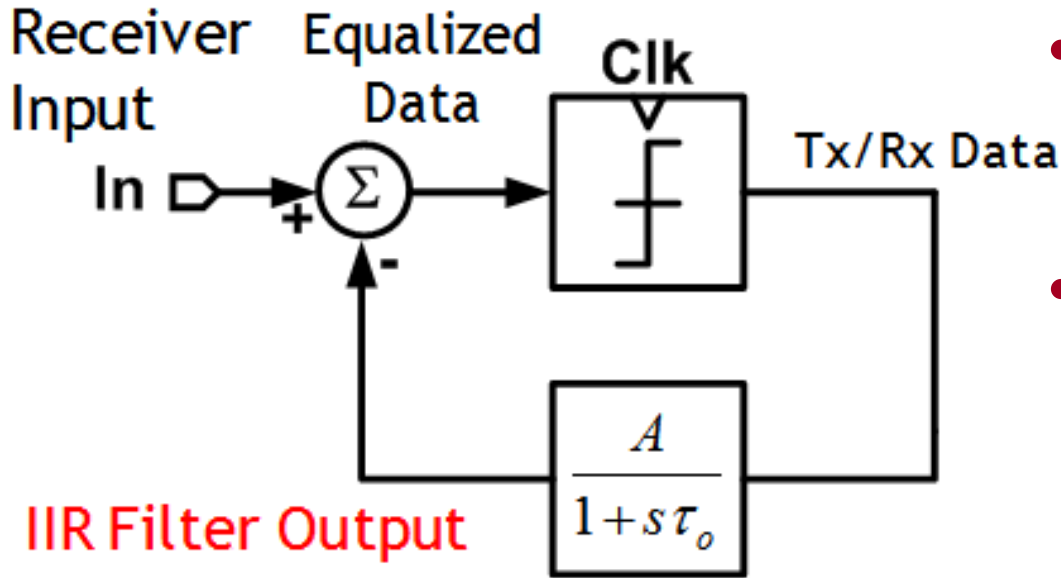

  - IIR feedback filter provides efficient long-tail ISI cancellation
- Typical backplane channel well approximated with 2 IIR taps




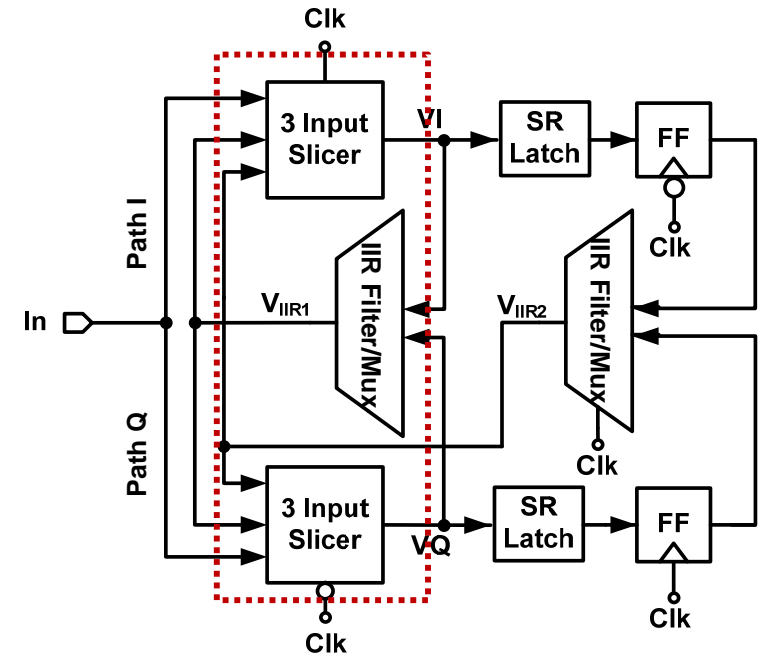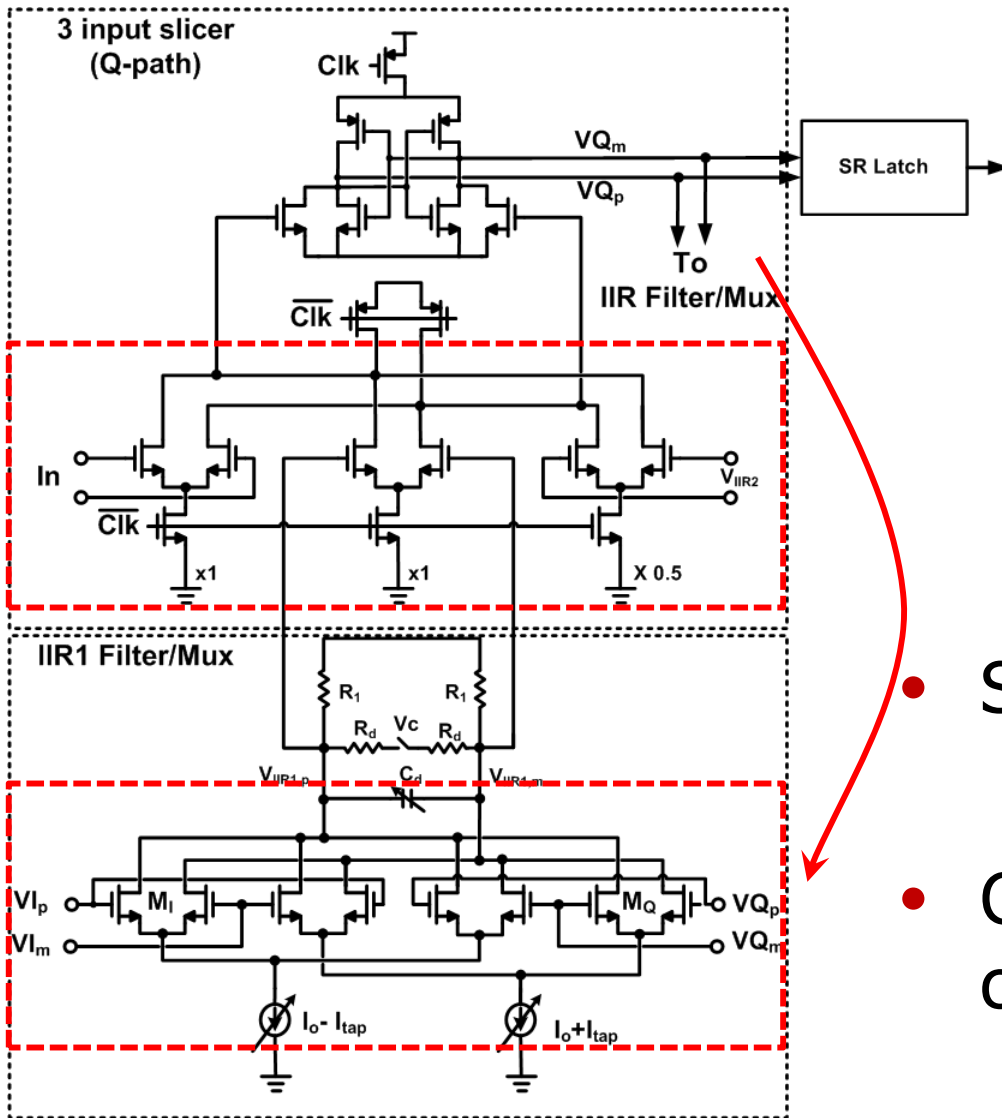10Gb/s 2-IIR-Tap DFE w/ 35dB Loss Compensation



- Summation/slicing merged
 - Three-input double-tail comparator
- Comparator output directly connected to the IIR1 Mux
 - Lowers critical path delay



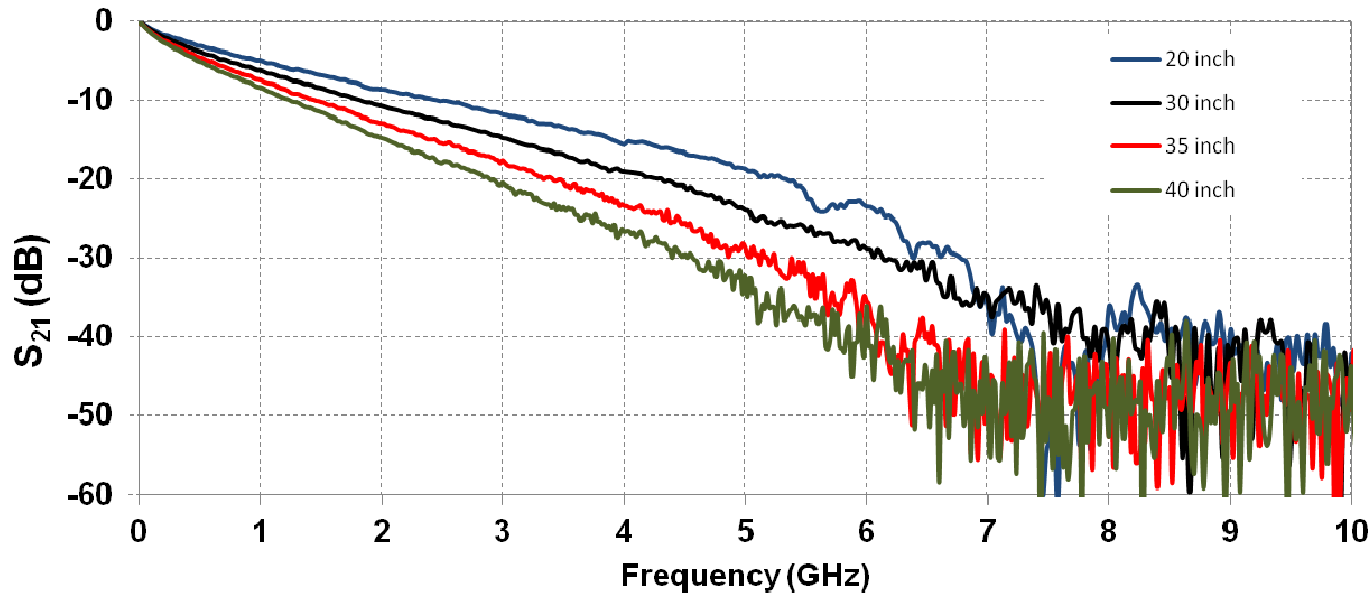
10Gb/s 2-IIR-Tap DFE w/ 35dB Loss Compensation



Specification	This Work	[2]	[3]	[4]
Data Rate	10 Gb/s	10 Gb/s	6 Gb/s	3.7 Gb/s
Architecture	2-IIR tap	1-IIR tap	1-IIR tap	3-IIR tap
Channel Loss @ Nyquist	35* dB	27* dB	32.7 dB	8 dB
Eye width	31 %	28 %	NA	6 %
BER	10^{-12}	10^{-9}	10^{-12}	10^{-12}
PRBS Code	PRBS7	PRBS7	PRBS7	PRBS7
Supply (V)	1	1	NA	1.2
Power (mW)	9.9	7	4	17.3
Area (mm ²)	0.0304	0.0175	0.089**	0.0535
Technology	65-nm	65-nm	90-nm	130-nm



* Including ~2 dB of setup loss.

** Include the area of a whole receiver.

   


O. El-Hadidy and S. Palermo, "A 10 Gb/s 2-IIR-Tap DFE Receiver with 35 dB Loss Compensation in 65-nm CMOS Technology," *IEEE Transactions on VLSI Circuits*, June 2013.

PAM4 Signaling

  


- PAM-4 modulation offers improved spectral efficiency over NRZ
- Main Characteristics:
 - ✓ Lower symbol rate
 - ✗ Lower voltage margin → **Higher sensitivity is required**

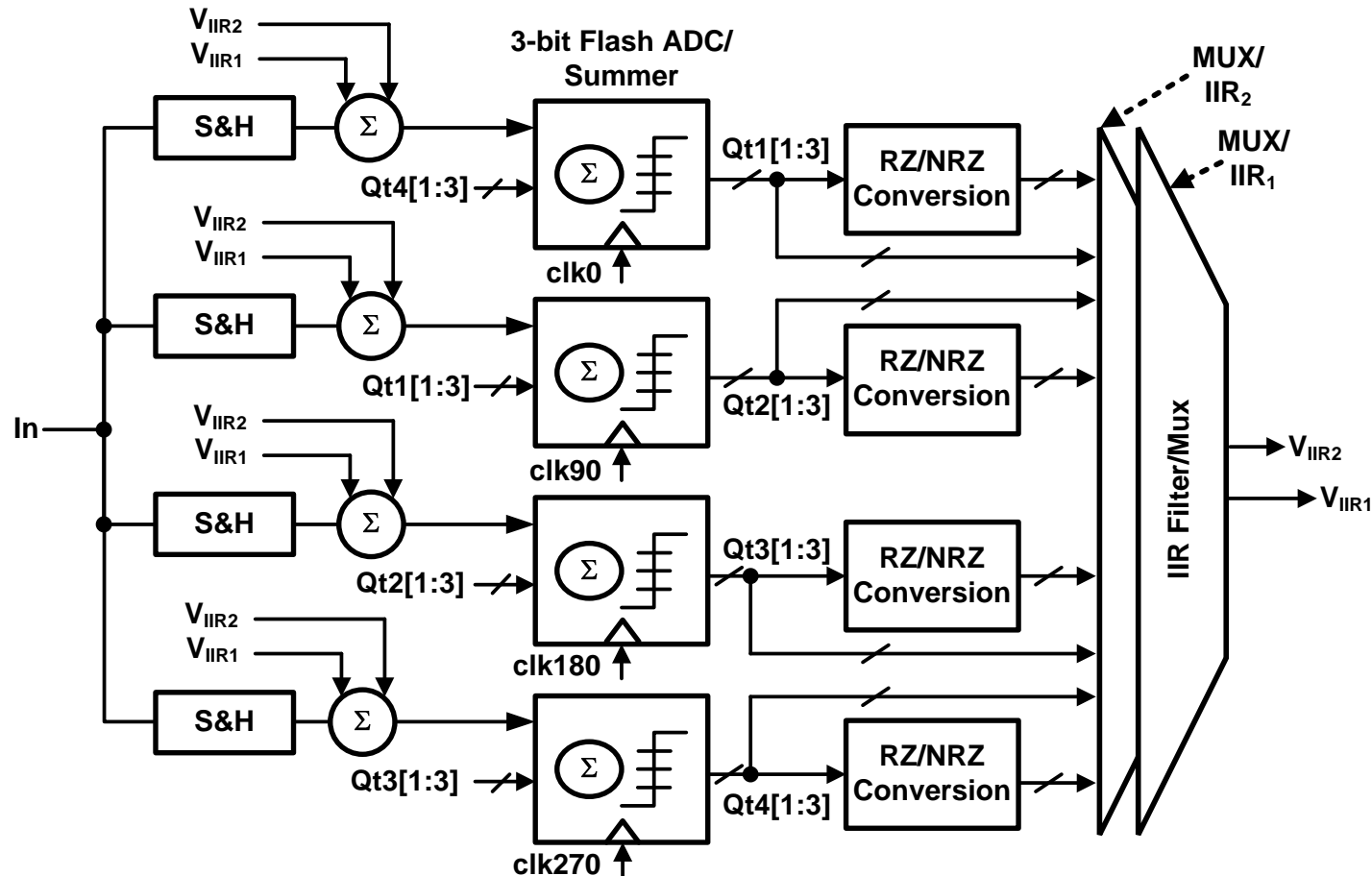A 32 Gb/s 0.55 mW/Gbps PAM4 1-FIR 2-IIR Tap DFE Receiver in 65-nm CMOS




- PAM4 DFE employs 1-FIR tap for 1st post-cursor multi-level ISI cancellation and 2-IIR taps for long tail ISI cancellation
- Multi-level ISI cancellation is achieved with thermometer feedback to tap DACs

Dynamic Regenerative Comparator



 


- ✓ Second stage regeneration through small Mn3, Mp3 in parallel with second stage
 - ✓ Full swing output
 - ✓ Smaller delay (versus regenerative comparator)
- ✓ Second stage regeneration current is controlled through NMOS transistor
- ✓ Only requires one clock phase

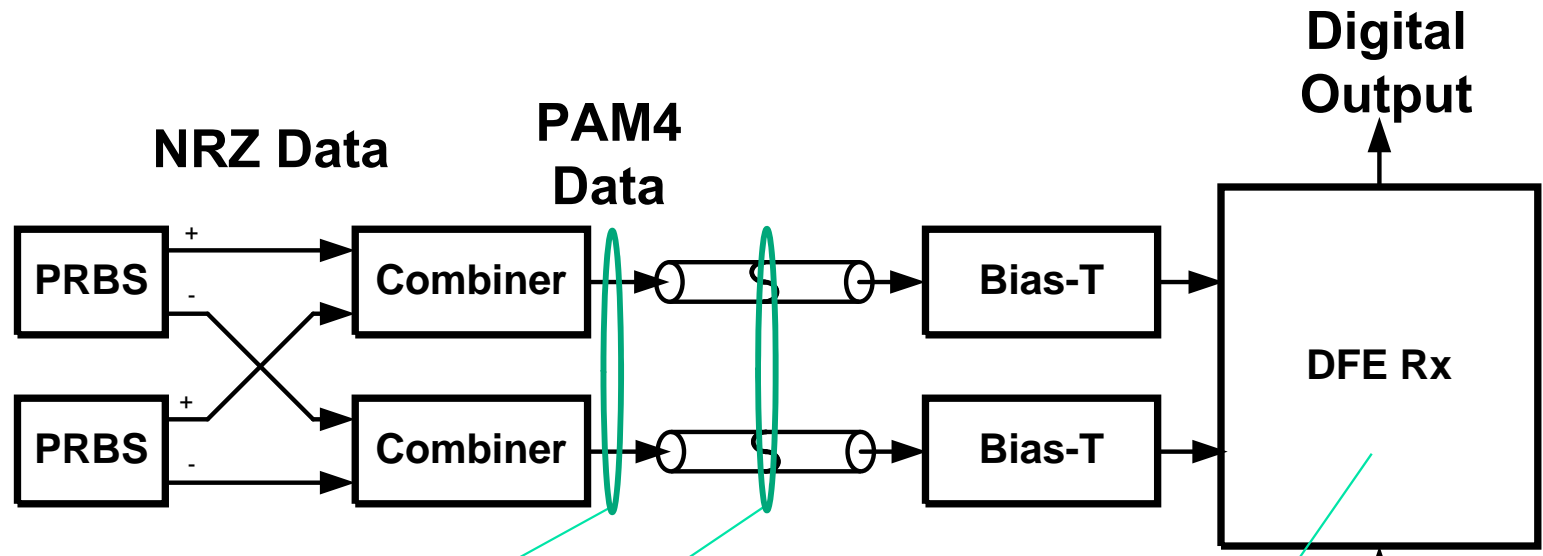GP 65nm CMOS Prototype & Measurement Results



600 mV_{ppd}
25Gb/s PAM4 Data

   

- At 32Gb/s consumes 17.7mW or 0.55mW/Gbps

Conclusion

- I/O transceivers need to achieve near 1pJ/b at 10+ Gb/s to support future systems
- Low-voltage operation with parallelism can achieve significant power savings
- Source synchronous architectures reduce clocking complexity
- Circuitry which supports fast power-state transitioning can reduce system average power
- Low-voltage equalizers are necessary to support channel loss for data rates $>10\text{Gb/s}$

Acknowledgements

- Many of the projects discussed today were collaborative works with Prof. Patrick Chiang's group at Oregon St
- Funding support from SRC and TI