

---

# Circuit Intuitions

Ali Sheikholeslami  
Dept. of Elec. & Comp. Engineering  
University of Toronto, Canada  
[ali@ece.utoronto.ca](mailto:ali@ece.utoronto.ca)

sponsored by **SSCS Distinguished Lecture Program**

August 23, 2019  
University of California, San Diego

# IEEE SOLID-STATE CIRCUITS

MAGAZINE

SUMMER 2017 • VOL. 9 • NO. 3




## Circuit Intuitions: Capacitor as a Resistor (Switched-Capacitors) as Taught by James Clerk Maxwell



Ali Shekholeslami






## CIRCUIT INTUITIONS

### Looking into a Node

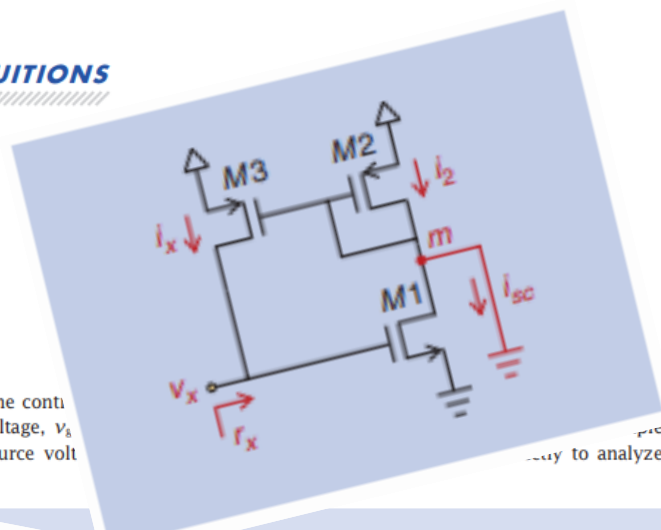

(one cont  
voltage,  $v_s$   
source volt

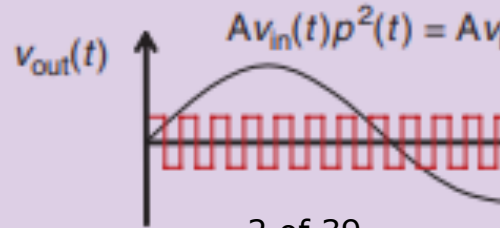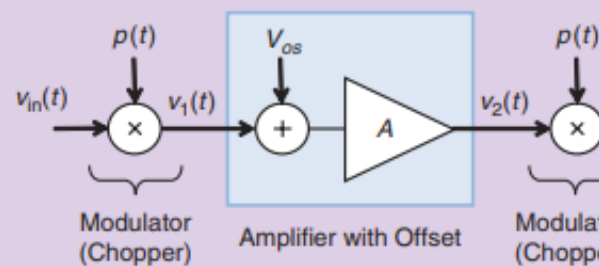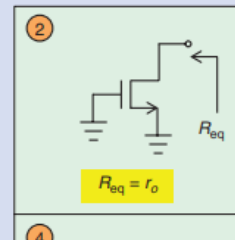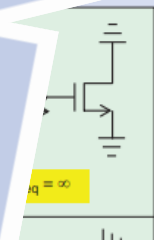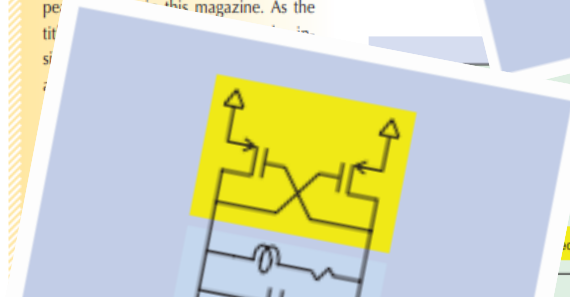Welcome to "Circuit Intuitions." This is the first article of a series that will appear in this magazine. As the



# Outline

---

- Why Circuit Intuitions?
- Overview of Articles Series
- Looking into a Node
  - Use of Thevenin and Norton Equivalent Circuits

# Why Circuit Intuitions?

---

- Turning circuit design/analysis into a fun game!
- Gain intimate understanding of how circuits behave
- Making things simple, obvious!
- A gateway to innovation!

# Circuit Intuitions Series

---

- Methods of Analysis
  - Looking into a Node
  - Source Degeneration; Bandwidth Extension
  - Miller's Theorem; Miller's Approximation
- Fundamental Concepts
  - Process Variation and Pelgrom's Law
  - Why Sinusoids? Reinventing the Wheels, Random Walk
  - Capacitor Analogy (3 articles)
  - Norton and Thevenin Equivalent Circuits (3 articles)
- Special Circuits
  - Negative Cap.; Chopper Amp.; Capacitor as a Resistor

# Focus of this Talk

---

- Methods of Analysis
  - Looking into a Node
  - Source Degeneration; Bandwidth Extension
  - Miller's Theorem; Miller's Approximation
- Fundamental Concepts
  - Process Variation and Pelgrom's Law
  - Why Sinusoids? Reinventing the Wheels
  - Capacitor Analogy (3 articles)
  - Norton and Thevenin Equivalent Circuits (3 articles)
- Special Circuits
  - Negative Cap.; Chopper Amp.; Capacitor as a Resistor

# Linear Time Invariant (LTI) Circuits

---

- Output is a linear combination of inputs!
  - Simple Case: If there are no storage elements (C or L)




$$y = h_1x_1 + h_2x_2 + h_3x_3 + \dots$$

- Superposition holds!

$$y = y_1 + y_2 + y_3 + \dots$$





- Output is sum of contributions from individual inputs!
- Thevenin/Norton Theorem: consequence of superposition

# Thevenin/Norton Theorems

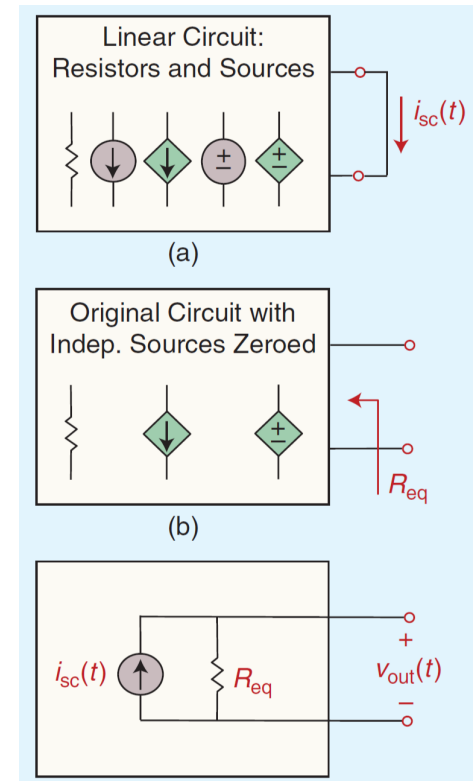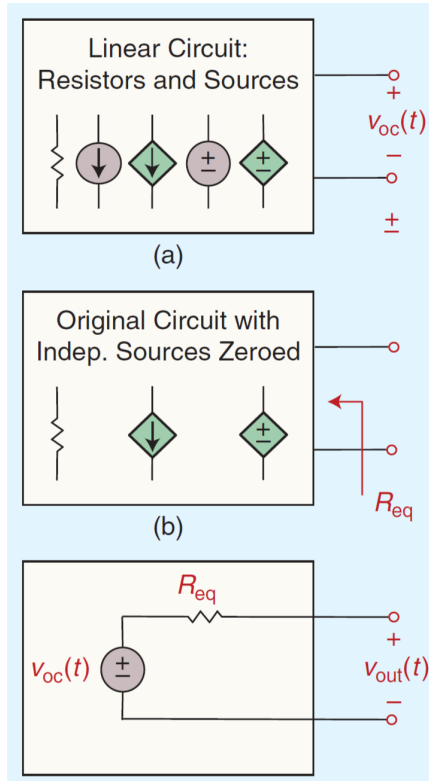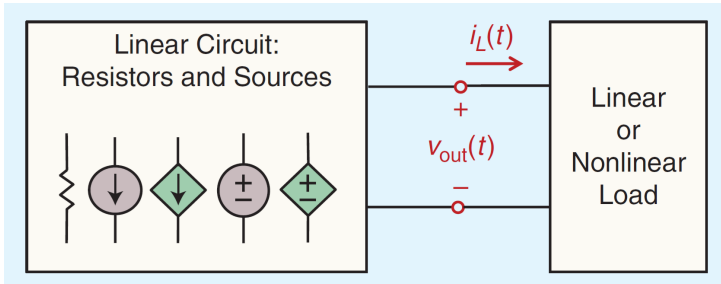







# An Intuitive Proof of Thevenin

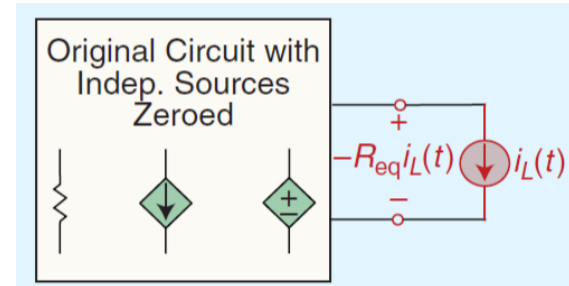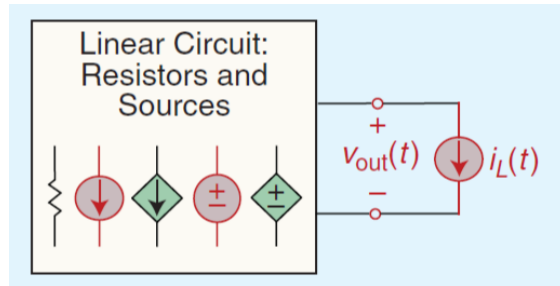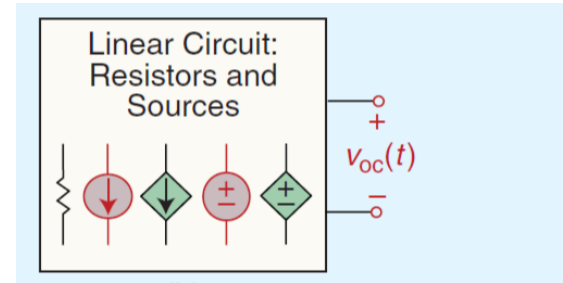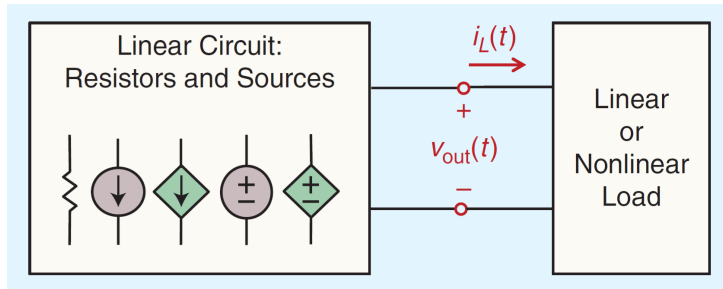



$$v_{out}(t) = v_{oc}(t) - R_{eq}i_L(t)$$

# An Intuitive Proof of Norton

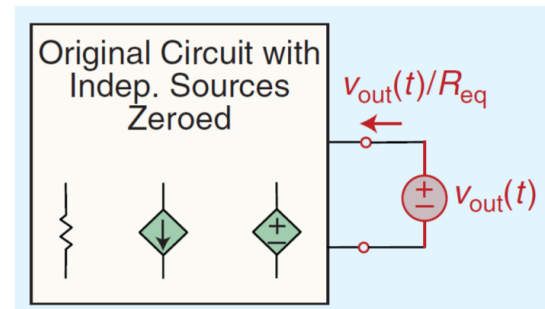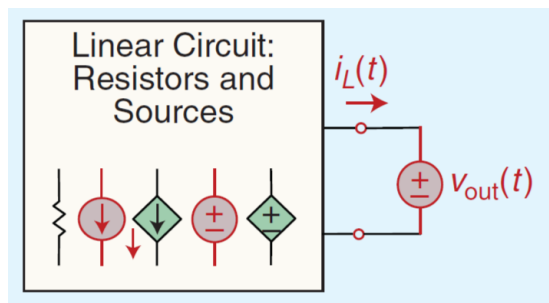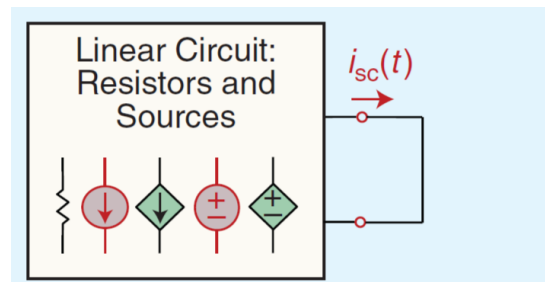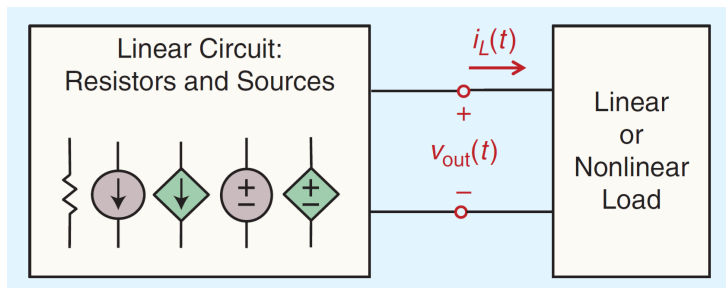

$$i_L(t) = i_{sc}(t) - v_{out}(t)/R_{eq}$$


# Small-Signal Model of NMOS/PMOS

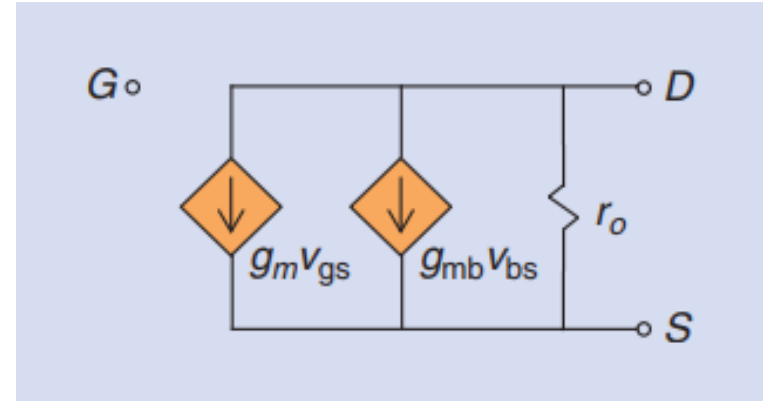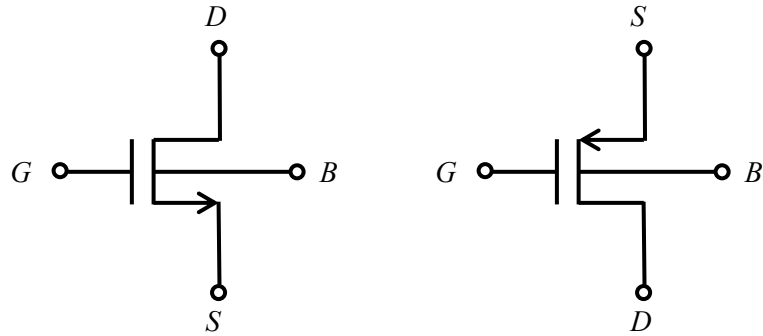

**Assumption: All transistors are in Saturation Region!**

- $g_m$  is the short-circuit transconductance of the transistor
- $g_{mb}$  is additional  $g_m$  due to non-zero  $v_{bs}$
- $r_o$  is the transistor output resistance

# Circuits with More Transistors

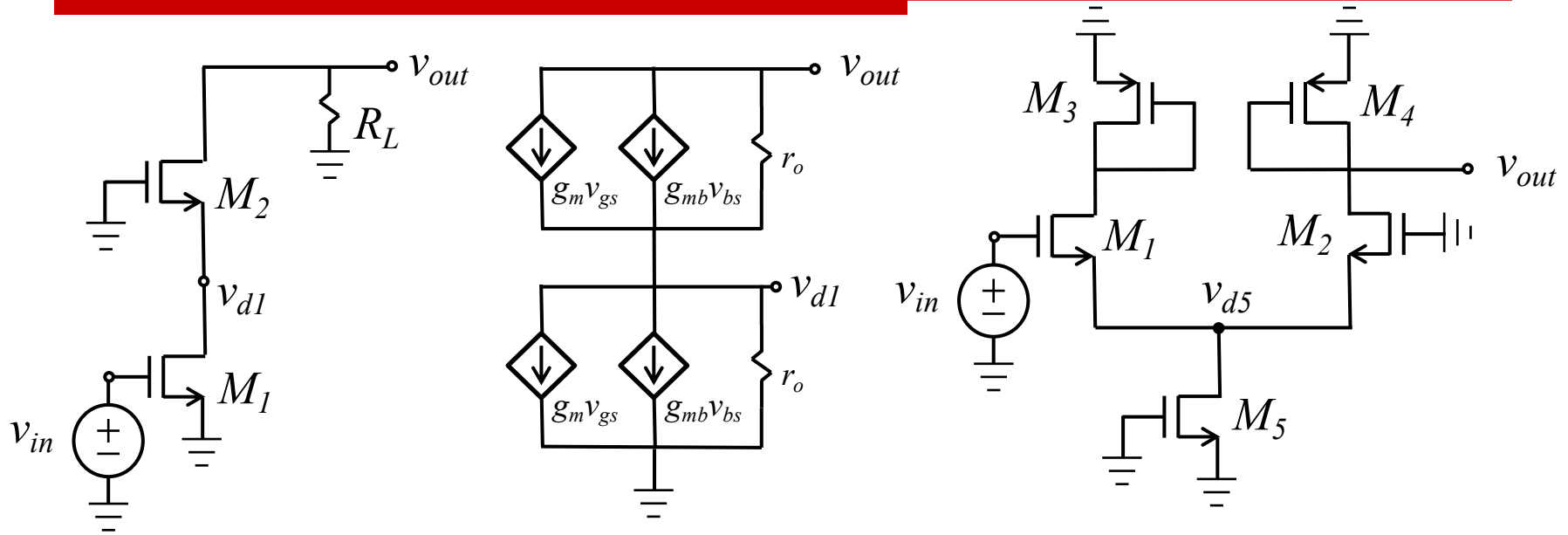

- ❑ Analysis becomes too cumbersome very quickly
- ❑ Practice of KVL/KCL, leaves no room for intuition

# Basic Premise

---


- Assume low-frequency analysis in this talk!
- That is, capacitors do not show up!
- In small-signal, transistors behave like LTI systems
- Superposition holds!
  
- Every circuit has a Thevenin/Norton equivalent circuit
  - Open-circuit voltage source ( $v_{oc}$ ) in series with  $R_{eq}$
  - Short-circuit current source ( $i_{sc}$ ) in parallel with  $R_{eq}$
  - When there is no input signal, they are just resistors!
  
- We rely on Thevenin/Norton equivalent circuits **ONLY!**

# “Library Elements”

---


- We call these “library elements”
- Commonly-Used Configurations
  - Looking into the gate and the drain
  - Looking into the source
  - Diode-Connected transistor
  - Looking into the drain with source degeneration
  - Looking into the source with load at the drain
  - Thevenin/Norton Equivalent looking into the drain
  - Thevenin/Norton Equivalent looking into the source
- Let us build this library; one element at a time

# Looking into the Gate

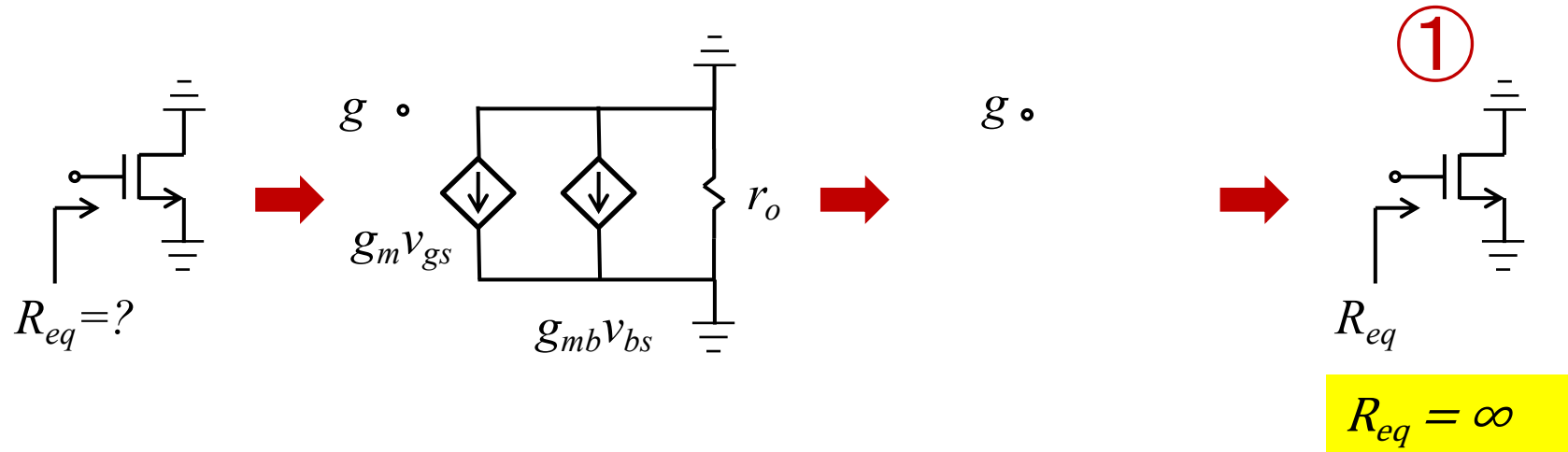

□ Looking into the gate, we see infinite resistance


# Looking into the Drain

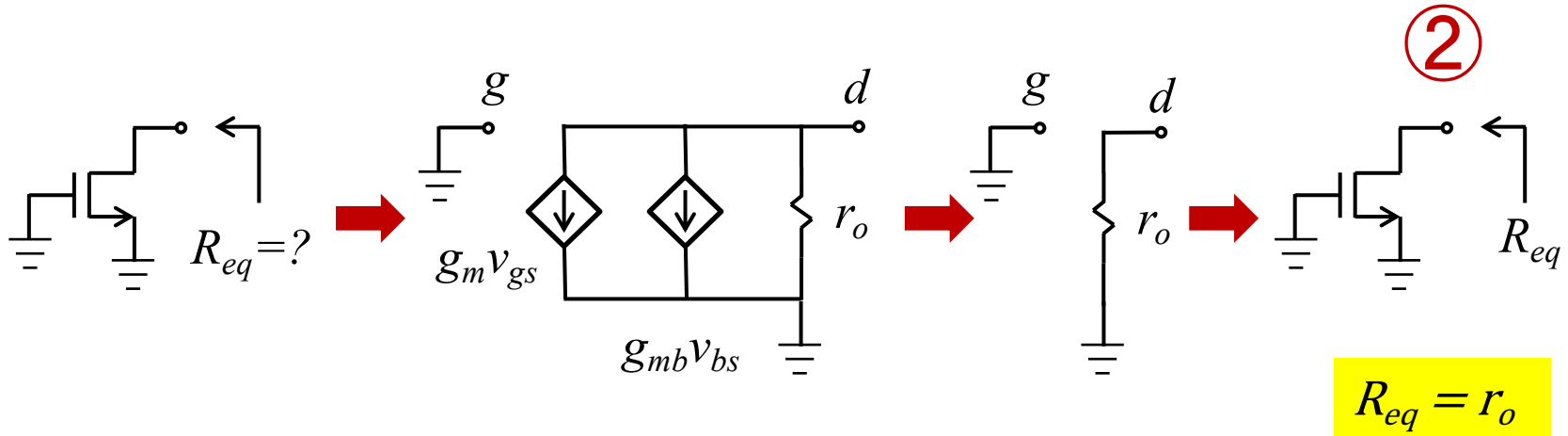

- Looking into the drain, while gate and source are grounded, we see  $r_o$ !




# Looking into the Source

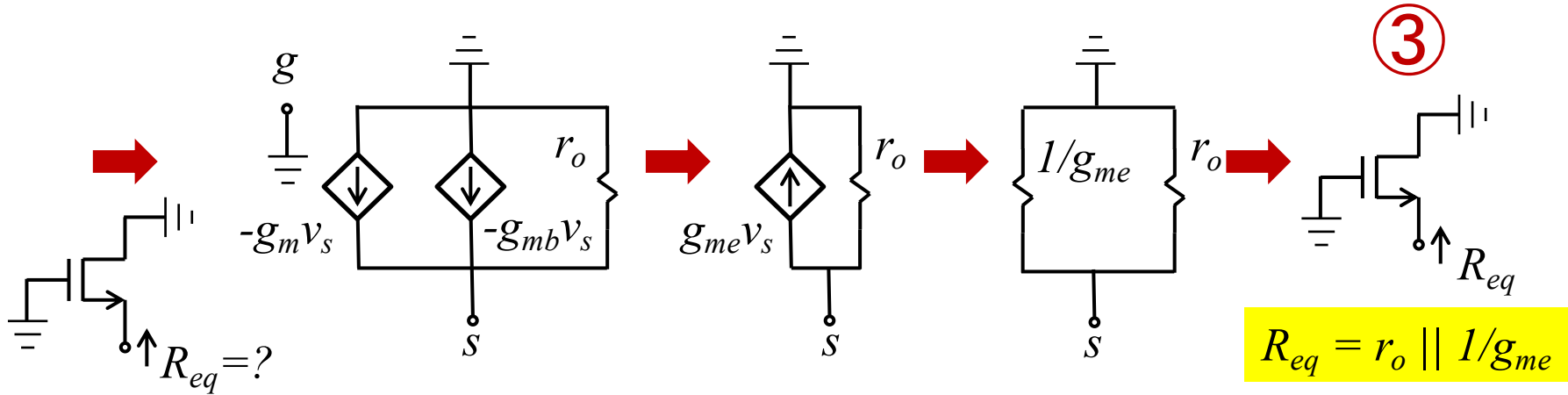


- $g_{me} = g_m + g_{mb} = 1.1-1.2 g_m$
- Looking into the source, while gate and drain are grounded, we see a resistor whose value is  $R_{eq} = r_o \parallel 1/g_{me} \approx 1/g_{me}$

# Diode-Connected Transistor

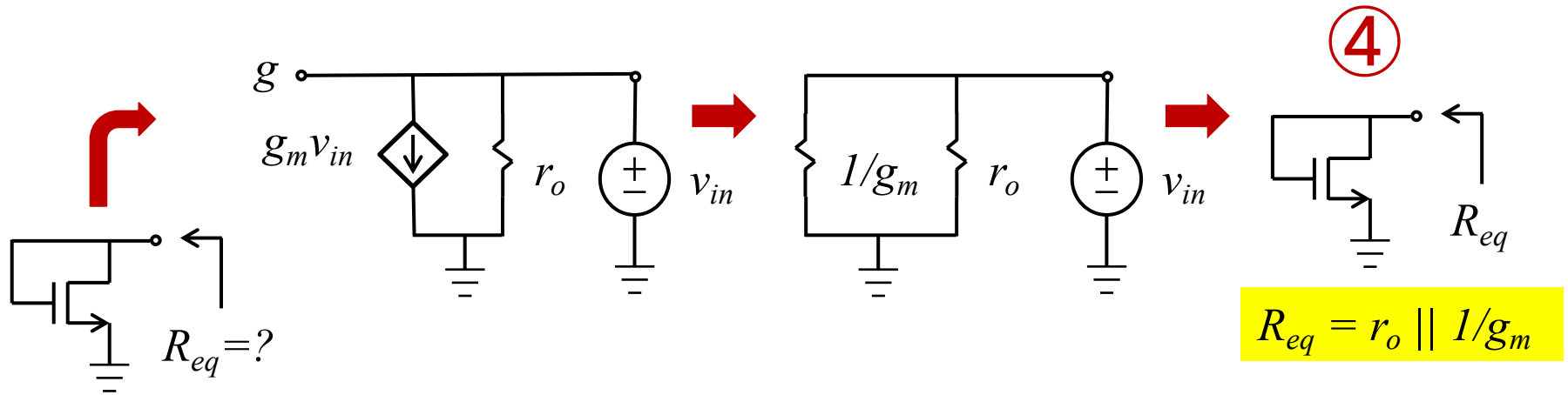


- A diode-connected transistor is a resistor whose value is  $R_{eq} = r_o \parallel 1/g_m \approx 1/g_m$

# Looking into the Drain with $R_S$

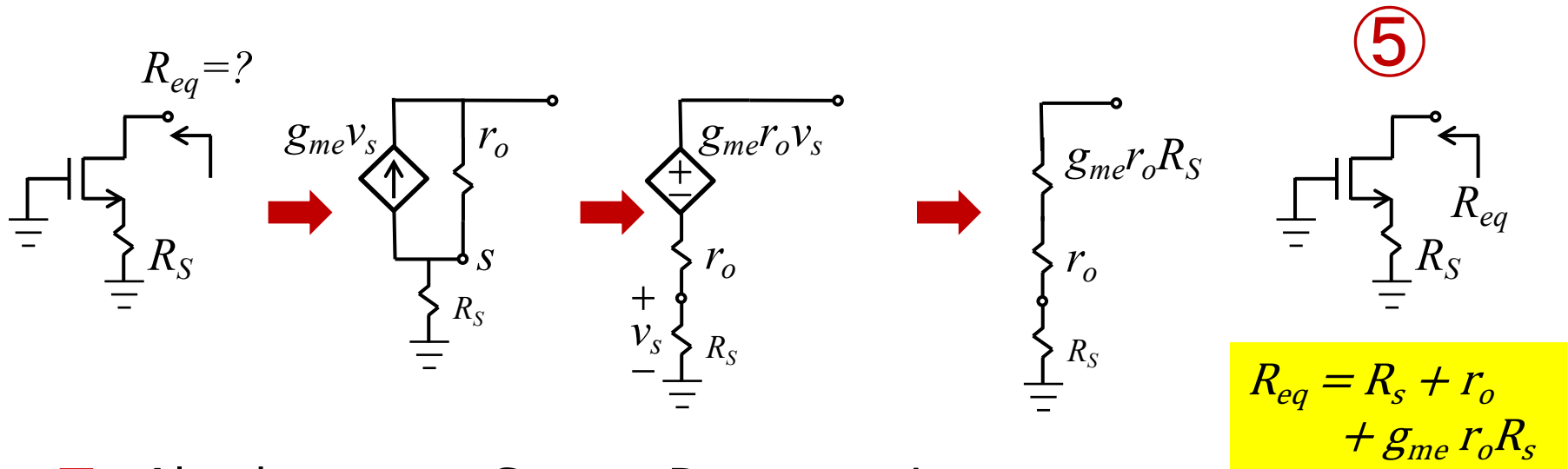

- Also known as Source Degeneration
- Effective way to increase the output impedance
- Multiplying the source resistance by  $g_{me}r_o$

# Looking into the Source with $R_D$

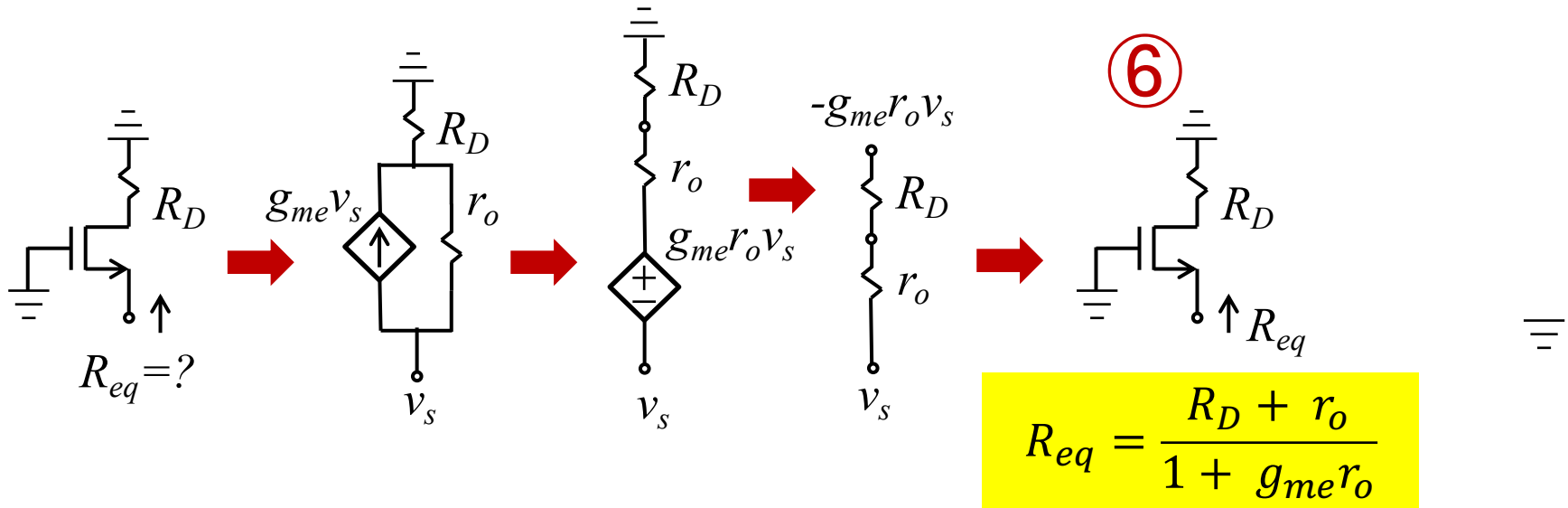

- If  $R_D \ll r_o$ , then  $R_{eq} \approx 1/g_m$
- $R_D$  is divided by  $(1 + g_m r_o)$  and appears at the source

# Looking into the Drain with Input

Two Methods:


- Find the Thevenin Equivalent Circuit:
  - open-circuit voltage  $v_{oc}$  in series with  $R_{eq}$
- Find Norton Equivalent Circuit:
  - short-circuit current  $i_{sc}$  in parallel with  $R_{eq}$
- Note that  $v_{oc} = i_{sc} \times R_{eq}$

In this circuit, easier to find  $v_{oc}$  first

→  $v_s = 0$ , no body effect,  $v_{oc} = -g_m r_o v_{in}$

→  $i_{sc} = v_{oc} / R_{eq}$

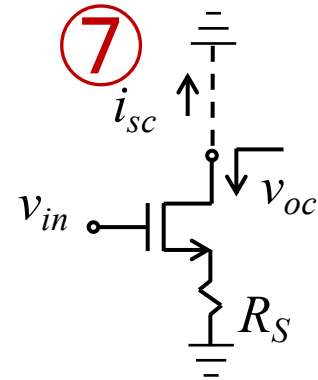
Norton more intuitive due to high  $R_{eq}$



$$v_{oc} = -g_m r_o v_{in}$$
$$i_{sc} = v_{oc} / R_{eq}$$
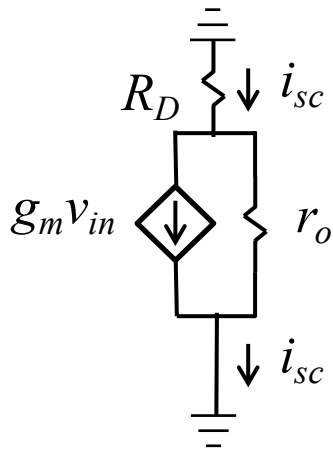
# Looking into the Source with Input


- Find Norton Equivalent Circuit first:
  - short-circuit current  $i_{sc}$  in parallel with  $R_{eq}$
- Shorting output to ground  $\rightarrow v_s=0$



→ Use current division


$$\rightarrow i_{sc} = g_m v_{in} \frac{r_o}{r_o + R_D}$$

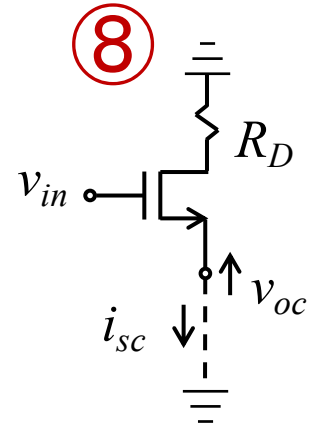→ Given small  $R_{eq}$ , Thevenin is more intuitive




$$i_{sc} = \frac{g_m v_{in} r_o}{r_o + R_D}$$
$$v_{oc} = i_{sc} R_{eq}$$


# Putting It All Together (1 to 4)

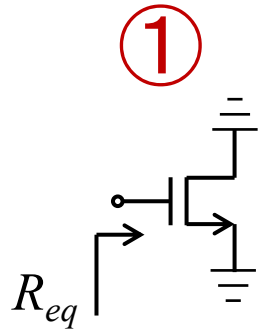


$$R_{eq} = \infty$$

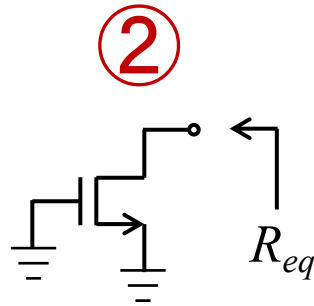

$$R_{eq} = r_o$$

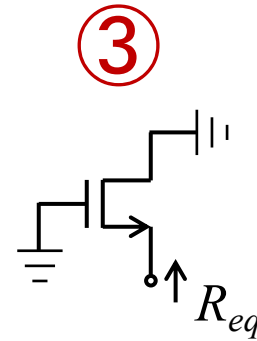

$$R_{eq} = r_o \parallel 1/g_{me}$$

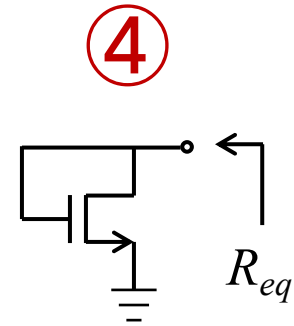


$$R_{eq} = r_o \parallel 1/g_m$$

- Looking into one terminal while the other two grounded
- Looking into the drain of a diode-connected transistor
- No additional resistor in the circuit


# Putting It All Together (5 to 8)

⑤

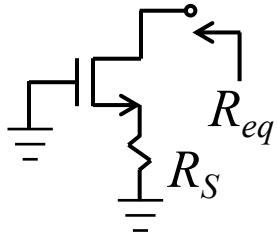


$$R_{eq} = R_S + r_o + g_{me} r_o R_S$$

⑥

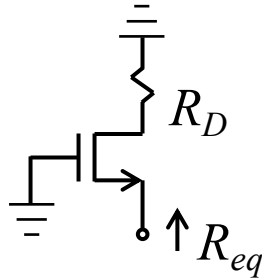


$$R_{eq} = \frac{R_D + r_o}{1 + g_{me} r_o}$$

⑦

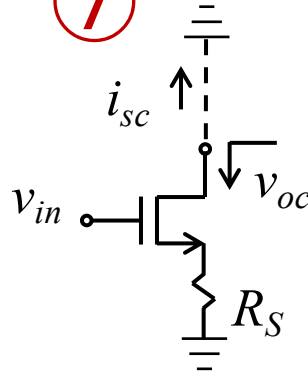

$$v_{oc} = -g_m r_o v_{in}$$
$$i_{sc} = v_{oc} / R_{eq}$$

⑧

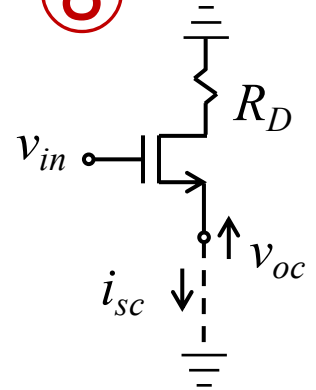

$$i_{sc} = \frac{g_m v_{in} r_o}{r_o + R_D}$$
$$v_{oc} = i_{sc} R_{eq}$$

□ Adding resistors and input to the circuit



# Finding Voltage of “any” Node

---


Method 1: Use Norton equivalent circuit

- Short the node to ground; find  $i_{sc}$
- Find  $R_{eq}$  (using library elements)
- Multiply the two:  $v_{out} = i_{sc} \times R_{eq}$

Method 2: Use Thevenin equivalent circuit

- Open the load; find  $v_{oc}$
- Find  $R_{eq}$  (same as in Method 1)
- Use voltage divider rule to find  $v_{out}$

# Example: Common-Source Amplifier

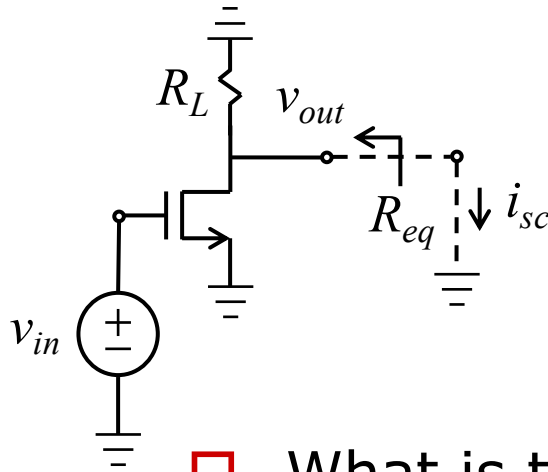

**Finding  $v_{out}$ :** Use  $i_{sc} \times R_{eq}$ :

$$\rightarrow i_{sc} = -g_m v_{in}$$

$$\rightarrow R_{eq} = R_L \parallel r_o$$

$$\rightarrow v_{out} = -g_m (R_L \parallel r_o) v_{in}$$

□ What is the intuition here?

■ How to increase the gain? How to increase  $v_{out}$  ?


■ Output voltage comes from  $i_{sc} \times R_{eq}$

■  $\rightarrow$  either increase  $i_{sc}$  or  $R_{eq}$

□ How can we increase these two?

# Example: Cascode Circuit

---

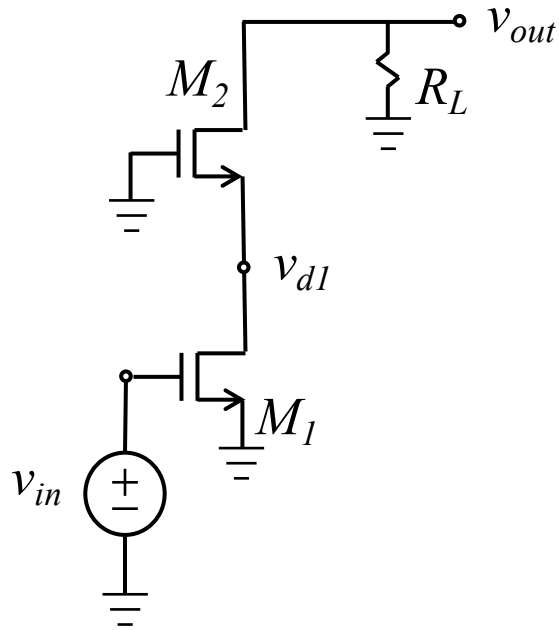


To find the output voltage

- Use  $i_{sc} \times R_{eq}$ :
- Find out how  $i_{sc}$  and  $R_{eq}$  change compared to those for CS amplifier
- Gain intuition on why the gain changes from one to the other.
- Also, find intermediate voltages (such as  $v_{d1}$ ) for added insight

# Cascode Circuit: Find any Voltage (1)

## Method 1:

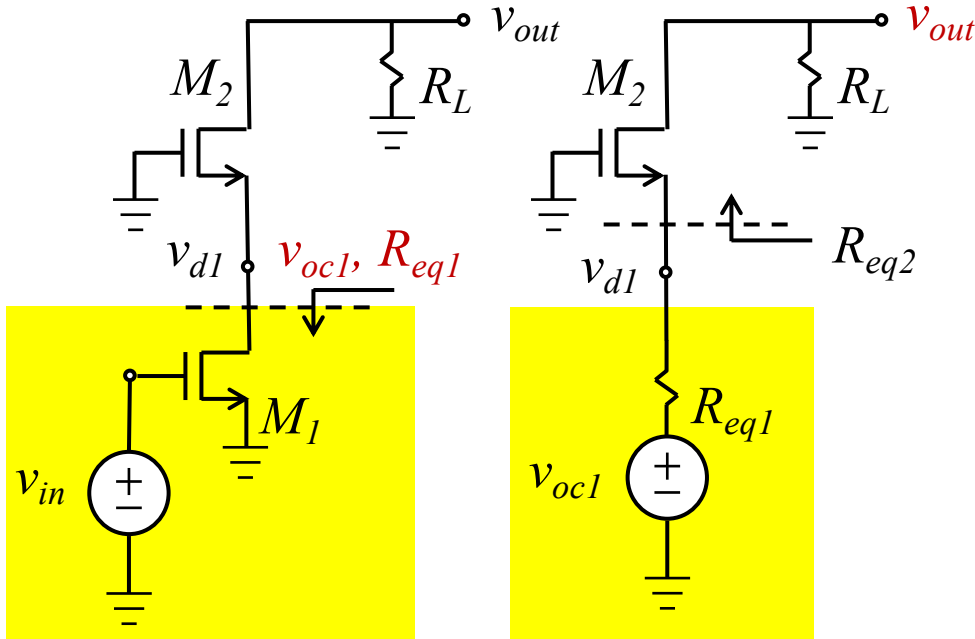

**Finding  $v_{d1}$ :** Use Thevenin:



$$\begin{aligned} \textcircled{2} &\rightarrow R_{eq1} = r_{o1} \\ \textcircled{7} &\rightarrow v_{oc1} = -g_m r_{o1} v_{in} \\ \textcircled{6} &\rightarrow R_{eq2} = (r_{o2} + R_L) / (1 + g_{me2} r_{o2}) \\ &\rightarrow v_{d1} = -g_m r_{o1} v_{in} (r_{o1} \parallel R_{eq2}) \end{aligned}$$

**Finding  $v_{out}$ :** Use  $R_{eq2}$  to find the load current first :

$$\begin{aligned} &\rightarrow i_L = v_{d1} / R_{eq2} \\ &\rightarrow v_{out} = i_L R_L = v_{d1} R_L / R_{eq2} \end{aligned}$$

# Cascode Circuit: Find any Voltage (2)

## Method 2:

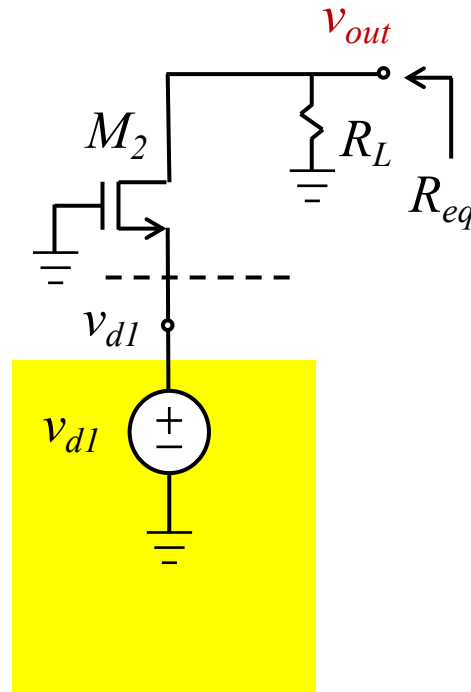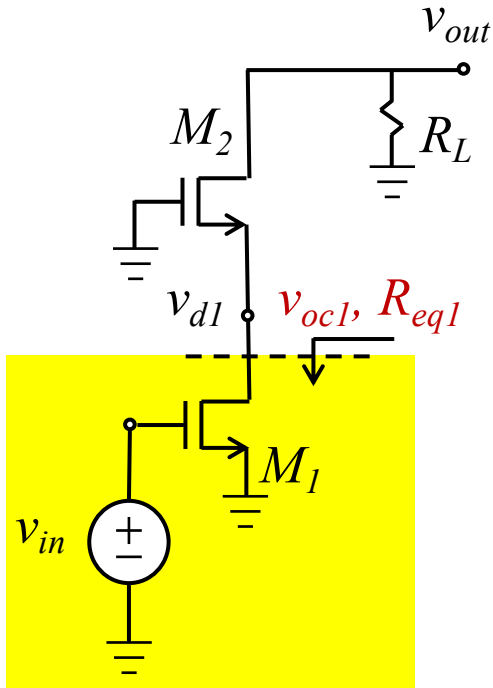

## Finding $v_{d1}$ :

(as in previous slide)

$$\rightarrow v_{d1} = -g_m r_{o1} v_{in} (r_{o1} \parallel R_{eq2})$$

## Treat $v_{d1}$ as ideal source:



Find  $i_{sc}$  and  $R_{eq}$  at the output:

$$\rightarrow i_{sc} = v_{d1} / (1/g_{m1} \parallel r_{o1})$$

$$\rightarrow R_{eq} = r_{o1} \parallel R_L \text{ (not } R_{eq} \text{ of original cct)}$$

$$\rightarrow v_{out} = i_{sc} R_{eq}$$


# What Is the Intuition here?

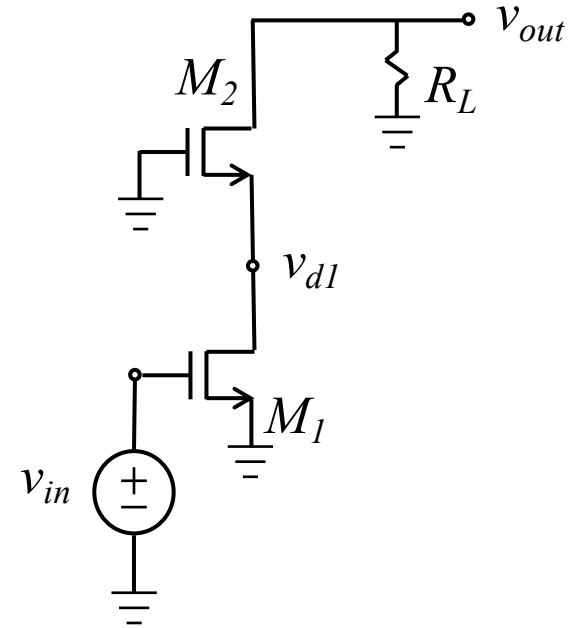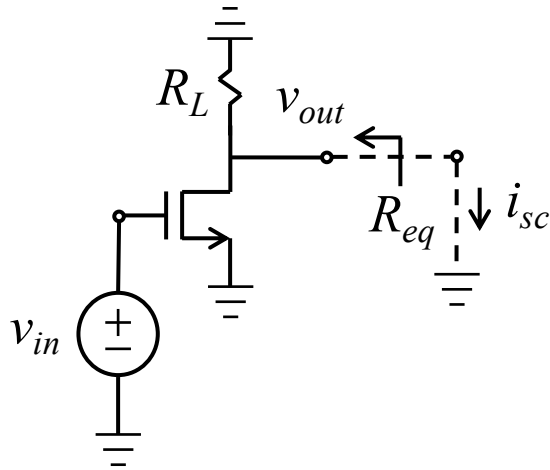

- $i_{sc}$  remained the same
- $R_{eq}$  increased by  $g_m r_o$
- Voltage gain increased by  $g_m r_o$

# Example: Differential Pair (1)

## Method 1:

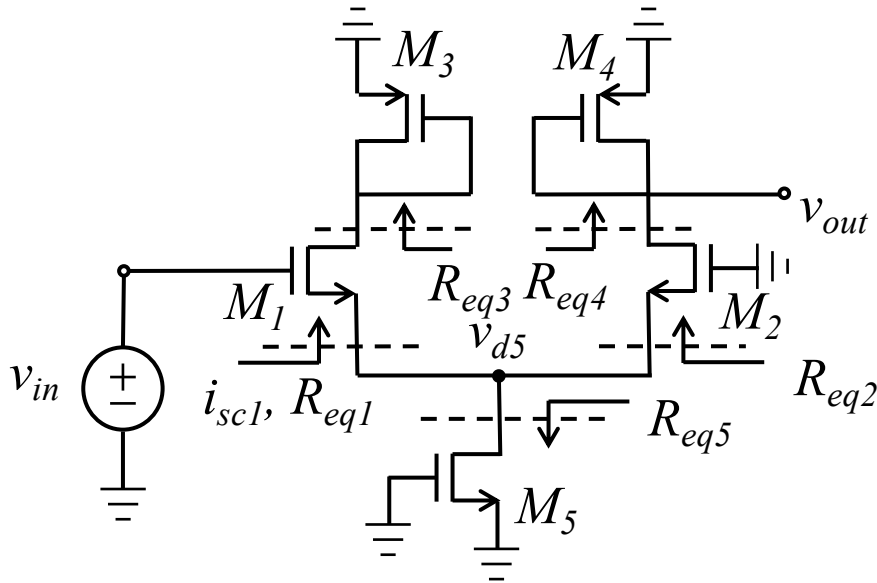

**Finding  $v_{d5}$ :** Use the Norton Equivalent at *the source of  $M_1$* :

$$\textcircled{4} \rightarrow R_{eq3} = r_{o3} \parallel 1/g_{m3}$$

$$\textcircled{6} \rightarrow R_{eq1} = (R_{eq3} + r_{o1}) / (1 + g_{m1}r_{o1})$$

$$\textcircled{8} \rightarrow i_{sc1} = g_{m1} v_{in} r_{o1} / (r_{o1} + R_{eq3})$$

$$\textcircled{2} \rightarrow R_{eq5} = r_{o5}$$

$$\textcircled{4} \rightarrow R_{eq4} = r_{o4} \parallel 1/g_{m4}$$

$$\textcircled{6} \rightarrow R_{eq2} = (R_{eq4} + r_{o2}) / (1 + g_{m2}r_{o2})$$


$$\rightarrow v_{d5} = i_{sc1} (R_{eq1} \parallel R_{eq5} \parallel R_{eq2})$$

**Finding  $v_{out}$ :**

$$\rightarrow v_{out} = (v_{d5} / R_{eq2}) R_{eq4}$$

# Example: Differential Pair (2)

## Method 2:

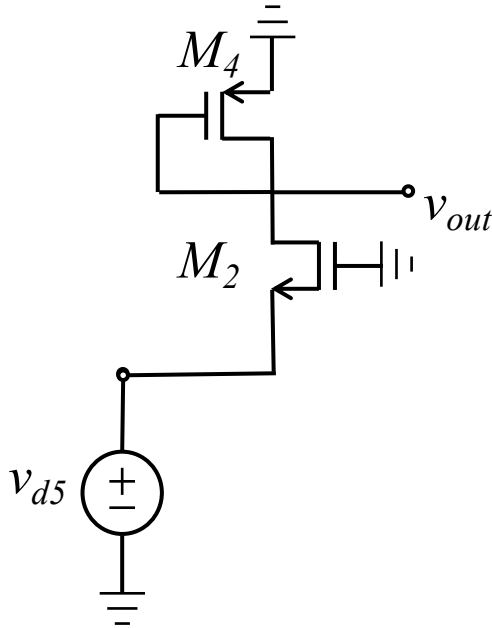

**Treat  $v_{d5}$  as ideal source:**  
(from previous slide)

$$\rightarrow v_{d5} = i_{sc1} (R_{eq1} \parallel R_{eq5} \parallel R_{eq2})$$

**Finding  $v_{out}$ :**

Find  $i_{sc}$  and  $R_{eq}$  at the output:

$$\rightarrow i_{sc} = v_{d5} / (r_{o2} \parallel 1/g_{me2})$$

$$\rightarrow R_{eq} = r_{o2} \parallel r_{o4} \parallel 1/g_{m4}$$


*Note: not equal to  $R_{eq}$  of original circuit*

$$\rightarrow v_{out} = i_{sc} R_{eq}$$




# Example: Diode-Connected Cascode

---

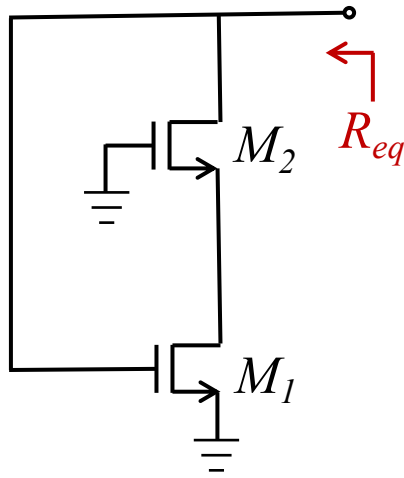


- Not one of the standard library elements
- Apply a voltage, measure current
- Use Superposition to find current
- Ratio of test voltage to current is  $R_{eq}$
- Intuition?

# Diode-Connected Cascode

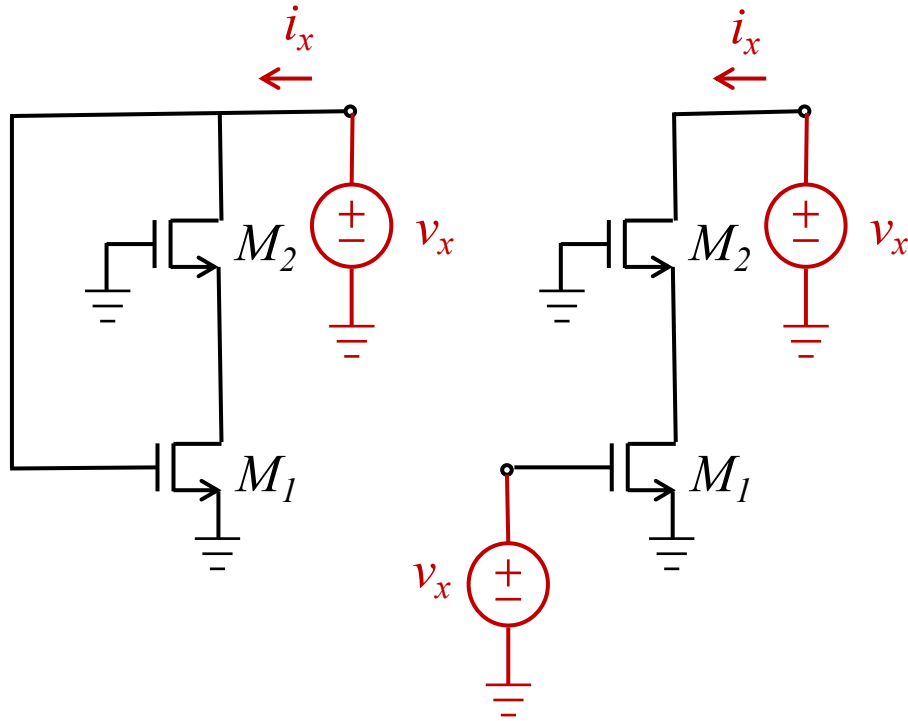

- The two circuits are equivalent
- Treat two sources as independent
- Use Superposition

# Diode-Connected Cascode

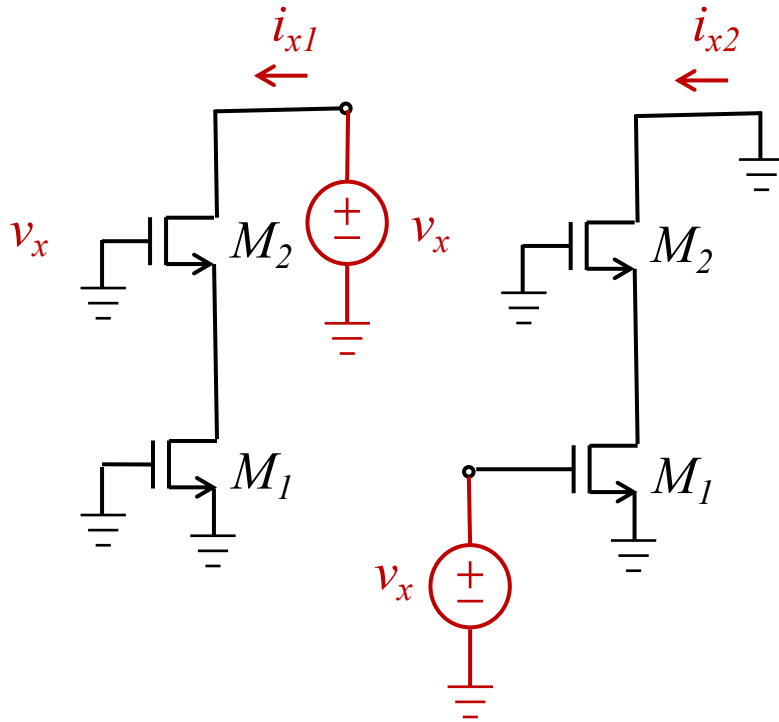

- $i_x = i_{x1} + i_{x2}$
- $R_{eq} = R_{eq1} \parallel R_{eq2}$
- $R_{eq1} \cong g_{m2} r_{o1} r_{o2}$
- $R_{eq2} \cong 1/g_{m1}$
- $R_{eq} \cong 1/g_{m1}$

# Summary

---

- In small-signal, all transistor circuits (assuming saturation region) can be treated as LTI circuit
- Transistor circuits without a signal source are resistors
  - This is for low-frequencies only
  - At high-frequencies, we should add capacitors
  - See other circuit intuition articles for high frequencies
- Transistor circuits with input signal are represented by:
  - Their Thevenin equivalent circuits, or
  - Their Norton equivalent circuits
- There are different ways to arrive at the solution
- Use the method that adds intuition!

# References (1 of 2)

---

## All in Solid-State Circuit Magazine

- [A20] Circuit Intuitions: Transfer Resistor, Winter 2019.
- [A19] Circuit Intuitions: Thevenin and Norton Equivalent Circuits, Part 3, Fall 2018.
- [A18] Circuit Intuitions: Thevenin and Norton Equivalent Circuits, Part 2, Su. 2018.
- [A17] Circuit Intuitions: Thevenin and Norton Equivalent Circuits, Spring 2018.
- [A16] Circuit Intuitions: Random Walk in a Ring, Winter 2018.
- [A15] Circuit Intuitions: Reinventing the Wheel, Fall 2017.
- [A14] Circuit Intuitions: Capacitor as a Resistor, Summer 2017.
- [A13] Circuit Intuitions: Why Sinusoids?, Spring 2017.
- [A12] Circuit Intuitions: A Capacitor Analogy, Part 3, Winter 2017.
- [A11] Circuit Intuitions: A Capacitor Analogy, Part 2, Fall 2016.
- [A10] Circuit Intuitions: A Capacitor Analogy, Part 1, Summer 2016.
- [A9] Circuit Intuitions: Chopper Amplifier, Spring 2016.

# References (2 of 2)

---

## All in Solid-State Circuit Magazine

- [A8] Circuit Intuitions: Offset Cancellation, Winter 2016.
- [A7] Circuit Intuitions: Miller's Approximation, Fall 2015.
- [A6] Circuit Intuitions: Miller's Theorem, Summer 2015.
- [A5] Circuit Intuitions: Bandwidth Extension, Spring 2015.
- [A4] Circuit Intuitions: Process Variation and Pelgrom's Law, Winter 2015.
- [A3] Circuit Intuitions: Negative Resistance, Fall 2014.
- [A2] Circuit Intuitions: Source Degeneration, Summer 2014.
- [A1] Circuit Intuitions: Looking into a Node, Spring 2014.
  - See also Correction to Looking Into a Node, Summer 2014.

# Acknowledgement

---

I would like to thank my undergraduate students at the University of Toronto, who have been the inspirations behind writing these articles.