


Dissecting Design Choices for Power Efficient Continuous-time $\Delta\Sigma$ Converters

Shanthi Pavan
Indian Institute of Technology, Madras
Chennai, India

Outline


- Introduction
- Architectural design choices
- Circuit techniques for low power
- Design details
- Measured results
- Conclusions

CT $\Delta\Sigma$ M in 1 minute

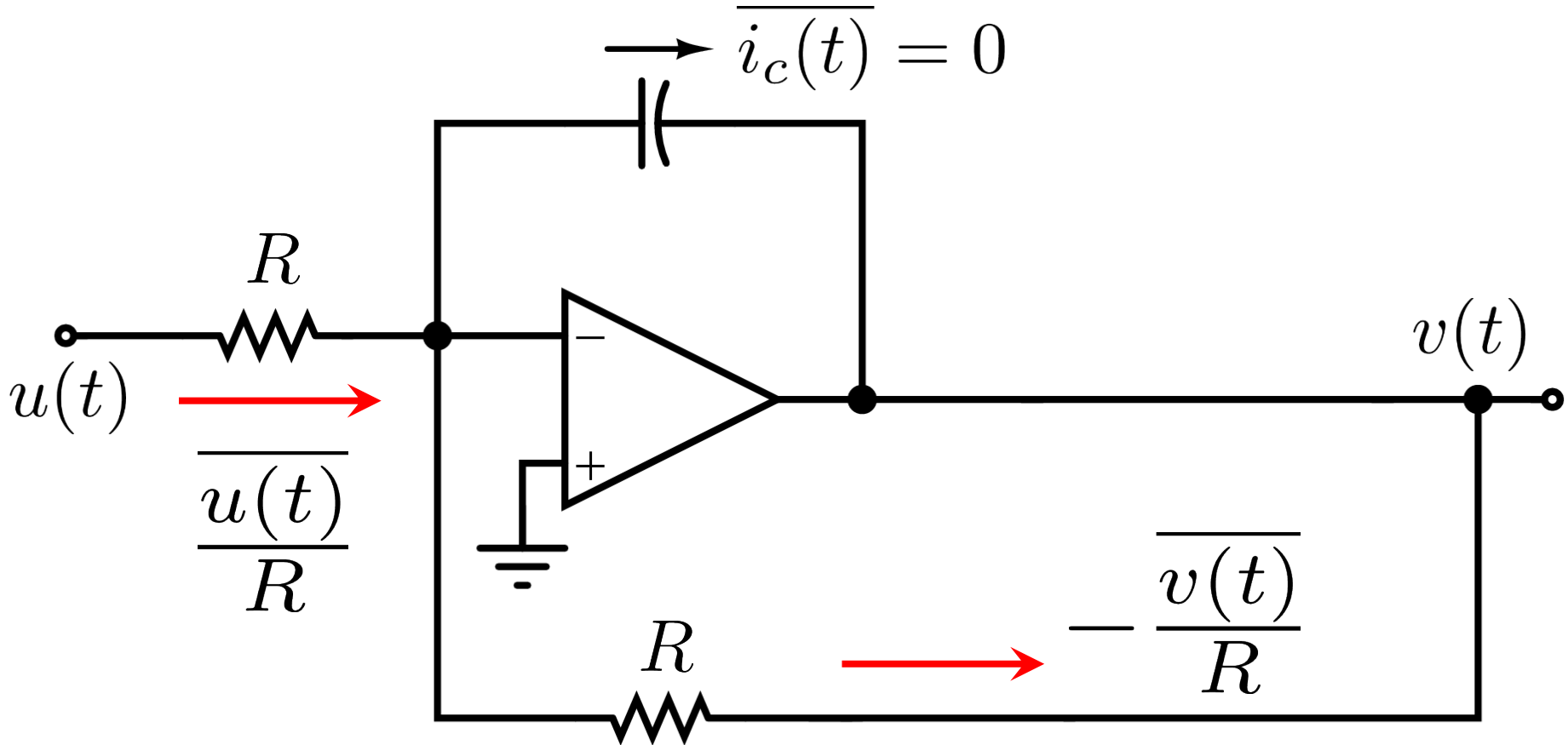


$$\overline{u(t)} = -\overline{v(t)}$$


CT $\Delta\Sigma$ M in 1 minute

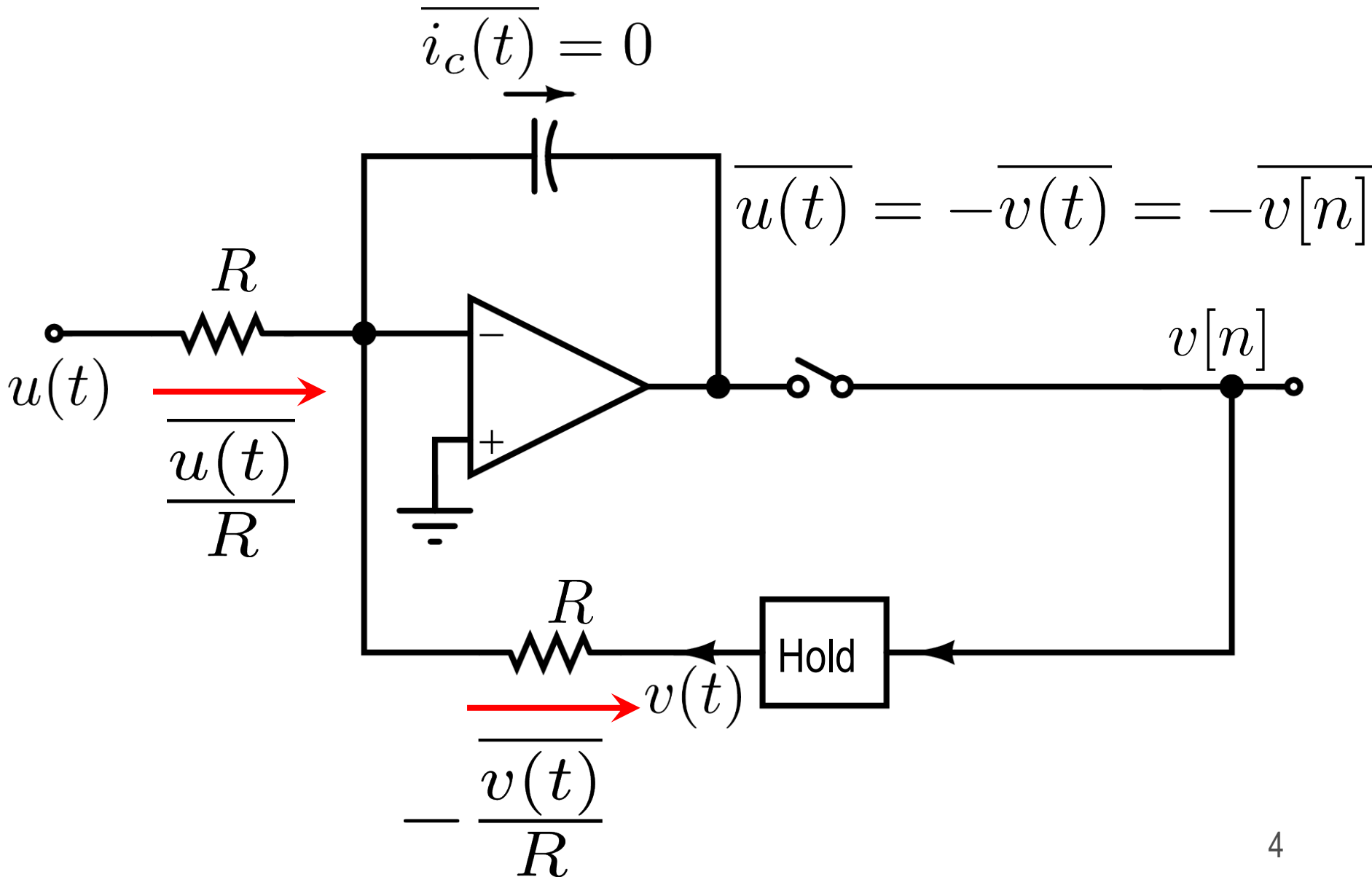

CT $\Delta\Sigma$ M in 1 minute

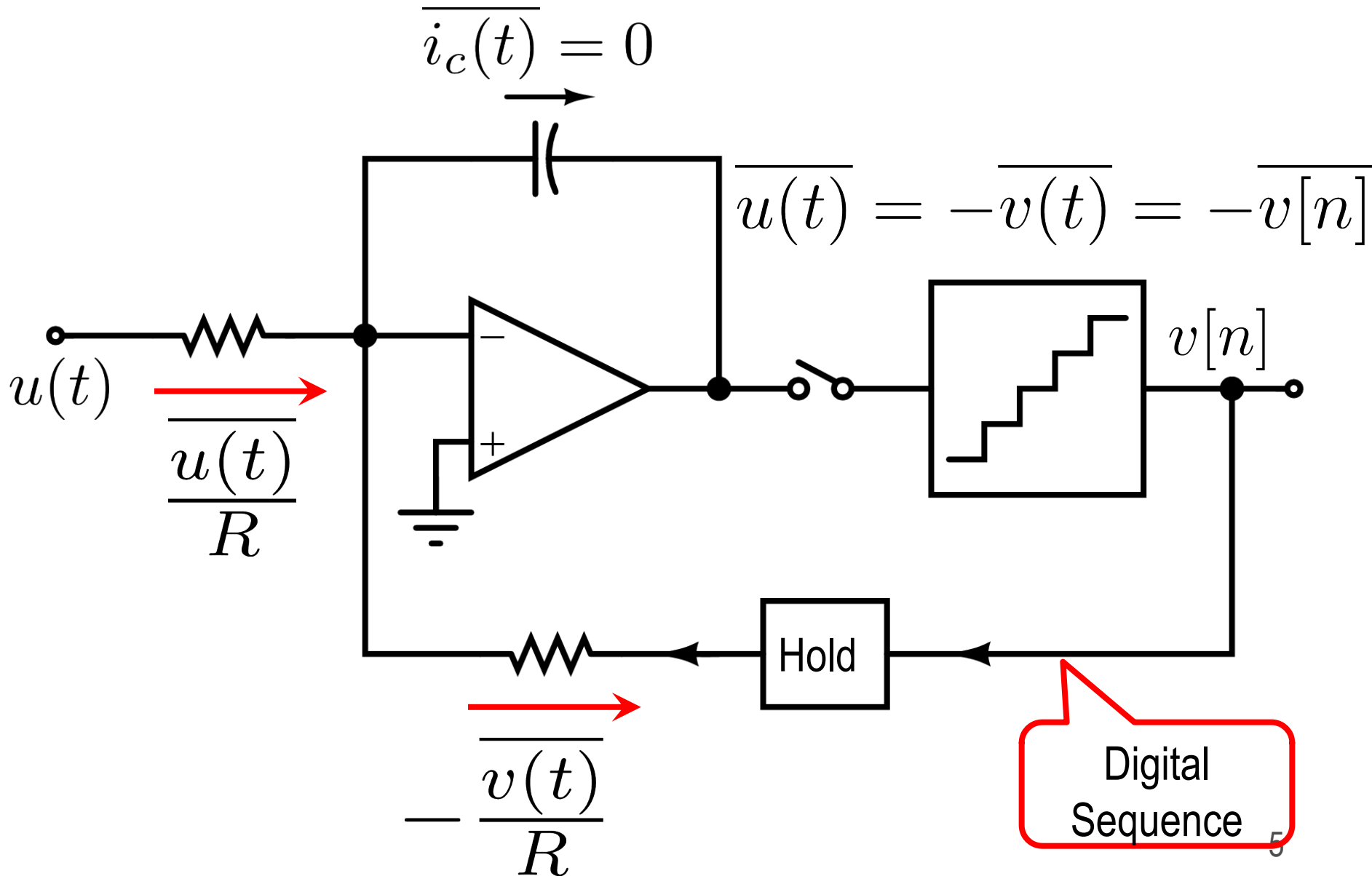


CT $\Delta\Sigma$ M in 1 minute

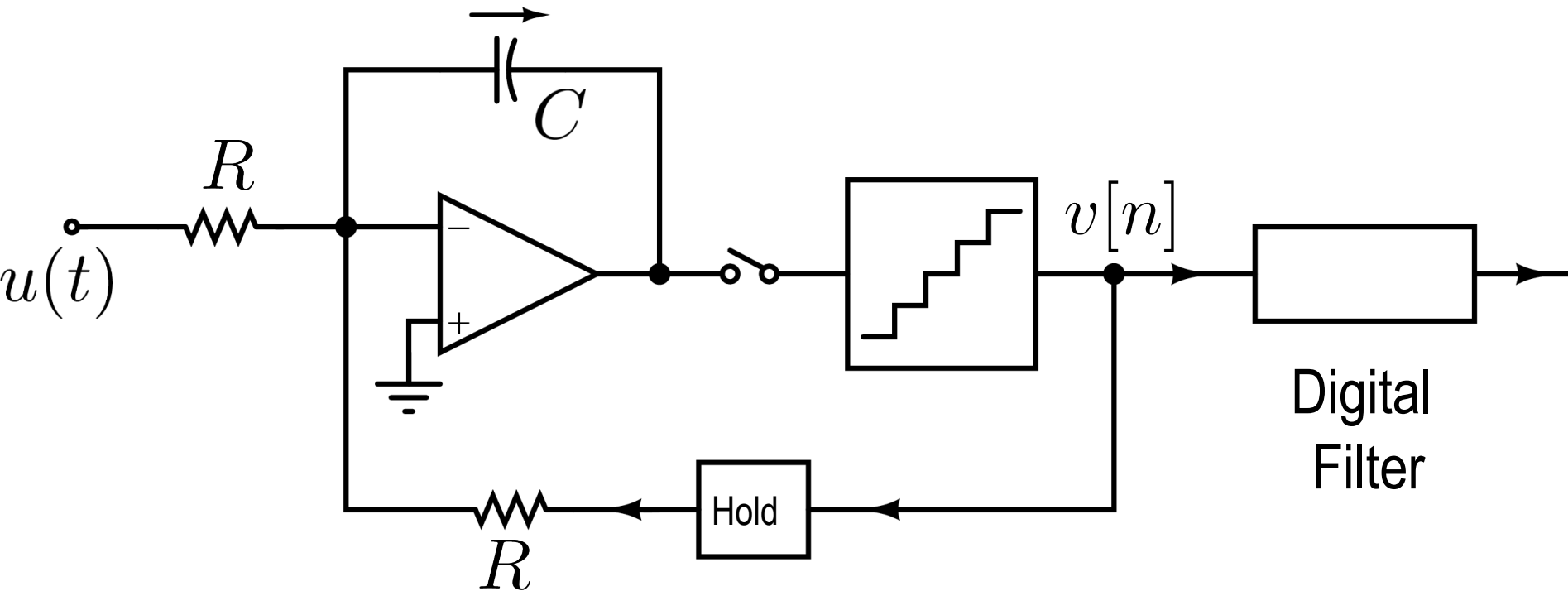


$$\text{Slow } u(t) \longrightarrow \overline{u(t)} \approx u(t)$$

Does the number of quantizer levels matter?


CT $\Delta\Sigma$ M in 1 minute

 

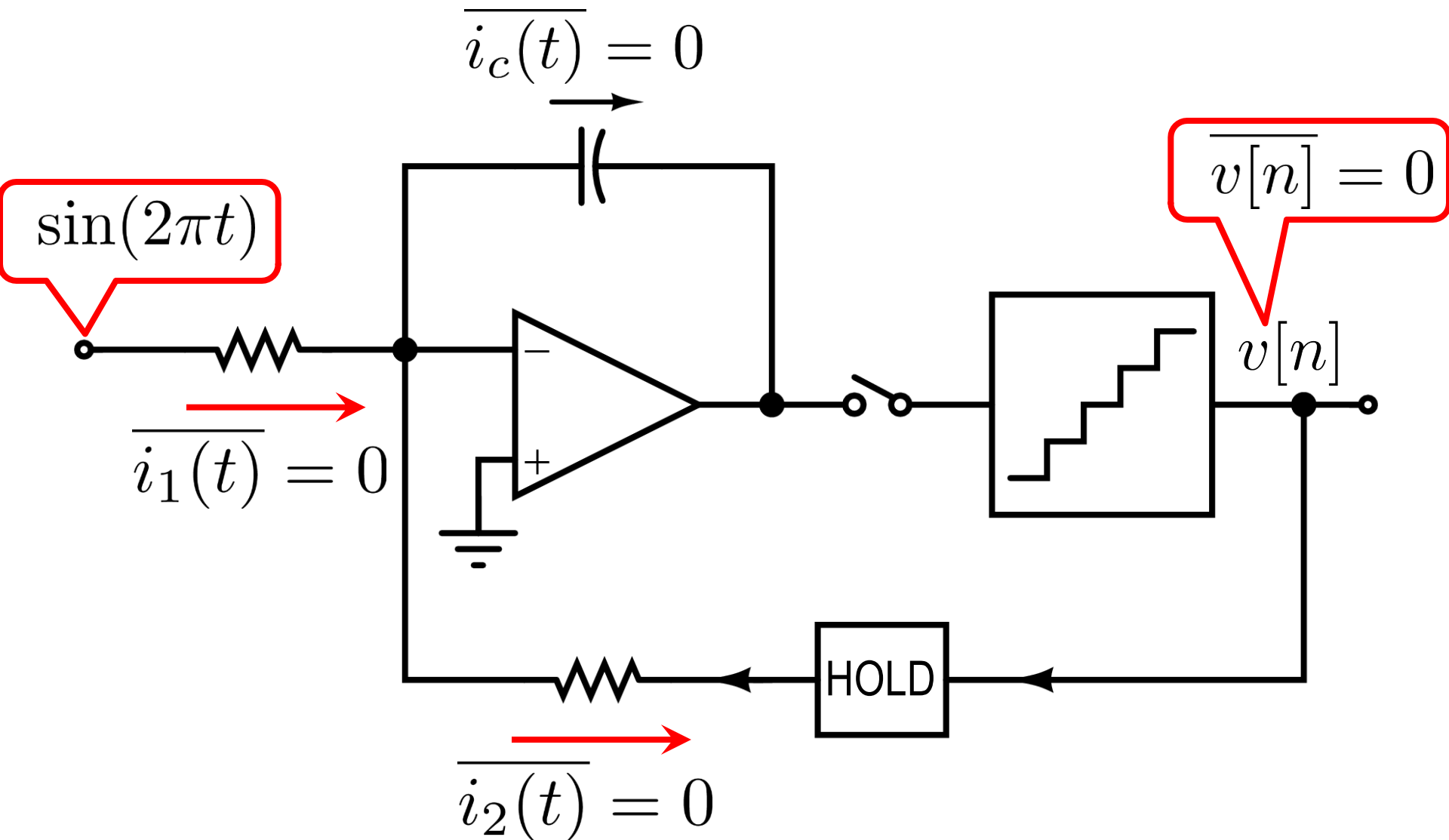CT $\Delta\Sigma$ M in 1 minute : Antialiasing




CT Δ Σ M : A System for all Seasons

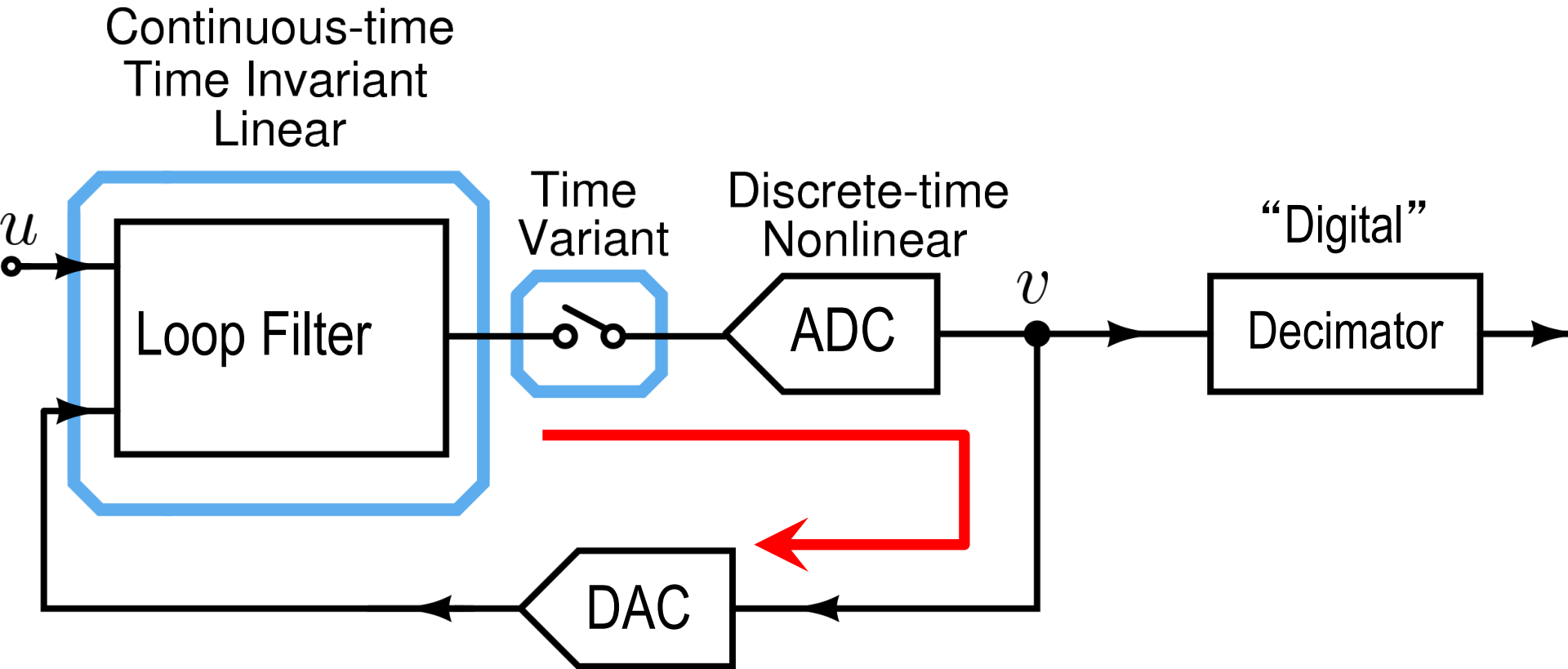

Negative Feedback

Industrially and Practically Relevant

(Too) Many Design Choices

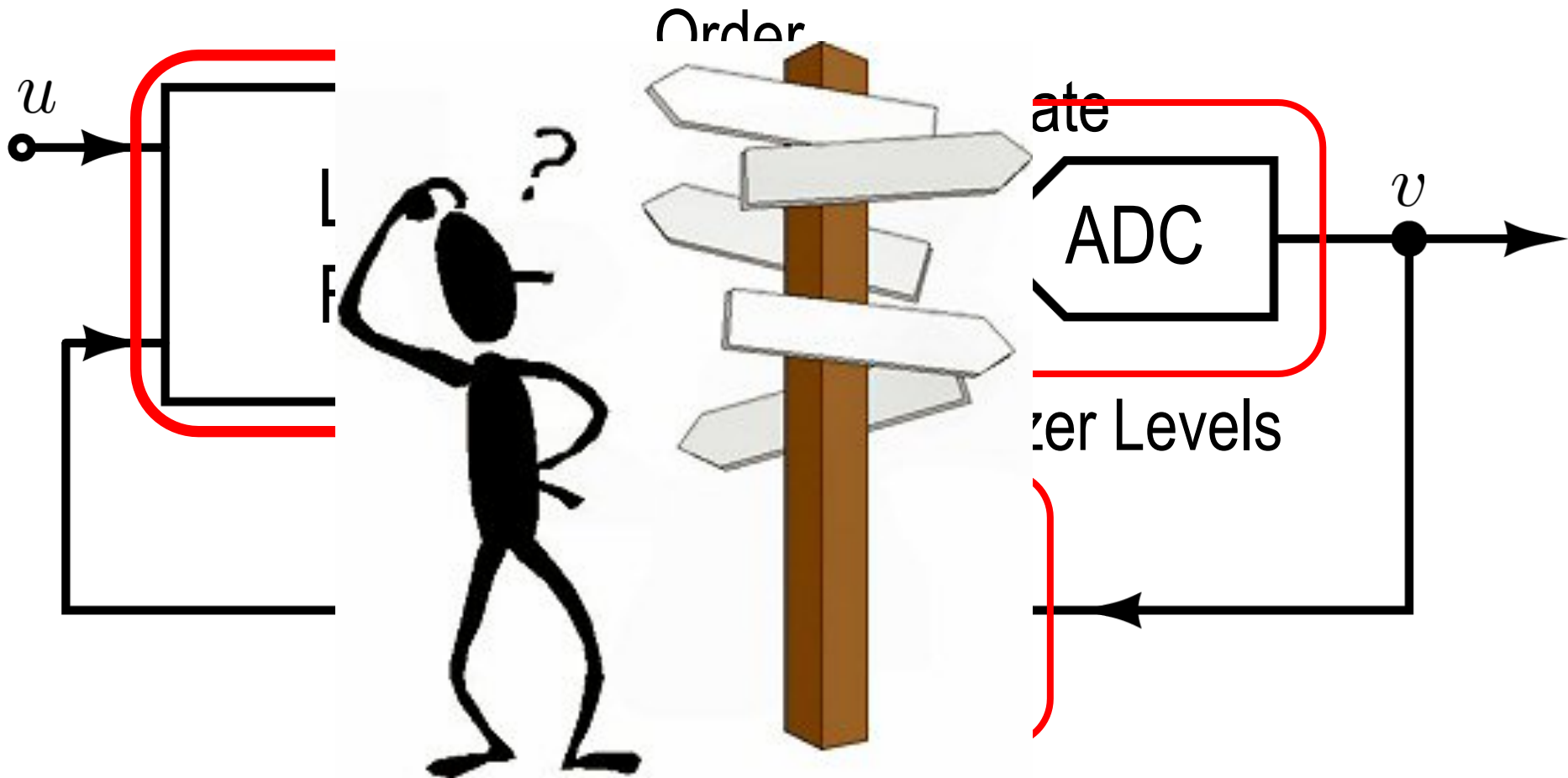


Curse of Too Many Choices

- Single bit quantizer + high OSR
 - Or multibit quantizer + low OSR?
- Flash ADC
 - Or SAR ADC?
- NRZ DAC
 - Or Switched capacitor DAC for low jitter?

Buridan's Ass



$\Delta\Sigma$ Designer ...

 


Motivation

- Aim : Audio DSM with > 100 dB DR
 - $0.18\mu\text{m}$ CMOS technology
 - As low power as possible
- Low distortion (~ 100 dB) audio $\Delta\Sigma$ converters
 - Typically realized with discrete-time, multi-bit loops

Single-bit versus Multibit Modulators


Quantizer : 1-bit versus 4-bit

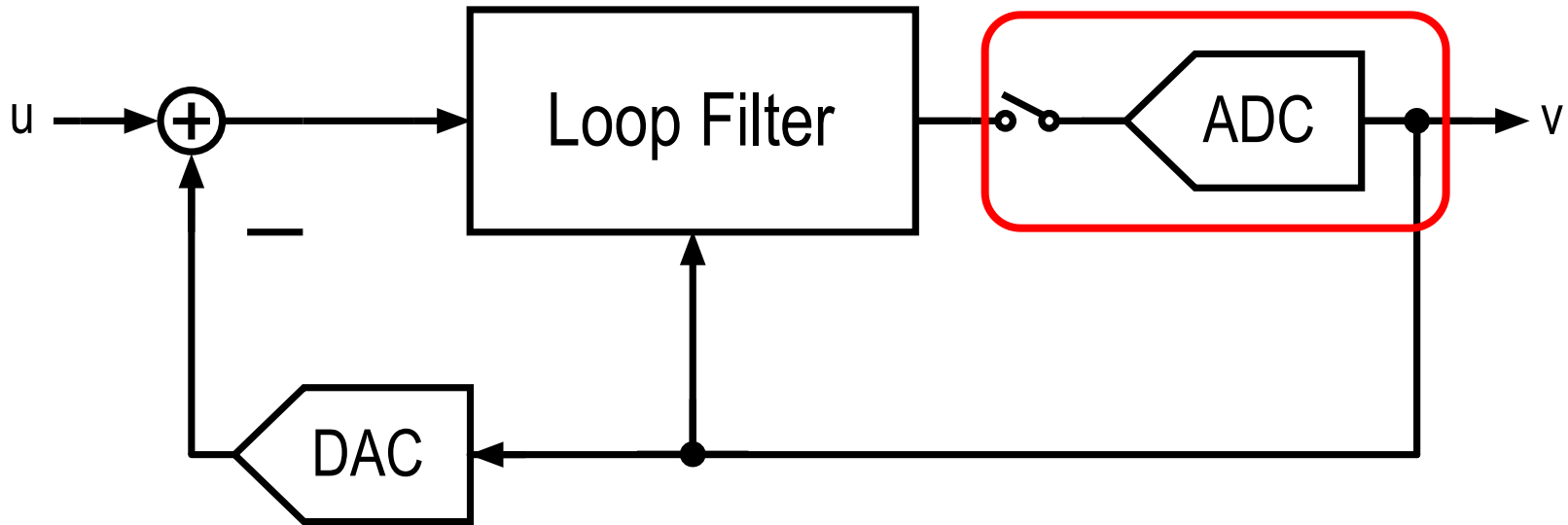

4-bit quantizer needs half the OSR
to achieve same in-band noise



(Baseline : 3rd Order Single-bit DSM, OSR =128)

ADC Resolution

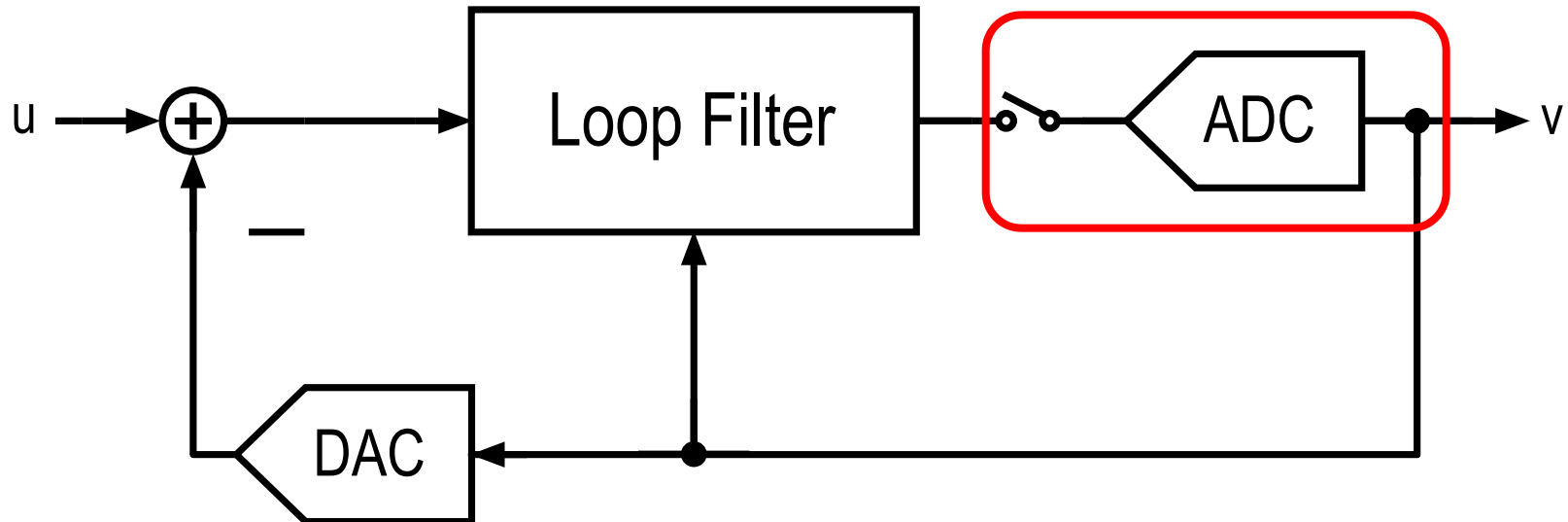


- 4 bit ADC
 - 15x more comparators @ 1/2 speed
 - 7x more ADC power, 15x more area
 - 15x loop filter & clock path loading

Comparator Random Offset

 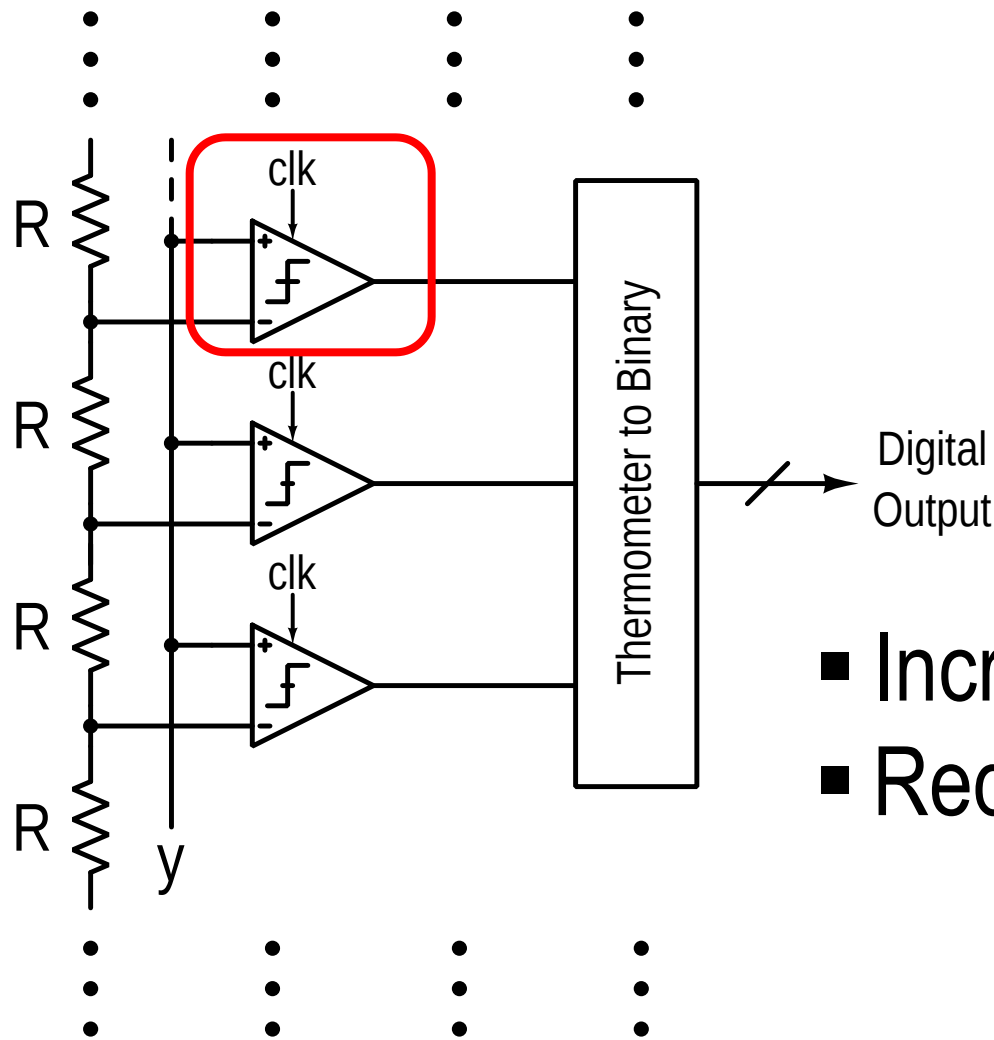


- Increased in-band noise
- Reduced stable amplitude

SNDR with Random Offset

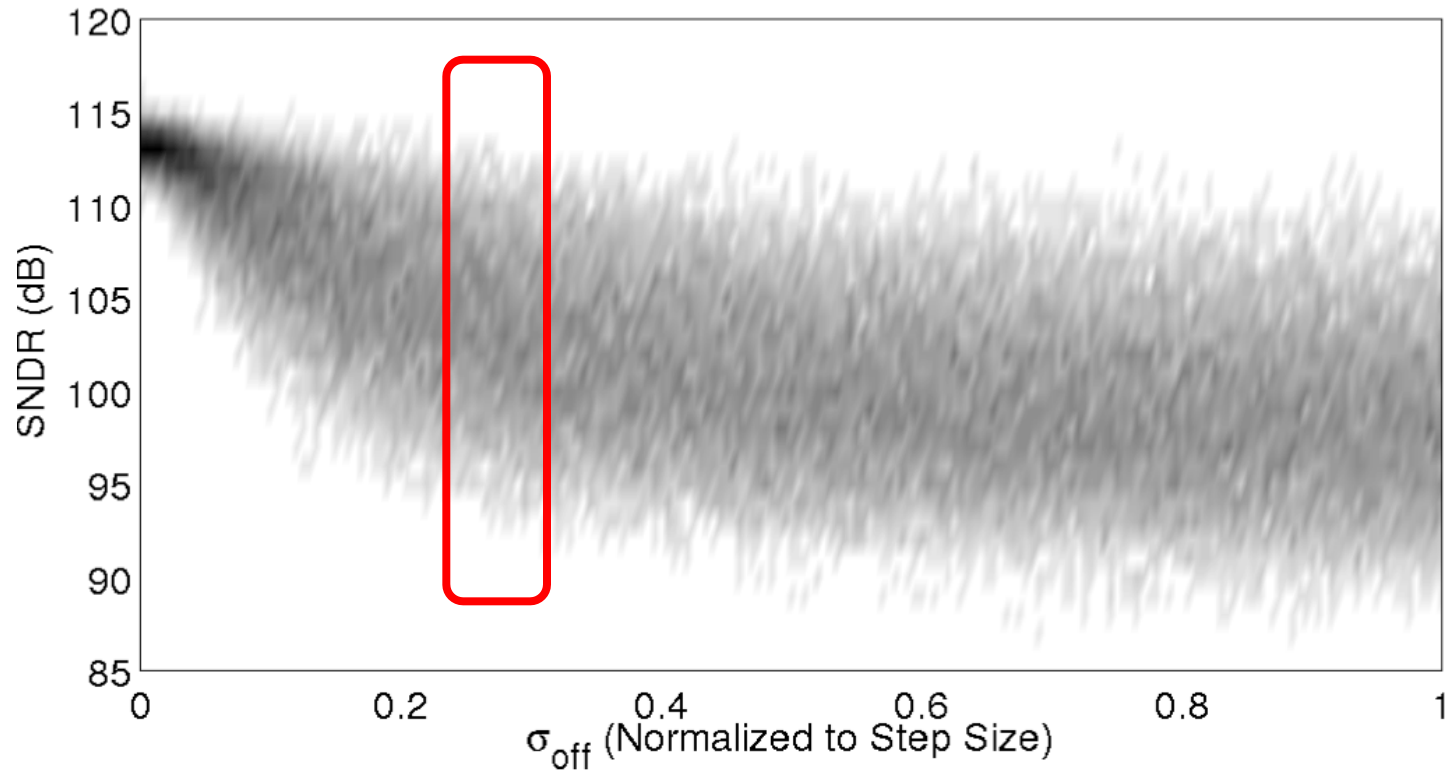


Third-order Modulator 16-level Quantizer

Loop Filter

 


- Loop filter should swing full-scale
- Difficult in high-speed designs

Loop Filter

 

- Comparator offset is benign
- Driving the 1-bit quantizer
 - Loop filter's last stage simpler to design
 - Particularly useful at high speeds


DAC : 1-bit versus 4-bit

 

A single bit quantizer consumes
lesser power
though it operates at 2x the speed


- Needs Dynamic Element Matching
- DEM adds excess delay & power

Single-bit CTDSM Issues : Clock Jitter

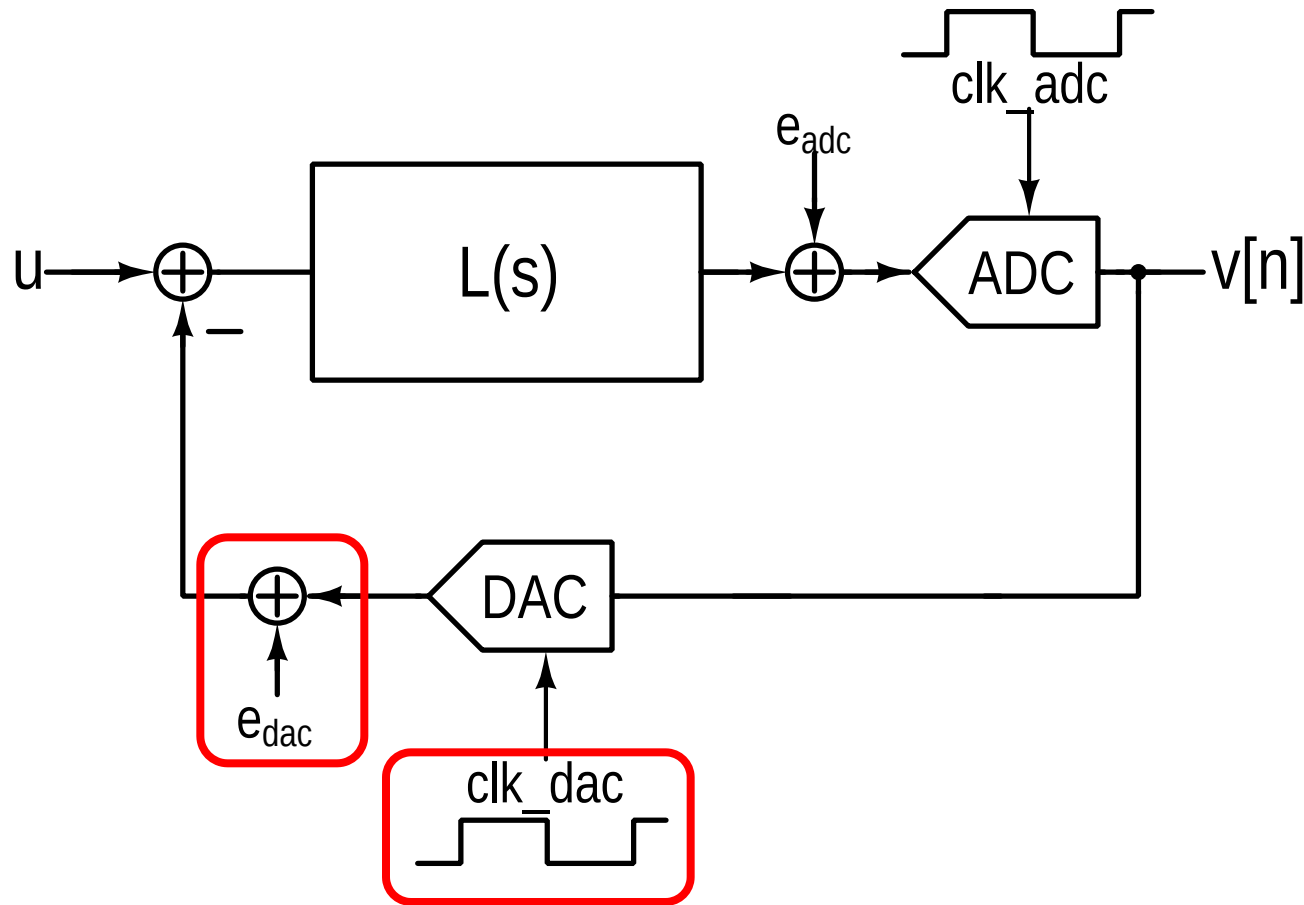


Jittery clock \rightarrow equivalent to error at the input

Single-bit CTDSM Issues : Clock Jitter

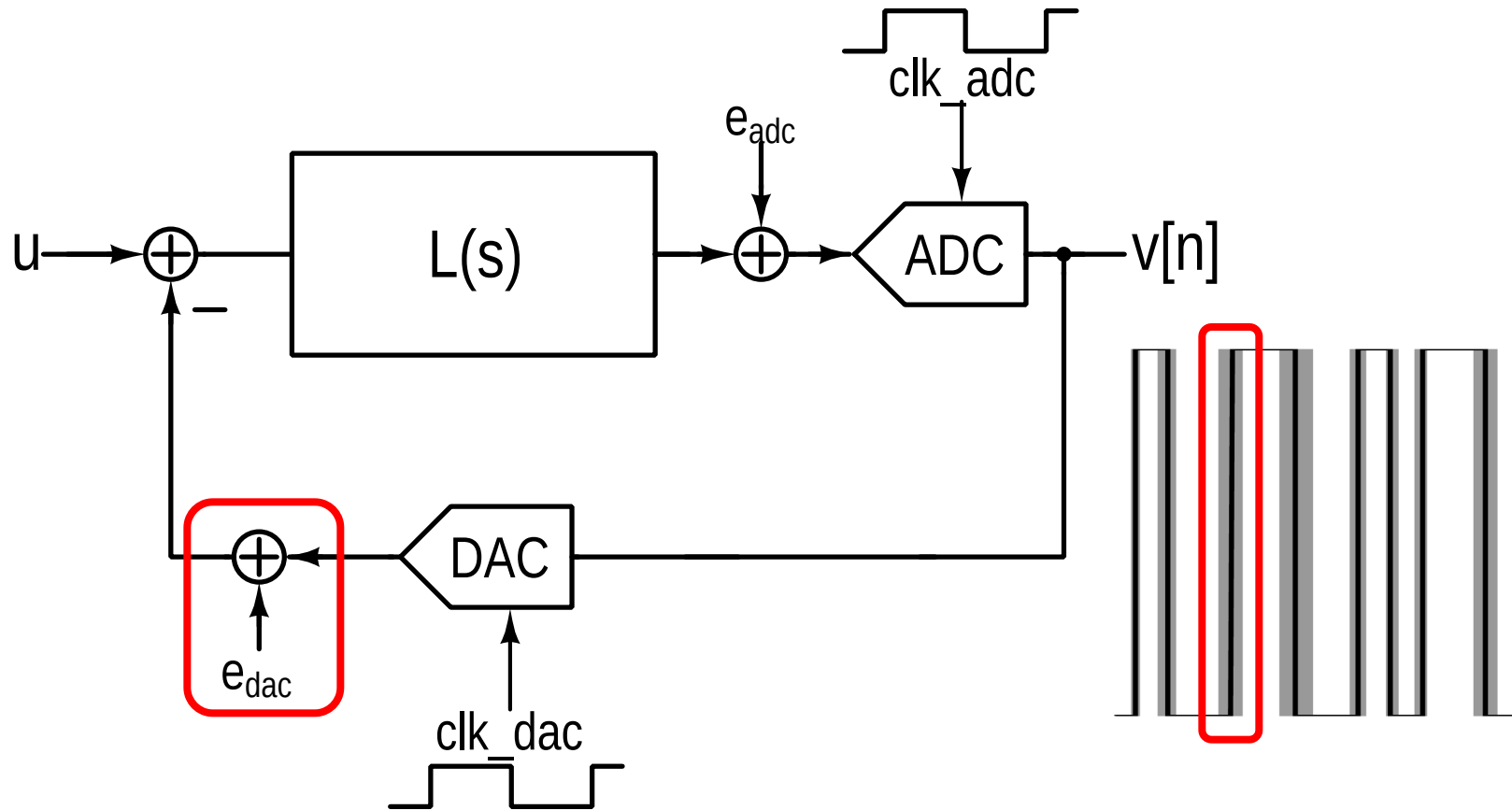


Large jitter error \rightarrow rail-to-rail feedback waveform

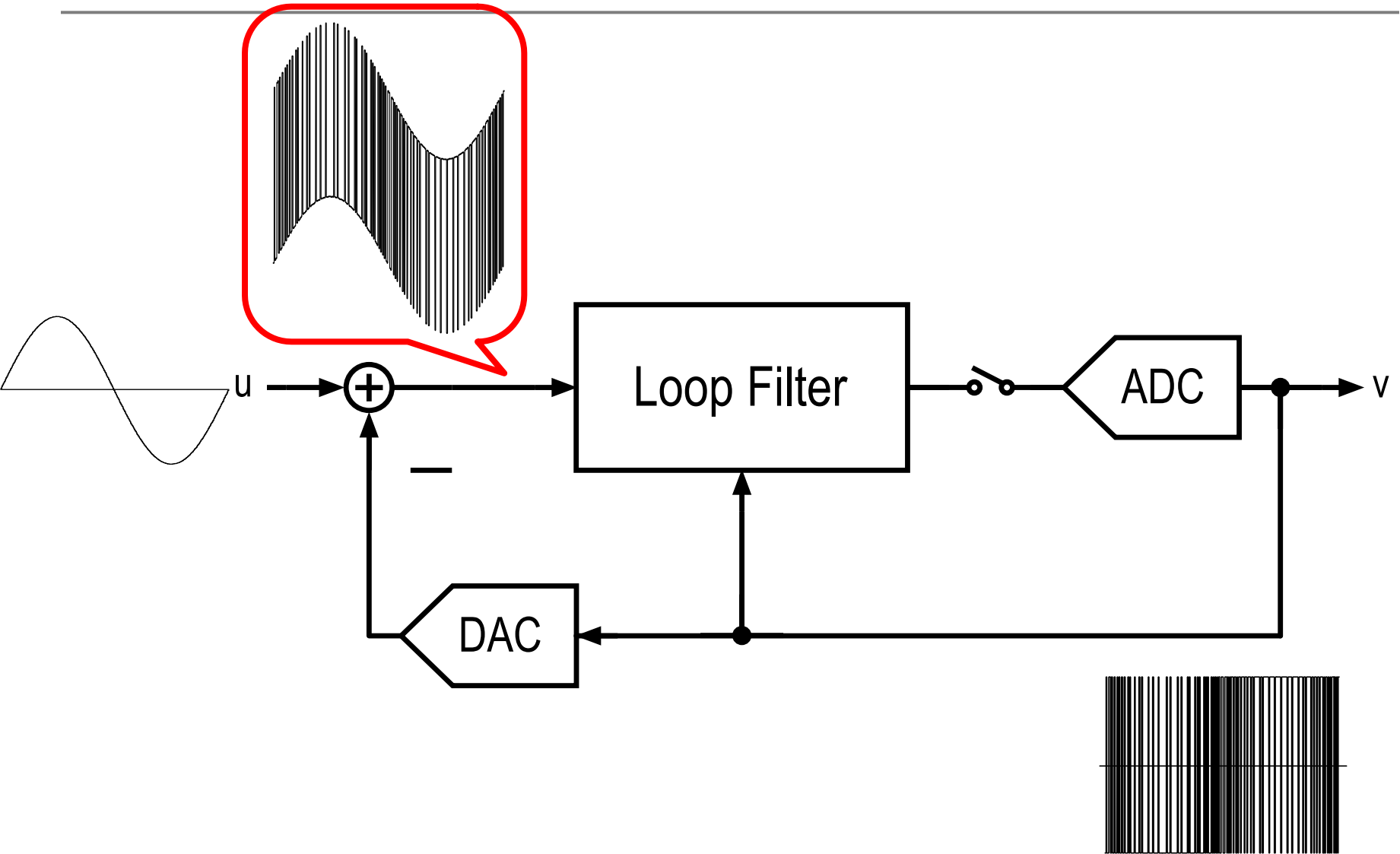Single-bit CTDSM Issues : Filter Linearity



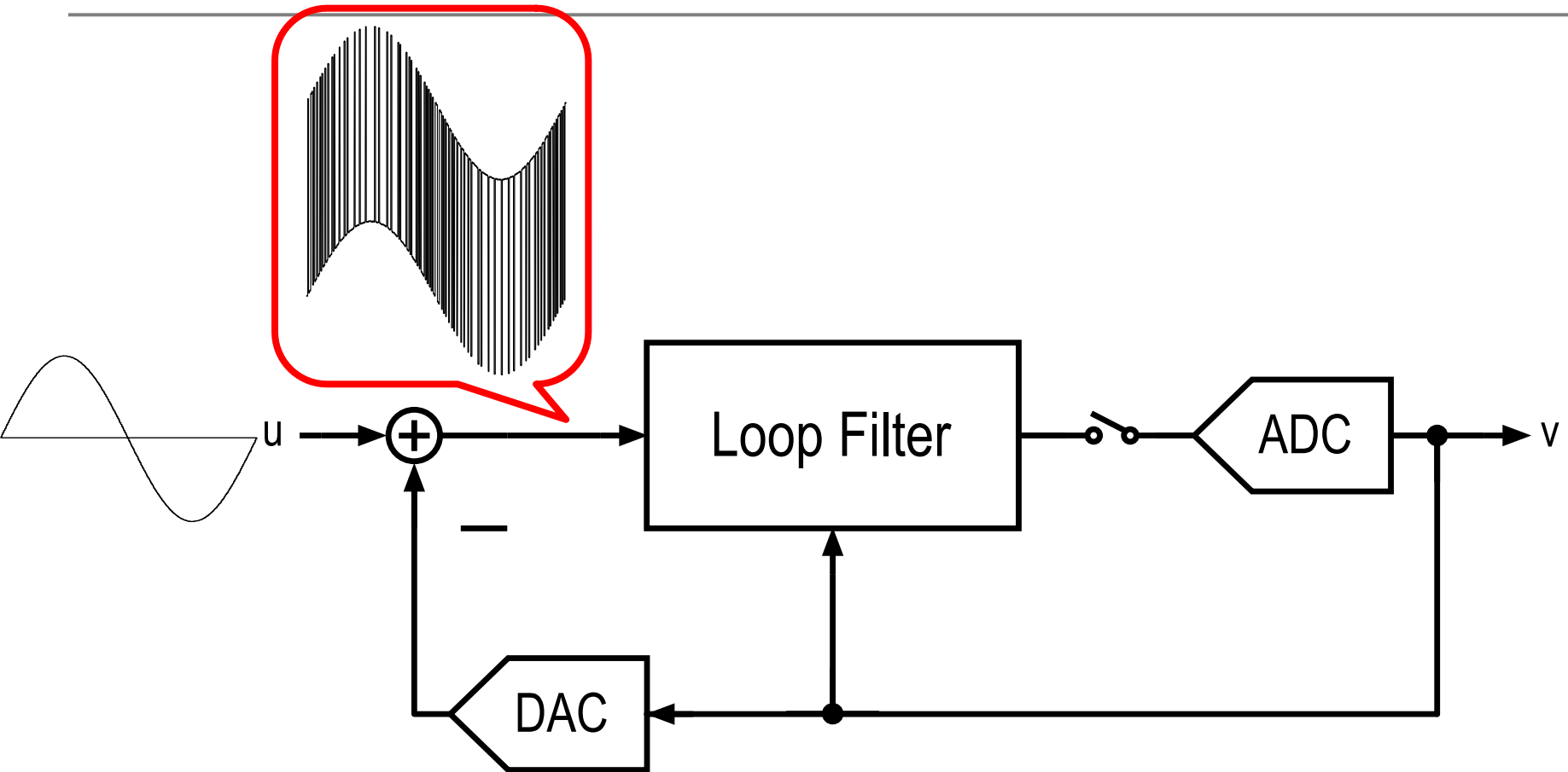Single-bit CTDSM Issues : Filter Linearity




Increased loop filter power dissipation needed to achieve linearity

Summary so far ...


- Single bit operation
 - Very efficient quantizer
 - Easy to drive
 - Sensitive to clock jitter
 - Loop filter needs to handle large swings
 - Increased power dissipation

Improved Single-bit CTDSM : FIR Feedback

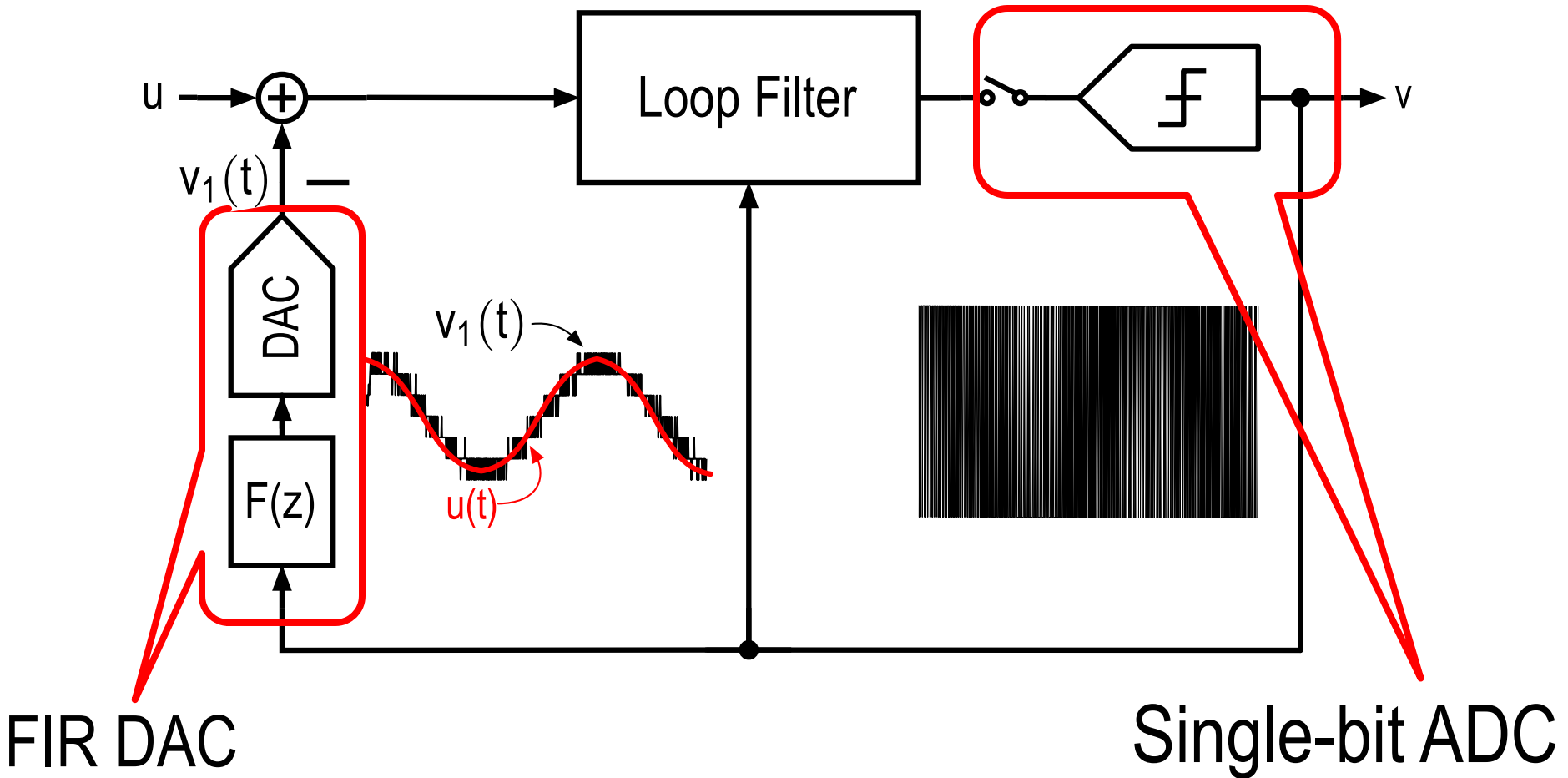


FIR filter in the feedback path

Improved 1-bit CTDSM : FIR Feedback

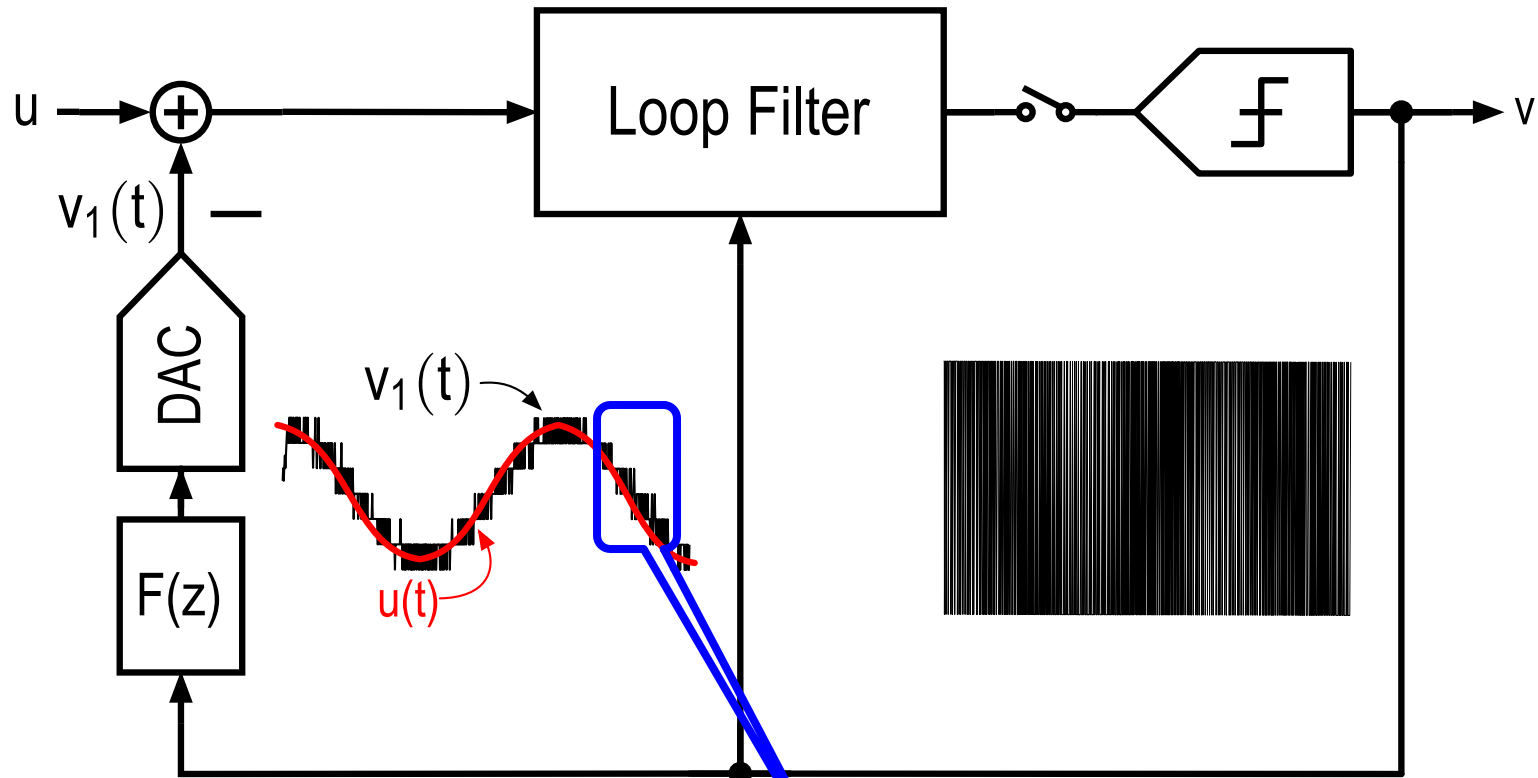


Height of steps \rightarrow Greatly reduced
 \rightarrow Reduced jitter sensitivity

Improved 1-bit CTDSM : FIR Feedback

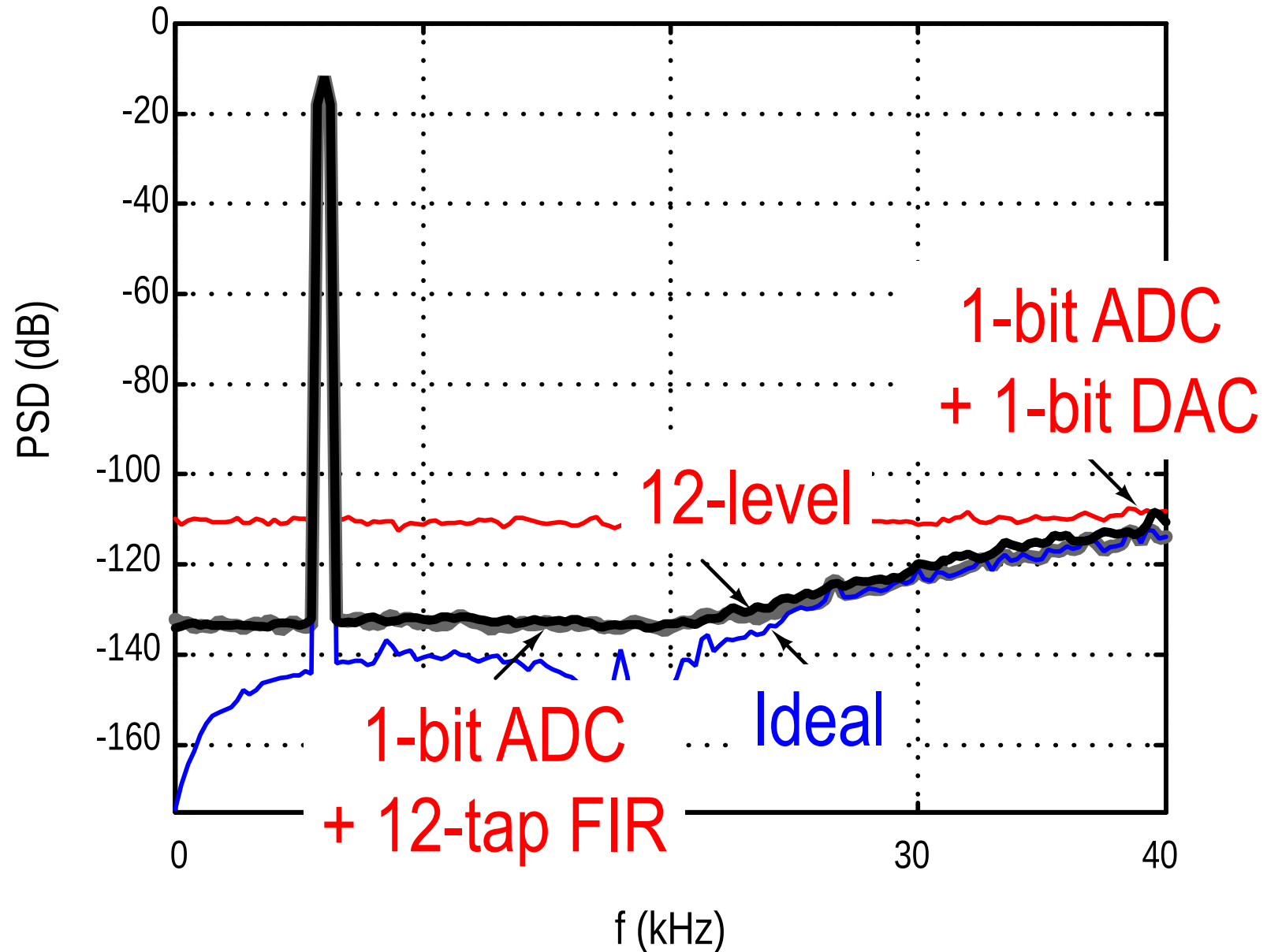


FIR DAC and Element Mismatch

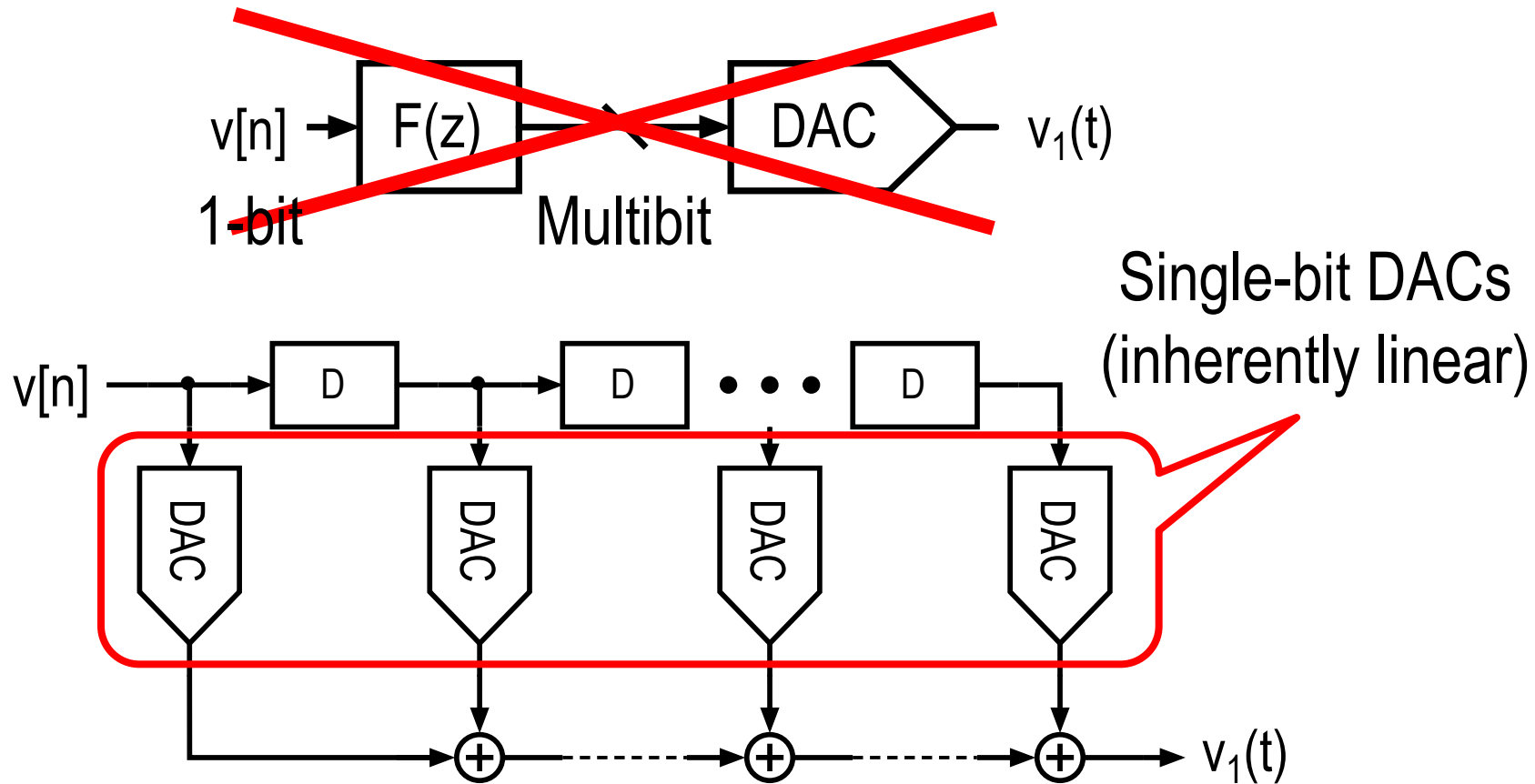

Semi-digital Implementation

Mismatch does not lead to non-linearity

Improved 1-bit CTDSM : FIR Feedback

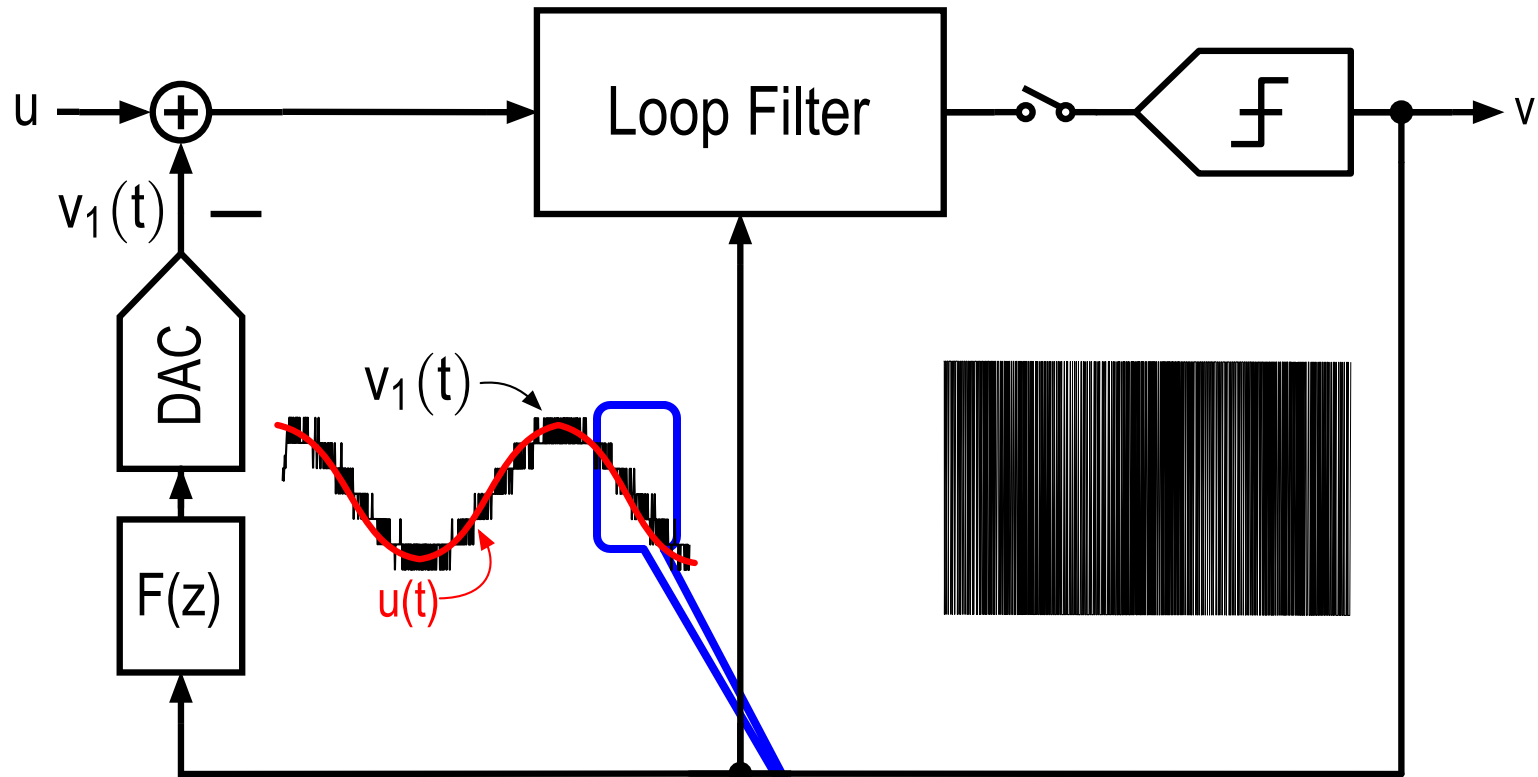

$u(t) - v_1(t) \rightarrow$ very small
 \rightarrow Improved loop filter linearity

Summary so far ...

- Single bit ADC + FIR DAC
 - Low power ADC, easy to drive
 - Inherently linear DAC, no DEM
 - Low jitter sensitivity
 - Improved loop filter linearity

~~Benefits of single-bit operation~~

Key Takeaway

Multi Bit DSM


- ✓ Tolerates jitter
- ✓ Low power loop filter

Single Bit DSM

- ✓ Low power ADC
- ✓ Inherently linear DAC

Single-bit ADC + FIR DAC combines benefits of 1-bit and multi-bit operation

Single-bit ADC + FIR DAC

 

(G)old Idea :


B.Putter, ISSCC 2003; O.Oliaei, TCAS-II 2003

- but dormant for a long while – why?
 - (?) Multibit & DEM well established by 2003
 - (?) More difficult to understand
 - (?) Stability


FIR DAC Summary

- Low power loop ADC
- Simple DAC – no DEM
- Multilevel feedback waveform
 - Improved loop filter linearity
 - Reduced clock jitter sensitivity
- Performance benefits of a multibit quantizer
 - But with low power

FIR DAC : Number of taps

 


 What prevents us from using a large number of taps
? (say 1000)




- More FIR taps \rightarrow Better filtering
- \rightarrow Reduced clock jitter sensitivity, better linearity


Increasing FIR Length

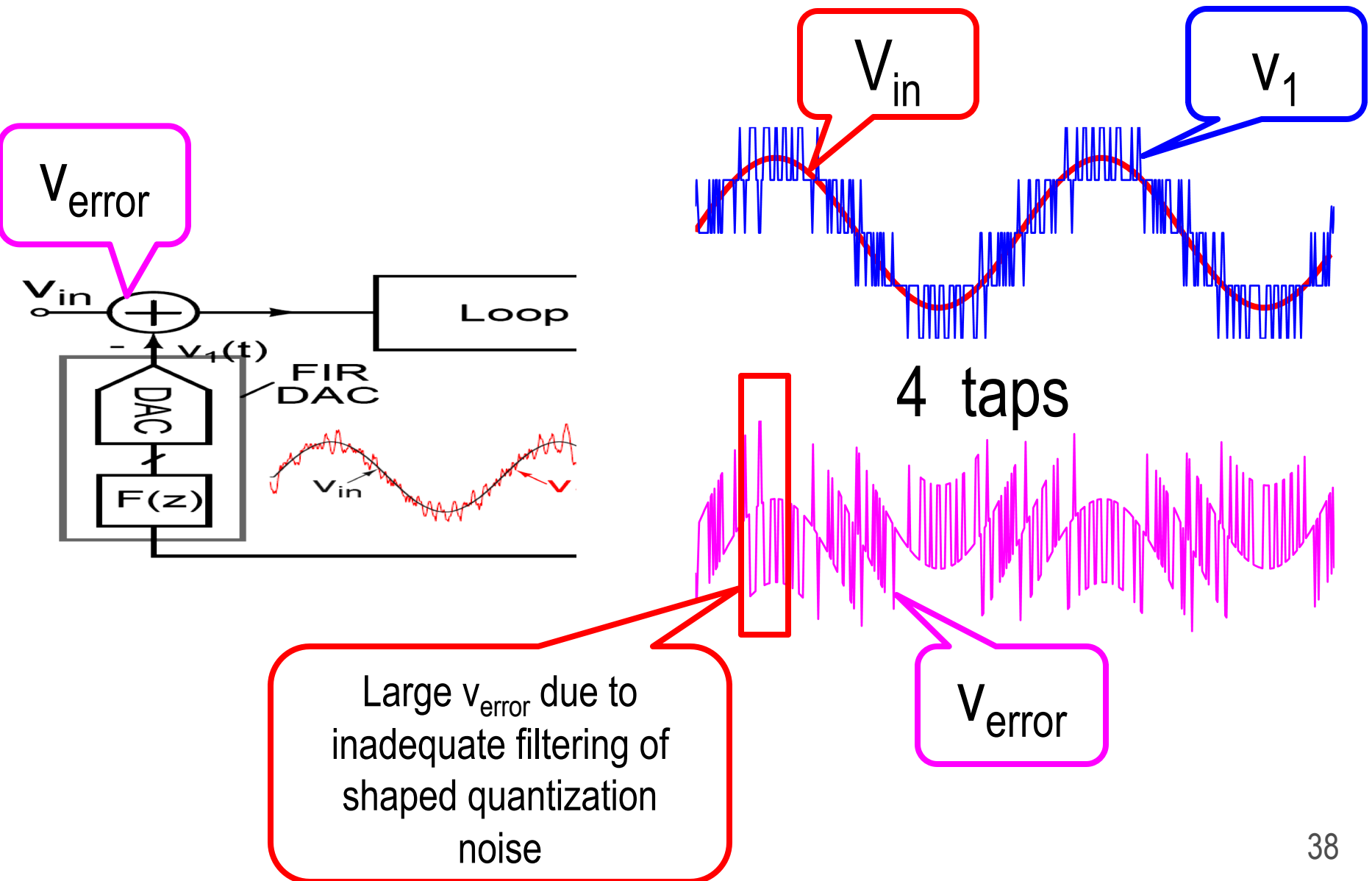


Increasing FIR Length

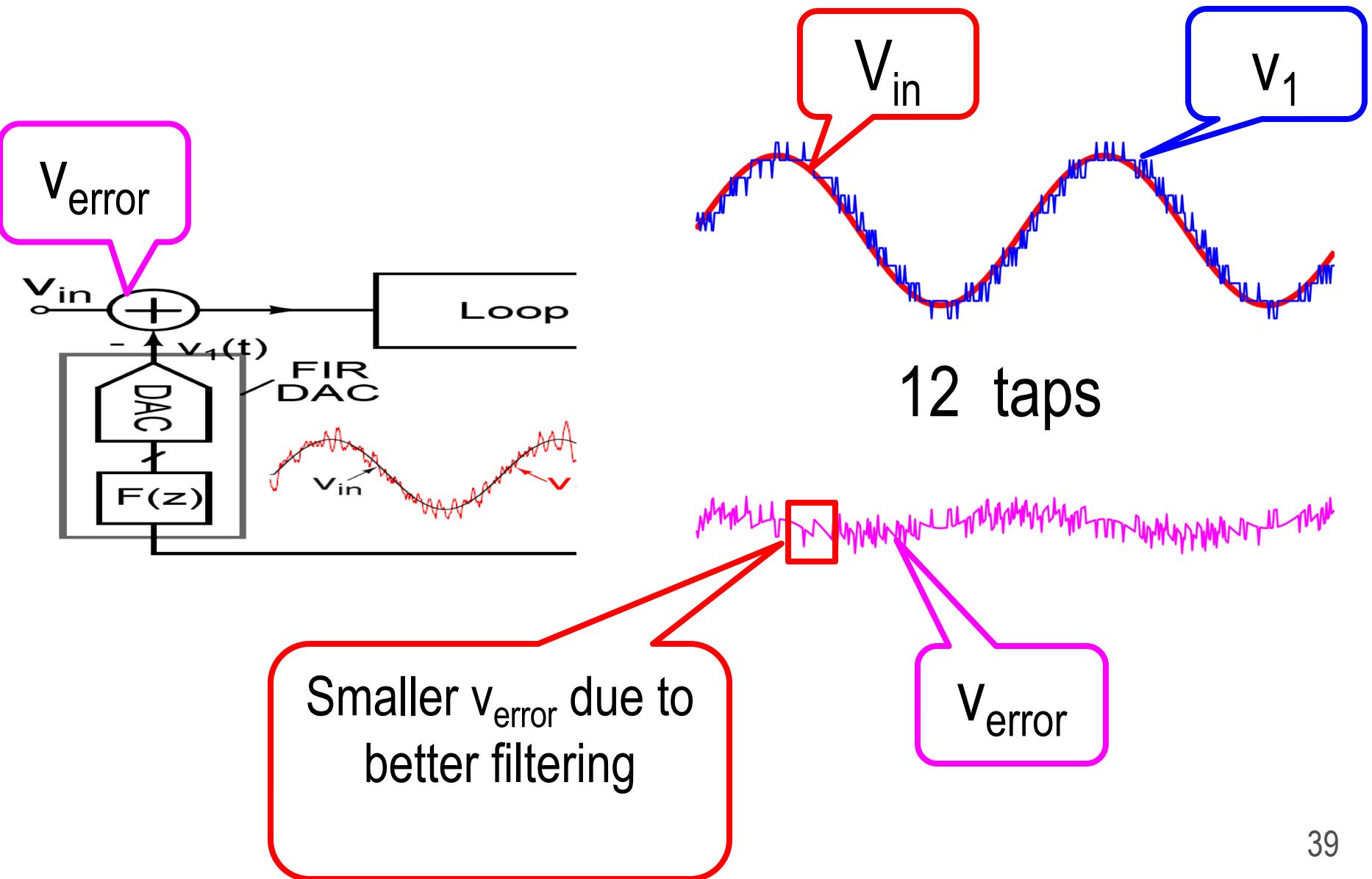


Increasing FIR Length

 

Error Signal Magnitude

 


Modulator Architecture

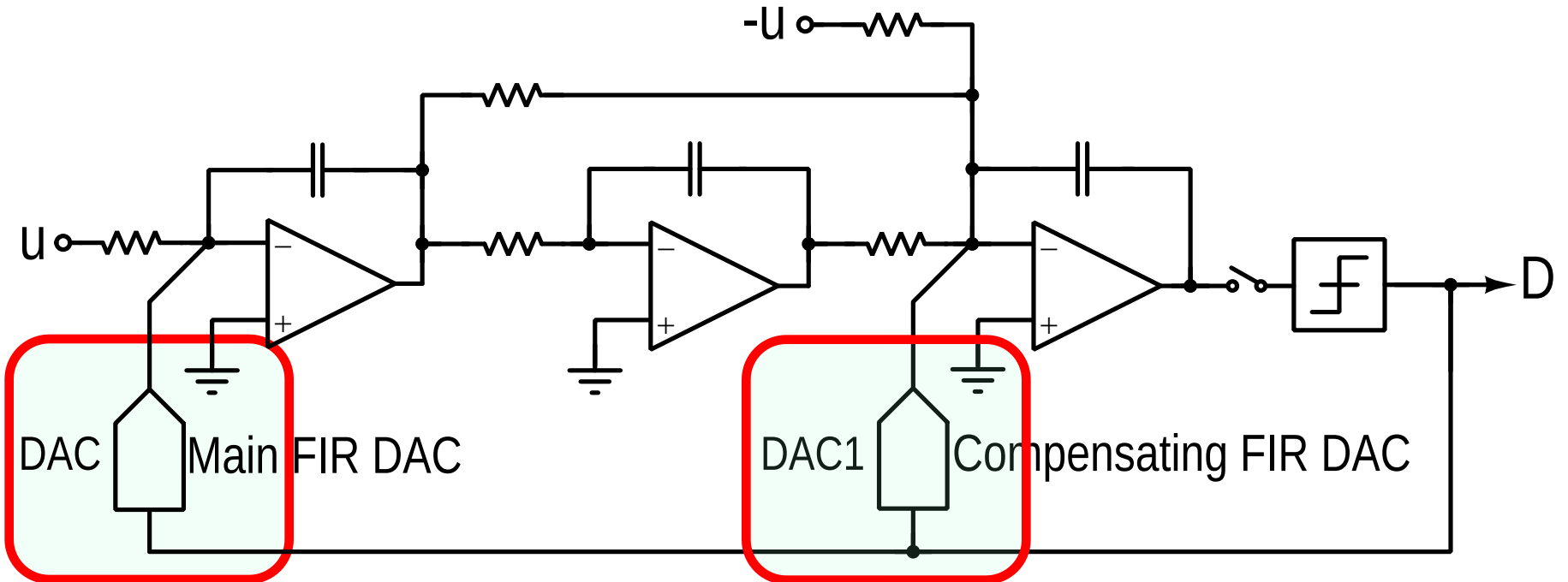


Third Order CIFF-B Prototype

FIR Feedback : More Benefits

1/f Noise in CTDSMs

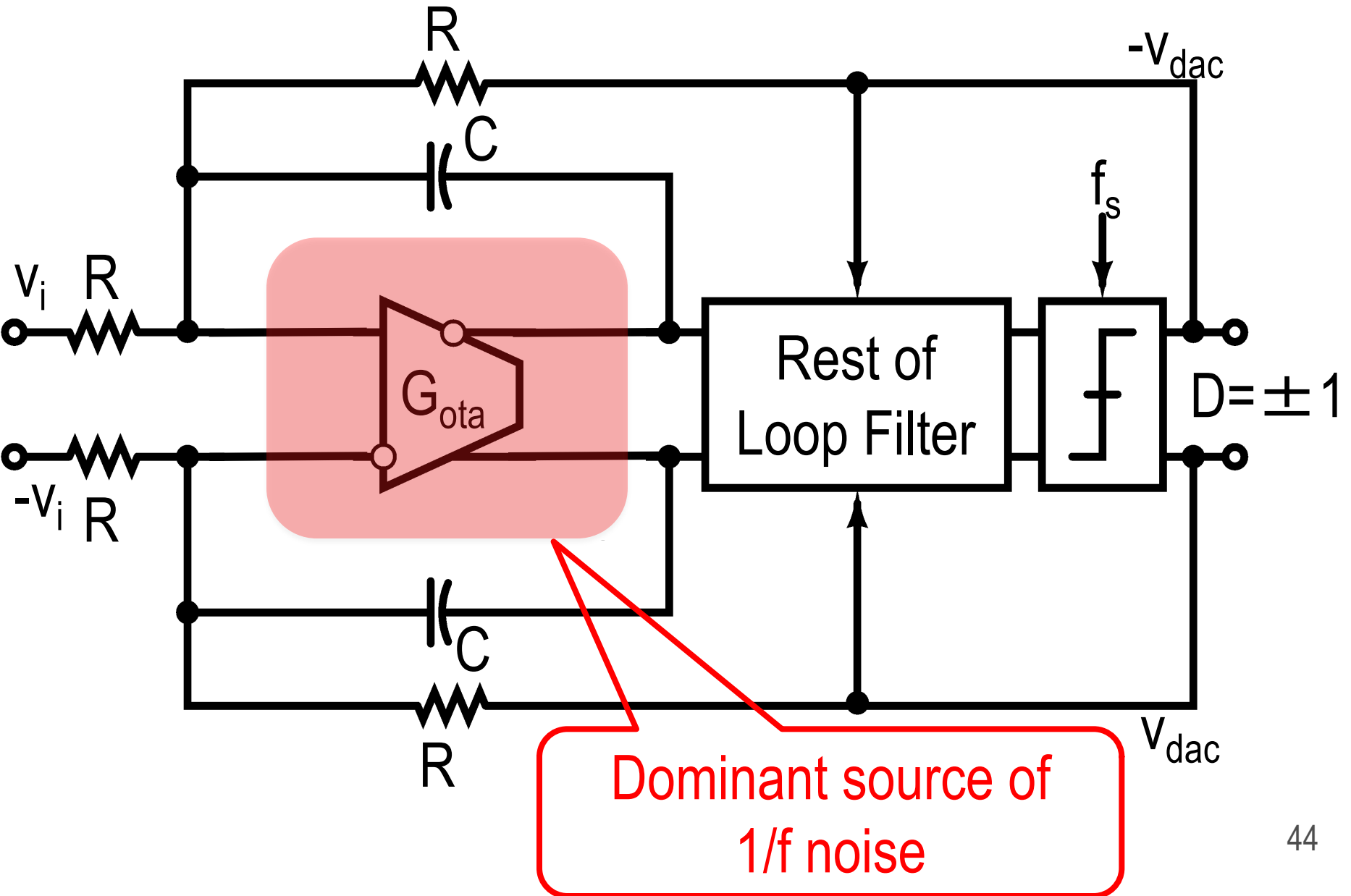


1/f Noise Mitigation in CTDSMs

 

Brute Force Solution

- Increase device sizes
- Increased parasitics
- Reduced loop gain
- Higher distortion
- Higher area

1/f Noise Mitigation in CTDSMs

 


Chopping


- Modulates 1/f noise out of the signal band

Chopping in CT $\Delta\Sigma$ -Modulators

Chopping in a CT $\Delta\Sigma$ M

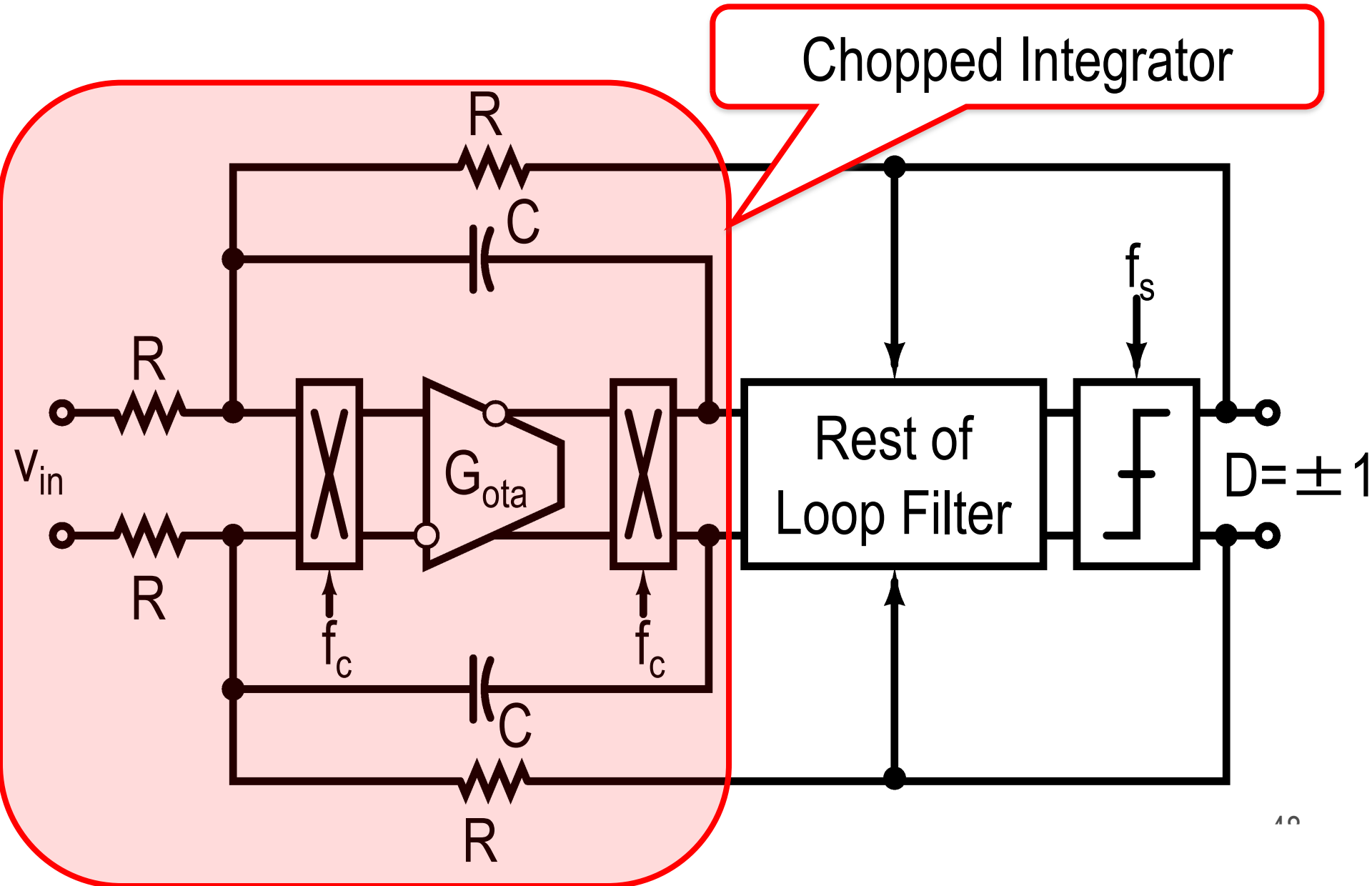

Chopping in a CT $\Delta\Sigma$ M

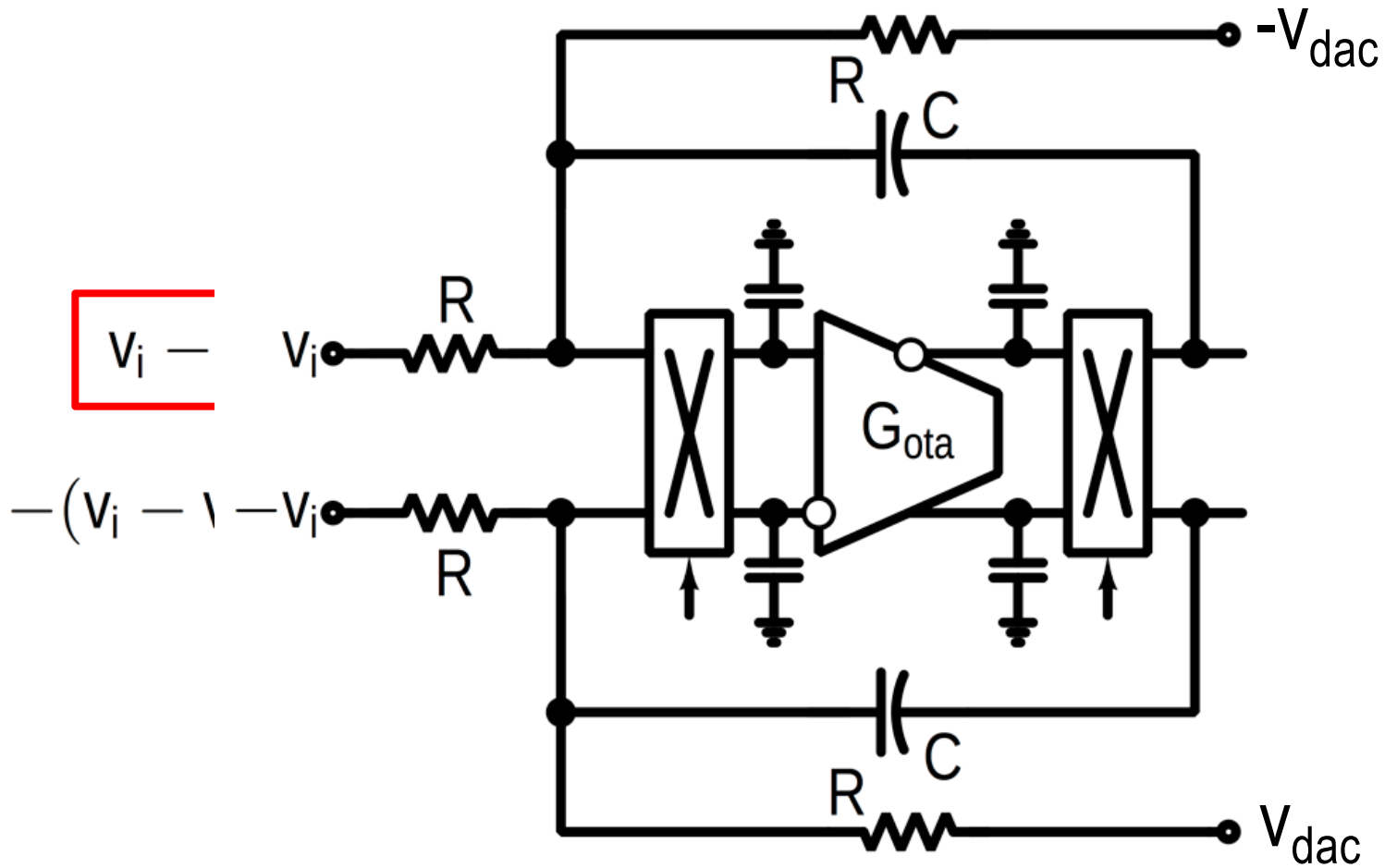

chop = 1

$t = t_1$

v_x

$$v_x(t) \approx \frac{v_d(t)}{RG_{ota}}$$

Chopping transition
at $t = t_1$

$t = t_1^-$

$v_x(t_1)$

v_x

V_d

$R/2$

C

C_i

C_o

G_{ota}

$-V_d$

$R/2$

$-v_x(t_1)$

$-v_x$


C

chop = 1

$t = t_1$


chop = -1
 
$$v_x(t) \approx \frac{v_d(t)}{RG_{ota}}$$




$t = t_1^-$

$t = t_1^+$

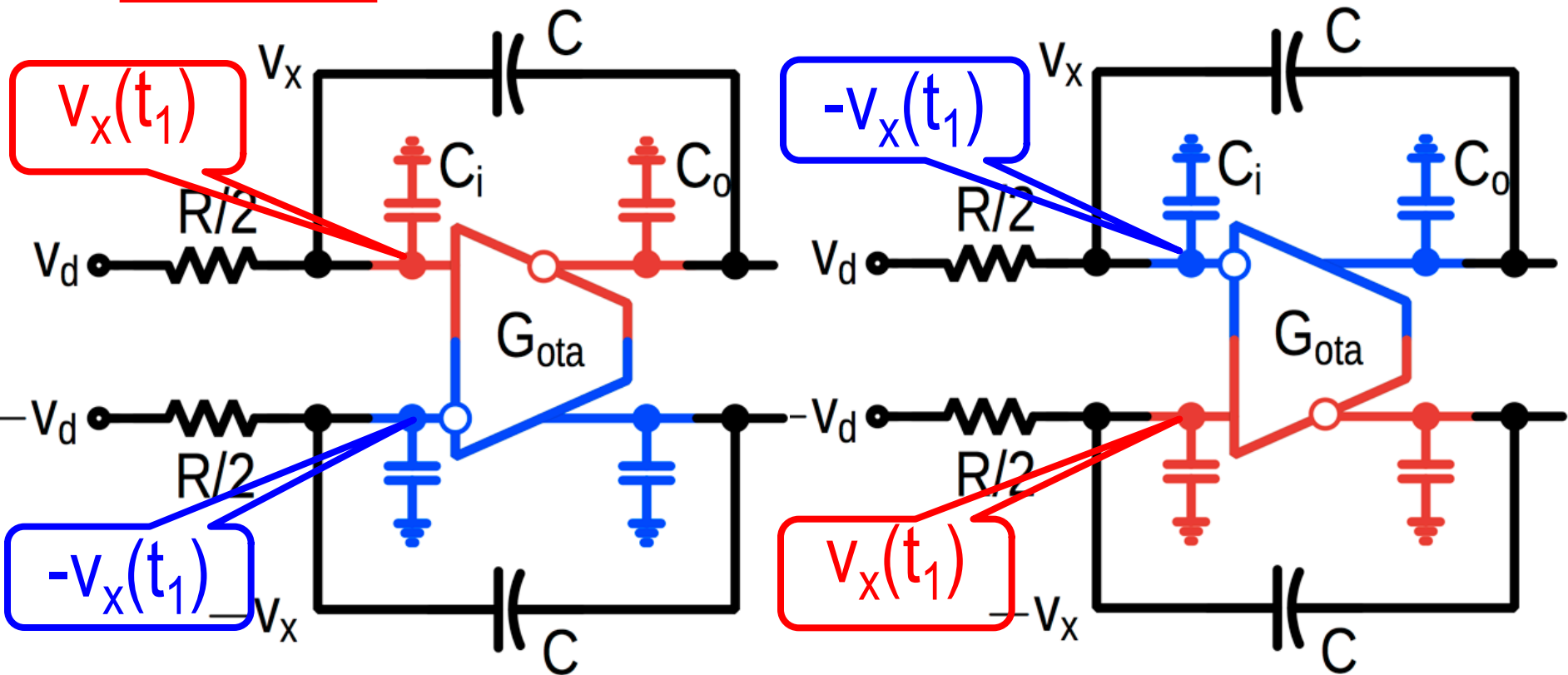

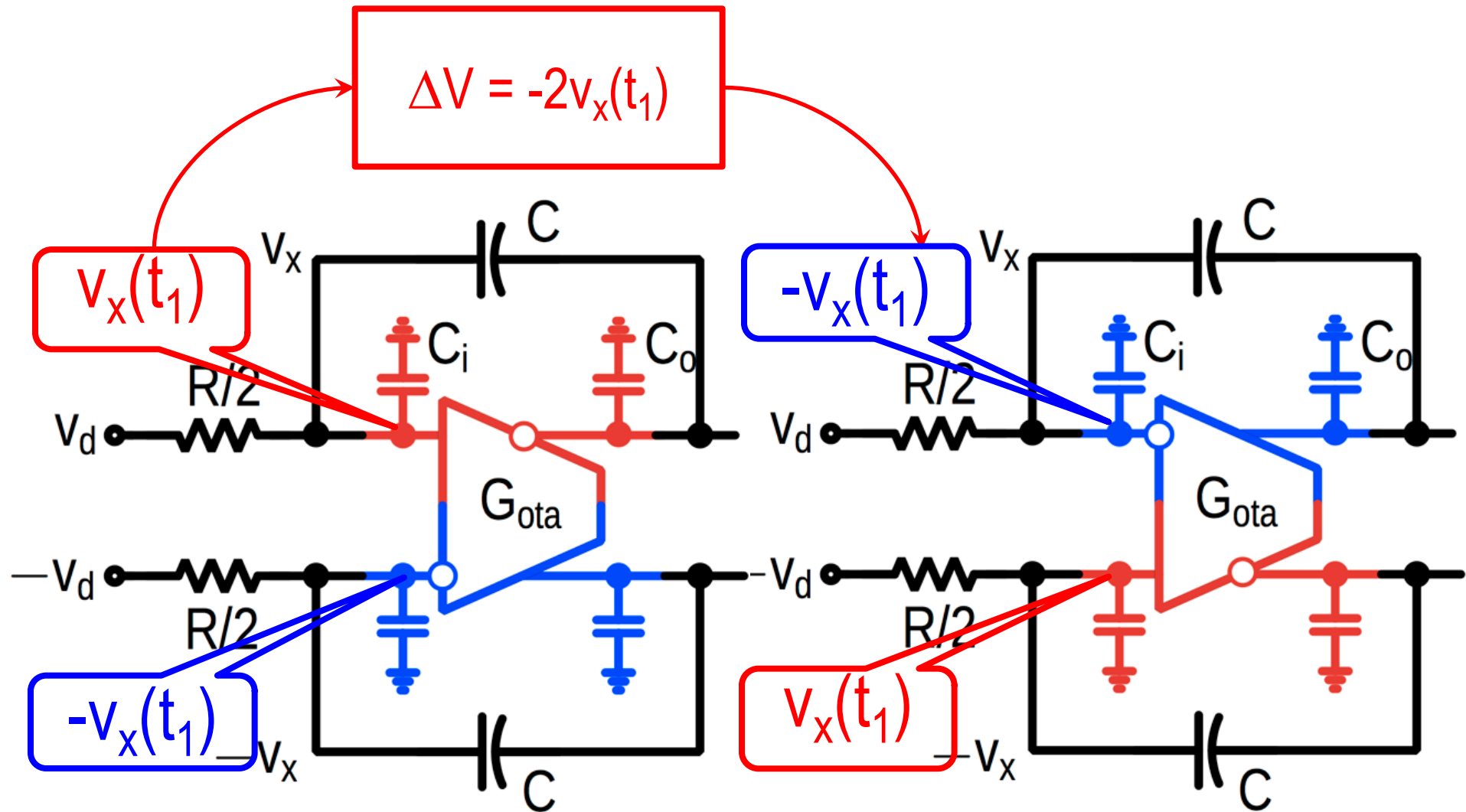At **EVERY** transition of the chopping clock




Error Model of a Chopped Integrator


$$i_x = -2C_i v_x(t_1) \delta(t - t_1)$$

OTA Input
Virtual
Ground
Voltage



Sampled at
chopping edge


$$V_x \approx \frac{V_d}{RG_{ota}}$$

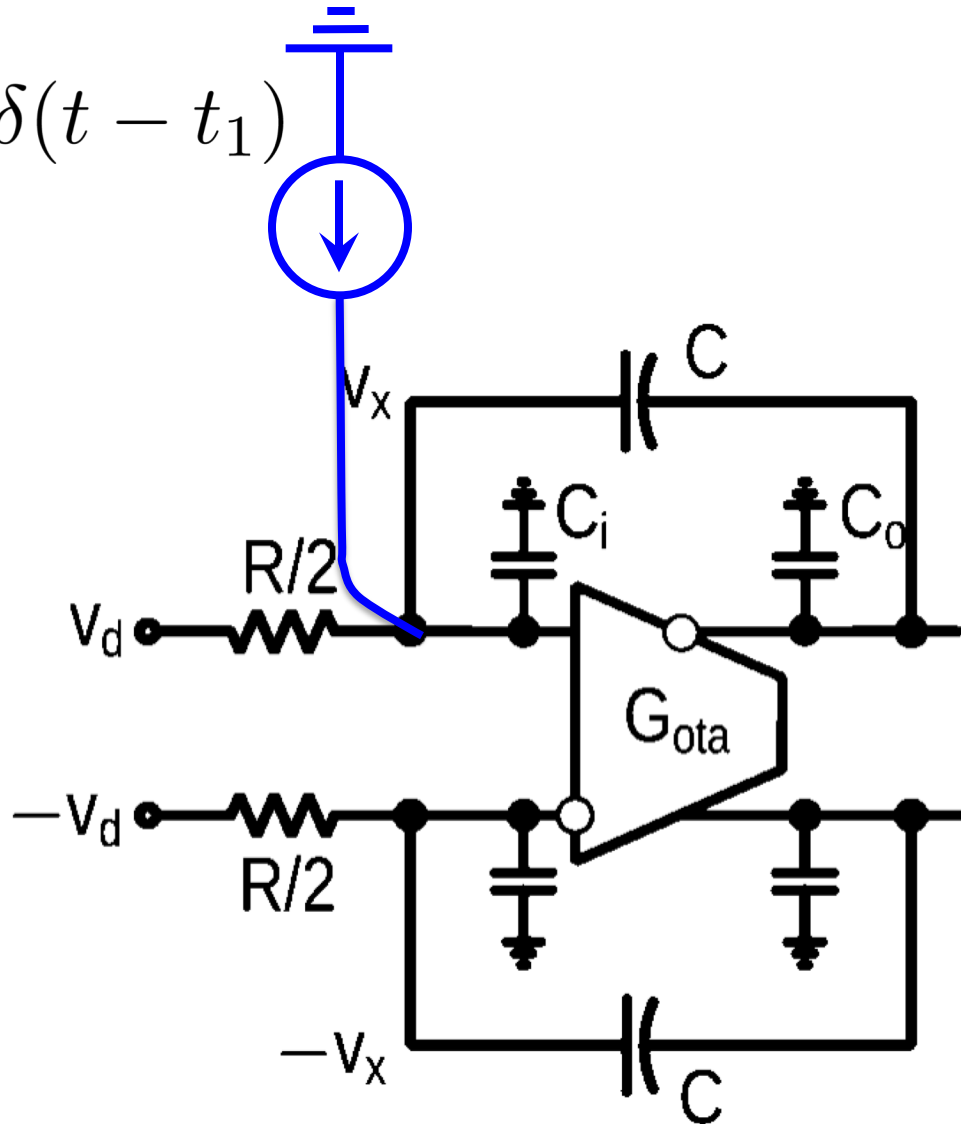

 

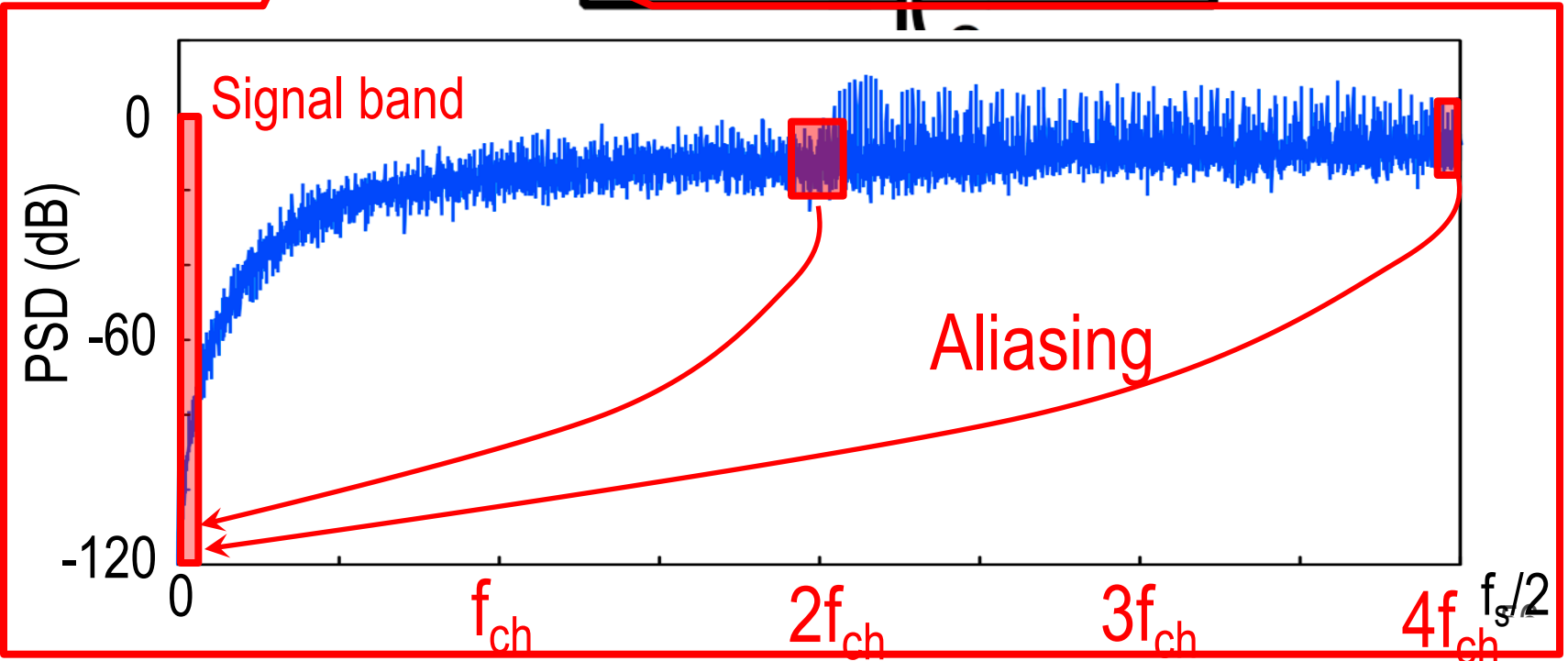 
Error current injected at **every edge** of f_{ch}
 → Sampling the virtual ground at $2f_{ch}$
 → Error proportional to C_i/RG_{ota}



 

Output parasitic switched at **every edge** of f_{ch}


Chopped C_o : Equivalent Resistor

 

Reduced Integrator DC Gain


Chopping in CTDSMs : Summary

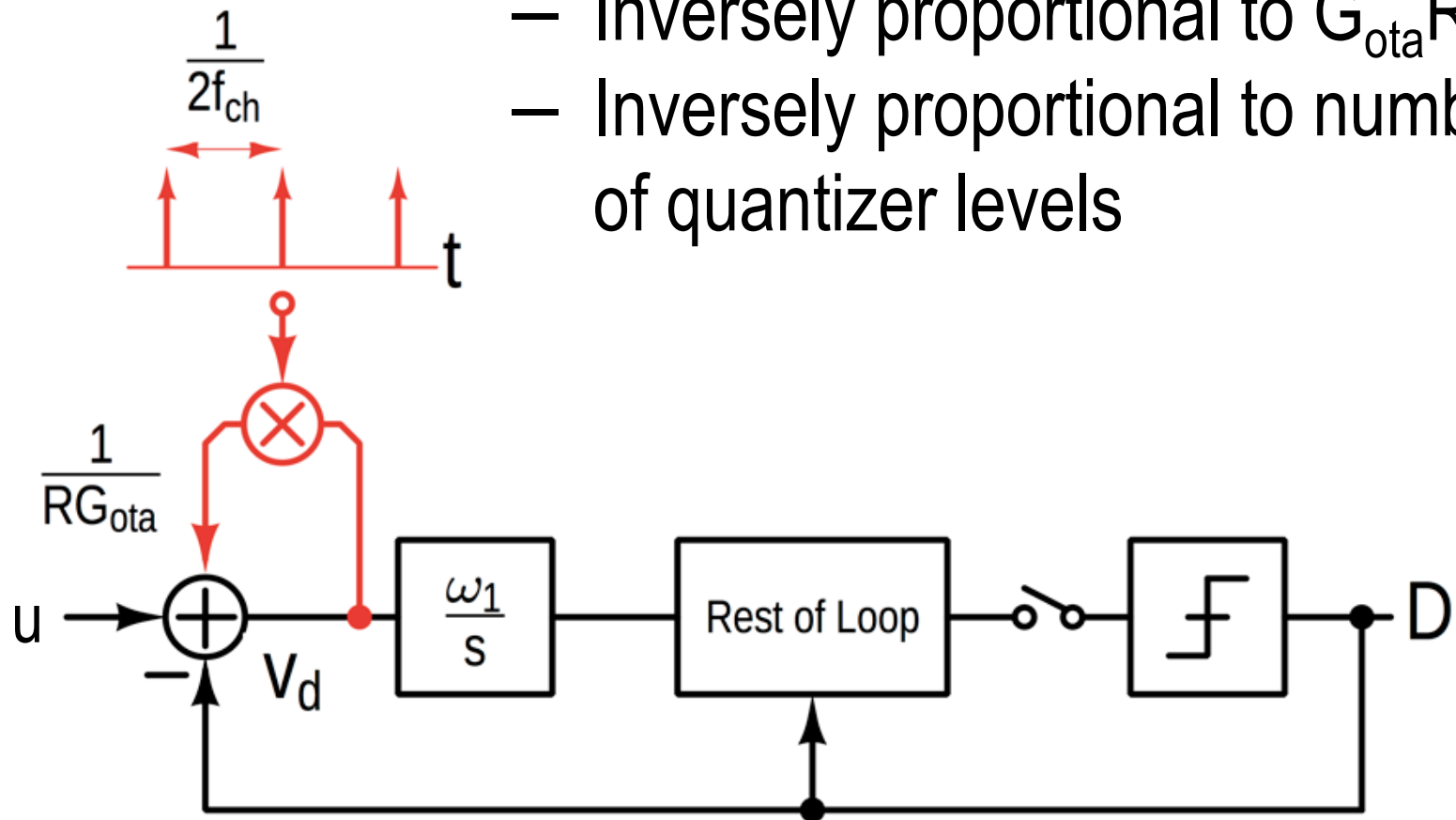- Aliases shaped noise from multiples of $2f_{ch}$
 - Inversely proportional to $G_{ota}R$
 - Inversely proportional to number of quantizer levels



Chopping in CTDSMs : Summary

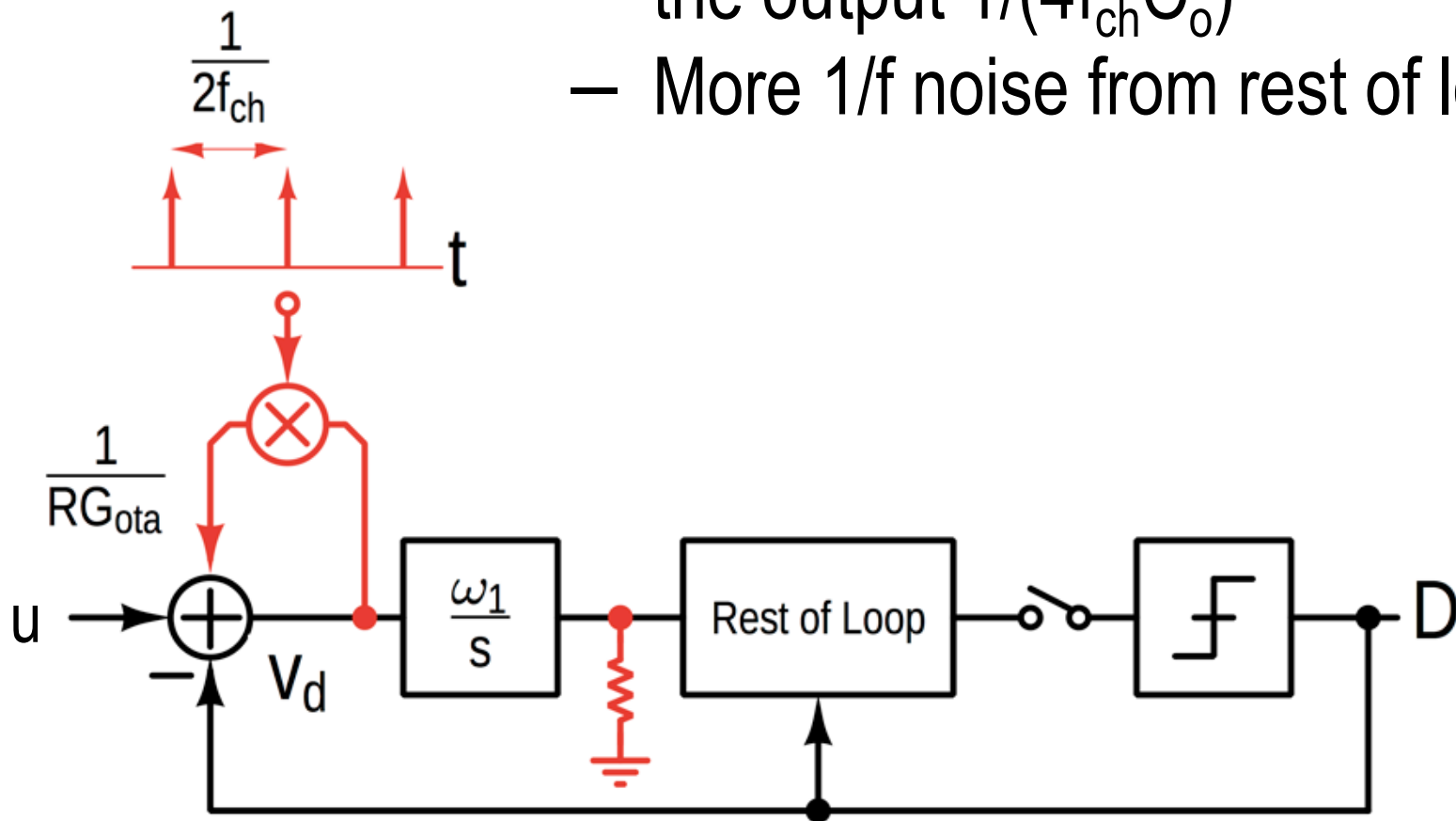- Reduced integrator gain
 - Switched capacitor resistor at the output $1/(4f_{ch} C_o)$
 - More $1/f$ noise from rest of loop



Chopping in CTDSMs : Summary

Solutions


Increase $G_{ota}R$

X 20dB reduction of alias noise dissipates
10x power


Increase number of quantizer levels

X 20dB reduction of alias noise needs 10x the
number of levels

FIR Feedback DAC

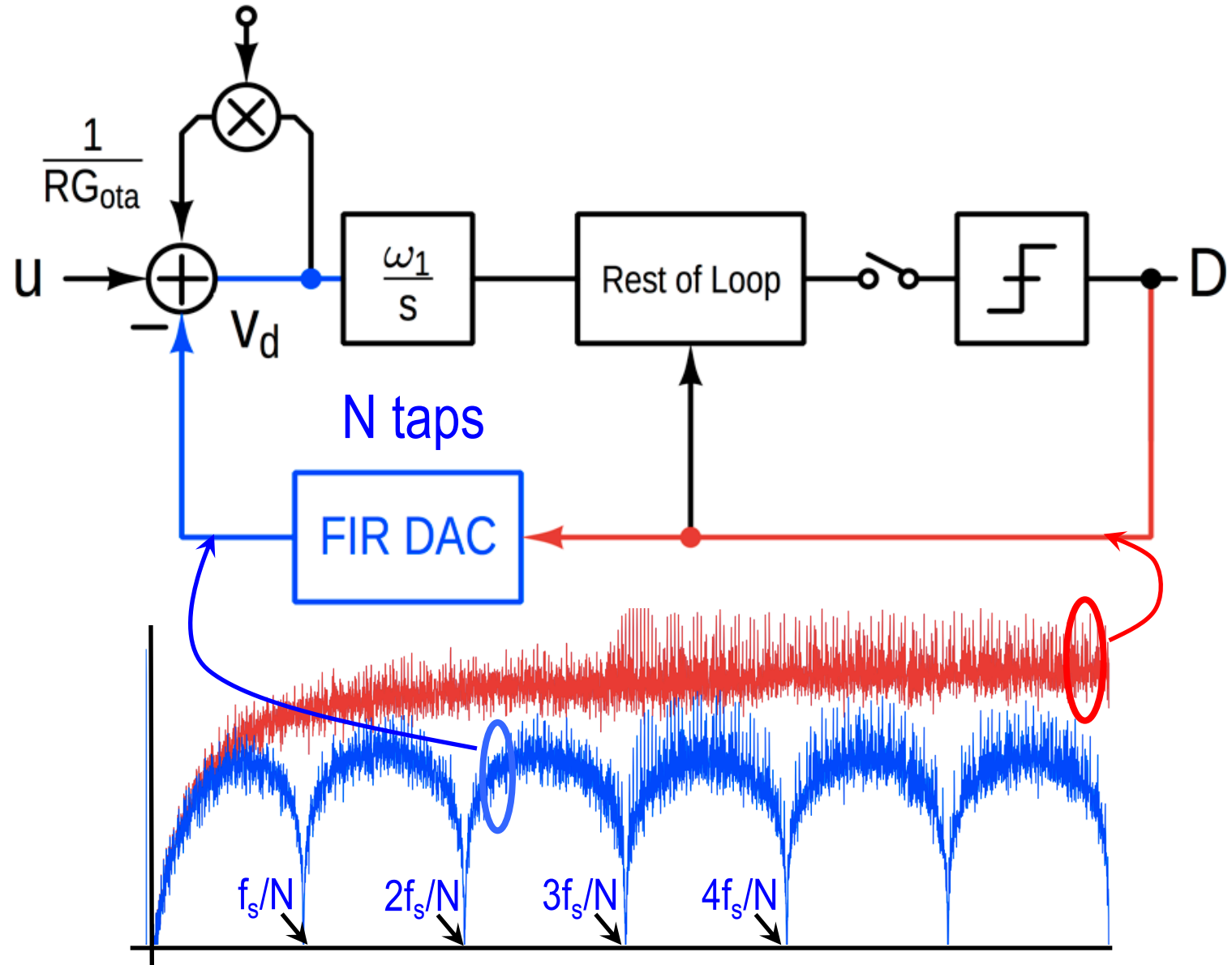


1-bit quantizer & FIR Feedback : Summary

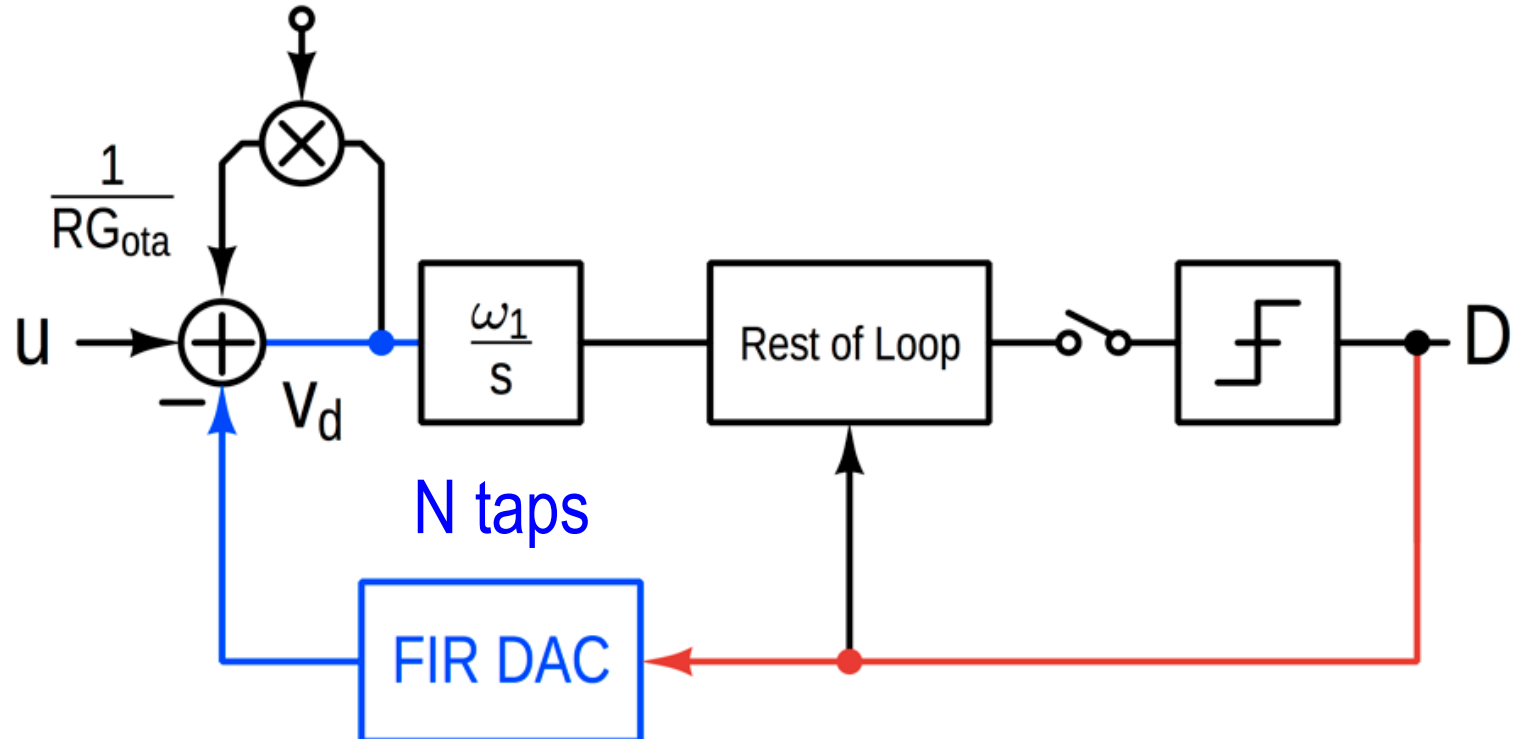


- ✓ Reduced jitter sensitivity
- ✓ Improved integrator linearity
- ✓ Reduced chopping artifacts
- ✓ Inherently linear DAC

Architecture and Circuit Design

3rd Order CTDSM Architecture



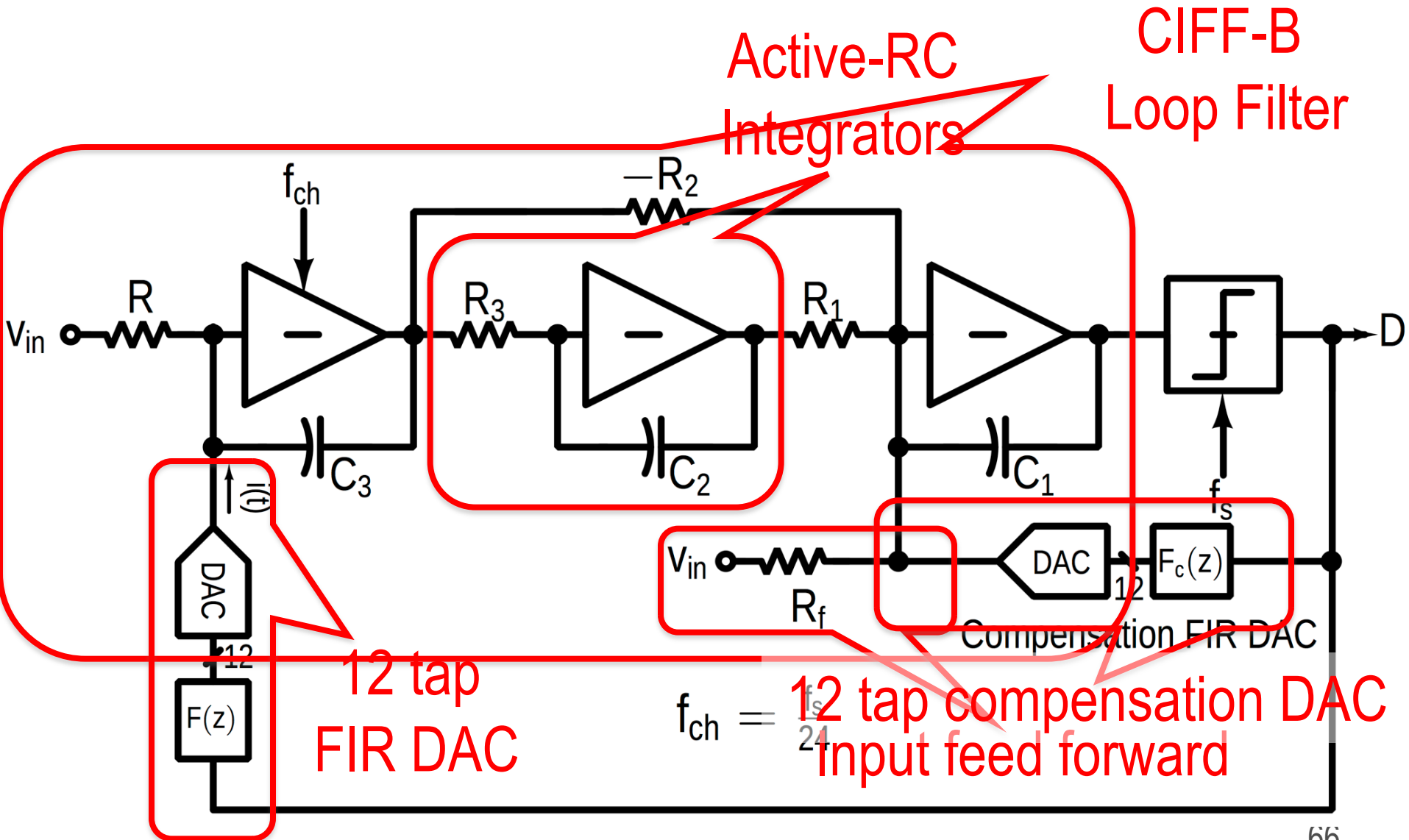


3rd Order CTDSM Architecture

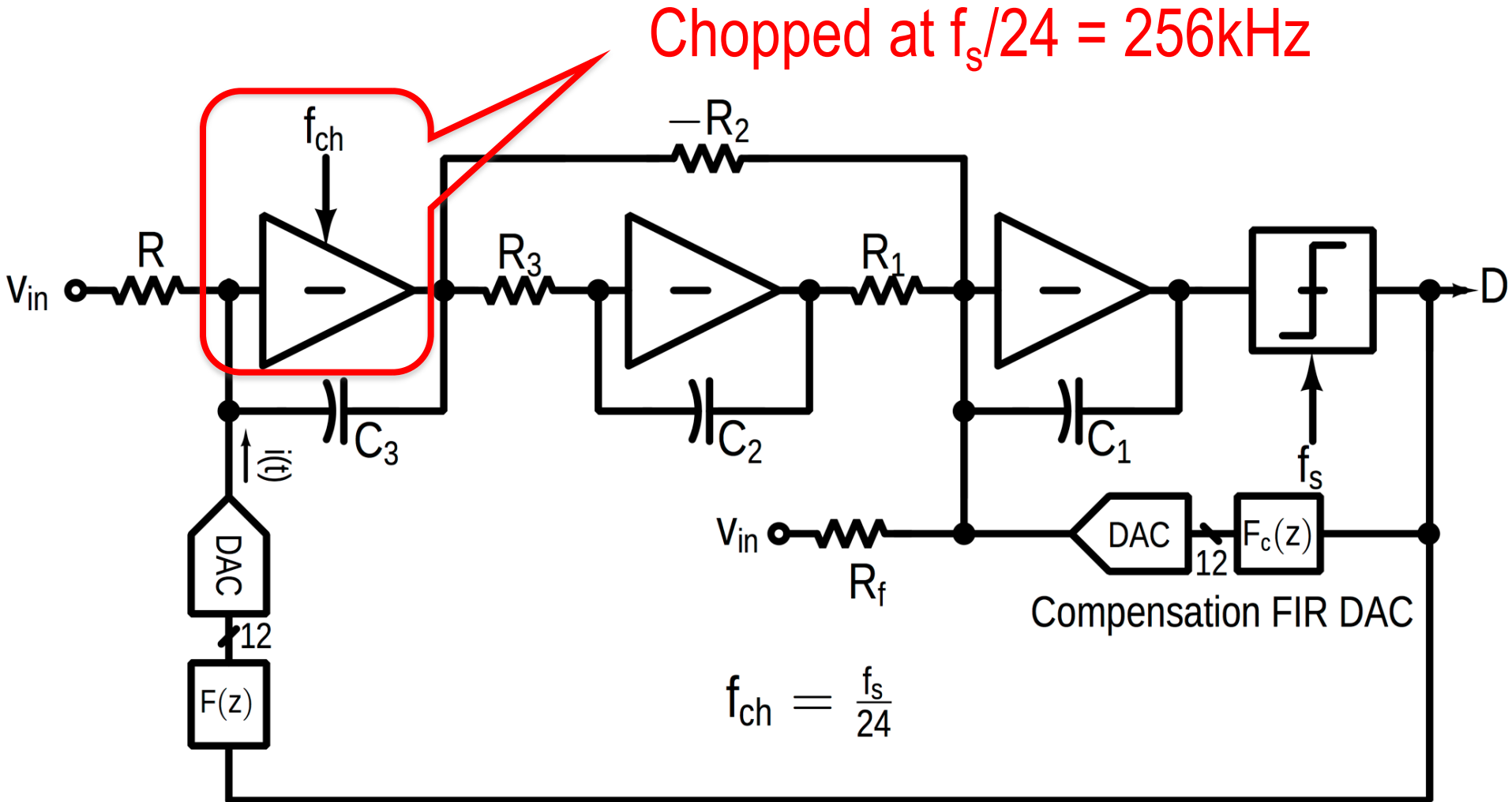


3rd Order CTDSM Architecture

Semidigital Implementation

   


Worst case attenuation > 35dB

Monte Carlo : 1% random tap mismatch

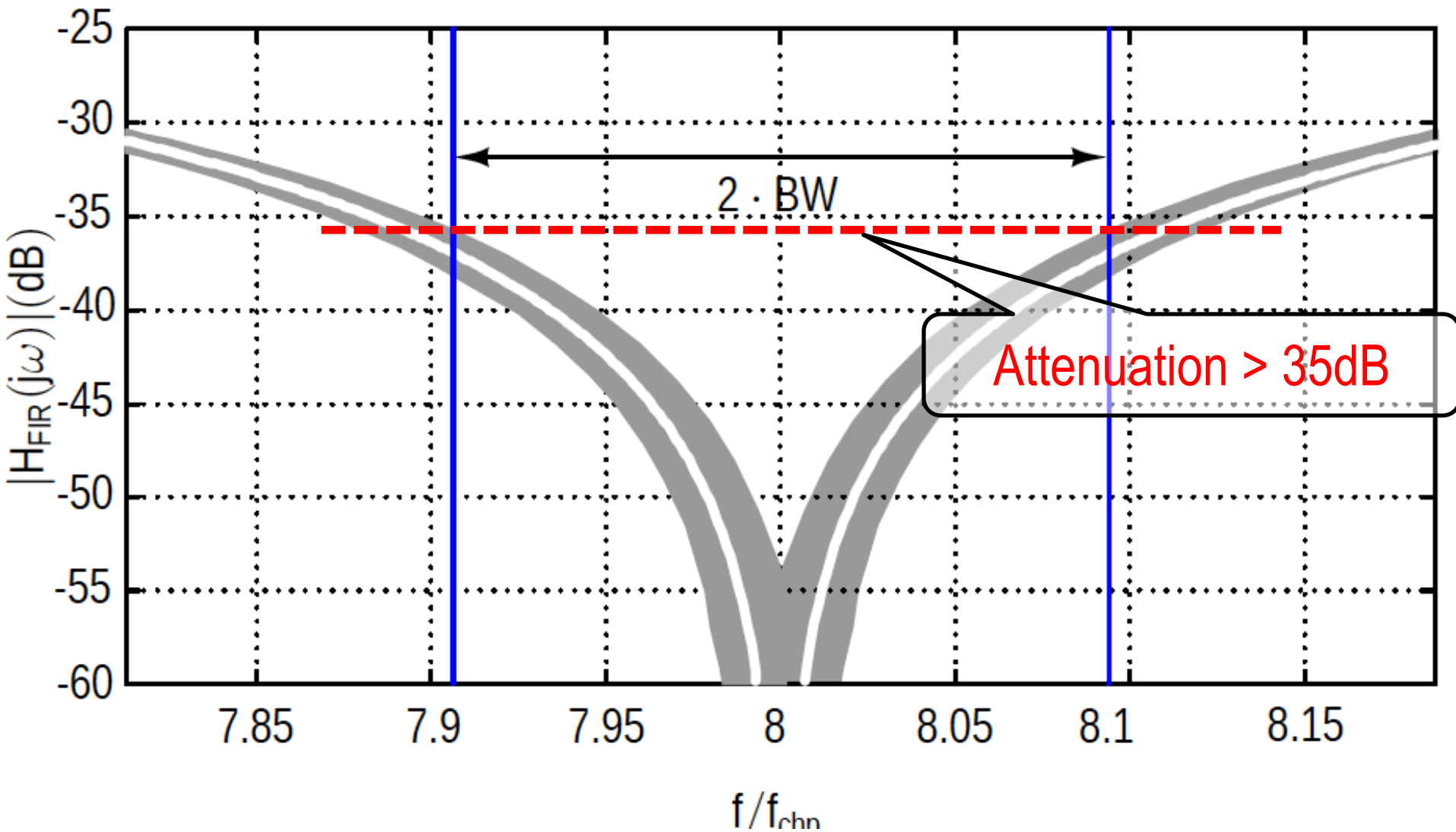


OTA Design

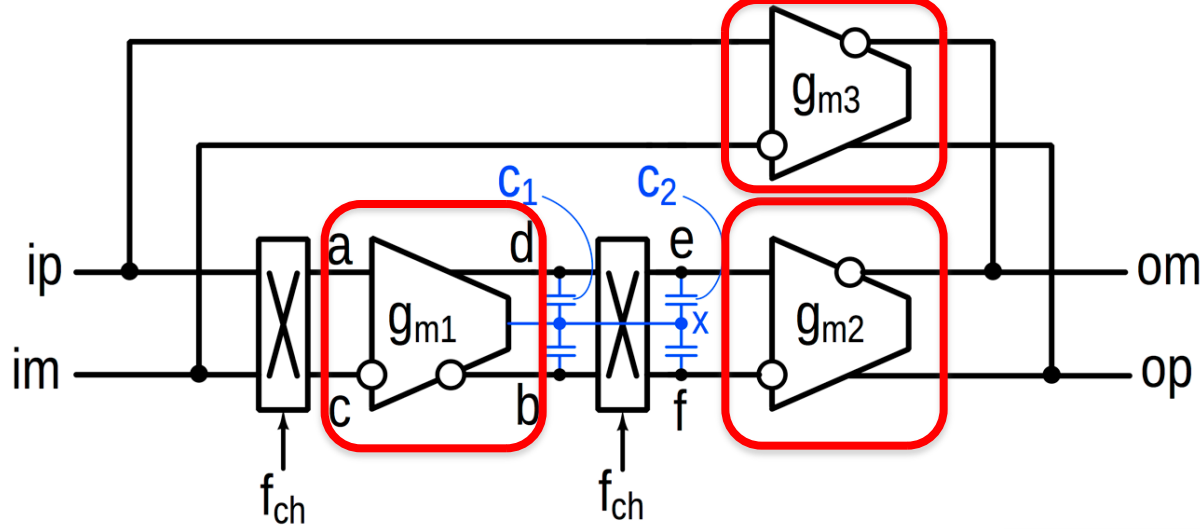



2 Stage
Feedforward
Compensated
OTA

2nd Stage

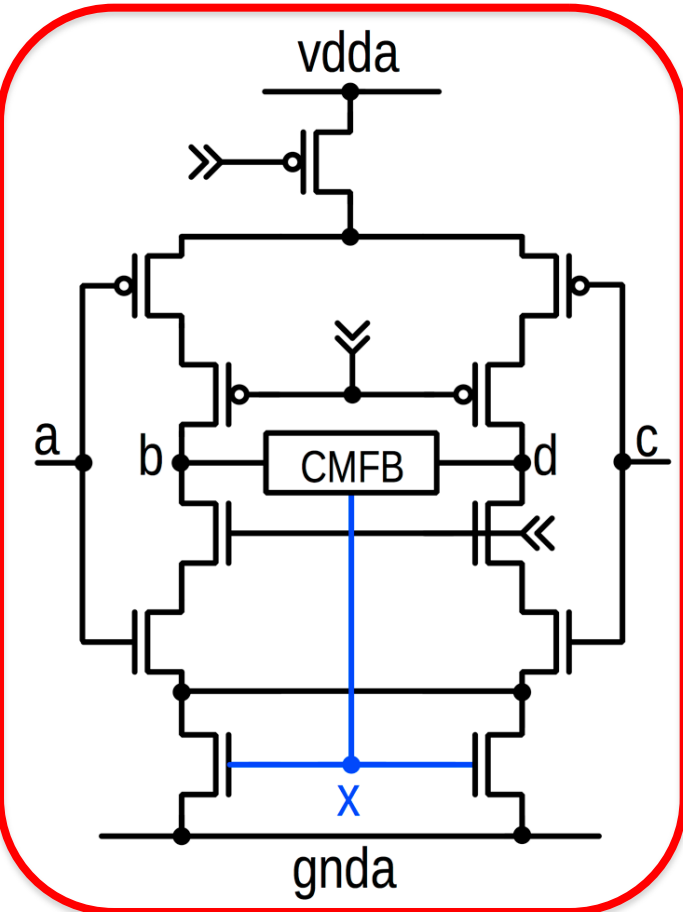

 NMOS/PMOS input pair
→ 2x g_m for the same current
Cascode
→ High DC gain
Feedforward




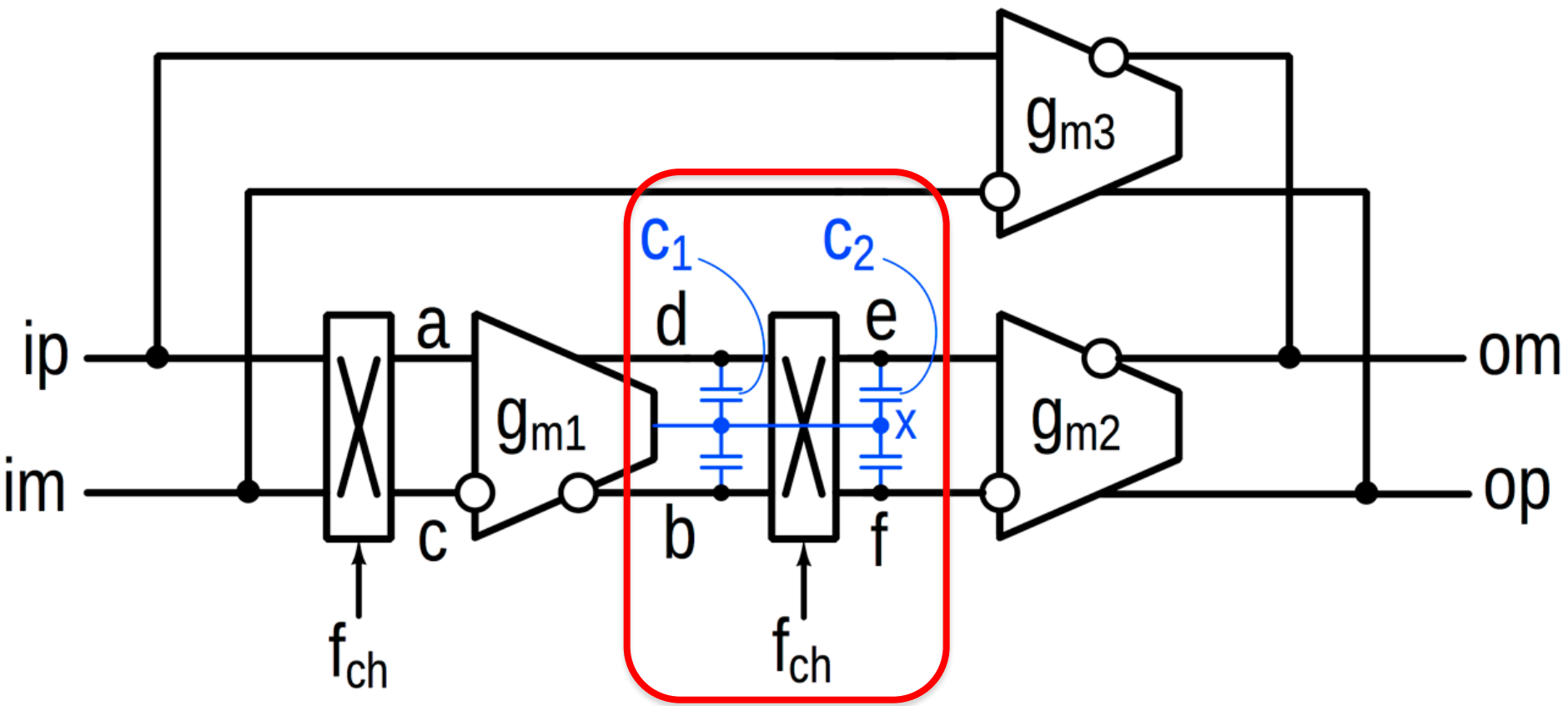

CMFB compensation capacitors
 Small fraction (c_1) inside chopper
 → Compensation during chop transitions


Measurement Results

Die Photo & Layout Snapshot

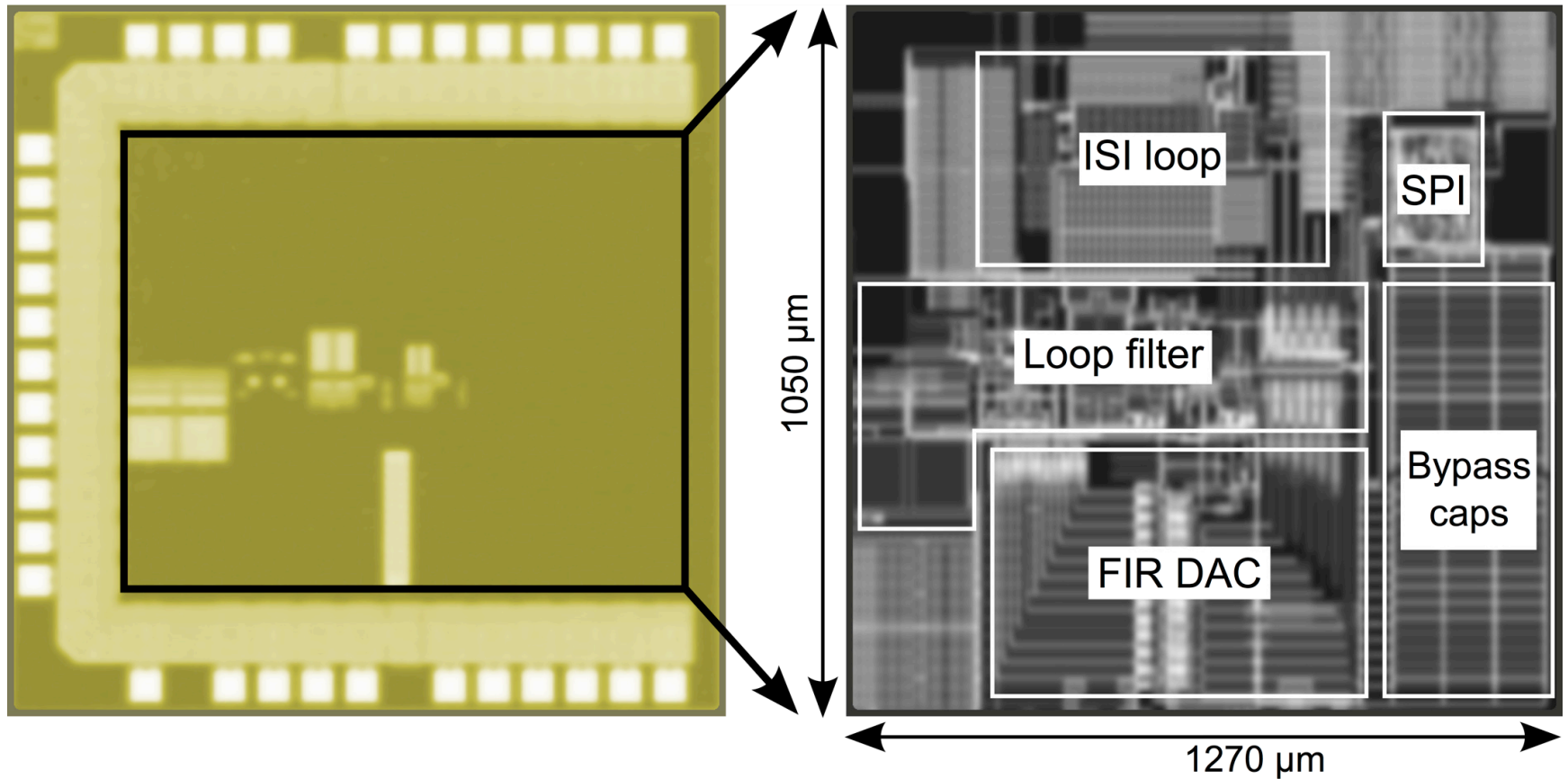


UMC 180nm CMOS process
(Europractice)


Dynamic Range Plot

 


PSD at Peak SNDR

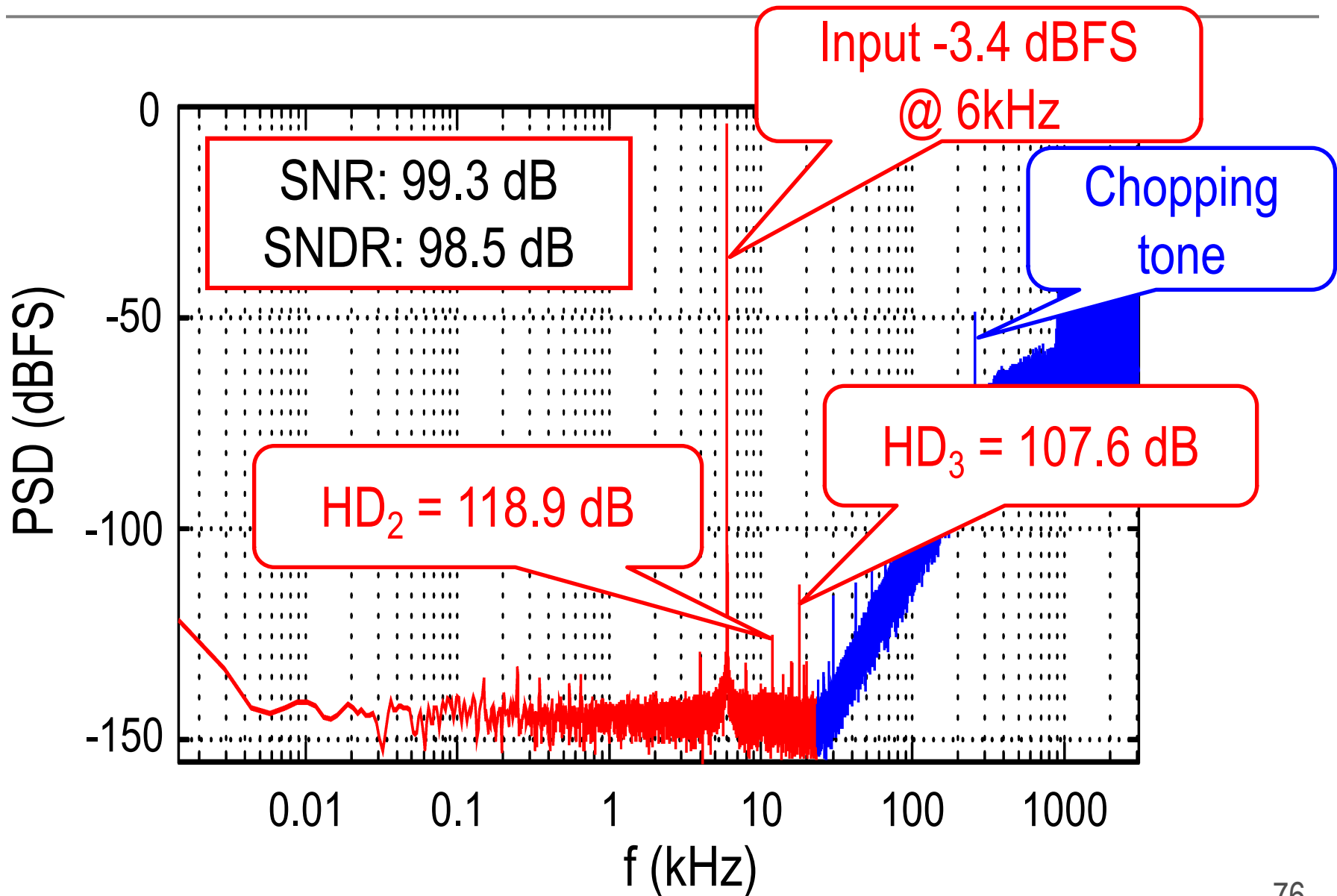


Low Frequency PSD

 


Low Frequency PSD

 

Low Frequency PSD

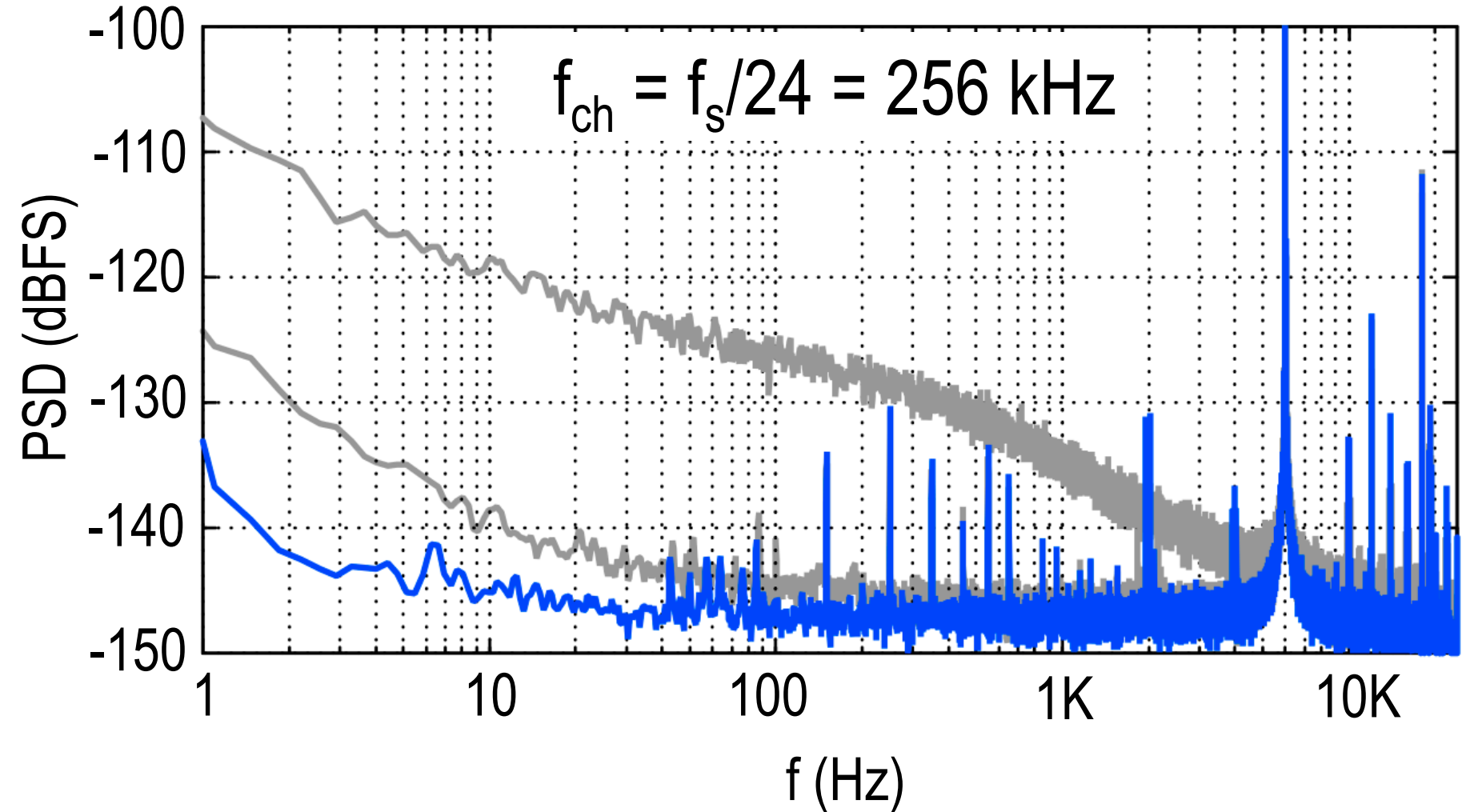


Low Frequency PSD

 


Effect of changing f_{ch}


Increased Aliasing

 

 PSD Comparison : $f_c = f_s/24$ & $f_s/20$



PSD Comparison

 

Performance Summary and Comparison

	This work	[3] JSSC 2014	[4] ISSCC 2008	[5] VLSI 2015	[6] ASSCC 2014
BW (kHz)	24	24	20	24	24
Feature Size (nm)	180	180	45	65	28
Supply (V)	1.8	1.8	1.1	1.1	1.1
Power (μ W)	280	280	1200	121	9900
Peak SNDR (dB)	98.5	98.2	76.5	85	98.5
DR (dB)	103.6	103	91.7	88	100.6
SFDR (dB)	107.6	106	80.5	90	102.6
Chop Freq. (kHz)	256	-	46	-	-
FoM _{SNDR} (fJ/ v)	85	88	500	173.4	342
FoM _{Schreier} (dB)	177.8	177.5	148.5	168	172 ^{0.1}

A Tale of 4 ADCs

- Multi-bit (4-bit ADC in the loop)
 - ESSCIRC 2007, JSSC 2008
- Single-bit ADC with linearity enhancement
 - ESSCIRC 2009, JSSC 2010
- Single-bit ADC + 12-tap FIR DAC
 - ASSCC 2013, JSSC 2014
- Single-bit ADC + 12-tap FIR DAC + Chopping
 - ISSCC 2016, JSSC 2017
- Same process, same design group

Multi-bit Modulator

- Third order CIFF loop
- 4-bit flash ADC
- OSR = 64 (Clock Rate = 3.072 MHz)
- NRZ Resistive DAC
- Data Weighted Averaging

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 43, NO. 2, FEBRUARY 2008

A Power Optimized Continuous-Time $\Delta\Sigma$ ADC for Audio Applications


Shanthi Pavan, Nagendra Krishnapura, Ramalingam Pandarinathan, and Prabu Sankar

Single-bit Modulator

- Third order ClFF loop
- 1-bit ADC
- OSR = 128 (Clock Rate = 6.144 MHz)
- NRZ Resistive DAC


Power Reduction in Continuous-Time Delta-Sigma Modulators Using the Assisted Opamp Technique

Modulator Architecture

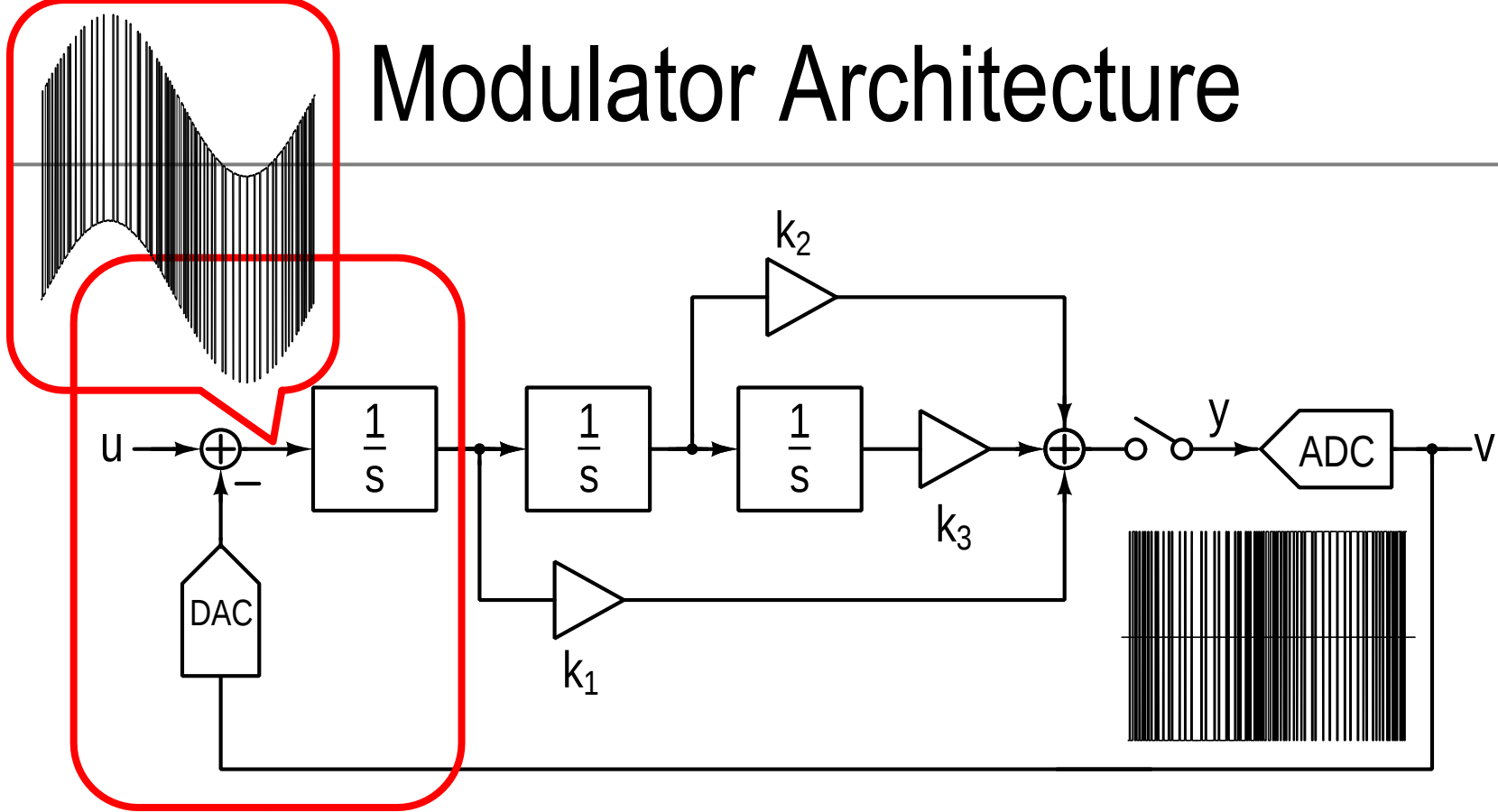

First integrator has to be very linear


The Assisted-Opamp Integrator

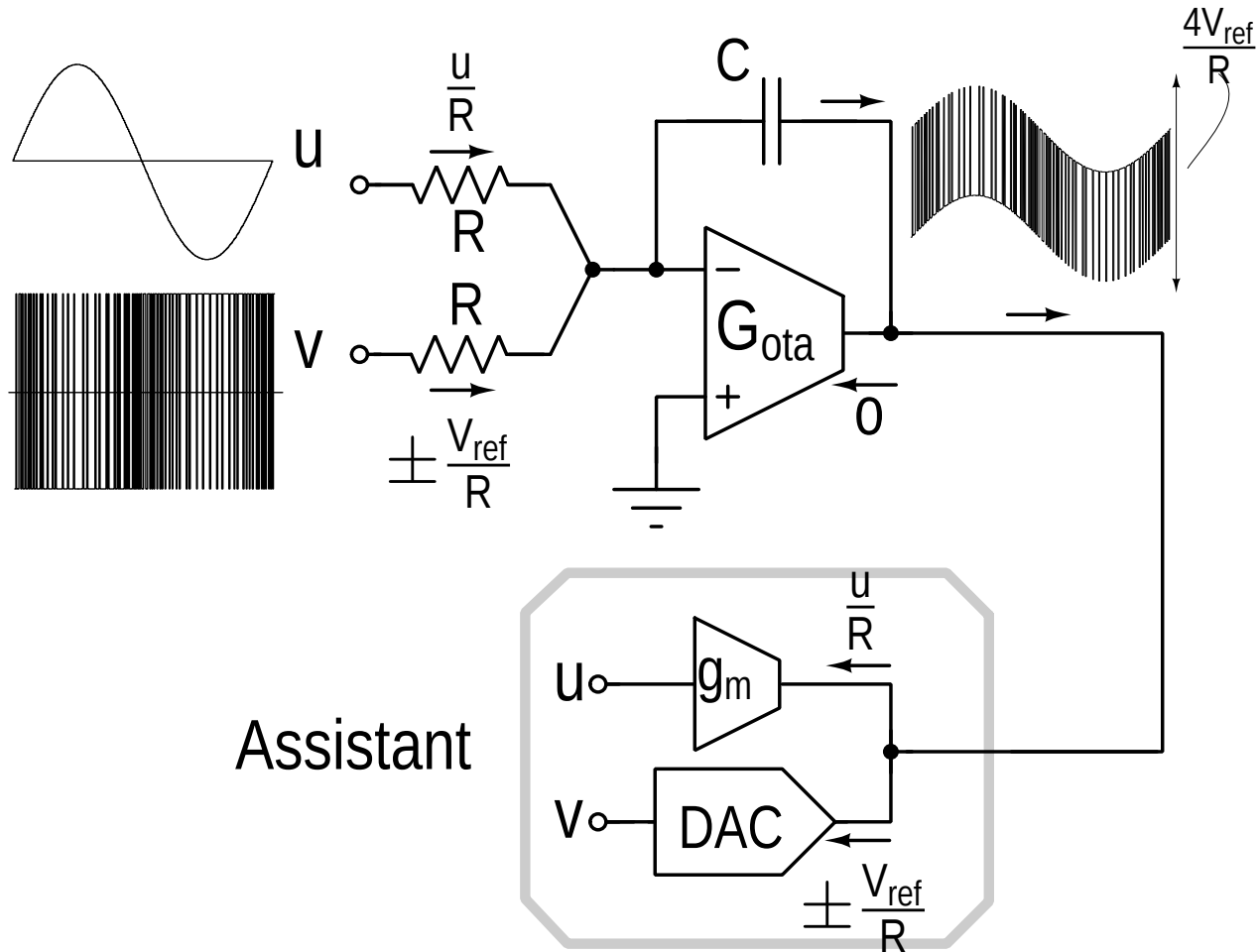

1-bit + FIR DAC Based Modulator

- Third order ClFF-B loop
- 1-bit ADC + 12-tap FIR DAC
- OSR = 128 (Clock Rate = 6.144 MHz)
- NRZ Resistive DAC

Modulator Architecture

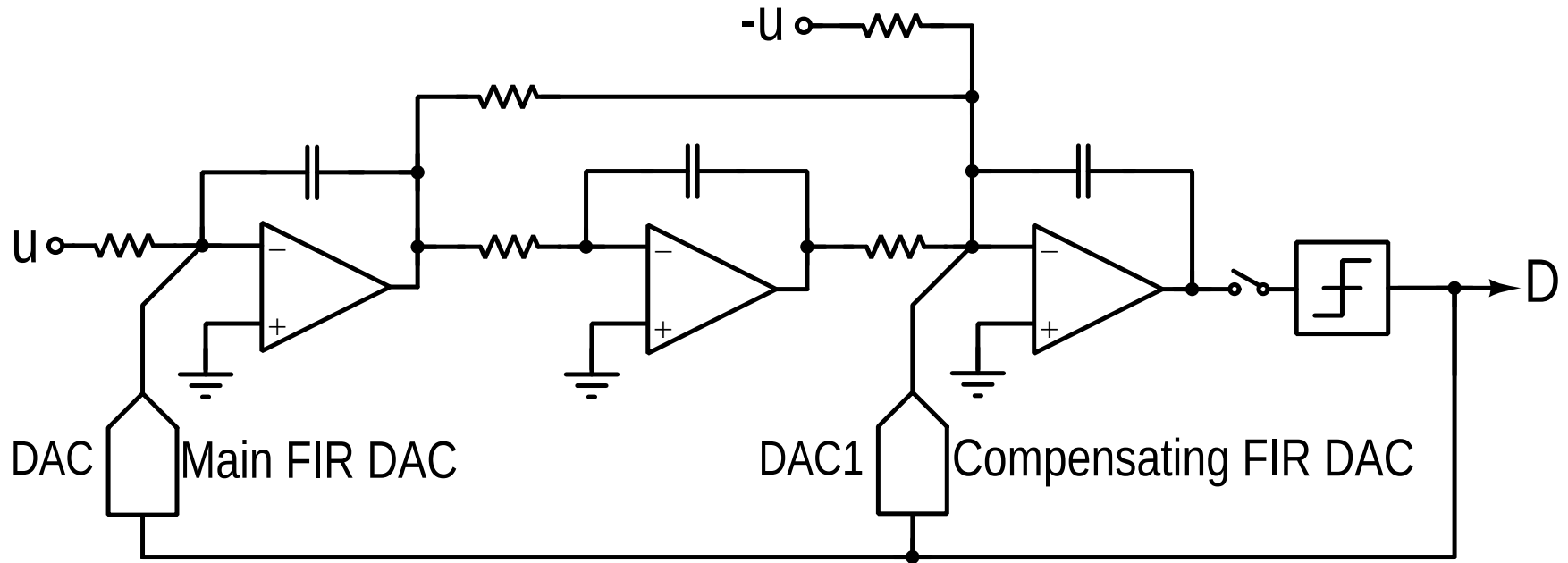

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 49, NO. 11, NOVEMBER 2014

Low Power Design Techniques for Single-Bit Audio Continuous-Time Delta Sigma ADCs Using FIR Feedback

Amrith Sukumaran and Shanthi Pavan, *Senior Member, IEEE*

1-bit + FIR DAC + Chopping

- Third order ClFF-B loop
- 1-bit ADC + 12-tap FIR DAC
- OSR = 128 (Clock Rate = 6.144 MHz)
- NRZ Resistive DAC
- First integrator chopped at $f_s/24$
- ISSCC 2016

Performance Summary and Comparison

	1-bit + FIR + chopping	1-bit ADC + FIR DAC	1-bit ADC	4-bit ADC
BW (kHz)	24	24	24	24
Feature Size (nm)	180	180	180	180
Supply (V)	1.8	1.8	1.8	1.8
Power (μ W)	280	280	110	121
Peak SNDR (dB)	98.5	98.2	88	90.8
DR (dB)	103.6	103	91.7	88
SFDR (dB)	107.6	106	95	94
FoM _{SNDR} (fJ/ v)	85	88	111	89
FoM _{Schreier} (dB)	177.8	177.5	171.4	173.7

Conclusions

- FIR feedback
 - ✓ Simple 1-bit ADC
 - ✓ Reduced ADC power and area
 - ✓ Simplified clock distribution
 - ✓ Inherently linear DAC → No DEM
 - ✓ Relaxes integrator linearity and jitter requirements
 - ✓ Chopping for free
 - ✓ Combines benefits of 1-bit and multi-bit operation
 - ✓ Highest Schreier FoM reported