

Measurements, models and extractions

Rüdiger Follmann



Contents

- Models
- Linear part
- Nonlinear part
- Current measurements
- S-parameter measurements
- Power measurements
- Noise
- Verification



Ways of modeling

- **Physical models:** Particle models or semiconductor equations
- **Table based models:** Bias dependent S-parameters are saved in a table
- **Mathematical models:** Transfer behavior is described by mathematical functions
- **Equivalent circuits:** Physical behavior is emulated by lumped elements



Ways of modeling


Linear models

- Description of DC behavior
- Description of RF behavior, e.g. in dependence of bias point. Only small signal amplitudes close to bias point are allowed

Non-linear models

- Large signal amplitudes and change of bias point (Harmonic balance).

Harmonic balance

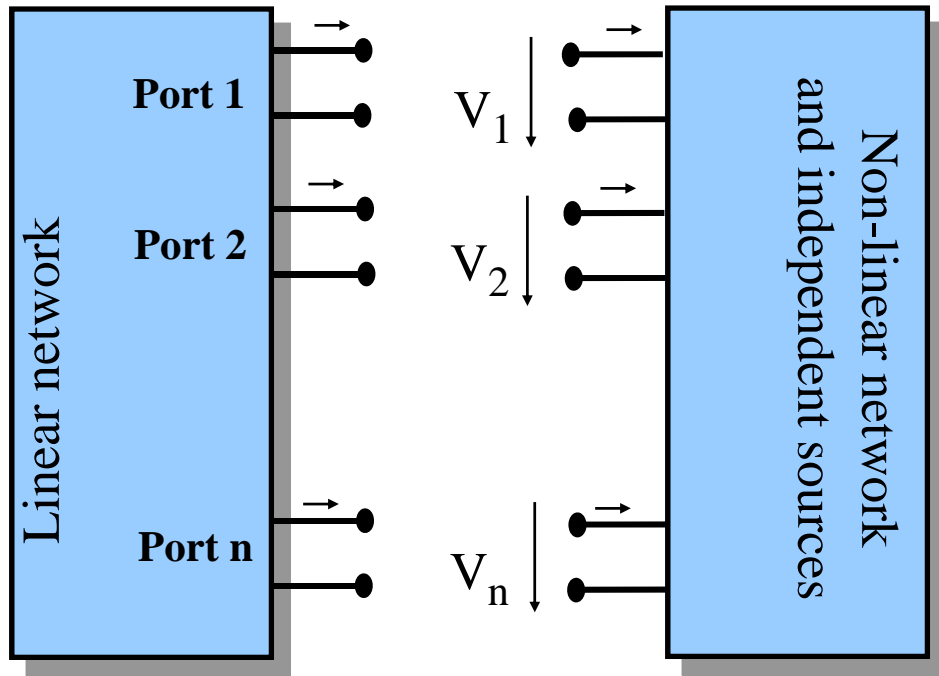

Only linear elements

Only non-linear elements


HB is a hybrid between time- and frequency domain calculations.

Non-linear part is calculated in time domain, linear part in frequency domain

Voltages and currents at each port are balanced, until they are equal for both part of network.


DC measurements

Port 1
Input


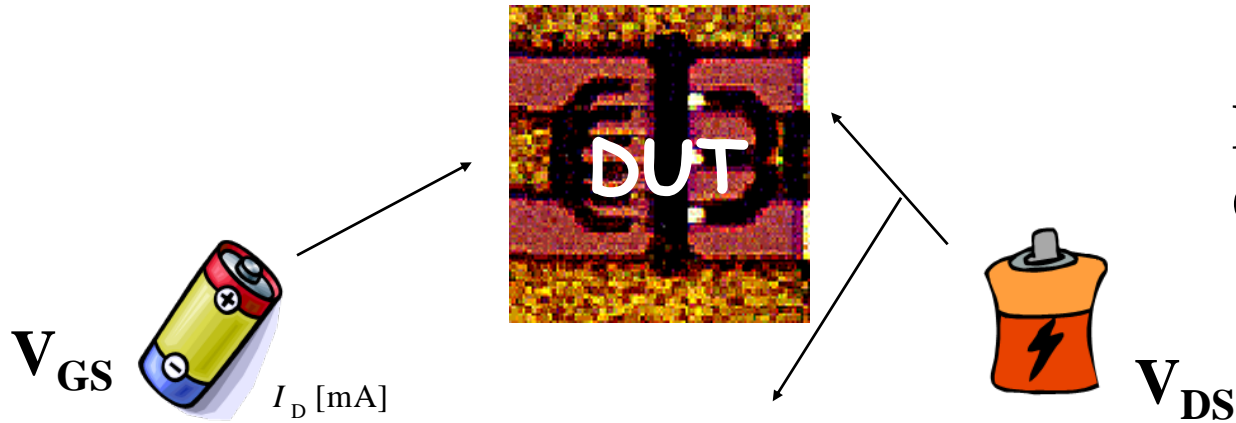


Port 2
Output


DC IV-
curves

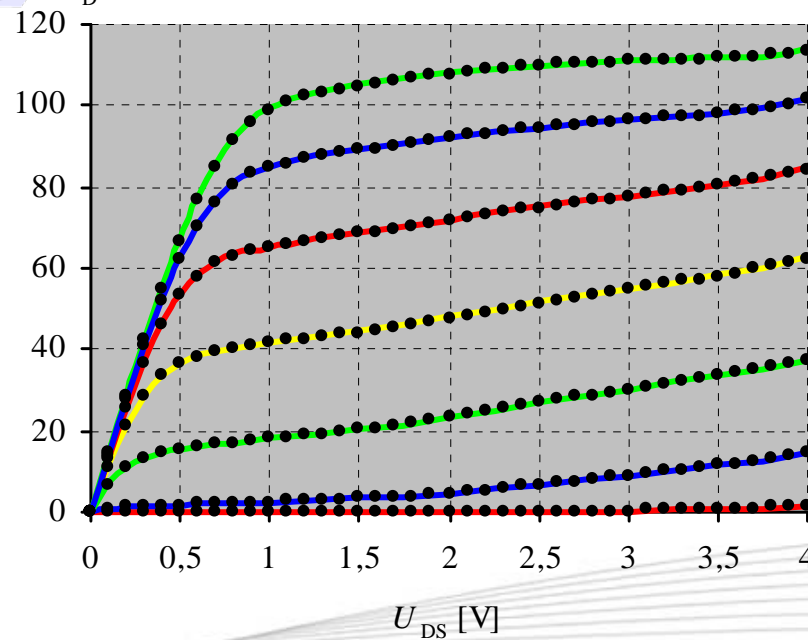

Transistor transfer curves

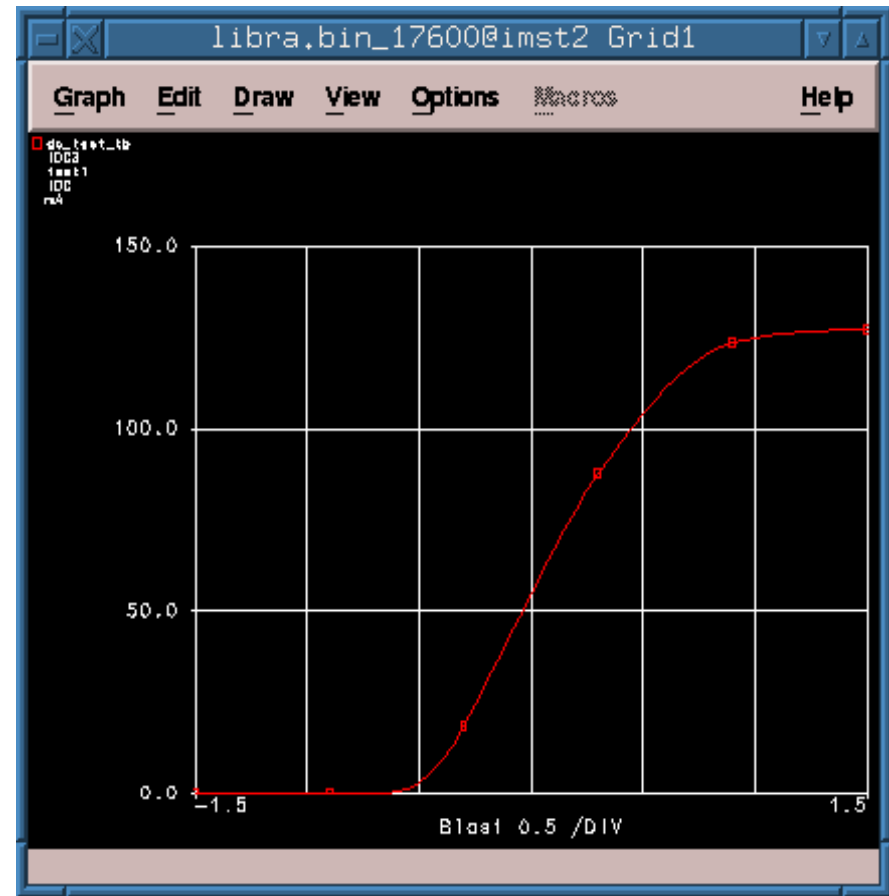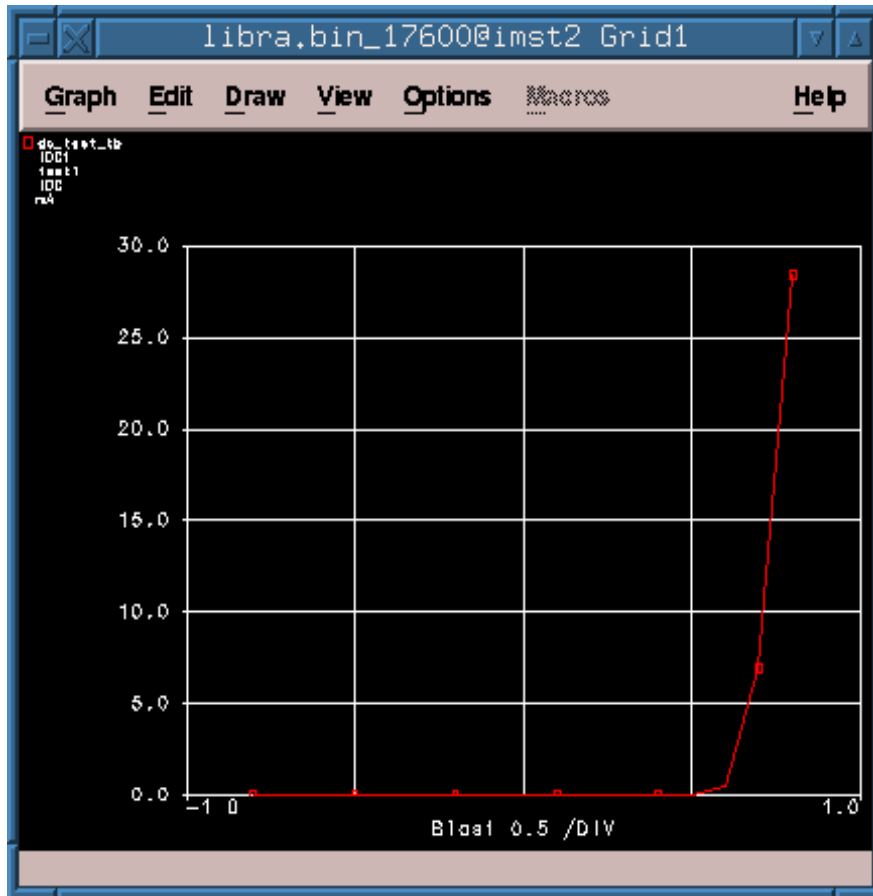


Gummel-Plots

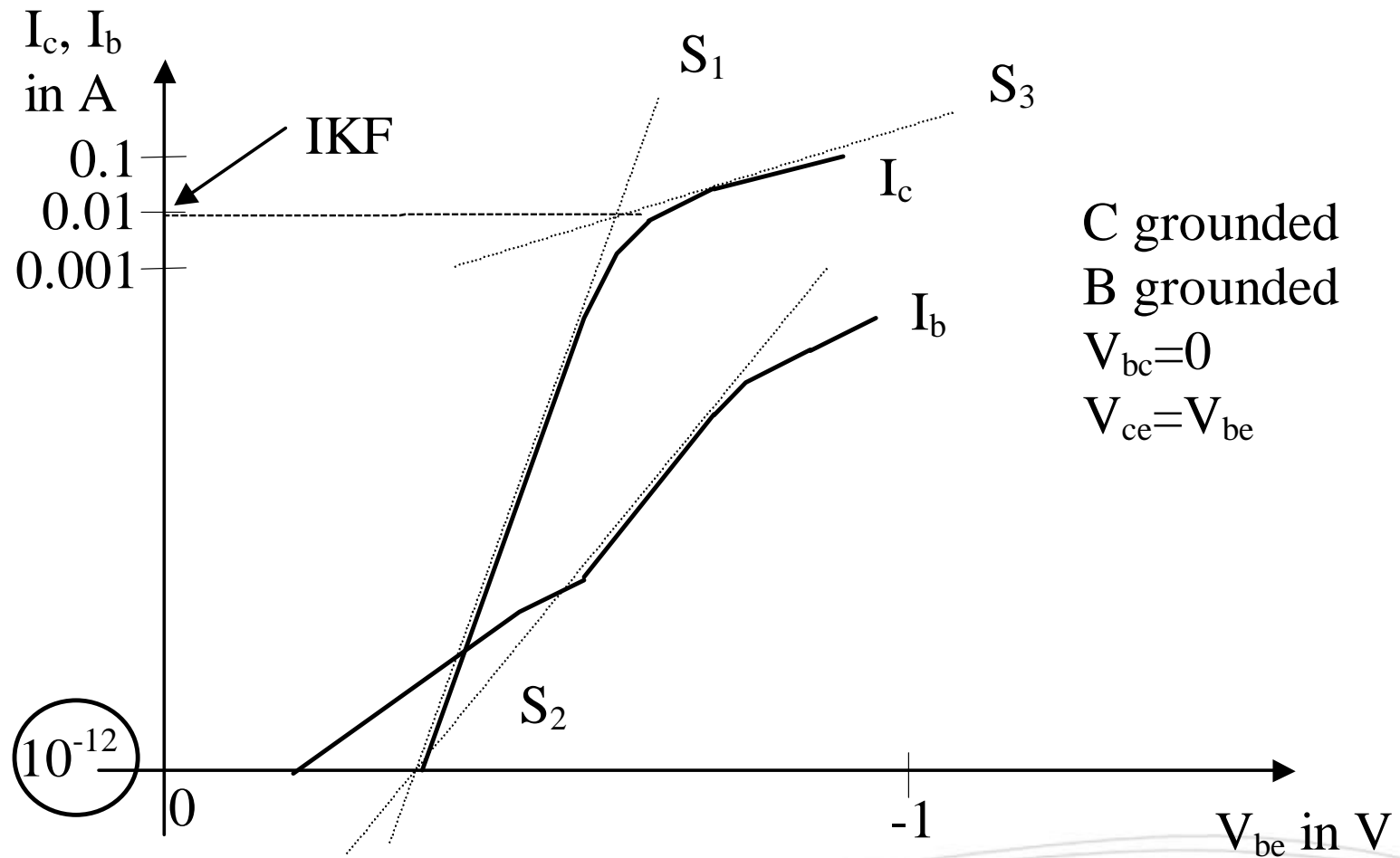

RF measurements



S-parameter measurements

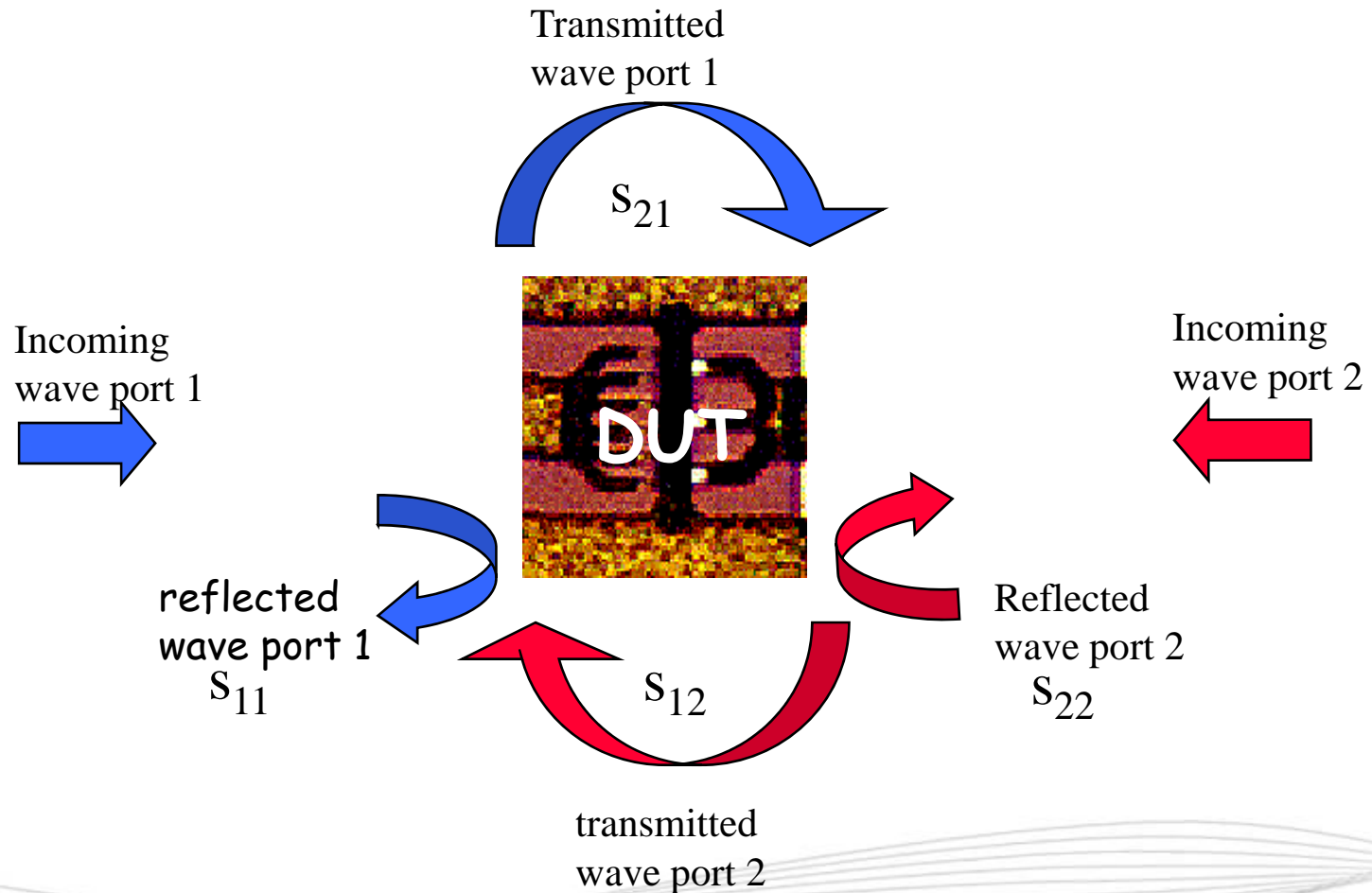



RF measurements

S-parameter measurements

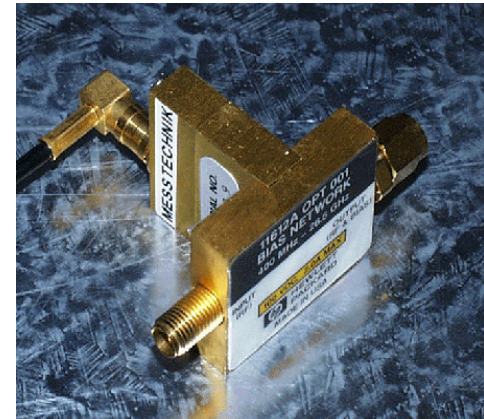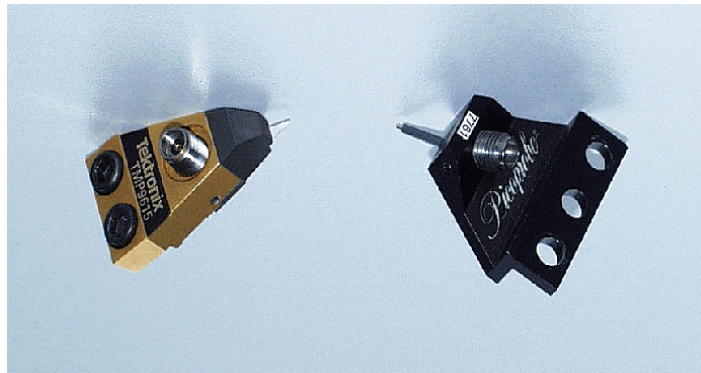




Qualification


- Pinch-off of transistor device
- Enhancement or depletion mode
- Slope and IV curves
- Gate diode current
- amplification s_{21} and attenuation
- Compression behavior
- Other s-parameters < 0 dB

Composition FET und equivalent circuit

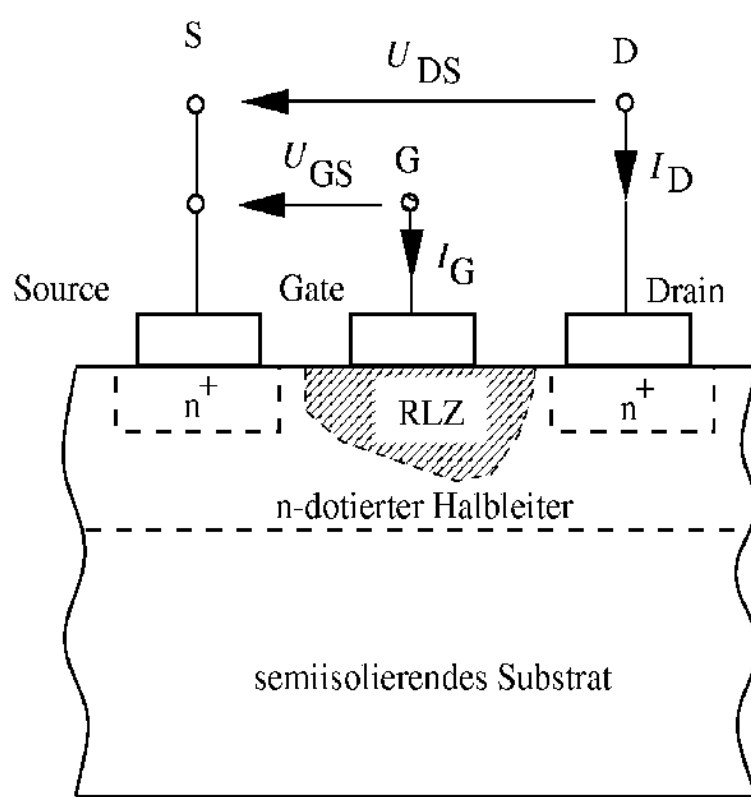


Das Bild kann nicht angezeigt werden. Dieser Computer verfügt möglicherweise über zu wenig Arbeitsspeicher, um das Bild zu öffnen, oder das Bild ist beschädigt. Starten Sie den Computer neu, und öffnen Sie dann erneut die Datei. Wenn weiterhin das rote x angezeigt wird, müssen Sie das Bild möglicherweise löschen und dann erneut einfügen.

Small signal equivalent circuit

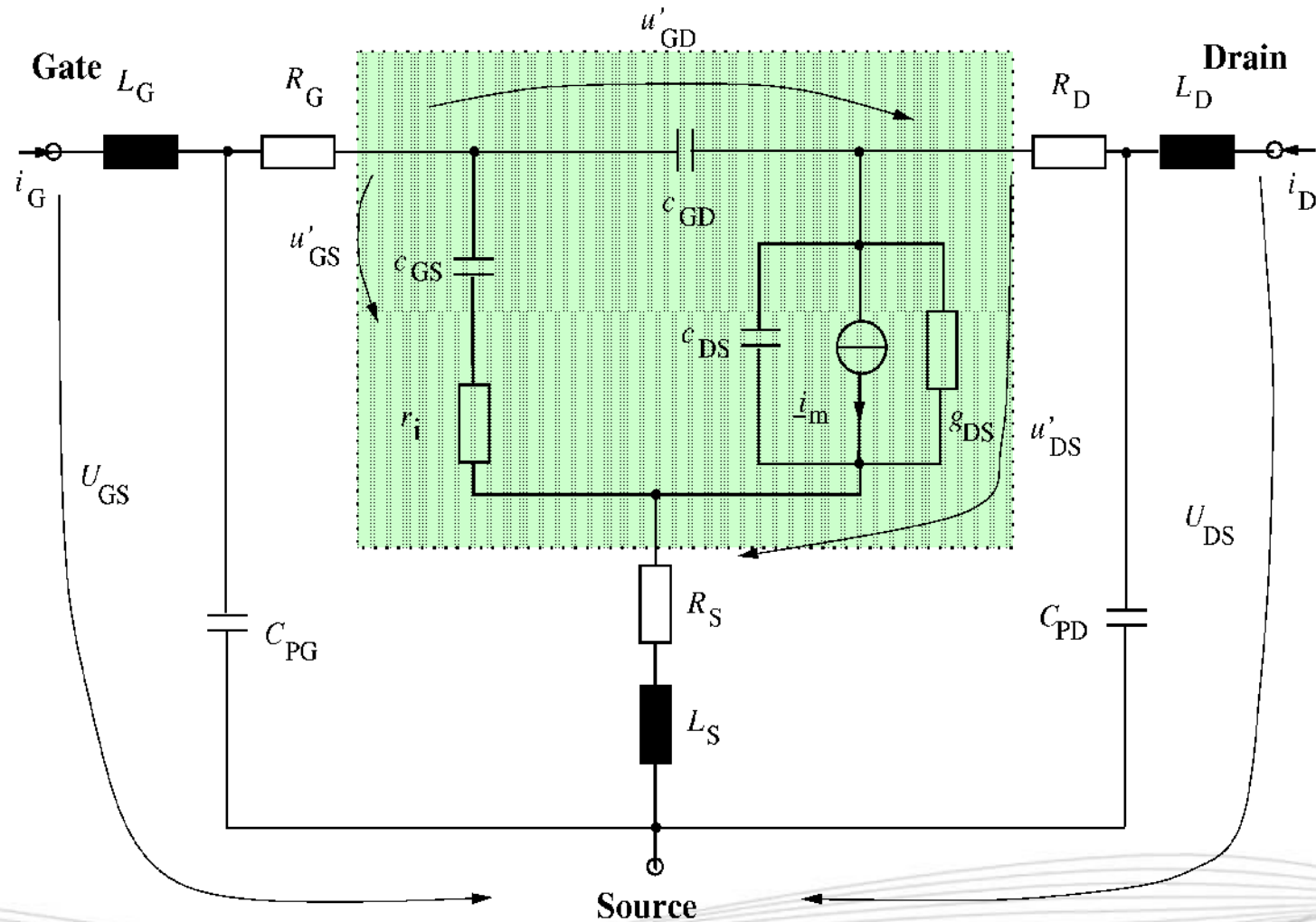


Enhanced small signal equivalent circuit

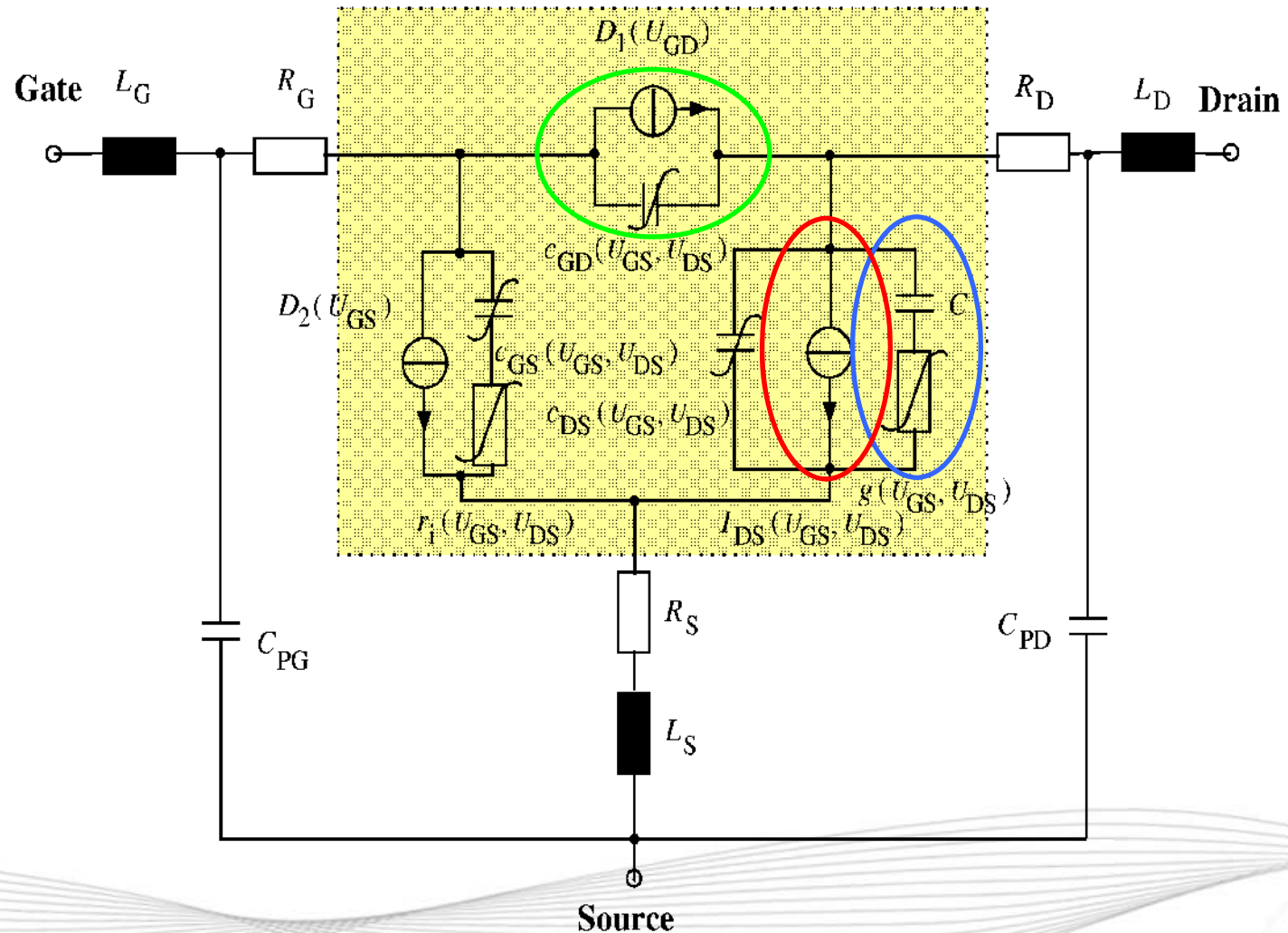

Parameter extraction


S-Parameter
IV curves

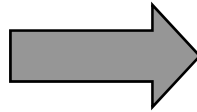

Extrinsic
elements





Intrinsic
elements

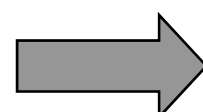


$$R_S = \text{Re}\{z_{12}\}$$
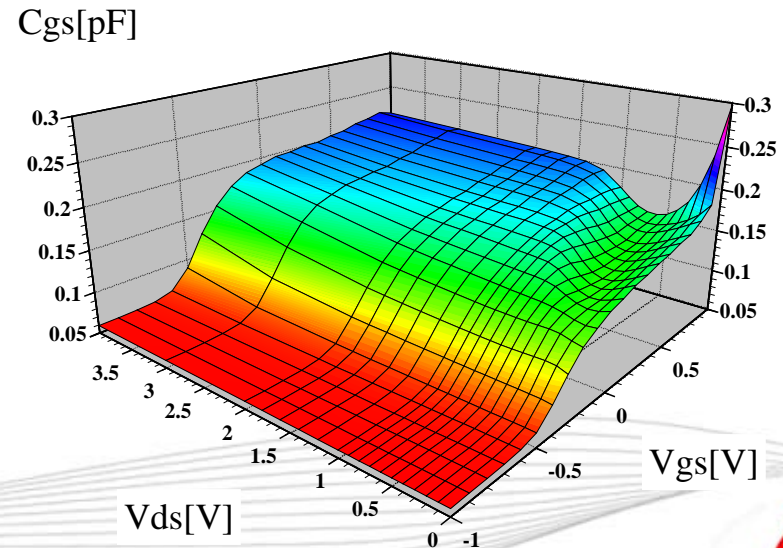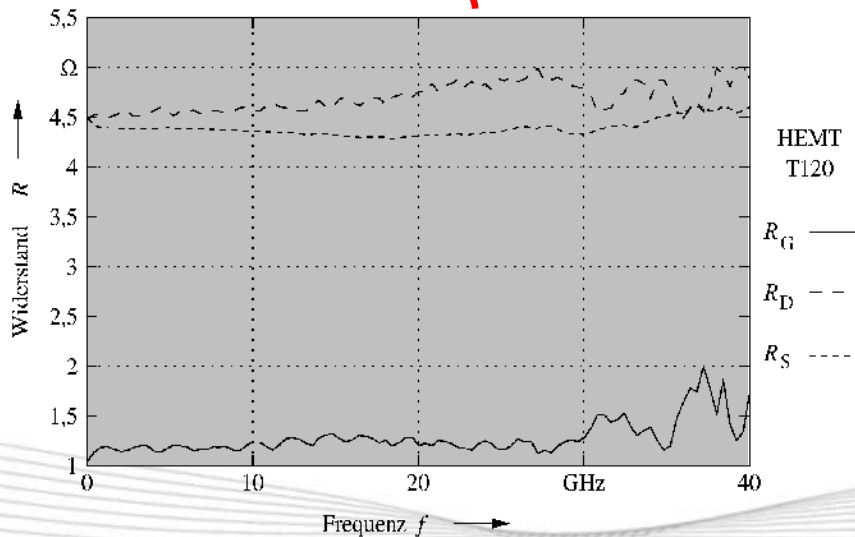
$$C_{GS}(V_{GS}, V_{DS}) = \sum_{f=f_1}^{f_2} \frac{1}{\omega} \left(\text{Im}\{y_{11}(V_{GS}, V_{DS})\} + \text{Im}\{y_{12}(V_{GS}, V_{DS})\} \right) / (n_{f2} - n_{f1})$$




Parameter extraction


Optimization of
intrinsic
elements

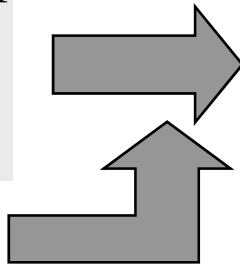

Calculation of
conductance g

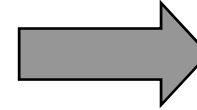

De-embedding
of
voltages

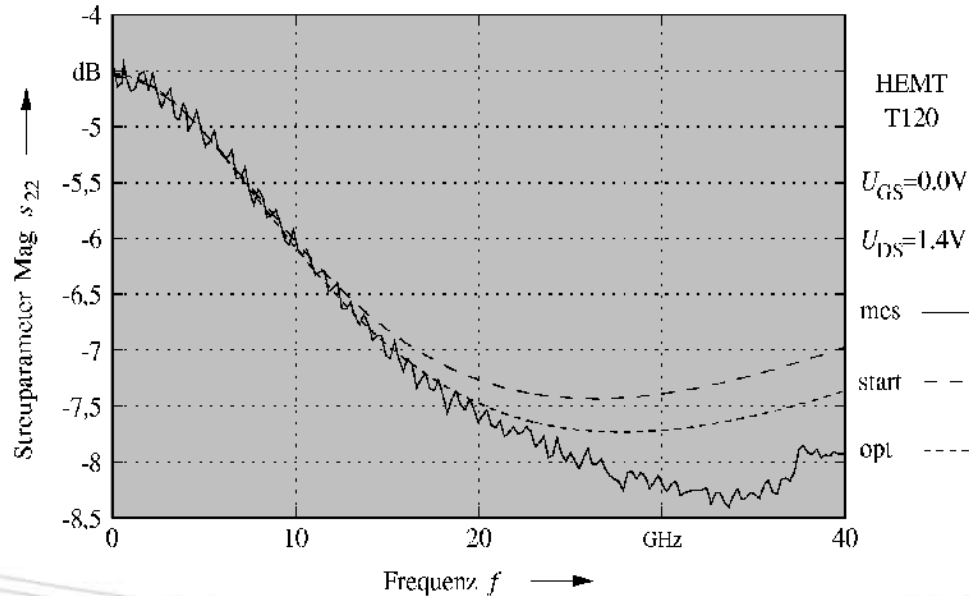


$$V'_{GS} = V_{GS} - I_{DS} R_S$$

$$V'_{DS} = V_{DS} - I_{DS} (R_D + R_S)$$

Parameterextraktion


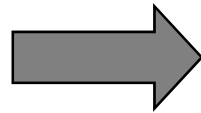
Calculation of scaling and noise parameters



Description of intrinsic elements



Store the Simulation file

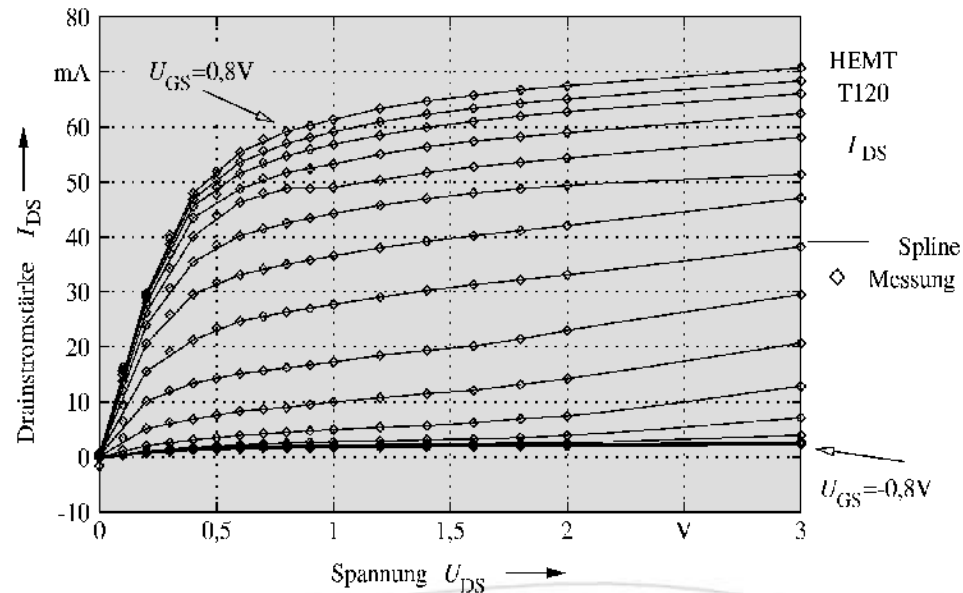
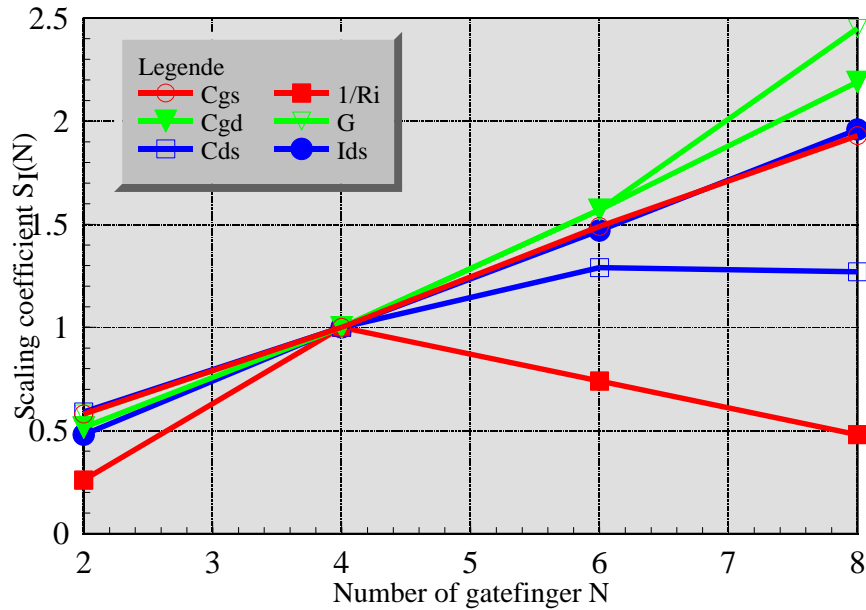


Extraction of extrinsic elements

Extraction of capacitances

$$V_{GS} < V_p$$

$$V_{DS} = 0 \text{ V}$$

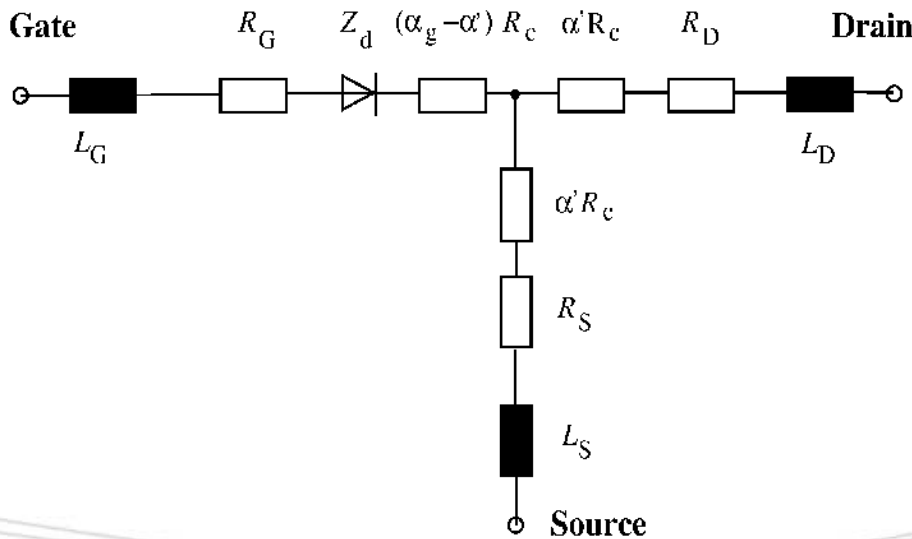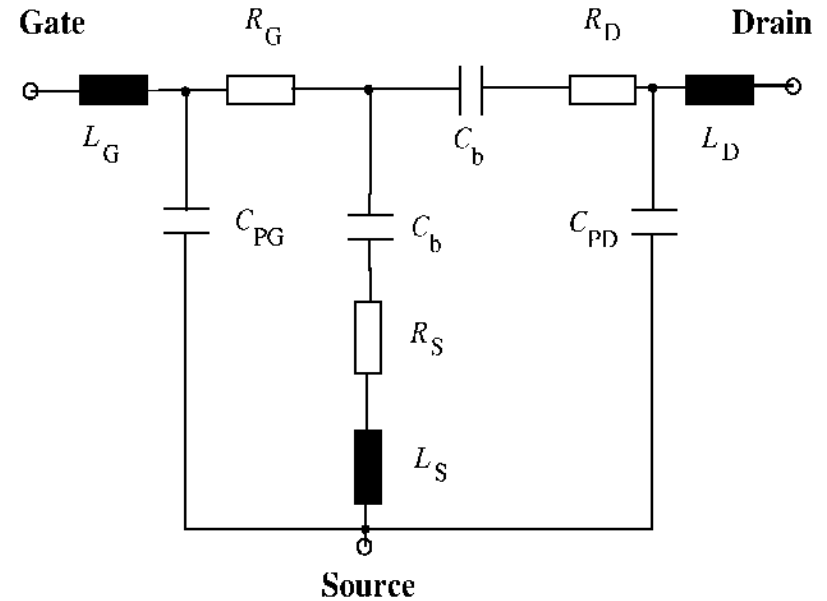

Extraction of inductances and resistors

$$V_{GS} > 0 \text{ V}$$


$$V_{DS} = 0 \text{ V}$$

Extraction of intrinsic elements

$$\underline{S} \rightarrow \underline{Z}$$



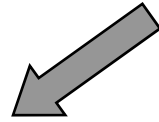
$$\begin{pmatrix} \underline{z}_{11} - j\omega L_G & \underline{z}_{12} \\ \underline{z}_{21} & \underline{z}_{22} - j\omega L_D \end{pmatrix}$$



$$\underline{Z} \rightarrow \underline{Y}$$


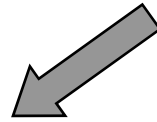
$$\begin{pmatrix} \underline{y}_{11} - j\omega C_{PG} & \underline{y}_{12} \\ \underline{y}_{21} & \underline{y}_{22} - j\omega C_{PD} \end{pmatrix}$$




$$\underline{Y} \rightarrow \underline{Z}$$



$$\begin{pmatrix} \underline{z}_{11} - R_S - R_G - j\omega L_S & \underline{z}_{12} - R_S - j\omega L_S \\ \underline{z}_{21} - R_S - j\omega L_S & \underline{z}_{22} - R_S - R_D - j\omega L_S \end{pmatrix}$$


Extraction of intrinsic elements

$C_{gd}[\text{pF}]$

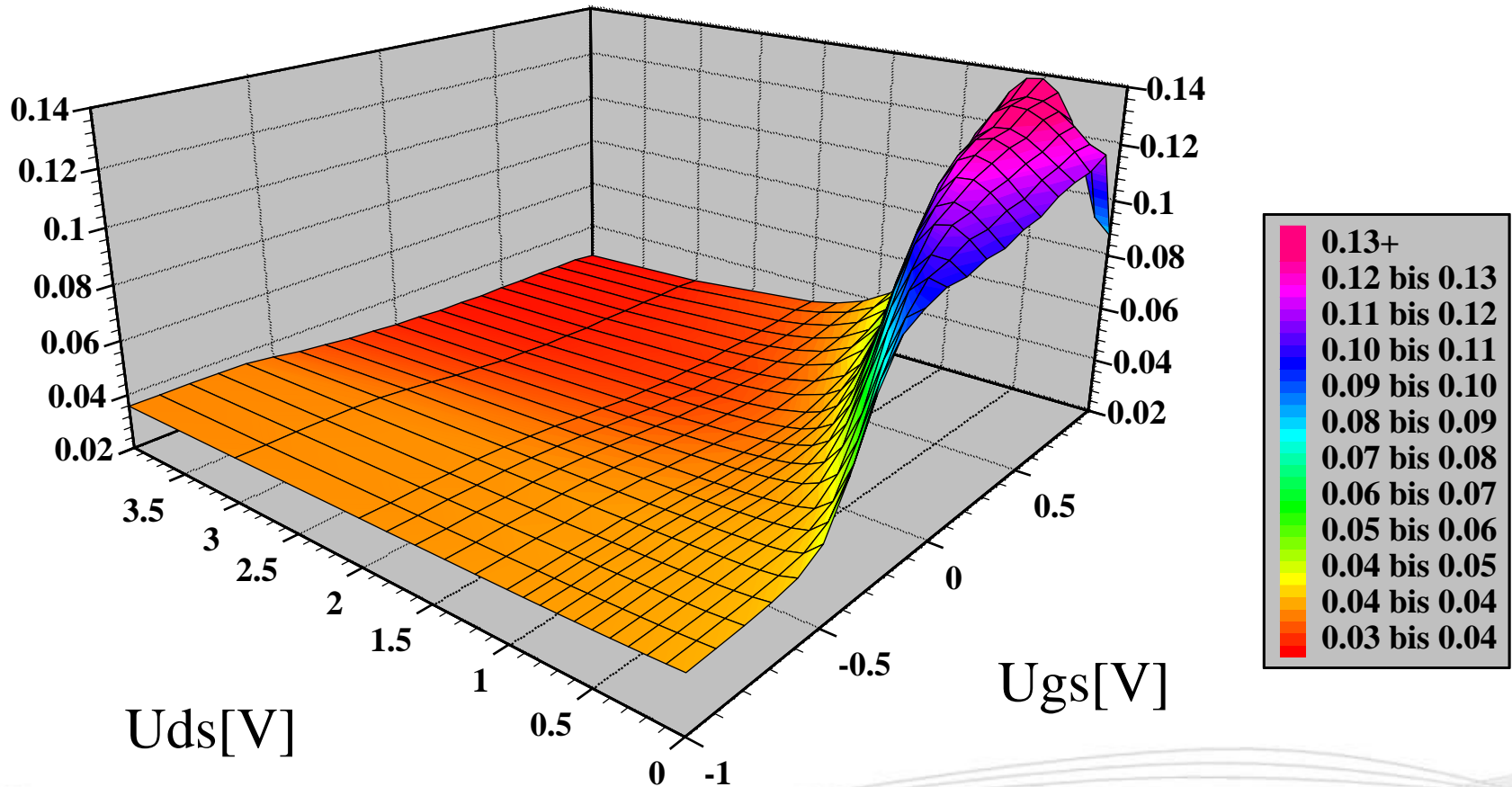




Extraction of intrinsic elements

C_{gs} [pF]

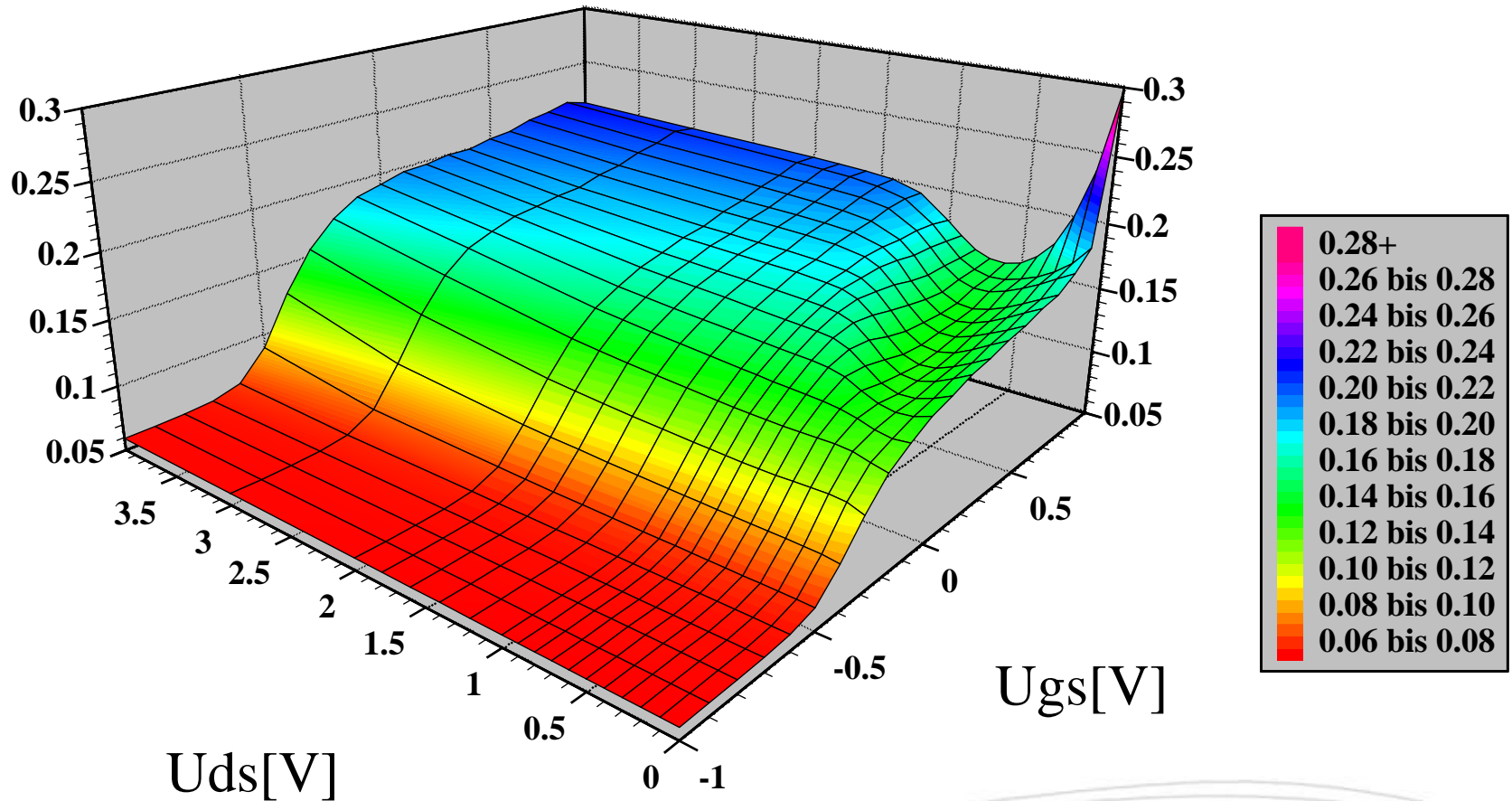


Calculation of output conductance

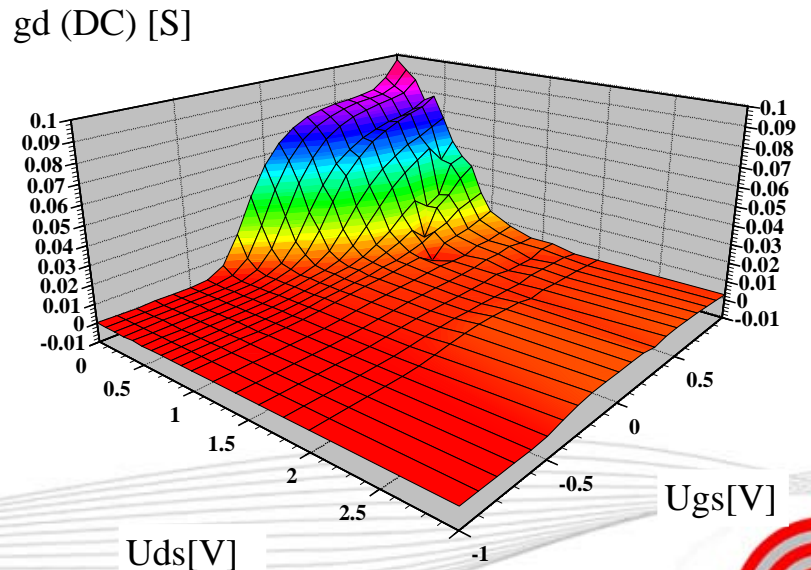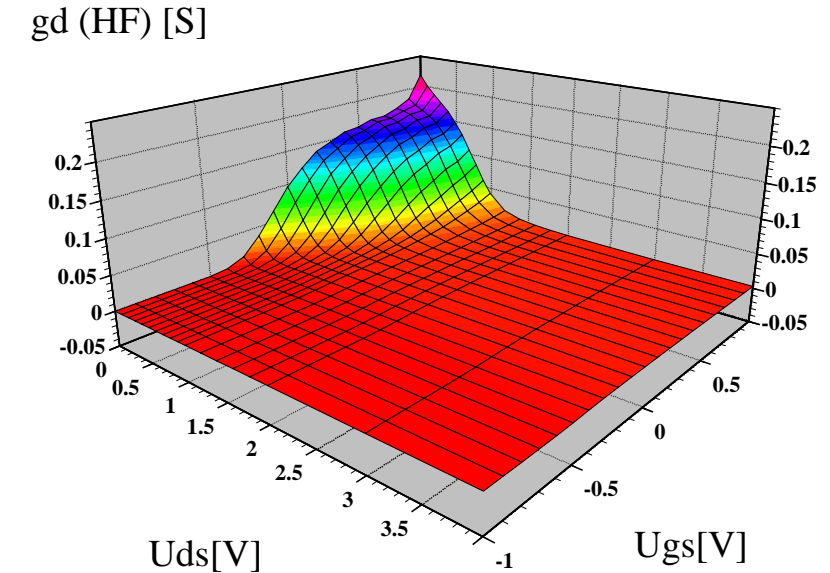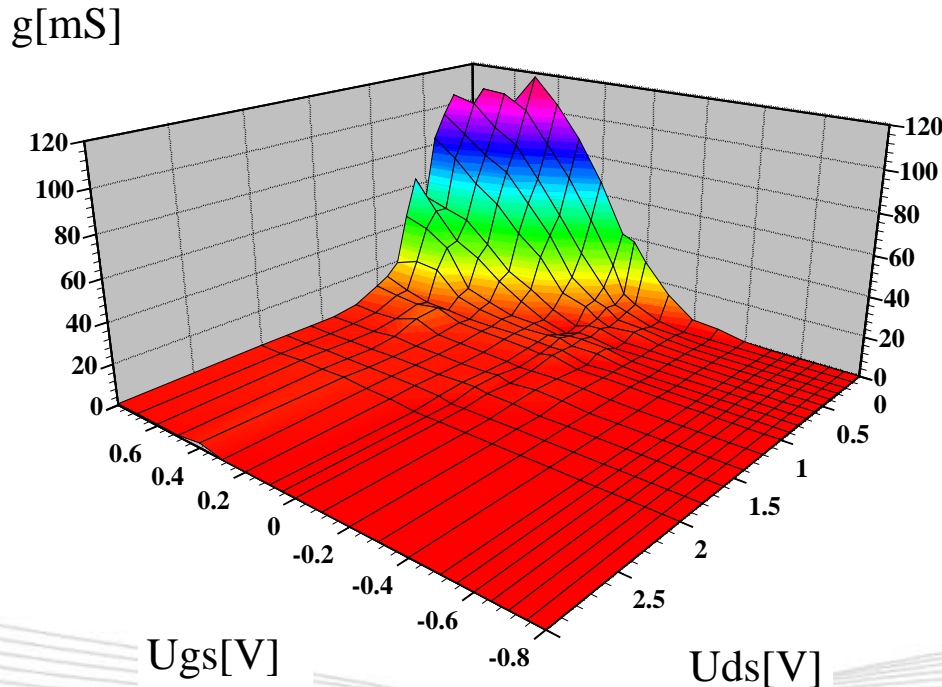Extraction of output conductance g using optimizing process



Extraction of I_S and n

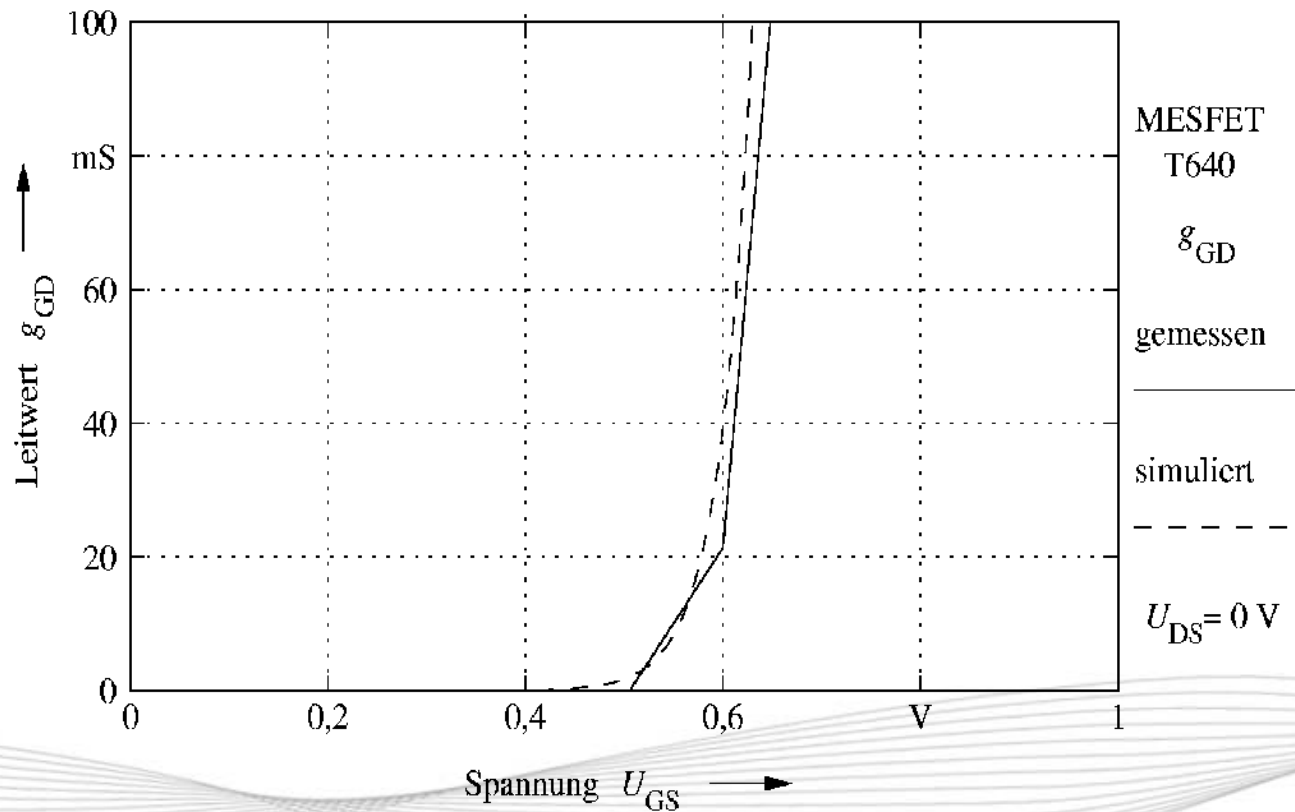
$$\operatorname{Re} \left\{ \underline{y}_{12} \right\} = - \frac{dI_{d1}}{dU_{GD}} = - \frac{I_S}{nU_t} \exp\left(\frac{U_{GD}}{nU_t} \right)$$



Outer and inner voltages

$$V'_{GS} = V_{GS} - I_{DS} R_S$$
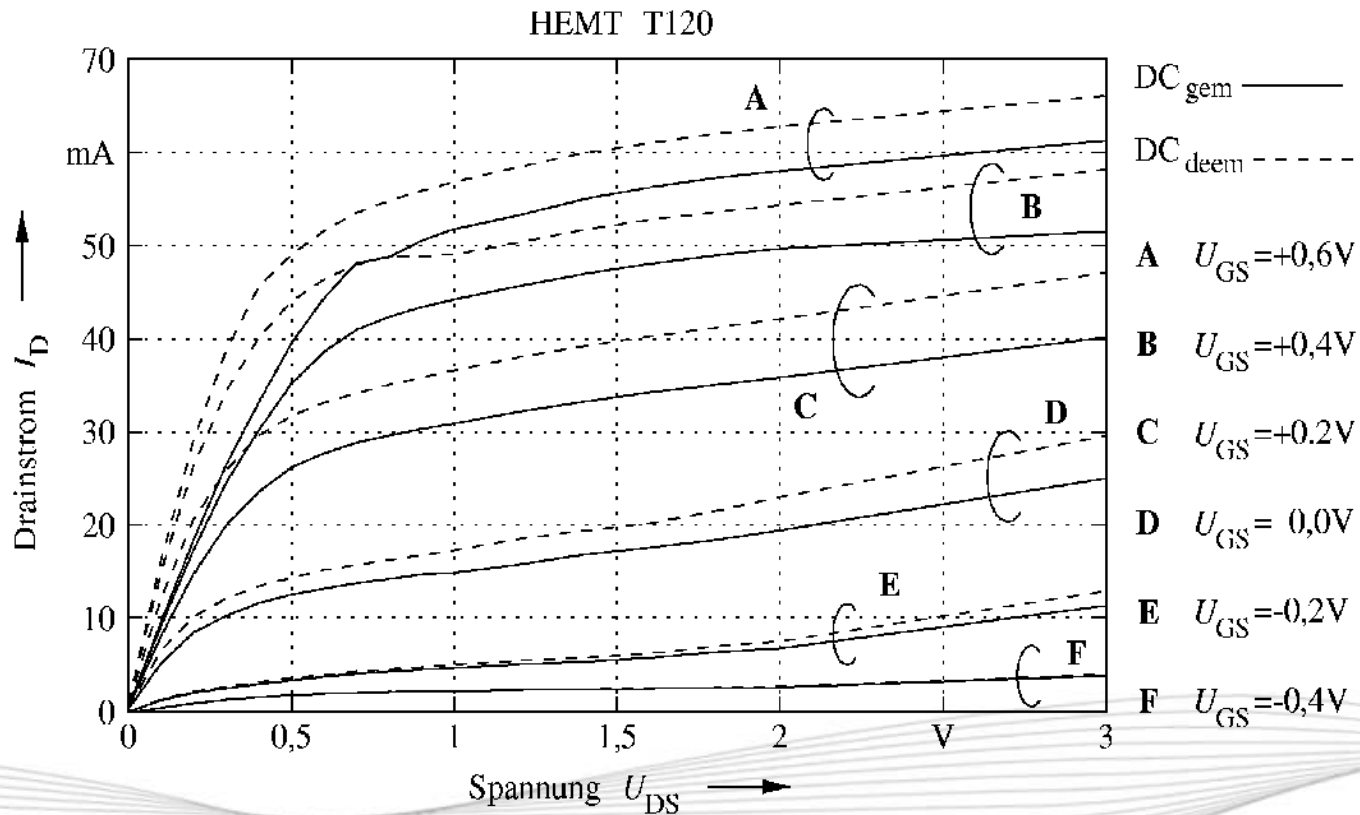
$$V'_{DS} = V_{DS} - I_{DS} (R_D + R_S)$$



Description of intrinsic elements

$$c_{GS} = \begin{cases} k_h + k_g U_{DS} + x_{20} & U_{DS} > 0 \\ k_h + x_{20} & \text{sonst} \end{cases}$$

$$k_a = \begin{cases} x_0 (U_{GS} - x_1)^2 & U_{GS} \geq x_1 \\ 0 & \text{sonst} \end{cases}$$

$$k_b = x_2 (\tanh(x_3 (U_{GS} - x_{17}))) + 1$$

$$k_h = k_a (\exp(k_b (U_{DS} - k_c)^2)) + k_d (\tanh(k_e (U_{DS} - k_f))) + 1$$


$$k_c = x_4 \exp(x_5 (U_{GS} - x_6)^2)$$

$$k_d = x_7 (\tanh(x_{21} (U_{GS} - x_8))) + 1$$

$$k_e = x_9 (U_{GS} - x_{10})^2 + x_{11}$$

$$k_f = x_{12} \exp(x_{13} (U_{GS} - x_{14})^2) + x_{18}$$
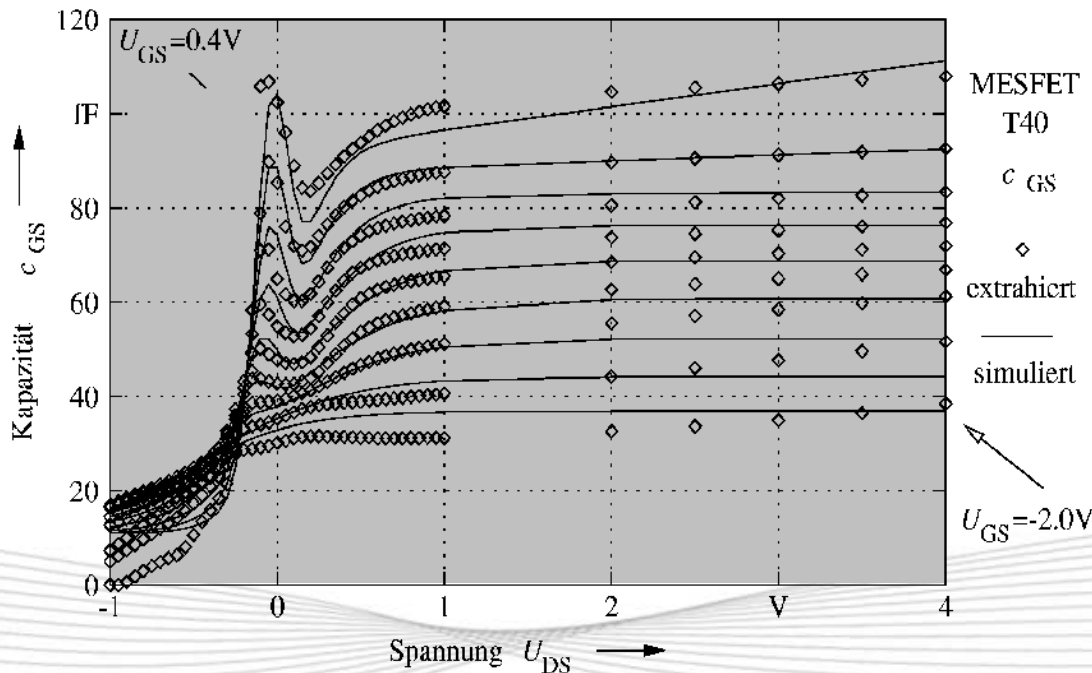
$$k_g = x_{15} \exp(x_{16} (U_{GS} - x_{19})^2)$$



Large signal simulation

$$Q_1(u_1) = \int_{u_{10}}^{u_1} c(\tilde{u}_1) d\tilde{u}_1$$

$$\Delta Q = \oint_{\partial\Omega} c(\tilde{u}_1) d\tilde{u}_1 = 0$$

$$Q_2(u_1, u_2) = \int_{u_{10}}^{u_1} c(\tilde{u}_1, u_2) d\tilde{u}_1 + Q'_1(u_2)$$

Defined charge cycle

Trans elements

$$C(u_1, u_2) = \sum_{i=0}^n c_i(u_1) T_i(u_2)$$

Complete gate current

$$i_G = i_{GS} + i_{GD}$$

$$u_{GS} = U_{GS} + u_{GS\sim} \Rightarrow \frac{du_{GS}}{dt} = \frac{du_{GS\sim}}{dt}$$

GS-part of gate current $i_{GS} = \frac{dQ_{GS}}{dt} = C'_{GS}(u_{GS}, u_{DS}) \frac{du_{GS}}{dt}$

Large signal simulation

$$i_{GS} = C'_{GS}(U_{GS} + u_{GS\sim}, U_{DS} + u_{DS\sim}) \frac{du_{GS\sim}}{dt}$$

Taylor-series


$$\begin{aligned} C'_{GS}(U_{GS} + u_{GS\sim}, U_{DS} + u_{DS\sim}) &= C'_{GS}(U_{GS}, U_{DS}) \\ &+ \left. \frac{\partial C'_{GS}(u_{GS}, u_{DS})}{\partial u_{GS}} \right|_{\substack{u_{GS}=U_{GS} \\ u_{DS}=U_{DS}}} u_{GS\sim} \\ &+ \left. \frac{\partial C'_{GS}(u_{GS}, u_{DS})}{\partial u_{DS}} \right|_{\substack{u_{GS}=U_{GS} \\ u_{DS}=U_{DS}}} u_{DS\sim} + \dots \end{aligned}$$

GS-part of gate current

$$i_{GS} = c_{GS}(U_{GS}, U_{DS}) \frac{du_{GS}}{dt}$$

Large signal simulation
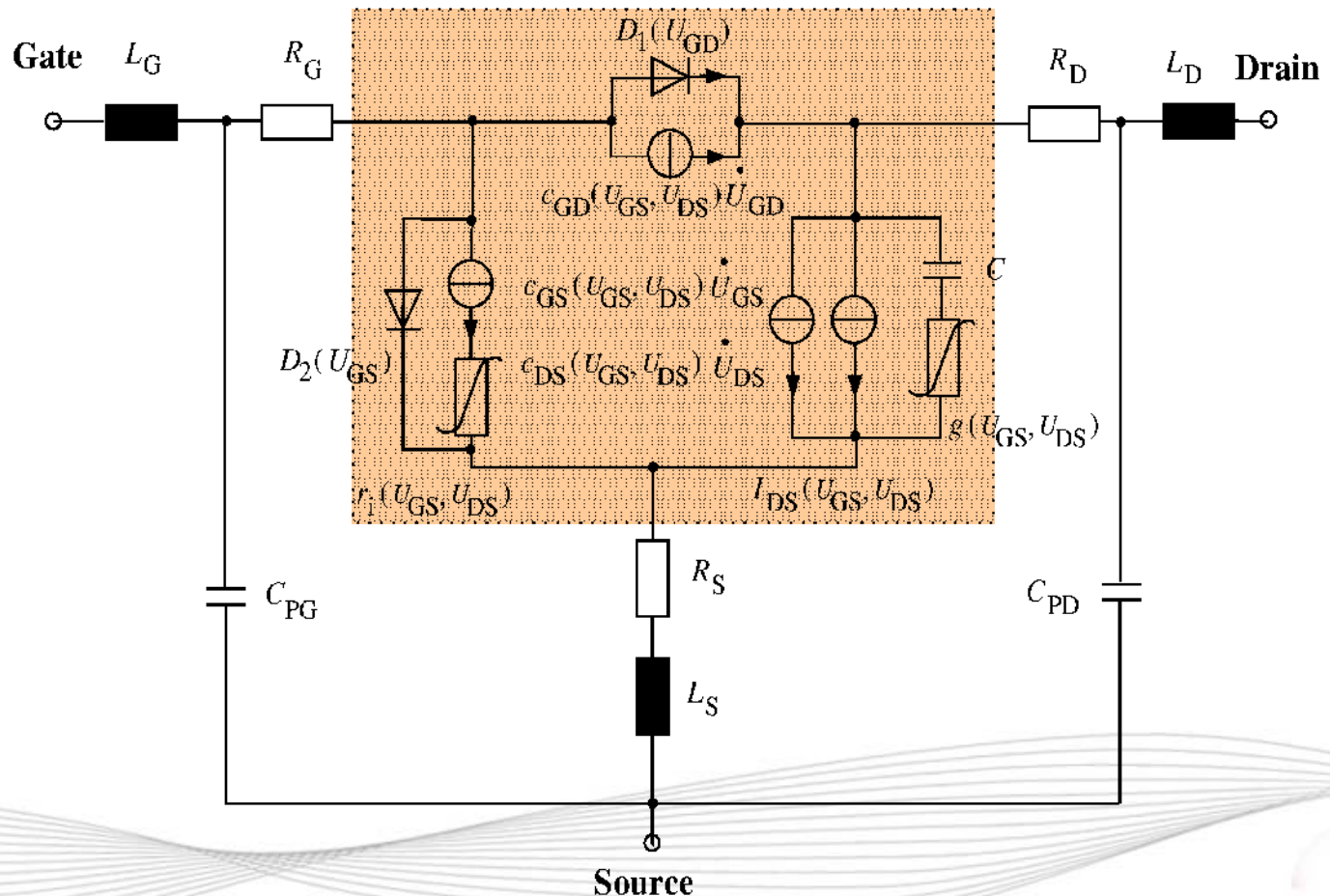
$$i_G = \frac{dQ(u_{GS}, u_{DS})}{dt} = \frac{\partial Q(u_{GS}, u_{GD})}{\partial u_{GS}} \frac{du_{GS}}{dt} + \frac{\partial Q(u_{GS}, u_{GD})}{\partial u_{GD}} \frac{du_{GD}}{dt}$$



Large signal simulation

Due to designation of 2 voltages of Vgs, Vds and Vgd, the third voltage is always defined!

Case 1: Gate charge is known

$$Q_G = au_{GS}^2 + bu_{GS}u_{DS} + au_{DS}^2$$

$$i_G = \frac{dQ(u_{GS}, u_{DS})}{dt} = \frac{\partial Q_G(u_{GS}, u_{GD})}{\partial u_{GS}} \frac{du_{GS}}{dt} + \frac{\partial Q_G(u_{GS}, u_{GD})}{\partial u_{GD}} \frac{du_{GD}}{dt}$$

$$u_{DS} = f \cos(\omega t) \quad u_{GS} = e \sin(\omega t)$$

$$i_G = \omega(A \sin(2\omega t) + B \cos(2\omega t))$$

$$A = ae^2 - cf^2$$

$$B = bef$$

Pure capacitive gate current, no DC part

Large signal simulation

Case 2: The capacitances are known

$$c_{DS}(u_{GS}, u_{DS}) = \left. \frac{\partial Q_G}{\partial u_{DS}} \right|_{u_{GS}=\text{const.}} = bu_{GS} + 2cu_{DS}$$

$$c_{GS}(u_{GS}, u_{DS}) = \left. \frac{\partial Q_G}{\partial u_{GS}} \right|_{u_{DS}=\text{const.}} = 2au_{GS} + bu_{DS}$$

$$i_{GS} = \omega(C + D \sin(2\omega t) + C \cos(2\omega t))$$

$$C = 0,5bef$$

$$D = ae^2$$

$$i_{GD} = \omega(-C + E \sin(2\omega t) + C \cos(2\omega t))$$



$$E = -cf^2$$

DC current parts, which compensate each other


Large signal simulation

$$i_R = \dot{q} = C \cdot \dot{V}$$


$$V_R = i_R R = CR \cdot \dot{V}$$

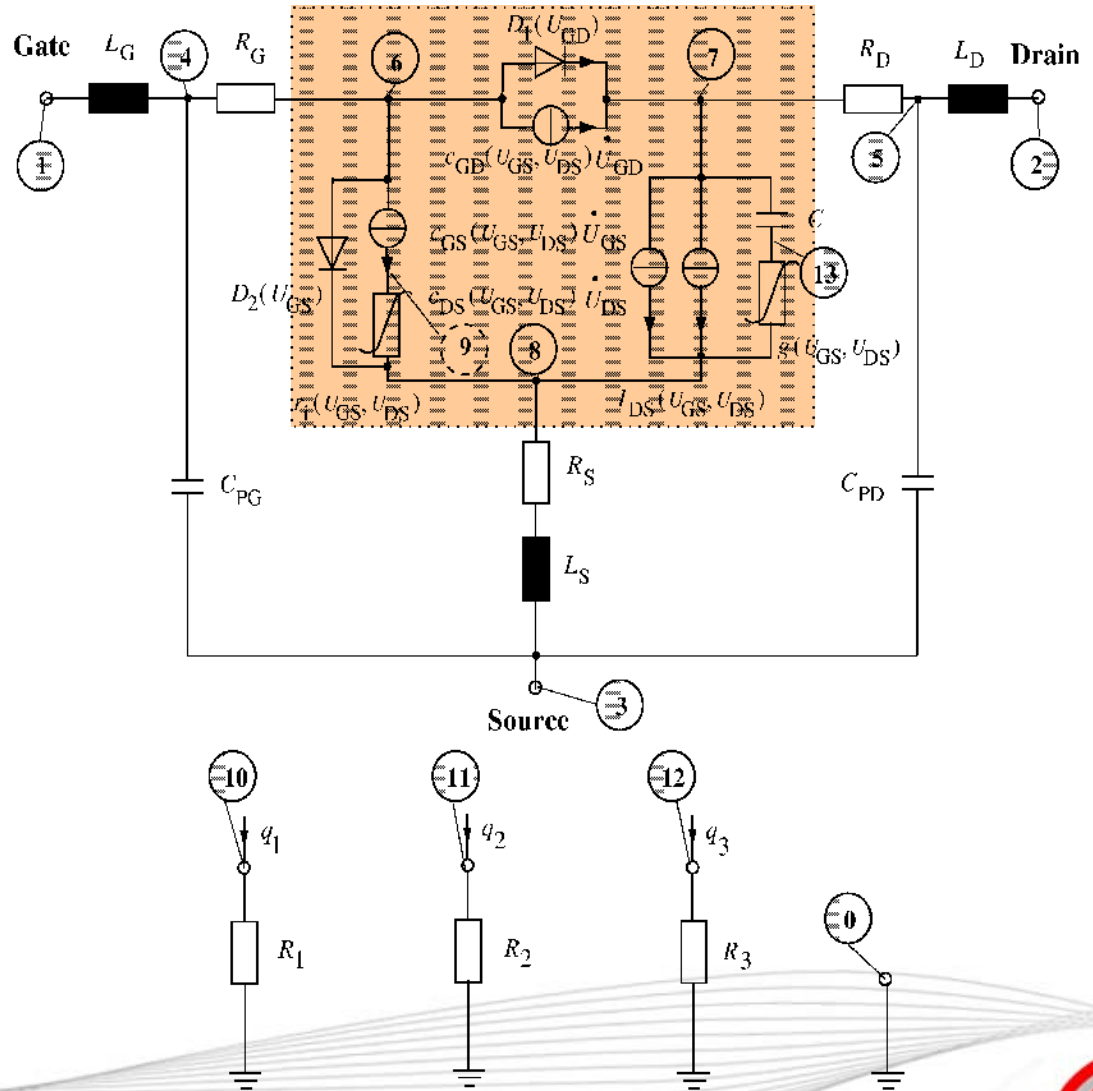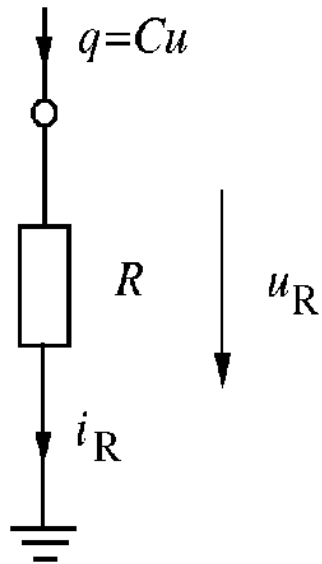

Example

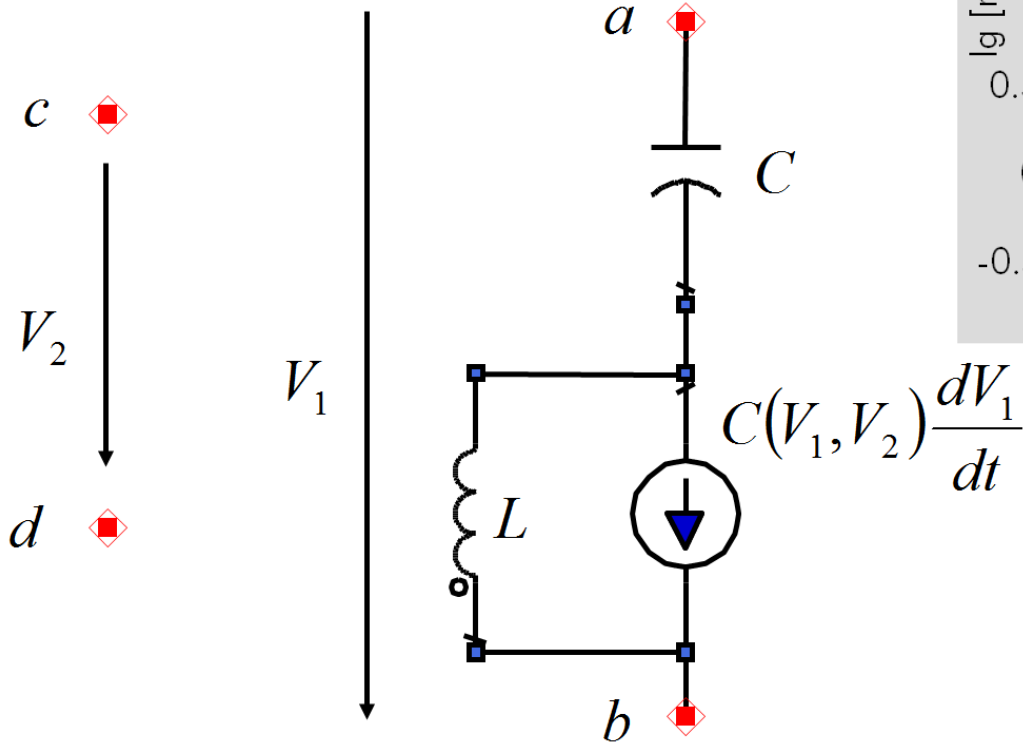


L, C large

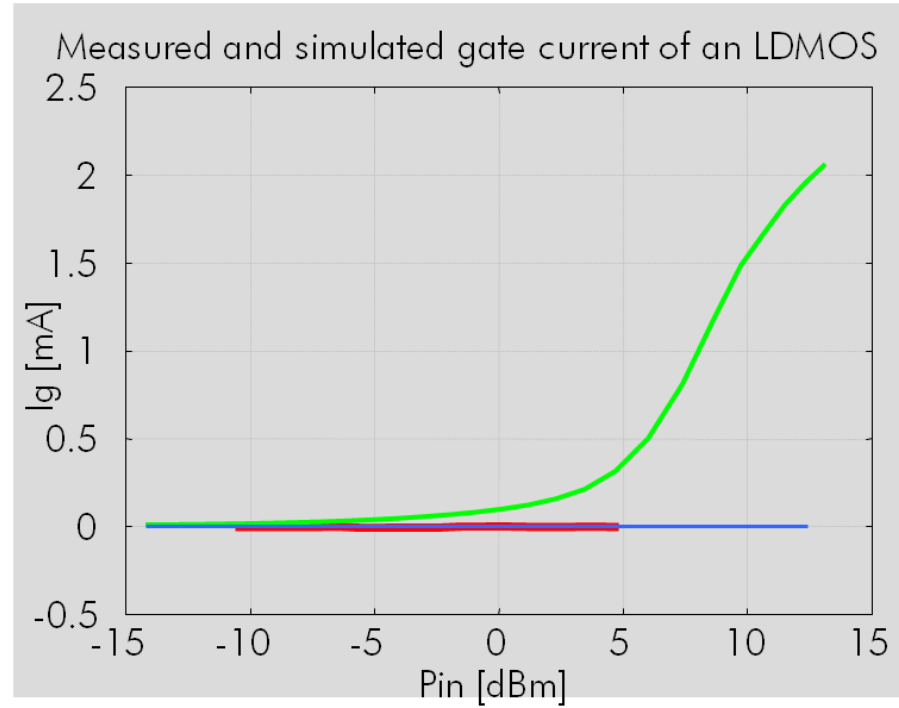

Consistent implementation

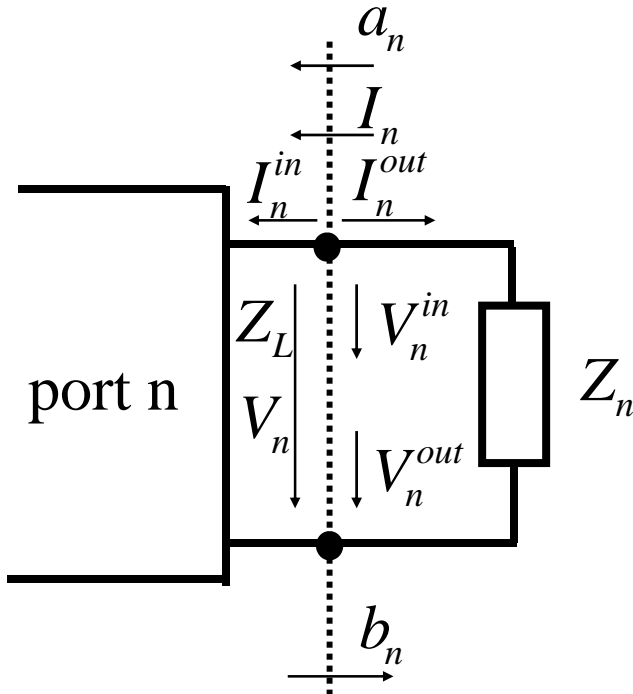Calculation of S-parameters using currents and voltages



Waves in an out of port n

$$a_n = \frac{V_n^{in}}{\sqrt{Z_{Ln}}} = I_n^{in} \sqrt{Z_{Ln}}$$

$$b_n = \frac{V_n^{out}}{\sqrt{Z_{Ln}}} = I_n^{out} \sqrt{Z_{Ln}}$$

Voltages and currents on the line

$$u_n = \frac{V_n}{\sqrt{Z_{Ln}}} = \frac{V_n^{in} + V_n^{out}}{\sqrt{Z_{Ln}}} = a_n + b_n$$

$$i_n = I_n \sqrt{Z_{Ln}} = (I_n^{in} - I_n^{out}) \sqrt{Z_{Ln}} = a_n - b_n$$

$$a_n = \frac{1}{2}(u_n + i_n)$$

$$b_n = \frac{1}{2}(u_n - i_n)$$

S-Matrix

$$\|b\| = \|s\| \cdot \|a\|$$


Example

$$s_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0}$$


$$s_{11,dB} = 20 \cdot \log \frac{u_1 - i_1}{u_1 + i_1}$$

Consistent implementation

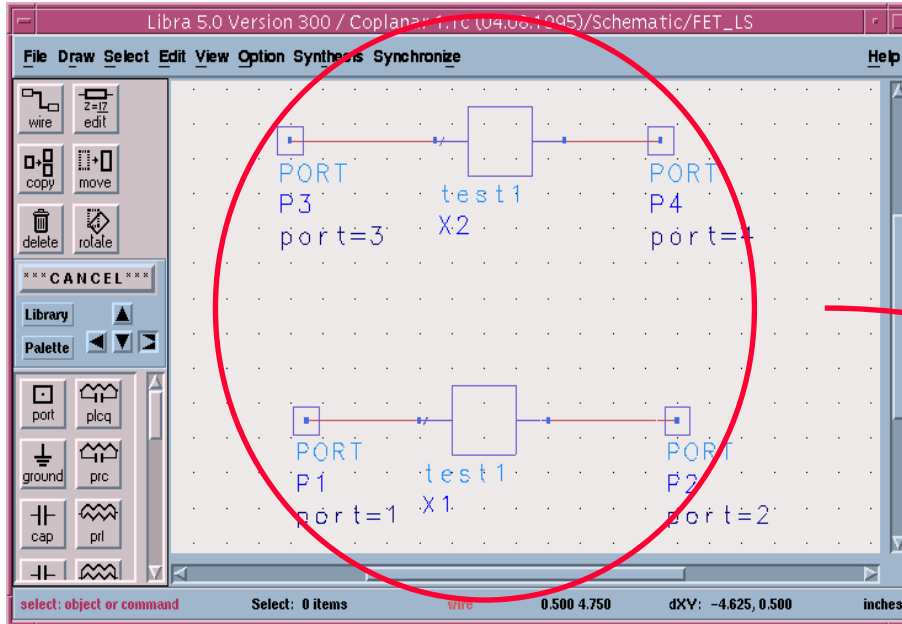Calculation of small signal s-parameters
Using a harmonic balance large signal testbench



Harmonic balance testbench

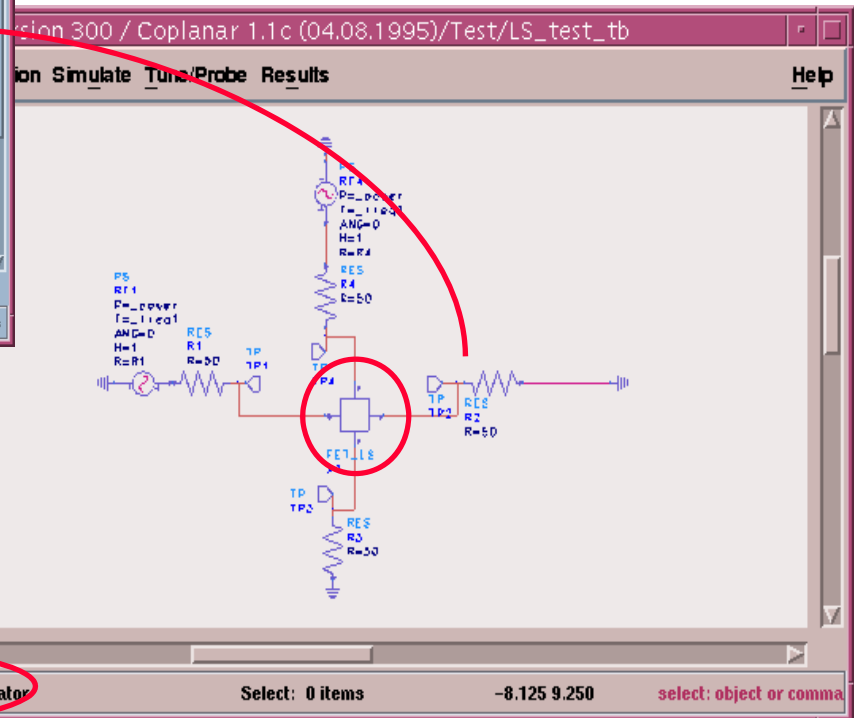

Consistent implementation

```

OUTPUT
EQUATION
OUTEON
_QUTEON
a11=VFC1/7.07+IFC1*7.07*1e-3
a22=VFC4/7.07+IFC4*7.07*1e-3
b11=VFC1/7.07-IFC1*7.07*1e-3
b22=VFC4/7.07-IFC4*7.07*1e-3
b21=VFC2/7.07-IFC2*7.07*1e-3
b12=VFC3/7.07-IFC3*7.07*1e-3
s11=20*log(b11/a11)
s11_ang=b11/a11
s22=20*log(b22/a22)
s22_ang=b22/a22
s21=20*log(b21/a11)
s21_ang=b21/a11
s12=20*log(b12/a22)
s12_ang=b12/a22
    
```


VFC1	IFC1	VFC2	IFC2	VFC3	IFC3
TP1 ID=TP1	ELEM=R1	TP1 ID=TP2	ELEM=R2	TP1 ID=TP3	ELEM=R3
TP2 ID=gnd	PIN=1	TP2 ID=gnd	PIN=1	TP2 ID=gnd	PIN=1
H1=1	H1=1	H1=1	H1=1	H1=1	H1=1
H2=0	H2=0	H2=0	H2=0	H2=0	H2=0
H3=0	H3=0	H3=0	H3=0	H3=0	H3=0

VFC4	IFC4
TP1 ID=TP4	ELEM=R4
TP2 ID=gnd	PIN=1
H1=1	H1=1
H2=0	H2=0
H3=0	H3=0


NH	Pout_RF	Pin	PSPEC
NH	TP1 ID=TP2	TP1 ID=TP1	PSPEC1
VALUE=5	TP2 ID=gnd	TP2 ID=gnd	TP1 ID=TP2
	ELEM=R2	ELEM=R1	TP2 ID=gnd
	H1=1	H1=1	ELEM=R2
	H2=0	H2=0	
	H3=0	H3=0	

FREQUENCY	B1AS1	B1AS2	
FPLAN	B1PLAN	B2PLAN	
value=SWEEP:0:10:40:1	value=STEP:0	value=STEP:2	

Small signal
-50 dBm

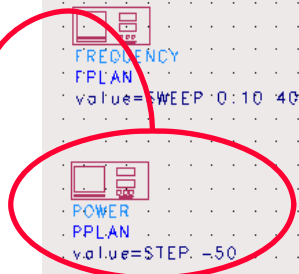


Consistent implementation

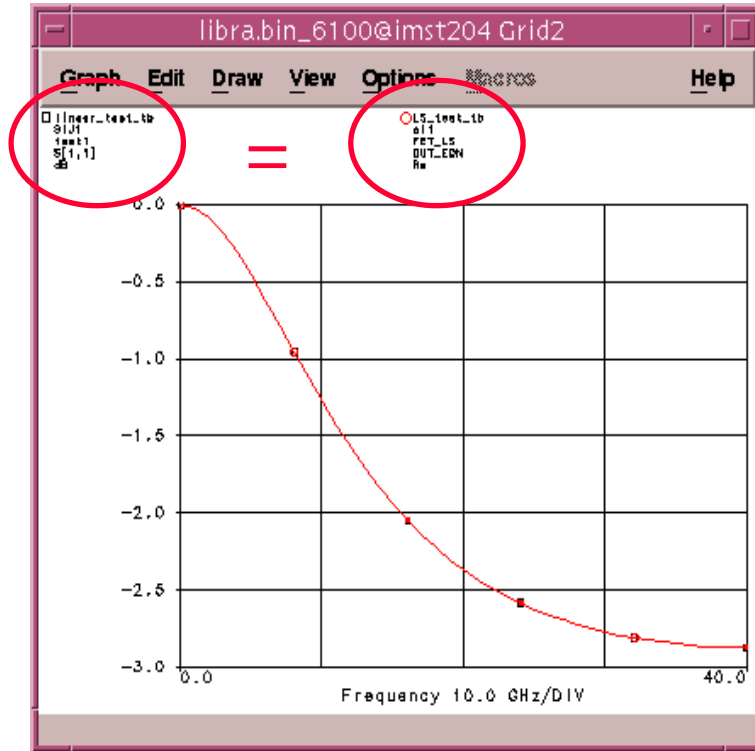

Mag(s_{11}), simulated using Small signal and HB testbench for very low input power (-50 dBm)

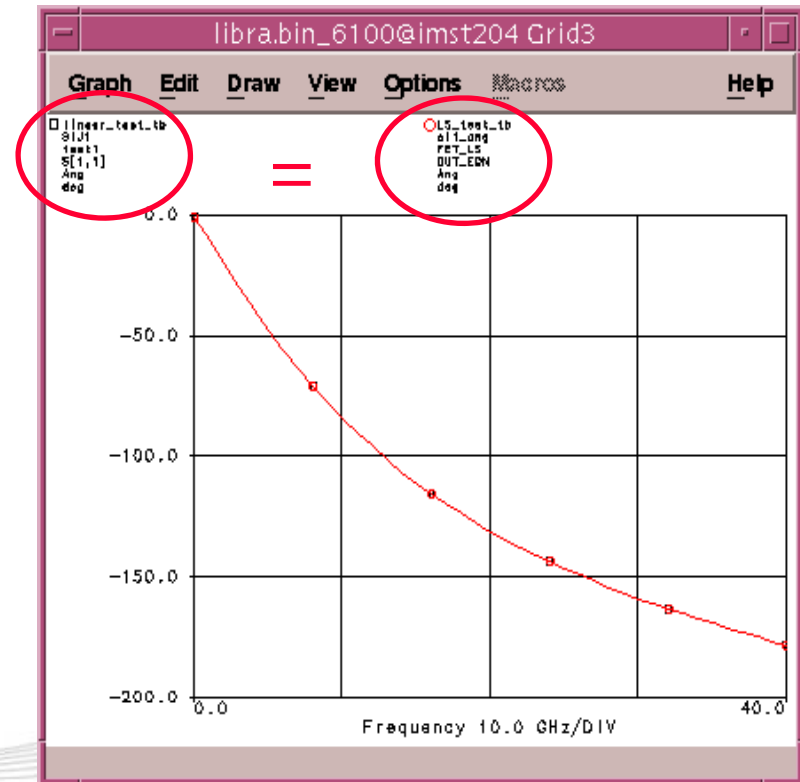Phase(s_{11}), simulated using Small signal and HB testbench for very low input power (-50 dBm)



Needful things

Linearize exp functions

$$f(x) = \begin{cases} \exp(x) & x \leq x_0 \\ mx + b & x > x_0 \end{cases}$$

Function must be continuous at x_0


$$f_1(x_0) = f_2(x_0)$$

$$\left. \frac{df_1}{dx} \right|_{x_0} = \left. \frac{df_2}{dx} \right|_{x_0}$$

$$\Rightarrow \exp(x_0) = mx_0 + b$$

$$m = \exp(x_0)$$
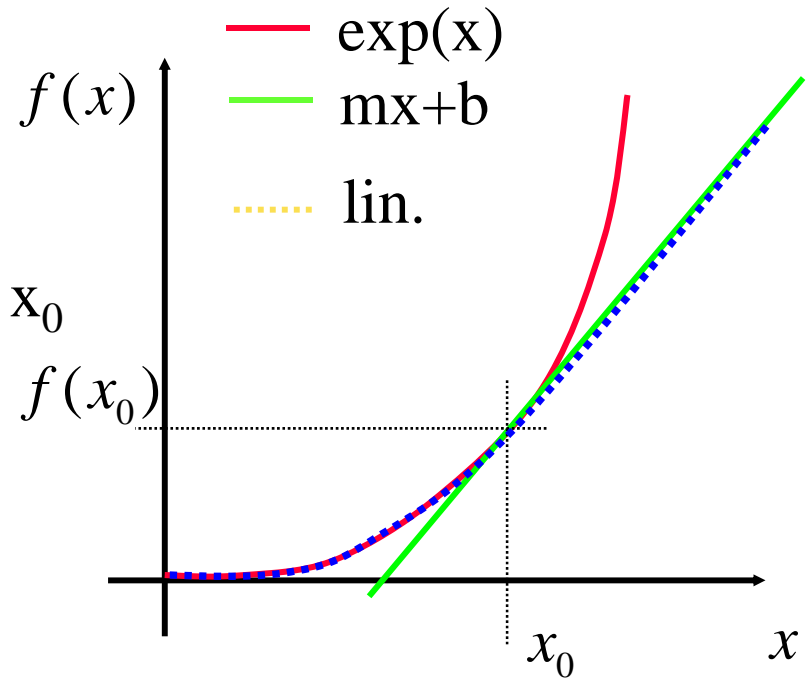
$$\Rightarrow b = \exp(x_0)(1 - x_0) \Rightarrow f_2(x) = \exp(x_0)(x + 1 - x_0)$$



Noise sources

Thermal noise

$$\langle i_{th}^2 \rangle = \frac{4kT_0}{R} \Delta f$$

Popcorn (burst)-
noise

$$\langle i_{burst}^2 \rangle = KB \frac{I_D^{CF}}{1 + \left(\frac{f}{f_{CF}} \right)^2} \Delta f$$

Shot-
noise

$$\langle i_{shot}^2 \rangle = 2qI_D \Delta f$$


Channel noise

$$\langle i_c^2 \rangle = \frac{8kTg_m}{3} \Delta f$$

1/f (flicker)-
noise

$$\langle i_{1/f}^2 \rangle = KF \frac{I_D^{AF}}{f^{FFE}} \Delta f$$

Noise equivalent circuit

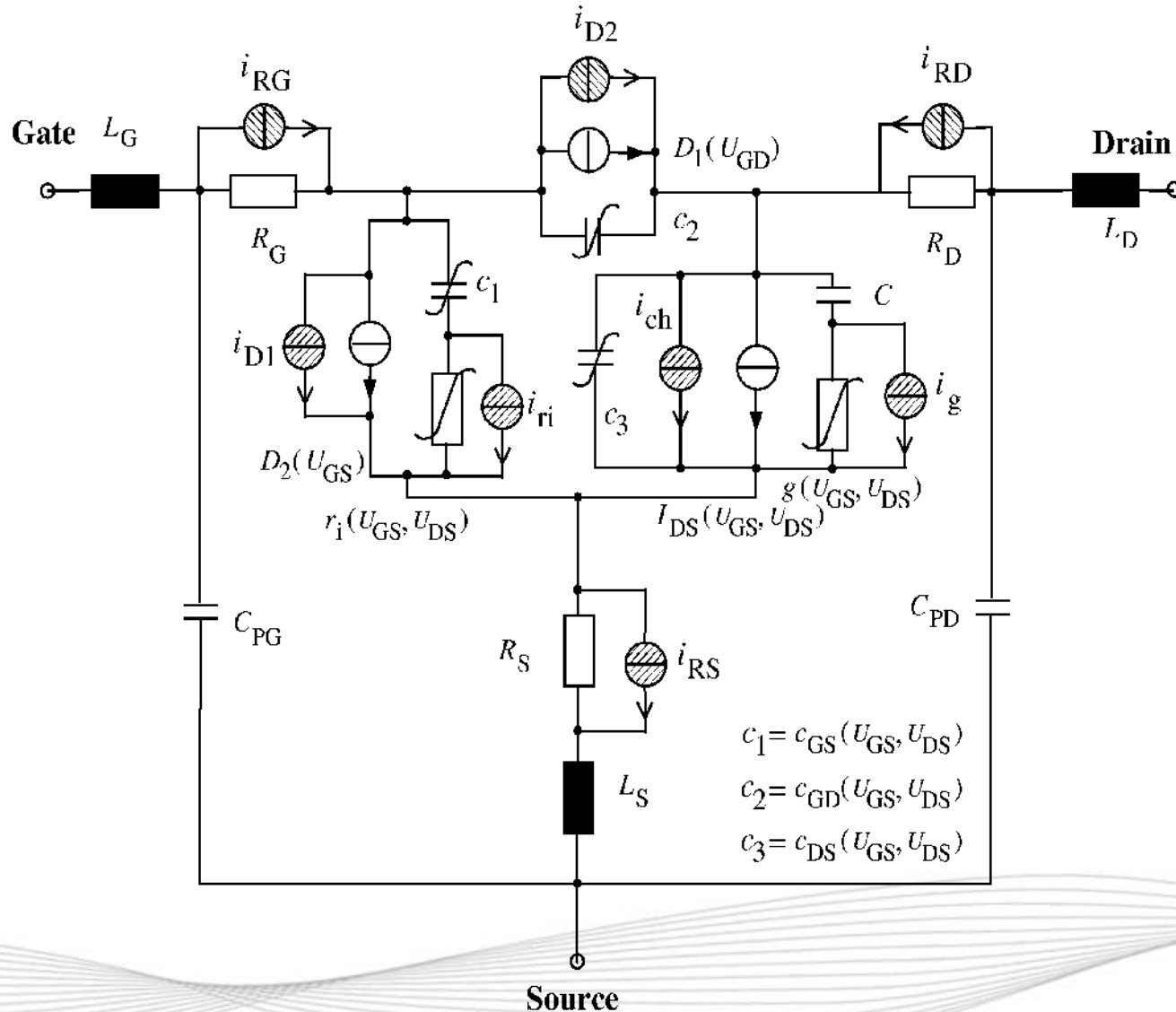

Noisy 2-ports

Transformation matrix


$$[T]^{(y \rightarrow a)} = \begin{bmatrix} 0 & -\frac{1}{y_{21}} \\ 1 & -\frac{y_{11}}{y_{21}} \end{bmatrix}$$

Noise matrix

$$\begin{bmatrix} v_i^{(a)} \\ i_o^{(a)} \end{bmatrix} = [T]^{(y \rightarrow a)} \begin{bmatrix} i_i^{(y)} \\ i_o^{(y)} \end{bmatrix}$$

input (green circle)
output (blue circle)


Transformation of noise sources.

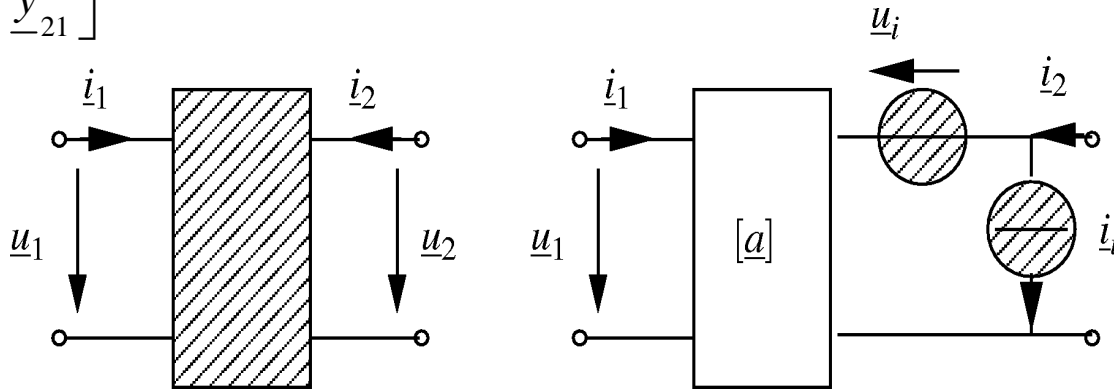

Correlation matrix, calculation of noise power

$$[C]^{(a)} = \frac{1}{4kT\Delta f} \left(\begin{bmatrix} v_i \\ i_i \end{bmatrix} \begin{bmatrix} v_i^* & i_i^* \end{bmatrix} \right)$$

Separation of noise sources

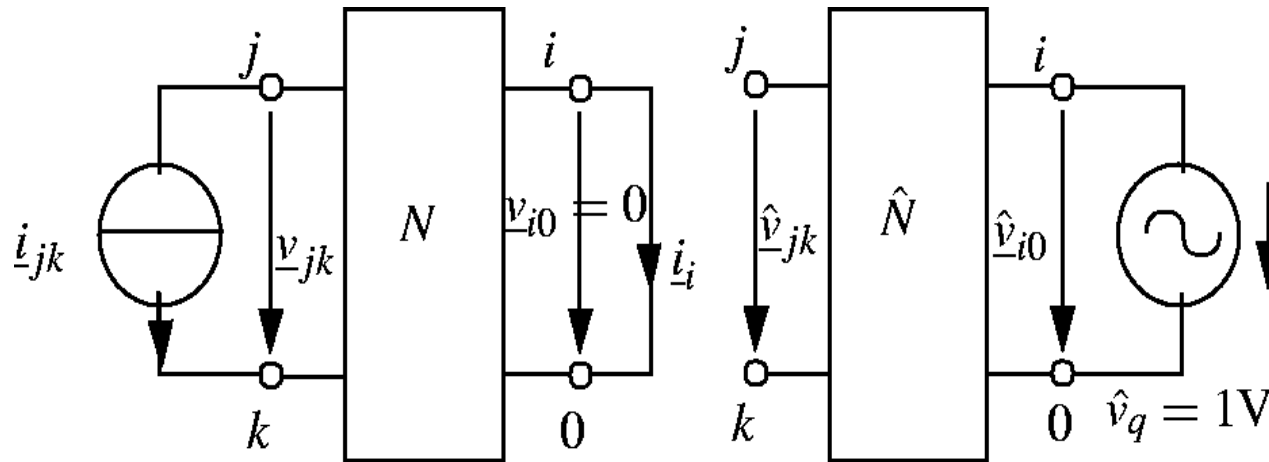

Calculation of transformation function


Network N
Y-Matrix

Adjoint network
transposed Y-Matrix

Current transforming function

$$\alpha_{i,jk} = \frac{i_i}{i_{jk}} = -\frac{\hat{v}_{jk}}{\hat{v}_q}$$

FET example

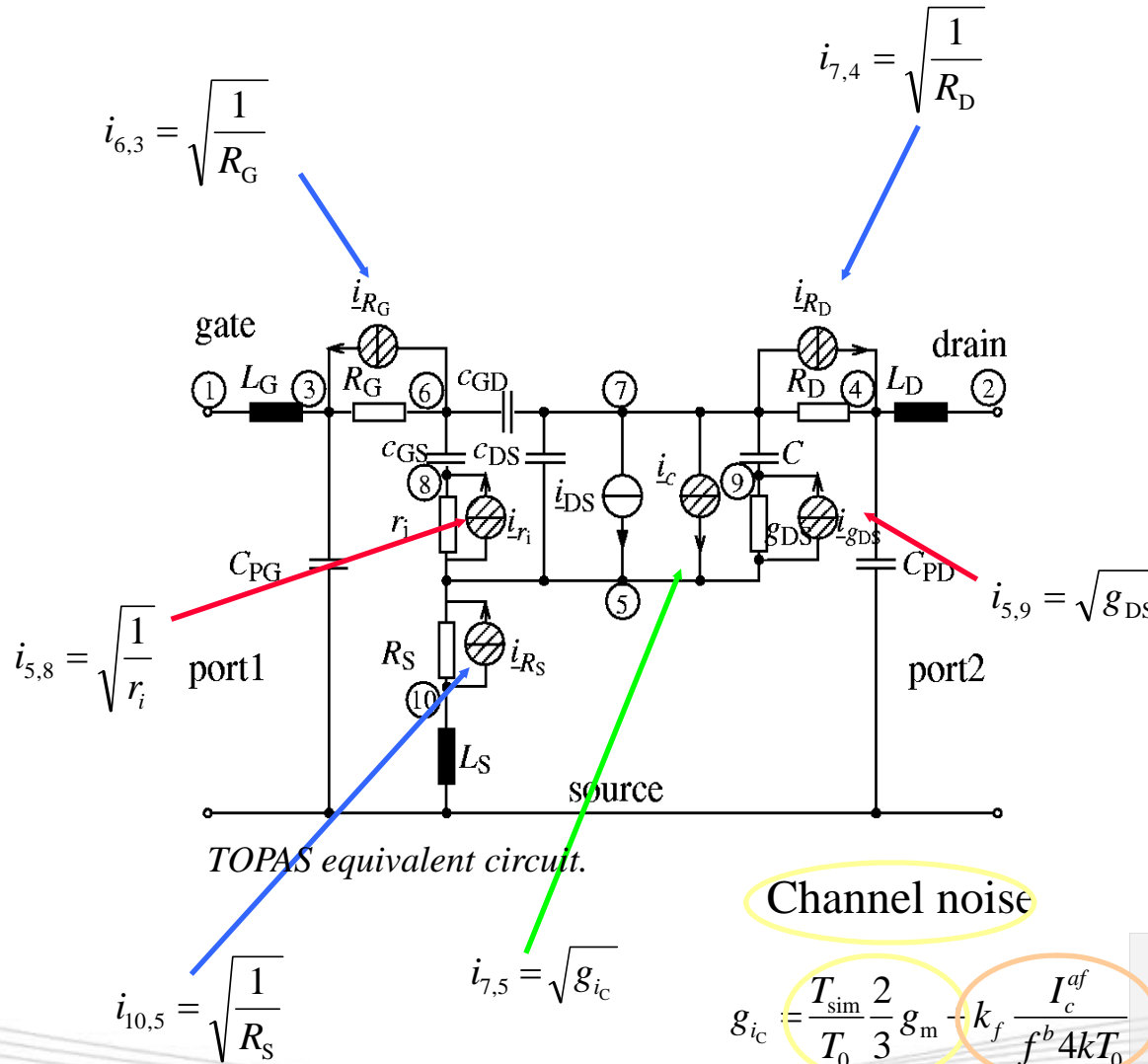

Noise current matrix



$$[i_N] = \sqrt{4kT\Delta f} \cdot \begin{pmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & i_{5,8} & i_{5,9} & 0 \\ 0 & 0 & i_{6,3} & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & i_{7,4} & i_{7,5} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & i_{10,5} & 0 & 0 & 0 & 0 & 0 & 0 \end{pmatrix}$$

Channel noise

$$g_{ic} = \frac{T_{sim}}{T_0} \frac{2}{3} g_m + k_f \frac{I_c^{af}}{f^b 4kT_0}$$

1/f-noise

Tellegen Thorem

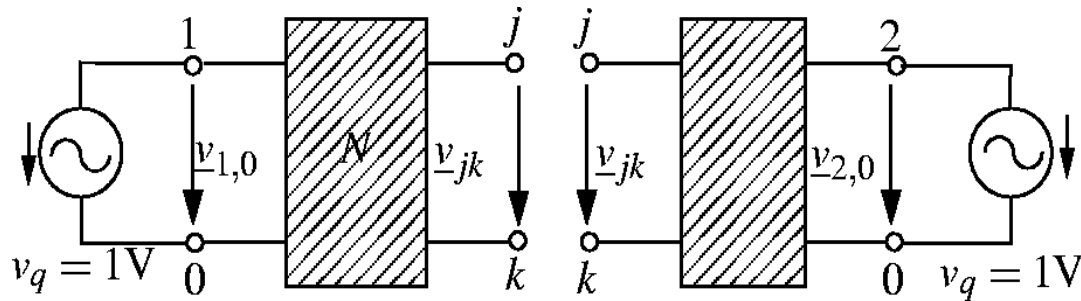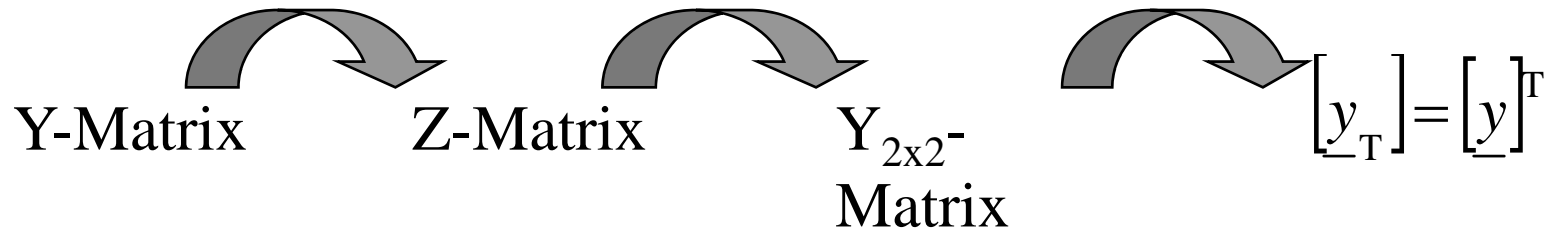

Tellegen Theorem for noisy n-ports


Adjoined network for calculation of transformation function

$$i_{Q_1} = v_q \cdot \underline{y}_{T,2 \times 2_{1,1}} \quad \text{and} \quad i_{Q_2} = v_q \cdot \underline{y}_{T,2 \times 2_{2,2}}$$

Tellegen Theorem

$$\begin{bmatrix} i_{Q1} \\ \vdots \\ i_{Q10} \end{bmatrix} = \begin{bmatrix} y_{T_{1,1}} & \cdots & y_{T_{1,10}} \\ \vdots & \ddots & \vdots \\ y_{T_{10,1}} & \cdots & y_{T_{10,10}} \end{bmatrix} \begin{bmatrix} v_1 \\ \vdots \\ v_{10} \end{bmatrix}$$

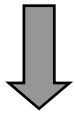
Solving the equation system for the voltages using the Gaussian algorithm



Voltage transformation factor



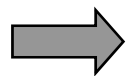One single noise source at Eingang, one at output



$$[T]^{(y \rightarrow a)} = \begin{bmatrix} 0 & -\frac{1}{y_{2 \times 2_{21}}} \\ 1 & -\frac{y_{2 \times 2_{11}}}{y_{2 \times 2_{21}}} \end{bmatrix}$$



1 current source, 1 voltage source at output

Correlation matrix

$$F = 1 - \frac{T_{\text{sim}}}{T_0} \frac{|y_{\underline{G}}|^2 C_{11}^{(a)} + C_{22}^{(a)} + 2\Re\{y_{\underline{G}} C_{12}^a\}}{g_G}$$

$$R_n = \frac{T_{\text{sim}}}{T_0} C_{11}^a$$

Korrelationsmatrix


$$[\underline{C}]^{(a)} = [\underline{T}]^{(y \rightarrow a)} [\underline{C}]^{(y)} [\underline{T}]^{(y \rightarrow a)+}$$

$$V_{\text{NF}} [\text{dBm}/\sqrt{\text{Hz}}] =$$

$$20 \log \left(\sqrt{\frac{T_{\text{sim}}}{T_0} \cdot i_0 i_0^* \frac{50\Omega}{50\Omega \Re(y_{\underline{2} \times \underline{2} 22}) + 1}} \cdot 1000 \right)$$


$$\Gamma_{G_{\text{opt}}} = \frac{1 - y_{\underline{G}_{\text{opt}}} Z_0}{1 + y_{\underline{G}_{\text{opt}}} Z_0}$$

Verifications

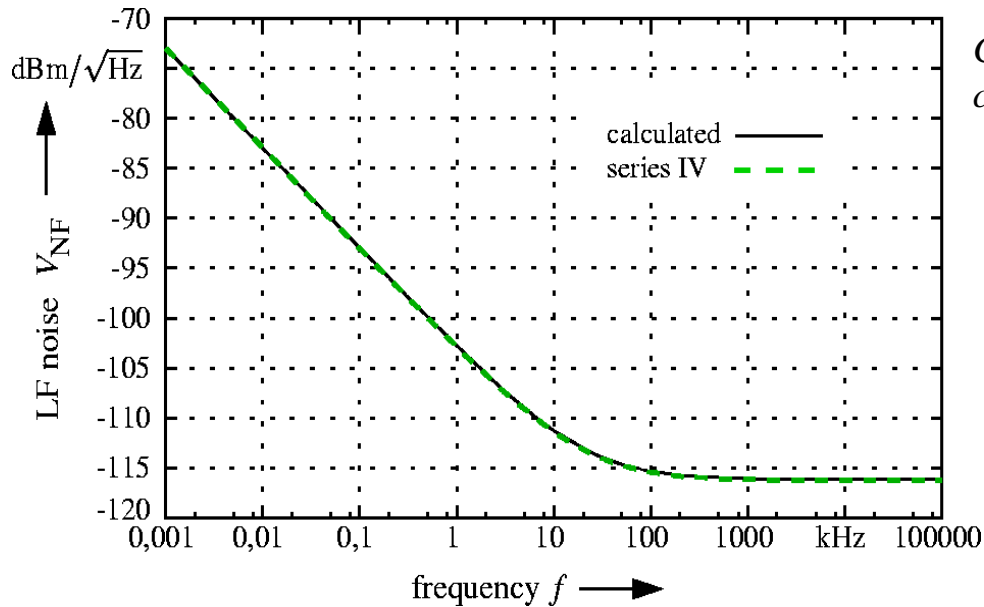


Calculation of $1/f$ noise..Simulation in comparison to calculation using the proposed algorithm.

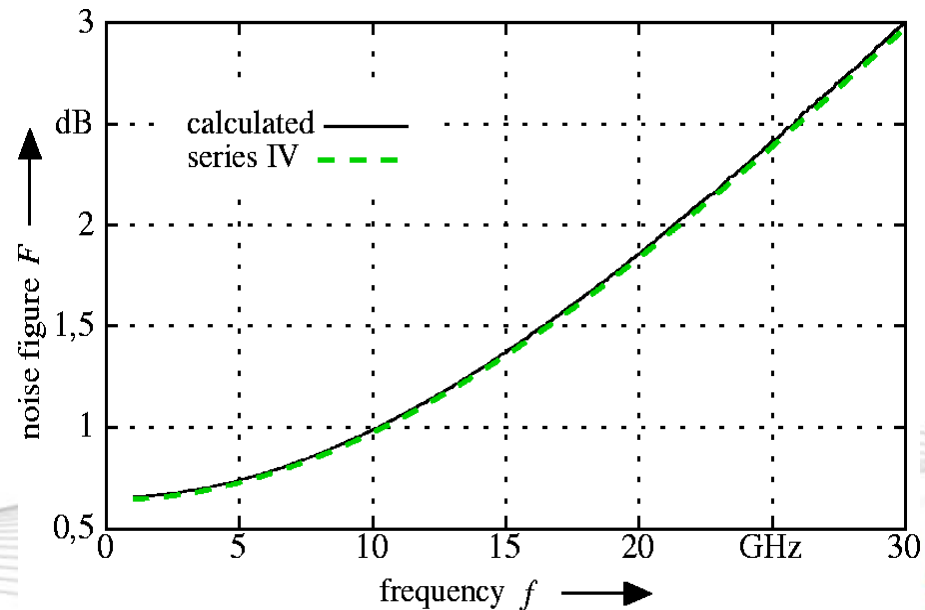Calculation of noise figure NF. Comparison of simulation and calculation.




Verifications

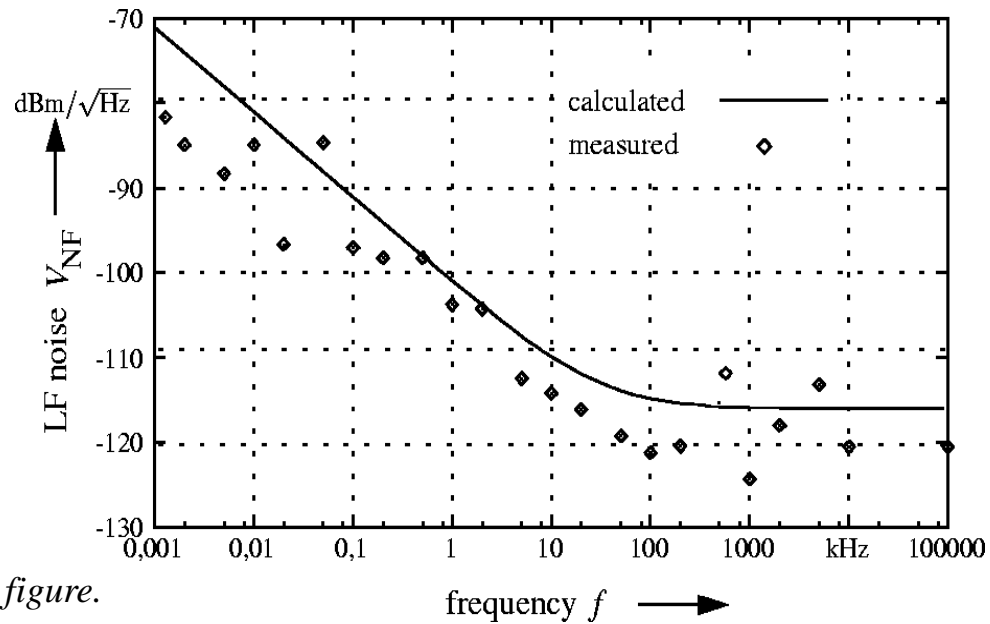


Simulation and measurement of minimum noise figure.


Simulation and measurement of 1/noise.

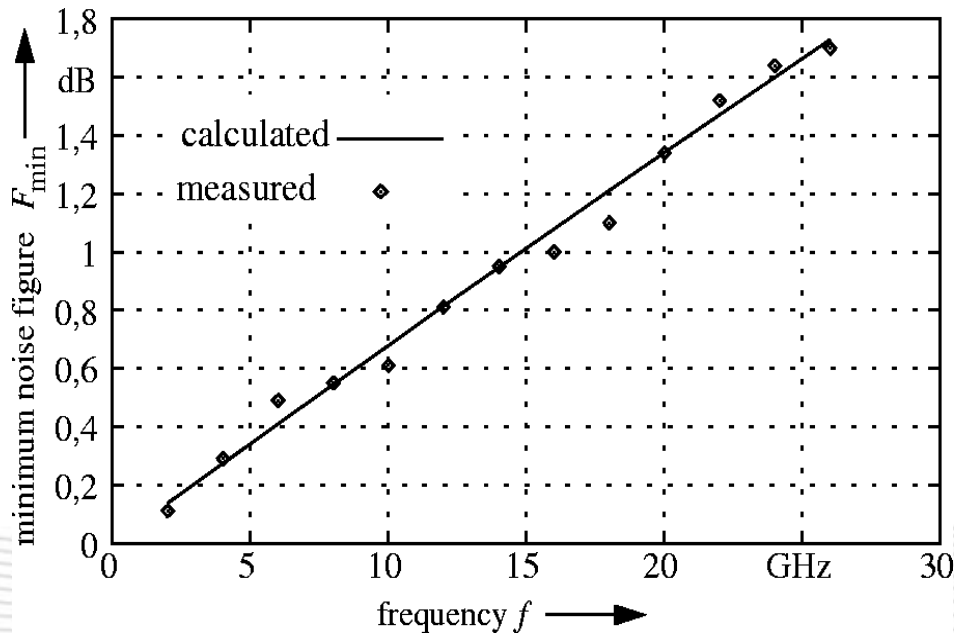

Verifications

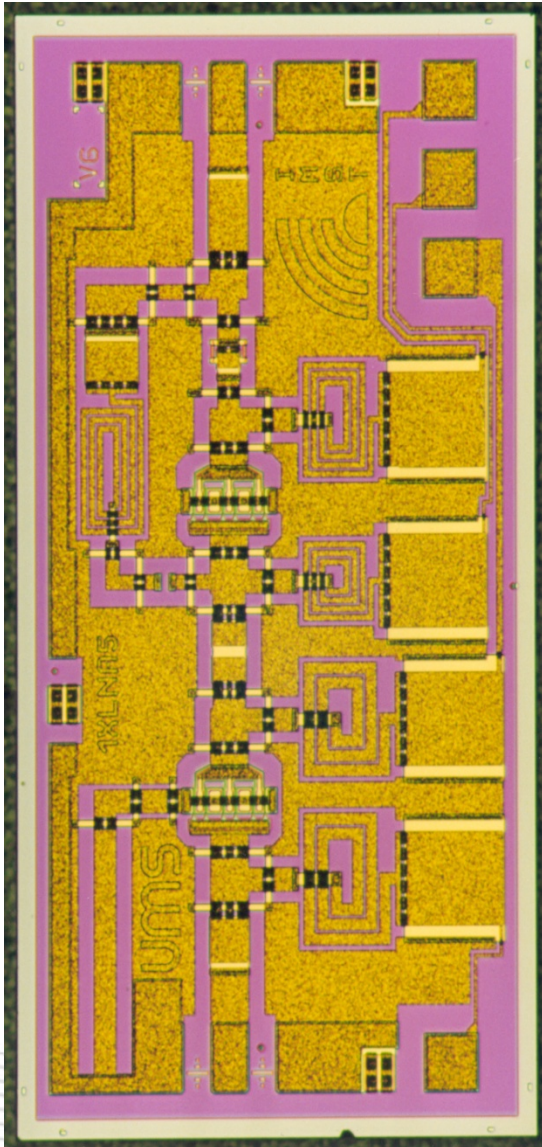


Realized LNA

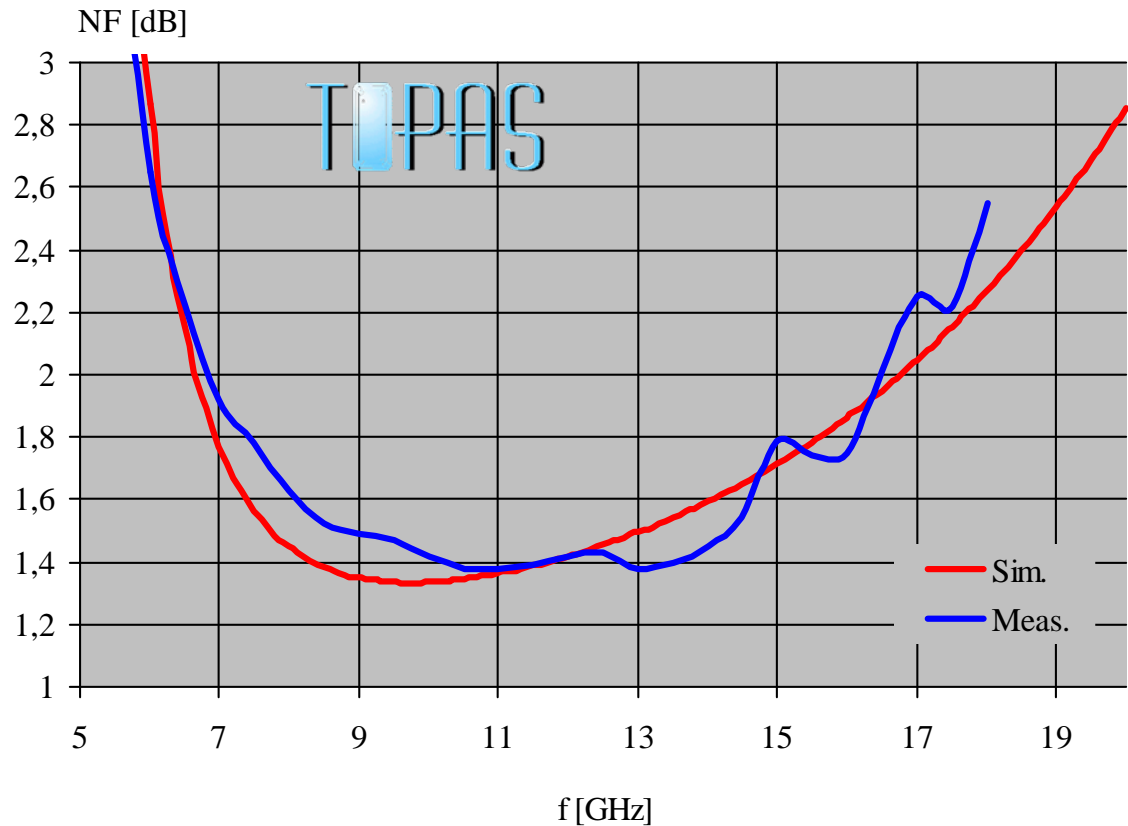

Minimum noise figure, simulation versus measurement.

Verifications

UMS 4x50 μm
HEMT


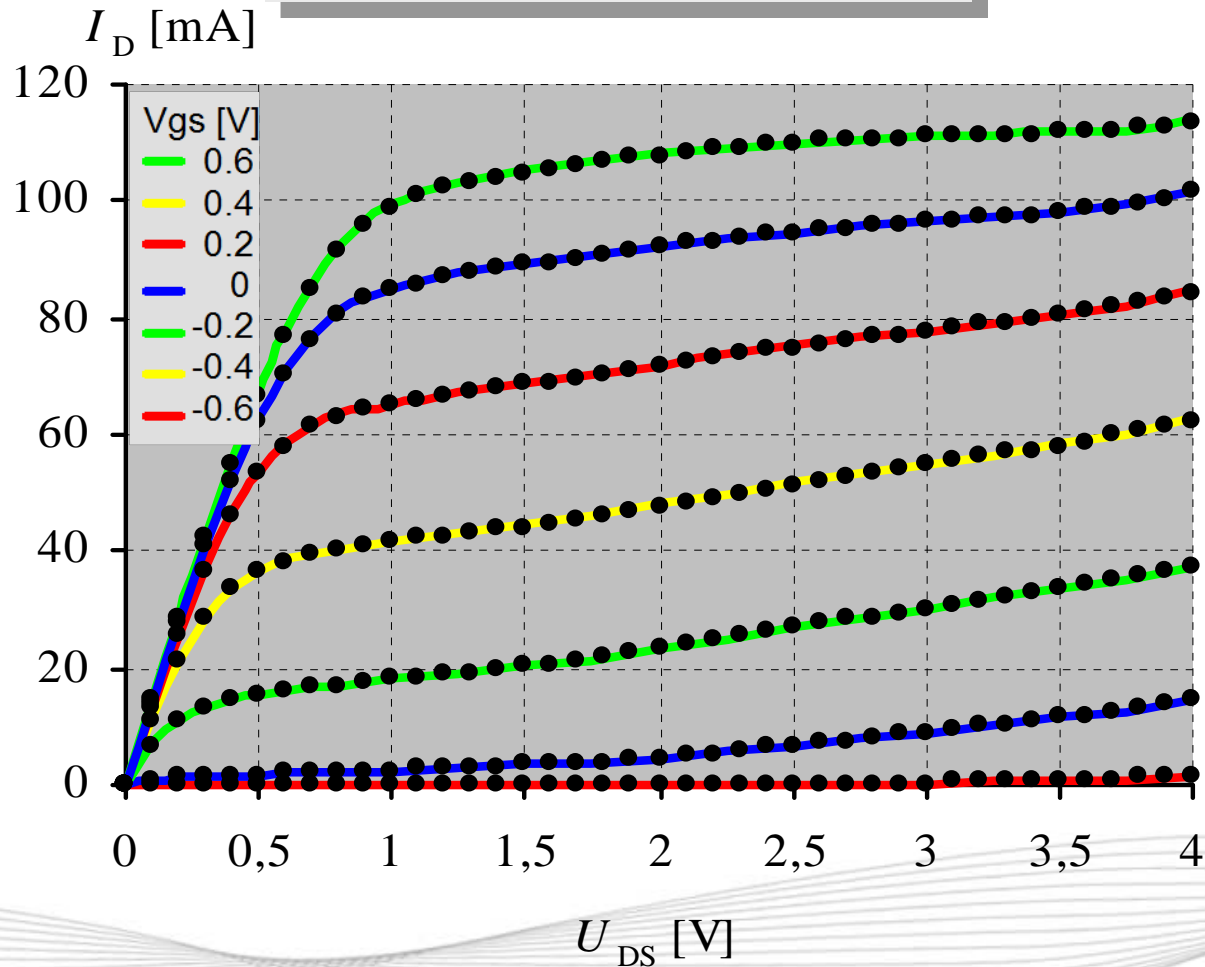


Verifications

Deviations
6x20 μm HEMT

4x50 μm ↗ 8x75 μm
 $V_{GS} = 0 \text{ V}$, $V_{DS} = 2 \text{ V}$



Fehler

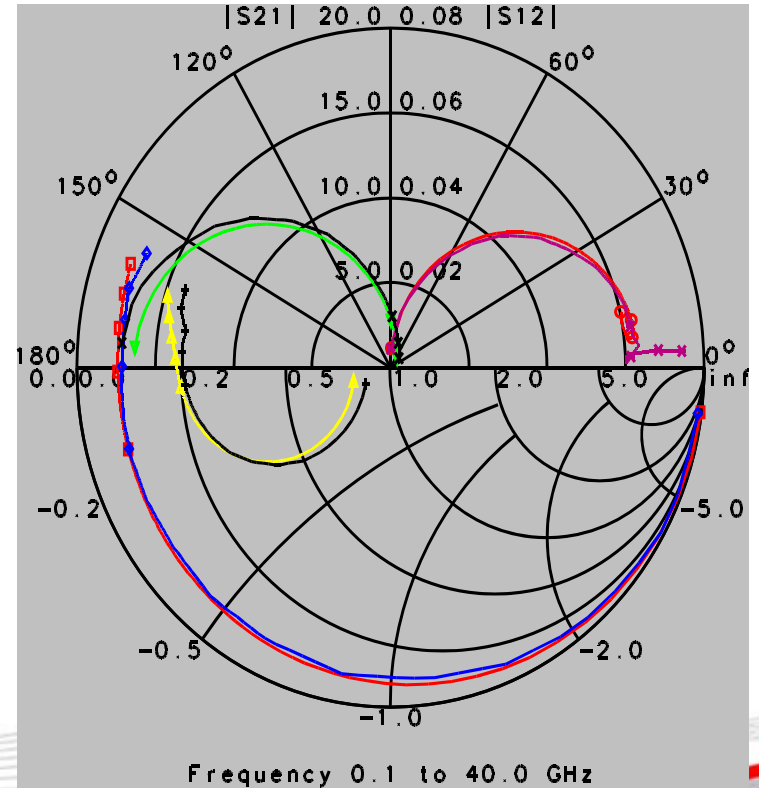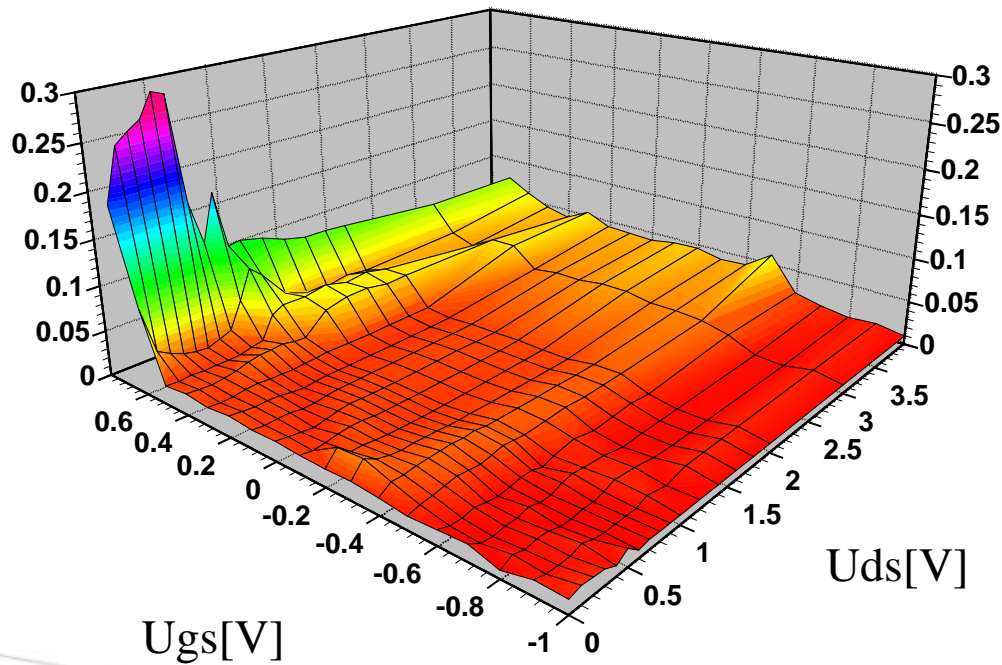

Verifications


4x50 μm ↗ 2x40 μm
 $V_{GS} = 0 \text{ V}$, $V_{DS} = 0 \text{ V}$

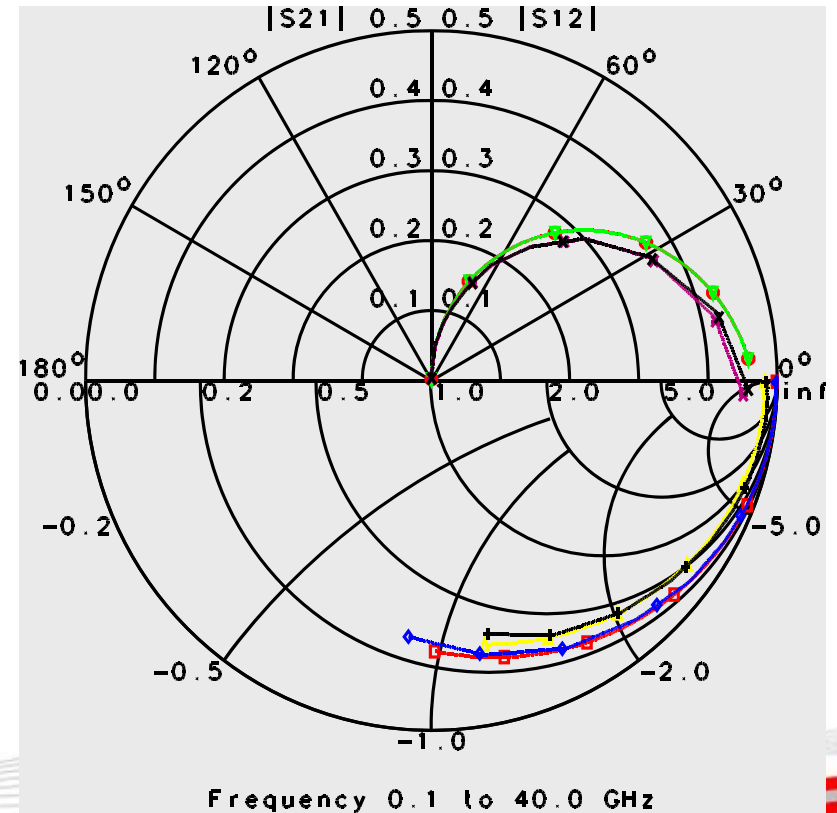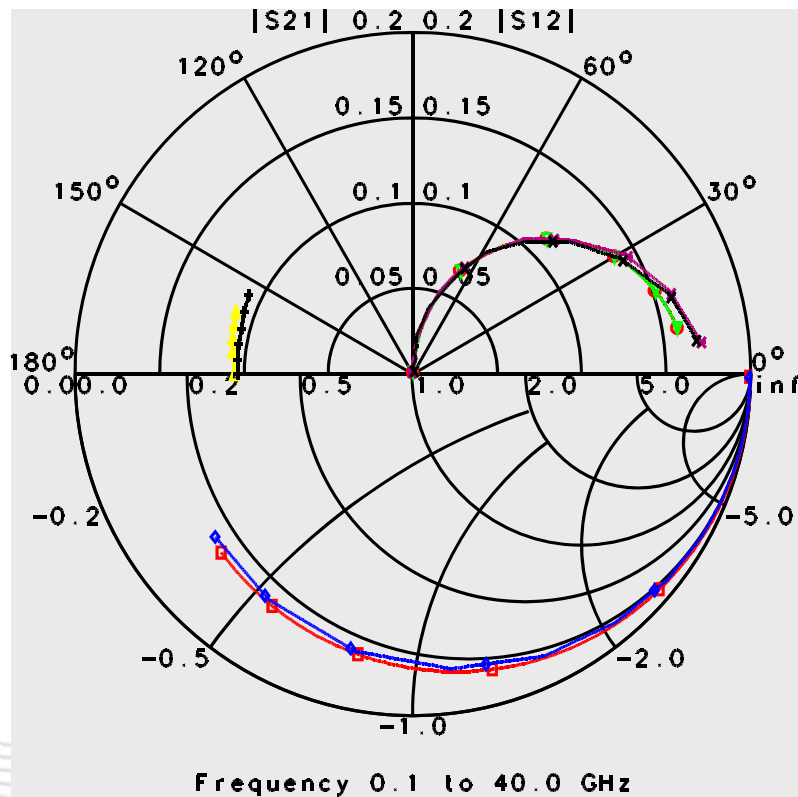4x50 μm ↗ 2x40 μm
 $V_{GS} = -0.8 \text{ V}$, $V_{DS} = 2 \text{ V}$




Verifications

Comp 1x600 2.1 GHz , 26 V, 2.1 mA

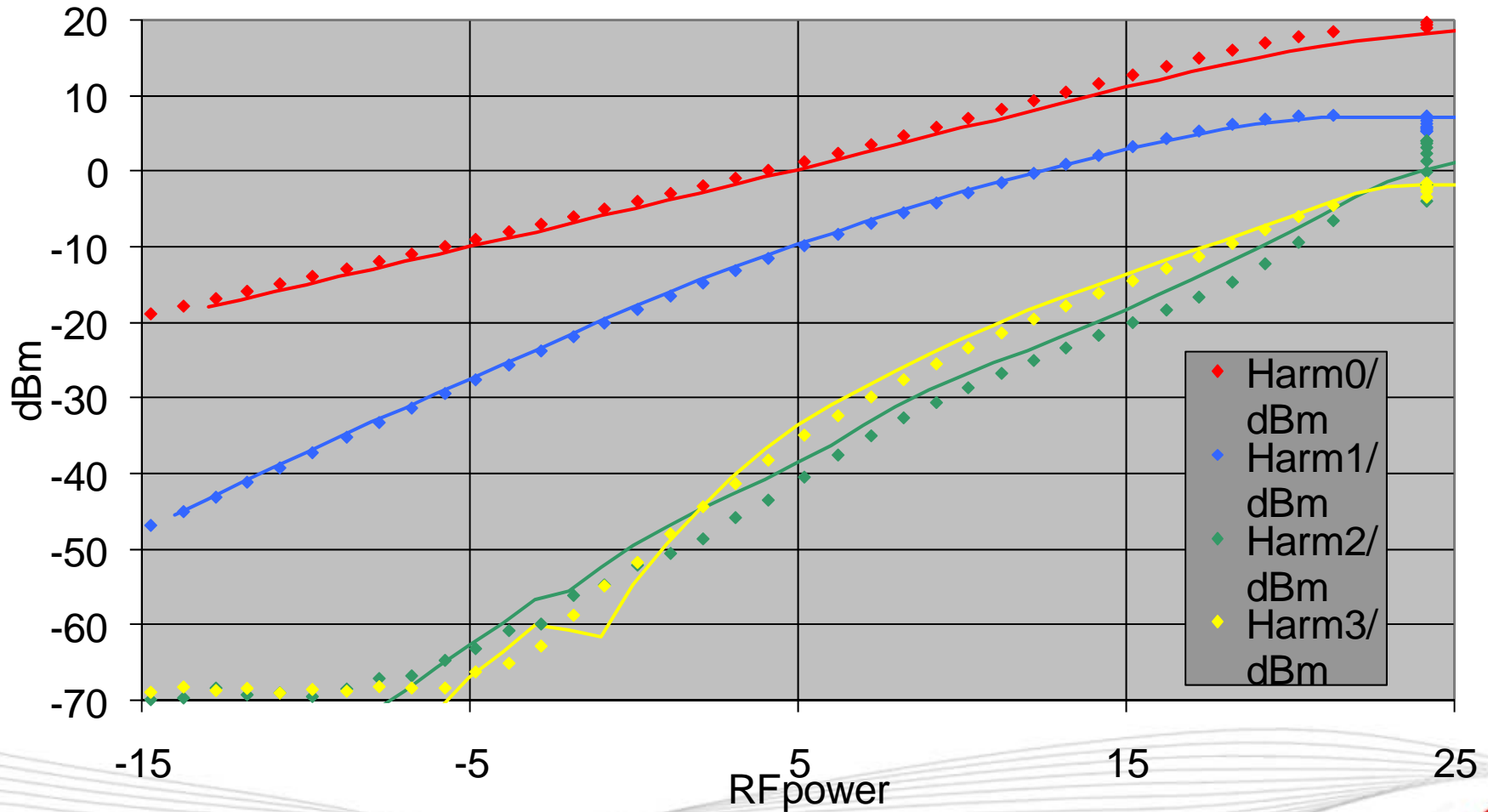


Verifications

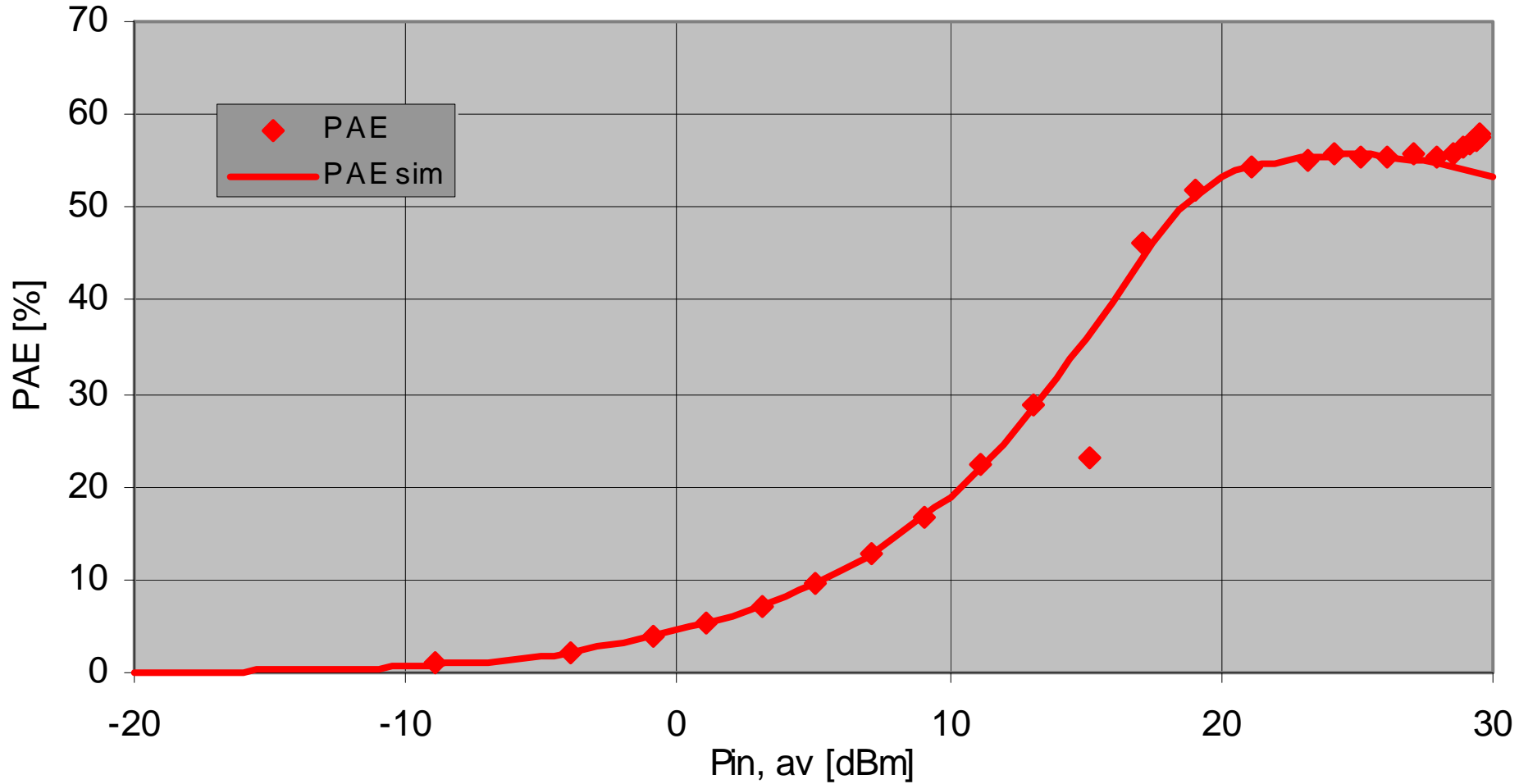PAE, 600um LDMOS device, class B bias, matched, $f = 2.0$ GHz





Verifications

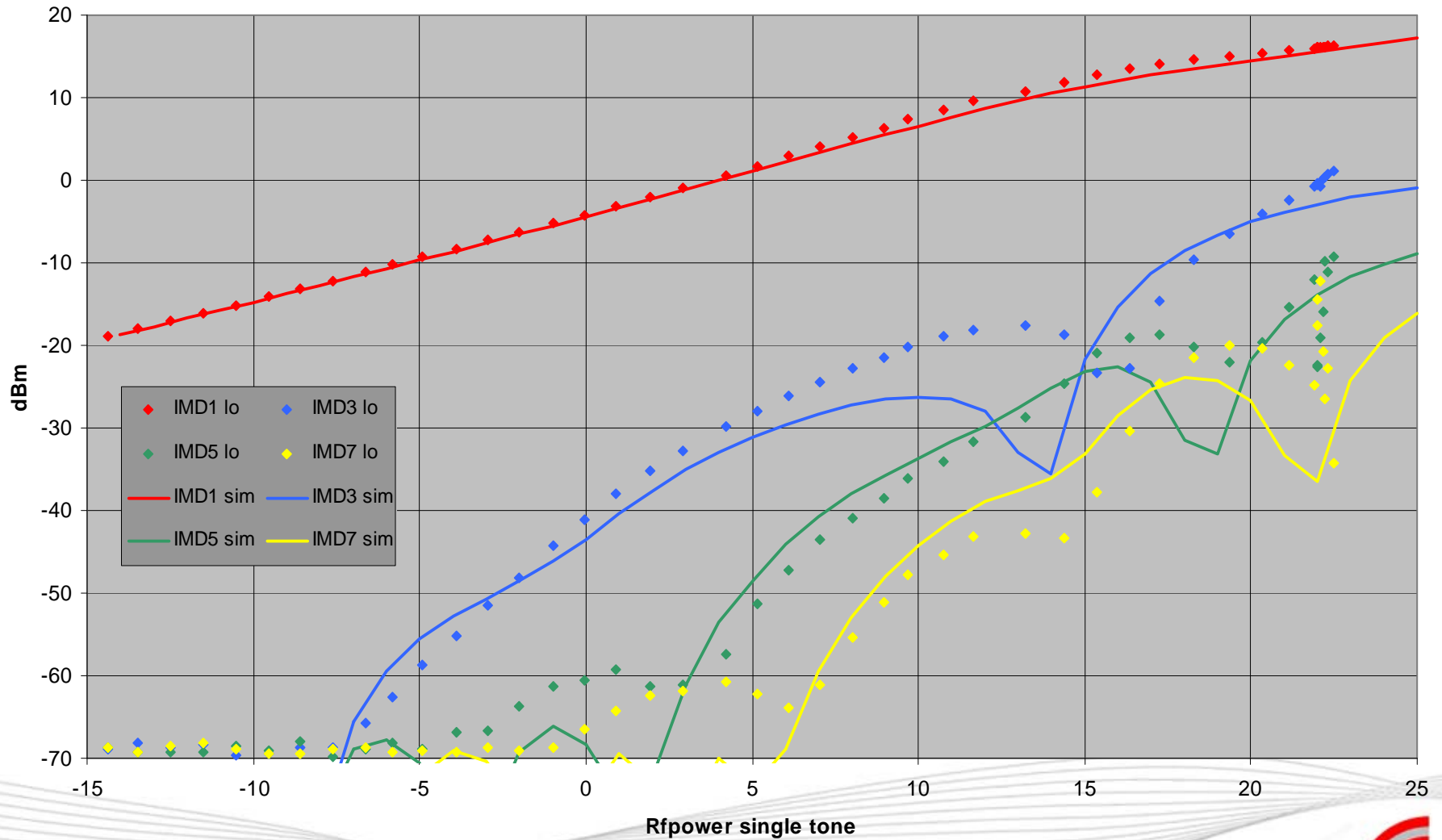IMD 6x100 1.8 GHz, 2 MHz offset, 26 V, 2.1 mA



Verifications


Times 5 multiplier

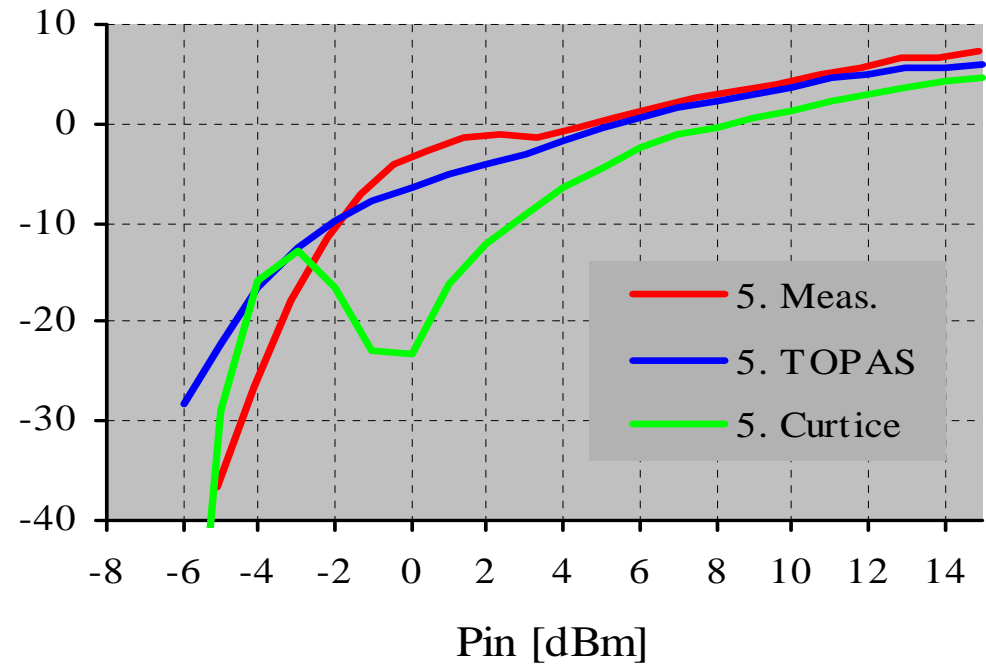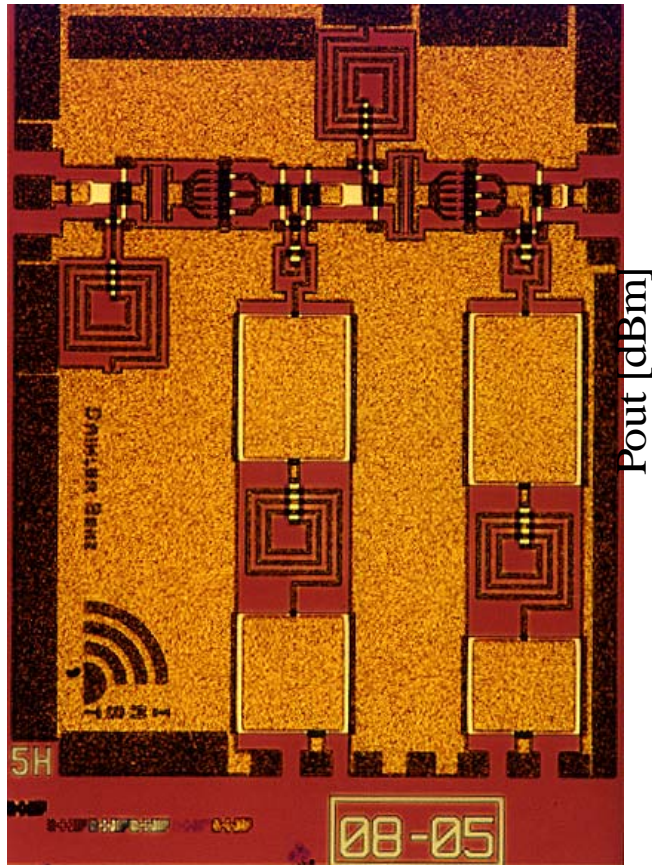



Oscillations


"FETplot.dc"

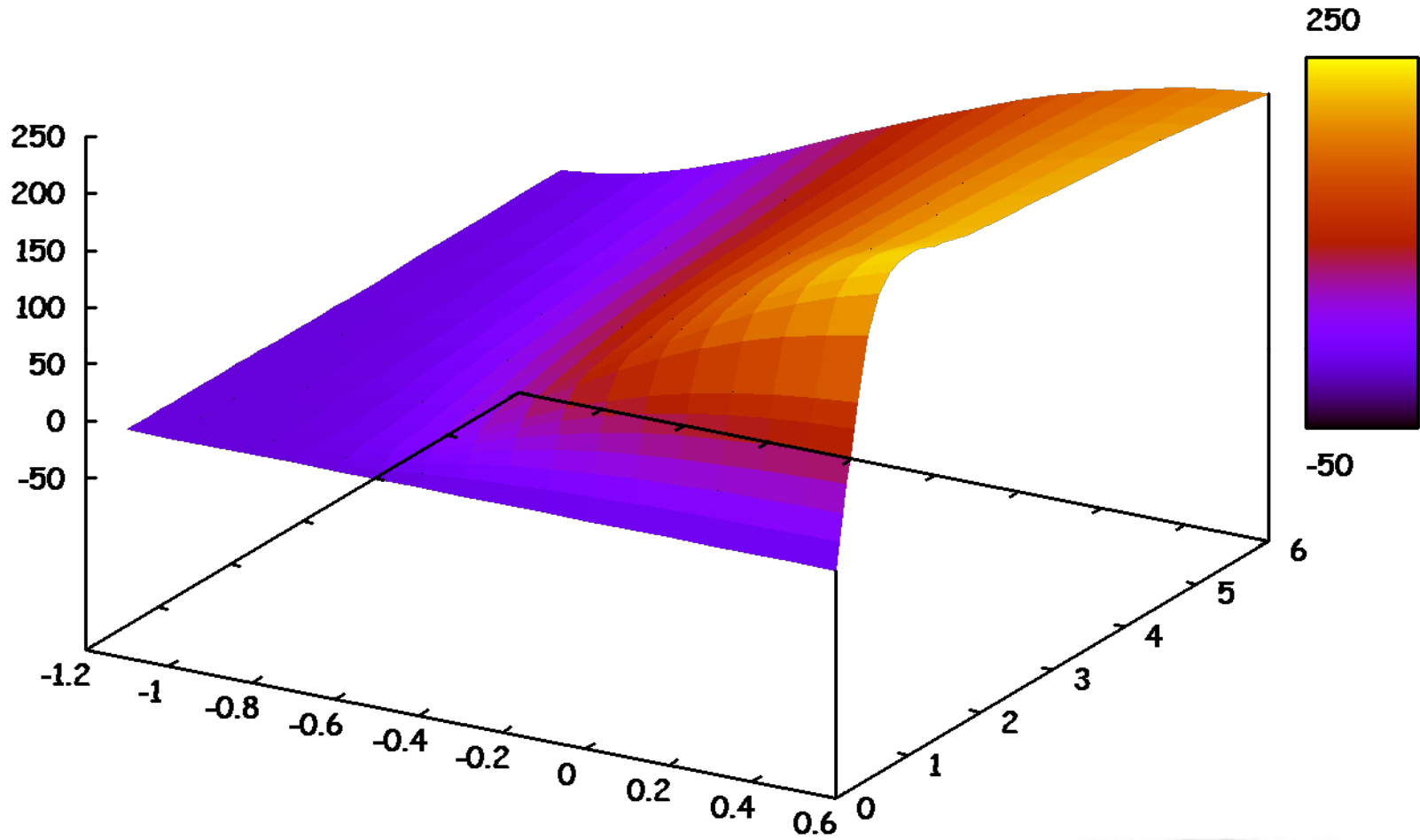



Oscillations


"Cgsintr.dat"

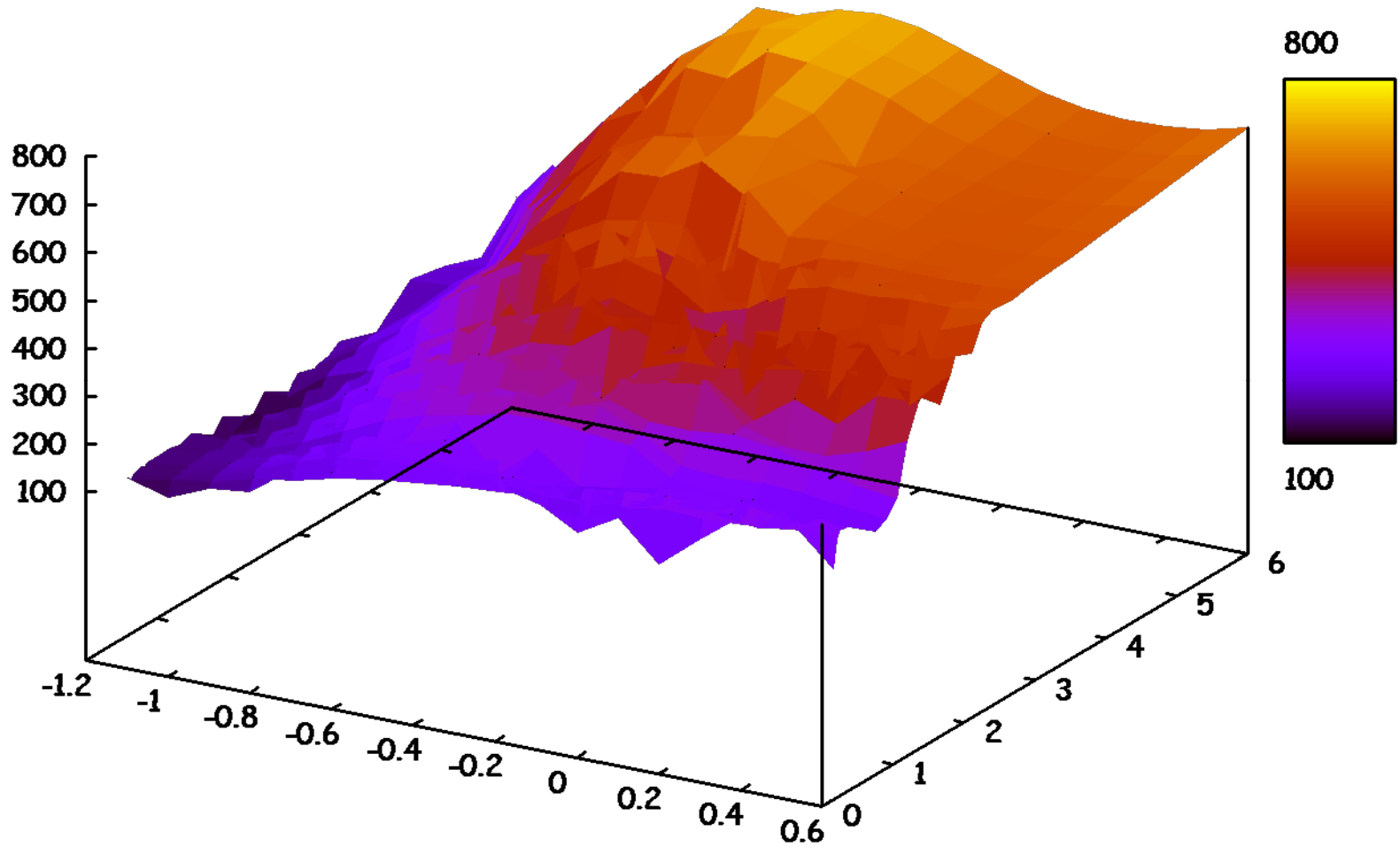



Oscillations


"FETplot.dc"

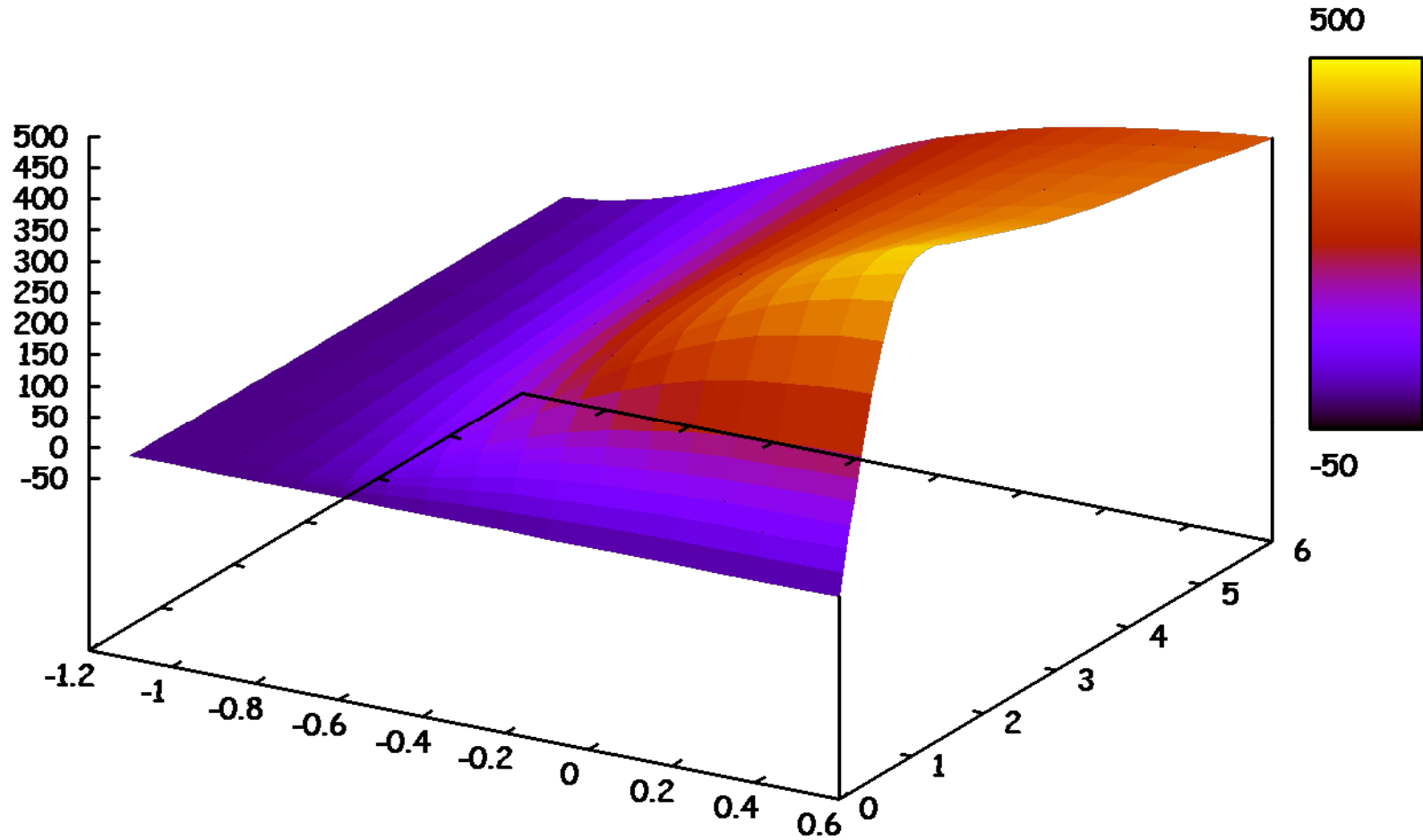



Oscillations


"Cgsintr.dat" u 2:1:3

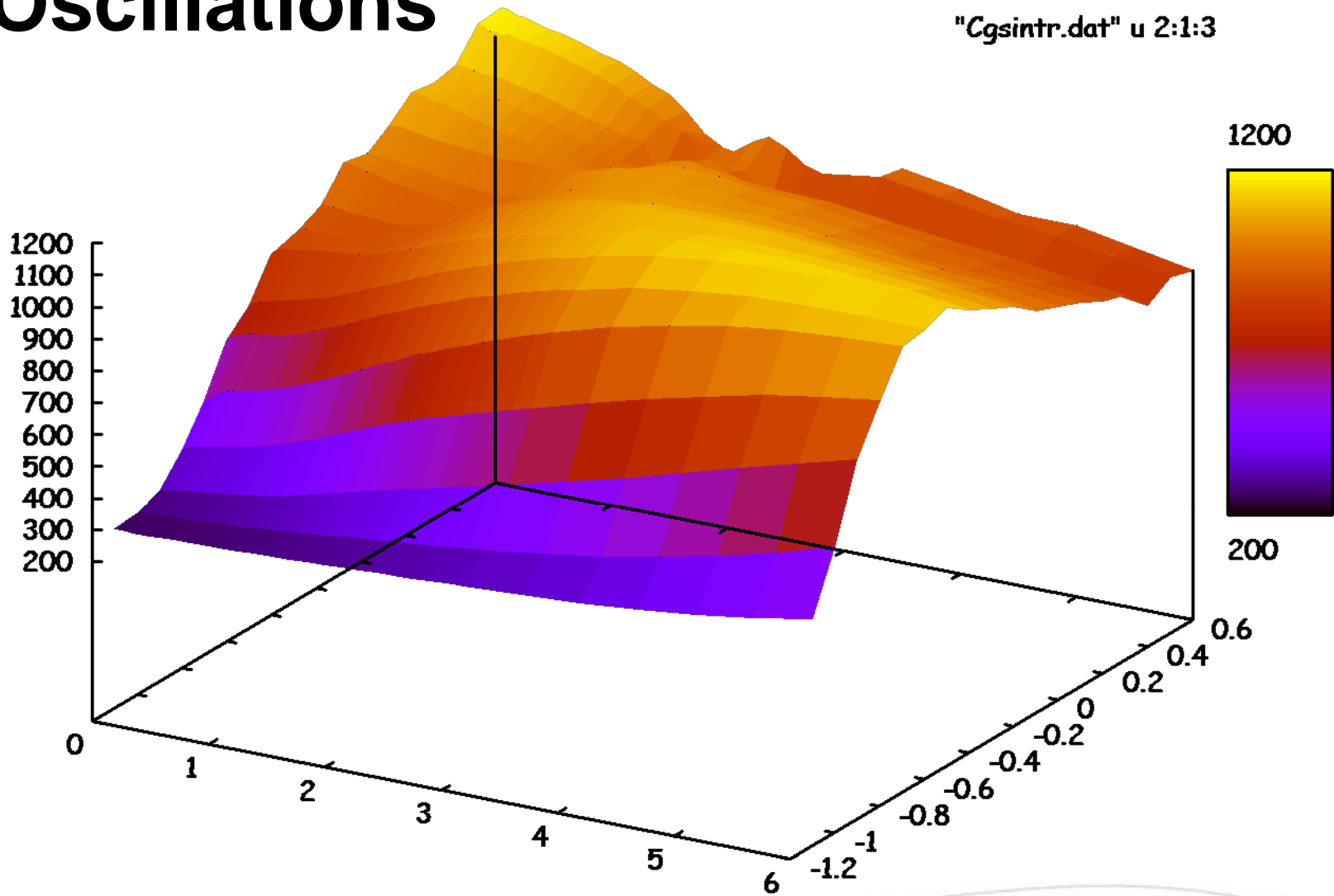



Oscillations


"Riintr.dat"

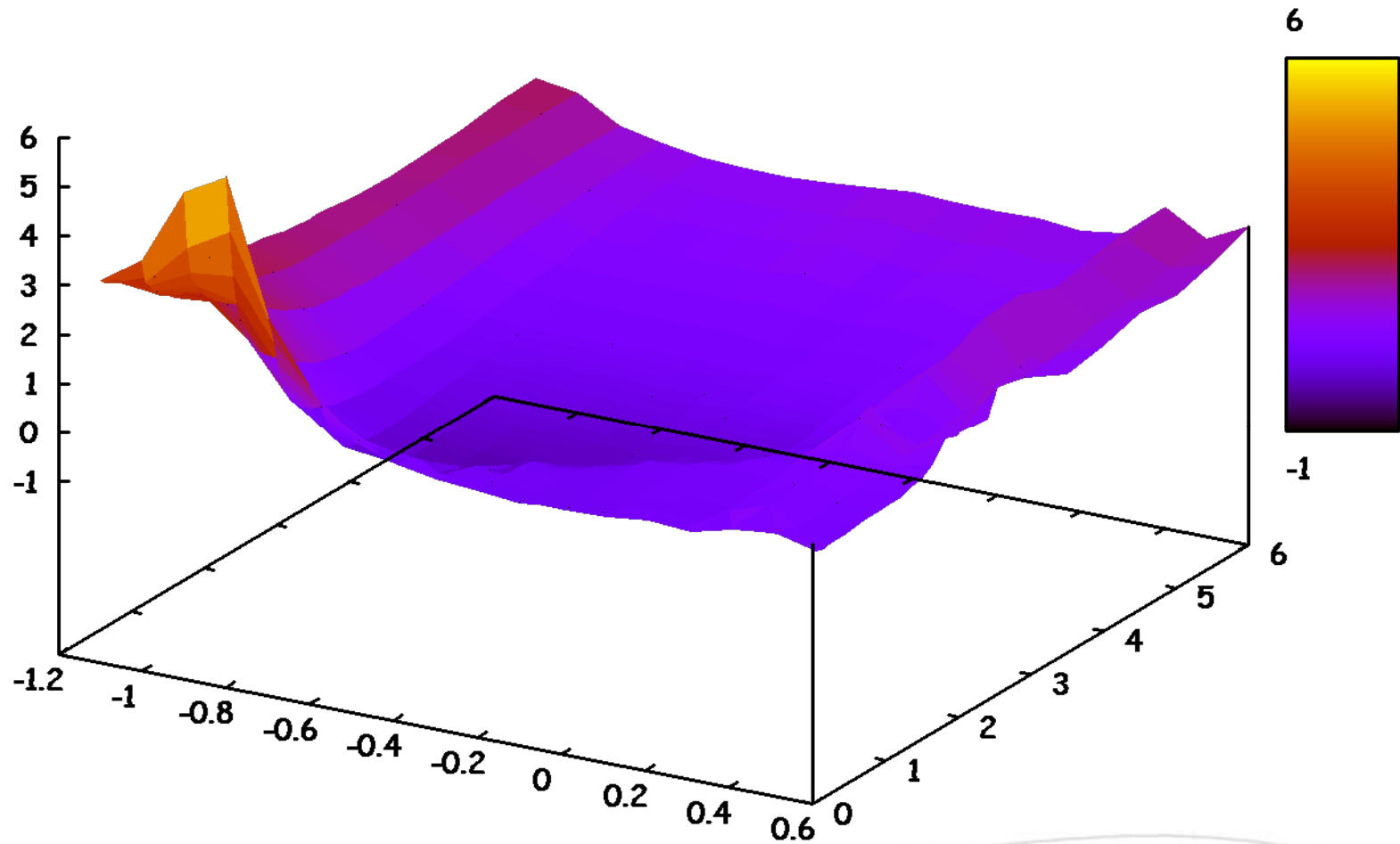




Oscillations


"Rintr.dat"

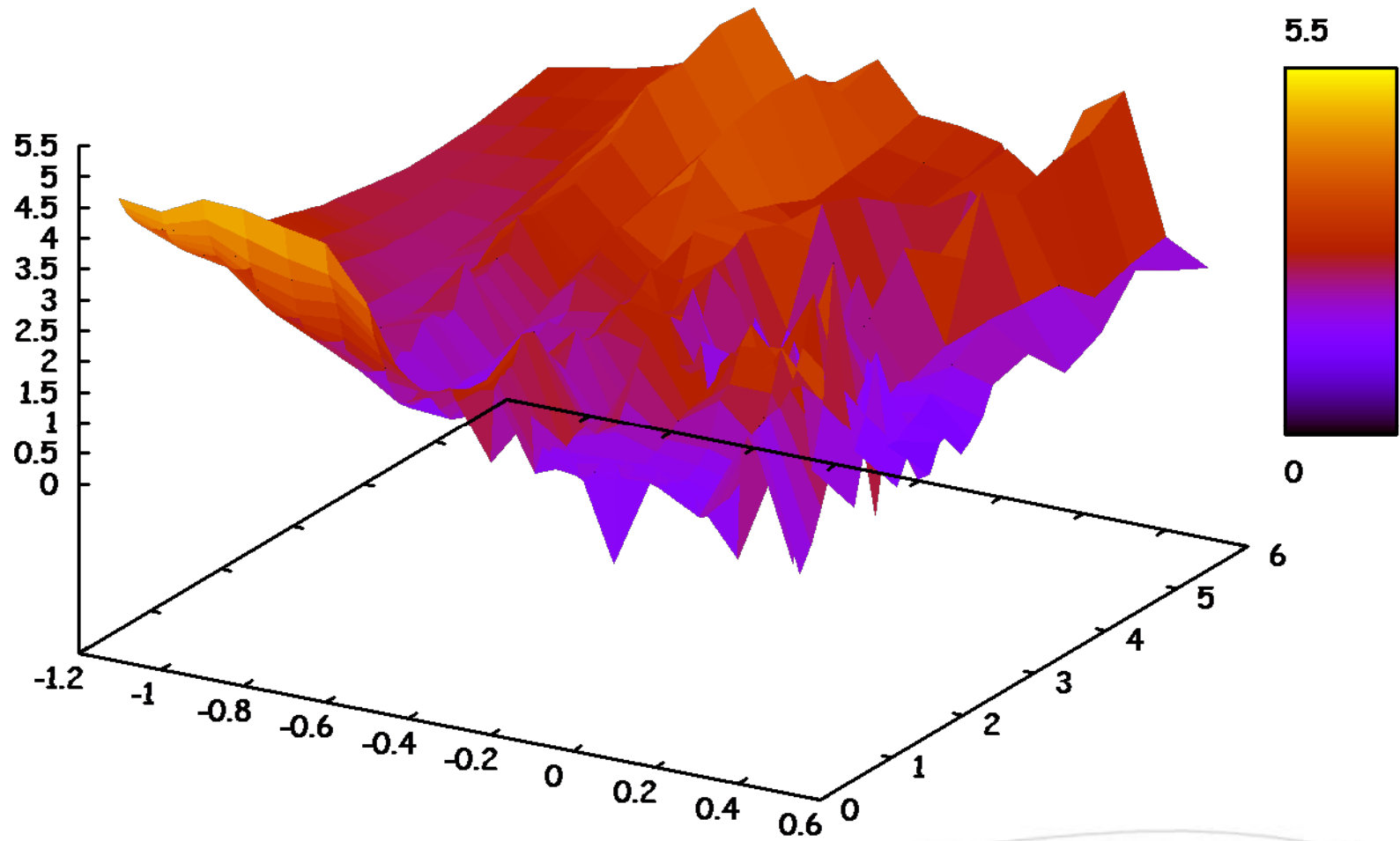


Switching problems

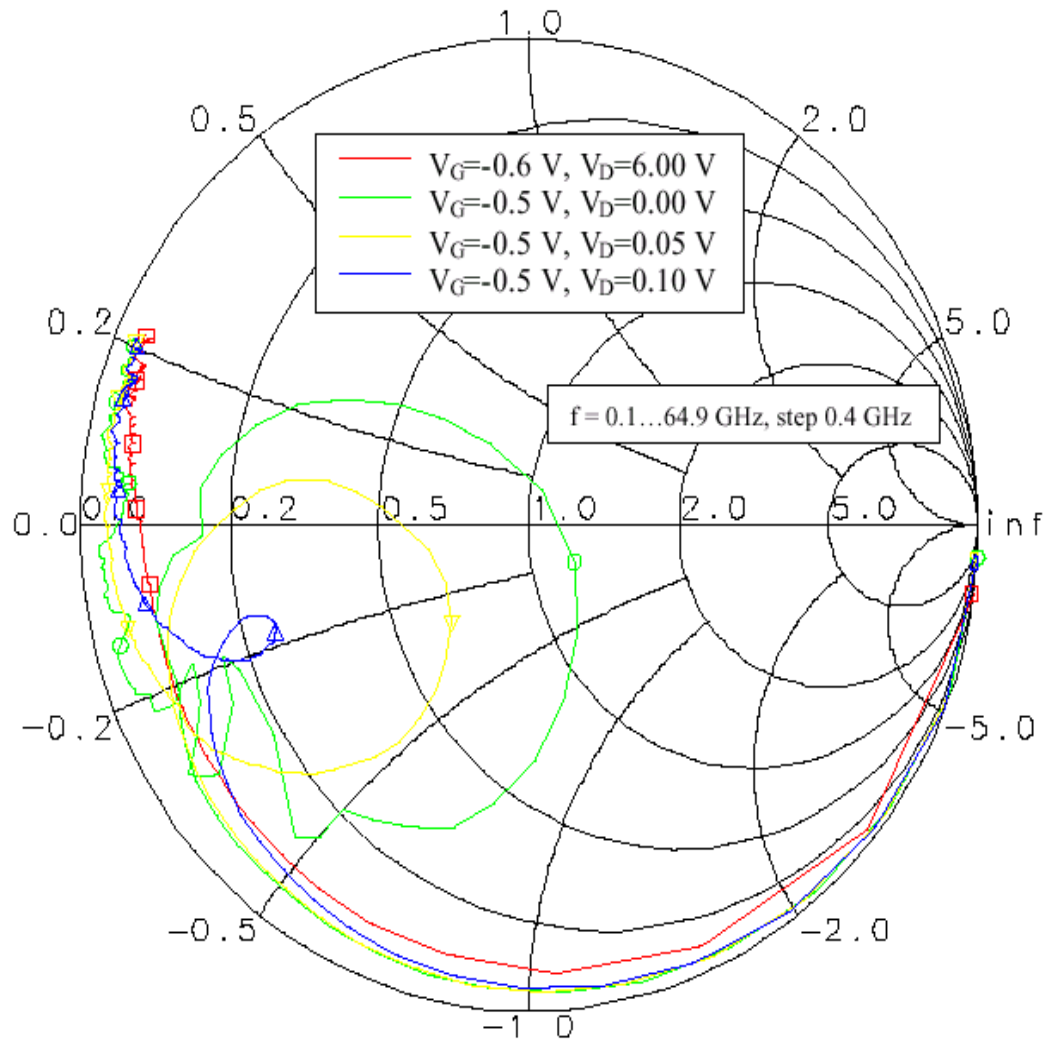



Burn-in effects

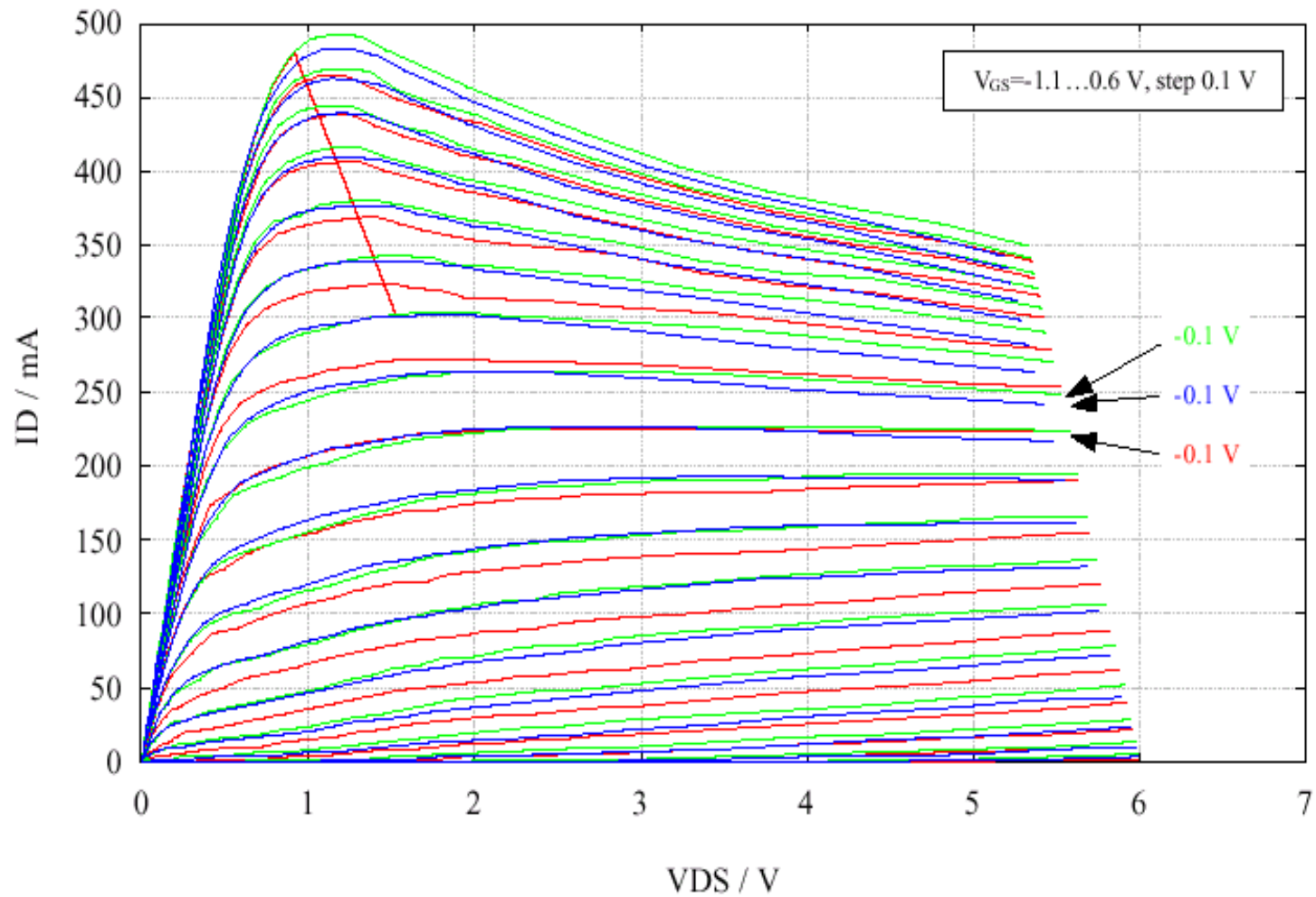


Scaling of extrinsic elements

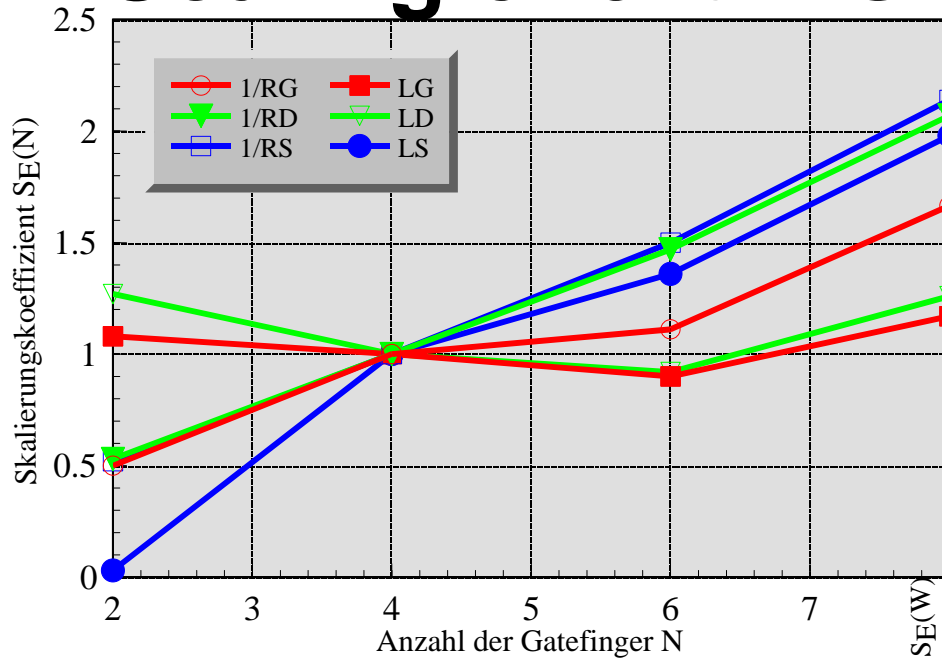

Variation of gate finger width

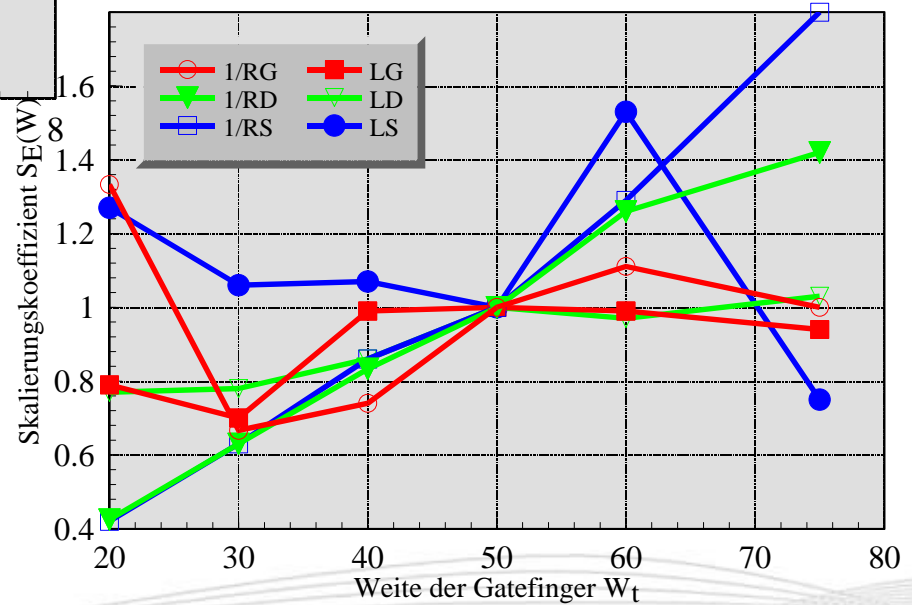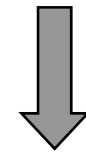


Variation of gate finger number

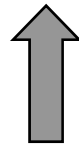

Scaling of extrinsic elements

$$S_E(N) = a_{EN} \cdot N + b_{EN}$$

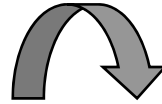

$$S_E(N, W_t) = S_E(N) \cdot S_E(W_t)$$



$$S_E(W_t) = a_{EW} \cdot W_t + b_{EW}$$

$S_E(N)$	$S_E(W)$	a_{EN}	b_{EN}	a_{EW}	b_{EW}
GG	GG	0.18	0.17	0.0	0.98
GD	GD	0.25	0.0	0.019	0.076
GS	GS	0.27	-0.04	0.024	-0.11
1/LG	LG	0.0	0.993	0.004	0.713
1/LD	LD	0.0	0.895	0.005	0.67
LS	1/LS	0.31	-0.46	0.006	0.68


Scaling of intrinsic elements

$$C_{old} = \frac{8 \times 75 \mu m}{4 \times 50 \mu m} = 3$$
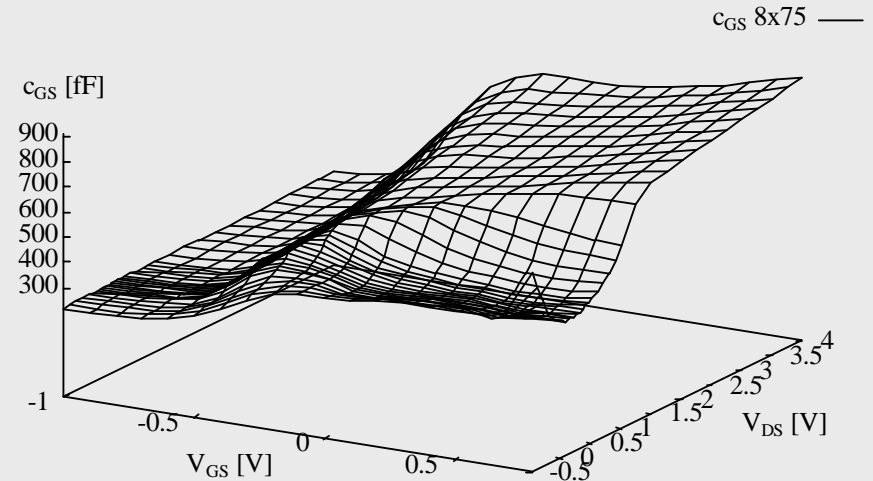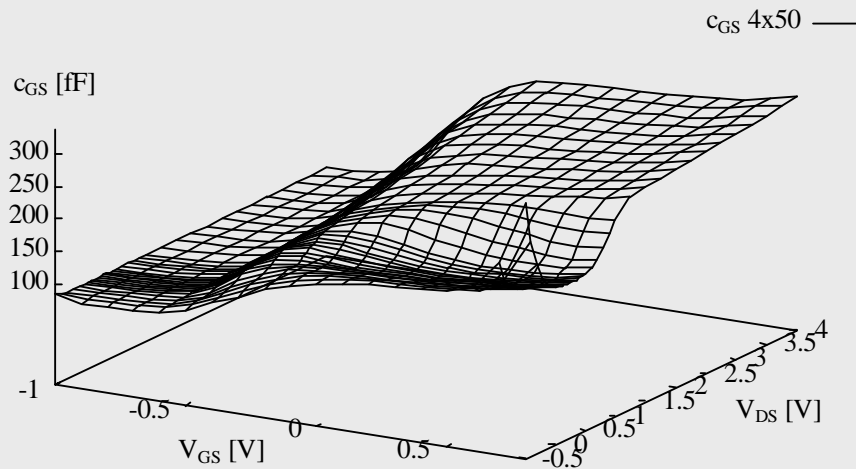
$$C = \frac{\sum_{V_{gs}, V_{ds}} \frac{G_x(V_{GS}, V_{DS})}{G_{ref}(V_{GS}, V_{DS})}}{n_{V_{GS}, V_{DS}}}$$




Scaling of intrinsic elements

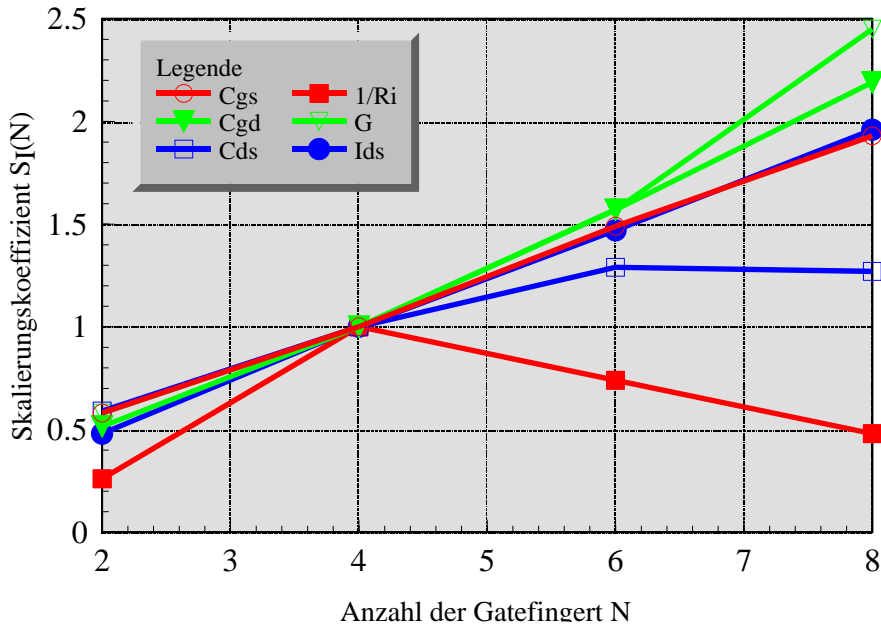

Variation of gate finger number


Variation of gate finger width

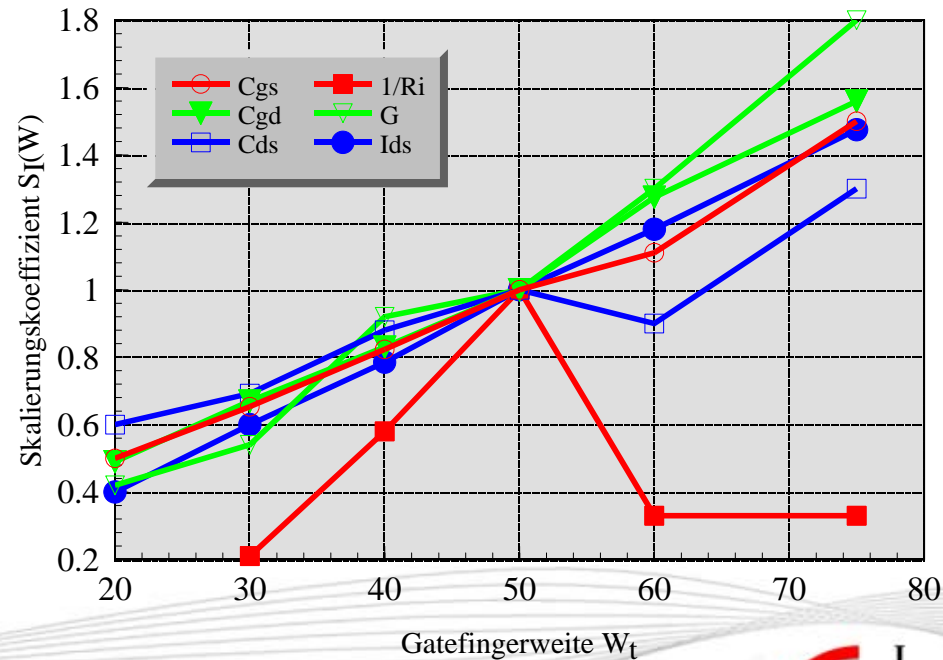

Scaling of intrinsic elements

$$S_I(N) = a_{IN} \cdot N + b_{IN}$$

$$S_I(W) = a_{IWt} \cdot W + b_{IWt}$$

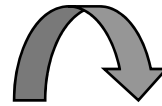


$$S_I(N, W) = S_I(N) \cdot S_I(W)$$

$S_I(N)$	$S_I(W)$	a_{IN}	b_{IN}	a_{IW}	b_{IW}
Cgs	Cgs	0.22	0.116	0.018	0.129
Cgd	Cgd	0.28	-0.08	0.019	0.077
Cds	Cds	0.12	0.459	0.011	0.371
Gi	Gi	0.02	0.52	-0.06	3.878
G	G	0.31	-0.14	0.025	-0.15
Id	Id	0.25	0.0	0.02	0.01

$$c_{new} = S_I(N = 4 \rightarrow N = 8) \cdot S_I(W_t = 50 \rightarrow W_t = 75)$$

$$1.93 \cdot 1.49 = 2.88$$

Thermal model

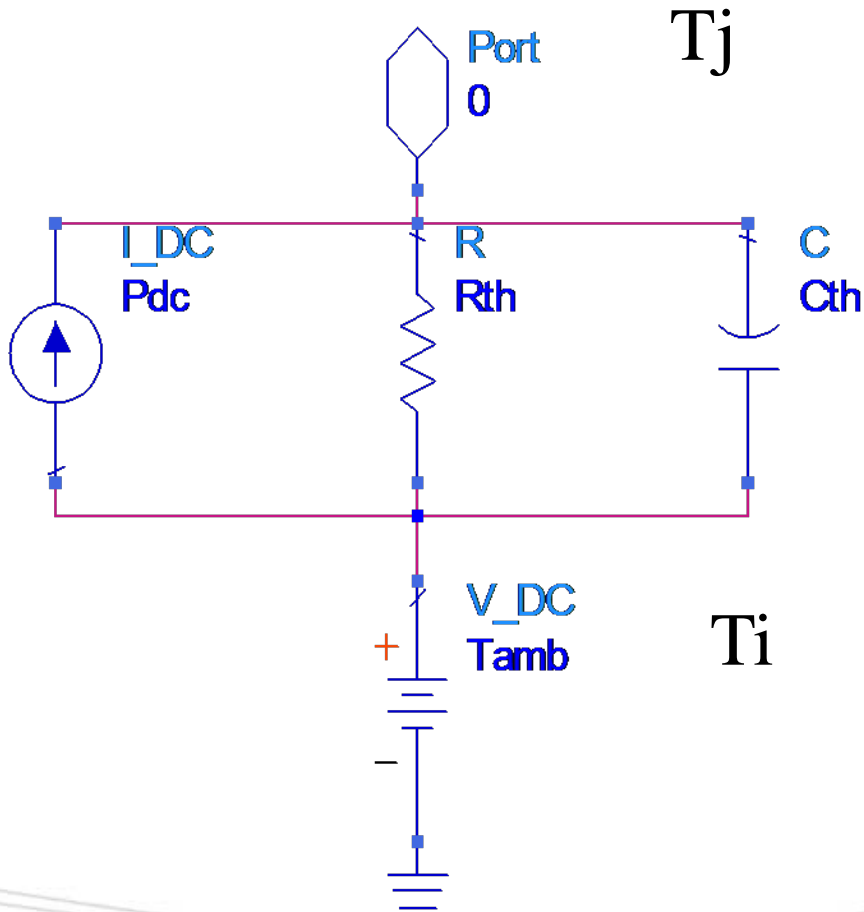

$$C_{TH} \frac{d\Delta T}{dt} = P - \frac{\Delta T}{R_{TH}}$$

$$P = I_D V_{DS}$$

$$I_D = \frac{V_{Rd1} - V_{Rd2}}{R_D(V_{GS}, V_{DS})}$$

4D spline interpolation


- Accurate description of $I_D(V_{GS}, V_{DS}, T_{junc})$

$$f(\vec{x}) = \sum_{i=0}^3 \sum_{j=0}^3 \sum_{k=0}^3 a_{ijk} x_1^i x_2^j x_3^k$$

- 64 unknown values, 8 points at same time

$$f, \frac{\partial f}{\partial x_i}, \frac{\partial^2 f}{\partial x_i \partial x_j} \Big|_{i \neq j}, \frac{\partial^3 f}{\partial x_1 \partial x_2 \partial x_3}$$




DC verification (LDMOS example)

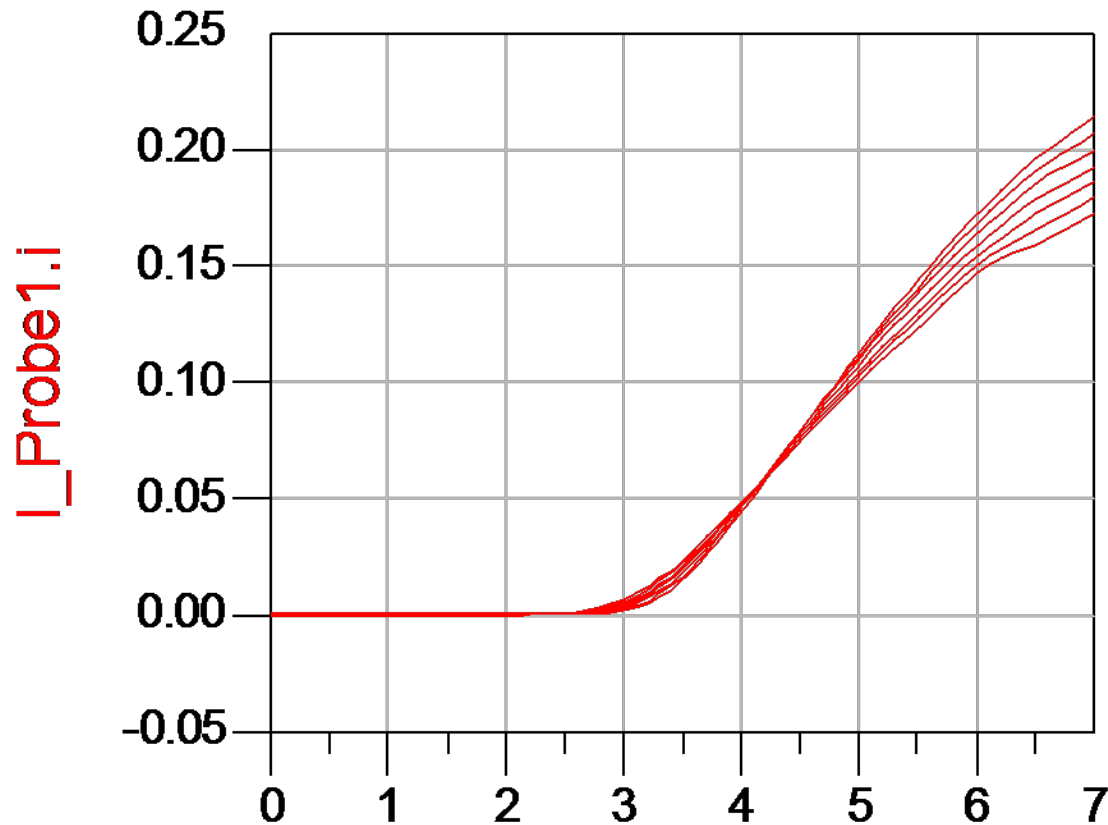

→ Intersection
in one point

V_{gs}
7x100 μm device

Transient analysis

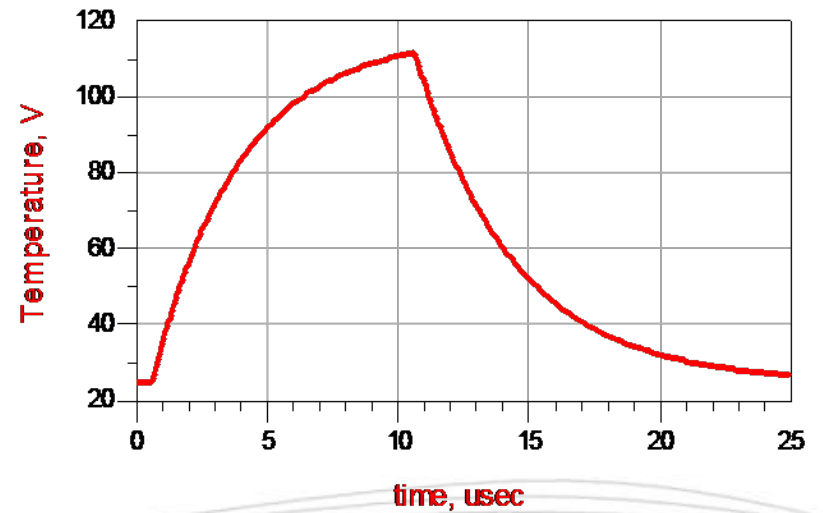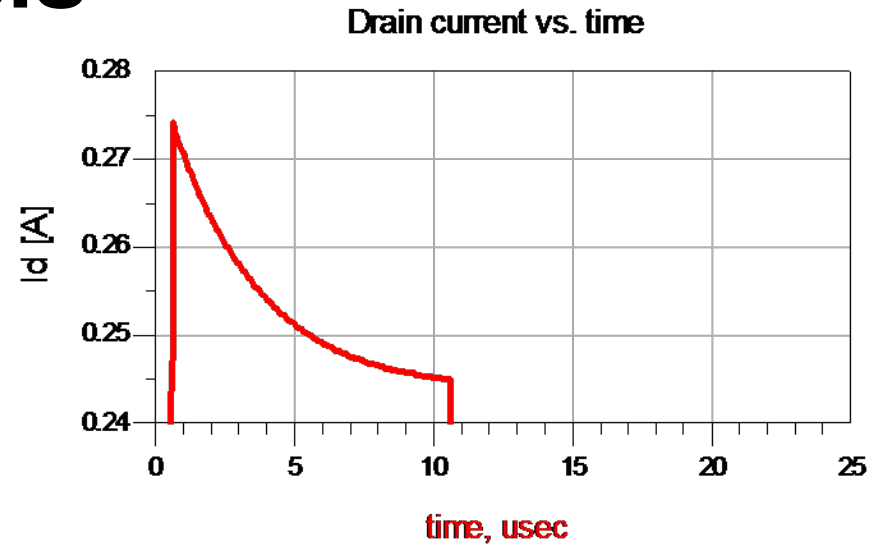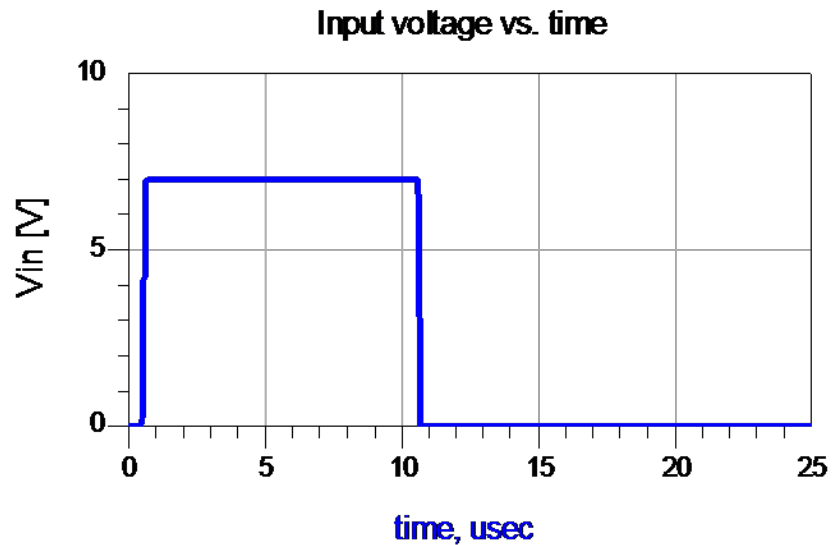

Rth/Cth extraction

→ Compare pulsed and CW currents at different temperatures

$$R_{TH} = \frac{T - T_{amb}}{V_{DS} I_{DS}}$$

→ Cth: Monitor current versus time

Thank you for you attention

→ Any questions?

