

- BASIC COMPONENTS OF A COMPUTER SYSTEM
- INFORMAL AND μ VHDL-BASED DESCRIPTION
 - ARCHITECTURE
 - IMPLEMENTATION
- OPERATION OF SIMPLE MICROCOMPUTER SYSTEM:
XMC: eXample MicroComputer
- ITS CYCLE TIME

BASIC COMPONENTS OF A COMPUTER

- PROCESSOR;
- MEMORY SUBSYSTEM;
- INPUT/OUTPUT (I/O) SUBSYSTEM

 


Figure 15.1: COMPUTER SYSTEM.

MEMORY HIERARCHY

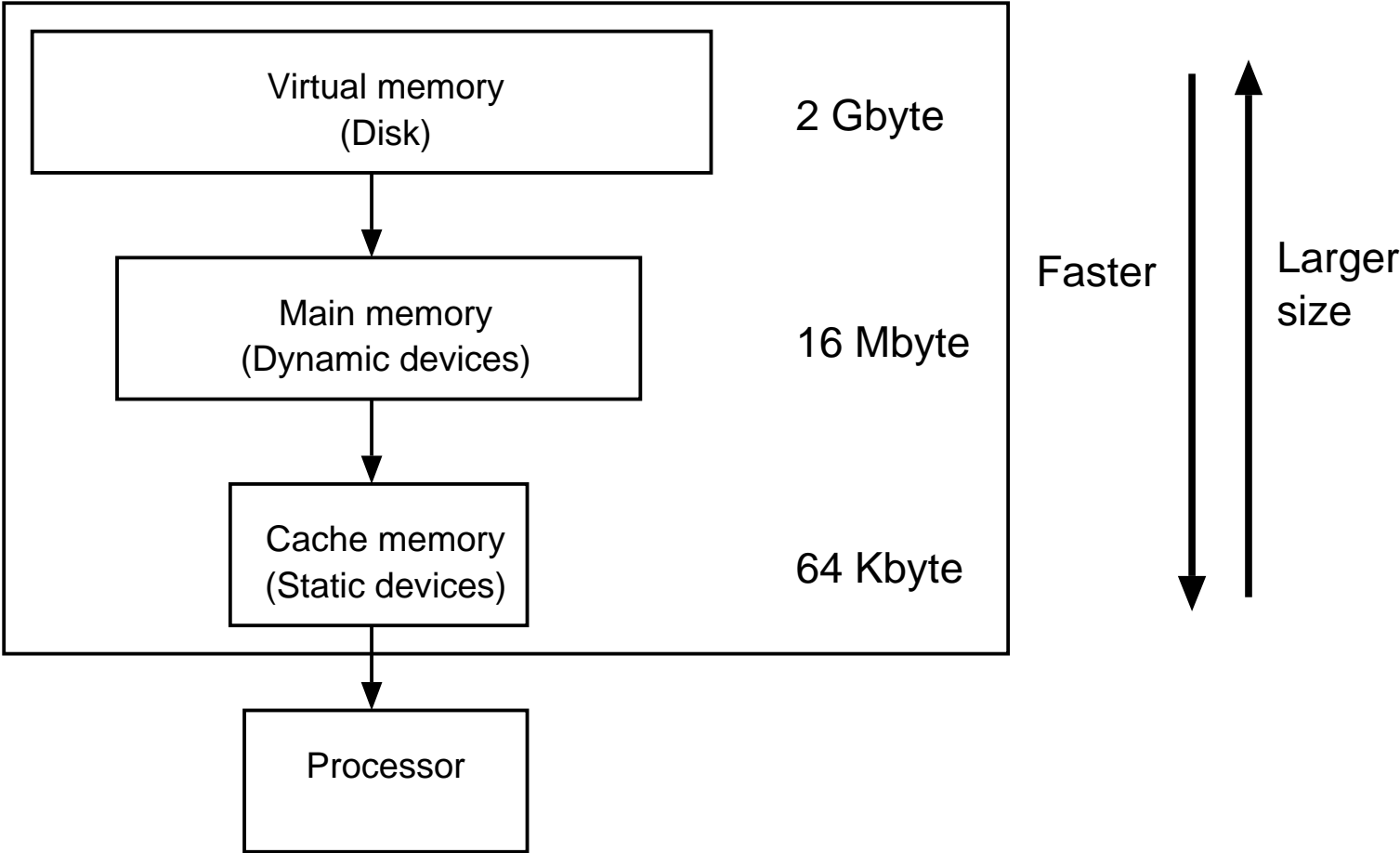


Figure 15.2: MEMORY HIERARCHY.

SPECIFICATION (architecture) OF A SIMPLE MICROCOMPUTER SYSTEM⁴

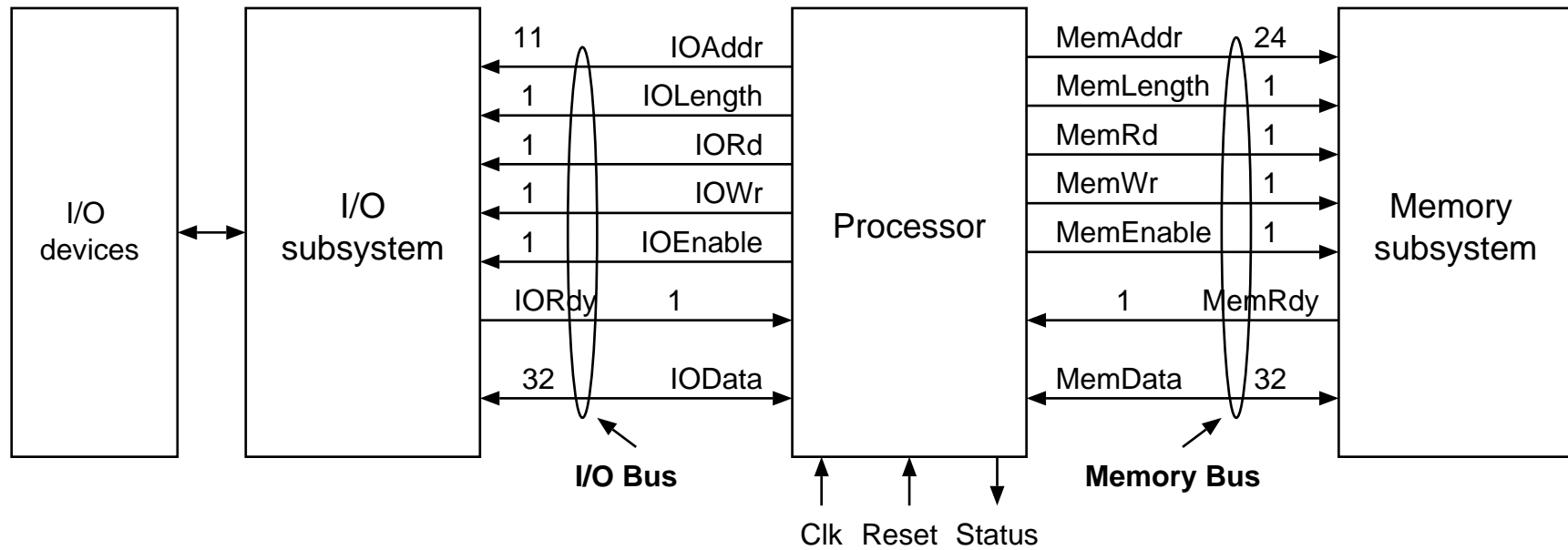


Figure 15.3: STRUCTURE OF XMC.

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

PACKAGE comp_pkg IS
    SUBTYPE WordT    IS STD_LOGIC_VECTOR(31 DOWNTO 0);
    SUBTYPE MAddrT   IS STD_LOGIC_VECTOR(23 DOWNTO 0);
    SUBTYPE IOAddrT  IS STD_LOGIC_VECTOR(10 DOWNTO 0);
    SUBTYPE ByteT    IS STD_LOGIC_VECTOR( 7 DOWNTO 0);
    TYPE    StatusT  IS (undef, p_reset, fetch, execute, memop, ioop);

    FUNCTION get_carry(RA_Data, RB_Data, Imm, Opcode: STD_LOGIC_VECTOR)
        RETURN STD_LOGIC;
    FUNCTION get_ovf (RA_Data, RB_Data, Imm, Opcode: STD_LOGIC_VECTOR)
        RETURN STD_LOGIC;
    FUNCTION get_cc (RA_Data, RB_Data, Opcode: STD_LOGIC_VECTOR)
        RETURN STD_LOGIC_VECTOR;
END comp_pkg;

PACKAGE BODY comp_pkg IS
    FUNCTION get_carry(RA_Data, RB_Data, Imm, Opcode: STD_LOGIC_VECTOR)
        RETURN STD_LOGIC
```

```
IS VARIABLE cy: STD_LOGIC:= '0';

BEGIN
    -- description of carry generation included here
    RETURN(cy);
END get_carry;

FUNCTION get_ovf (RA_Data, RB_Data, Imm, Opcode: STD_LOGIC_VECTOR)
    RETURN STD_LOGIC
IS VARIABLE ovf: STD_LOGIC:= '0';
BEGIN
    -- description of overflow generation included here
    RETURN(ovf);
END get_ovf;

FUNCTION get_cc (RA_Data, RB_Data, Opcode: STD_LOGIC_VECTOR)
    RETURN STD_LOGIC_VECTOR
IS VARIABLE cc: STD_LOGIC_VECTOR(3 DOWNTO 0):= "0000";
BEGIN
    -- description of cc generation included here
    RETURN(cc);
END get_cc;
END comp_pkg;
```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE WORK.ALL, WORK.comp_pkg.ALL;

ENTITY Computer IS
  PORT (Reset, Clk : IN STD_LOGIC);
END Computer;

ARCHITECTURE structural OF Computer IS
  SIGNAL MemAddr          : MAddrT   ; -- memory address bus
  SIGNAL MemLength, MemRd : STD_LOGIC; -- memory control signals
  SIGNAL MemWr, MemEnable : STD_LOGIC;
  SIGNAL MemRdy           : STD_LOGIC; -- memory status signal
  SIGNAL MemData          : WordT     ; -- memory data bus

  SIGNAL IOAddr          : IOAddrT   ; -- I/O address bus
  SIGNAL IOLength, IORd  : STD_LOGIC; -- I/O control signals
  SIGNAL IOWr, IOEnable  : STD_LOGIC;
  SIGNAL IORdy           : STD_LOGIC; -- I/O status signal
  SIGNAL IOData          : WordT     ; -- I/O data bus

  SIGNAL Status          : StatusT;

```

```
BEGIN
  U1: ENTITY Memory
    PORT MAP (MemAddr, MemLength, MemRd, MemWr, MemEnable,
              MemRdy, MemData);

  U2: ENTITY IO
    PORT MAP (IOAddr, IOLength, IORd, IOWr, IOEnable,
              IORdy, IOData);

  U3: ENTITY Processor
    PORT MAP (MemAddr, MemData, MemLength, MemRd, MemWr,
              MemEnable, MemRdy,
              IOAddr, IOData, IOLength, IORd, IOWr,
              IOEnable, IORdy,
              Status, Reset, Clk);

END structural;
```


MEMORY SUBSYSTEM

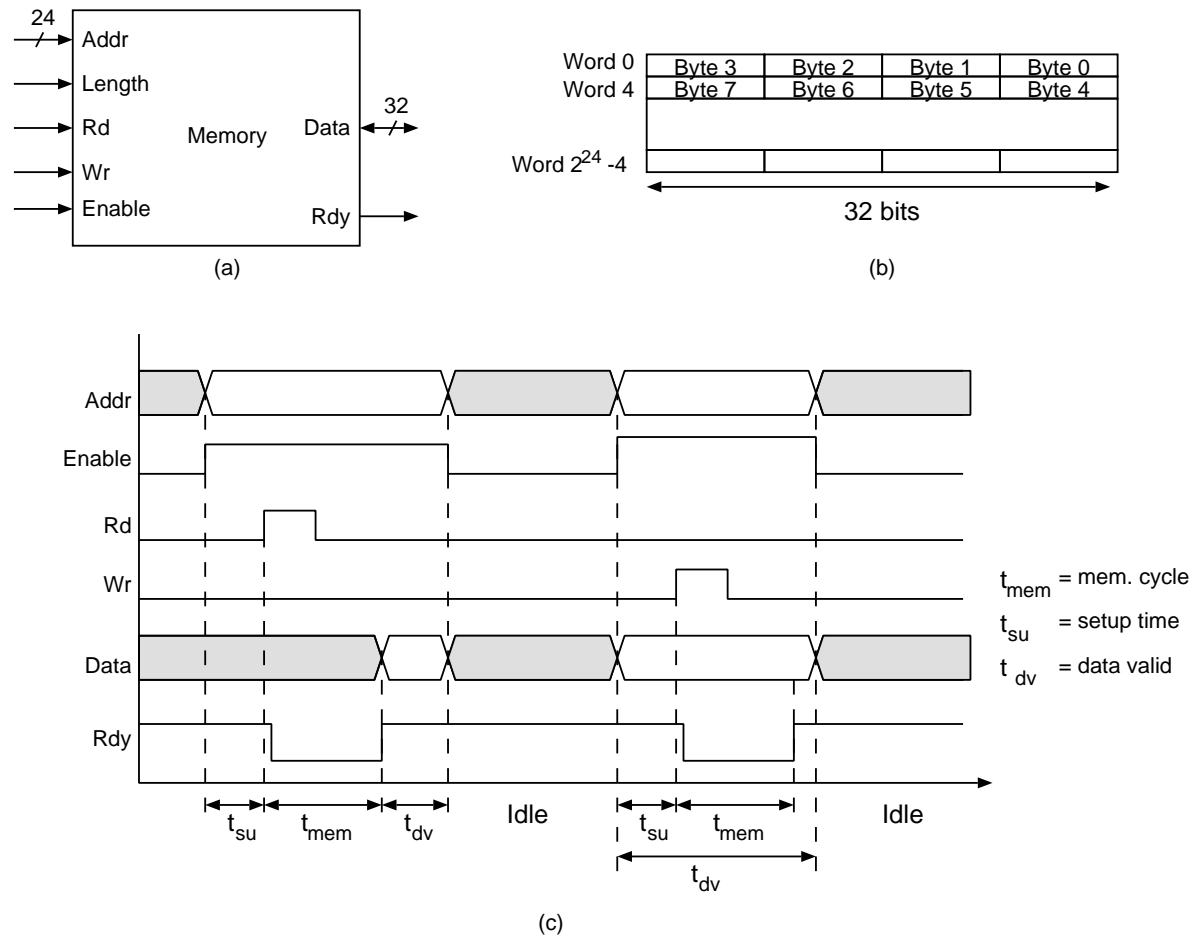


Figure 15.4: MEMORY SUBSYSTEM. (a) EXTERNAL SIGNALS. (b) INTERNAL ORGANIZATION. (c) TIMING DIAGRAM

μ VHDL ENTITY DECLARATION FOR MEMORY SUBSYSTEM

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE WORK.comp_pkg.ALL;
ENTITY Memory IS
    PORT (Addr      : IN      MAddrT   ; -- memory address bus
          Length    : IN      STD_LOGIC; -- byte/word operand
          Rd, Wr    : IN      STD_LOGIC; -- access control signals
          Enable    : IN      STD_LOGIC; -- enable signal
          Rdy       : OUT     STD_LOGIC; -- access completion signal
          Data      : INOUT   WordT    ); -- memory data bus
END Memory;
```

```
LIBRARY ieee;
USE ieee.std_logic_unsigned.ALL;

ARCHITECTURE behavioral OF Memory IS
    CONSTANT Tmem  : TIME := 8 ns;    -- nanoseconds
    CONSTANT Td    : TIME := 200 ps;  -- picoseconds
    CONSTANT Tsu   : TIME := 200 ps;  -- picoseconds
BEGIN
    PROCESS (Rd, Wr, Enable)
        CONSTANT byte_1: STD_LOGIC:= '0'; -- constant declarations
        CONSTANT word_1: STD_LOGIC:= '1';
                                           -- memory declaration
        CONSTANT MaxMem  : NATURAL := 16#FFFFFF#; -- 2**24 bytes
        TYPE MemArrayT IS ARRAY(0 TO MaxMem-1) OF ByteT;
        VARIABLE Mem     : MemArrayT;
                                           -- working variables

        VARIABLE tAddr  : NATURAL;
        VARIABLE tData  : WordT ;
        VARIABLE tCtrls: STD_LOGIC_VECTOR(2 DOWNTO 0);
```

```

BEGIN
  tCtrls:= Rd & Wr & Enable; -- group signals for simpler decoding
  CASE tCtrls IS
                                -- output to tri-state
    WHEN "000" => Data <= (OTHERS => 'Z') AFTER Td;

    WHEN "011" =>                -- write access;
                                -- indicate module busy
    Rdy <= '0' AFTER Td, '1' AFTER Tmem;
    IF (Length = byte_1) THEN    -- read address
      tAddr:= CONV_INTEGER(Addr); -- bit-vector to integer
                                -- from pkg std_logic_unsigned
    ELSE
      tAddr:= CONV_INTEGER(Addr(23 DOWNTO 2) & "00");
    END IF;
    CASE Length IS
      WHEN byte_1 => Mem(tAddr) := (Data( 7 DOWNTO  0));
      WHEN word_1 => Mem(tAddr) := (Data( 7 DOWNTO  0));
                        Mem(tAddr+1):= (Data(15 DOWNTO  8));
                        Mem(tAddr+2):= (Data(23 DOWNTO 16));
                        Mem(tAddr+3):= (Data(31 DOWNTO 24));
      WHEN OTHERS => NULL;
  
```

```

        END CASE;

    WHEN "101" =>
        -- read access
        -- indicate module busy
        Rdy <= '0' AFTER Td, '1' AFTER Tmem;
        IF (Length = byte_1) THEN
            -- read address
            tAddr:= CONV_INTEGER(Addr); -- bit-vector to integer
        ELSE
            tAddr:= CONV_INTEGER(Addr(23 DOWNTO 2) & "00");
        END IF;
        CASE Length IS
            WHEN byte_1 => tData( 7 DOWNTO  0):= (Mem(tAddr));
            WHEN word_1 => tData( 7 DOWNTO  0):= (Mem(tAddr));
                        tData(15 DOWNTO  8):= (Mem(tAddr+1));
                        tData(23 DOWNTO 16):= (Mem(tAddr+2));
                        tData(31 DOWNTO 24):= (Mem(tAddr+3));
            WHEN OTHERS => NULL;
        END CASE;
        Data <= tData AFTER Tmem; -- deliver data

    WHEN OTHERS => NULL; -- memory not enabled
END CASE;
END PROCESS;

```

```
                                -- timing verifications
ASSERT NOT (Rd'EVENT AND Rd='1' AND NOT Addr'STABLE(Tsu))
    REPORT "Read address setup time violation";

ASSERT NOT (Rd'EVENT AND Rd='1' AND NOT Enable'STABLE(Tsu))
    REPORT "Read enable setup time violation";

ASSERT NOT (Wr'EVENT AND Wr='1' AND NOT Addr'STABLE(Tsu))
    REPORT "Write address setup time violation";

ASSERT NOT (Wr'EVENT AND Wr='1' AND NOT Enable'STABLE(Tsu))
    REPORT "Write enable setup time violation";

END behavioral;
```

INPUT/OUTPUT (I/O) SUBSYSTEM

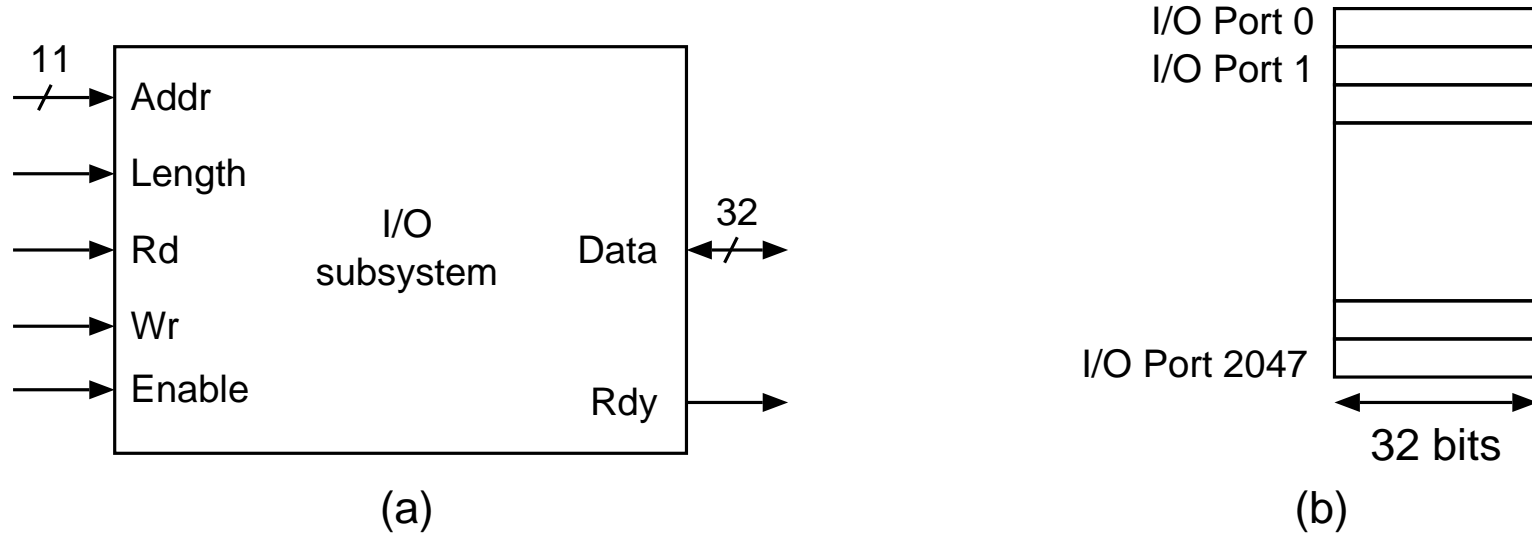


Figure 15.5: INPUT/OUTPUT SUBSYSTEM.

μ VHDL I/O ENTITY DECLARATION

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE WORK.comp_pkg.ALL;
ENTITY IO IS
    PORT (Addr      : IN      IOAddrT  ; -- I/O address bus
          Length    : IN      STD_LOGIC; -- byte/word control
          Rd, Wr    : IN      STD_LOGIC; -- I/O access control
          Enable    : IN      STD_LOGIC; -- I/O enable control
          Rdy       : OUT     STD_LOGIC; -- I/O completion signal
          Data      : INOUT   WordT     ); -- I/O data bus
END IO;
```


Processor state

- 32 general-purpose registers (32-bits wide), called R0, R1, . . . , R31;
- a 24-bit Program Counter register (PC);
- a 4-bit Condition Register (CR); and
- a 32-bit Instruction Register (IR).

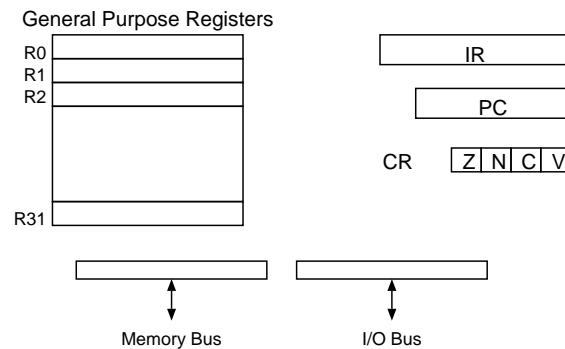


Figure 15.6: PROCESSOR STATE.

BEHAVIOR OF PROCESSOR

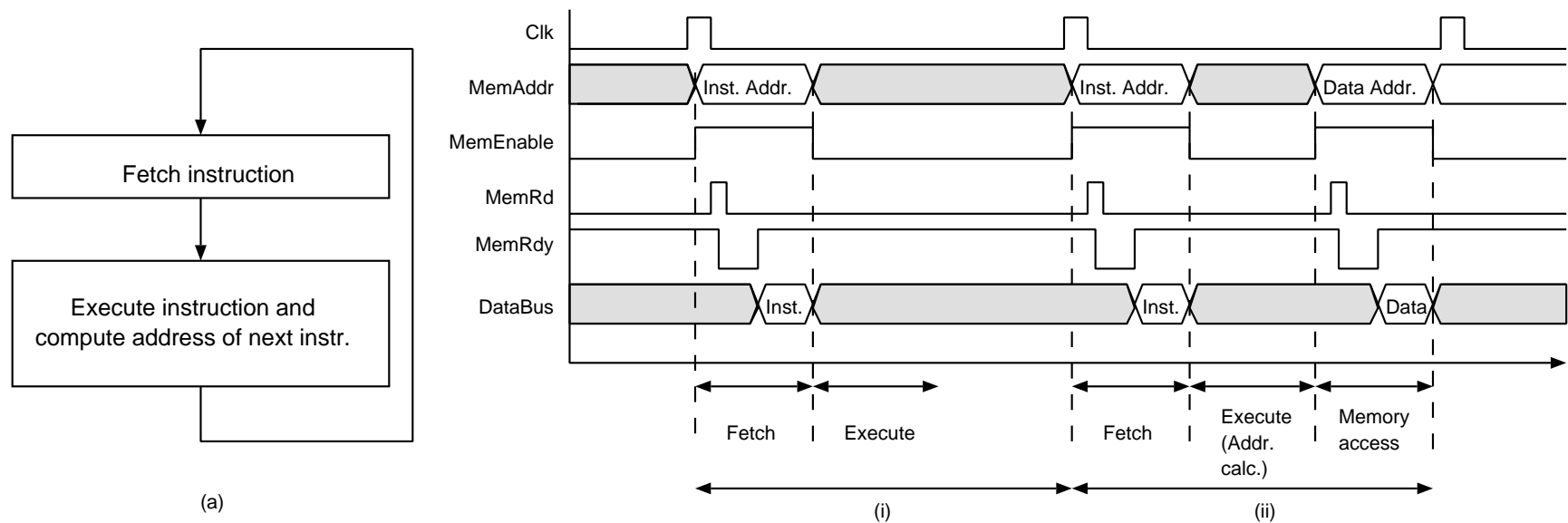


Figure 15.7: BEHAVIOR OF THE PROCESSOR. (a) INSTRUCTION LOOP. (b) MEMORY BUS BEHAVIOR FOR REGISTER OPERATION. (c) MEMORY BUS BEHAVIOR FOR LOAD OPERATION.

BEHAVIOR OF INSTRUCTIONS

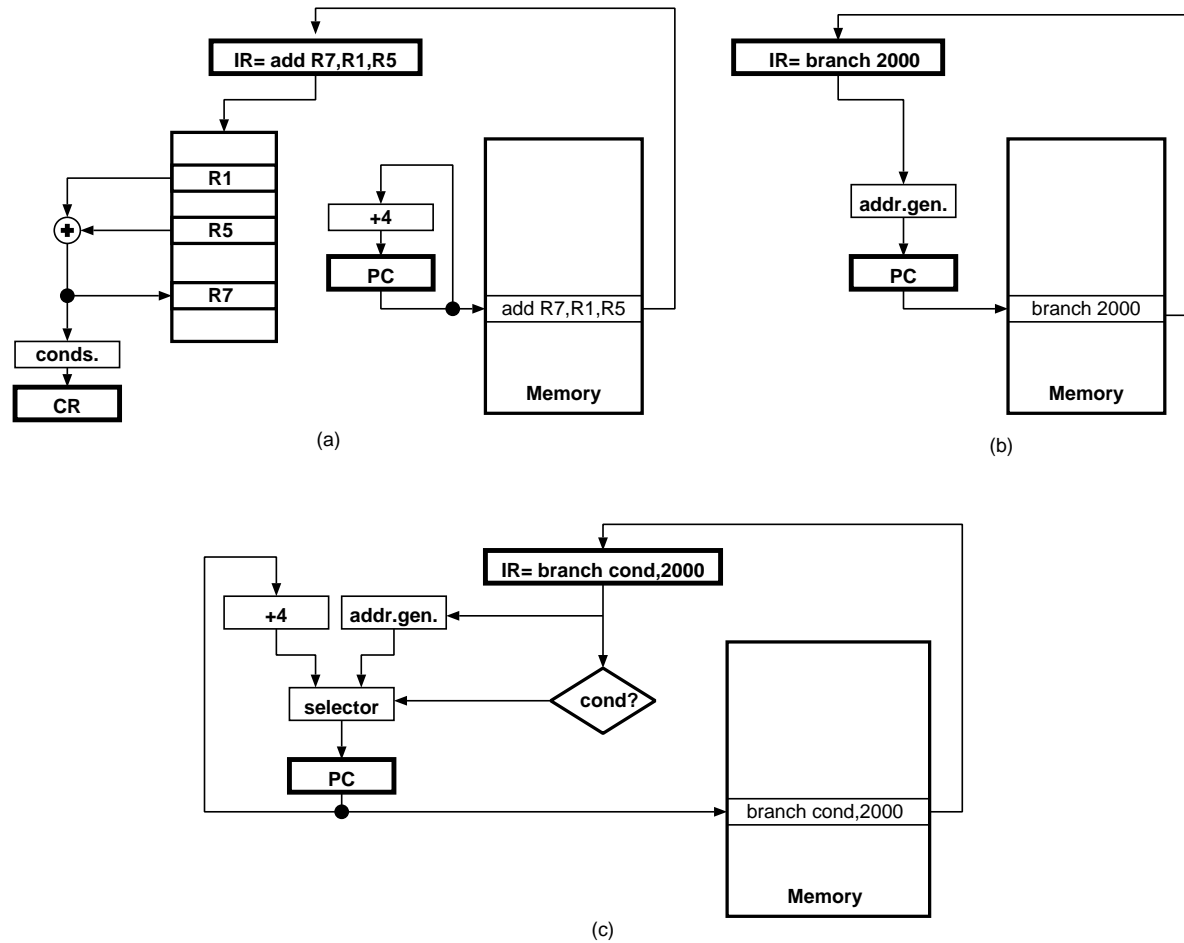


Figure 15.8: BEHAVIOR OF INSTRUCTIONS. (a) ADD instruction. (b) UNCONDITIONAL BRANCH INSTRUCTION. (c) CONDITIONAL BRANCH INSTRUCTION.

INSTRUCTION SEQUENCING

- SEQUENTIAL UNLESS
 1. UNCONDITIONAL BRANCH
 2. CONDITIONAL BRANCH

	31		25		20		15		10		0												
RT := op(RA)	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RT</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RA</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">--</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> </tr> </table>											Opcode			RT			RA			--		
Opcode			RT			RA			--														
RT := RA op RB	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RT</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RA</td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RB</td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">--</td> <td style="width: 5%;"></td> </tr> </table>											Opcode			RT			RA		RB		--	
Opcode			RT			RA		RB		--													
RT := RA op SI	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RT</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RA</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">SI</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> </tr> </table>											Opcode			RT			RA			SI		
Opcode			RT			RA			SI														
RT := RA op UI	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RT</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RA</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">UI</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> </tr> </table>											Opcode			RT			RA			UI		
Opcode			RT			RA			UI														
RT := M[RA+D]	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RT</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RA</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">D</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> </tr> </table>											Opcode			RT			RA			D		
Opcode			RT			RA			D														
M[RA+D] := RS	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RS</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RA</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">D</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> </tr> </table>											Opcode			RS			RA			D		
Opcode			RS			RA			D														
RT := IO[PN]	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RT</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RA</td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">--</td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">PN</td> <td style="width: 5%;"></td> </tr> </table>											Opcode			RT			RA		--		PN	
Opcode			RT			RA		--		PN													
IO[PN] := RS	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RS</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RA</td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">--</td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">PN</td> <td style="width: 5%;"></td> </tr> </table>											Opcode			RS			RA		--		PN	
Opcode			RS			RA		--		PN													
PC := PC + 4 + D	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">D</td> <td style="width: 5%;"></td> </tr> </table>											Opcode										D	
Opcode										D													
PC := RA	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 5%;">Opcode</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">--</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">RA</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%; text-align: center;">--</td> <td style="width: 5%;"></td> </tr> </table>											Opcode			--			RA				--	
Opcode			--			RA				--													

Figure 15.9: INSTRUCTION FORMATS.

Table 15.2: INSTRUCTION SET

Name	Opcode	Function	CR	Assembly Language
No-op	000000	no operation		nop
NOT	000010	$RT := \text{not}(RA)$	Y	not RT,RA
Left shift	000100	$RT := \text{lshift}(RA)$	Y	lsh RT,RA
Right shift	000110	$RT := \text{rshift}(RA)$	Y	rsh RT,RA
Left rotate	001000	$RT := \text{lrot}(RA)$	Y	lrt RT,RA
Right rot.	001010	$RT := \text{rrot}(RA)$	Y	rrt RT,RA
Add	010000	$RT := RA + RB$	Y	add RT,RA,RB
Add immed.	010001	$RT := RA + SI$	Y	adi RT,RA,SI
Subtract	010010	$RT := RA - RB$	Y	sub RT,RA,RB
Sub. immed.	010011	$RT := RA - SI$	Y	sbi RT,RA,SI
AND	010100	$RT := RA \text{ and } RB$	Y	and RT,RA,RB
AND immed.	010101	$RT := RA \text{ and } UI$	Y	ani RT,RA,UI
OR	010110	$RT := RA \text{ or } RB$	Y	or RT,RA,RB
OR immed.	010111	$RT := RA \text{ or } UI$	Y	ori RT,RA,UI
XOR	011000	$RT := RA \text{ xor } RB$	Y	xor RT,RA,RB
XOR immed.	011001	$RT := RA \text{ xor } UI$	Y	xri RT,RA,UI

Table 15.3: INSTRUCTION SET (cont.)

Name	Opcode	Function	CR	Assembly Language
Load byte	100000	$RT(7 \text{ to } 0) := \text{Mem}(RA+D,1)$		ldb RT,D(RA)
Load word	100001	$RT(31 \text{ to } 0) := \text{Mem}(RA+D,4)$		ldw RT,D(RA)
Store byte	100010	$\text{Mem}(RA+D,1) := RS(7 \text{ to } 0)$		stb RS,D(RA)
Store word	100011	$\text{Mem}(RA+D,4) := RS(31 \text{ to } 0)$		stw RS,D(RA)
I/O Rd byte	100100	$RT(7 \text{ to } 0) := \text{IO}(PN,1)$		irb RT,PN
I/O Rd word	100101	$RT(31 \text{ to } 0) := \text{IO}(PN,4)$		irw RT,PN
I/O Wr byte	100110	$\text{IO}(PN,1) := RS(7 \text{ to } 0)$		iwb RS,PN
I/O Wr word	100111	$\text{IO}(PN,4) := RS(31 \text{ to } 0)$		iww RS,PN

Table 15.4: INSTRUCTION SET (cont.)

Name	Opcode	Function	CR	Assembly Language
Branch	111000	$PC := PC + 4 + D$		br D
Branch indirect	111001	$PC := RA$		bri RA
Branch if N=0	110000	If N=0 then $PC := PC + 4 + D$		brp D
Branch if N=1	110001	If N=1 then $PC := PC + 4 + D$		brn D
Branch if Z=0	110010	If Z=0 then $PC := PC + 4 + D$		bnz D
Branch if Z=1	110011	If Z=1 then $PC := PC + 4 + D$		brz D
Branch if C=0	110100	If C=0 then $PC := PC + 4 + D$		bnc D
Branch if C=1	110101	If C=1 then $PC := PC + 4 + D$		brc D
Branch if V=0	110110	If V=0 then $PC := PC + 4 + D$		bnv D
Branch if V=1	110111	If V=1 then $PC := PC + 4 + D$		brv D

μ VHDL SPECIFICATION OF PROCESSOR

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE WORK.comp_pkg.ALL;

ENTITY processor IS
  PORT (MemAddr  : OUT    MAddrT   ; -- memory address bus
        MemData  : INOUT  WordT    ; -- data bus to/from memory
        MemLength: OUT    STD_LOGIC; -- memory operand length
        MemRd    : OUT    STD_LOGIC; -- memory read control signal
        MemWr    : OUT    STD_LOGIC; -- memory write control signal
        MemEnable: OUT    STD_LOGIC; -- memory enable signal
        MemRdy   : IN     STD_LOGIC; -- memory completion signal
        IOAddr   : OUT    IOAddrT  ; -- I/O address bus
        IOData   : INOUT  WordT    ; -- data bus to/from I/O
        IOLength : OUT    STD_LOGIC; -- I/O operand length
        IORd    : OUT    STD_LOGIC; -- I/O read control signal
        IOWr    : OUT    STD_LOGIC; -- I/O write control signal
        IOEnable : OUT    STD_LOGIC; -- memory enable signal
        IORdy   : IN     STD_LOGIC; -- I/O completion signal
        Status   : OUT    StatusT  ; -- processor status signal
        Reset    : IN     STD_LOGIC; -- reset signal
        Clk     : IN     STD_LOGIC); -- clock signal
END processor;

```

μ VHDL SPECIFICATION OF BEHAVIOR

```

LIBRARY ieee;
USE ieee.std_logic_arith.all;      -- use definitions and operations
USE ieee.std_logic_signed.all;    -- on signed values

ARCHITECTURE behavioral OF processor IS
  -- registers (processor state)
  TYPE      RegFileT IS ARRAY(0 to 31) OF WordT;
  SIGNAL    GPR: RegFileT          ; -- general registers
  SIGNAL    PC : MAddrT            ; -- Program Counter register
  SIGNAL    CR : STD_LOGIC_VECTOR( 3 DOWNTO 0); -- Condition Register
  SIGNAL    IR : STD_LOGIC_VECTOR(31 DOWNTO 0); -- Instruction register

  -- signals used by output function
  SIGNAL    Phase: StatusT        ; -- instr. cycle phase
  SIGNAL    tMemAddr: WordT       ; -- memory address
  SIGNAL    tData   : WordT       ; -- memory/io data

  ALIAS     Z  : STD_LOGIC IS CR(0) ; -- Condition code Zero
  ALIAS     N  : STD_LOGIC IS CR(1) ; -- Condition code Negative
  ALIAS     C  : STD_LOGIC IS CR(2) ; -- Condition code Carry
  ALIAS     O  : STD_LOGIC IS CR(3) ; -- Condition code Overflow

```

```

ALIAS    Opcode : STD_LOGIC_VECTOR(5 DOWNT0 0) IS IR(31 DOWNT0 26);
ALIAS    RT      : STD_LOGIC_VECTOR(4 DOWNT0 0) IS IR(25 DOWNT0 21);
ALIAS    RA      : STD_LOGIC_VECTOR(4 DOWNT0 0) IS IR(20 DOWNT0 16);
ALIAS    RB      : STD_LOGIC_VECTOR(4 DOWNT0 0) IS IR(15 DOWNT0 11);
ALIAS    RS      : STD_LOGIC_VECTOR(4 DOWNT0 0) IS IR(15 DOWNT0 11);
ALIAS    Imm     : STD_LOGIC_VECTOR(15 DOWNT0 0) IS IR(15 DOWNT0 0);
ALIAS    D       : STD_LOGIC_VECTOR(15 DOWNT0 0) IS IR(15 DOWNT0 0);
ALIAS    PN      : STD_LOGIC_VECTOR(10 DOWNT0 0) IS IR(10 DOWNT0 0);
ALIAS    dlength: STD_LOGIC                      IS IR(26)          ;

```

```
-- other declarations
```

```

CONSTANT delay      : TIME := 200 ps; -- register delay
CONSTANT Reset_delay: TIME := 5 ns;
CONSTANT Exec_delay : TIME := 10 ns; -- Execute delay
CONSTANT Mdelay     : TIME := 600 ps; -- MemEnable signal delay
CONSTANT Pulse_Width: TIME := 2.6 ns; -- memory signals width
CONSTANT Fetch_delay: TIME := 3 ns;  -- disable memory after
                                         -- access completed

```

```

BEGIN
  PROCESS                                -- transition function
  -- working variables
  VARIABLE RS_data, RA_data, RB_data    : WordT;
  VARIABLE RT_addr, RA_addr, RB_addr, RS_addr : Natural;

  BEGIN
  WAIT ON Clk,Reset;

  IF (Reset'Event AND Reset = '1') THEN                                -- reset function
    PC <= (OTHERS => '0'); CR <= "0000"; IR <= (OTHERS => '0');

    FOR i IN 0 TO 31 LOOP
      GPR(i) <= (OTHERS => '0');
    END LOOP;

    Phase <= p_reset;
    Status <= p_reset;

    WAIT UNTIL (Reset = '0') AND (Clk = '1');
  END IF;

```

```

IF (Clk'Event AND Clk='1') THEN
  -- Instruction cycle
  Status    <= Fetch AFTER delay;
  Phase     <= Fetch AFTER delay;

                                                    -- instruction fetch
  PC        <= PC + 4  AFTER Exec_delay;
  WAIT UNTIL MemRdy='1';    -- wait instr. fetch completed
  IR        <= MemData;
  WAIT FOR  Fetch_delay;

                                                    -- instruction execution

  Status    <= Execute;
  Phase     <= Execute;
  RA_addr   := CONV_INTEGER('0' & RA); RB_addr := CONV_INTEGER('0' & RB);
                                                    -- '0' to force bit-vector to positive value
  RA_data   := GPR(RA_addr)    ; RB_data := GPR(RB_addr)    ;
  RT_addr   := CONV_INTEGER('0' & RT);
  RS_addr   := CONV_INTEGER('0' & RS); -- source reg. for store
  RS_data   := GPR(RS_addr)    ; -- or I/O write
  WAIT FOR  Exec_delay;

```

```

CASE Opcode IS
WHEN "000000" => null;                -- nop
WHEN "000010" => GPR(RT_Addr) <= not(RA_data);    -- not
WHEN "000100" => GPR(RT_Addr) <= RA_data(30 DOWNT0 0) & '0'; -- lshift
WHEN "000110" => GPR(RT_Addr) <= '0' & RA_data(31 DOWNT0 1); -- rshift
                                                    -- lrotate
WHEN "001000" => GPR(RT_Addr) <= RA_data(30 DOWNT0 0) & RA_data(31);
                                                    -- rrotate
WHEN "001010" => GPR(RT_Addr) <= RA_DATA(0) & RA_data(31 DOWNT0 1);

WHEN "010000" => GPR(RT_Addr) <= RA_data + RB_data      ; -- add
WHEN "010001" => GPR(RT_Addr) <= RA_data + Imm;
WHEN "010010" => GPR(RT_Addr) <= RA_data - RB_data      ; -- sub
WHEN "010011" => GPR(RT_Addr) <= RA_data - Imm;
WHEN "010100" => GPR(RT_Addr) <= RA_data and RB_data    ; -- and
WHEN "010101" => GPR(RT_Addr) <= RA_data and ext(Imm,RA_data'LENGTH);
                                                    -- ext: zero extension from ieee pkg
WHEN "010110" => GPR(RT_Addr) <= RA_data or  RB_data    ; -- or
WHEN "010111" => GPR(RT_Addr) <= RA_data or  ext(Imm,RA_data'LENGTH);

```

```

WHEN "011000" => GPR(RT_Addr) <= RA_data xor RB_data ; -- xor
WHEN "011001" => GPR(RT_Addr) <= RA_data xor ext(Imm, RA_data'LENGTH);

WHEN "100000" | "100001" => -- ldb, ldw
    Phase      <= MemOp;
    Status      <= MemOp;
    tMemAddr    <= RA_data + D; -- mem.addr.
    WAIT until MemRdy = '1';

WHEN "100010" | "100011" => -- stb, stw
    Phase      <= MemOp;
    Status      <= MemOp;
    tMemAddr    <= RA_data + D; -- mem. addr.
    tData       <= RS_data; -- mem. data
    WAIT until MemRdy = '1';

WHEN "100100" | "100101" => -- irb, irw
    Phase      <= IOOp;
    Status      <= IOOp;
    WAIT until IORdy = '1' ;

```

```

WHEN "100110" | "100111" =>                                -- iwb, iww
    Phase      <= IOOp;
    Status     <= IOOp;
    tData      <= RS_data;                                -- io data
    WAIT until IORdy = '1' ;

WHEN "111000" => PC <= PC + D;                               -- branch
WHEN "111001" => PC <= RA_data(23 DOWNT0 0);                -- br.ind.
WHEN "110000" | "110001"
    => IF (N = Opcode(0)) THEN                               -- br on N
        PC <= PC + D;
    END IF;
WHEN "110010" | "110011"
    => IF (Z = Opcode(0)) THEN                               -- br on Z
        PC <= PC + D;
    END IF;
WHEN "110100" | "110101"
    => IF (C = Opcode(0)) THEN                               -- br on C
        PC <= PC + D;
    END IF;
WHEN "110110" | "110111"
    => IF (O = Opcode(0)) THEN                               -- br on V
        PC <= PC + D;

```



```

                                END IF;
WHEN others    => null;
END CASE;

IF ((Opcode(5 DOWNT0 4) = 0) or (Opcode(5 DOWNT0 4) = 1))
  and (Opcode /= 0) THEN
  -- set condition register
  IF (GPR(RT_Addr) = 0) THEN CR(0) <= '1';          -- zero result
  ELSE                        CR(0) <= '0';
  END IF;
  IF (GPR(RT_Addr)(31) = '1') THEN CR(1) <= '1'; -- negative result
  ELSE                        CR(1) <= '0';
  END IF;
  -- check if operation Opcode generates carry out
  CR(2) <= get_carry(RA_Data,RB_Data,Imm,Opcode);
  -- check if operation Opcode generates overflow
  CR(3) <= get_ovf(RA_Data,RB_Data,Imm,Opcode);
END IF;

WAIT FOR 0 ns;                -- force signals to be updated

```

```

IF (Phase = MemOp) THEN
  IF (dlength = '1') THEN                                -- ldw
    GPR(RT_addr) <= MemData;
  ELSE                                                    -- ldb
    GPR(RT_addr)( 7 DOWNT0 0) <= MemData(7 DOWNT0 0);
    GPR(RT_addr)(31 DOWNT0 8) <= (OTHERS => '0');
  END IF;
  WAIT FOR Fetch_delay;
END IF;

IF (Phase = IOOp) THEN
  IF (dlength = '1') THEN                                -- irw
    GPR(RT_addr) <= IOData;
  ELSE                                                    -- irb
    GPR(RT_addr)( 7 DOWNT0 0) <= IOData(7 DOWNT0 0);
    GPR(RT_addr)(31 DOWNT0 8) <= (OTHERS => '0');
  END IF;
  WAIT FOR Fetch_delay;
END IF;
END IF;
END PROCESS;

PROCESS                                                    -- output function

```

```

BEGIN
-- Instruction cycle
WAIT ON Phase;
IF (Phase = p_reset) THEN          -- reset
    MemRd <= '0'; MemWr <= '0'; MemEnable <= '0'; MemLength <= '0';
    MemData <= (OTHERS => 'Z');
    IORd  <= '0'; IOWr  <= '0'; IOEnable  <= '0'; IOLength  <= '0';
    IOData <= (OTHERS => 'Z');

ELSIF (Phase = Fetch) THEN        -- instruction fetch
    MemAddr  <= PC  AFTER delay;
    MemEnable <= '1' AFTER delay;
    MemRd    <= '1' AFTER Mdelay, '0' AFTER Pulse_Width;
    MemLength <= '1' AFTER delay;
    WAIT UNTIL MemRdy='1';        -- wait instr. fetch completed
    MemEnable <= '0' AFTER Fetch_delay;

ELSIF (Phase = Execute) THEN NULL; -- instruction execution
                                         -- no output signals

ELSIF (Phase = MemOp) THEN
    MemAddr  <= tMemAddr(23 DOWNT0 0) AFTER delay;
    MemEnable <= '1' AFTER delay;

```

```

MemLength <= dlength AFTER delay;
IF ((To_Bitvector(Opcode) = "100000") OR
    (To_Bitvector(Opcode) = "100001")) THEN    -- ldb, ldw
    MemRd      <= '1' AFTER Mdelay, '0' AFTER Pulse_Width;
    WAIT until MemRdy = '1';
    MemEnable  <= '0' AFTER Fetch_delay;
    WAIT FOR Fetch_delay;
END IF;
IF ((To_Bitvector(Opcode) = "100010") OR
    (To_Bitvector(Opcode) = "100011")) THEN    -- stb, stw
    MemWr      <= '1' AFTER Mdelay, '0' AFTER Pulse_Width;
    IF (dlength = '1') THEN                    -- stw
        MemData <= tData AFTER delay;
    ELSE                                        -- stb
        MemData(7 DOWNT0 0) <= tData(7 DOWNT0 0) AFTER delay;
    END IF;
    WAIT until MemRdy = '1';
    MemEnable  <= '0' AFTER delay;
    MemData    <= (OTHERS => 'Z') AFTER delay;
    WAIT FOR delay;
END IF;

ELSIF (Phase = IOOp) THEN

```

```

IOAddr      <= PN AFTER delay;
IOEnable    <= '1' AFTER delay;
IOLength    <= dlength AFTER delay;
IF ((To_Bitvector(Opcode) = "100100") OR
    (To_Bitvector(Opcode) = "100101")) THEN -- irb, irw
    IORd      <= '1' AFTER Mdelay, '0' AFTER Pulse_Width;
    WAIT until IORdy = '1' ;
    IOEnable  <= '0' AFTER Fetch_delay;
    WAIT FOR Fetch_delay;
END IF;
IF ((To_Bitvector(Opcode) = "100110") OR
    (To_Bitvector(Opcode) = "100111")) THEN -- iwb, iww
    IF (dlength = '1') THEN -- iww
        IOData <= tData AFTER delay;
    ELSE -- iwb
        IOData(7 DOWNT0 0) <= tData(7 DOWNT0 0) AFTER delay;
    END IF;
    IOWr      <= '1' AFTER Mdelay, '0' AFTER Pulse_Width;
    WAIT until IORdy = '1';
    IOEnable  <= '0' AFTER delay;
    IOData    <= (OTHERS => 'Z') AFTER delay;
    WAIT FOR delay;
END IF;

```

```
END IF;  
END PROCESS;  
END behavioral;
```

μ VHDL SPECIFICATION OF MEMORY CONTENTS

```

-- memory declaration
CONSTANT MaxMem: NATURAL:= 16#FFF#;    -- 4Kbytes
TYPE      MemArrayT IS ARRAY(0 to MaxMem-1) OF ByteT;
VARIABLE Mem : MemArrayT:=
  (
    -- program
    3=>"01100000", 2=>"00000000", 1=>"00000000", 0=>"00000000",
    7=>"01000100", 6=>"00100000", 5=>"00000000", 4=>"00110010",
    11=>"10000110", 10=>"10000001", 9=>"00000000", 8=>"00000000",
    15=>"10000110", 14=>"10100001", 13=>"00000000", 12=>"00000100",
    19=>"01000100", 18=>"01000000", 17=>"00000000", 16=>"00111111",
    23=>"10001000", 22=>"01000001", 21=>"00000000", 20=>"00000000",
    -- data
    51=>"00110011", 50=>"00001111", 49=>"11110000", 48=>"11001100",
    55=>"00110011", 54=>"00001111", 53=>"11110000", 52=>"11001100",
    OTHERS => "00000000");

```

where the memory contents corresponds to the following instructions:

```

0x000000: xor R0,R0,R0    ; R0 = 0
0x000004: adi R1,R0,50    ; R1 = 50
0x000008: ldw R20,0(R1)   ; R20= Mem(50,4)= Mem(48,4)
0x00000C: ldw R21,4(R1)   ; R21= Mem(54,4)= Mem(52,4)
0x000010: adi R2,R0,63    ; R2 = 63
0x000014: stb R2,0(R1)    ; Mem(50,1) = 63

0x000048: 0x330FF0CC
0x000052: 0x330FF0CC

```

IMPLEMENTATION OF XMC

- MEMORY SUBSYSTEM
- PROCESSOR
 1. DATA SUBSYSTEM
 2. CONTROL SUBSYSTEM

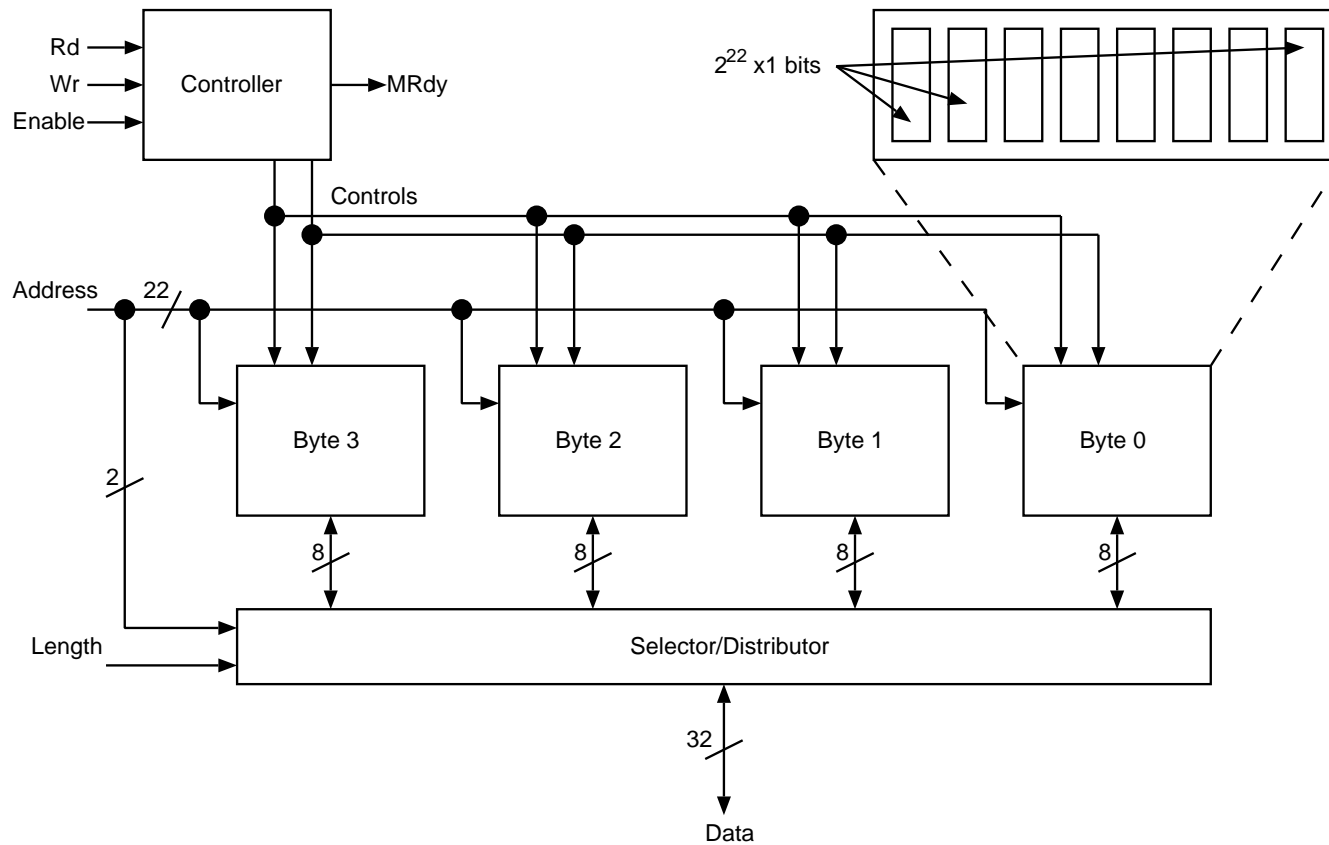


Figure 15.10: IMPLEMENTATION OF THE MEMORY SUBSYSTEM.

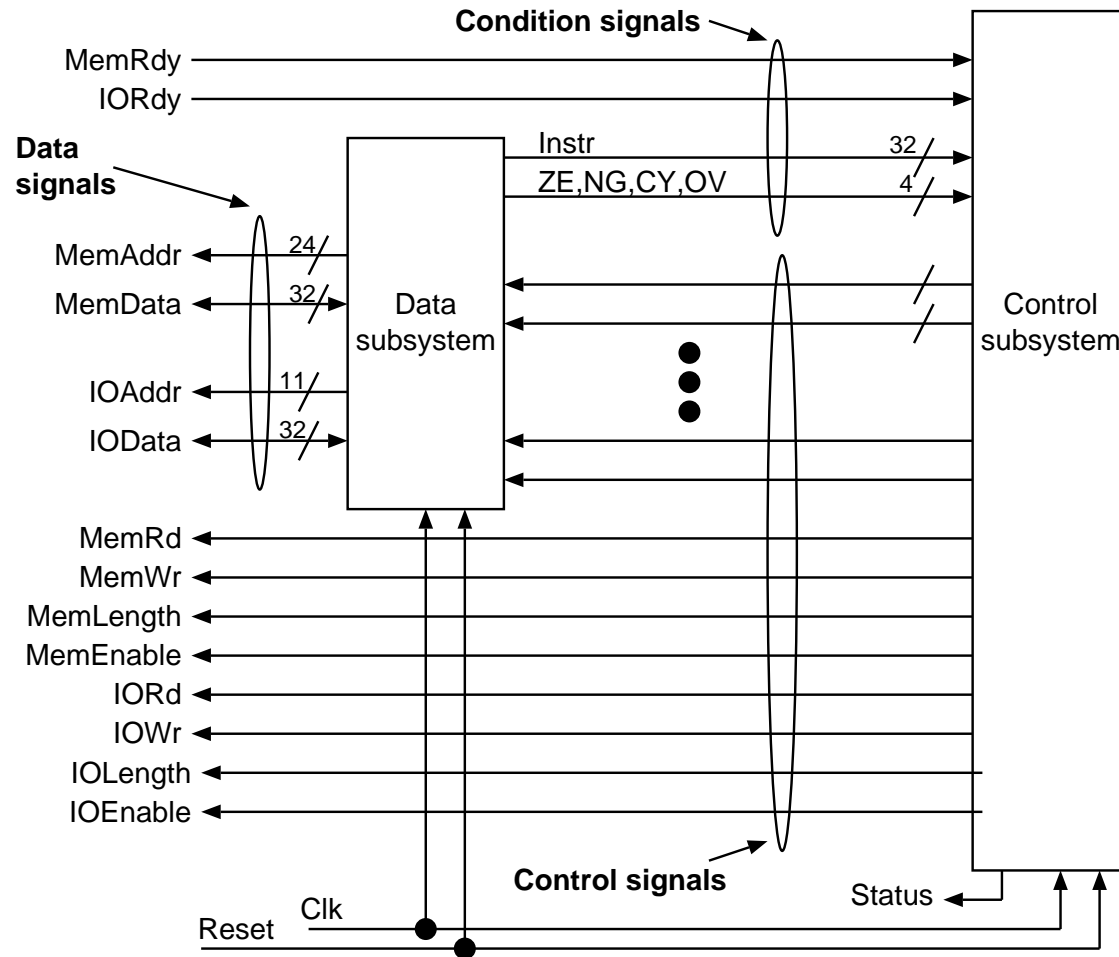


Figure 15.11: IMPLEMENTATION OF THE PROCESSOR.

DATA SUBSYSTEM

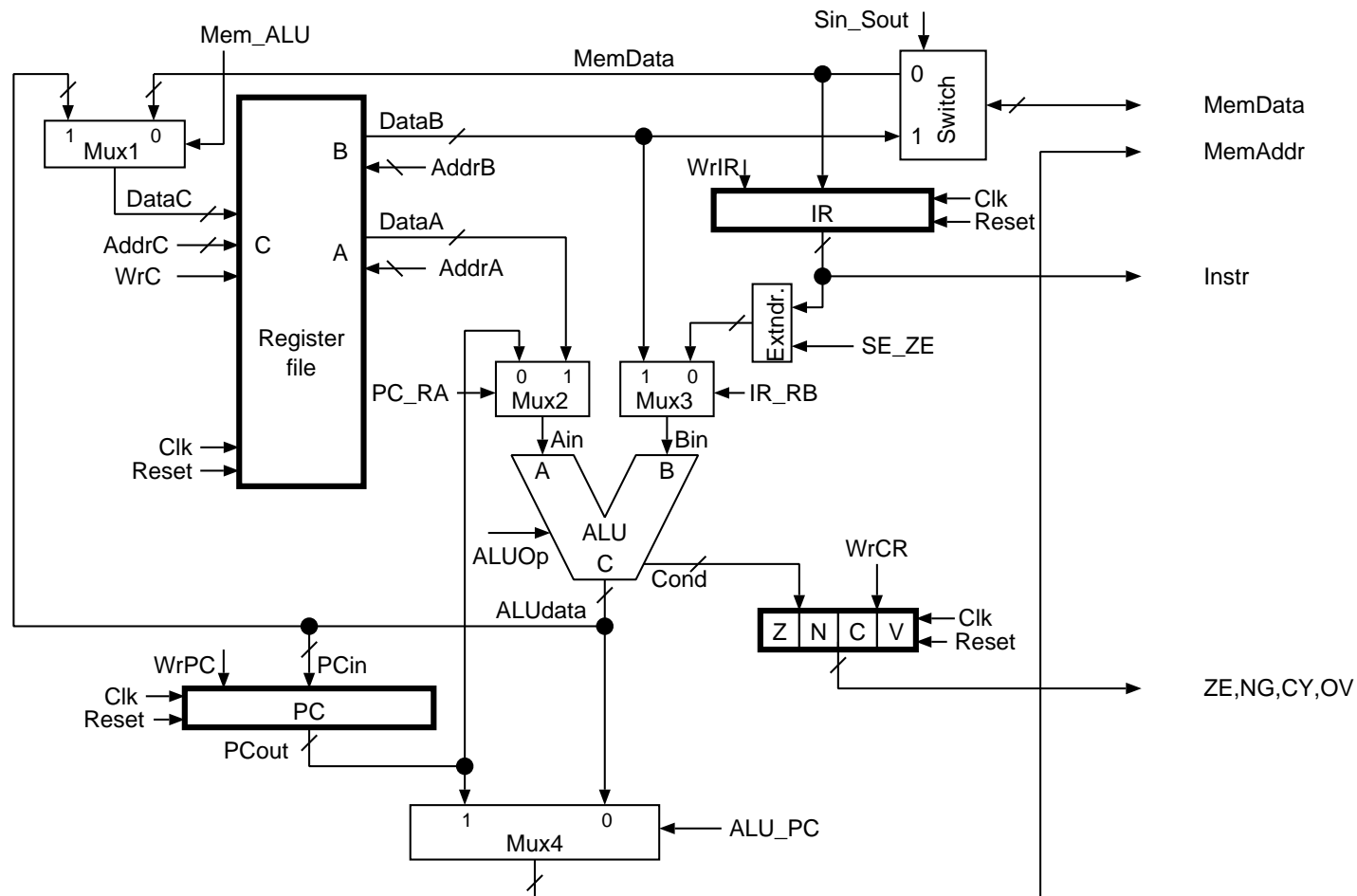


Figure 15.12: IMPLEMENTATION OF DATA SUBSYSTEM (I/O signals not shown).

ALU

ALUop	Operation
0000	Zero_32
0001	$A + B$
0010	$A - B$
0011	$-B$
0100	A and B
0101	A or B
0110	A xor B
0111	not(B)
1000	unused
1001	B
1010	shifl(A)
1011	shiftr(A)
1100	rotl(A)
1101	rotr(A)
1110	$A + 4$
1111	unused

EVENT SEQUENCE FOR ALU INSTRUCTION

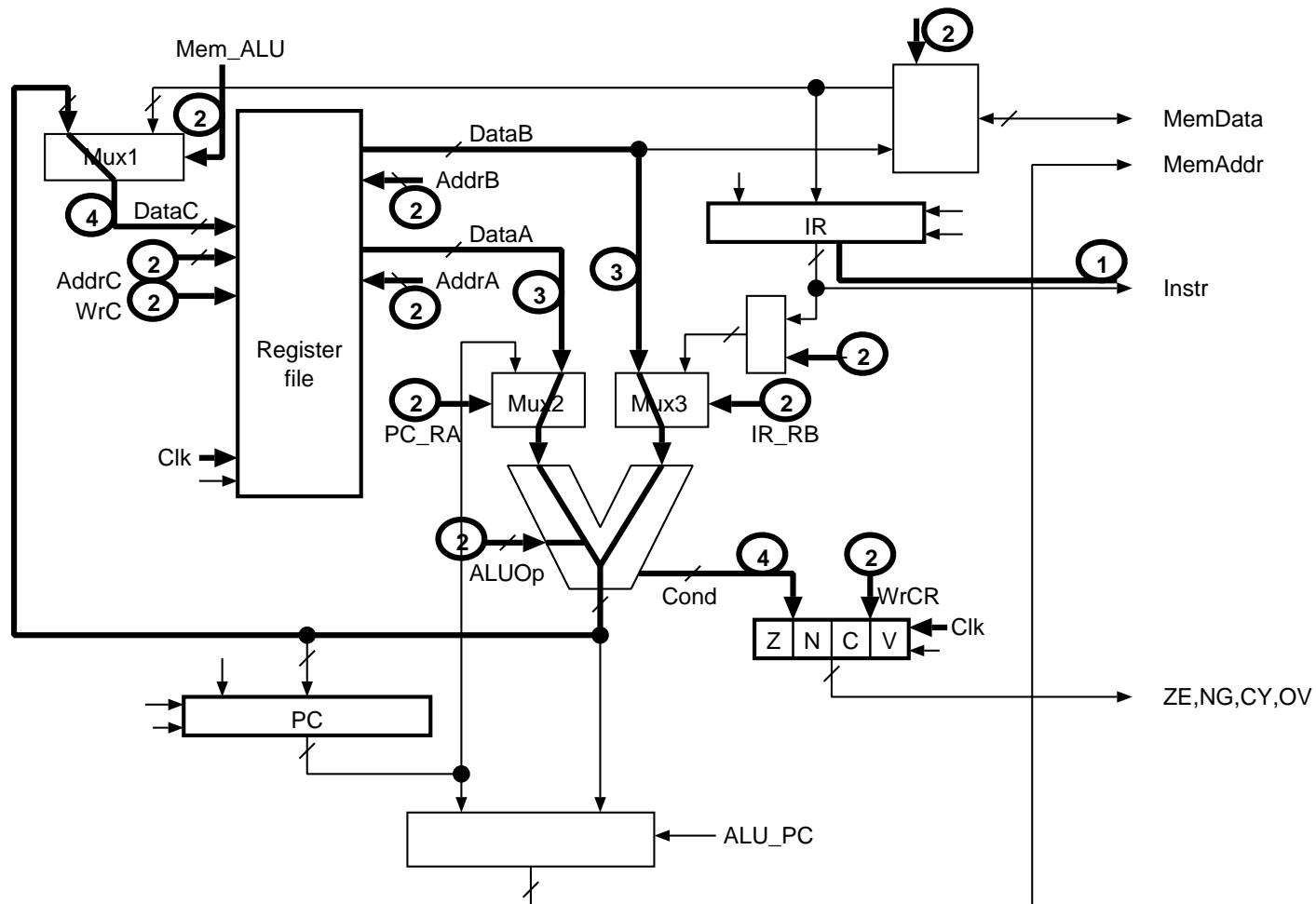


Figure 15.13: SEQUENCE OF EVENTS IN DATA SUBSYSTEM FOR ALU INSTRUCTION.

TIMING DIAGRAM FOR ALU INSTRUCTION

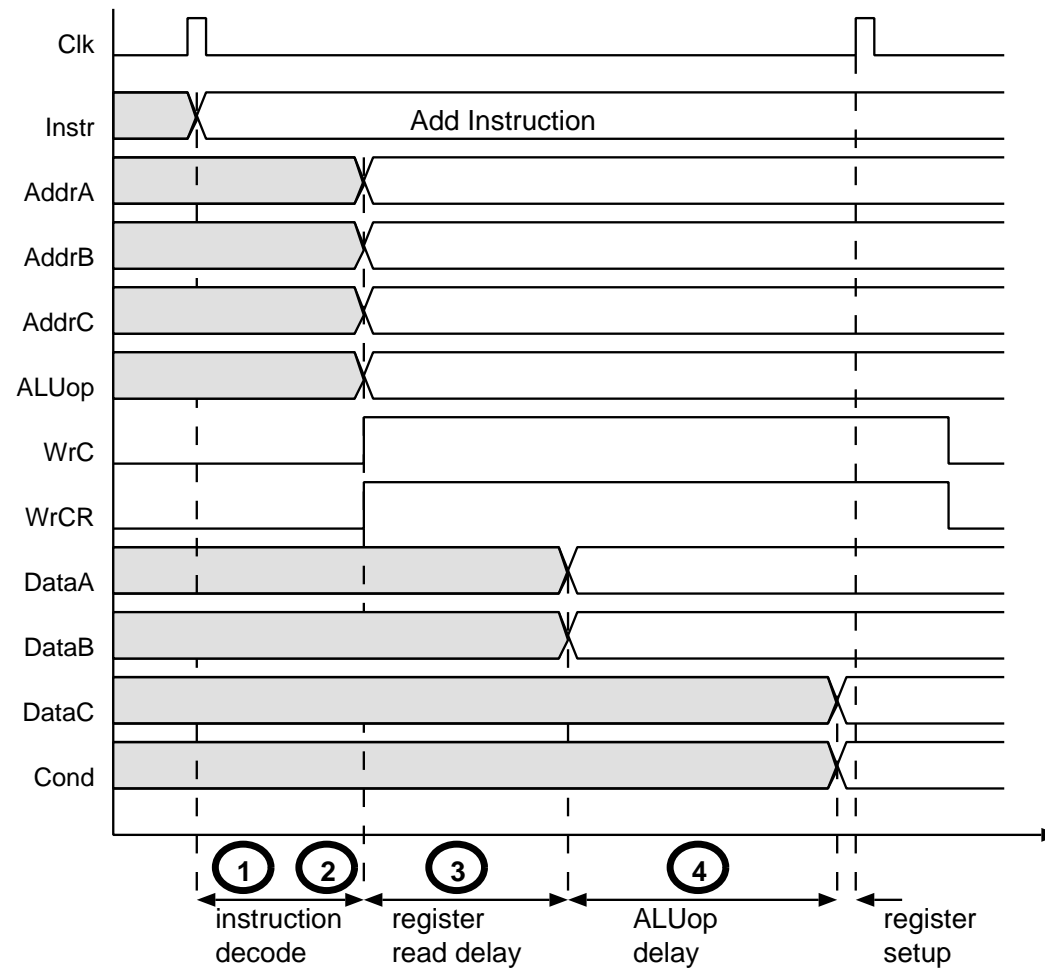


Figure 15.14: TIMING DIAGRAM FOR ALU INSTRUCTION IN DATA SUBSYSTEM.

CONTROL SUBSYSTEM

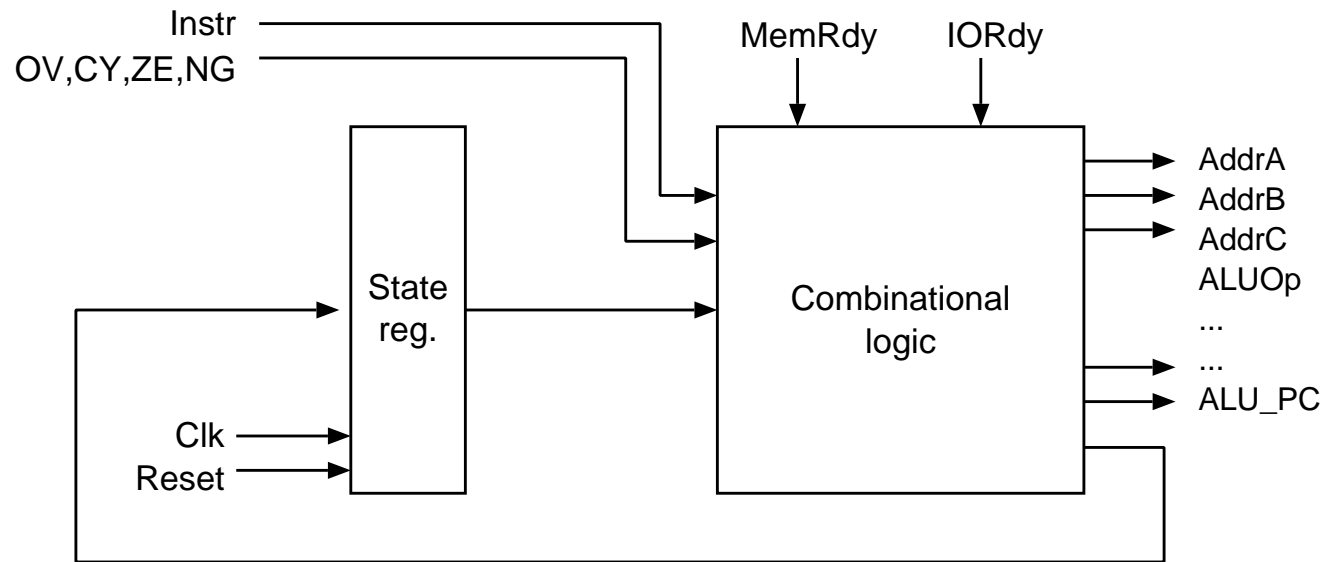


Figure 15.15: CONTROL SUBSYSTEM.

STATE DIAGRAM AND TIMING

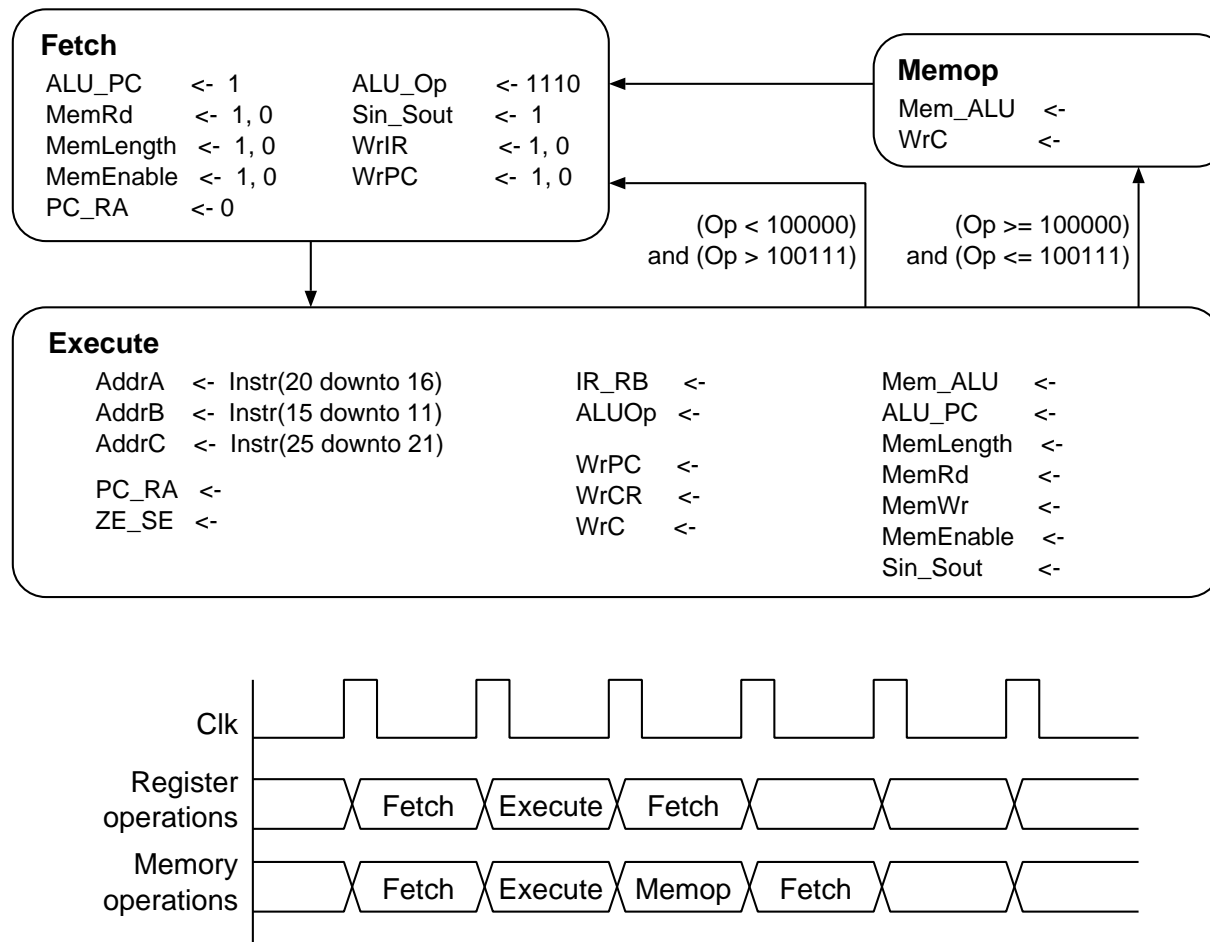


Figure 15.16: STATE DIAGRAM AND TIMING FOR CONTROL SUBSYSTEM OF THE PROCESSOR.

OPERATION OF THE COMPUTER AND CYCLE TIME

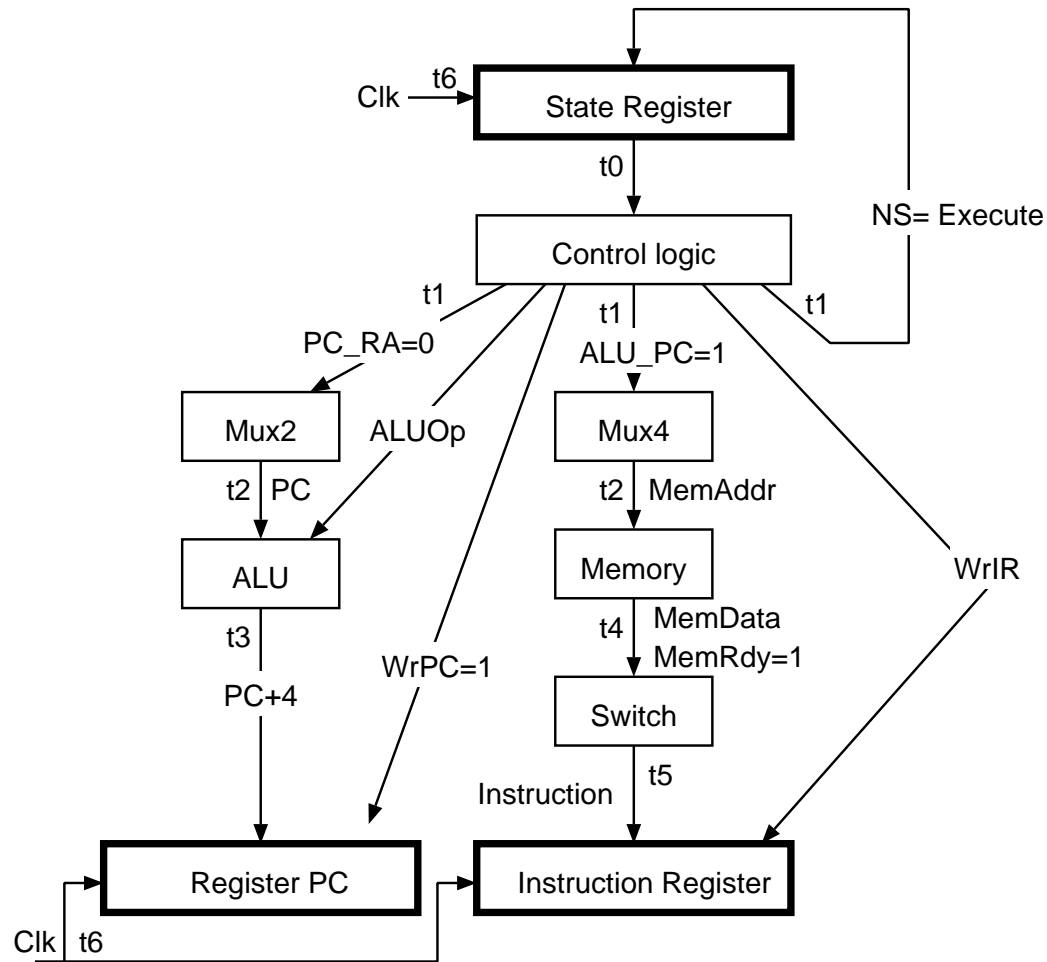


Figure 15.17: DEPENDENCIES FOR STATE FETCH.

STATE EXECUTE

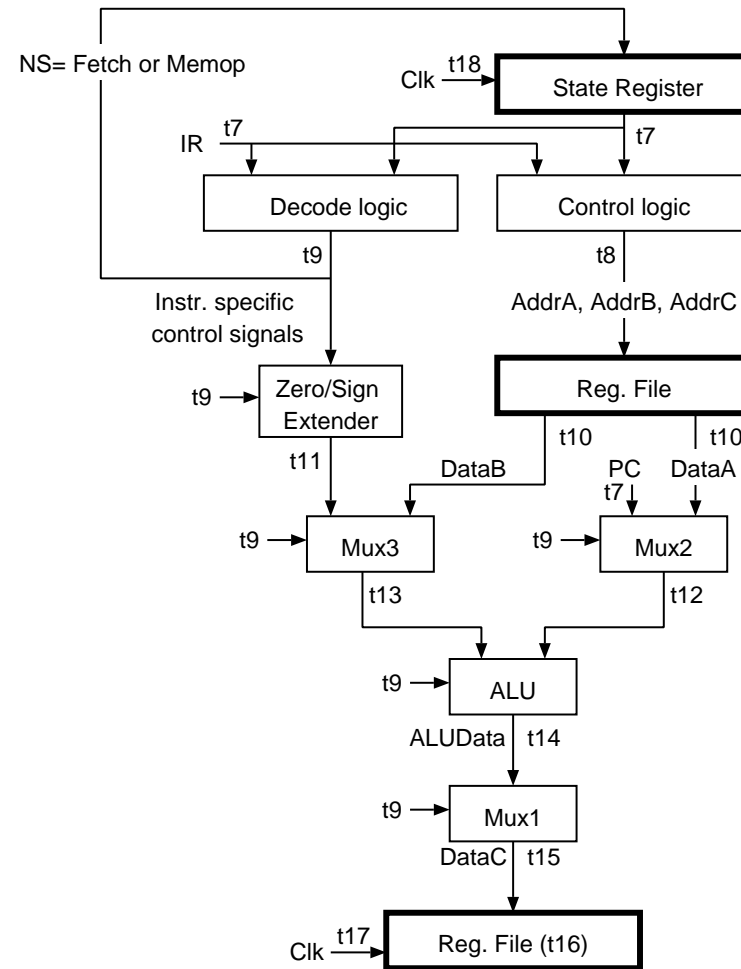


Figure 15.18: DEPENDENCIES FOR STATE EXECUTE.

STATE MEMOP

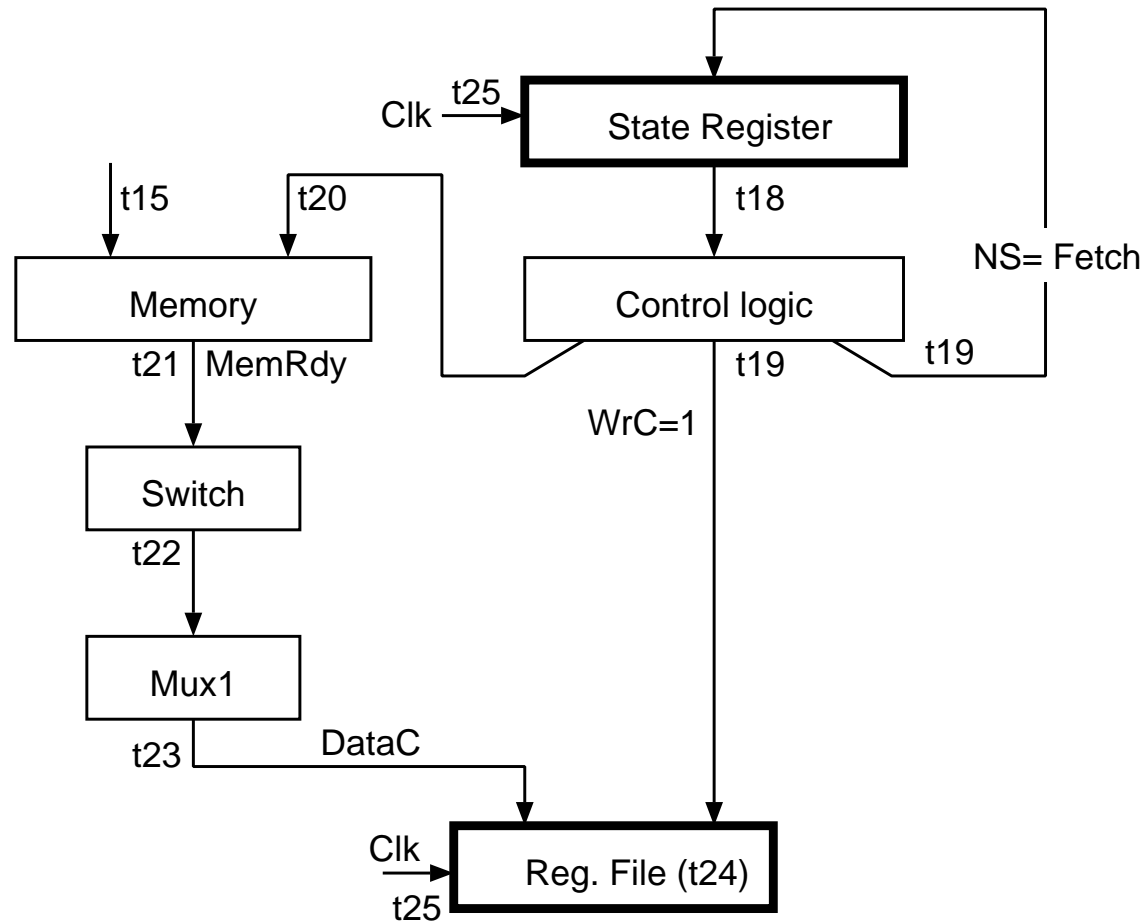


Figure 15.19: DEPENDENCIES FOR STATE Memop.

EXAMPLE 15.1: OBTAIN MIN CYCLE PERIOD

Register	Reg_delay	t_R	2 ns (setup and propagation delay)
Register file	RF_delay	t_{RF}	4 ns
ALU	ALU_delay	t_{ALU}	6 ns
Multiplexer	Mux_delay	t_{mux}	0.5 ns
Zero/sign ext.	Ext_delay	t_{ZSE}	0.5 ns
Switch	Switch_delay	t_{sw}	0.5 ns
Control delay	Ctrl_delay	t_{ctl}	0.5 ns
Decode delay	Dec_delay	t_{dec}	3 ns
Memory	Mem_delay	t_{mem}	8 ns (static memory)

CRITICAL PATHS ARE OBTAINED:

$$\begin{aligned} t_{fetch} &= t_R + t_{ctl} + t_{mux} + t_{mem} + t_{sw} \\ &= 2 + 0.5 + 1 + 8 + 0.5 = 12ns \end{aligned}$$

$$\begin{aligned} t_{exec} &= t_R + t_{ctl} + t_{RF} + t_{mux} + t_{ALU} + t_{mux} + t_{RF} \\ &= 2 + 0.5 + 4 + 0.5 + 6 + 0.5 + 4 = 17.5ns \end{aligned}$$

$$\begin{aligned} t_{memop} &= t_R + t_{ctl} + t_{mem} + t_{sw} + t_{mux} + t_{RF} \\ &= 2 + 0.5 + 8 + 0.5 + 0.5 + 4 = 15ns \end{aligned}$$

μ VHDL DESCRIPTION OF IMPLEMENTATION

```
LIBRARY ieee; USE ieee.std_logic_1164.ALL; USE WORK.comp_pkg.ALL, WORK.ALL;
```

```
ARCHITECTURE structural OF Processor IS
```

```
    SIGNAL Instr           : WordT;
    SIGNAL ZE, NG, CY, OV  : STD_LOGIC;
    SIGNAL AddrA, AddrB, AddrC : STD_LOGIC_VECTOR(4 DOWNTO 0);
    SIGNAL ALUOp           : STD_LOGIC_VECTOR(3 DOWNTO 0);
    SIGNAL WrC, WrPC, WrCR, WrIR : STD_LOGIC;
    SIGNAL Mem_ALU, PC_RA, IR_RB : STD_LOGIC;
    SIGNAL ALU_PC, ZE_SE, SinSout: STD_LOGIC;
```

```
BEGIN
```

```
    P1: ENTITY Data_Subsystem
```

```
        PORT MAP (MemAddr, MemData, IOAddr, IOData,
                  Instr, ZE, NG, CY, OV, AddrA, AddrB, AddrC, ALUOp,
                  WrC, WrPC, WrCR, WrIR, Mem_ALU, PC_RA, IR_RB, ALU_PC,
                  ZE_SE, SinSout, Clk, Reset);
```

```
    P2: ENTITY Ctrl_Subsystem
```

```
        PORT MAP (Instr, ZE, NG, CY, OV, AddrA, AddrB, AddrC, ALUOp,
                  WrC, WrPC, WrCR, WrIR, Mem_ALU, PC_RA, IR_RB, ALU_PC,
                  ZE_SE, SinSout, MemRd, MemWr, MemLength, MemEnable,
                  MemRdy, IORd, IOWr, IOLength, IOEnable, IORdy, Status,
                  Clk, Reset);
```

```
END structural;
```

μ VHDL DESCRIPTION OF DATA SUBSYSTEM

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE WORK.comp_pkg.ALL, WORK.ALL;
ENTITY Data_Subsystem IS
  PORT(MemAddr          : OUT  MAddrT    ;
        MemData         : INOUT WordT    ;
        IOAddr          : OUT  IOAddrT   ;
        IOData          : INOUT WordT    ;
        Instr           : OUT  WordT     ;
        ZE, NG, CY, OV  : OUT  STD_LOGIC ;
        AddrA, AddrB, AddrC : IN  STD_LOGIC_VECTOR(4 DOWNTO 0);
        ALUOp           : IN  STD_LOGIC_VECTOR(3 DOWNTO 0);
        WrC, WrPC, WrCR, WrIR : IN  STD_LOGIC ;
        Mem_ALU, PC_RA, IR_RB : IN  STD_LOGIC ;
        ALU_PC, ZE_SE, Sin_Sout: IN  STD_LOGIC ;
        Clk, Reset      : IN  STD_LOGIC);
END Data_Subsystem;

```

μ VHDL DESCRIPTION OF DATA SUBSYSTEM (cont.)

```

ARCHITECTURE structural OF Data_Subsystem IS
  SIGNAL DataA, DataB, DataC : WordT      ;
  SIGNAL Ain  , Bin          : WordT      ;
  SIGNAL ALUdata, IRdata     : WordT      ;
  SIGNAL tMemdata           : WordT      ;
  SIGNAL Cond, CRout        : STD_LOGIC_VECTOR(3 DOWNTO 0);
  SIGNAL IRreg, IReXT       : WordT      ;
  SIGNAL PCout              : WordT:= (OTHERS => '0');

BEGIN
  ALU1: ENTITY ALU
    PORT MAP(Ain,Bin,ALUop,ALUdata,Cond);
  GPR: ENTITY Reg_File
    PORT MAP(AddrA,AddrB,AddrC,DataA,DataB,DataC,
             WrC,Reset,Clk);
  PC:  ENTITY Reg
    PORT MAP(ALUdata(23 DOWNTO 0),PCout(23 DOWNTO 0),
             WrPC,Reset,Clk);
  CR:  ENTITY Reg
    PORT MAP(Cond,CRout,WrCR,Reset,Clk);

  ZE <= CRout(0);  CY <= CRout(1);
  NG <= CRout(2);  OV <= CRout(3);

```

```

IR: ENTITY Reg
    PORT MAP(tMemData,IRReg,WrIR,Reset,Clk);

    Instr <= IRReg;

MX1: ENTITY Mux
    PORT MAP(tMemData,ALUdata,Mem_ALU,DataC);
MX2: ENTITY Mux
    PORT MAP(PCout,DataA,PC_RA,Ain);
ZSE: ENTITY Extender
    PORT MAP(IRreg,ZE_SE,IRe xt);
MX3: ENTITY Mux
    PORT MAP(IRe xt,DataB,IR_RB,Bin);
MX4: ENTITY Mux
    PORT MAP(ALUdata(23 DOWNTO 0),PCout(23 DOWNTO 0),
              ALU_PC,MemAddr);

SL : ENTITY Switch
    PORT MAP(MemData,tMemData,DataB,Sin_Sout);
END structural;

```


μ VHDL DESCRIPTION OF REGISTER FILE

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;
USE WORK.comp_pkg.ALL;

ENTITY Reg_File IS
    PORT(AddrA, AddrB, AddrC : IN  STD_LOGIC_VECTOR(4 DOWNTO 0);
          DataA, DataB      : OUT WordT;
          DataC             : IN  WordT;
          WrC               : IN  STD_LOGIC ;
          Reset, Clk        : IN  STD_LOGIC);
END Reg_File;

ARCHITECTURE behavioral OF Reg_File IS
    TYPE      RegFileT IS ARRAY(0 to 31) OF WordT;
    SIGNAL    GPR : RegFileT      ;
BEGIN
    PROCESS(AddrA,AddrB)          -- output function
        CONSTANT RF_delay      : TIME := 4 ns;
    BEGIN
        DataA <= GPR(CONV_INTEGER(AddrA)) AFTER RF_delay;
        DataB <= GPR(CONV_INTEGER(AddrB)) AFTER RF_delay;
    END PROCESS;

```

```
PROCESS(Reset,Clk)           -- transition function
BEGIN
  IF (Reset'EVENT and (Reset = '1')) THEN
    FOR i IN 0 TO 31 LOOP
      GPR(i) <= (OTHERS => '0');
    END LOOP;
  END IF;

  IF (Clk'EVENT AND Clk = '1' AND WrC = '1') THEN
    GPR(CONV_INTEGER(AddrC)) <= DataC;
  END IF;
END PROCESS;
END behavioral;
```

μ VHDL DESCRIPTION OF ALU

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_signed.ALL;
USE WORK.comp_pkg.ALL;

ENTITY ALU IS
  PORT(A, B: IN  STD_LOGIC_VECTOR(31 DOWNT0 0);
       Op  : IN  STD_LOGIC_VECTOR( 3 DOWNT0 0);
       C   : OUT STD_LOGIC_VECTOR(31 DOWNT0 0);
       Cond: OUT STD_LOGIC_VECTOR( 3 DOWNT0 0));
END ALU;

ARCHITECTURE behavioral OF ALU IS
BEGIN
  PROCESS(A,B,Op)
    CONSTANT ALU_delay  : TIME := 6 ns;
  BEGIN
    CASE Op IS
      WHEN "0000" => C <= (OTHERS => '0') AFTER ALU_delay;
      WHEN "0001" => C <= A + B           AFTER ALU_delay;
      WHEN "0010" => C <= A - B           AFTER ALU_delay;
      WHEN "0011" => C <= (OTHERS => '0') AFTER ALU_delay;
      WHEN "0100" => C <= A and B        AFTER ALU_delay;
      WHEN "0101" => C <= A or  B        AFTER ALU_delay;
      WHEN "0110" => C <= A xor B        AFTER ALU_delay;
      WHEN "0111" => C <= (OTHERS => '0') AFTER ALU_delay;
    END CASE;
  END PROCESS;
END ARCHITECTURE behavioral;

```

```
    WHEN "1000" => C <= A                AFTER ALU_delay;
    WHEN "1001" => C <= B                AFTER ALU_delay;
    WHEN "1010" => C <= A(30 DOWNT0 0) & '0'  AFTER ALU_delay;
    WHEN "1011" => C <= '0' & A(31 DOWNT0 1)  AFTER ALU_delay;
    WHEN "1100" => C <= A(30 DOWNT0 0) & A(31) AFTER ALU_delay;
    WHEN "1101" => C <= A(0) & A(31 DOWNT0 1)  AFTER ALU_delay;
    WHEN "1110" => C <= A + 4            AFTER ALU_delay;
    WHEN "1111" => C <= not(A)          AFTER ALU_delay;
    WHEN OTHERS => NULL;
END CASE;
Cond <= get_cc(A,B,Op) AFTER ALU_delay;
END PROCESS;
END behavioral;
```

μ VHDL DESCRIPTION OF REGISTERS

```

LIBRARY ieee; USE ieee.std_logic_1164.ALL;

ENTITY Reg IS
  PORT(Data_in : IN  STD_LOGIC_VECTOR;
        Data_out: OUT STD_LOGIC_VECTOR;
        Wr      : IN  STD_LOGIC ;
        Reset   : IN  STD_LOGIC ;
        Clk     : IN  STD_LOGIC);
END Reg;

ARCHITECTURE behavioral OF Reg IS
BEGIN
  PROCESS(Wr,Reset,Clk)
    CONSTANT Reg_delay: TIME := 2 ns;
    VARIABLE BVZero: STD_LOGIC_VECTOR(Data_in'RANGE):= (OTHERS => '0');
  BEGIN
    IF (Reset = '1') THEN
      Data_out <= BVZero AFTER Reg_delay;
    END IF;

    IF (Clk'EVENT AND Clk = '1' AND Wr = '1') THEN
      Data_out <= Data_in AFTER Reg_delay;
    END IF;
  END PROCESS;
END behavioral;

```

μ VHDL DESCRIPTION OF OTHER MODULES: MUX

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Mux IS
    PORT(A_in,B_in: IN  STD_LOGIC_VECTOR;
         Sel      : IN  STD_LOGIC      ;
         Data_out : OUT STD_LOGIC_VECTOR);
END Mux;

ARCHITECTURE behavioral OF Mux IS
BEGIN
    PROCESS(A_in, B_in, Sel)
        CONSTANT Mux_delay: TIME := 500 ps;
    BEGIN
        IF (Sel = '0') THEN
            Data_out <= A_in AFTER Mux_delay;
        ELSE
            Data_out <= B_in AFTER Mux_delay;
        END IF;
    END PROCESS;
END behavioral;
```

μ VHDL DESCRIPTION OF EXTENDER

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Extender IS
  PORT(X_in  : IN  STD_LOGIC_VECTOR(31 DOWNT0 0);
        ZE_SE : IN  STD_LOGIC
        ;
        X_out : OUT STD_LOGIC_VECTOR(31 DOWNT0 0));
END Extender;

ARCHITECTURE behavioral OF Extender IS
BEGIN
  PROCESS(X_in, ZE_SE)
    CONSTANT Ext_delay: TIME := 500 ps;
  BEGIN
    IF (ZE_SE = '0') THEN
      X_out(31 DOWNT0 16) <= (OTHERS => '0') AFTER Ext_delay;
      X_out(15 DOWNT0 0) <= X_in(15 DOWNT0 0) AFTER Ext_delay;
    ELSE
      X_out(31 DOWNT0 16) <= (OTHERS => X_in(15)) AFTER Ext_delay;
      X_out(15 DOWNT0 0) <= X_in(15 DOWNT0 0) AFTER Ext_delay;
    END IF;
  END PROCESS;
END behavioral;

```

μ VHDL DESCRIPTION OF SWITCH

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Switch IS
    PORT(A      : INOUT STD_LOGIC_VECTOR;
          B_out: OUT   STD_LOGIC_VECTOR;
          C_in  : IN   STD_LOGIC_VECTOR;
          Sel   : IN   STD_LOGIC       );
END Switch;

ARCHITECTURE behavioral OF Switch IS
BEGIN
    PROCESS(A, C_in, Sel)
        CONSTANT Switch_delay: TIME := 500 ps;
        CONSTANT dataZ: STD_LOGIC_VECTOR(A'RANGE) := (OTHERS => 'Z');
    BEGIN
        IF (Sel = '0') THEN
            B_out <= A AFTER Switch_delay;
            A      <= dataZ;
        ELSE
            A      <= C_in AFTER Switch_delay;
        END IF;
    END PROCESS;
END behavioral;
```


μ VHDL DESCRIPTION OF CONTROL SYSTEM

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE WORK.comp_pkg.ALL;

ENTITY Ctrl_Subsystem IS
  PORT(Instr           : IN      WordT           ;
        ZE, NG, CY, OV : IN      STD_LOGIC      ;
        AddrA, AddrB, AddrC : OUT    STD_LOGIC_VECTOR(4 DOWNTO 0);
        ALUOp          : OUT    STD_LOGIC_VECTOR(3 DOWNTO 0);
        WrC, WrPC, WrCR, WrIR : OUT    STD_LOGIC      ;
        Mem_ALU, PC_RA, IR_RB : OUT    STD_LOGIC      ;
        ALU_PC, ZE_SE, Sin_Sout: OUT    STD_LOGIC      ;
        MemRd, MemWr      : OUT    STD_LOGIC      ;
        MemLength        : OUT    STD_LOGIC      ;
        MemEnable        : OUT    STD_LOGIC      ;
        MemRdy           : IN      STD_LOGIC      ;
        IORd, IOWr       : OUT    STD_LOGIC      ;
        IOLength         : OUT    STD_LOGIC      ;
        IOEnable         : OUT    STD_LOGIC      ;
        IORdy            : IN      STD_LOGIC      ;
        Status           : OUT    StatusT        ;
        Clk, Reset       : IN      STD_LOGIC     );
END Ctrl_Subsystem;

```

μ VHDL DESCRIPTION OF CONTROL SYSTEM (cont.)

```

LIBRARY ieee;
USE ieee.std_logic_signed.ALL;

ARCHITECTURE behavioral OF Ctrl_Subsystem IS
    SIGNAL State: StatusT;
BEGIN
PROCESS                                     -- transition function
    ALIAS    Opcode : STD_LOGIC_VECTOR(5 DOWNT0 0) IS Instr(31 DOWNT0 26);
    CONSTANT Reset_delay: TIME:= 500 ps ;
    CONSTANT Ctrl_delay : TIME:= 500 ps ;
BEGIN
    WAIT ON Clk,Reset;
    IF (Reset'EVENT AND Reset = '1') THEN
        State  <= p_reset AFTER Reset_delay;
        Status <= p_reset AFTER Reset_delay;
        WAIT UNTIL Clk = '1';
    END IF;

    IF (Clk'EVENT) AND (Clk = '1') THEN
        CASE State IS
        WHEN p_reset      => Status <= fetch    AFTER Ctrl_delay;
                           State  <= fetch    AFTER Ctrl_delay;
        WHEN fetch       => Status <= execute  AFTER Ctrl_delay;
                           State  <= execute  AFTER Ctrl_delay;
        
```

```

WHEN execute      => CASE Opcode IS
  WHEN "100000" | "100001" => State  <= memop AFTER Ctrl_delay;
                           Status <= memop AFTER Ctrl_delay;
  WHEN "100010" | "100011" => State  <= memop AFTER Ctrl_delay;
                           Status <= memop AFTER Ctrl_delay;
  WHEN OTHERS      => State  <= fetch AFTER Ctrl_delay;
                           Status <= fetch AFTER Ctrl_delay;
                           END CASE;
WHEN memop | ioop => Status <= fetch  AFTER Ctrl_delay;
                           State  <= fetch  AFTER Ctrl_delay;
WHEN undef       => NULL;
END CASE;
END IF;
END PROCESS;

PROCESS(State,Instr,MemRdy)                                -- output function
  ALIAS  Opcode : STD_LOGIC_VECTOR( 5 DOWNT0 0) IS Instr(31 DOWNT0 26);
  ALIAS  Imm    : STD_LOGIC_VECTOR(15 DOWNT0 0) IS Instr(15 DOWNT0  0);
  ALIAS  D      : STD_LOGIC_VECTOR(15 DOWNT0 0) IS Instr(15 DOWNT0  0);
  ALIAS  PN     : STD_LOGIC_VECTOR(10 DOWNT0 0) IS Instr(10 DOWNT0  0);

  CONSTANT Dec_delay  : TIME:= 3 ns;
  CONSTANT Ctrl_delay : TIME:= 500 ps;
  CONSTANT MemRd_delay: TIME:= 2500 ps;
  CONSTANT MemRd_pulse: TIME:= MemRd_delay + 3 ns ;
  CONSTANT MemWr_delay: TIME:= 2500 ps;
  CONSTANT MemWr_pulse: TIME:= MemWr_delay + 3 ns ;

```

```

TYPE      Ctrl_LineT IS
  RECORD
    MemOp, WrMem      : STD_LOGIC;
    RS_RB, IR_RB      : STD_LOGIC;
    WrC, WrPC, WrCR   : STD_LOGIC;
    ZE_SE              : STD_LOGIC;
    ALUop              : STD_LOGIC_VECTOR(3 DOWNTO 0);
  END RECORD;

VARIABLE Ctrl_Line   : Ctrl_LineT;

TYPE      Ctrl_TableT IS ARRAY(NATURAL RANGE 0 TO 63) OF Ctrl_LineT;

CONSTANT Ctrl_Table: Ctrl_TableT:=
  --      Mem   Wr   RS   IR   Wr   Wr   Wr   ZE   ALU
  --      Op    Mem  RB   RB   C    PC   CR   SE   op
  (0 => ('0', '0', '1', '1', '0', '0', '0', '0', "0000"), -- nop
  2 => ('0', '0', '1', '1', '1', '0', '1', '0', "1111"), -- not
  4 => ('0', '0', '1', '1', '1', '0', '1', '0', "1010"), -- lsh
  6 => ('0', '0', '1', '1', '1', '0', '1', '0', "1011"), -- rsh
  8 => ('0', '0', '1', '1', '1', '0', '1', '0', "1100"), -- lrt
  10=> ('0', '0', '1', '1', '1', '0', '1', '0', "1101"), -- rrt

  16=> ('0', '0', '1', '1', '1', '0', '1', '0', "0001"), -- add
  17=> ('0', '0', '1', '0', '1', '0', '1', '1', "0001"), -- adi
  18=> ('0', '0', '1', '1', '1', '0', '1', '0', "0010"), -- sub
  19=> ('0', '0', '1', '0', '1', '0', '1', '1', "0010"), -- sbi
  20=> ('0', '0', '1', '1', '1', '0', '1', '0', "0100"), -- and
  21=> ('0', '0', '1', '0', '1', '0', '1', '0', "0100"), -- ani

```

```

22=> ('0', '0', '1', '1', '1', '0', '1', '0', "0101"), -- or
23=> ('0', '0', '1', '0', '1', '0', '1', '0', "0101"), -- ori
24=> ('0', '0', '1', '1', '1', '0', '1', '0', "0110"), -- xor
25=> ('0', '0', '1', '0', '1', '0', '1', '0', "0110"), -- xri

32=> ('1', '0', '0', '0', '1', '0', '0', '1', "0001"), -- ldb
33=> ('1', '0', '0', '0', '1', '0', '0', '1', "0001"), -- ldw
34=> ('1', '1', '0', '0', '0', '0', '0', '1', "0001"), -- stb
35=> ('1', '1', '0', '0', '0', '0', '0', '1', "0001"), -- stw
36=> ('1', '0', '0', '1', '1', '0', '0', '0', "1001"), -- irb
37=> ('1', '0', '0', '1', '1', '0', '0', '0', "1001"), -- irw
38=> ('1', '1', '0', '1', '0', '0', '0', '0', "1001"), -- iwb
39=> ('1', '1', '0', '1', '0', '0', '0', '0', "1001"), -- iww

56=> ('0', '0', '1', '0', '0', '1', '0', '1', "0001"), -- br
57=> ('0', '0', '1', '0', '0', '1', '0', '1', "1000"), -- bri
48=> ('0', '0', '1', '0', '0', '1', '0', '1', "0001"), -- brp
49=> ('0', '0', '1', '0', '0', '1', '0', '1', "0001"), -- brn
50=> ('0', '0', '1', '0', '0', '1', '0', '1', "0001"), -- bnz
51=> ('0', '0', '1', '0', '0', '1', '0', '1', "0001"), -- brz
52=> ('0', '0', '1', '0', '0', '1', '0', '1', "0001"), -- bnc
53=> ('0', '0', '1', '0', '0', '1', '0', '1', "0001"), -- brc
54=> ('0', '0', '1', '0', '0', '1', '0', '1', "0001"), -- bnv
55=> ('0', '0', '1', '0', '0', '1', '0', '1', "0001"), -- brv
OTHERS => ('0', '0', '1', '1', '0', '0', '0', '1', "0000")
);

```

```

BEGIN
IF (State'EVENT) THEN
  CASE State IS
  WHEN undef      => NULL;
  WHEN p_reset    => ALUOp  <= "0000";
                   MemRd   <= '0';   MemWr <= '0';
                   MemEnable <= '0'; MemLength <= '0';
                   IORd    <= '0';   IOWr <= '0';
                   IOEnable <= '0';  IOLength <= '0';

  WHEN fetch      =>
    -- disable write signals from previous cycle
    WrCR          <= '0' AFTER Ctrl_delay;
    WrC           <= '0' AFTER Ctrl_delay;

    -- fetch instruction
    ALU_PC        <= '1' AFTER Ctrl_delay;
    MemLength<= '1' AFTER Ctrl_delay;
    MemEnable<= '1' AFTER Ctrl_delay;
    MemRd         <= '1' AFTER MemRd_delay, '0' AFTER MemRd_pulse;
    Sin_Sout      <= '0' AFTER Ctrl_delay;           -- switch in

    -- increment PC
    PC_RA         <= '0' AFTER Ctrl_delay;
    ALUOp         <= "1110" AFTER Ctrl_delay;       -- PC + 4
    WrIR          <= '1' AFTER Ctrl_delay;
    WrPC          <= '1' AFTER Ctrl_delay;

```

```

WHEN execute =>
    -- disable signals from fetch cycle
    WrIR      <= '0' AFTER Ctrl_delay;
    WrPC      <= '0' AFTER Ctrl_delay;
    MemEnable<= '0' AFTER Ctrl_delay;

    -- other actions done by Instr'EVENT

WHEN memop | ioop =>
    -- initiate memory access
    ALU_PC    <= '0' AFTER Ctrl_delay;      -- address to memory
    MemEnable<= '1' AFTER Ctrl_delay;
    MemLength<= Opcode(0) AFTER Ctrl_delay; -- operand length
    WrC       <= Ctrl_Line.WrC AFTER Ctrl_delay;
    IF (Ctrl_Line.WrMem = '0') THEN
        MemRd      <= '1' AFTER MemRd_delay, '0' AFTER MemRd_pulse;
        Mem_ALU    <= '0' AFTER Ctrl_delay;
    ELSE
        MemWr      <= '1' AFTER MemWr_delay, '0' AFTER MemWr_pulse;
        Sin_Sout   <= '1' AFTER Ctrl_delay;
    END IF;
END CASE;
END IF;

```

```

IF (Instr'EVENT) THEN
  -- decode opcode
  Ctrl_Line:= Ctrl_Table(CONV_INTEGER('0' & Opcode));

  -- decode registers
  AddrA  <= Instr(20 DOWNT0 16) AFTER Dec_delay;
  IF (Ctrl_Line.RS_RB = '0') THEN
    AddrB <= Instr(25 DOWNT0 21) AFTER Dec_delay;
  ELSE
    AddrB <= Instr(15 DOWNT0 11) AFTER Dec_delay;
  END IF;
  AddrC  <= Instr(25 DOWNT0 21) AFTER Dec_delay;

  -- decode control signals
  PC_RA  <= not(Ctrl_Line.WrPC) AFTER Ctrl_delay;
  ZE_SE  <= Ctrl_Line.ZE_SE AFTER Ctrl_delay;
  IR_RB  <= Ctrl_Line.IR_RB AFTER Ctrl_delay;
  ALUOp  <= Ctrl_Line.ALUop AFTER Ctrl_delay;
  WrPC   <= Ctrl_Line.WrPC  AFTER Ctrl_delay;
  WrCR   <= Ctrl_Line.WrCR  AFTER Ctrl_delay;

  IF (Ctrl_Line.MemOp = '0') THEN
    WrC    <= Ctrl_Line.WrC AFTER Ctrl_delay;
    Mem_ALU <= '1' AFTER Ctrl_delay;
  END IF;
END IF;

```



```
IF (MemRdy'EVENT AND MemRdy='1') THEN
  CASE State IS
    WHEN memop => IF (Ctrl_Line.WrMem = '1') THEN
      -- deactivate data bus
      Sin_Sout <= '0' AFTER Ctrl_delay;
    END IF;
    WHEN OTHERS => NULL;
  END CASE;
END IF;
END PROCESS;
END behavioral;
```