

# Chameleon: A Dual-Mode Bluetooth/WiFi Receiver Design



IEEE CAS Society  
Chapter at Dallas, Texas

Ahmed Emira, Alberto Valdes-Garcia, Bo Xia, Ahmed Mohieldin,  
Ari Valero-Lopez, Sung Tae Moon and Chunyu Xin.


**Faculty Advisor: Dr. Edgar Sánchez-Sinencio**

**Analog & Mixed-Signal Center (AMSC)**  
**Texas A&M University**

# Outline

- Previous work: Bluetooth Receiver in CMOS 0.35 $\mu$ m
- System Level Design
  - Technology features
  - Main Bluetooth and Wi-Fi specs
  - Previously reported architectures
  - Proposed dual-mode architecture
  - Impact of non-idealities on the BER performance
- Building Blocks
  - LNA
  - Mixer
  - VCO and PLL
  - VGA
  - ADC
- Experimental Results


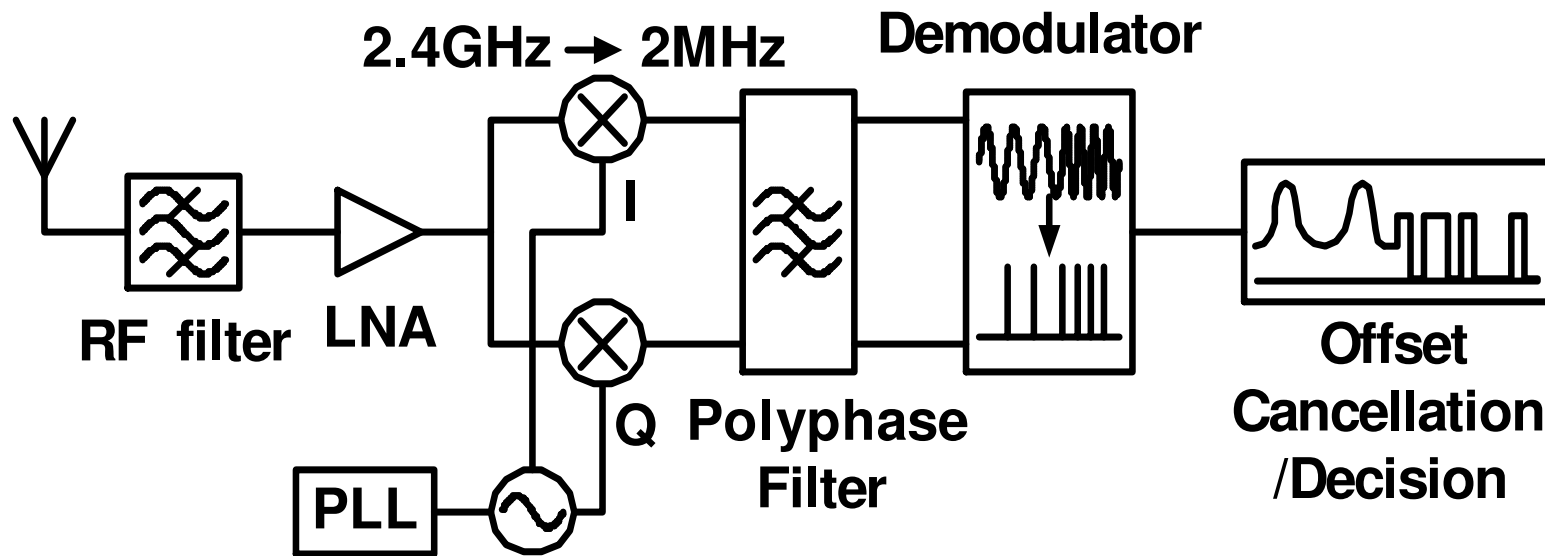
# 0.35 $\mu\text{m}$ CMOS Bluetooth Low-IF Receiver IC



Developed during 2001 and 2002 at the AMSC.

Authors: Wenjun Sheng, Bo Xia, Ahmed Emira, Chunyu Xin, Ari Ari Valero-Lopez, Sung Tae Moon and Edgar Sanchez-Sinencio.
  
# 0.35 $\mu$ m CMOS Bluetooth Low-IF Receiver IC



- Publications:

- 2002 RFIC Conference, Best Student Paper Award (third place).
- Journal of Solid-State Circuits: January 2003 (Receiver) and August 2003 (Demodulator).
- Transactions on Circuits and Systems – II: November 2003 (Complex Filter).

# Chameleon Receiver: Timeline

<i>Phase</i>	<i>2002</i>			<i>2003</i>		
	Spring	Summer	Fall	Spring	Summer	Fall
802.11b/Bluetooth standards study	■					
Dual-mode architectures survey	■					
Baseband BER simulations		■				
Rx System Specifications		■				
Building Block Specifications		■				
Circuit Level Design			■			
Layout and Chip Submission				■		
PCB Design for Block and System Testing					■	
Block and System Testing					■	
Paper Submission to ISSCC						■

# Chameleon Receiver

- Previous work: Bluetooth Receiver in CMOS 0.35 $\mu$ m
- **System Level Design**
  - Technology features
  - Main Bluetooth and Wi-Fi specs
  - Previously reported architectures
  - Proposed dual-mode architecture
  - Impact of non-idealities on the BER performance
- Building Blocks
  - LNA
  - Mixer
  - VCO and PLL
  - VGA
  - ADC
- Experimental Results

# Technology features

- IBM SiGe BiCMOS 6HP 0.25um
- Transit frequency ( $f_T$ ) 47GHz
- 6 aluminum metal layers
- Analog metal (4um thick,  $0.00725 \Omega/\square$ )
- Varactor diode (intrinsic base-collector diode)
- Metal to metal cap ( $1.4\text{fF}/\mu\text{m}^2$ )
- MOS cap ( $3.1 \pm 15\%\text{fF}/\mu\text{m}^2$ )
- Poly resistors ( $210 \pm 20\%$ ,  $3600 \pm 25\% \square$  )


# Standards Overview

	Bluetooth	802.11b
Data rate	1Mb/s	1-11Mb/s
Power	Lower	<b>Higher</b>
Modulation	FH-GFSK	DSSS-CCK
Freq band	2.4 – 2.48GHz	2.4 – 2.48GHz



 
# Dual-Mode Receiver Architecture

- 3 possible alternatives for Bluetooth and Wi-Fi dual mode architectures:




Low-IF and DCR

 Best fit for each standard ☺  
Sharing ↓ ☹



Low-IF and Low-IF

Power ↑ ☹ ☹  
Sharing ↓ ☹

 


DCR and DCR

Area and power ↓ ☺  
Sharing ↑ ☺  
DC offset & 1/f noise ↑ ☹
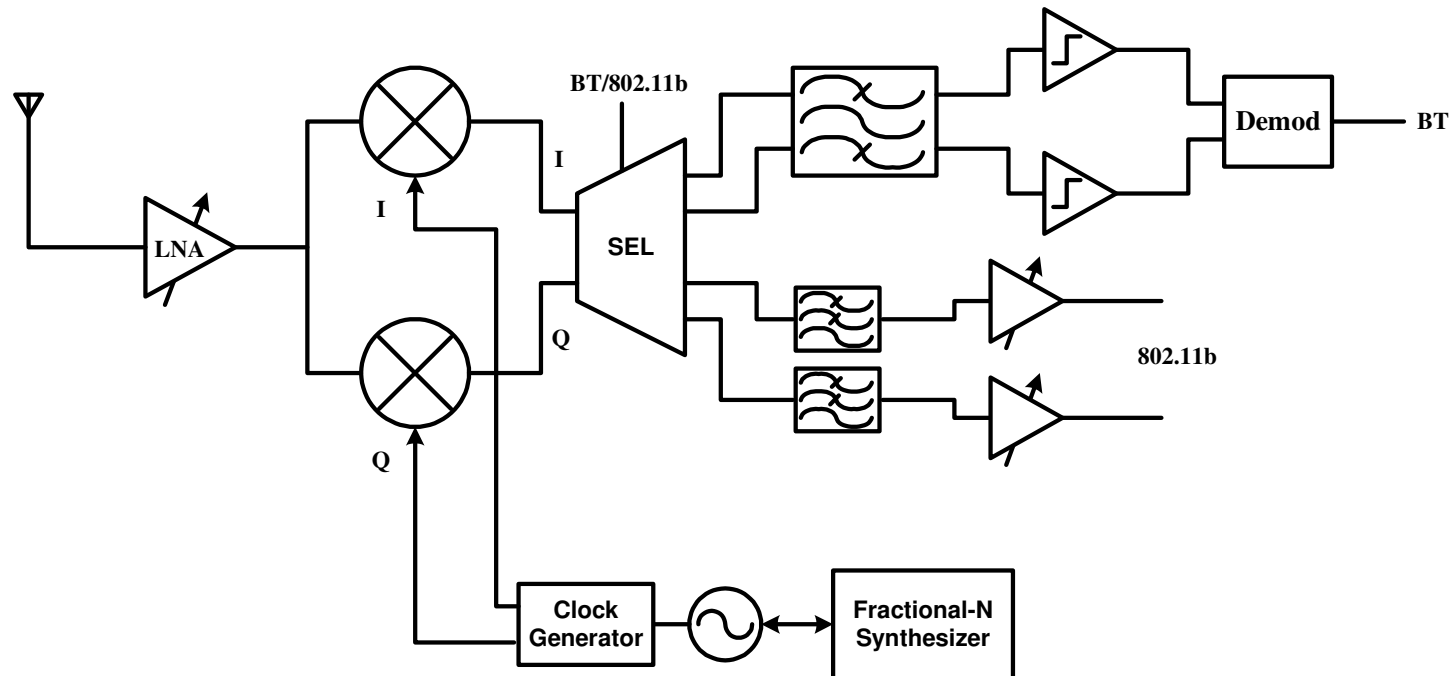
# Previously Reported Dual-Mode Receivers


- DCR for WiFi, low-IF for Bluetooth.
- Shared RF front-end.
- Separate baseband circuits



[1] J. C. H. Darabi, et al "A Dual Mode 802.11b/Bluetooth Radio in 0.35mm CMOS," ISSCC 2003, San Francisco, CA.

 
# Previously Reported Dual-Mode Receivers

- Double downconversion to avoid LO self mixing and injection locking between PA and VCO.
- **DCR for Wi-Fi** and **low-IF for Bluetooth**.
- Shared RF and programmable dual-mode baseband.



[2] D. K. T. Cho, et al "A 2.4Ghz Dual-Mode 0.18mm CMOS Transceiver for Bluetooth and 802.11b," ISSCC 2003, San Francisco, CA.

# Proposed Dual-Mode Architecture

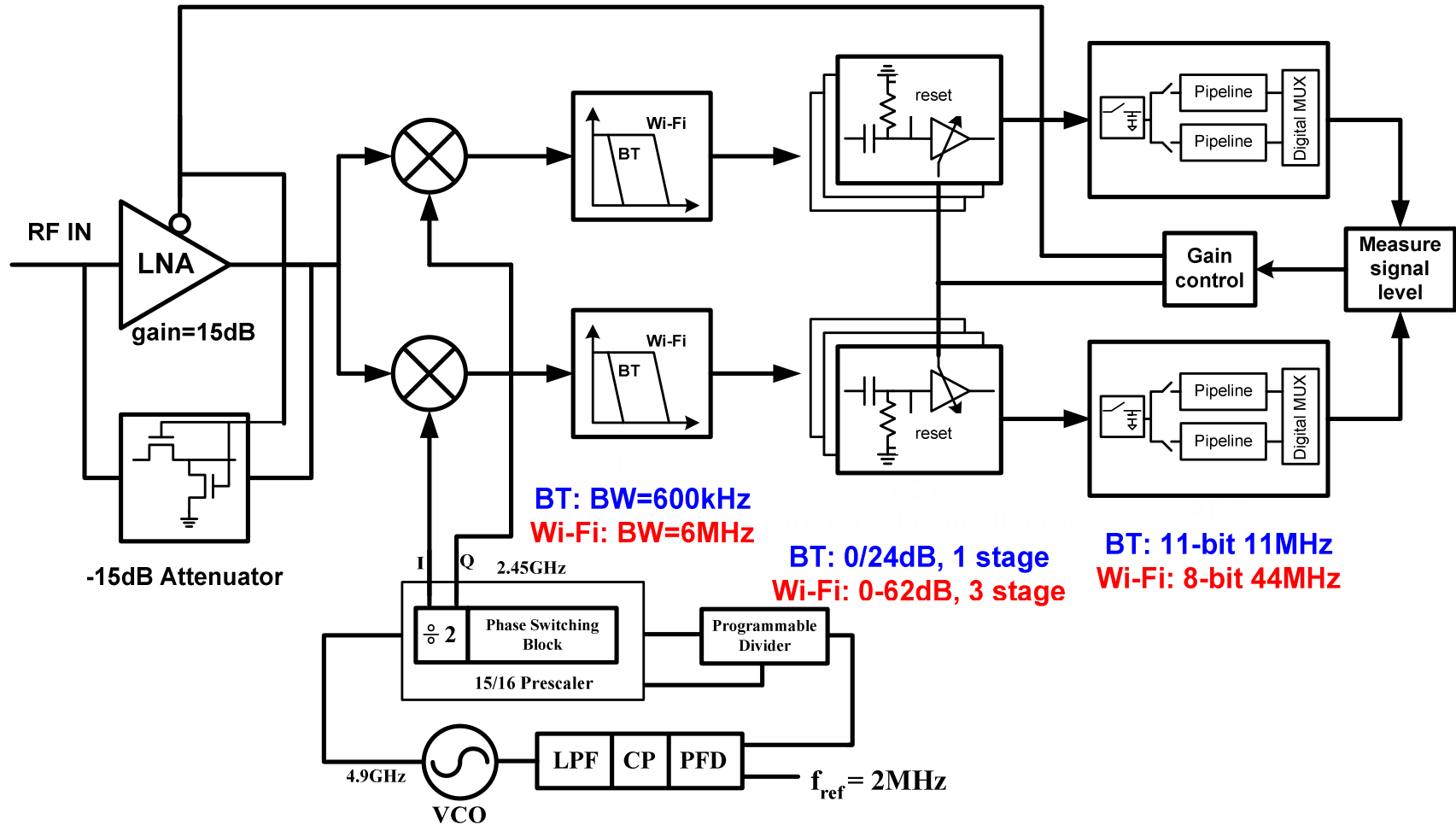


Direct-conversion **BT/WiFi** receiver architecture

# Remarks

- Direct-conversion architecture is used for both standards to save power and avoid the image problem in IF architectures.
- LNA & Mixer are shared between BT and Wi-Fi.
- Gm-C LPF with programmable bandwidth is used to accommodate both standards.
- Parallel Pipeline ADC architecture is used:
  - **BT**: sampling rate = 11MHz, 11bits
  - **Wi-Fi**: sampling rate 44MHz, 8bits
- Due to the short allowed settling time, the VGA has only two gain steps in **BT** mode and the signal level at the ADC input will vary by 24dB.
- In Wi-Fi mode, gain steps of 2dB are employed.

 
# Impact of DC offset and DC offset correction on the BER performance (Wi-Fi mode)




**A:** 0 offset. **B:** 5% offset, **C:** 10% offset, **D:** 15% offset **E:** offset cancelled with 4 HP poles at 5KHz, **F:** offset cancelled with 4 HP poles at 10KHz.
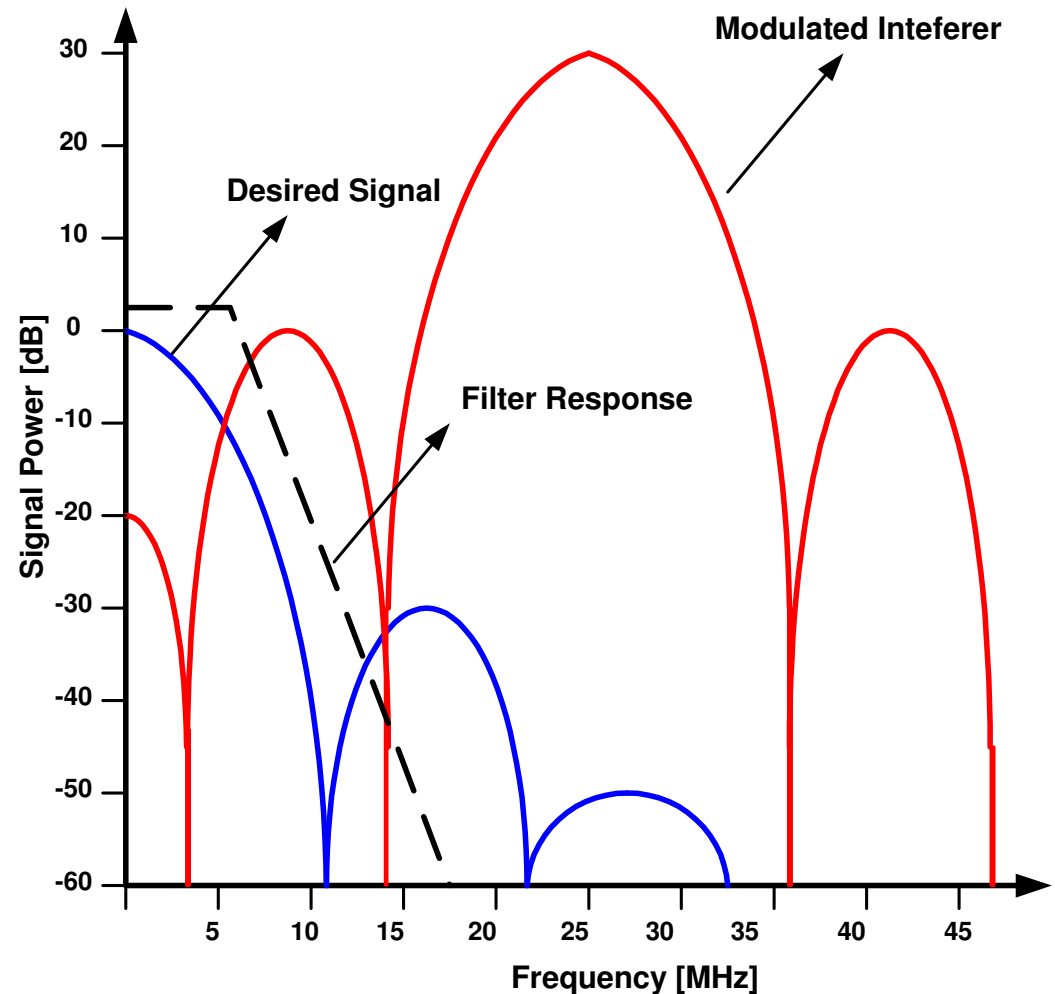
# Wi-Fi Interferer Rejection Requirements

- In the presence of a modulated interferer at 25MHz with a power 35dB above the signal of interest, the receiver should show  $1E-5$  BER for an SNR 6dB above the minimum sensitivity.
- The channel selection filter should reject an **strong interferer** while not affecting the **spectrum of interest**.



 
# Impact of the channel selection filter characteristics on the BER performance (Wi-Fi mode)



- 5<sup>th</sup> order Butterworth filter with  $f_c=5.5\text{MHz}$  with (B) and without an interferer (A).
- 4<sup>th</sup> Chebyshev filter with  $f_c=6\text{MHz}$  with (D) and without an interferer (C).



 
# Impact of the mismatch between I and Q channels on the BER performance (Wi-Fi mode)




- A: Receiver performance including channel selection filter and DC offset correction.
- B: Performance with a  $10^\circ$  error in the generation of I and Q signals.
- C: Performance with 1.5dB gain mismatch between I and Q channels in addition to the phase error.

# Adjacent Channel Test

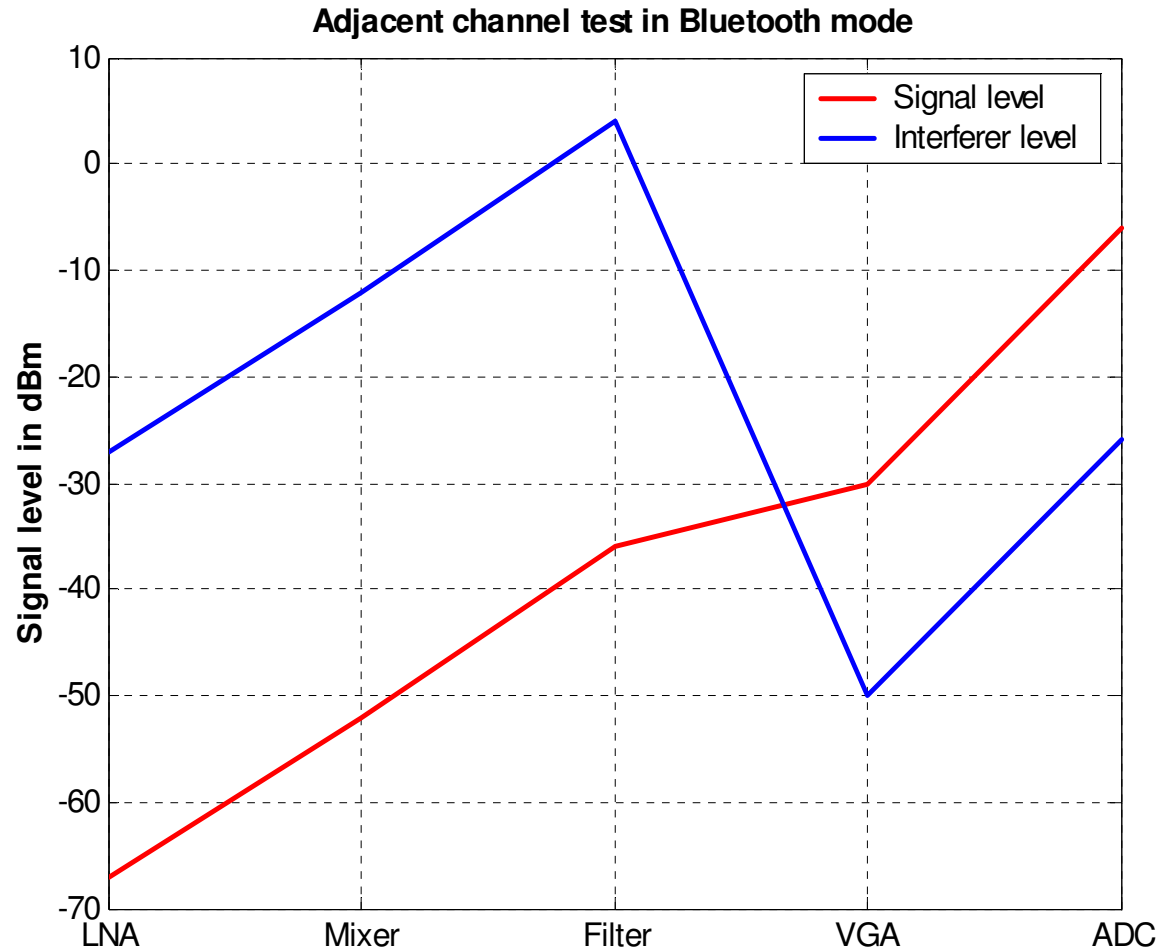


# NF, IIP3, and IIP2 contributions


Noise contributions of different blocks

 



IIP3 contributions of different blocks

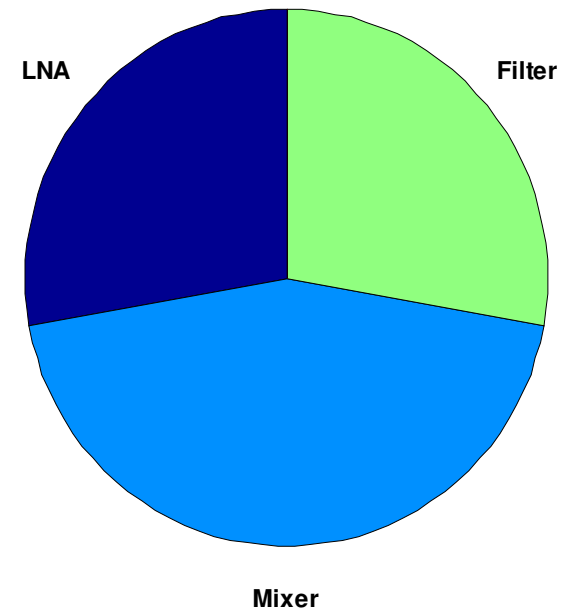

IIP2 contributions of different blocks

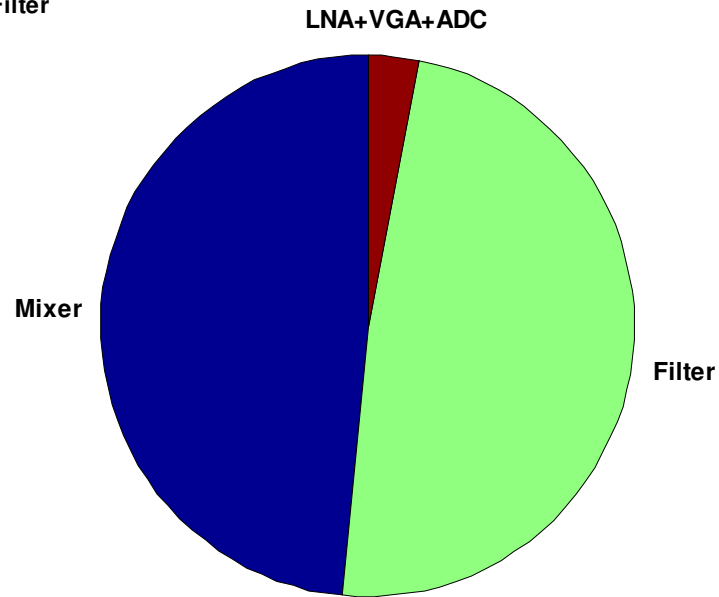
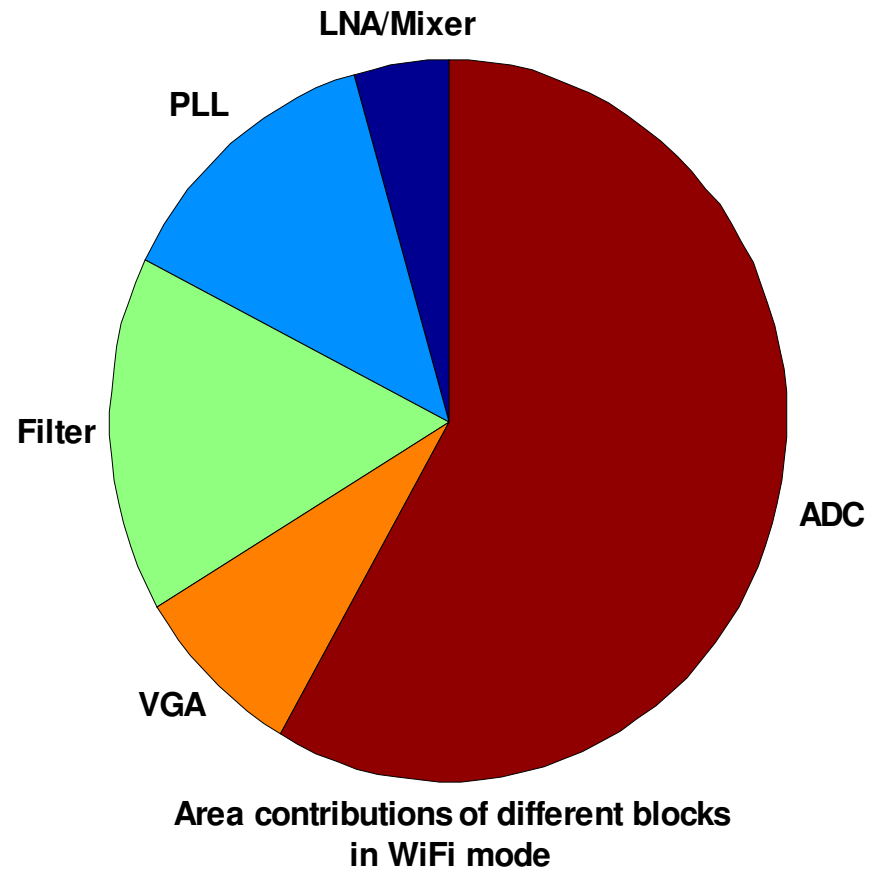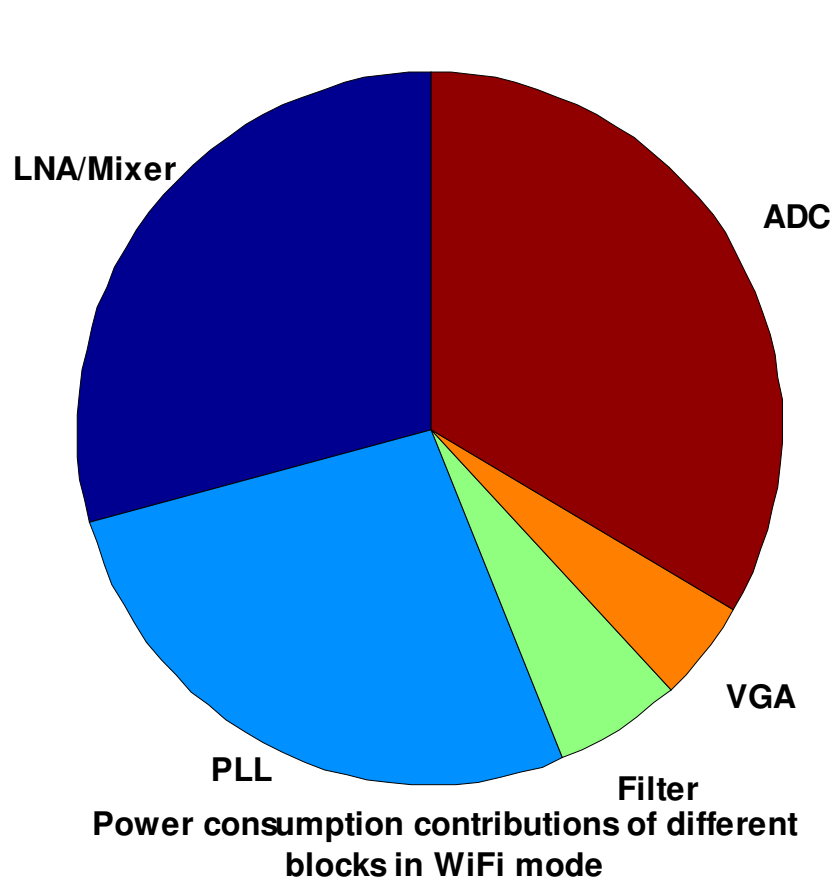
# Power consumption and area contributions




# Chameleon Receiver


- Previous work: Bluetooth Receiver in CMOS 0.35 $\mu$ m
- System Level Design
  - Technology features
  - Main Bluetooth and Wi-Fi specs
  - Previously reported architectures
  - Proposed dual-mode architecture
  - Impact of non-idealities on the BER performance
- **Building Blocks**
  - LNA
  - Mixer
  - VCO and PLL
  - VGA
  - ADC
- Experimental Results
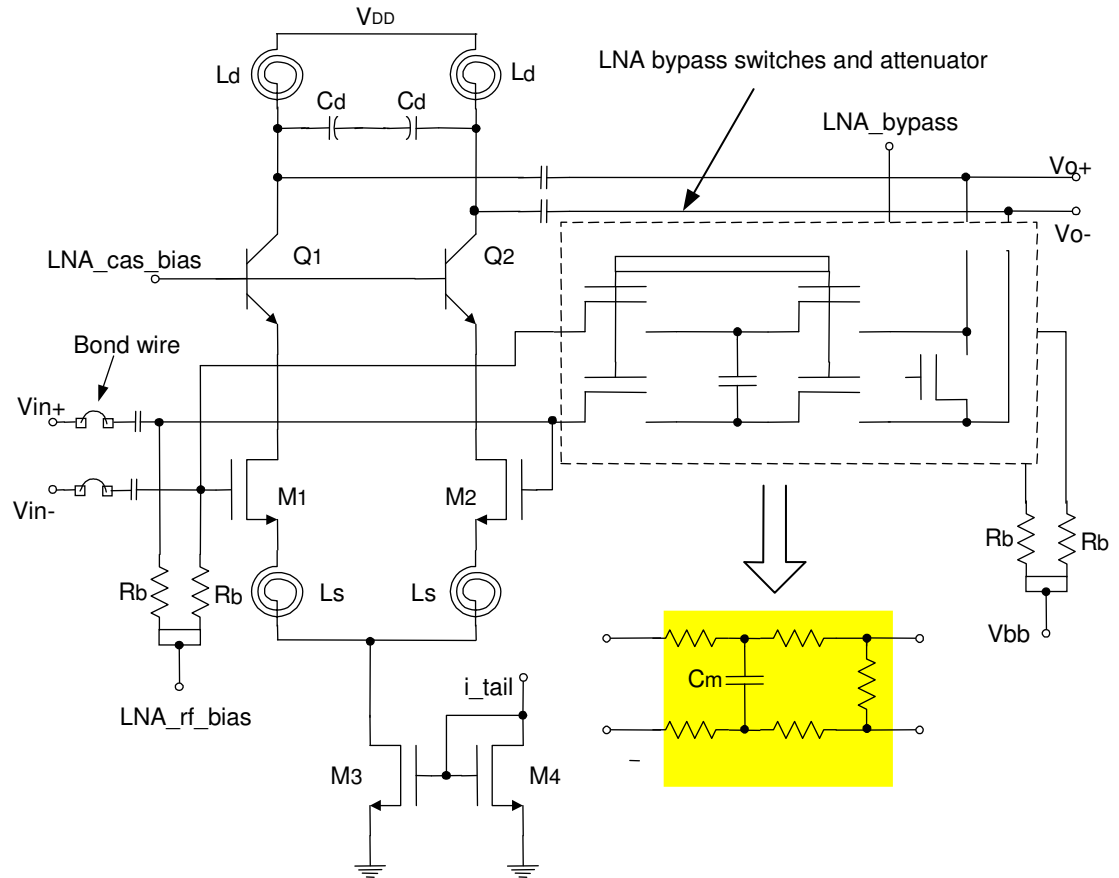
# Low Noise Amplifier

- Gain = 15/-15dB
- NMOS drive is used for better linearity.
- $C_m$  ensures matching in low-gain mode.




# I/Q Downconversion Mixer

 

- I & Q share the same RF drive stage
- NMOS drive for better linearity
- NPN switch to reduce LO drive and 1/f noise

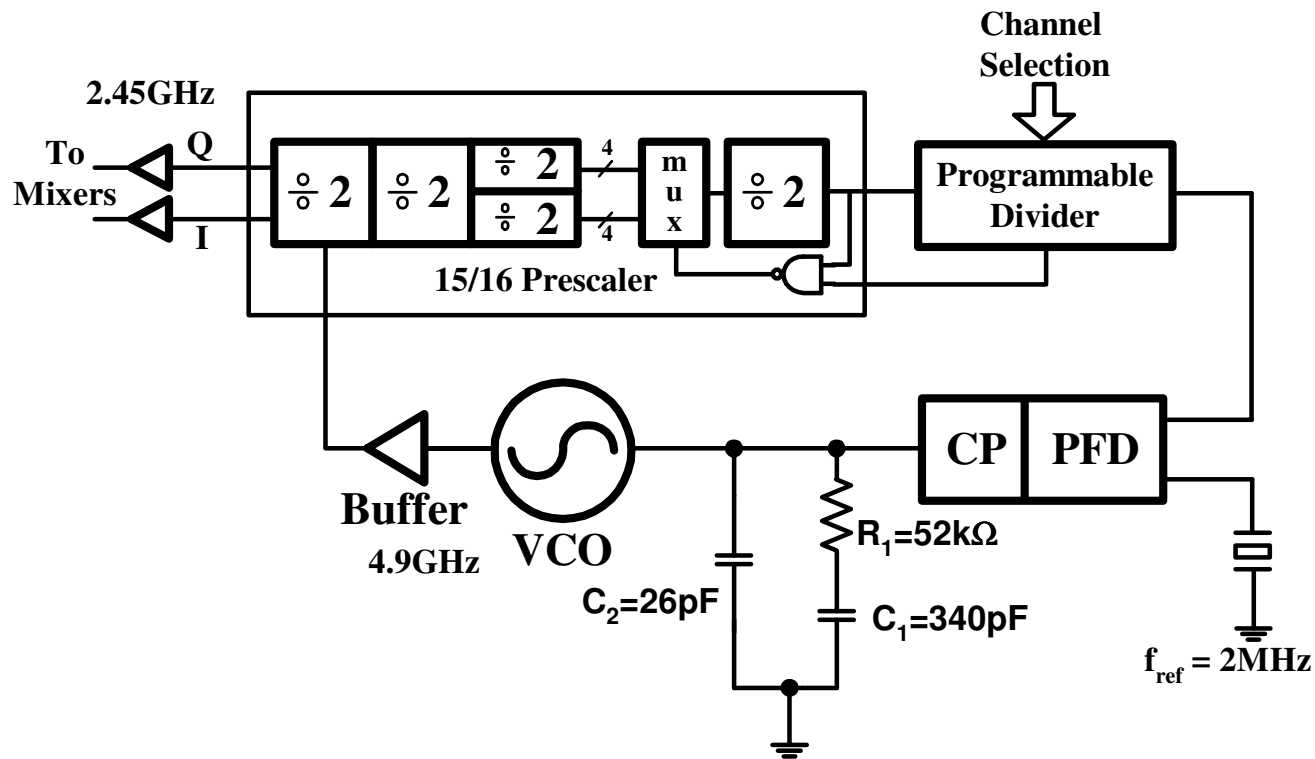
# Frequency Synthesizer

- VCO running at  $2f_0$
- I/Q generation using divide-by-2 flip flop.
- Capacitor multiplier to integrate loop filter cap.







# Phase Switching Prescaler

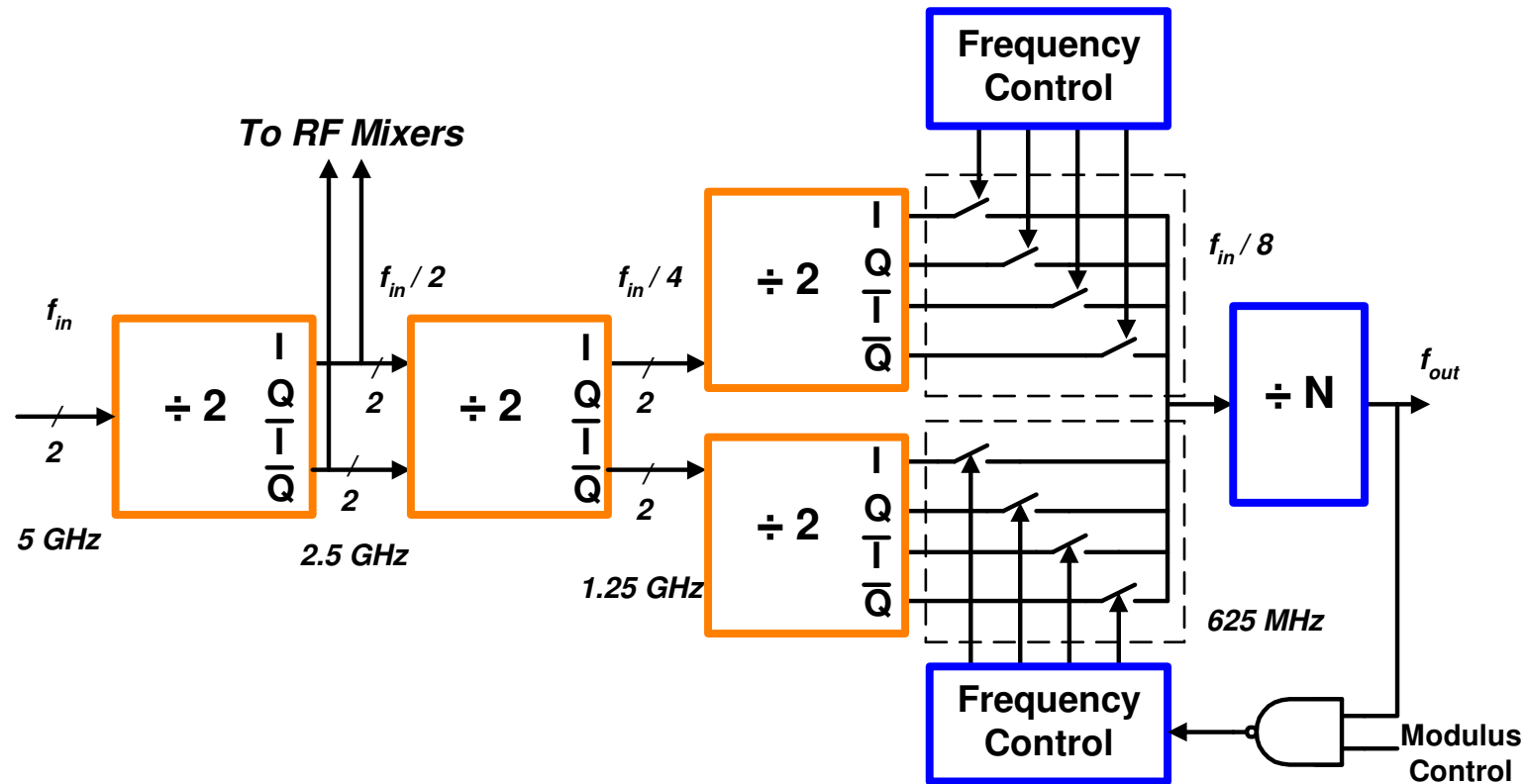

- Phase switching prescaler for reduced power consumption compared with traditional architectures.
- No feedback in flip-flops.

# Charge Pump

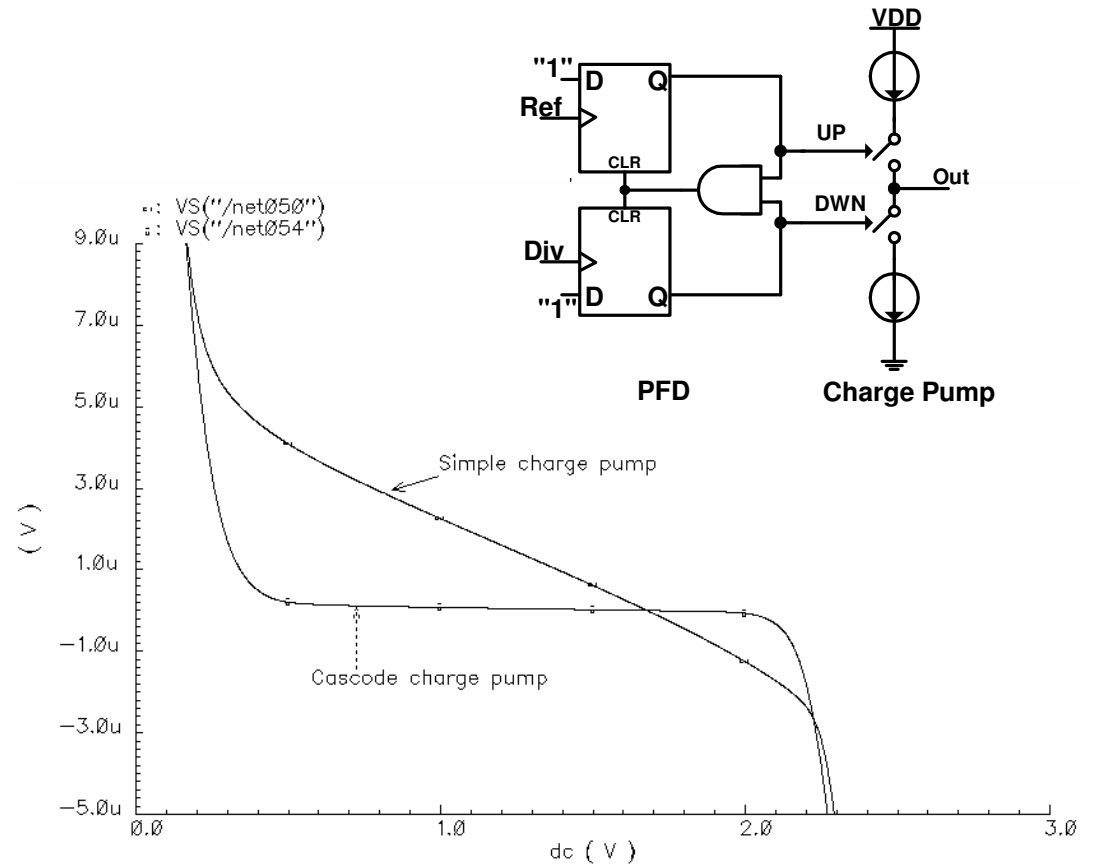
 


Cascode current mirrors minimize the current mismatch in Up and Dwn operation.

# Capacitance Multiplier


$$Z_{in} = \frac{Z_0}{M + 1}$$

$$1/Mg_{m1} \ll R1$$

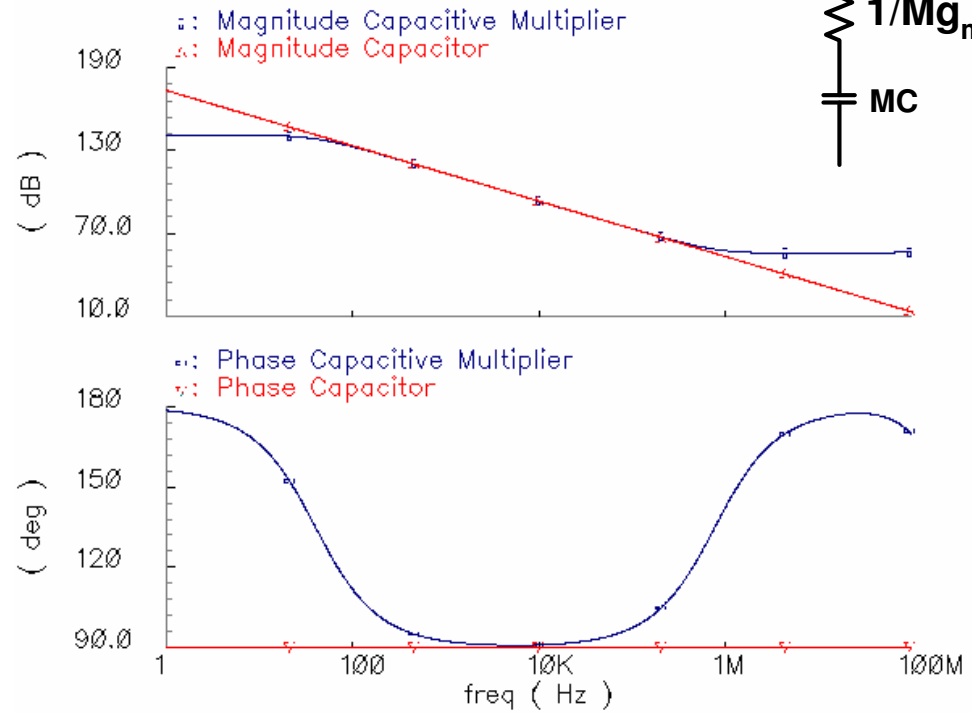 

**Total Current: 150 μA**


# VCO

 


- LC tuned negative- $g_m$  VCO
- Analog metal inductor
- Varactor diode
- DC-decoupling for driver base to improve linearity and noise
- Bypass capacitor improves phase noise 2dB
- $L=1.5\text{nH}$ ,  $Q=13$
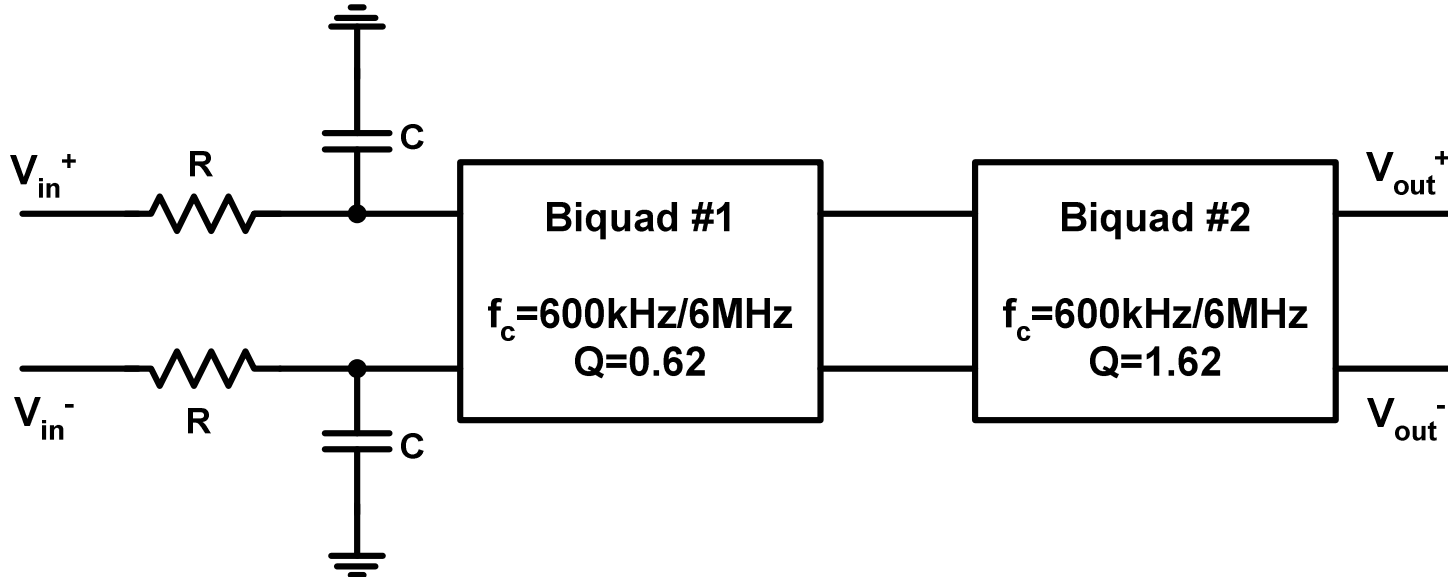
# Channel Selection Filter

- 5<sup>th</sup> order Butterworth OTA-C filter.
- Passive 1<sup>st</sup> pole is used to relax the biquad (OTA) linearity requirements.
- Programmable bandwidth through switching R&C.



# Biquadratic Section

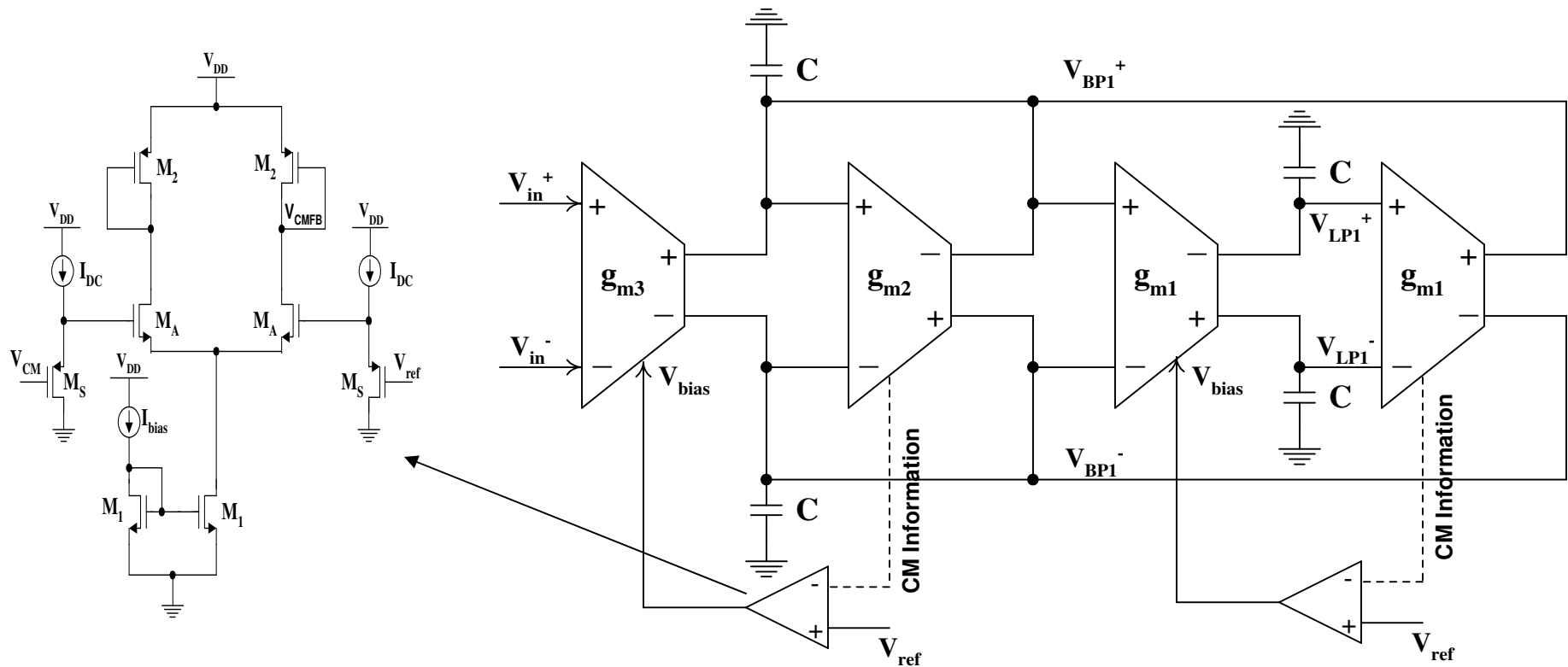


$$\omega_0 = \frac{g_{m1}}{C}$$

$$Q = \frac{g_{m1}}{g_{m2}}$$

$$V_{DC} = 1.6V$$

Direct connection between consecutive OTAs in the filter is exploited in the implementation of the CMFB circuit.


# Dual-mode OTA

 

- Source degeneration
  - Current scaling
- $$I_{\text{bias}} \times R = \text{constant}$$

- The standard is chosen by switching R (coarse tuning)
- Fine frequency tuning using bank of capacitors C

# Variable Gain Amplifier

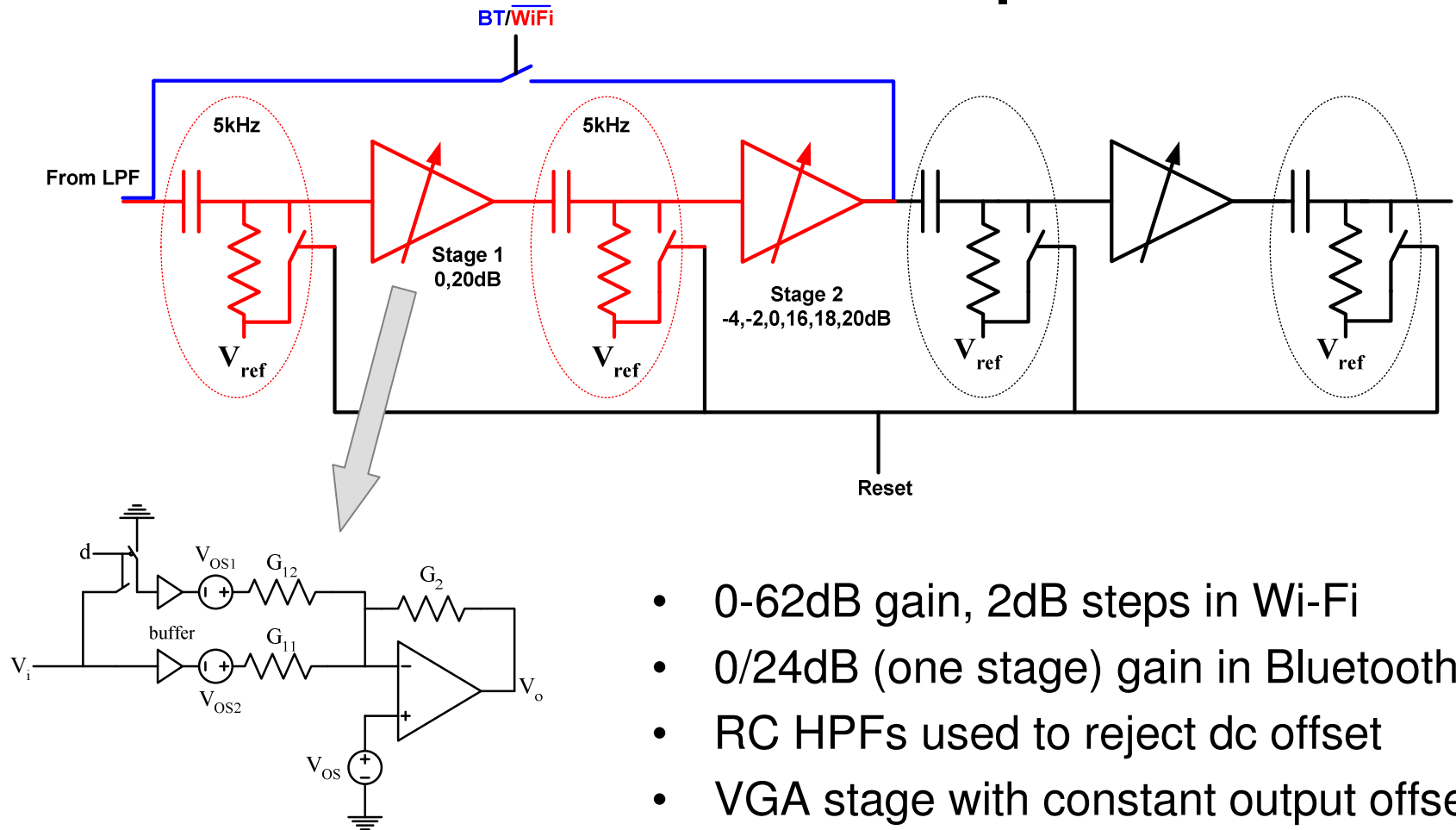

- 0-62dB gain, 2dB steps in Wi-Fi
- 0/24dB (one stage) gain in Bluetooth
- RC HPFs used to reject dc offset
- VGA stage with constant output offset



# Constant output offset VGA


- The gain is controlled by  $d$ :

$$Gain = \frac{G_{11} + dG_{12}}{G_2}$$

- The output offset is independent of  $d$ .


$$output\ offset = \frac{G_{11} + G_{12}}{G_2} V_{os}$$

 - This assumes that the offset in  $V_i$  is completely removed by the RC HPF.
- Problem:**  $G_{11}$  and  $G_{12}$  will load the HPF  $\Rightarrow$  we have to use a buffer at each input resistor



 
# Constant output offset VGA, Cont'd

- A buffer is used to drive each input resistor.
- The feedback factor is independent of the gain. This makes the OpAmp design easier.
- Bandwidth and phase margin are independent of the gain.
- Note that the capacitor  $C$  does not load the previous stage since it is in series.
- However, the parasitic capacitance of the top and bottom plates to ground will load the previous stage!



# Time-Interleaved Pipeline ADC

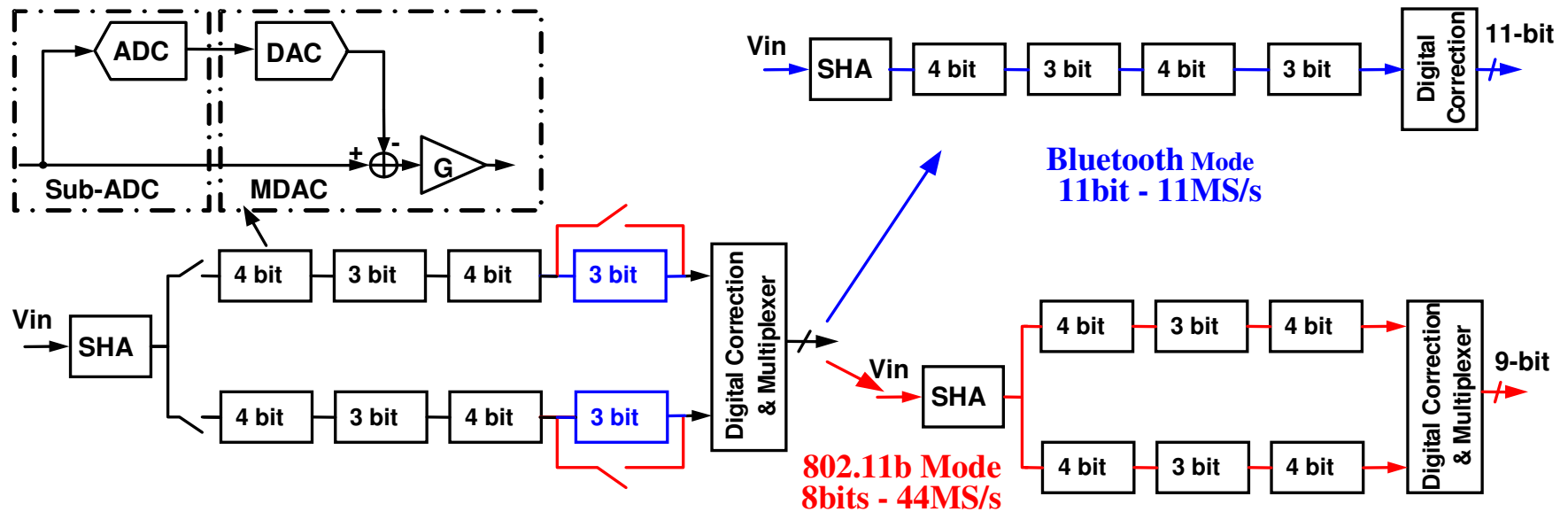


- Programmable resolution and sampling rate.
- On line digital calibration.


# Chameleon Receiver

- Previous work: Bluetooth Receiver in CMOS 0.35 $\mu$ m
- System Level Design
  - Technology features
  - Main Bluetooth and Wi-Fi specs
  - Previously reported architectures
  - Proposed dual-mode architecture
  - Impact of non-idealities on the BER performance
- Building Blocks
  - LNA
  - Mixer
  - VCO and PLL
  - VGA
  - ADC
- **Experimental Results**

# Receiver Die Photo

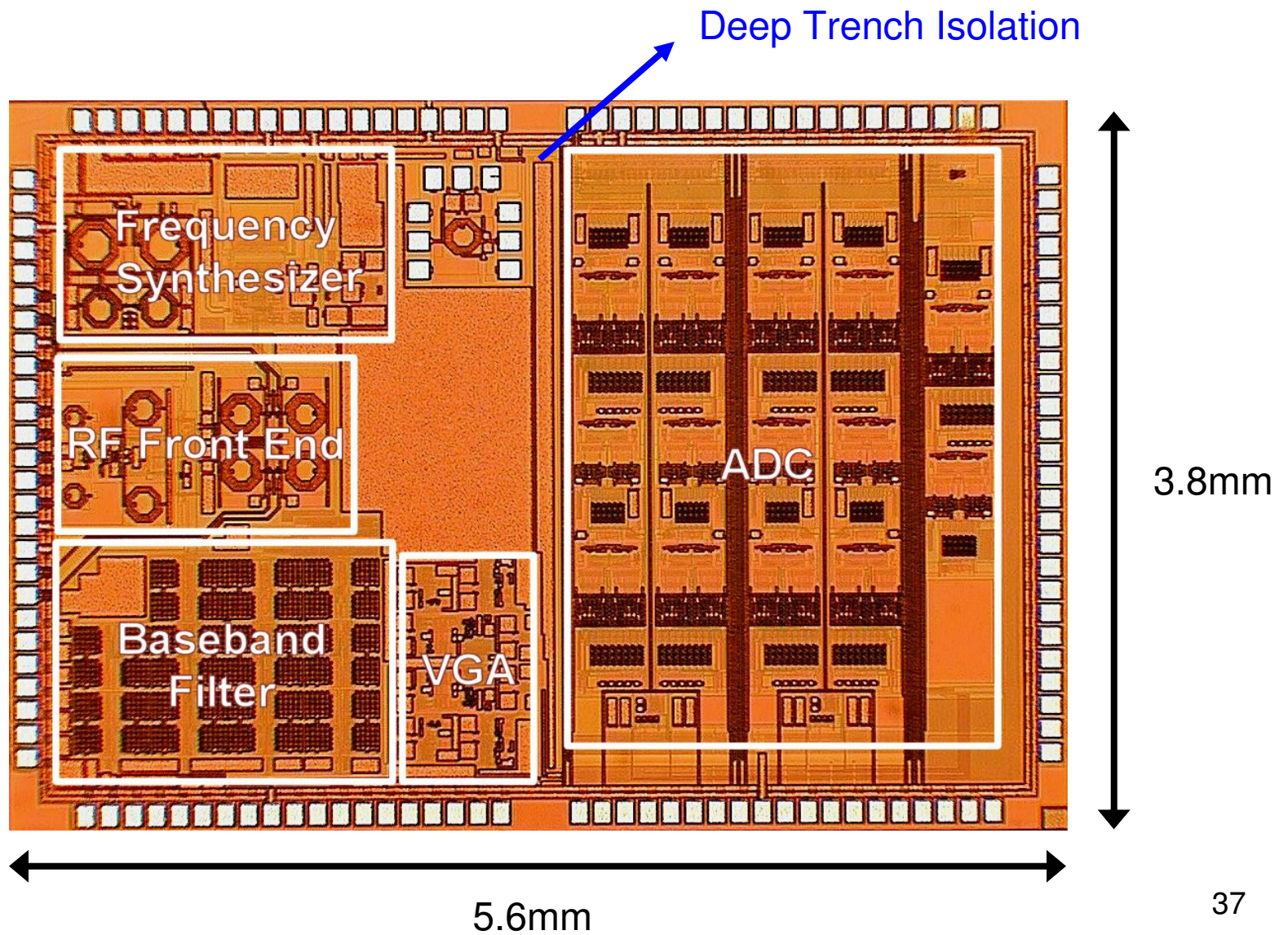


# Testing Board

 

# Receiver Sensitivity

Bluetooth = -91dBm


Wi-Fi (11Mb/s) = -86.5dBm

 


# Receiver Linearity

Both **BT** / **Wi-Fi** modes

IIP2 = 10dBm

 


IIP3 = -13dBm

 




# LO Phase Noise

 


**-124 dBc/Hz @ 3MHz**

# LPF Programmability

 


# SNR Measurement for ADC

BT

 

Wi-Fi

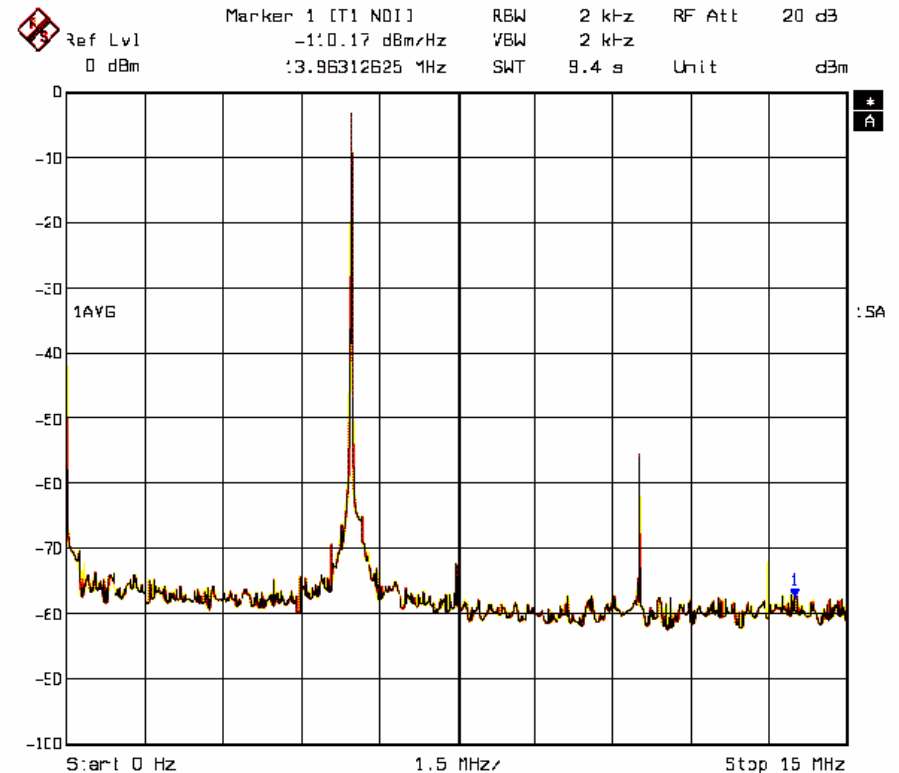

64.2 dB at 11MSample/s for the 550 kHz BT signal

59.7 dB at 44MSample/s for the 5.5 MHz 802.11b signal

# Comparison Table

	[1]		[2]		This design	
	BT	WiFi	BT	WiFi	BT	Wi-Fi
Receiver Architecture	Low-IF	DCR	Low-IF	DCR	DCR	DCR
Offset cancellation	Programmable loop		Injection at AGC input		AC coupling	
Channel select filter	separate		programmable		Programmable	
Baseband amplifier	separate		shared		Shared	
ADC	Not included		Not included		Included	
Filter bandwidth	1MHz (BPF)	7.5MHz (LPF)	1MHz (BPF)	7.5MHz (LPF)	600kHz (LPF)	6MHz (LPF)
Sensitivity	-82dbm	-88dBm	-80dBm	-92dBm (0dB SNR)	-91dBm	-86dBm
Technology	0.35 $\mu\text{m}$ CMOS		0.18 $\mu\text{m}$ CMOS		0.25 $\mu\text{m}$ BiCMOS	
Rx active current	46mA	65mA	60mA		27.9mA (w/o ADC)	30mA (w/o ADC)
ADC active current	-	-	-	-	13.4mA	15.6mA
IIP3	-7dBm	-8dBm	-12dBm		-13dBm	
IIP2	N/A	N/A	20dBm		10dBm	
Rx area (w/ pads)	N/A		16mm <sup>2</sup> (transceiver)		9mm <sup>2</sup> (w/o ADC)	
ADC area (w/ pads)	-	-	-	-	10mm <sup>2</sup>	
Supply voltage	2.7V		1.8V		2.5V	

# Summary

- Direct conversion architecture for BT / Wi-Fi allows maximum level of block sharing
- Lower consumption than previous dual-mode implementations (27.9 mA / 30mA)
- Shared RF front-end and programmable baseband components
- Programmable channel selection filter with constant linearity
- AC coupled VGA with constant output offset
- On-chip time interleaved pipeline ADC

