

IEEE Dallas CAS Chapter

Frequency Synthesizers in Nanometer CMOS

R. Bogdan Staszewski



TEXAS INSTRUMENTS

Outline


- RF frequency synthesis fundamentals
 - Motivation for digitally-intensive PLL
- New paradigm in nanometer-scale CMOS
- All-digital phase-locked loop (ADPLL)
- ADPLL wideband frequency modulation
- Conclusion

Frequency Synthesis in Radio Transceivers

Local Oscillator in a Radio Transceiver

- Local oscillator (LO) is needed in every radio TX and RX
 - Irrespective of the architecture
- Needed to translate RF frequency down to IF or baseband (in RX) and vice versa (in TX)
- LO has to be tunable across the RF wanted frequency band and the frequency resolution has to be at least equal to the channel spacing
- **Frequency synthesizer** is used as LO
- RF frequency synthesizers remain one of the most challenging blocks in mobile wireless communication systems



Local Oscillator

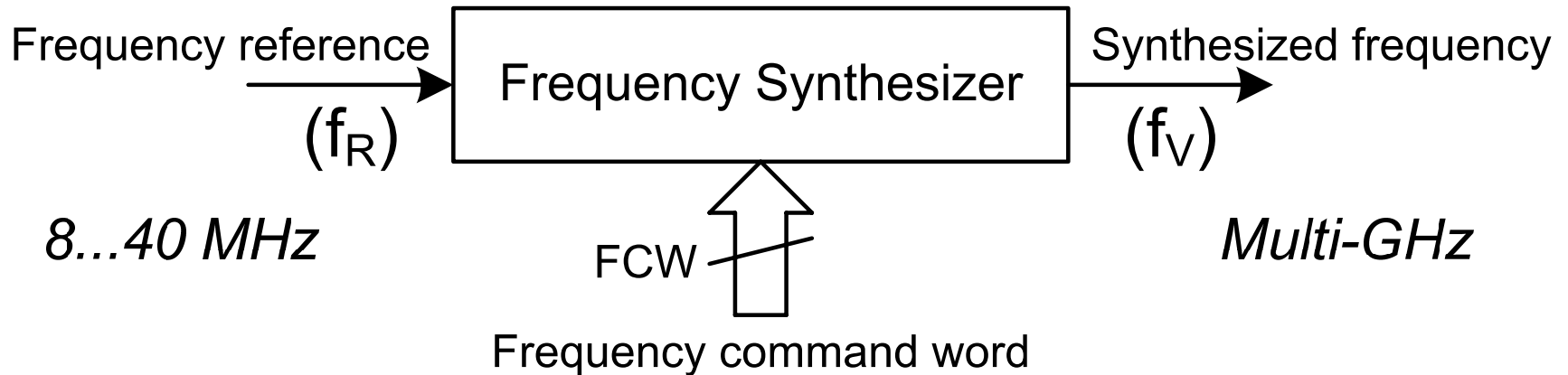

- Frequency reference (FREF) source usually built as tunable crystal oscillator (XO)
 - Voltage-controlled temperature-compensated XO (VCTCXO)
 - External module; expensive (~\$1)
 - Digitally-controlled XO (DCXO)
 - Requires external XTAL (~\$0.2)
 - MEMS resonators
 - Emerging technology
- Three major frequency synthesis techniques:
 - Direct-analog (error correction process is avoided)
 - Direct-digital
 - Indirect or phase-locked loop

Phase Noise in Oscillators

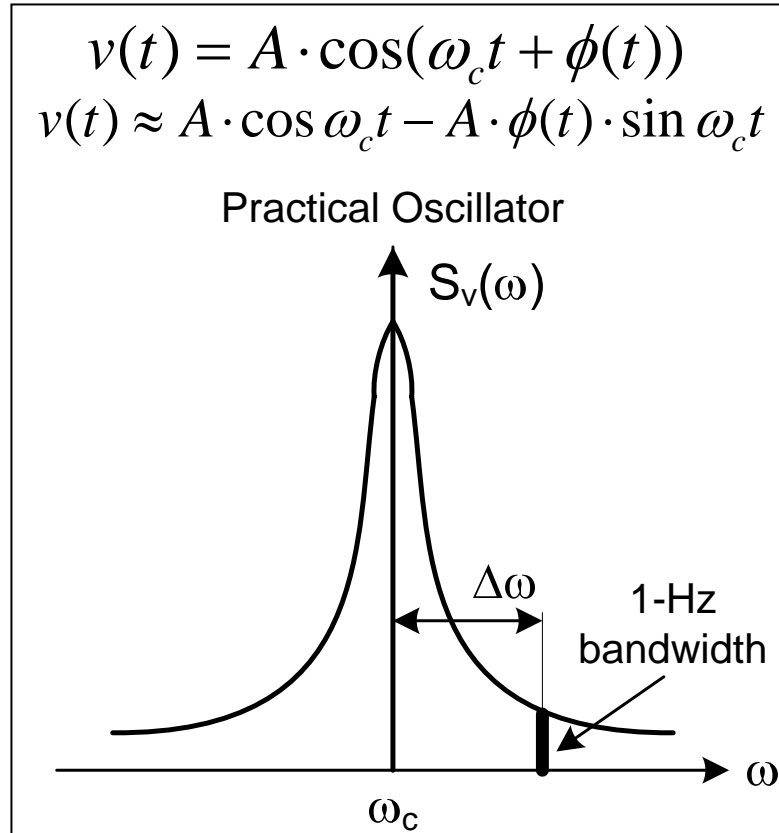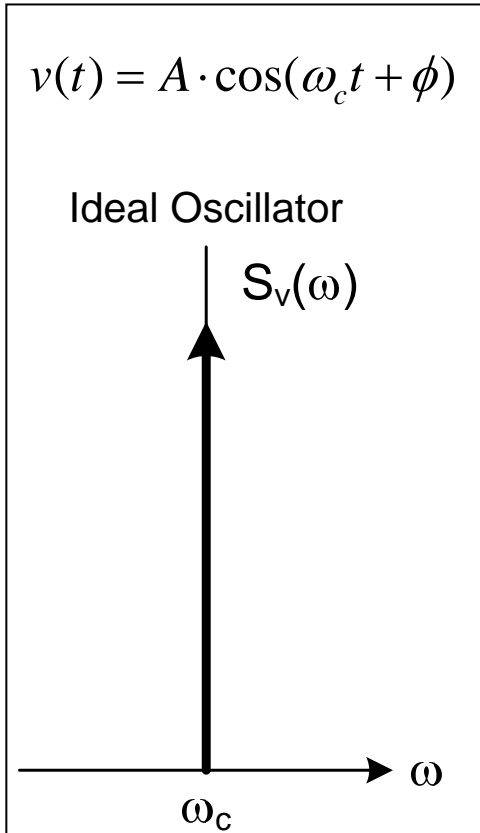- Ideal oscillator: power concentrated at ω_c
 - Dirac pulse in frequency domain
- Real oscillator: phase is time-varying
 - Spectrum will exhibit “skirt” around the carrier frequency




Single side
band noise

$$L(\Delta\omega) = \frac{S_\phi(\Delta\omega)}{2}$$

Phase Noise Profile

- $1/\omega^0$: thermal noise added to the clock outside of the oscillator proper; does not affect the oscillation time base
- $1/\omega^2$: upconverted thermal (AWGN) noise; caused by uncorrelated timing fluctuations in the period of oscillation; modeled as random walk
- $1/\omega^3$: upconverted flicker ($1/f$) noise; significant in thin-oxide MOS transistors

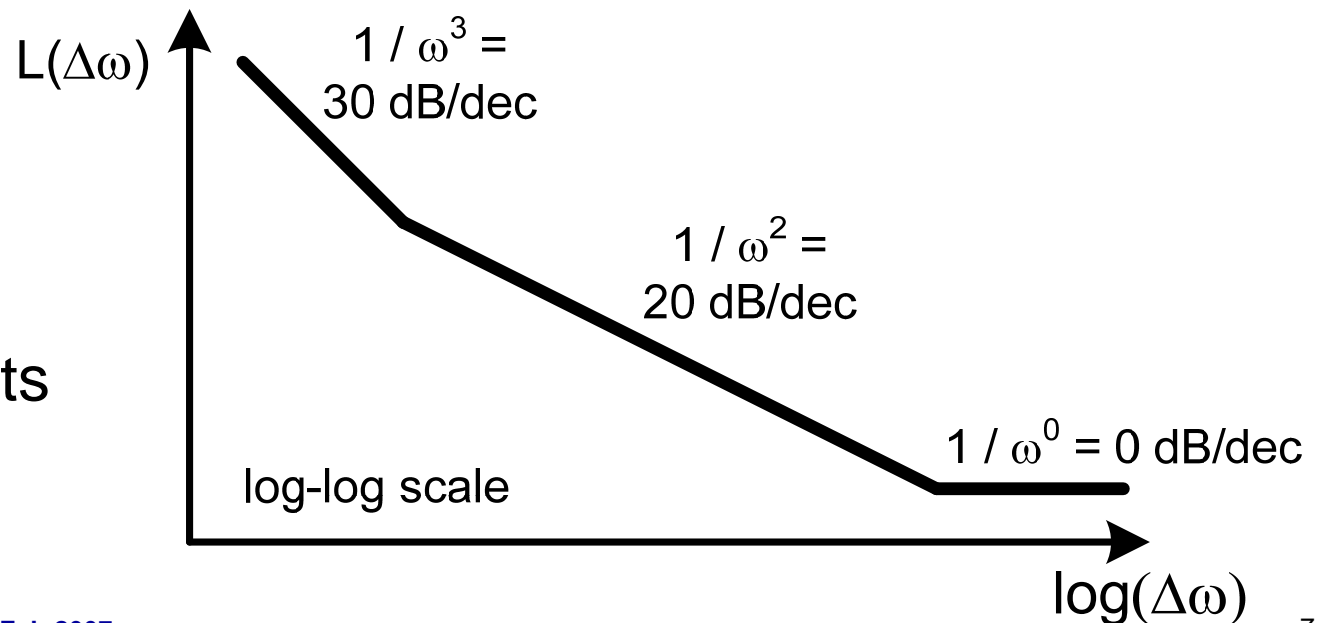- RF oscillator phase noise spectrum exhibits three regions




Oscillator Spurious Tones

- Periodic (systematic) content in the phase noise will exhibit itself as undesired spurious tone sidelobes upconverted around the carrier




$$\phi(t) = \phi_p \cdot \sin(\omega_m t)$$

$$v(t) = A \cdot \cos(\omega_c t + \phi(t))$$


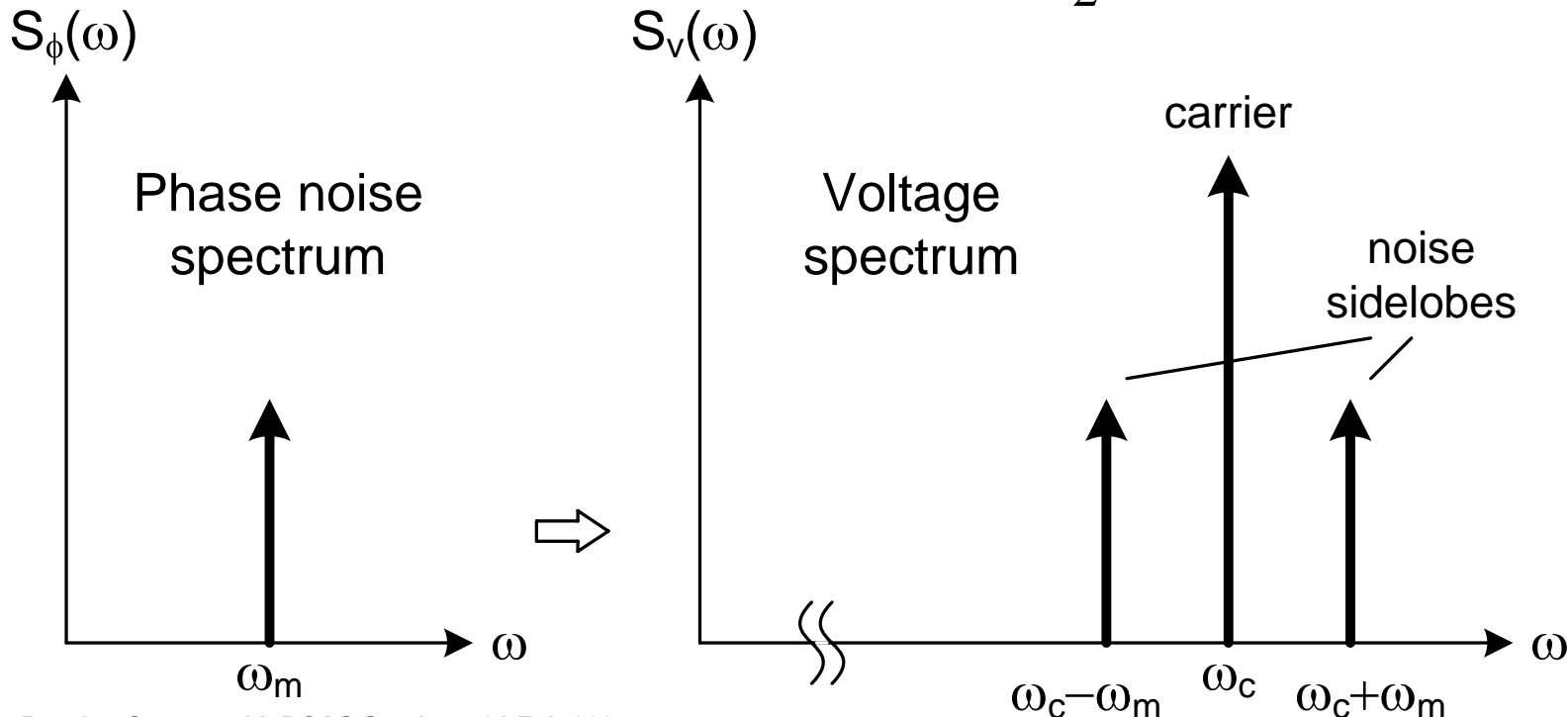
$$v(t) \approx A \cdot \cos \omega_c t + \frac{A \cdot \phi_p}{2} \cdot [\cos(\omega_c + \omega_m)t - \cos(\omega_c - \omega_m)t]$$



LO in Transmitter

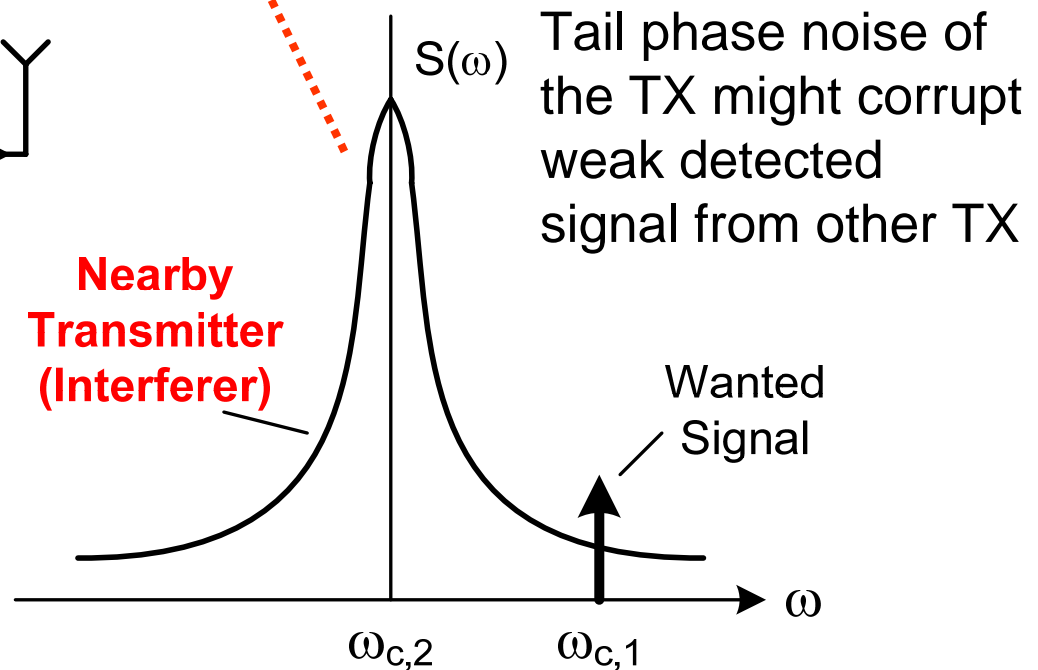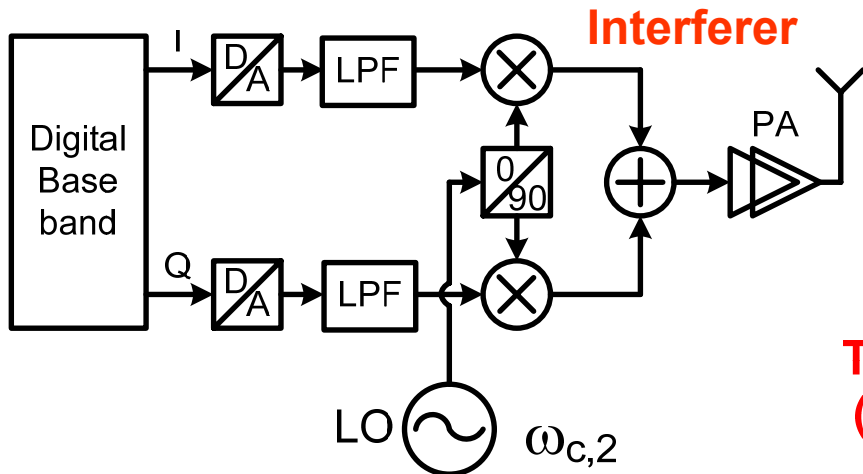 


LO in Receiver

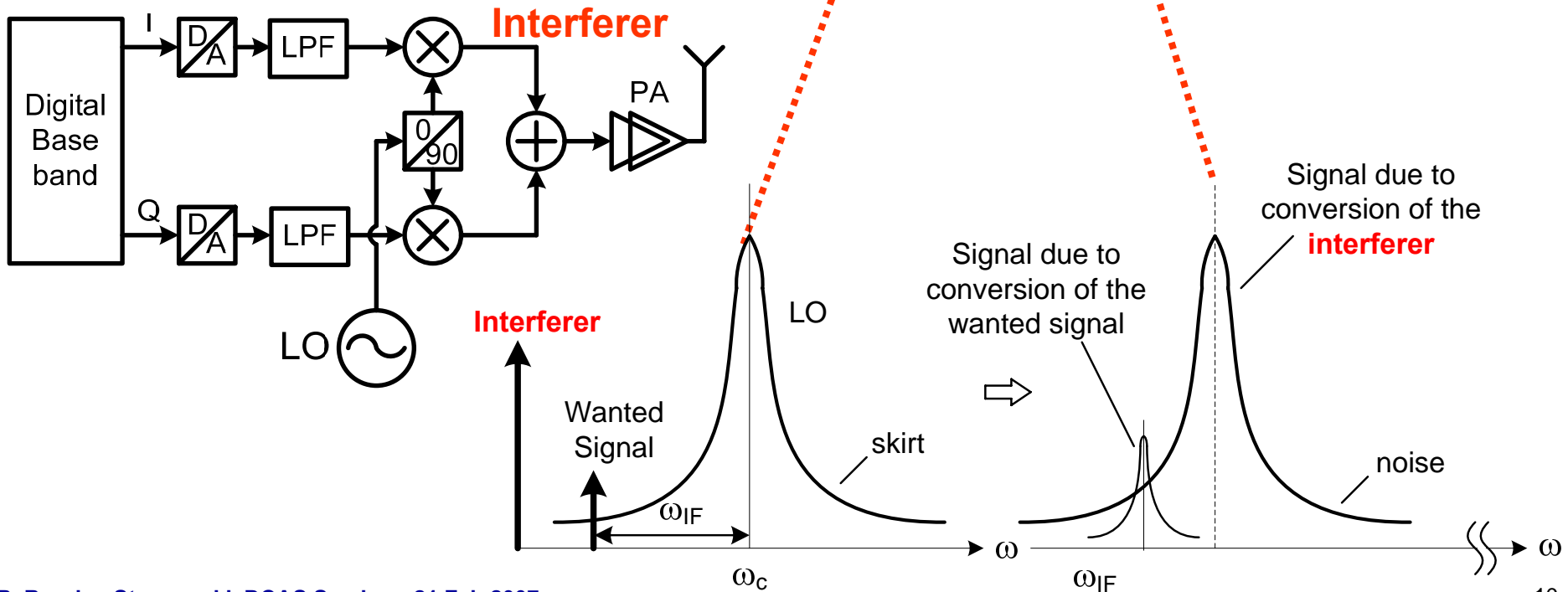 


Synchronization of a Mobile Station

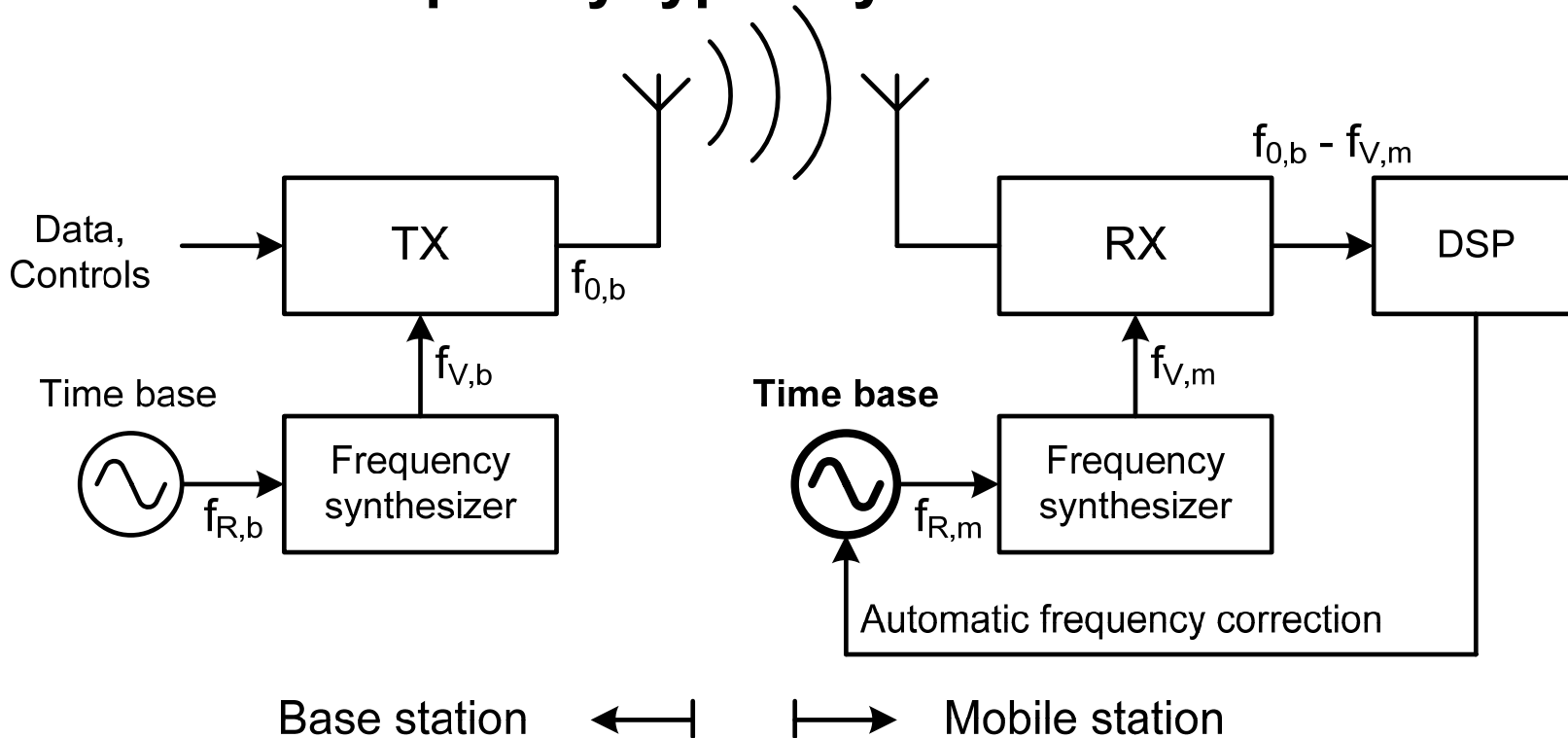- LO needs to be accurate and stable to 0.1 ppm
 - i.e., 200 Hz at 2 GHz
- Crystal's inaccuracy more than 10 ppm
- Mobile station uses base station for synchronization
 - Automatic frequency control (AFC)
- => **Reference frequency typically needs to be tunable**



Frequency Synthesizer Ranking

- Phase noise performance
- Discrete spurious noise performance
- Switching speed – for channel hopping, sleep modes
- Frequency and tuning range – operational band plus PVT margin
- Power consumption – battery operated mobile devices
- Size – mass production deployment
- Integrateability – integrate with digital logic and memory
- Cost – no extra cost added to the process; minimal count of external components
- Testability – low testing costs; built-in self test (BIST)
- Portability – ability to transfer the design from one application to another and from one process to another


 


Frequency Synthesis Types

Direct Digital Synthesis (DDS)

- Developed by Tierney [1] in 1970s

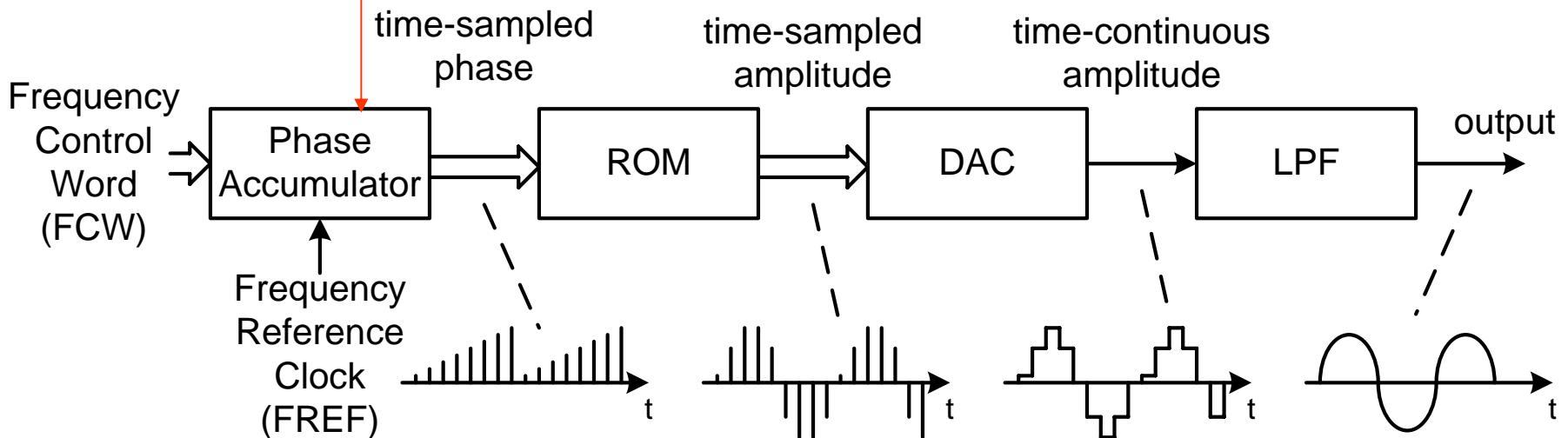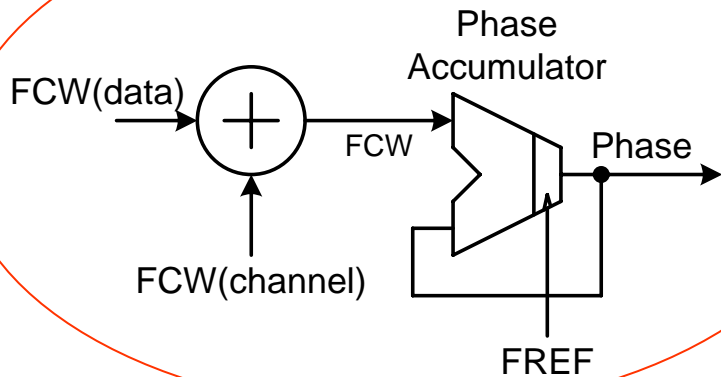
- Digitally constructs the desired signal
 - Amplitude, frequency and phase are known and controlled at all times
- Not entirely digital
 - Requires DAC and LPF
- Not feasible at GHz frequencies
 - Clock has to be at least 3x of the output frequency



Indirect Synthesis: Charge-pump PLL

- Phase difference estimated in PFD by measuring time difference between f_{ref} and f_{div} closest edges, hence fundamentally slow acquisition
- Frequency acquisition time is proportional to the initial $\Delta f / f_{BW}$
- Disadvantage: slow acquisition and difficult to integrate
 - Difficult to integrate: VCO and large charge-pump caps
- Conflict in frequency switching time and suppression of spurs
- Only suitable for narrowband transmit modulation

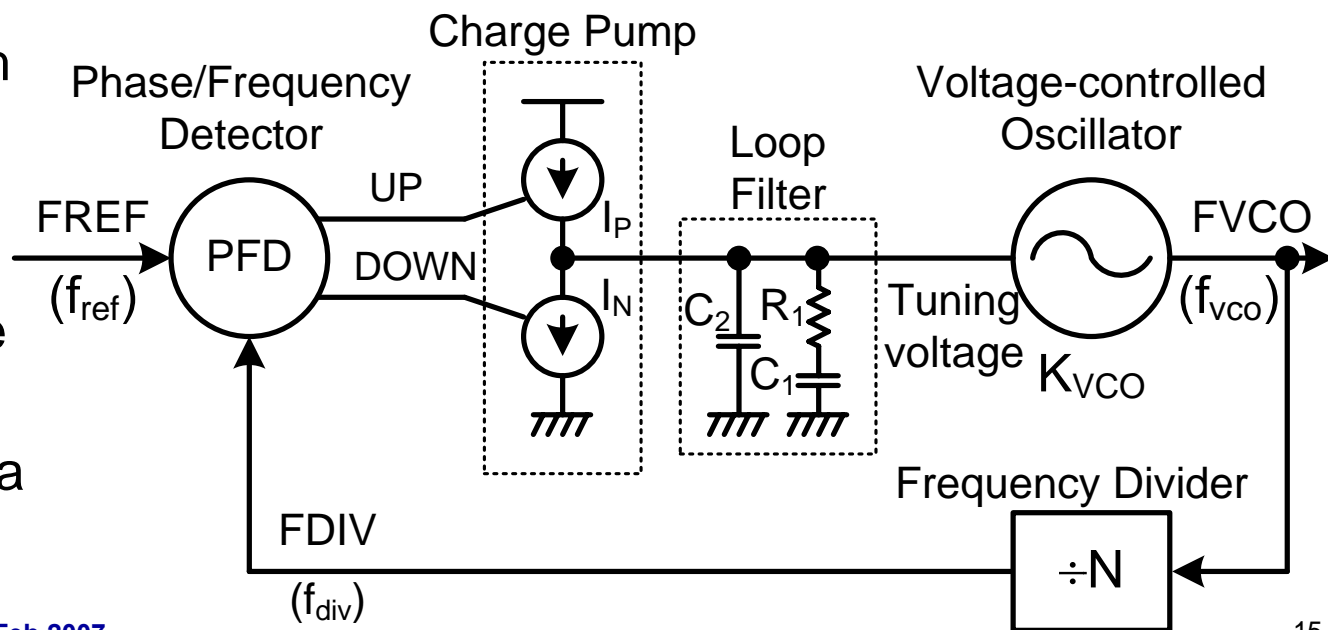- PFD produces current pulse I_p with prop. duty cycle
- Loop filter converts the current into a VCO tuning voltage
- C_2 is an integrating capacitor and puts a pole at dc





Fractional-N Synthesizer

- Frequency tones (spurs) due to repetitive phase shift
- Easy to predict in a digital manner -- accumulator

Kingsford-Smith
US patent 3,928,813
1974 (filing date)

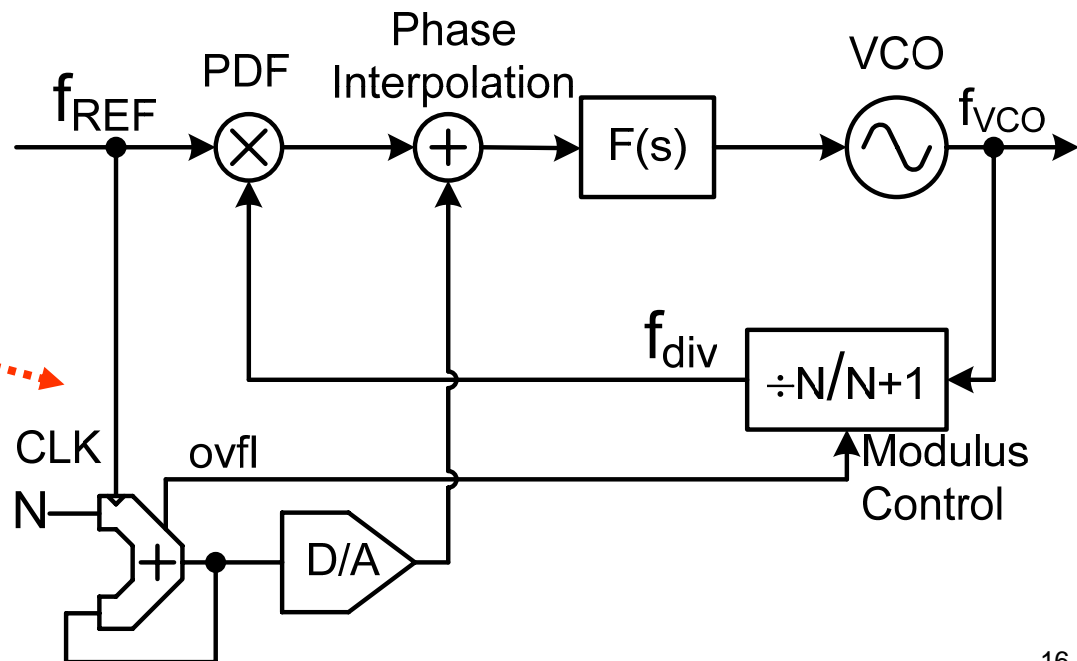 - Spur reduction techniques:
- Analog compensation schemes – phase interpolation
 - Sigma-Delta modulator







Sigma-Delta Fractional-N Divider

Riley
US patent 4,965,531
1989 (filing date)


Wells
US patent 4,609,881
1984 (filing date)

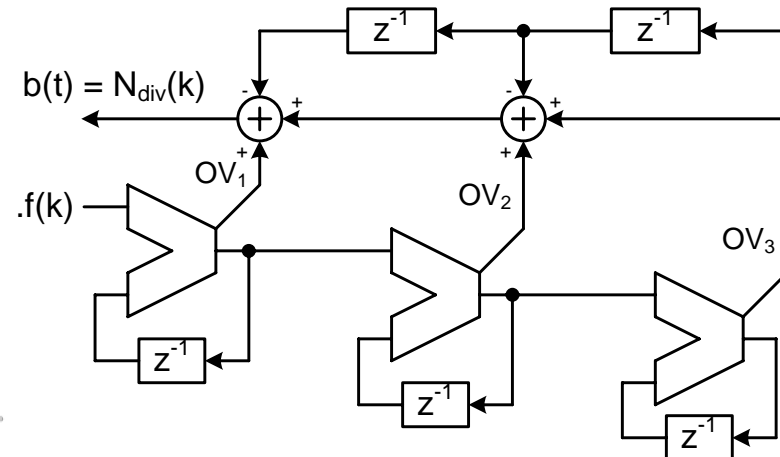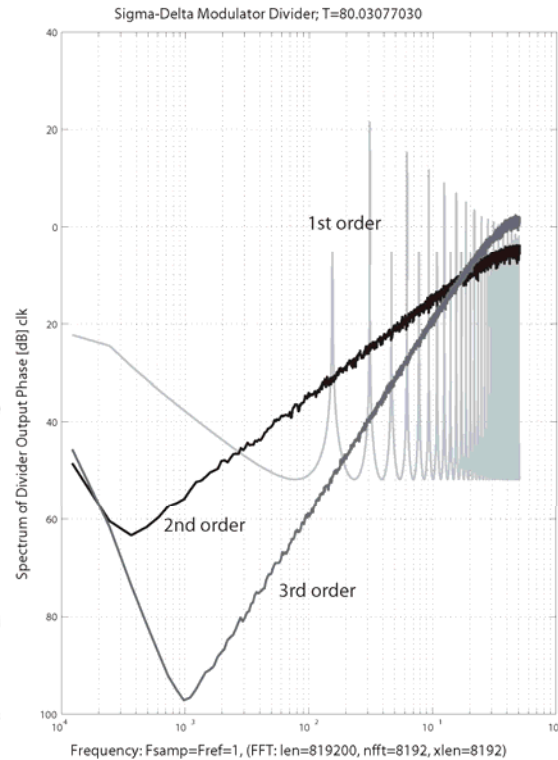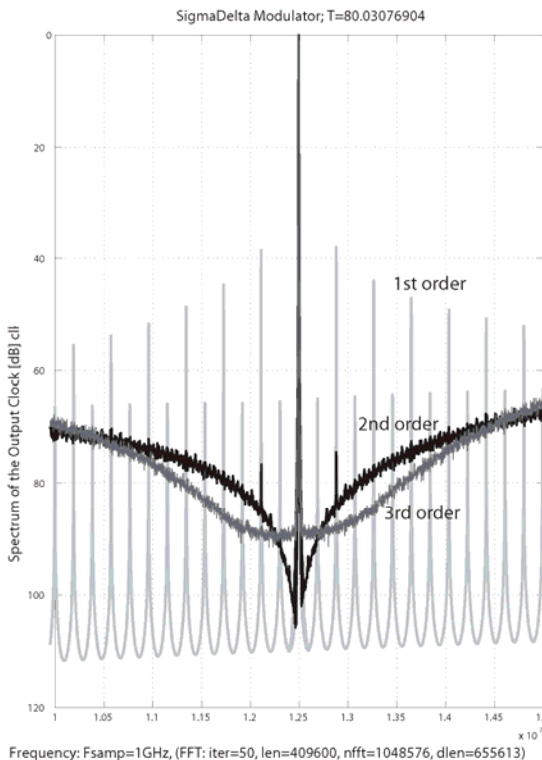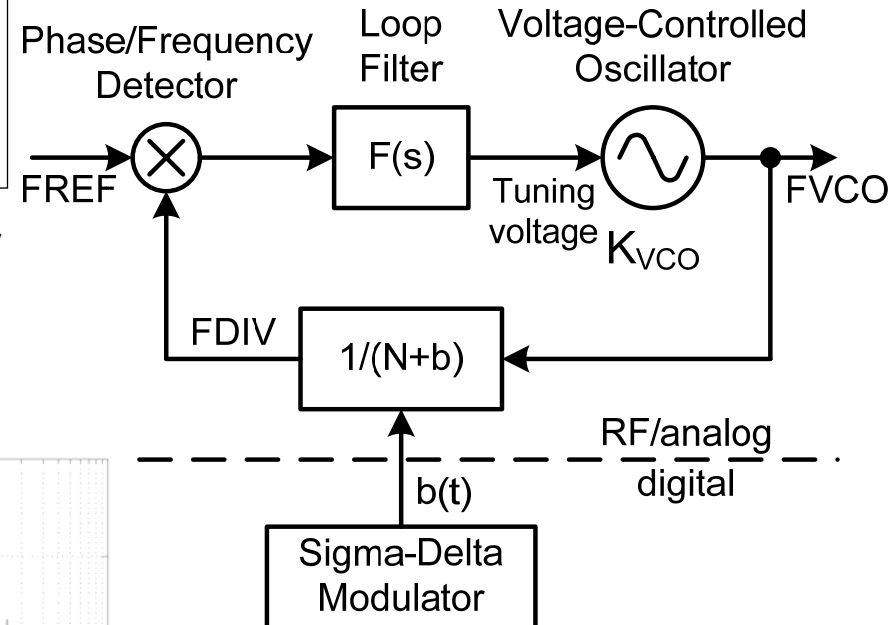$\Sigma\Delta$ modulator shapes the quantization error energy into higher frequencies which are then easy to filter out



Hybrid of DDS and PLL

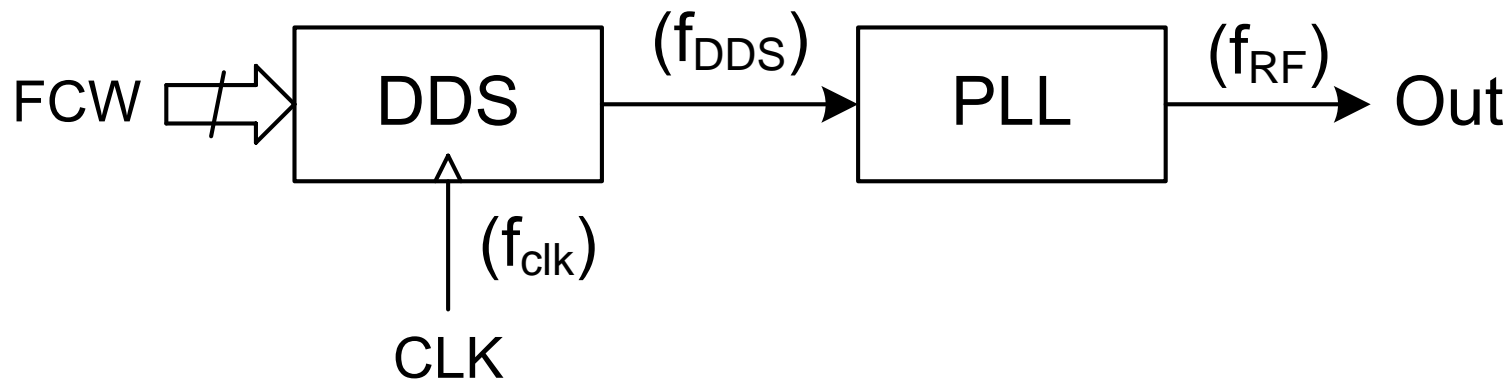
- DDS combined with PLL
- DDS operates at lower frequency: wideband modulation and fast channel hopping capability
- PLL used as frequency multiplier to up-convert the DDS output to RF band
- Used in basestations
 - Fast settling time



Motivation for (All?)-Digital PLL


- Frequency synthesizers in commercial wireless applications traditionally use charge-pump PLL's
- No prior reports on successful low-cost synthesizer architectures for mass-market mobile communications employing *all-digital* approach
- Design flow and circuit techniques are analog intensive

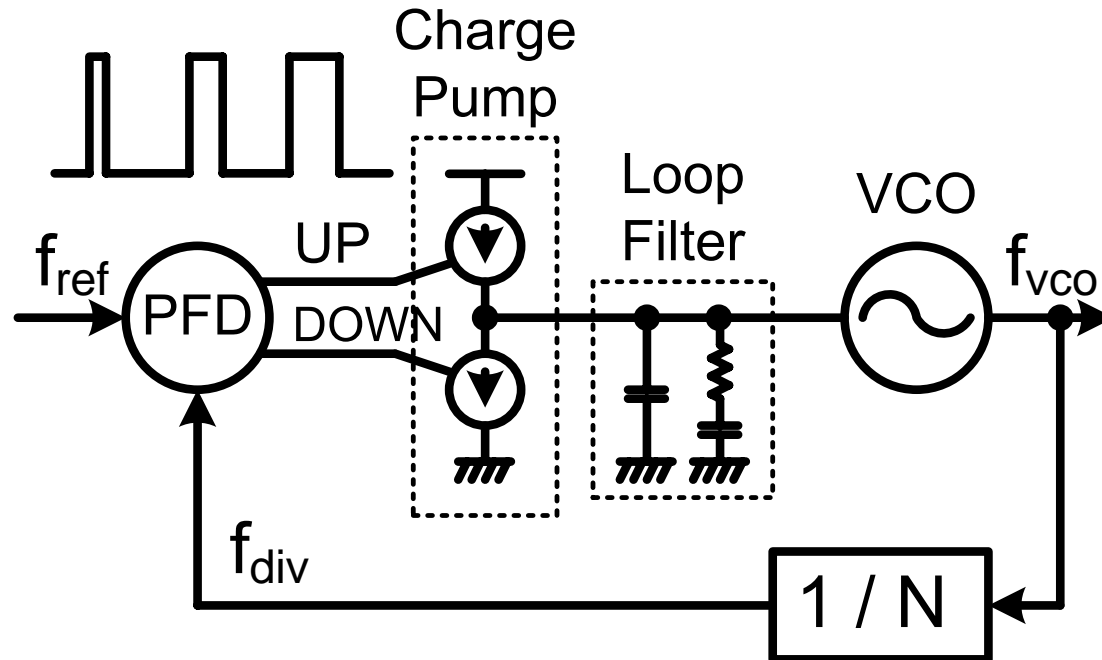- Technology incompatible with modern digital baseband processors
 - Use low-voltage nanoscale CMOS



Phase Domain Operation

 
- Charge-pump PLL does not truly operate in the phase domain: only approximation under lock
 - [2: Gardner'80] describes: “converting the timed logic levels into analog quantities”
 - Generates reference spurs that require filter




- Consequence: tradeoff between the reference spur level and settling time
- No such tradeoff with true phase-domain operation
 - See [3: Kajiwara'92]

Preview: All-Digital PLL

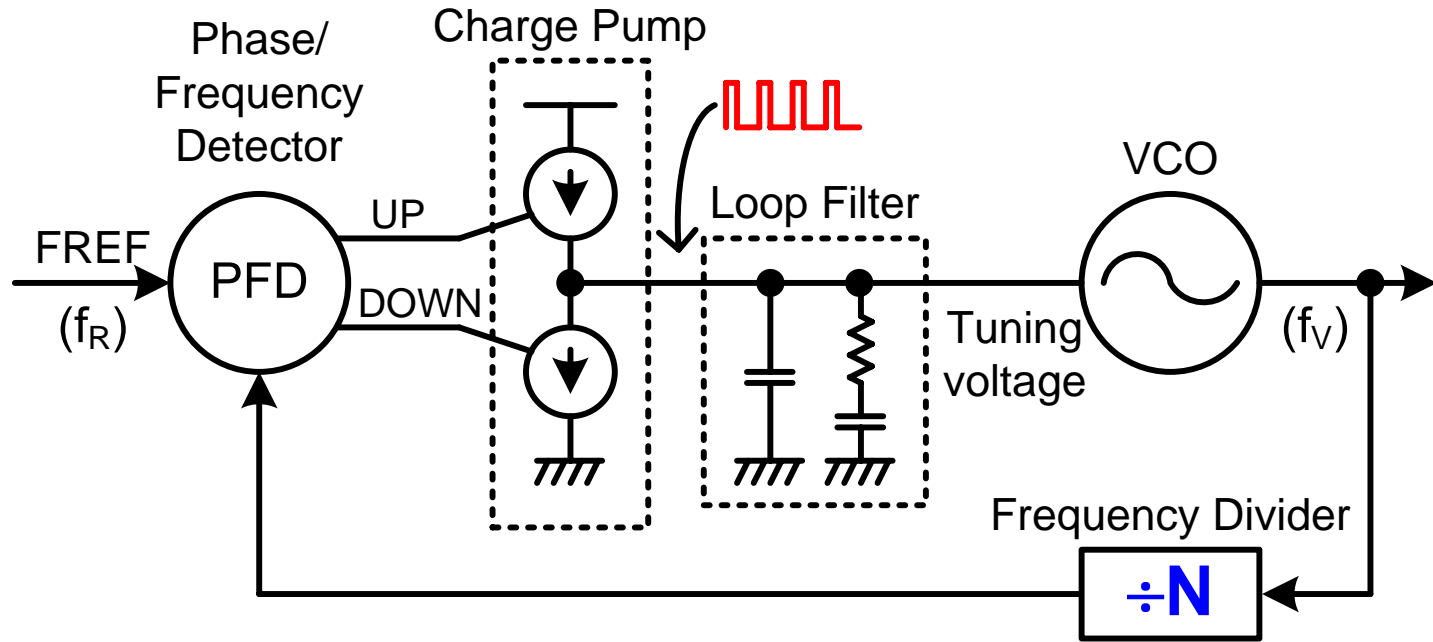- Charge-pump PLL:
- Suffers from reference spurs
- Tradeoff: bandwidth against spur level




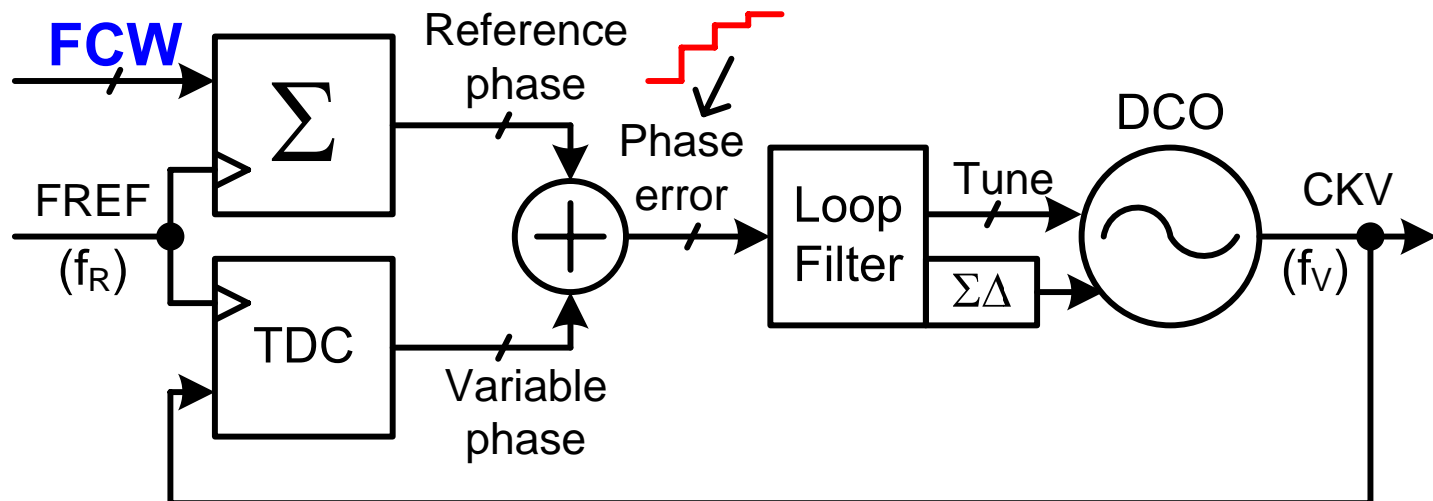- All-digital PLL:
- True phase domain operation
- (Details to come...)



Nanoscale CMOS

SoC Drives Cost Reduction

 


- 2x area reduction each process technology node
- RF/analog is 20-30% of SoC

- SoC Integration Includes:
 - RF
 - Analog
 - Power management
 - Digital baseband
 - SRAM
 - Processors
 - Software
- Most advanced process technology used to maximize integration while minimizing cost
 - 90nm (shipping)
 - 65nm (mature design)
 - 45nm and beyond (preliminary)

Why Single-Chip Radio?

 - "Integration is like gravity"
 - Already happened in hard-disk drives, ADSL, etc
 - Not a single example of reversal
- "\$20 phones"
- Large untapped market in India and China
- More "real estate" space for advanced features
- Better reliability
 - Today, more than half of the total components on a board are analog RF components
- Longer talk time



Old Platform


Technology Trends for 45 nm CMOS

- 45 nm doubles transistor density over 65 nm and quadruples over 90 nm technology
 - To support more standards, radios and multimedia in mobile phones
- Smaller transistor capacitances hence lower power dissipation
- Nominal supply voltage of 1.1 V; ranging from 0.9 V to 1.2 V
- SRAM size of 0.24 μm^2 optimized for size
- Conventional gate stack of nitrated silicon dioxide and polysilicon gate
 - Metal gate only for high-performance process (SUN Sparc)
- No high-k dielectric
 - Very little performance gain compared with higher complexity and cost
- New package technology
 - Stacked die for embedding of large memories
 - Dies embedded in a board to maximize space and performance


Nanoscale CMOS Technology Trends

- Variability of minimum size devices gets worse with each process node
- Source: ISSCC 04, Microprocessor Forum, p29

Relative Gate Length (CD) Variation

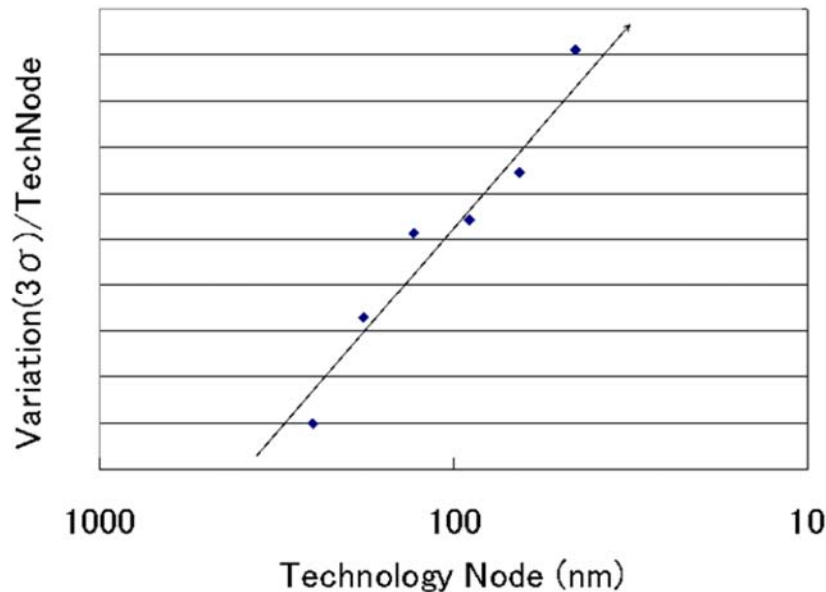

Relative NMOS Vth Variation

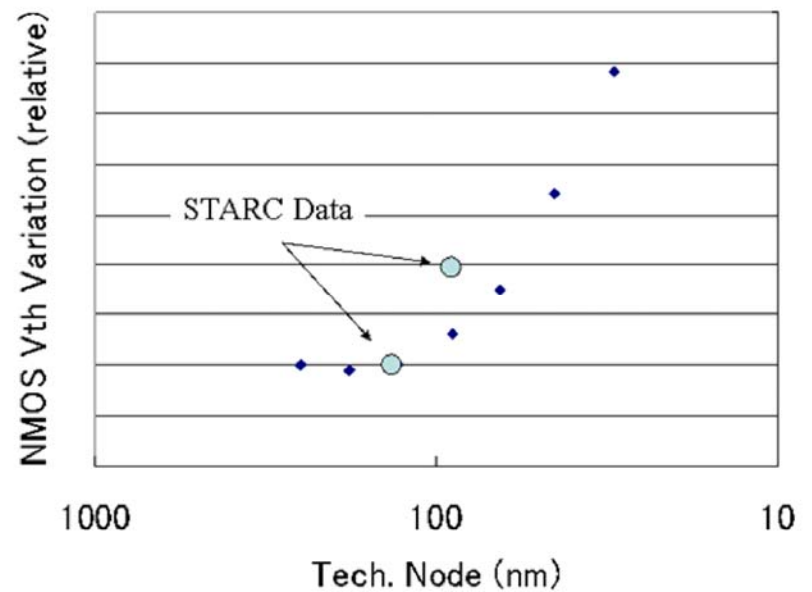

New Paradigm

In a highly-scaled CMOS technology, time-domain resolution of a digital signal edge transition is superior to voltage resolution of analog signals


Rules of nm-Scale CMOS

- **Exploit:**
 - Fast switching characteristics of MOS transistors
 - 20 ps transition and f_T of 250 GHz in 45-nm CMOS
 - Improves 20% per process node (18—24 months)
 - Small device geometries and precise device matching
 - High density of digital logic: 1 M gates/mm² in 45-nm CMOS
 - 2x scaling at each process node (18—24 months)
 - High density of SRAM memory: 4 Mbits/mm² in 45-nm CMOS
- **Avoid:**
 - Biasing currents for analog circuits
 - Reliance on voltage resolution
 - Nonstandard devices not needed for memory and logic


Trend towards Digitization (e.g.#1)

 - (Example)
- A/D => **ACCUM** => D/A
- Gets rid of the large leaky integrating capacitor
 - Leakage acts like an additional resistor
- Integrating pole stays at zero




Perrott et al
US patent 6,630,868
2001 (filing date)



Mitigation through Architecture (e.g.#1)

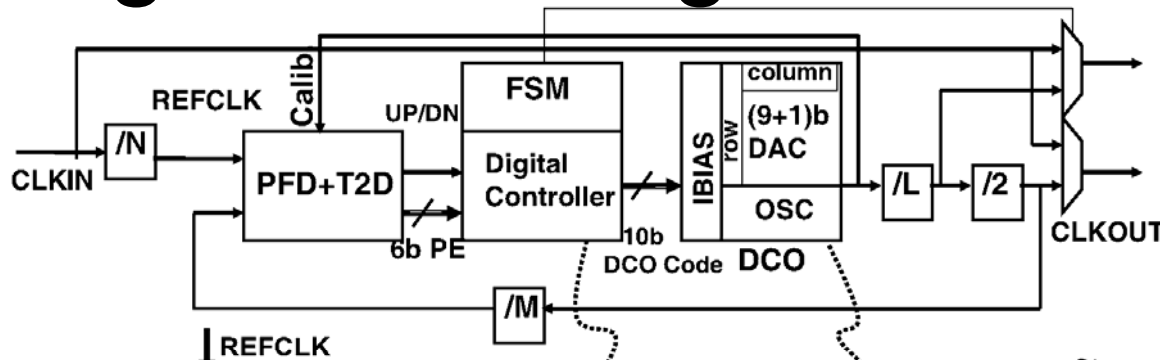

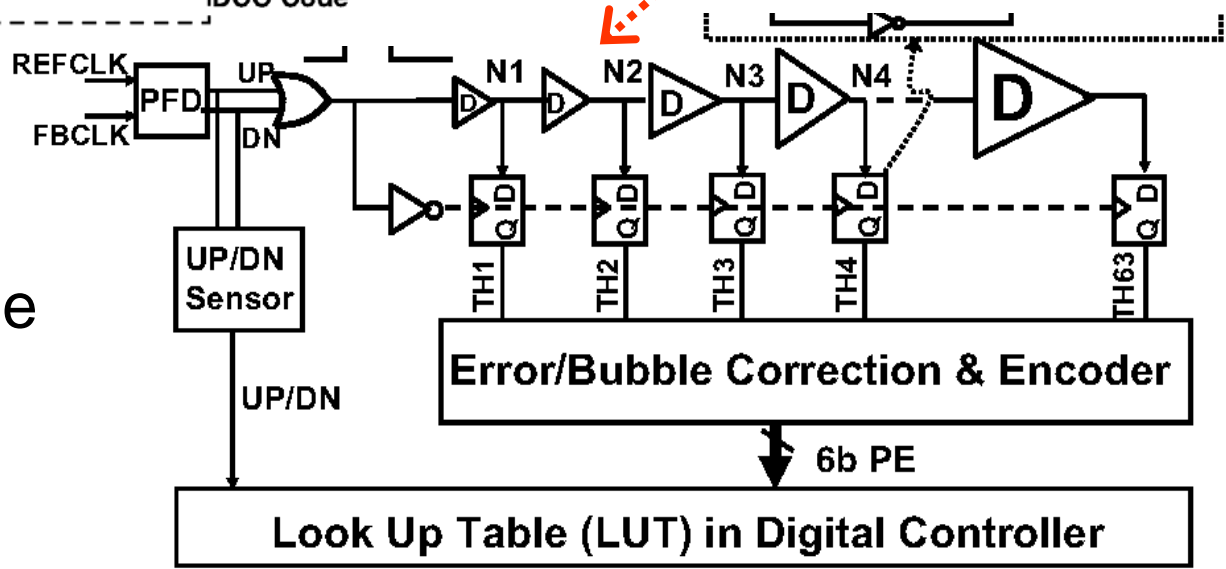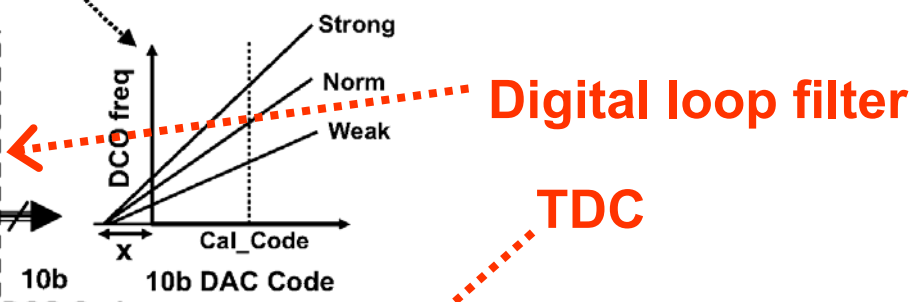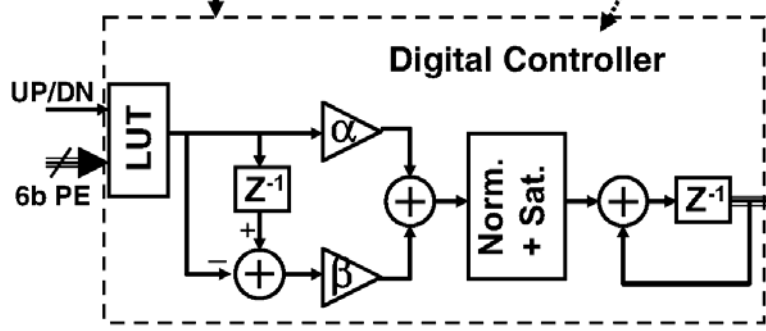
- [8: Lin'04]
- Also see
 - [5: Dunning'95]



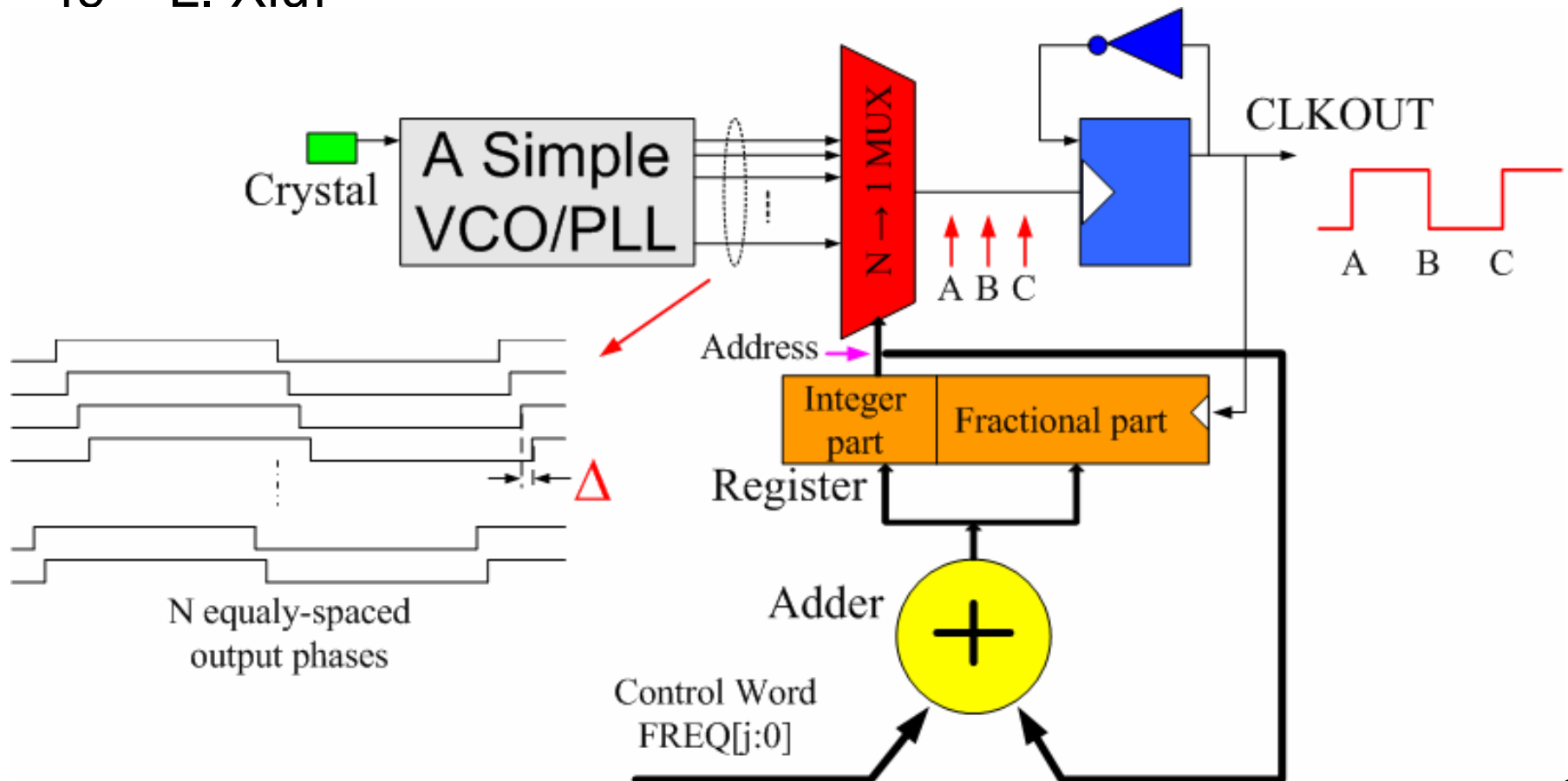- **(Example)**
- DPLL in 90-nm
- Uses TDC for phase detection
- Digital loop filter

Flying-Adder Frequency/Phase Synthesis


- Using multiple equally-spaced phases generated from a VCO to synthesis various *frequency* and *phase*, by triggering the flip-flops at predestined time
- Principle idea: see diagram below (just the principle).
- [9 – L. Xiu]




Flying-Adder Frequency/Phase Synthesis

- An example:

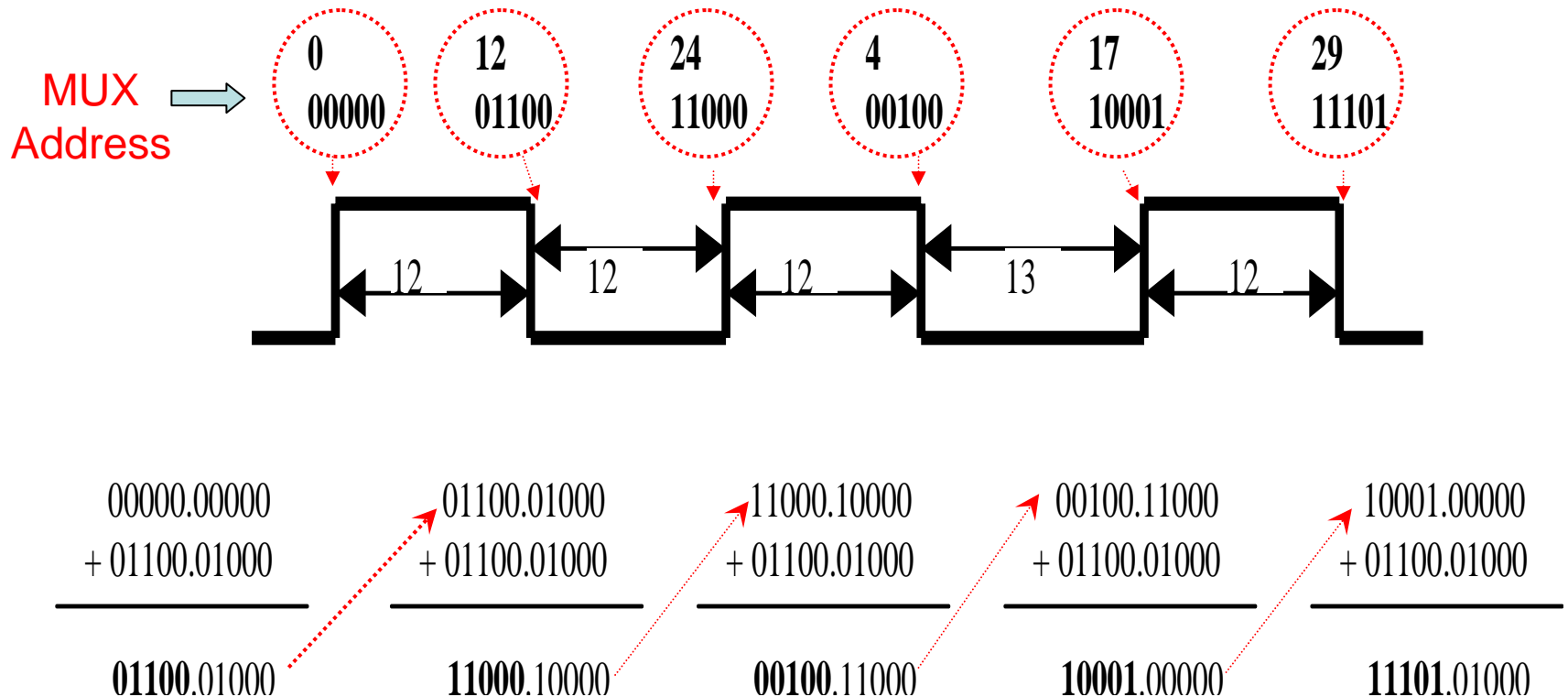- VCO at 156.25 MHz (6.4 ns) $\rightarrow \Delta = 6.4/32 = 0.2$ ns (assume $N=32$)
- Wanted: 204.08 MHz, or $T = 4.9$ ns $\rightarrow \text{FREQ}[9:0] = T/(2\Delta) = 4.9/0.4 = 12.25 = 01100.01000b$
- Integer portion is used for selecting tick, fractional portion is for accumulation.




All-Digital Phase-Locked Loop

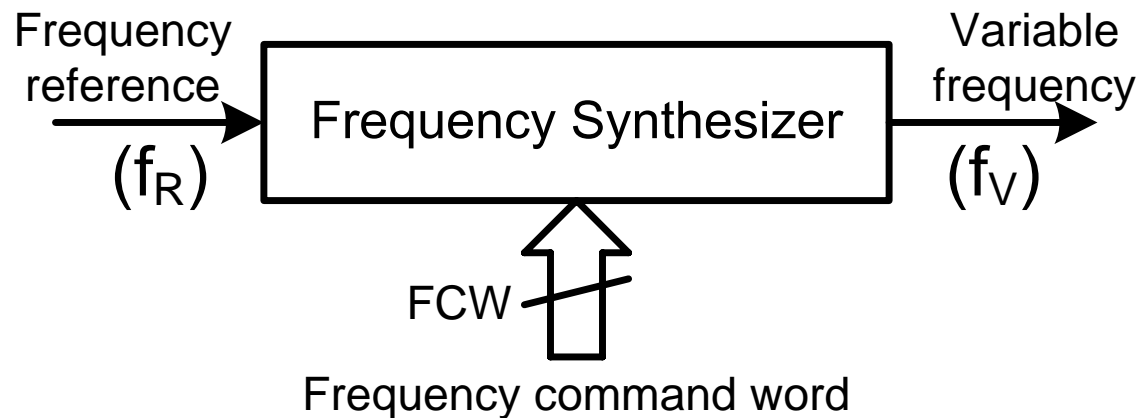


Simple Idea of Phase Domain

 - Construct expected or ideal timestamps
 - “Reference phase”
- Measure the actual timestamps
 - “Variable phase”
- Their difference is the time error
 - Used for future timing corrections as negative feedback




Issues with the Simple Idea

 - Synthesized (variable) frequency is typically much higher than the reference frequency
- Non-integer relationship
- How to truly operate in time domain, i.e., “timestamps”?




Proposed Solution

 - Reference and variable signals are digital clocks
 - Use only their (rising) edges
- Phase error calculation to be performed on reference edges
- Turn the phase detection problem around
 - Measure the reference timestamps with the variable clock
 - Sample the count of variable clock cycles with each reference edge
 - If variable phase drifts, their sampled count will get affected



Hardware Needed for Digital Operation

 - Accumulator of FCW
- Interpolator or normalize estimator of edge separation
 - Time-to-digital converter (TDC)
- RF oscillator needs to be numerically controlled:
 - Digitally-controlled oscillator (DCO)
- Digital phase detector and loop filter



Digitally-Controlled Oscillator (DCO)


$\Sigma\Delta$ Modulator and DCO Interface

Time-to-Digital Converter (TDC)

Digital Loop Filter (LF)


All-Digital PLL (ADPLL)

ADPLL Wideband Frequency Modulation

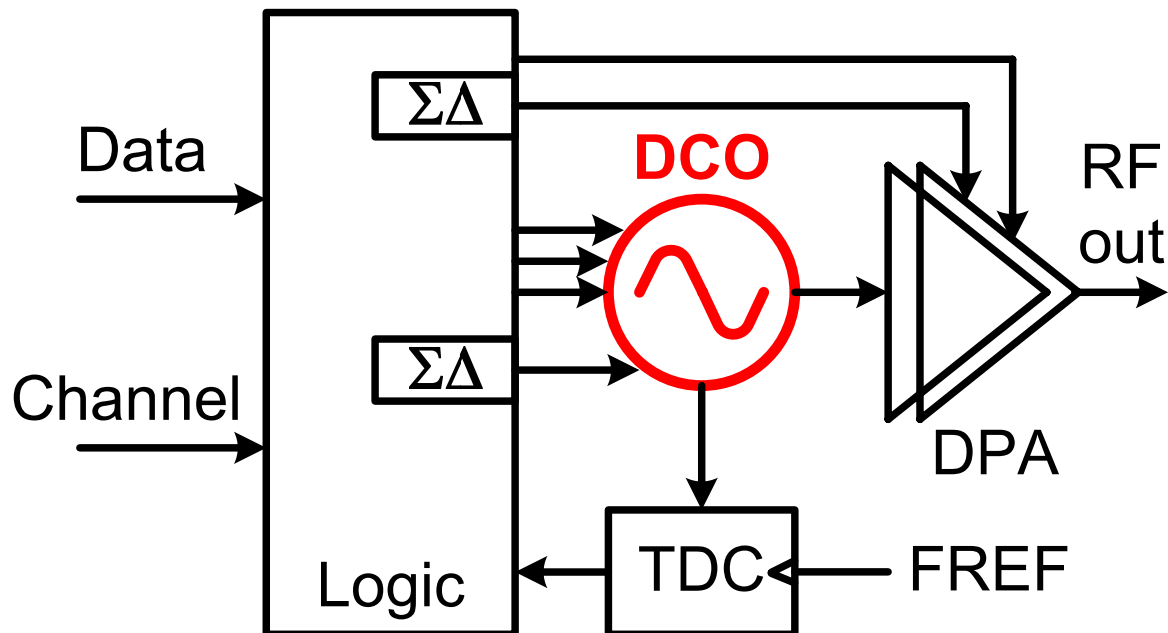

MOS Varactor

 
- Only simplest varactors in the digital CMOS
- Perceived poor quality of varactors in a nanoscale CMOS for conventional VCO's



- Conventional CMOS varactors
 - Large linear range for precise and wide frequency control
- Nanometer CMOS varactor
 - Linear range is compressed with high noise sensitivity

Digital Tuning of DCO


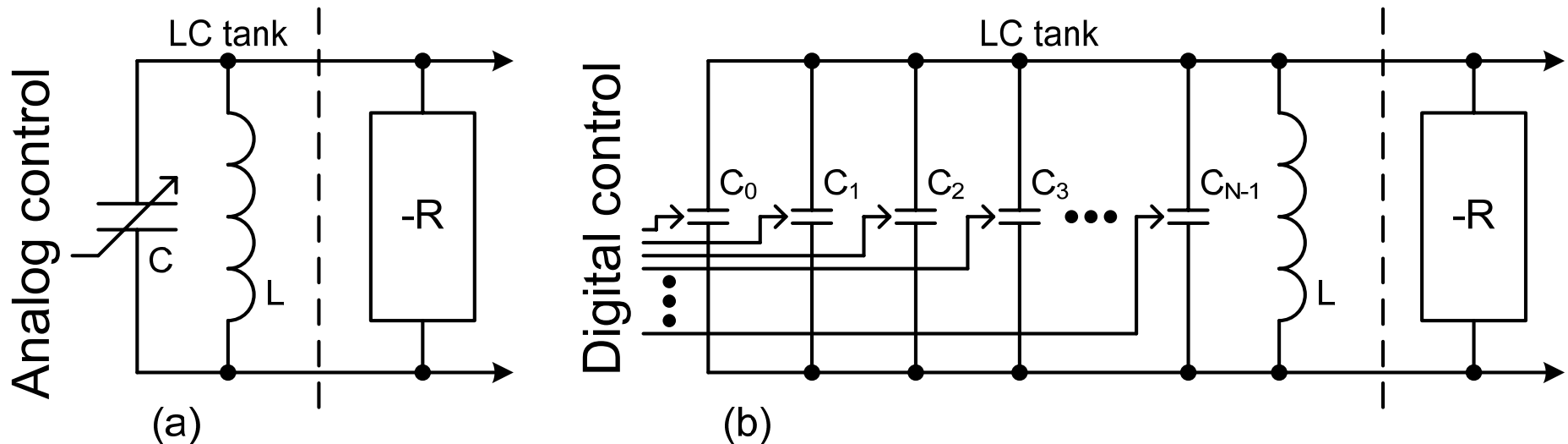
- A large linear varactor in conventional VCO replaced with a large number of tiny binary-controlled varactors in a digitally-controlled oscillator (DCO)
 - Smallest varactor size: tens of atto-farad
- Deliberate avoidance of any analog tuning
- The feedback loop could now be fully digital



DCO Varactor Functional Banks


- Process/voltage/temperature (PVT) calibration mode
- Acquisition mode (during channel select)
- Tracking mode (during the actual TX and RX)
 - Dithering to improve resolution

Varactor model:

  


GSM Bands

 - Single oscillator covers four GSM bands
 - $\div 2/\div 4$ clock division



DCO ASIC Cell

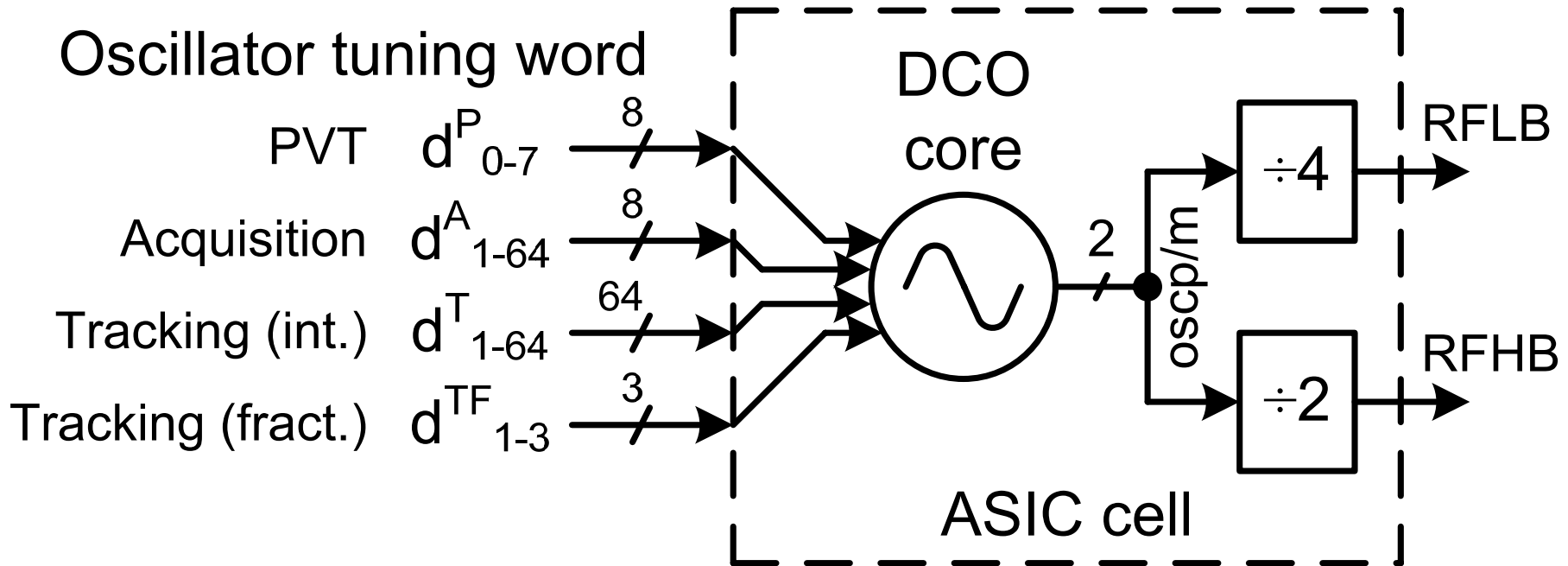

- Truly digital I/O's even at 1.8 GHz output – $t_r < 50$ ps
- DCO built as a digital ASIC cell despite analog underlying internals
- DCO analog nature does not propagate
- Circuitry around it can be digital

Digitally-Controlled Oscillator (DCO)


$\Sigma\Delta$ Modulator and DCO Interface

Time-to-Digital Converter (TDC)

Digital Loop Filter (LF)


All-Digital PLL (ADPLL)

ADPLL Wideband Frequency Modulation

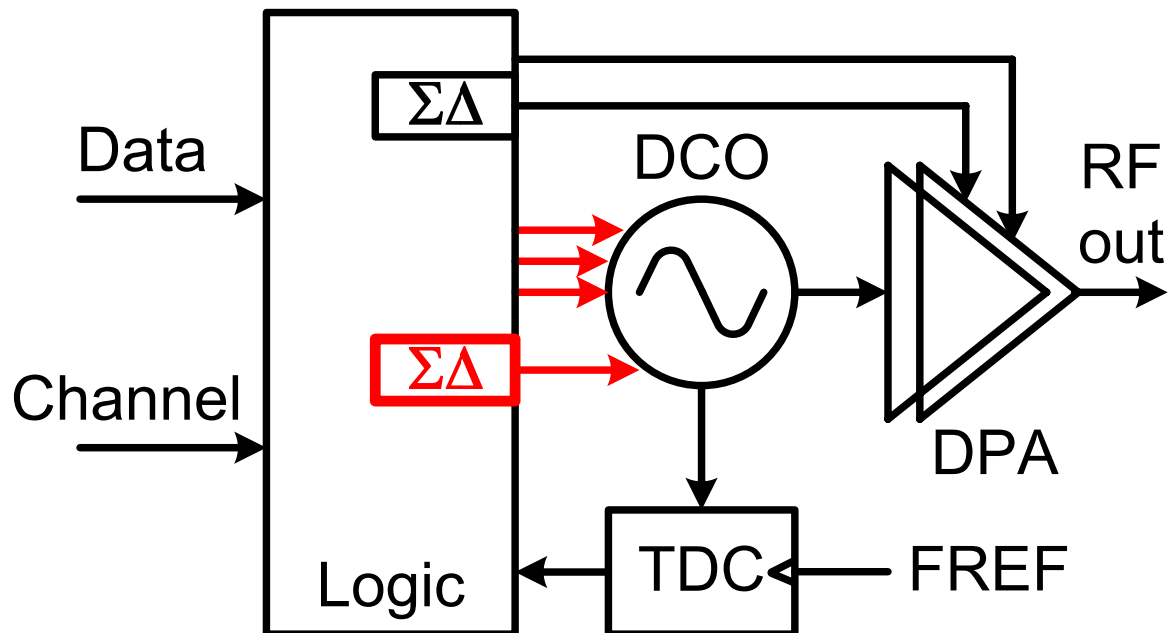


DCO Varactor Dithering Principle

- Frequency resolution enhanced by high-speed dithering of the finest varactors
- Produces spurious tone at the oscillator output with power inversely proportional to the dithering speed
 - Spur power = $-20 \log(\beta/2)$ [dBc], where β is a dimensionless ratio of the peak frequency deviation (low) to the modulating frequency (high)
 - e.g., $\beta = 12 \text{ kHz} / 225 \text{ MHz} \Rightarrow -91 \text{ dBc spur}$

 


Sigma-Delta DCO Dither

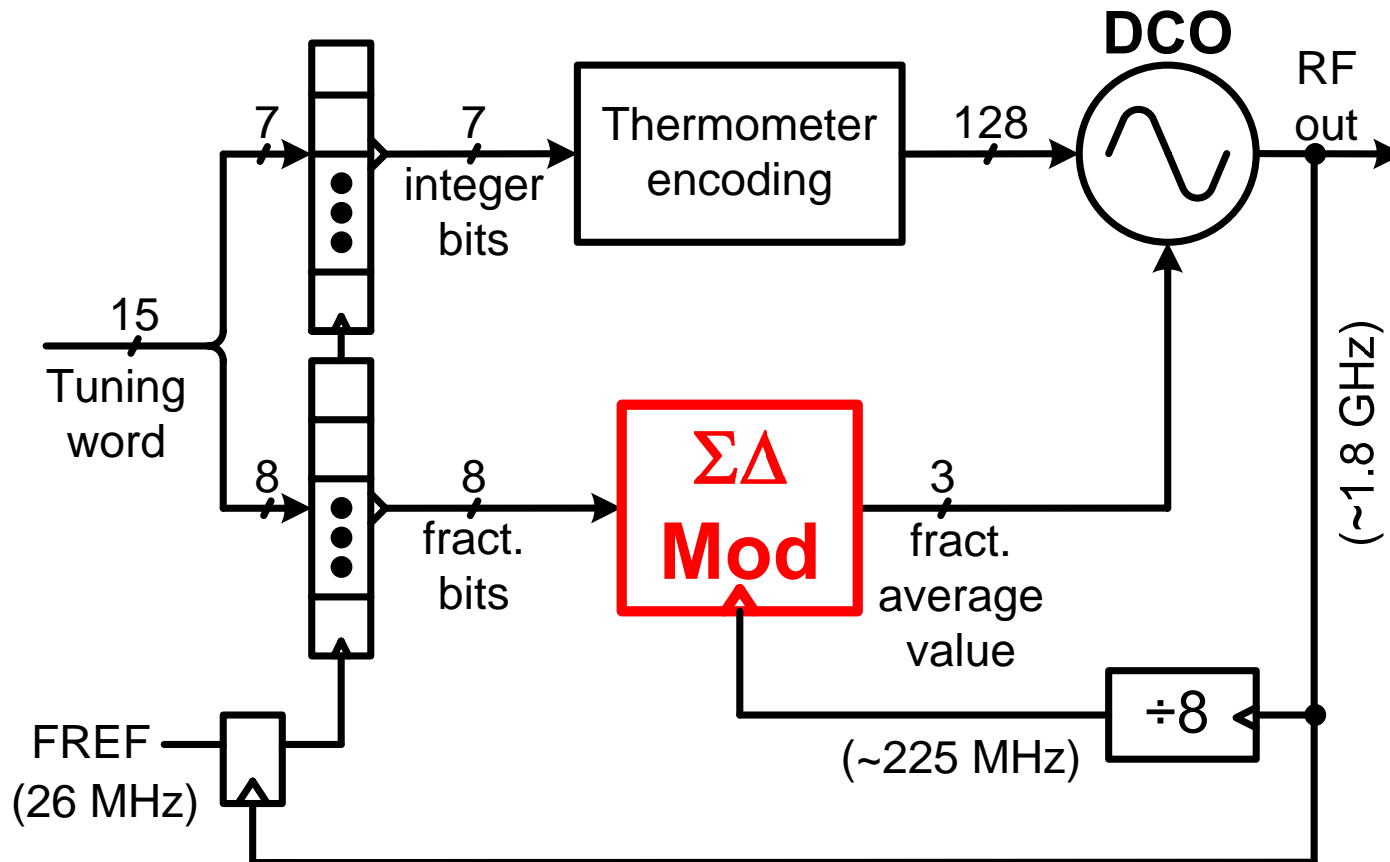- Improves time-averaged DCO frequency resolution over the basic $\Delta f = 12$ kHz
 - New resolution: $12 \text{ kHz} / 2^8 = 47 \text{ Hz}$



$\Sigma\Delta$ Modulator

 - 2nd order MASH structure
- Inspired by [4] (Riley'93)
 - Critical path retimed for high-speed operation
- Addition of $\Sigma\Delta$ polynomial inside the DCO





Simulation Example of $\Sigma\Delta$ DCO Dither

- 2nd order MASH $\Sigma\Delta$ Modulator

- Fixed-point DCO tuning word

  - **Red:** Integer DCO input word
- **Black:** running average
 - Faithful reproduction of the input!



DCO Quantization Noise Derivation



Total Q-noise power:

$$\sigma_{\Delta f}^2 = \frac{\Delta f_{res}^2}{12}$$

  [17: JSSC Nov'05]

Q-noise spectrum:

$$\frac{S_{\Delta f}}{2} = \frac{\sigma_{\Delta f}^2}{f_{dith}} = \frac{\Delta f_{res}^2}{12 \cdot f_{dith}}$$



Phase noise (PN) due to white dither:

$$L(\Delta f) = \frac{1}{12} \left(\frac{\Delta f_{res}}{\Delta f} \right)^2 \frac{1}{f_{dith}} \left(\text{sinc} \frac{\Delta f}{f_{dith}} \right)^2$$

PN due to $\Sigma\Delta$:

$$L(\Delta f) = \frac{1}{12} \left(\frac{\Delta f_{res}}{\Delta f} \right)^2 \frac{1}{f_{dith}} \left(2 \sin \frac{\pi \Delta f}{f_{dith}} \right)^{2n}$$


PN is frequency shaped!

Theoretical Phase Noise Spectra


Dithering of the DCO tracking bank varactors

 [17: JSSC Nov'05]

- $\Delta f = 12$ kHz
- $f_R = 26$ MHz
- $f_{\text{dith}} = 225$ MHz
- 2nd order $\Sigma\Delta$
- **Quantization noise energy at high-freq.**




Measured DCO Phase Noise

 


Dynamic Element Matching

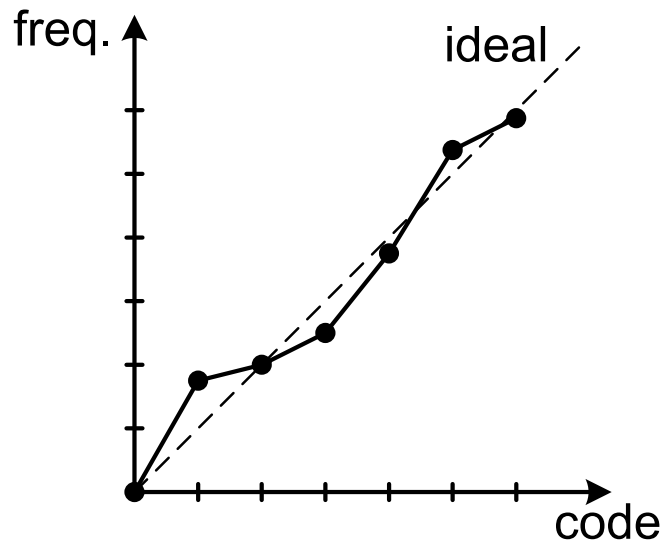- Unit-weighted varactors have slightly different capacitive values
- As capacitors are turned on and off, non-linearities will be evident in the output
- Dynamic element matching (DEM) to improve digital-to-frequency conversion linearity






8x8 varactor encoding matrix:

 

Progression of time (shown 8 cycles)


Synchronously-Optimal Sampling

   Phase noise at 400 kHz offset vs flyback delay



- DCO is a time-variant system
- Digital input controls the oscillating frequency by modifying the total capacitance
- Oscillator input word changes only at precise DCO state where it causes least amount of perturbations

Normalized DCO

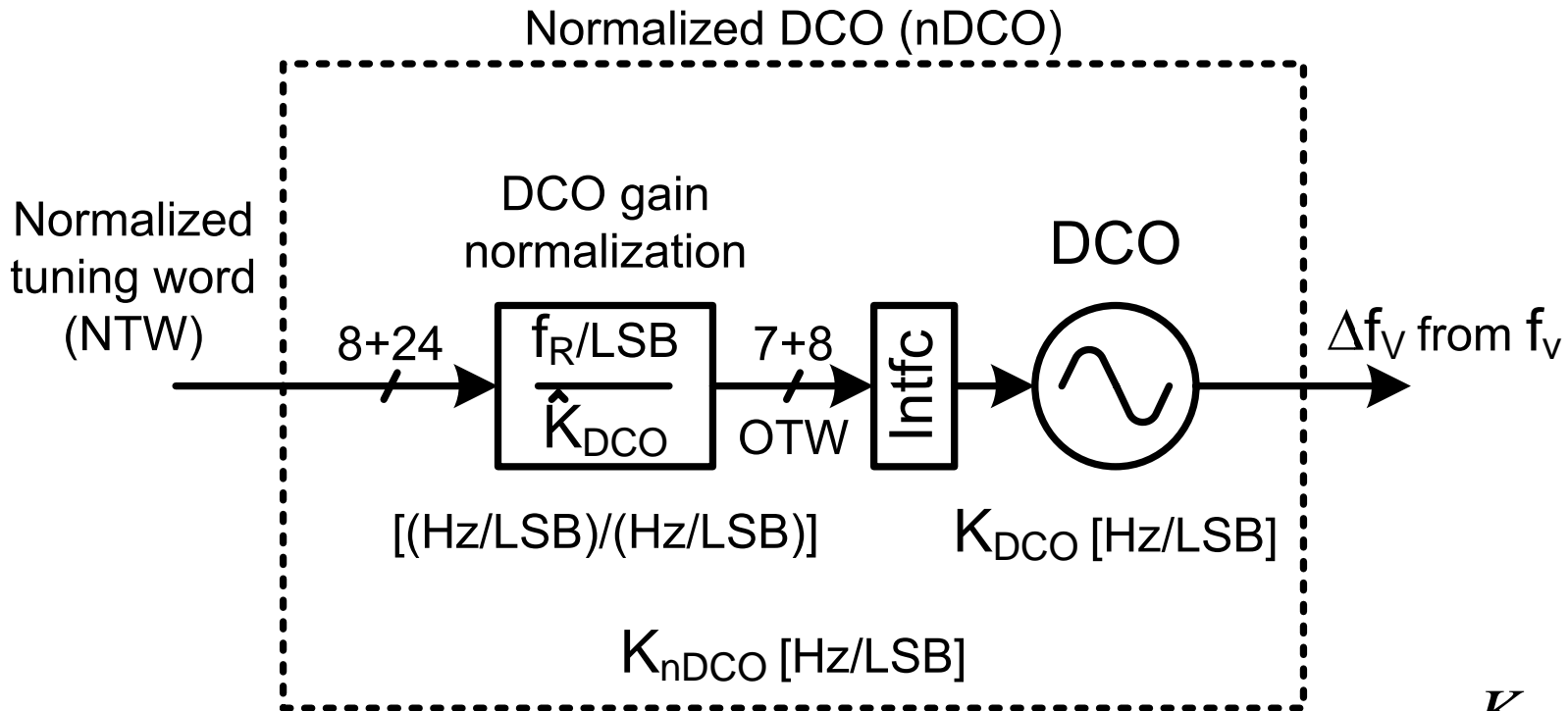

$$K_{\text{nDCO}}(f) = f_R \frac{K_{\text{DCO}}}{\hat{K}_{\text{DCO}}} = f_R \cdot r$$

- K_{DCO} is dependent upon PVT
- K_{DCO} therefore is tracked and normalized
- Decouples the phase and frequency info from process, voltage and temperature


Digitally-Controlled Oscillator (DCO)
 $\Sigma\Delta$ Modulator and DCO Interface

Time-to-Digital Converter (TDC)

Digital Loop Filter (LF)



All-Digital PLL (ADPLL)

ADPLL Wideband Frequency Modulation

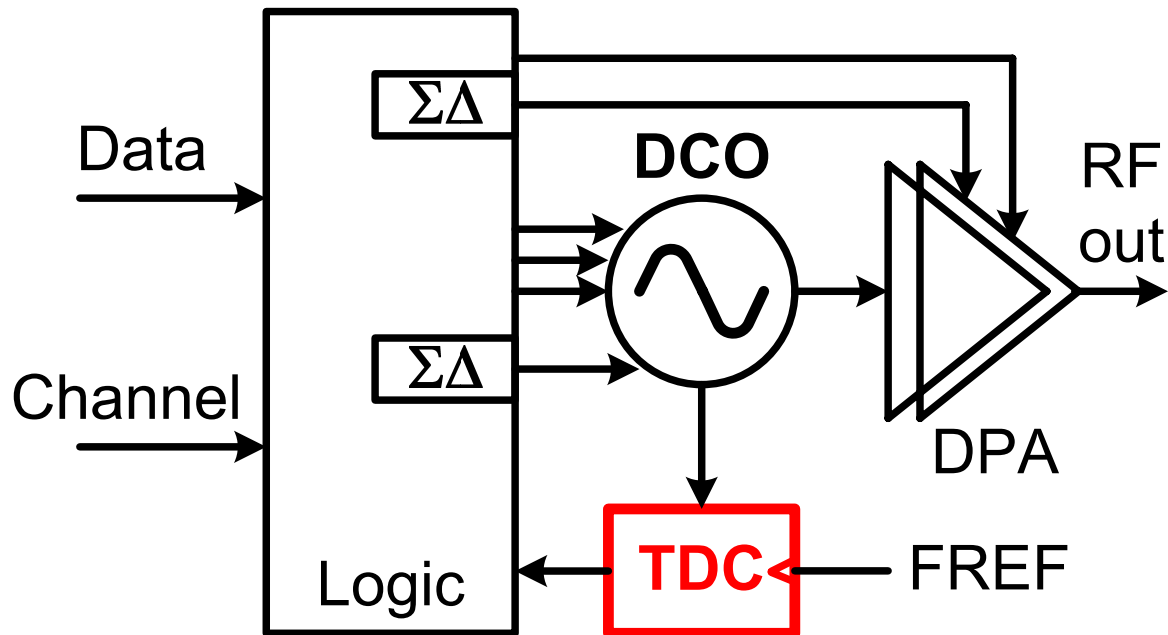


Time-to-digital Converter (TDC)

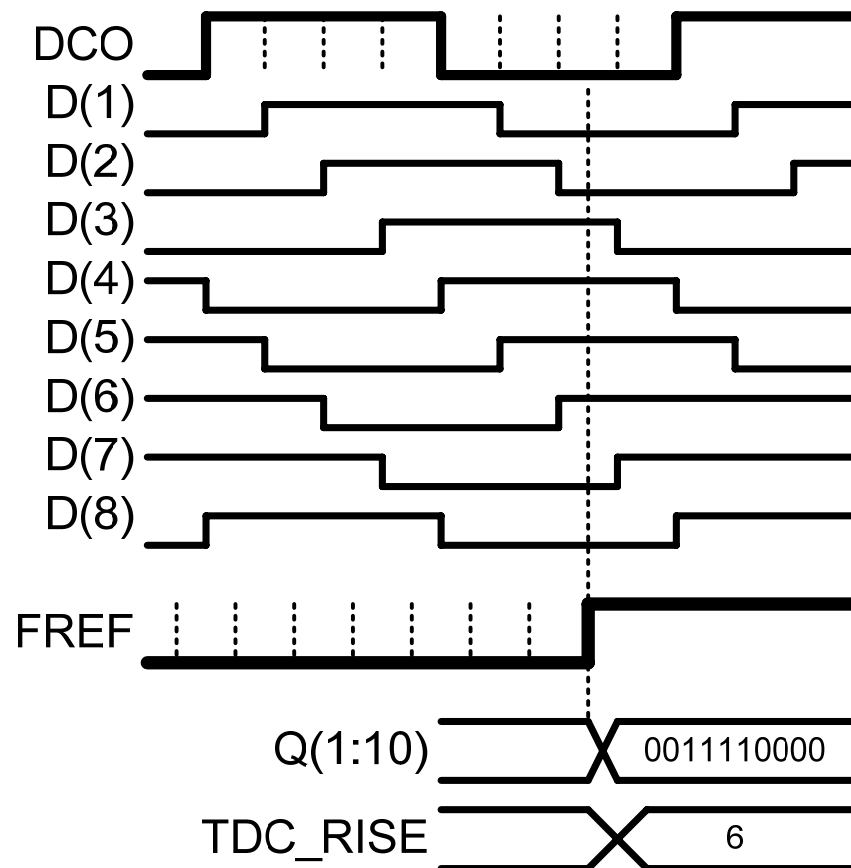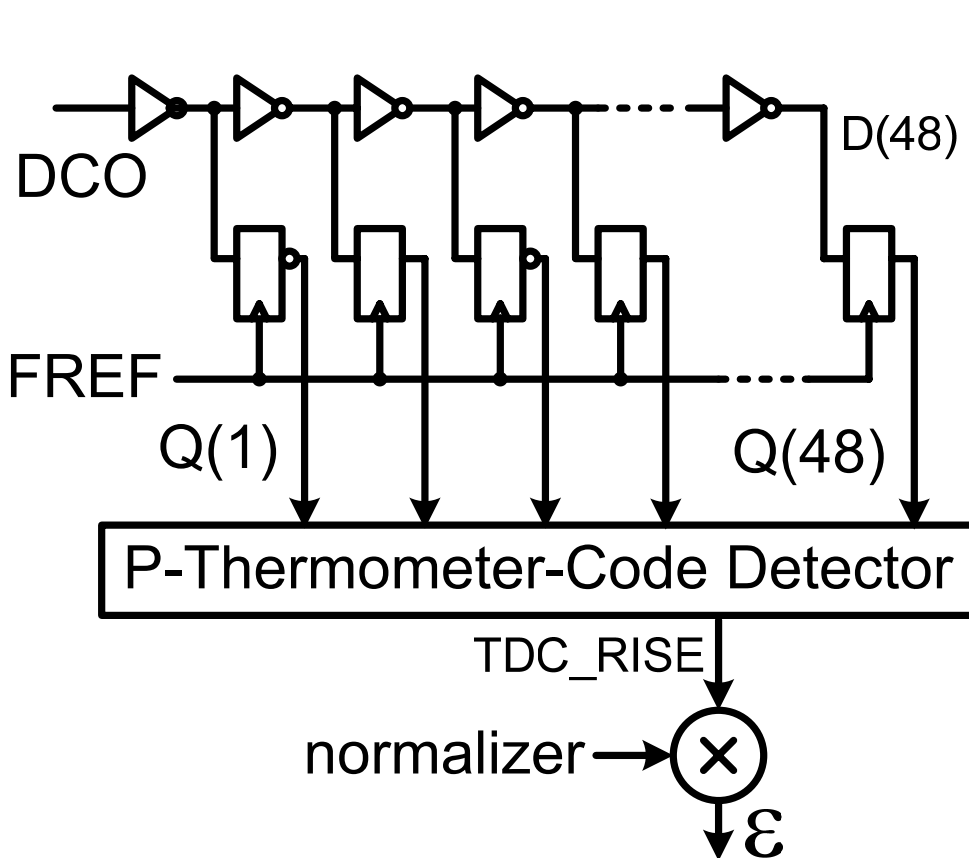- Quantized phase detector with resolution of about 20 ps
- DCO clock passes through the inverter chain
- Delayed outputs are sampled by FREF



TDC Core Implementation

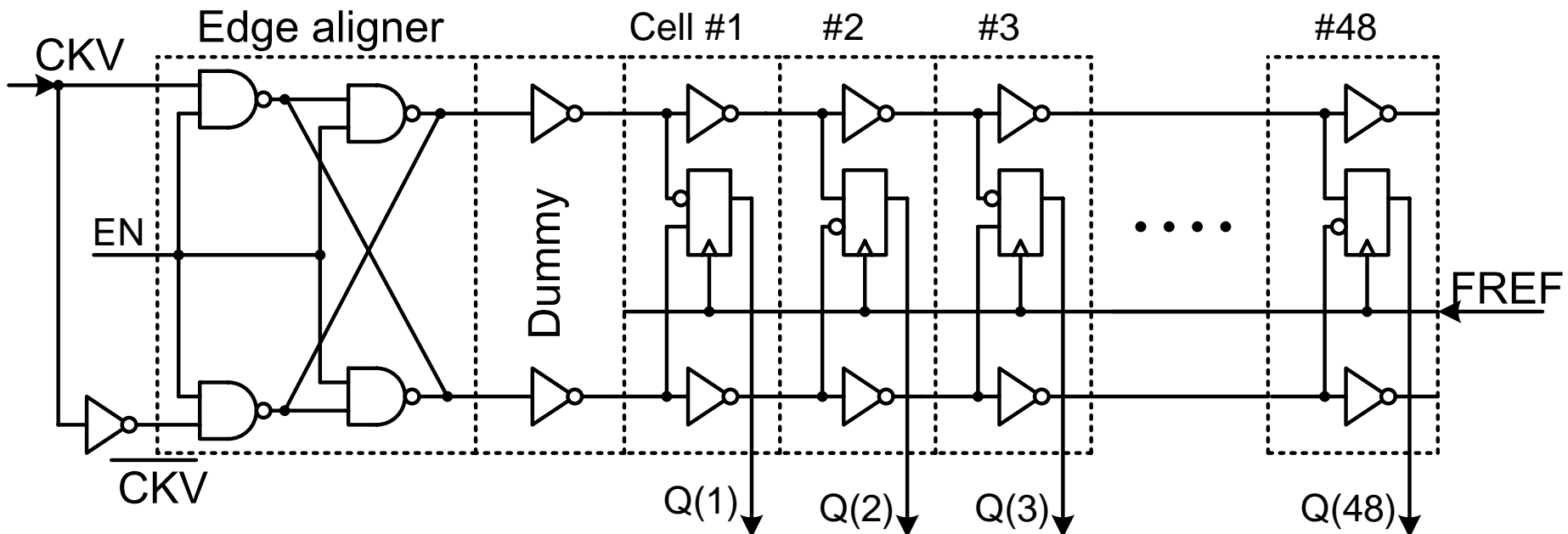- Novel pseudo-differential architecture
- Insensitive to NMOS and PMOS mismatches
- TDC resolution close to an inverter delay
 - 15 – 20 ps
 - Fastest logic-level regenerative delay in CMOS





High-Resolution Flip-Flop

- Adapted from [Nikolic, JSSC'00]
- Symmetric along the vertical axis
- Identical resolution of rising and falling edges
- Light input loading

- Simulated metastability


Flipflop Metastability Curve

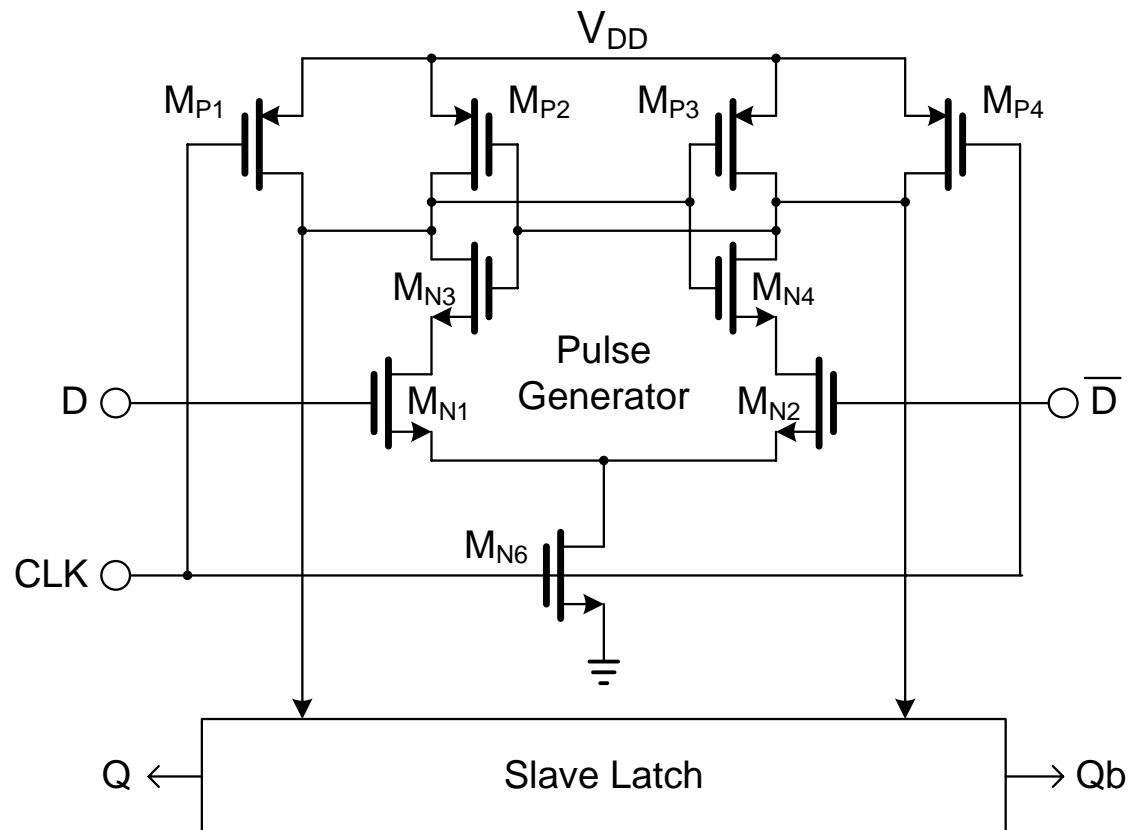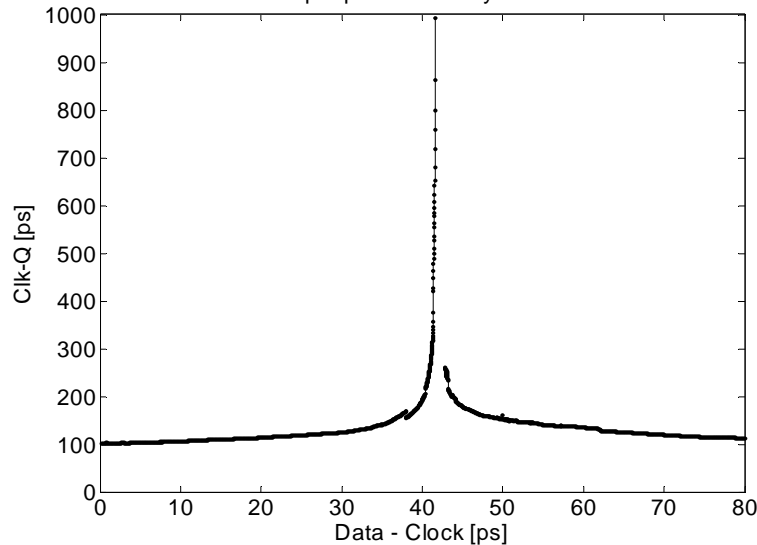

Measured TDC Transfer Function

- Only even-odd nonlinearity


TDC transfer function

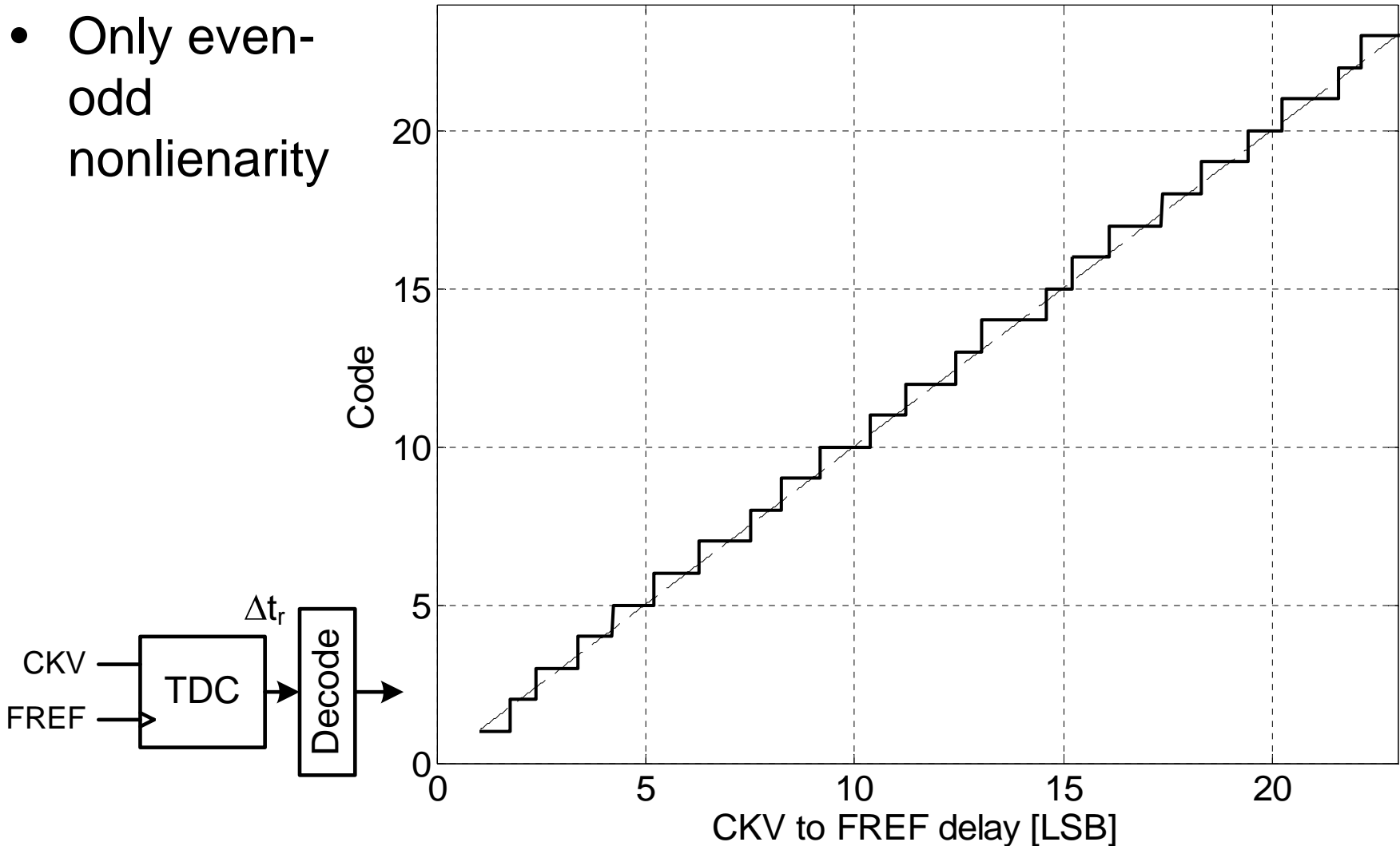

TDC Normalization


- Expected output between 0.0 – 1.0 UI
 
$$-\varepsilon = \frac{2^{W_F}}{\bar{T}_V / \Delta t_{inv}}$$





- Accurate calibration of the inverter delay
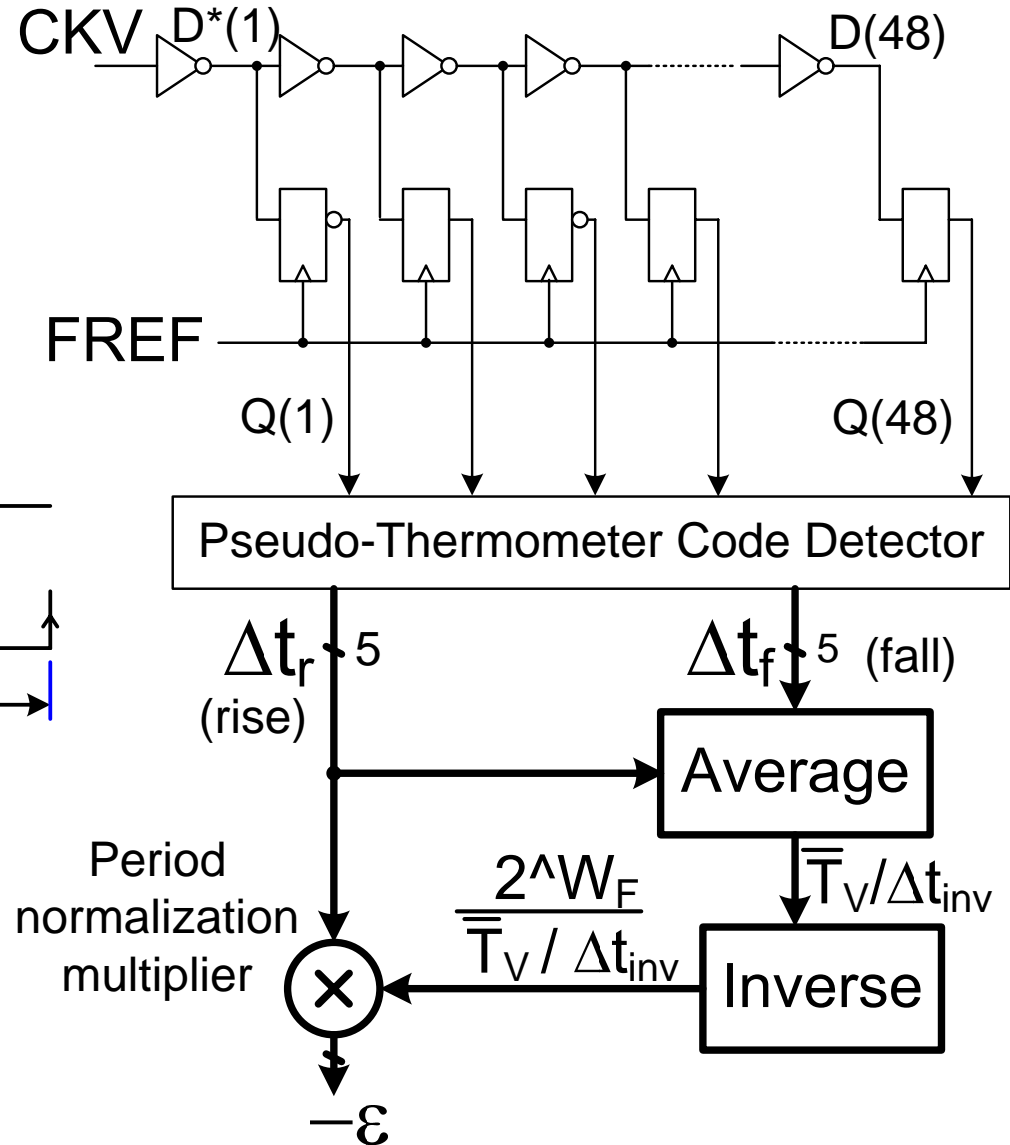
$$\bar{T}_V = \frac{1}{N_{avg}} \sum_{k=1}^{N_{avg}} T_V[k]$$




TDC System

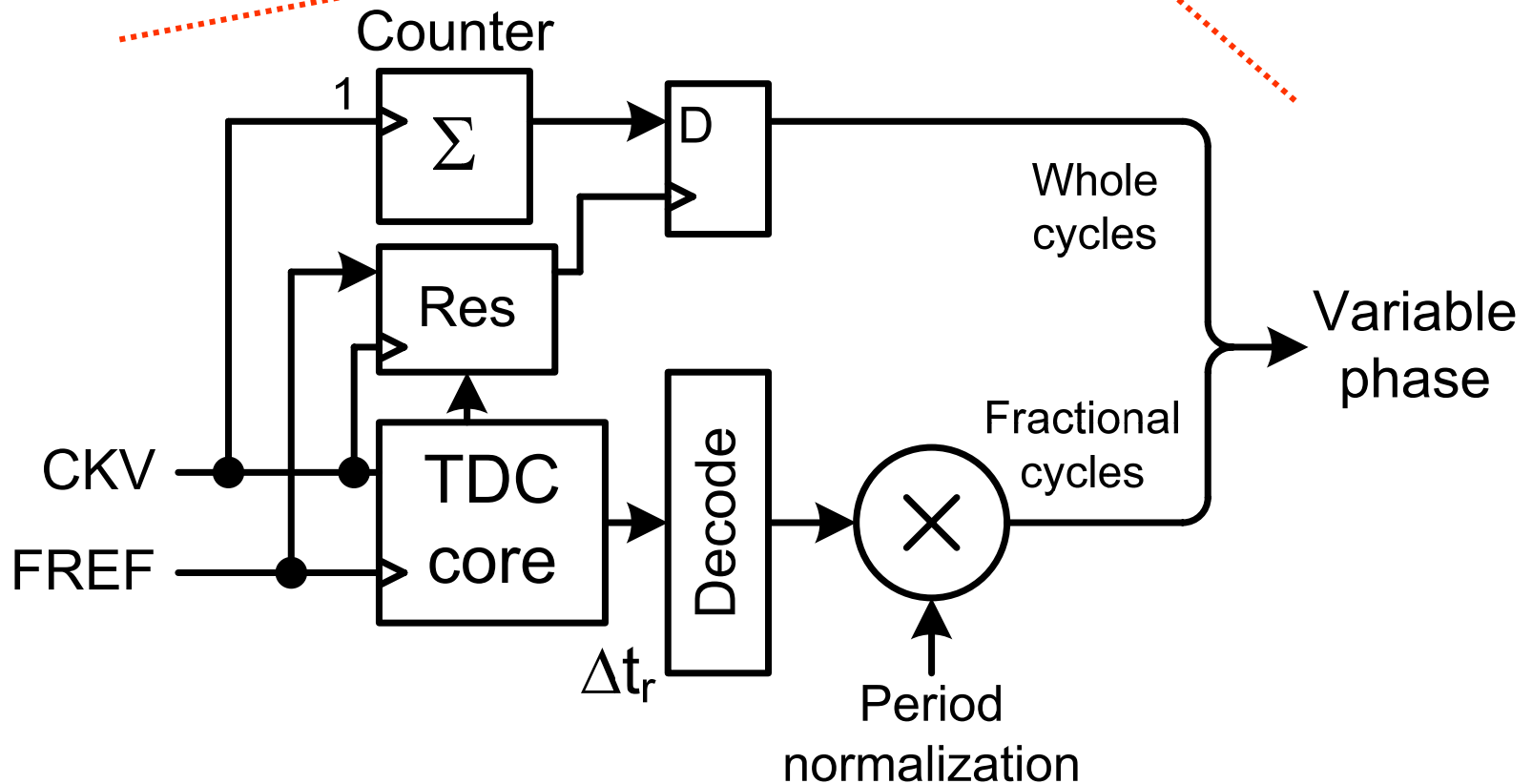 - Extended dynamic range
- Resampler needed to avoid metastability




TDC-Based All-Digital PLL

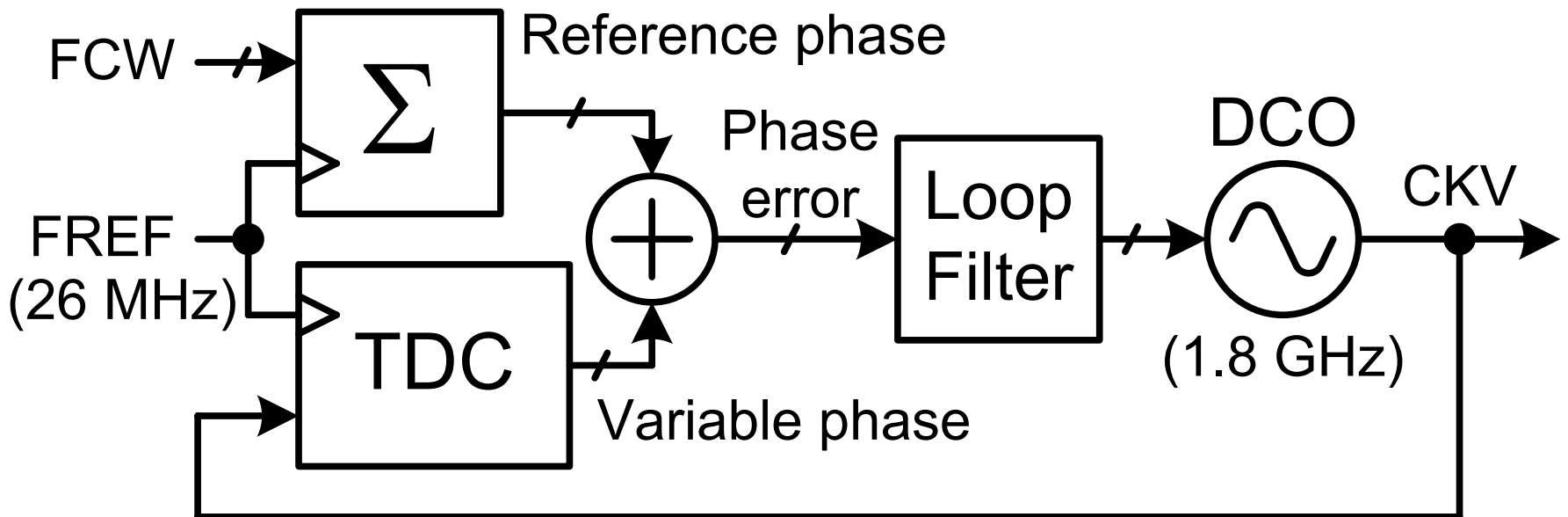- TDC replaces the conventional PFD and charge pump
- TDC measures the actual FREF timestamps
- FCW is a fixed-point frequency multiplication ratio
- FREF timestamps compared with accumulated FCW



Phase Noise Due to TDC

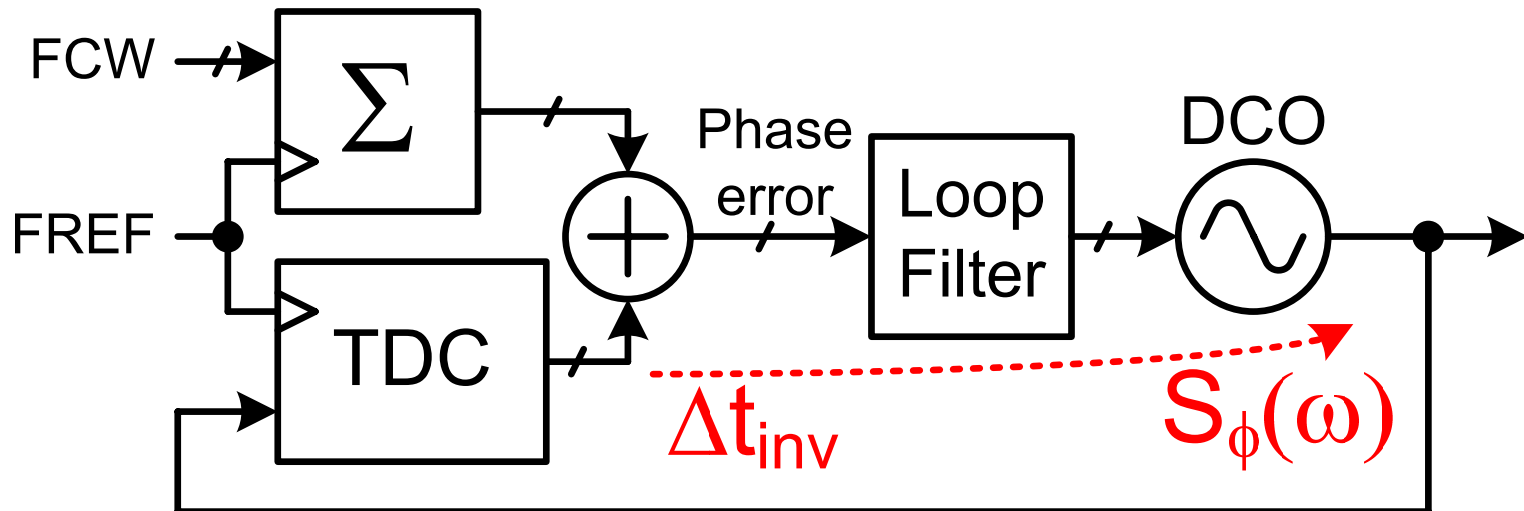

- In-band phase noise at RF output [TCAS-II'06]

$$L = \frac{(2\pi)^2}{12} \left(\frac{\Delta t_{inv}}{T_V} \right)^2 \cdot \frac{1}{f_R}$$


- E.g., $\Delta t_{inv}=20\text{ps}$, $f_V=1.8\text{GHz}$, $f_R=26\text{MHz}$, **$L = -97.8\text{dBc/Hz}$**
- Good enough for GSM: can get only better

Digitally-Controlled Oscillator (DCO)
 $\Sigma\Delta$ Modulator and DCO Interface
Time-to-Digital Converter (TDC)

Digital Loop Filter (LF)


All-Digital PLL (ADPLL)

ADPLL Wideband Frequency Modulation

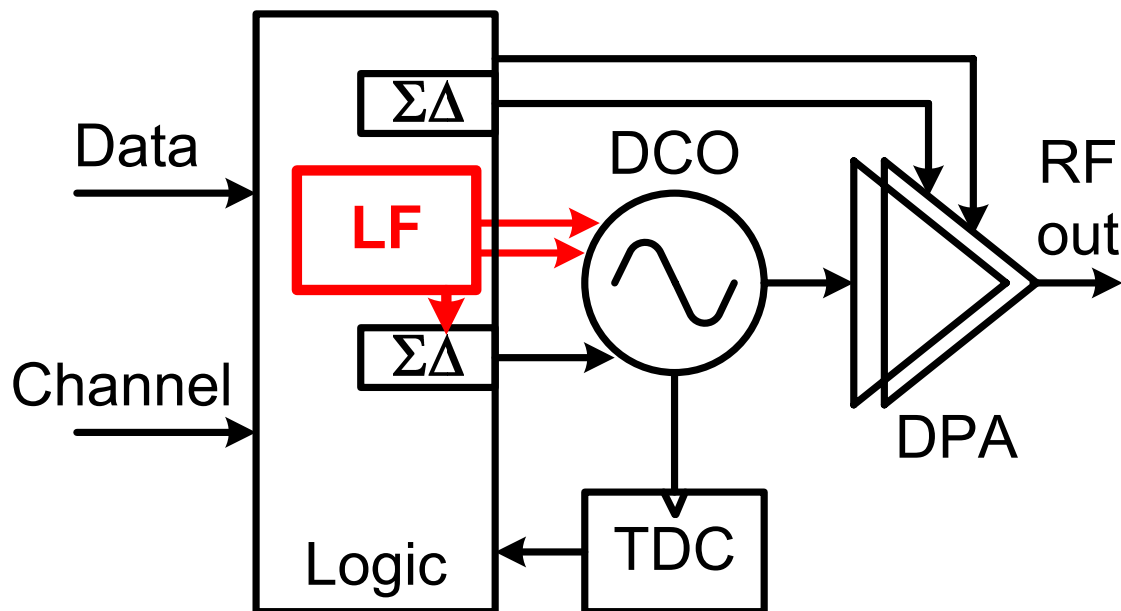


Type-II Loop Filter

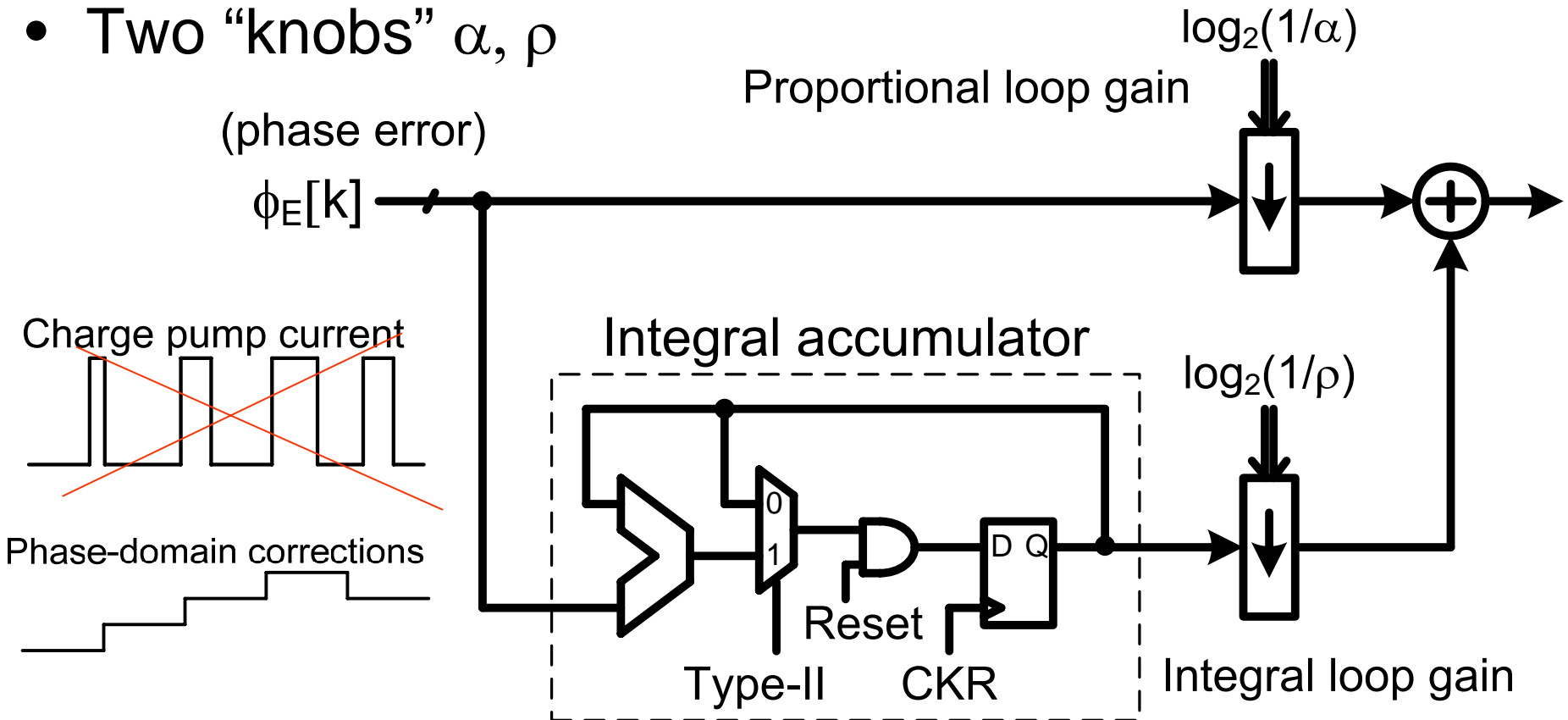- No correlative detection spurs
- Software programmed PLL loop:
 - Gentle transition of type-I to type-II
- Two “knobs” α , ρ




Loop filter with IIR Filtering

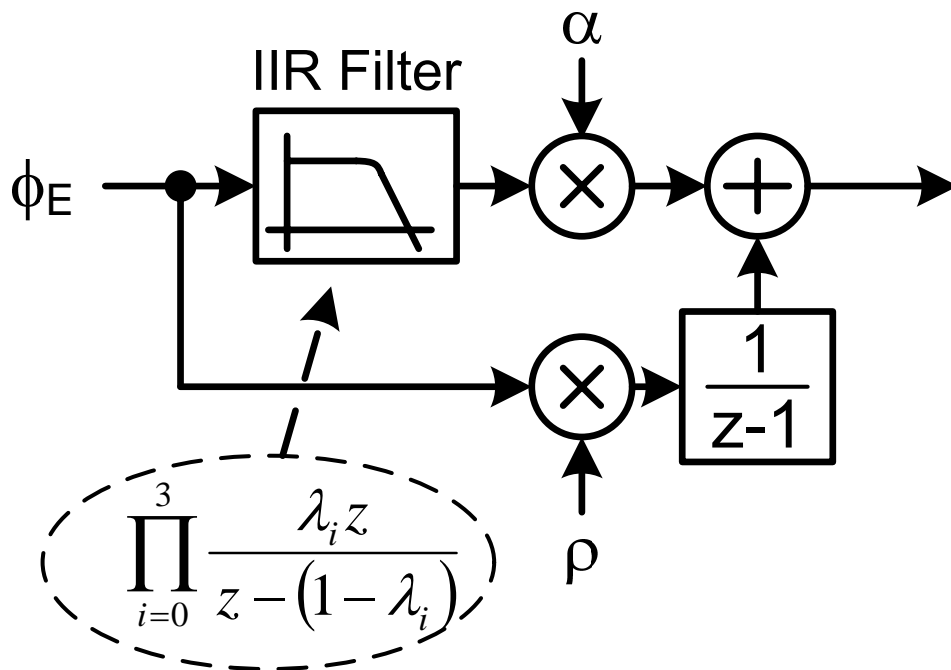- 4th order digital IIR loop filter to suppress the frequency reference and TDC quantization noise
- Unconditionally stable IIR filter



Single-pole IIR stage:

 
$$y[k] = (1 - \lambda) \cdot y[k - 1] + \lambda \cdot x[k]$$



Digitally-Controlled Oscillator (DCO)
 $\Sigma\Delta$ Modulator and DCO Interface
Time-to-Digital Converter (TDC)
Digital Loop Filter (LF)

All-Digital PLL (ADPLL)


ADPLL Wideband Frequency Modulation

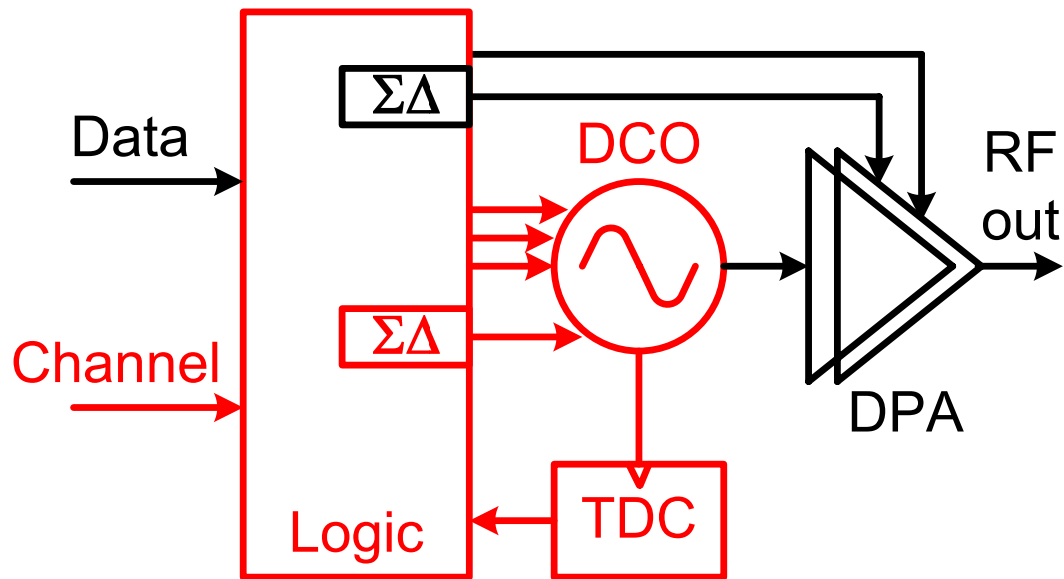

All-Digital PLL (ADPLL)




- Phase domain operation
- Digitally synchronous fixed-point arithmetic
- Phase signals cannot be corrupted by noise
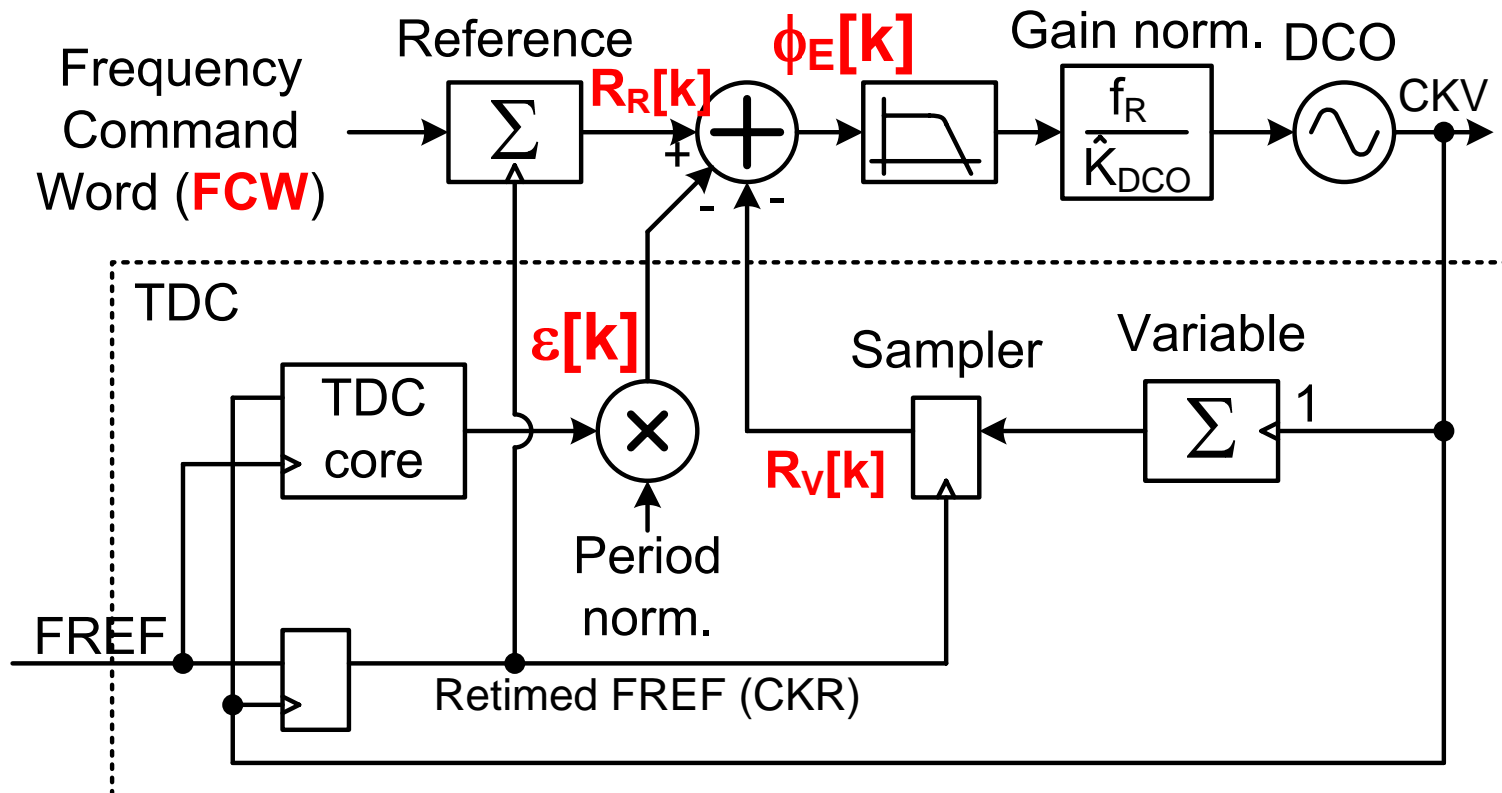
$$\phi_E = R_R[k] - (R_V[k] + \varepsilon[k])$$





Modulo Arithmetic

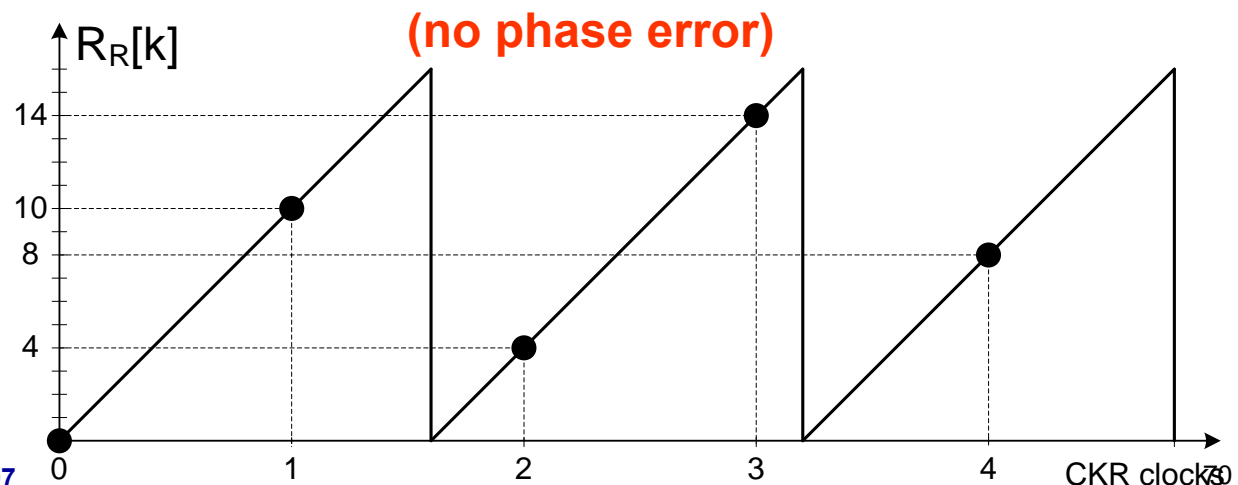  - Theoretically, reference θ_R and variable θ_V phases grow without bound
- θ_R and θ_V implemented in modulo arithmetic to limit wordlength: $W_I = 8$, $W_F = 15$



Reference Phase Retiming

 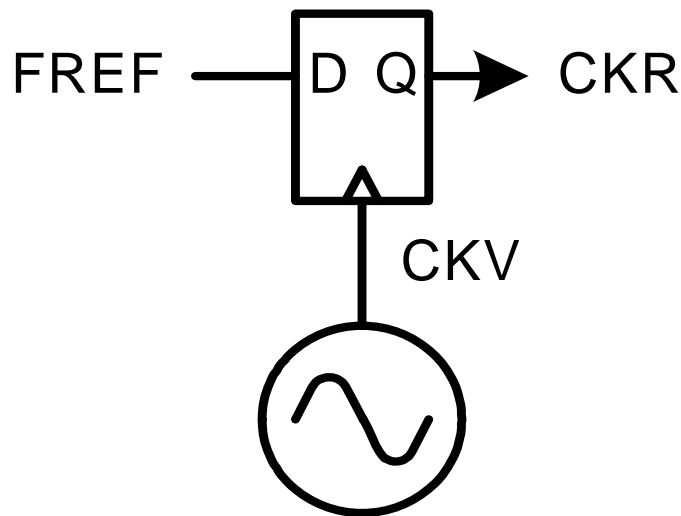
- DCO clock and FREF domains are not entirely synchronous despite being in phase lock
- Variable and reference phases cannot be compared in hardware: metastability!
- Solution: Oversampling FREF by CKV and using the resulting CKR



Frequency Response of 2nd-order PLL

- IIR filter turned off
- Type-II second-order PLL loop
- “knobs” α, ρ
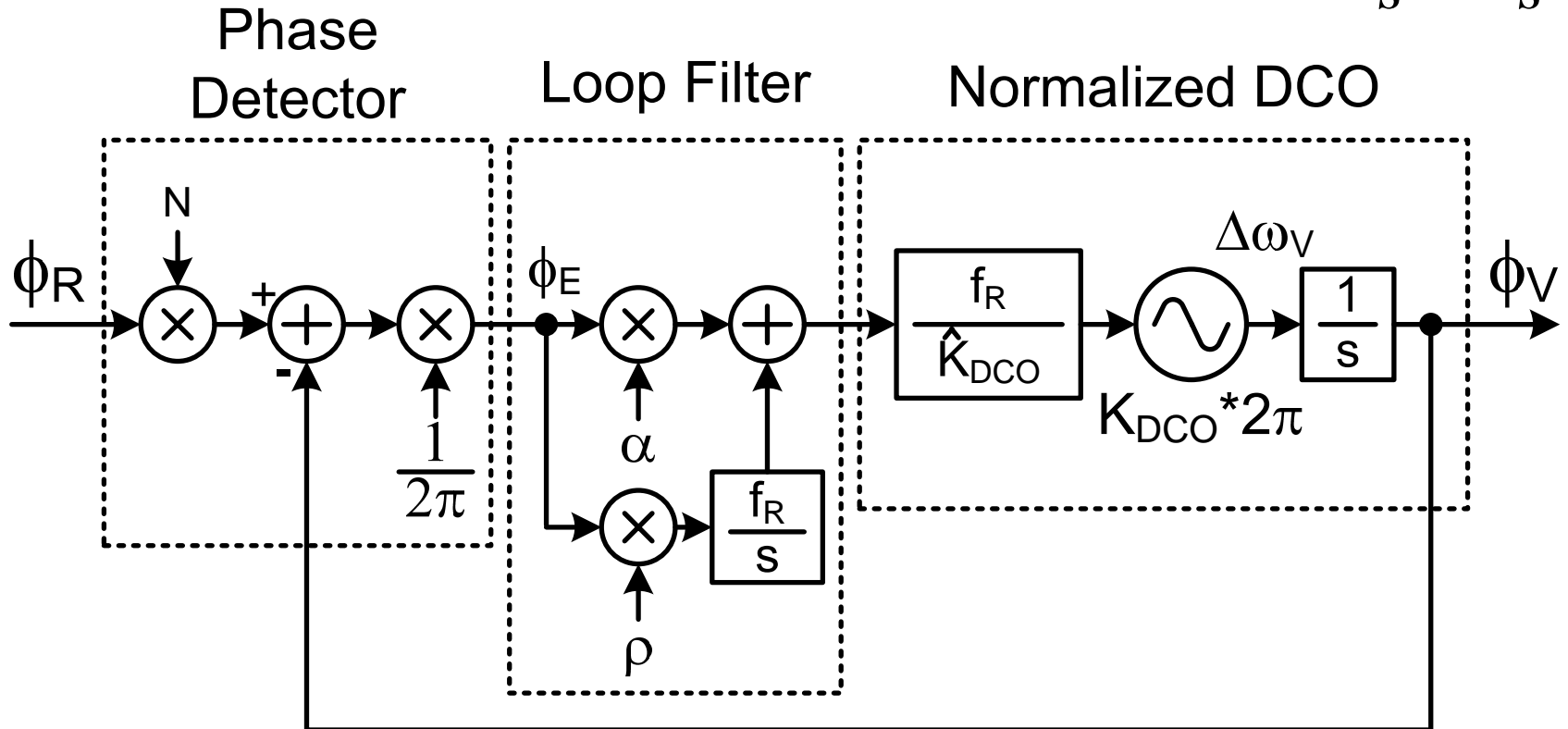
$$H_{ol}(s) = \left(\alpha + \frac{\rho f_R}{s} \right) \frac{f_R}{s}$$



2nd-order PLL: Closed-Loop Response

- Closed-loop transfer function

$$H_{cl}(s) = N \frac{\alpha f_R s + \rho f_R^2}{s^2 + \alpha f_R s + \rho f_R^2}$$

- Canonical two-pole control system

$$H_{cl}(s) = N \frac{2\xi\omega_n s + \omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

Natural frequency

$$\omega_n = \sqrt{\rho} f_R$$


Damping factor

$$\xi = \frac{1}{2} \frac{\alpha}{\sqrt{\rho}}$$

FREF/TDC Transfer Function


Type-II second-order PLL loop; Reference phase; $N = 1$

- Type-II 2nd order PLL
- Weak filtering

 

DCO Transfer Function

 
- Type-II 2nd order PLL
- 20 dB/dec – Type-I
- 40 dB/dec – Type-II
- 1/f noise attenuation



z-Domain Model of the ADPLL



- “knobs” $\alpha, \rho, \lambda_{1-4}$
- Type-I or Type-II PLL loop
- 1st through 6th order
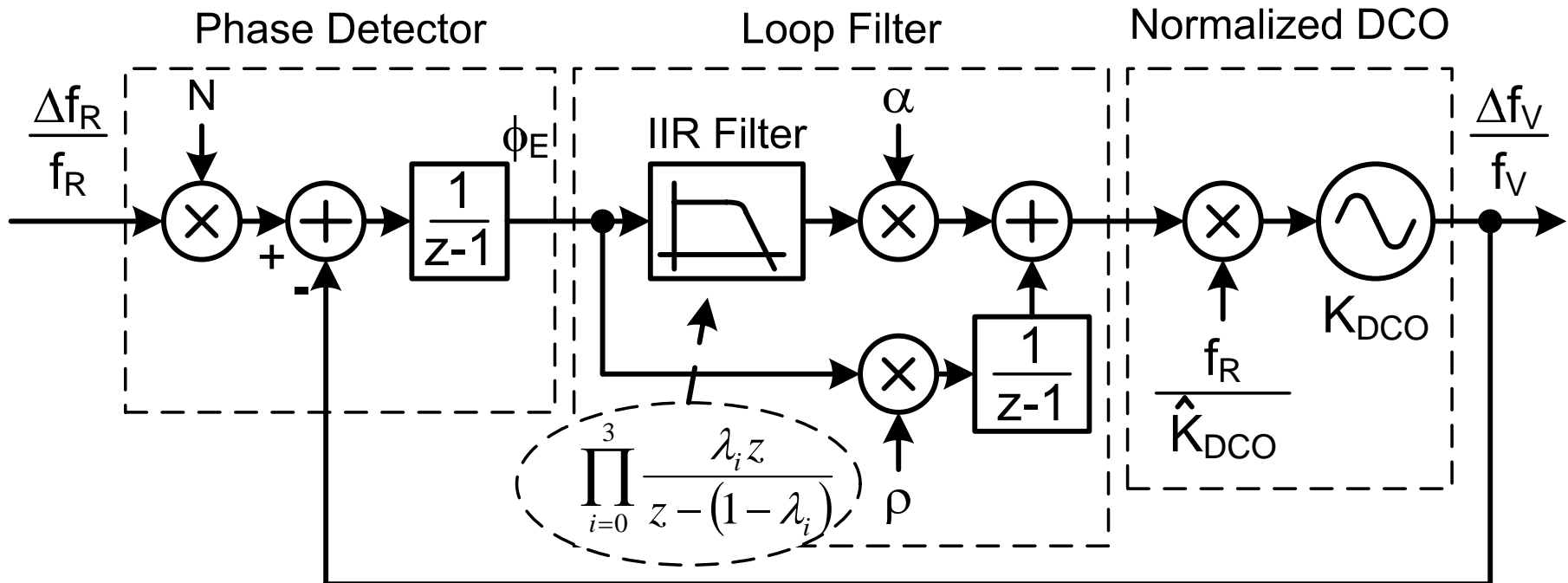
$$H_{ol}(s) = \left[\alpha \cdot H_{iir}(s) + \frac{\rho \cdot f_R}{s} \right] \frac{f_R}{s}$$




ADPLL Transfer Function

  - Type-II 6th-order PLL
- Settings: $\alpha = 2^{-7}$, $\rho = 2^{-15}$, $\lambda = 2^{-[3\ 3\ 3\ 4]}$
- Provides 33 dB of attenuation at 400 kHz
- Provides 40 dB/dec filtering of 1/f DCO noise




Measured Carrier Phase Noise

 - 824.2 MHz carrier
- 26 MHz FREF
- -92...-95 dBc/Hz in-band phase noise
- 0.5 deg rms phase noise
 - Spec: 5 deg
- -122 dBc/Hz @ 400 kHz




ADPLL with Zero Phase Restart

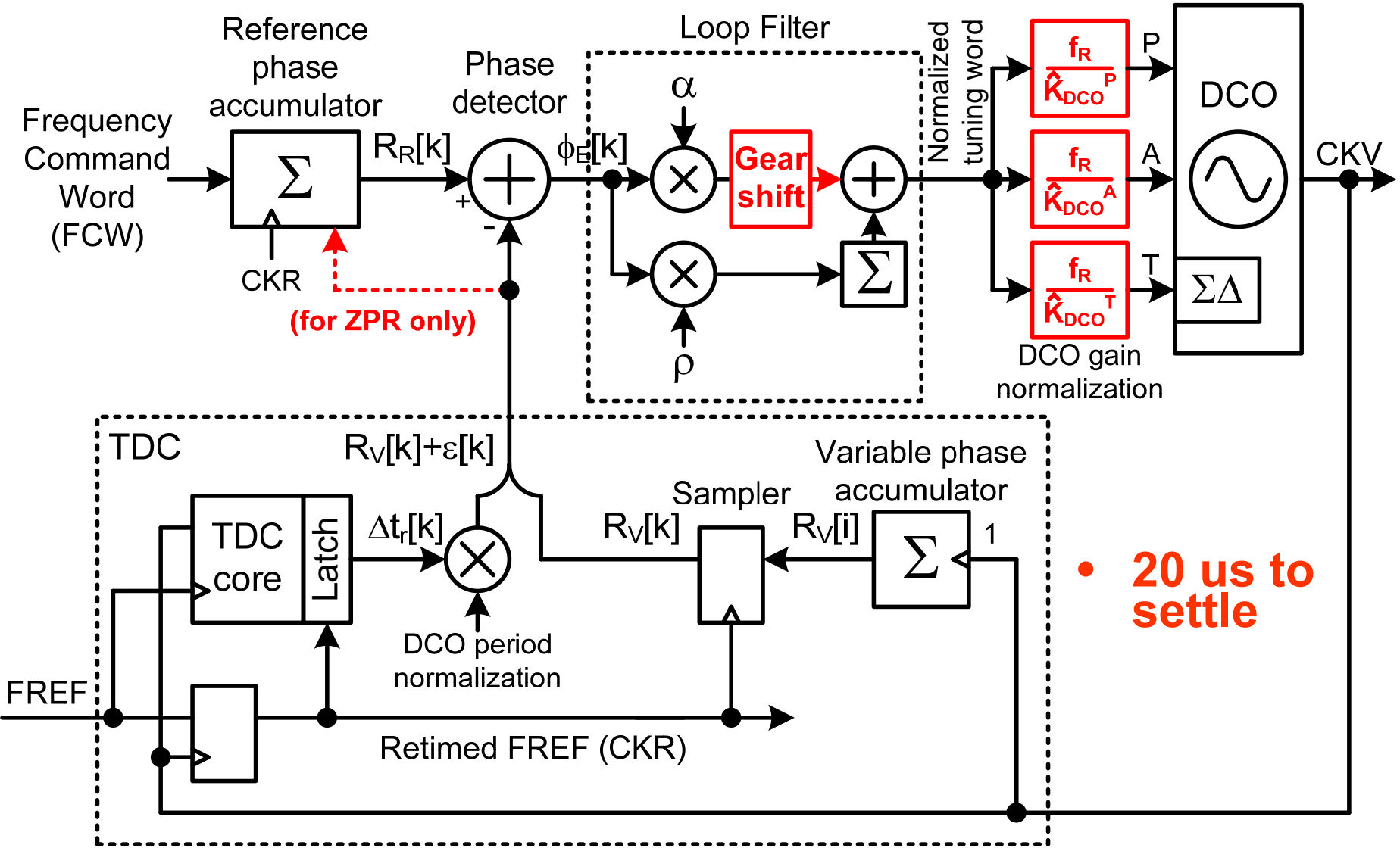

Gear Shifting of PLL Bandwidth


- Executed in tracking mode after the acquisition is completed
- Normalized tuning word continuity before and after the event
- Guarantees no frequency perturbation of the oscillator
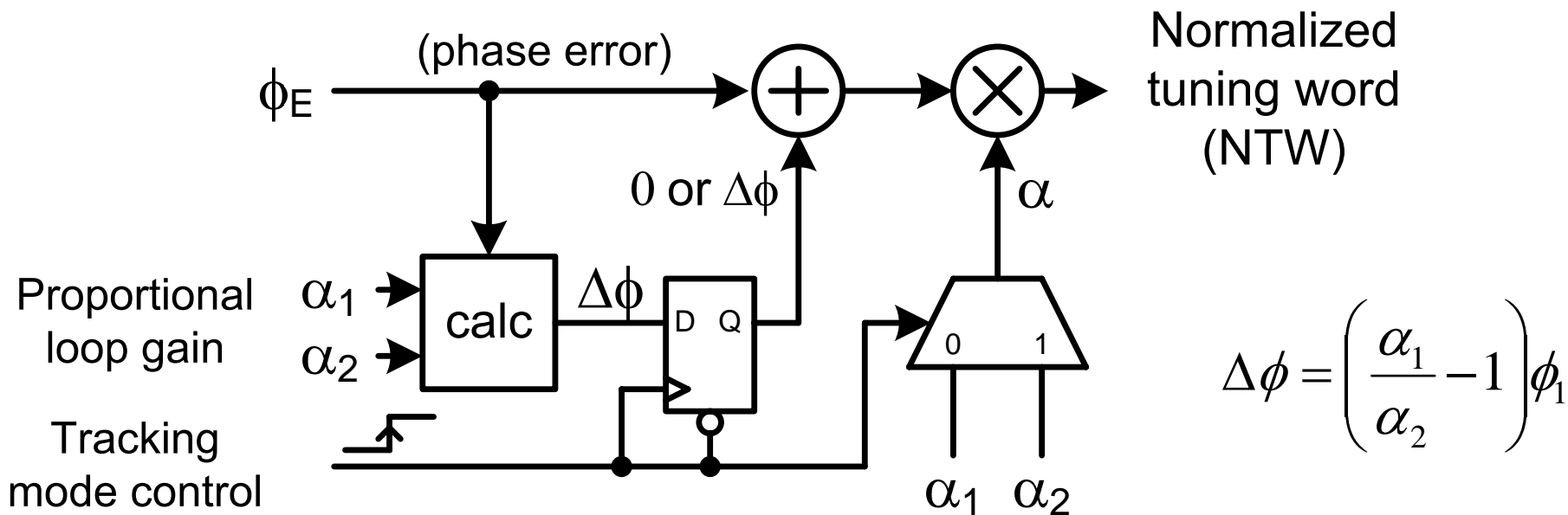
$$\alpha_1 \cdot \phi_1 = \alpha_2 \cdot (\phi_1 + \Delta\phi)$$




PLL Modes: Close-In Phase Noise

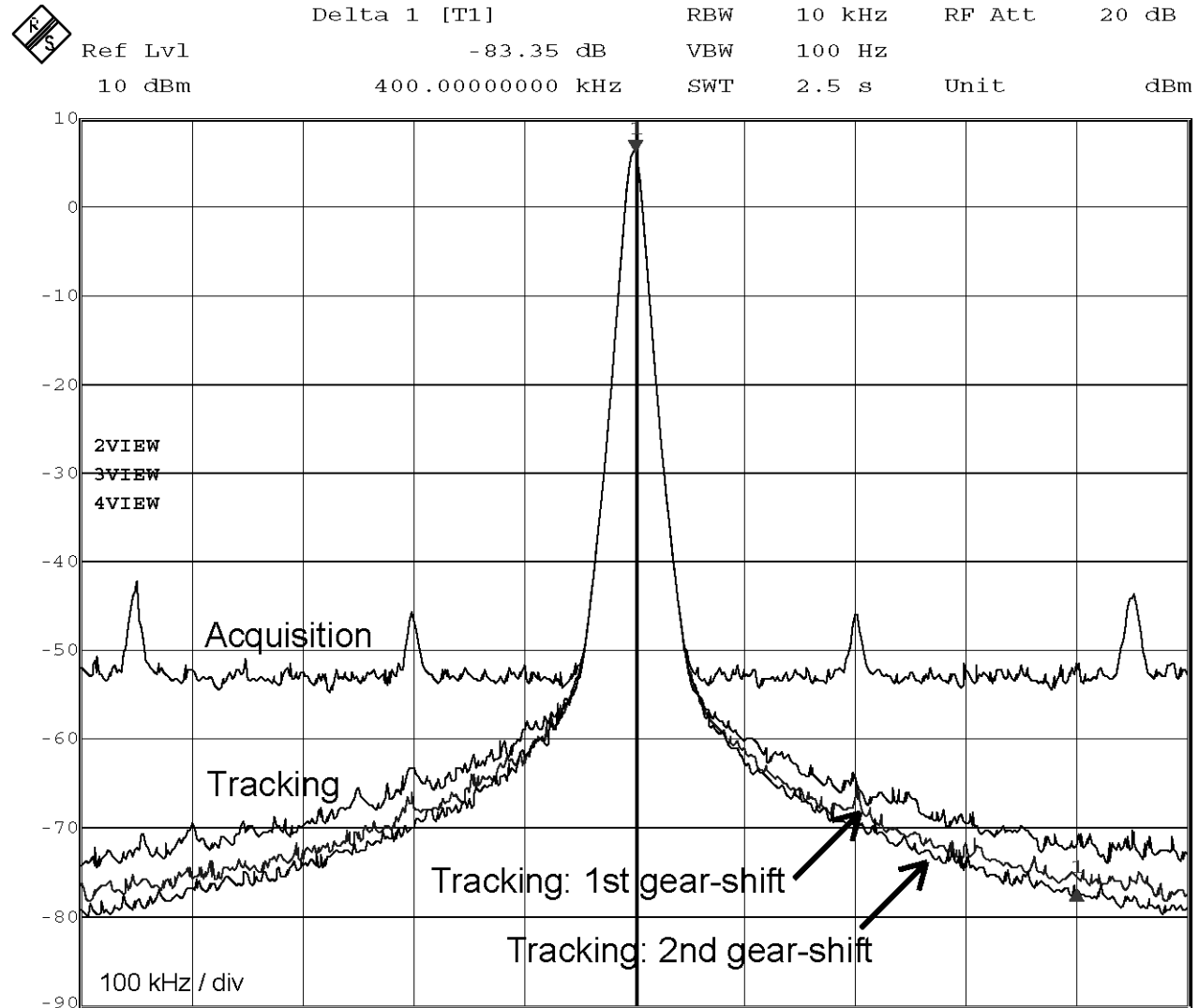- Gradual phase noise improvement with narrowing down the loop bandwidth
- Little improvement after second gear shift when the DCO noise predominates



Measured Trajectory during Settling

- Gear shift at 23 us

 

Digitally-Controlled Oscillator (DCO)


$\Sigma\Delta$ Modulator

Time-to-Digital Converter (TDC)

Digital Loop Filter (LF)


All-Digital PLL (ADPLL)

ADPLL Wideband Frequency Modulation

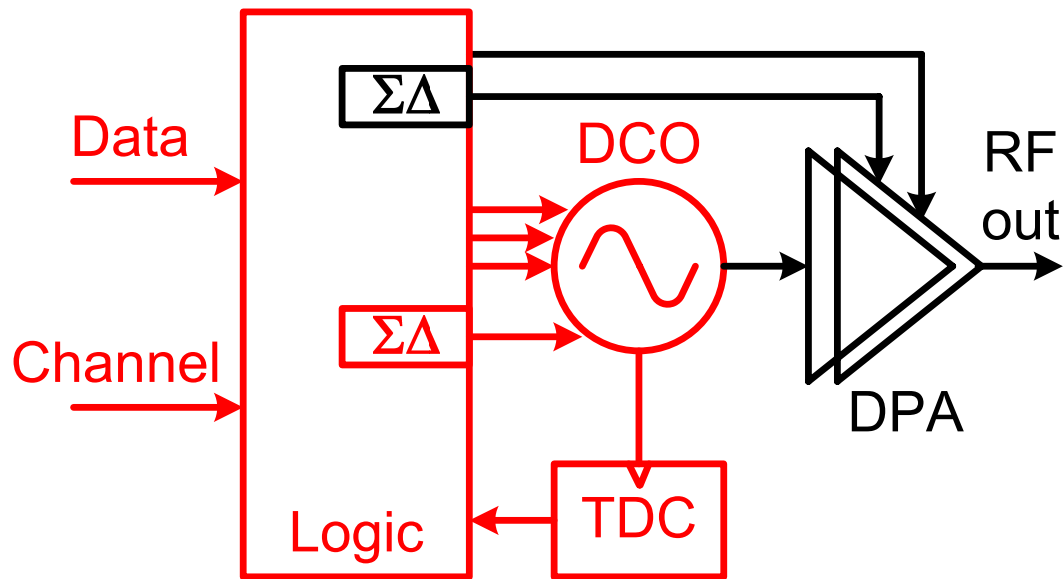


ADPLL with Wideband Modulation

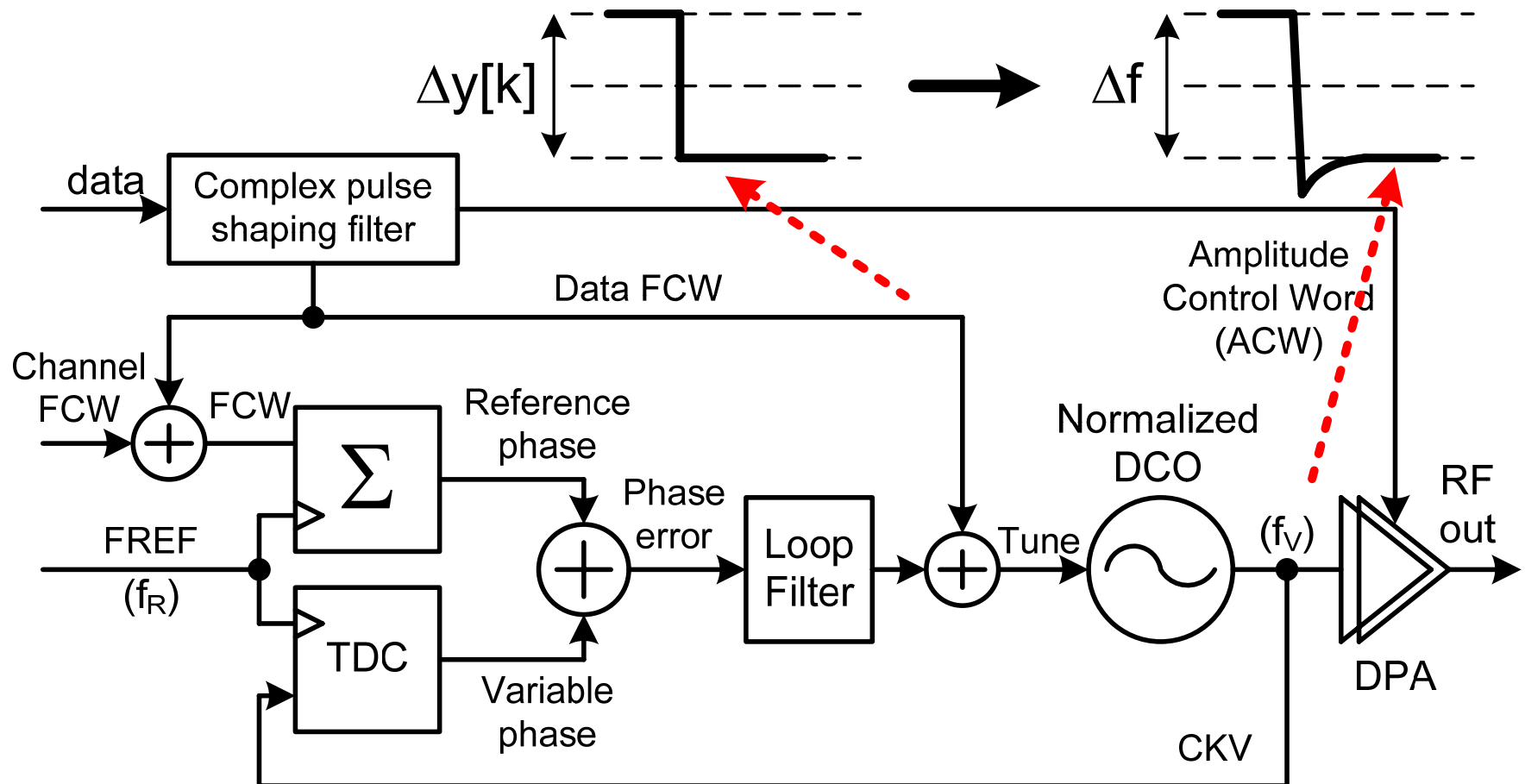- Two-point frequency modulation
 - Direct feedforward path – $y[k]$ directly drives the DCO
 - Compensating path – $y[k]$ added to the channel FCW



DCO Gain Estimation

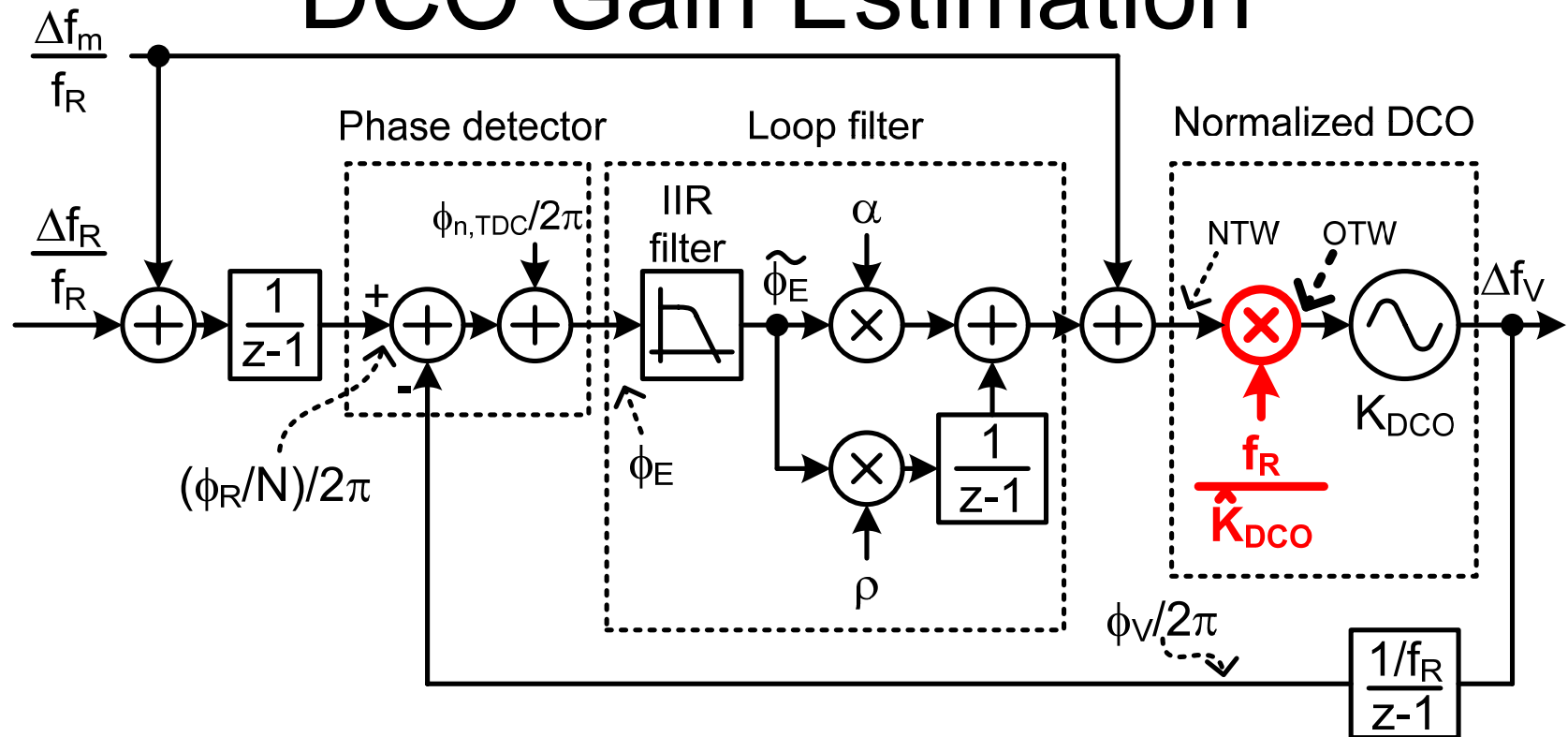


- Estimation of RF oscillator gain is critical in low-cost high-volume transceivers
 - RX: sets the loop bandwidth
 - TX: sets transfer function of the direct frequency modulation path
 - Tolerated gain estimation error from less than 1% (CDMA) to several % (GSM, Bluetooth)


K_{DCO} Error Effect on GSM Modulation

Effect of KDCO estimation error on ADPLL modulation

 - Y-axis: RMS phase error [deg]
- X-axis: KDCO estimation error [%]
- KDCO estimation error of several % allowed




Just-in-time DCO Gain Estimation

 

- Forces Δf through the PLL
- Measures steady-state ΔOTW
- Could be repeated a few times for better estimation



Measured GSM Output Spectrum

 - Meets GSM spec
 - 8 dB margin @ 400 kHz
- Phase error
 - 1° rms (5° spec)
 - 3° peak (20° spec)




All-Digital Polar TX Architecture

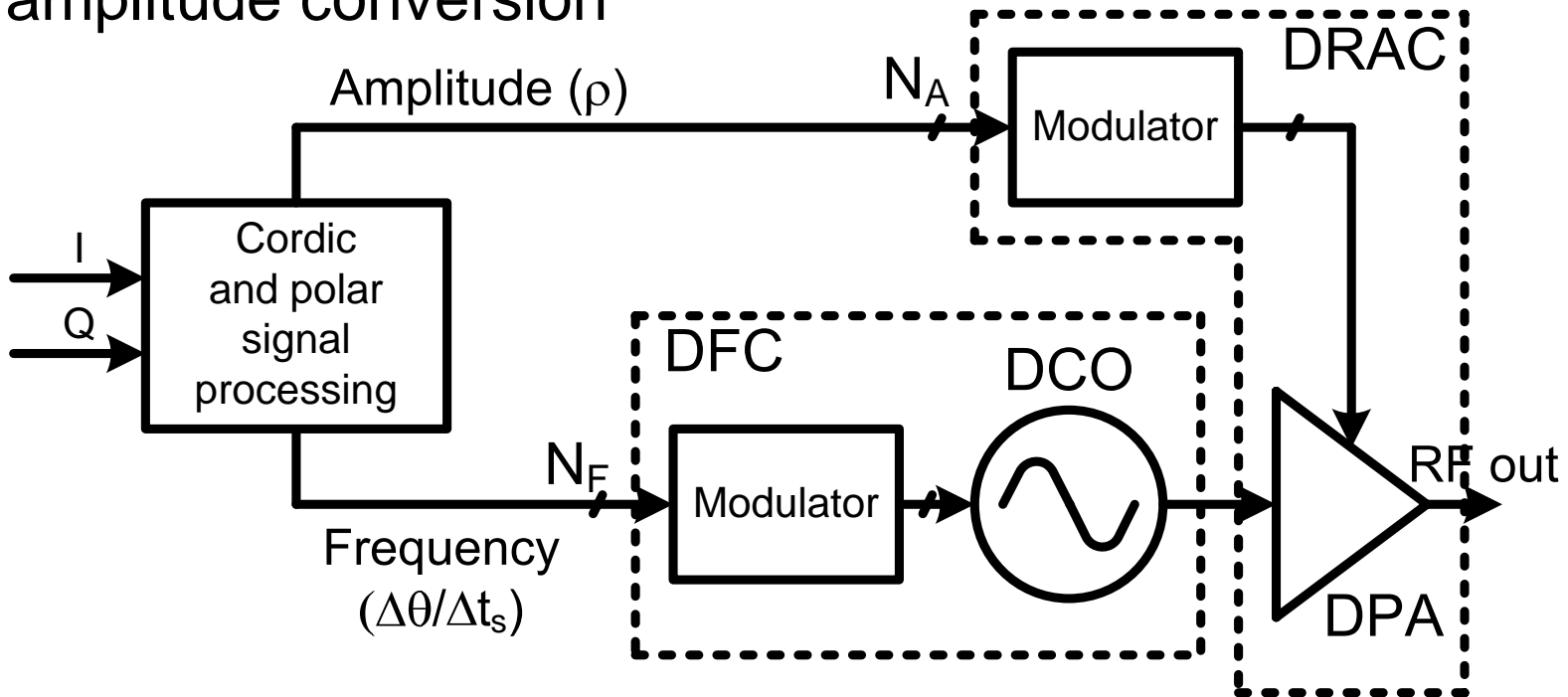 - Dense logic for digital signal processing
- DCO for digital-to-frequency conversion
- DPA for digital-to-RF-amplitude conversion




Digitally-Controlled Power Amplifier

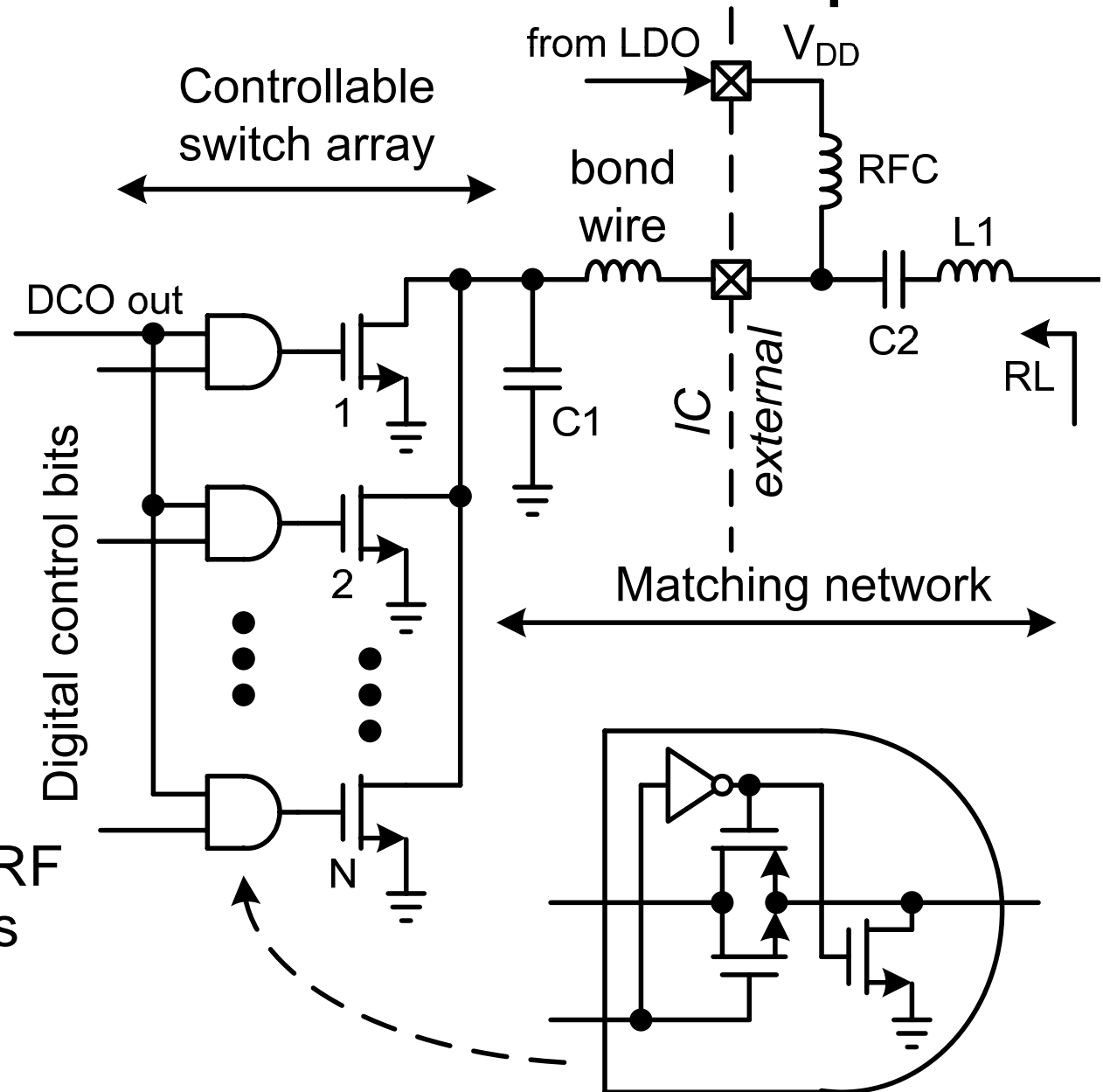
- Array of unit-weighted MOS switches
- Each switch contributes a conductance
- Near class-E operation
- Fine amplitude through $\Sigma\Delta$ modulation
- The DPA can be thought of as an RF DAC, where “A” is RF “amplitude”



Measured EDGE Modulation

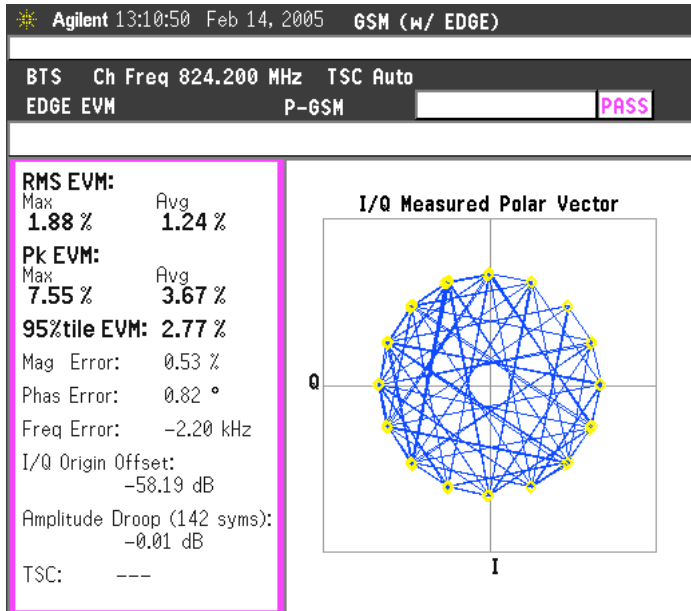


 
- Meets the spectral mask with 10 dB margin



 
 
- 1.24% meets the rms EVM spec of 9%
- 3.67% meets the peak EVM spec of 30%

Single-Chip GSM Radio in 90 nm

- 90 nm CMOS
- All-digital PLL
- All-digital TX
- Digitally-intensive RX
- w/o
 - 2-W PA
 - Battery management



Single-Chip GSM Radio in 90 nm

  

Digital

Memory

DRP

RF

Analog

- First single-chip GSM radio
- In volume production
- Logic density of 250 kgates/mm²
- SRAM density of 1 Mbits/mm²

Conclusions

- Survey of RF wireless frequency synthesizers
- Highly-scaled CMOS is extremely unfriendly for RF and analog designs
- Radio architecture must transform voltage-domain circuits into time-domain operation and high-speed digital logic
- All-digital PLL (ADPLL)
 - ADPLL features wideband frequency modulation
- All-digital and digitally-intensive architecture in nanometer CMOS can replace traditional RF circuits
- Performance demonstrated in a commercial single-chip GSM radio

General References

- [1] J. Tierney, C. M. Radar, B. Gold, “A digital frequency synthesizer,” *IEEE Trans. on Audio Electroacoust.*, vol. AU-19, pp. 48–57, Mar 1971.
- [2] F. M. Gardner, “Charge-pump phase-locked loops,” *IEEE Trans. on Communications*, vol. COMM-28, pp. 1849–1858, Nov. 1980.
- [3] A. Kajiwara and M. Nakagawa, “A new PLL frequency synthesizer with high switching speed,” *Trans. on Vehicular Technology*, vol. 41, no. 4, pp. 407–413, Nov 1992.
- [4] T. Riley, M. Copeland, T. Kwasniewski, “Delta-sigma modulation in fractional-N frequency synthesis,” *IEEE Journal of Solid-State Circuits*, vol. 28, no. 5, pp. 553–559, May 1993.
- [5] J. Dunning, G. Garcia, J. Lundberg, E. Nuckolls, “An all-digital phase-locked loop with 50-cycle lock time suitable for high performance microprocessors,” *Journal of Solid-State Circuits*, vol. 30, pp. 412–422, Apr. 1995.

General References

- [6] M. H. Perrott, M. D. Trott, C. G. Sodini, “A modeling approach for S-D fractional-N frequency synthesizers allowing straightforward noise analysis,” *IEEE Journal of Solid-State Circuits*, vol. 37, pp. 1028–1038, Aug. 2002.
- [7] M. H. Perrott, R. T. Rex, and Y. Huang, “Digitally-synthesized loop filter circuit particularly useful for a phase locked loop,” *US patent 6,630,868*, issued Oct. 7, 2003.
- [8] J. Lin, B. Haroun, T. Foo, “A PVT tolerant 0.18MHz to 600MHz self-calibrated digital PLL in 90nm CMOS process,” *Proc. of IEEE Solid-State Circuits Conf.*, sec. 26.10, pp. 488–489, 541, Feb. 2004.
- [9] L. Xiu, “A Novel All Digital Phase Lock Loop with Software Adaptive Filter,” *IEEE Journal of Solid-State Circuits*, vol. 39, no. 3, pp. 476-483, Mar. 2004.
- [10] A. A. Abidi, “RF CMOS comes of age,” *IEEE Journal of Solid-State Circuits*, vol. 39, iss. 4, pp. 549–561, April 2004.
- [11] W. Krenik, D. Buss and P. Rickert, “Cellular handset integration – SIP vs. SOC,” *Proc. of 2004 IEEE Custom IC Conf.*, pp. 63–70, Oct. 2004.

References on ADPLL

- [12] R. B. Staszewski, C.-M. Hung, D. Leipold, et al., “A first multigigahertz digitally controlled oscillator for wireless applications,” *IEEE Trans. on Microwave Theory and Techniques*, vol. 51, no. 11, pp. 2154–2164, Nov. 2003.
- [13] R. B. Staszewski, D. Leipold, K Muhammad, et al., “Digitally controlled oscillator (DCO)-based architecture for RF frequency synthesis in a deep-submicrometer CMOS process,” *IEEE Trans. on Circuits and Systems II*, vol. 50, no. 11, pp. 815–828, Nov. 2003.
- [14] R. B. Staszewski, K. Muhammad, D. Leipold, et al., “All-digital TX frequency synthesizer and discrete-time receiver for Bluetooth radio in 130-nm CMOS,” *IEEE Journal of Solid-State Circuits*, vol. 39, iss. 12, pp. 2278–2291, Dec. 2004.
- [15] R. B. Staszewski and P. T. Balsara, “Phase-domain all-digital phase-locked loop,” *IEEE Trans. on Circuits and Systems II*, vol. 52, no. 3, pp. 159–163, Mar. 2005.

References on ADPLL

- [16] R. B. Staszewski, C. Fernando, and P. T. Balsara, “Event-driven simulation and modeling of phase noise of an RF oscillator,” *IEEE Trans. on Circuits and Systems I*, vol. 52, no. 4, pp. 723–733, Apr. 2005.
- [17] R. B. Staszewski, C.-M. Hung, N. Barton, M.-C. Lee, and D. Leipold, “A digitally-controlled oscillator in a 90 nm digital CMOS process for mobile phones,” *IEEE Journal of Solid-State Circuits*, vol. 40, no. 11, pp. 2203–2211, Nov. 2005.
- [18] R. B. Staszewski, J. Wallberg, S. Rezeq, et al., “All-digital PLL and transmitter for mobile phones,” *IEEE Journal of Solid-State Circuits*, vol. 40, iss. 12, pp. 2469–2482, Dec. 2005.
- [19] R. B. Staszewski, S. Vemulapalli, P. Vallur, J. Wallberg, and P. T. Balsara, “1.3 V 20 ps time-to-digital converter for frequency synthesis in 90-nm CMOS,” *IEEE Trans. on Circuits and Systems II*, vol. 53, no. 3, pp. 220–224, Mar. 2006.
- [20] R. B. Staszewski and P. T. Balsara, “All-Digital Frequency Synthesizer in Deep-Submicron CMOS,” New Jersey: John Wiley & Sons, 2006.