

Direct RF Sampling for Digital Radio Processing: Principles and Methods

Khurram Muhammad

Wireless Terminal Business Unit

Texas Instruments, Dallas, TX

Outline


- Motivation
- Deep-submicron low-complexity design
 - Direct rf sampling
 - Discrete-time signal processing receiver architecture
 - Digital Backend
- Analog impairments
- Bluetooth Receiver example (sens: -83dBm)
- GSM/GPRS Receiver example (sens: -110dBm)
- Conclusion

Motivation

- Low-cost
 - Base digital deep-submicron CMOS process
 - Low-power
 - Amenable to migration to newer processes
 - Excellent performance; marketing reasons!
 - Fully integrated
 - Transceiver + Digital BB + Memory + Power Management + RFBIST
 - Analog/RF functions like important “guests” on application centric solutions
 - very large RAM
 - Analog/rf typically occupy < 5% area
 - Built-in calibration mechanisms


I. Direct RF Sampling

Receiver Architecture Example

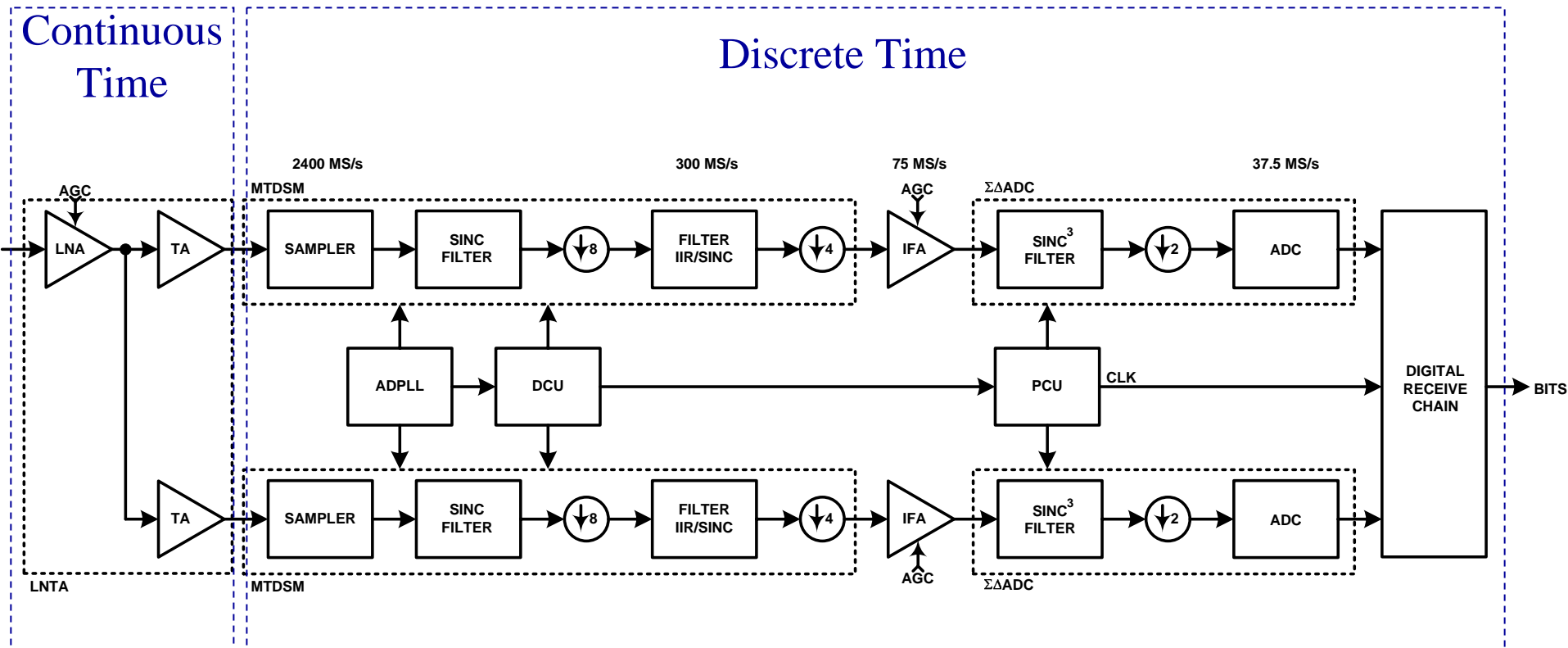


Source: K. Muhammad *et. al.*, "A Discrete-Time Bluetooth Receiver in a 0.13 μ m Digital CMOS Process," paper 15.1, ISSCC 2004.

Discrete Time Receiver

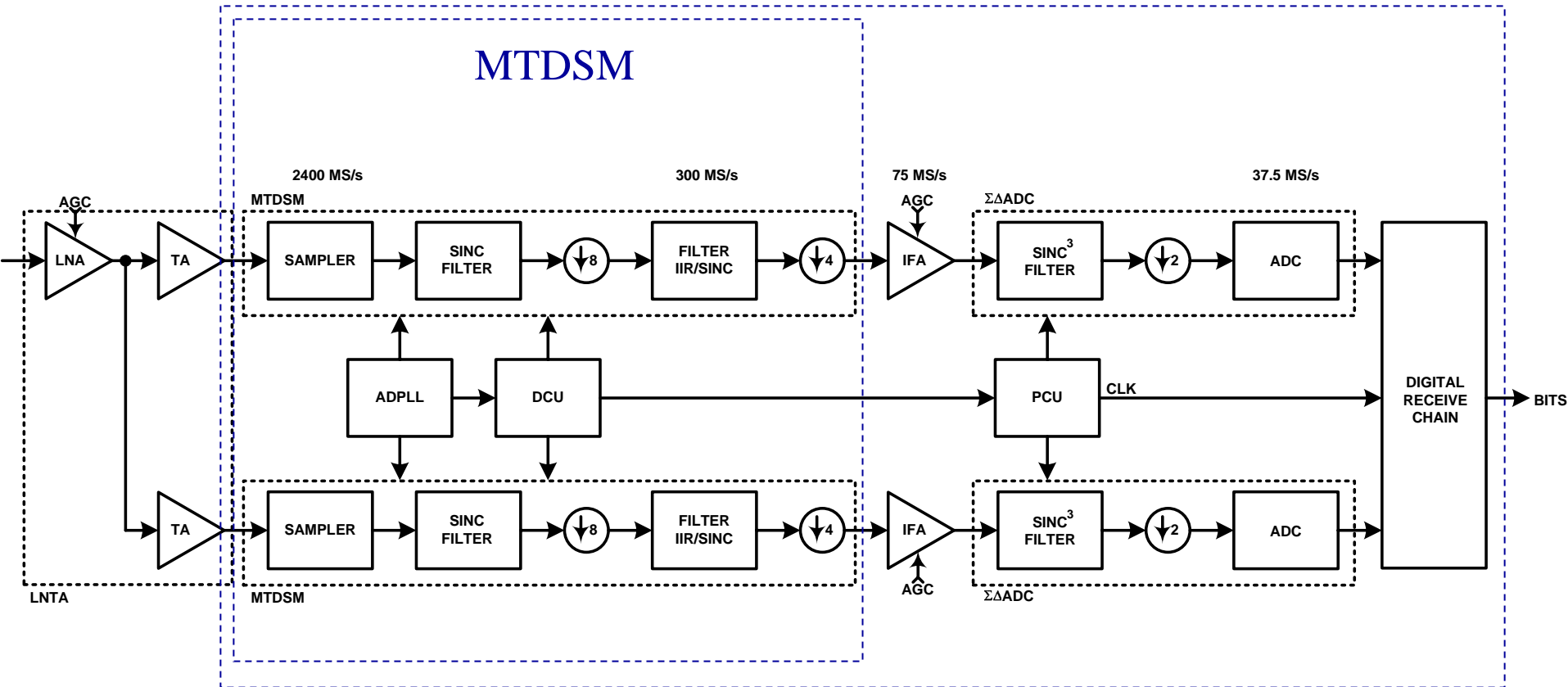

MTDSM: Multi-tap Direct Sampling Mixer

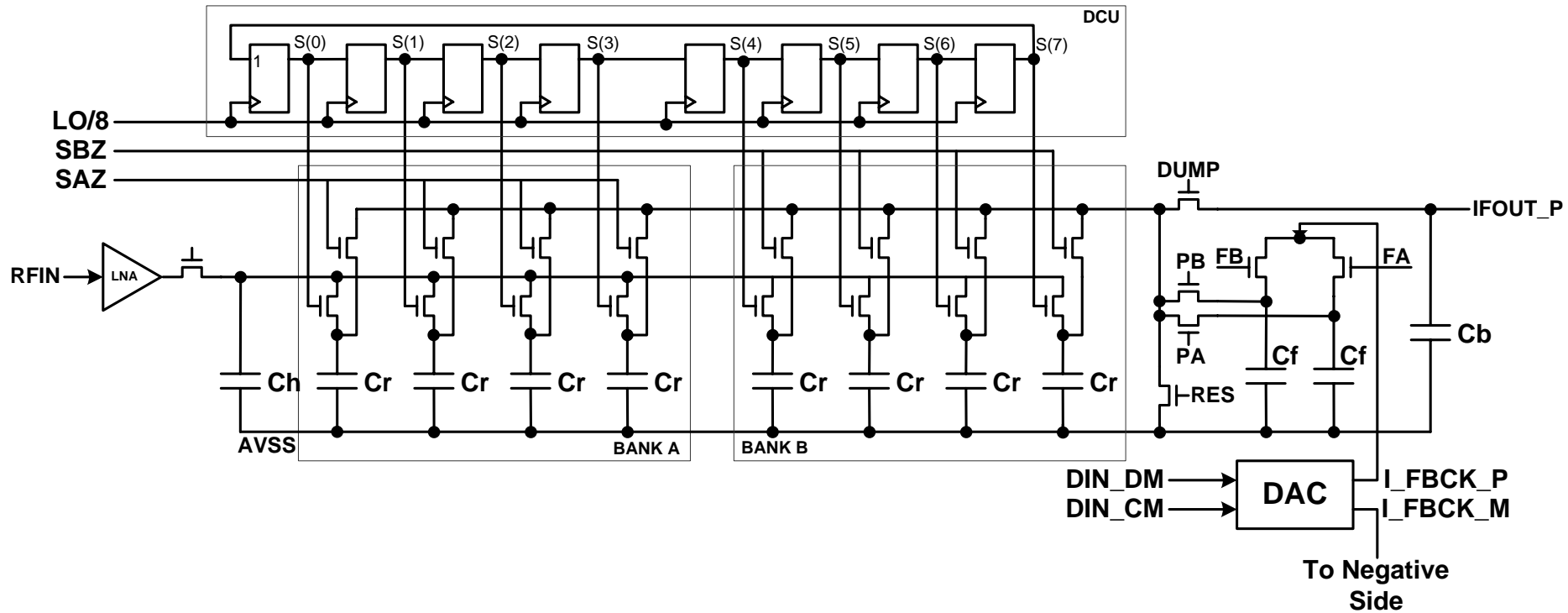


MTDSM Sub-Blocks

Mix & Sample

Readout

Charge

 



Voltage gain over single RF half cycle:

$$G_{v,RF} = \frac{1}{\pi} \cdot \frac{1}{f_0} \cdot \frac{g_m}{C_s}$$

TEMPORAL AVERAGING SINC FILTER

$$w_i = \sum_{l=0}^{N-1} u_{i-l}$$


PREPARING FOR PRECHARGE

 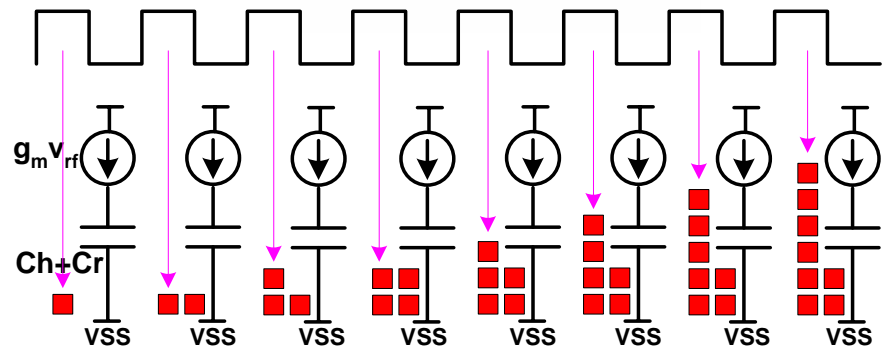

IIR Filtering

Readout


Charge

 

$$s_j = a_1 s_{j-1} + w_j$$


$$x_j = (1 - a_1) s_{j-1}$$

$$a_1 = \frac{C_H}{C_H + C_R}$$

 


$$f_{c1} = \frac{1}{2\pi N} \frac{f_0}{(1 - a_1)} = \frac{1}{2\pi N} \frac{f_0}{C_H + C_R} C_R$$

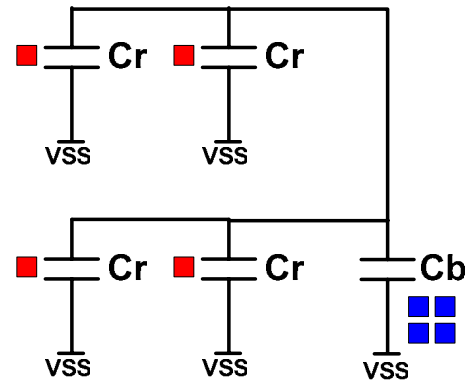SPATIAL AVERAGING
SINC FILTER
+ 1-POLE IIR FILTER



PREPARING
FOR
PRECHARGE

 

Combined Response


 




Fig. 5. Transfer function of the temporal moving average with a decimation of 8 and the IIR filter operating at RF/8 rate. The solid line is the composite transfer of both filters.

Ref: K.Muhammad *et. al*, "Direct RF sampling mixer with recursive filtering in charge domain," ISCAS 2004

Offset and CM Control

 

PRECHARGE

  


- No dc current
- charge packets diverted from plus to minus or vice versa under digital control

 II. Digital Controls


Offsets, Common Mode

- LO leakage and dc offset
- 1/f noise
 - No continuous current flow






Programmable filtering

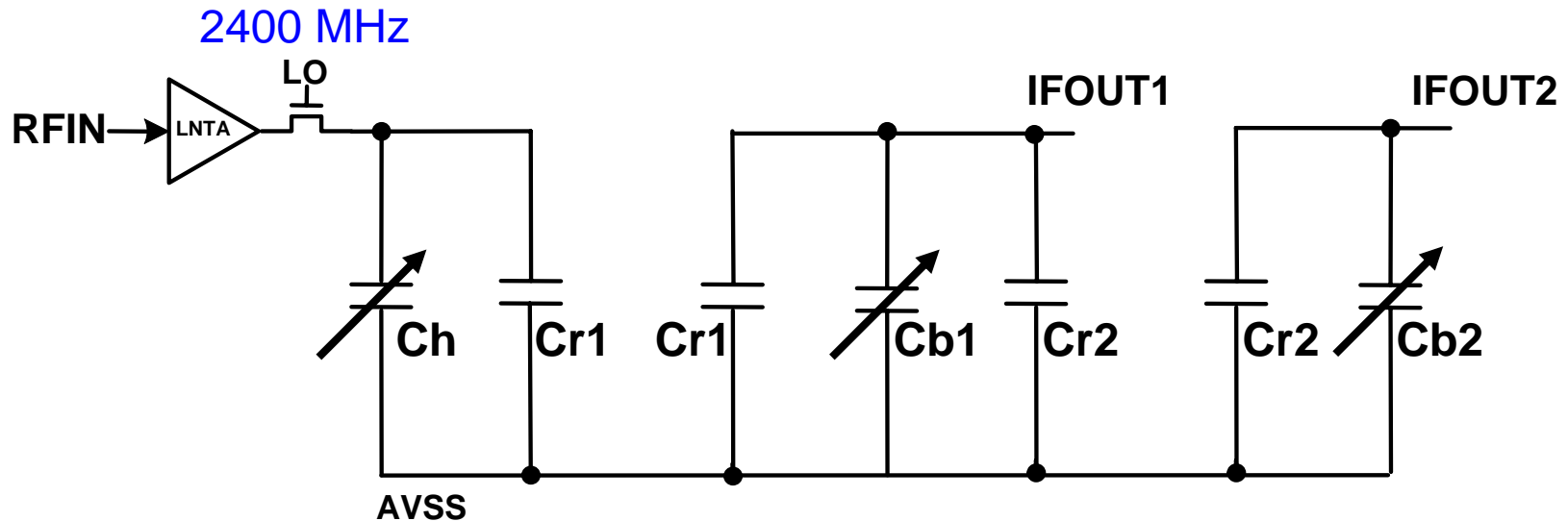- Corner frequency
- Order
- Rotation rate






III. Operation

Phase 1

  
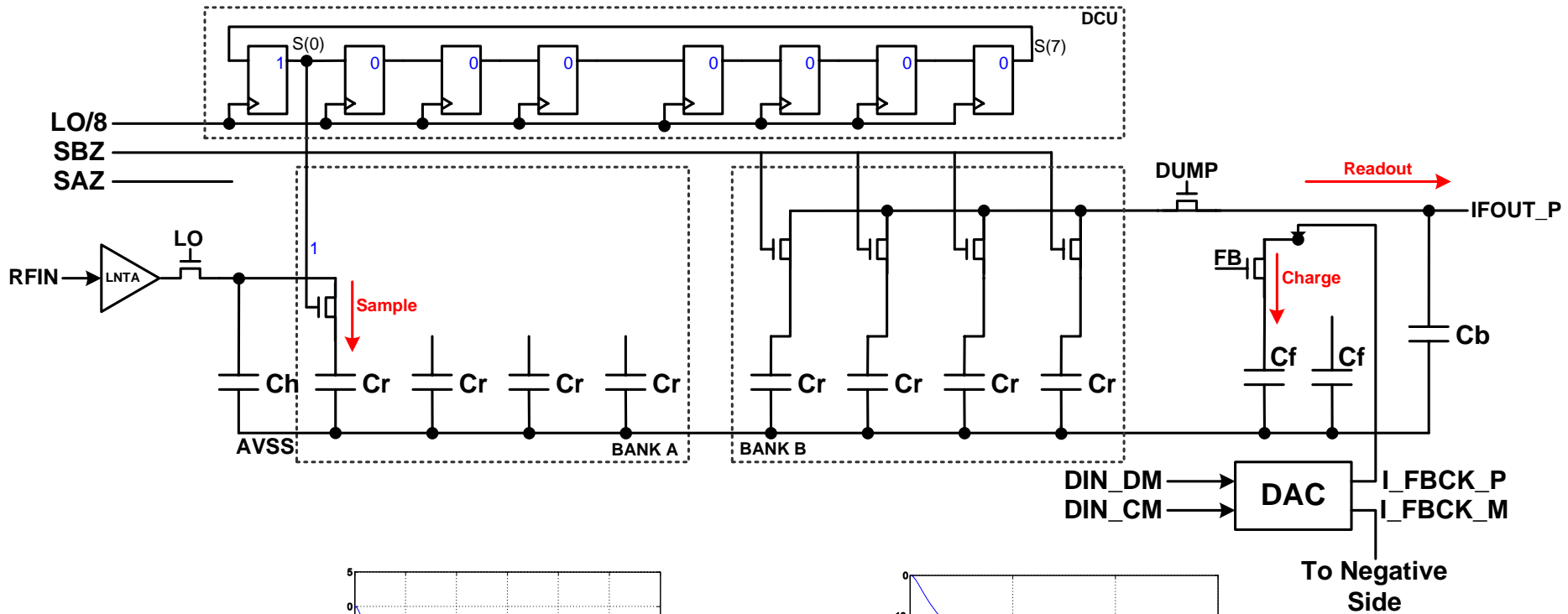


Phase 2

  
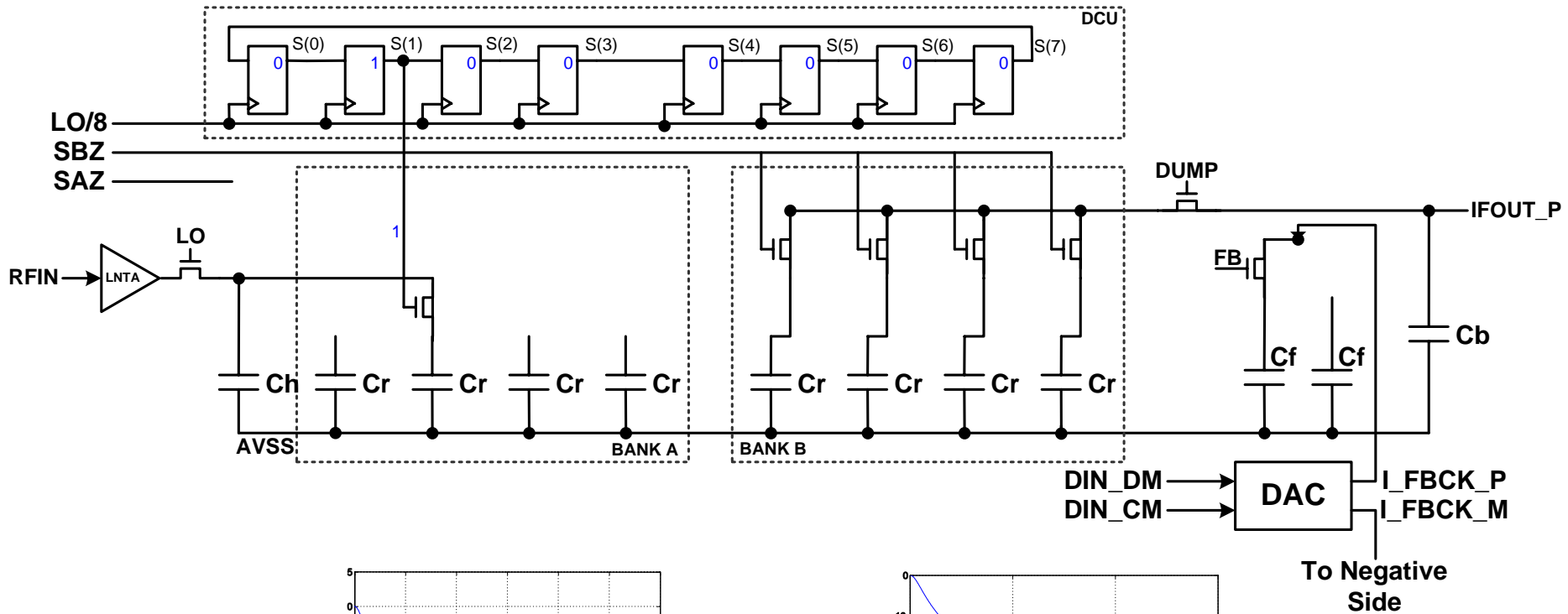


To Negative Side




Phase 3

 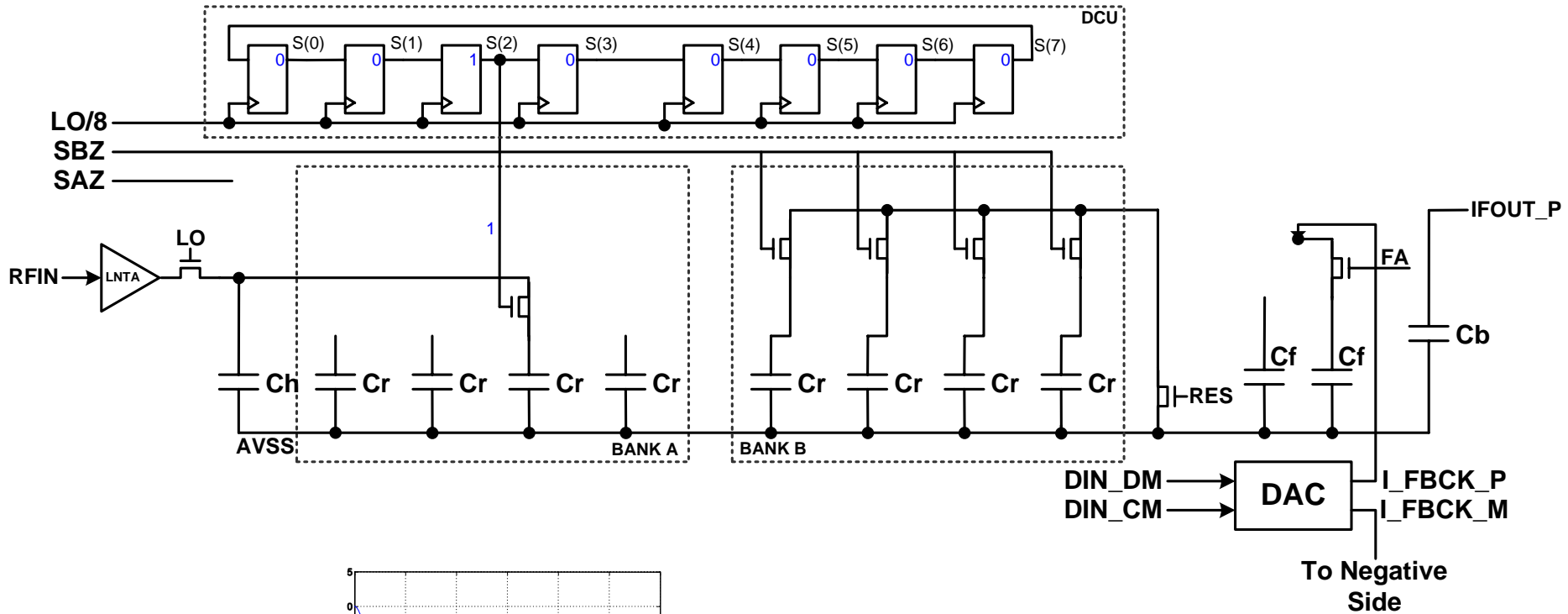




Phase 4

 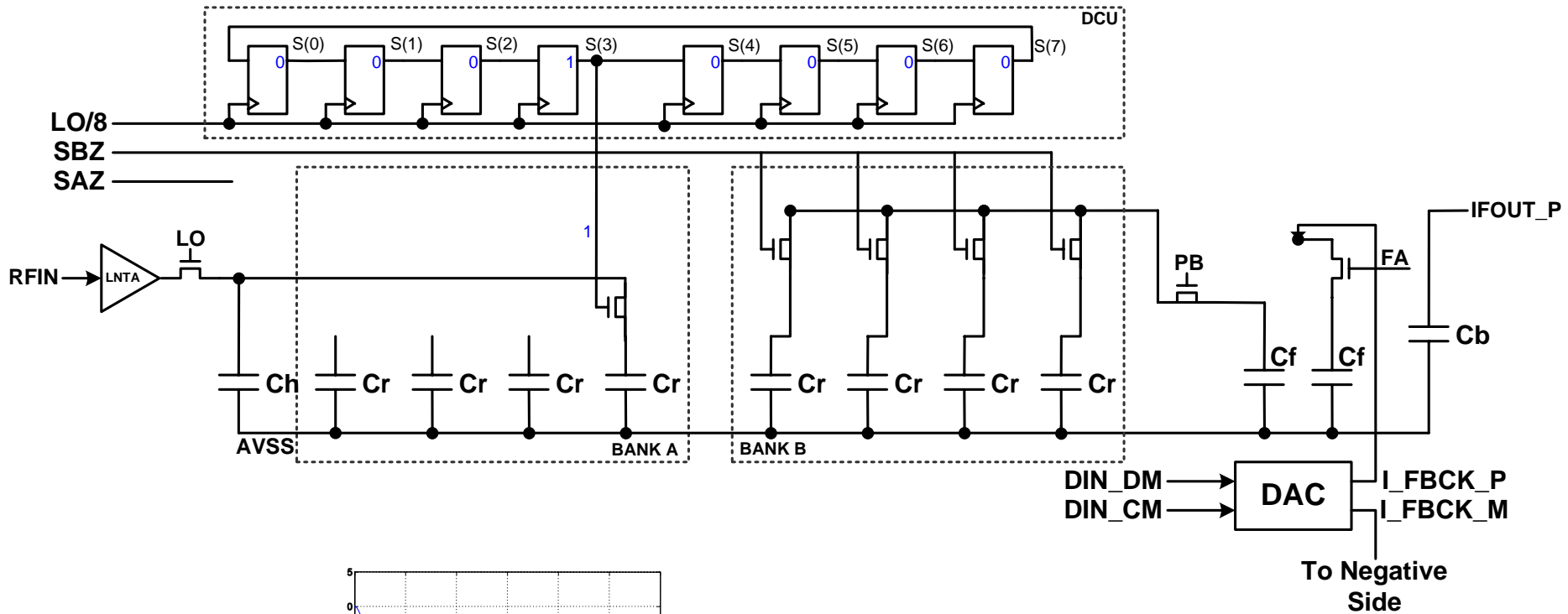



Phase 5

  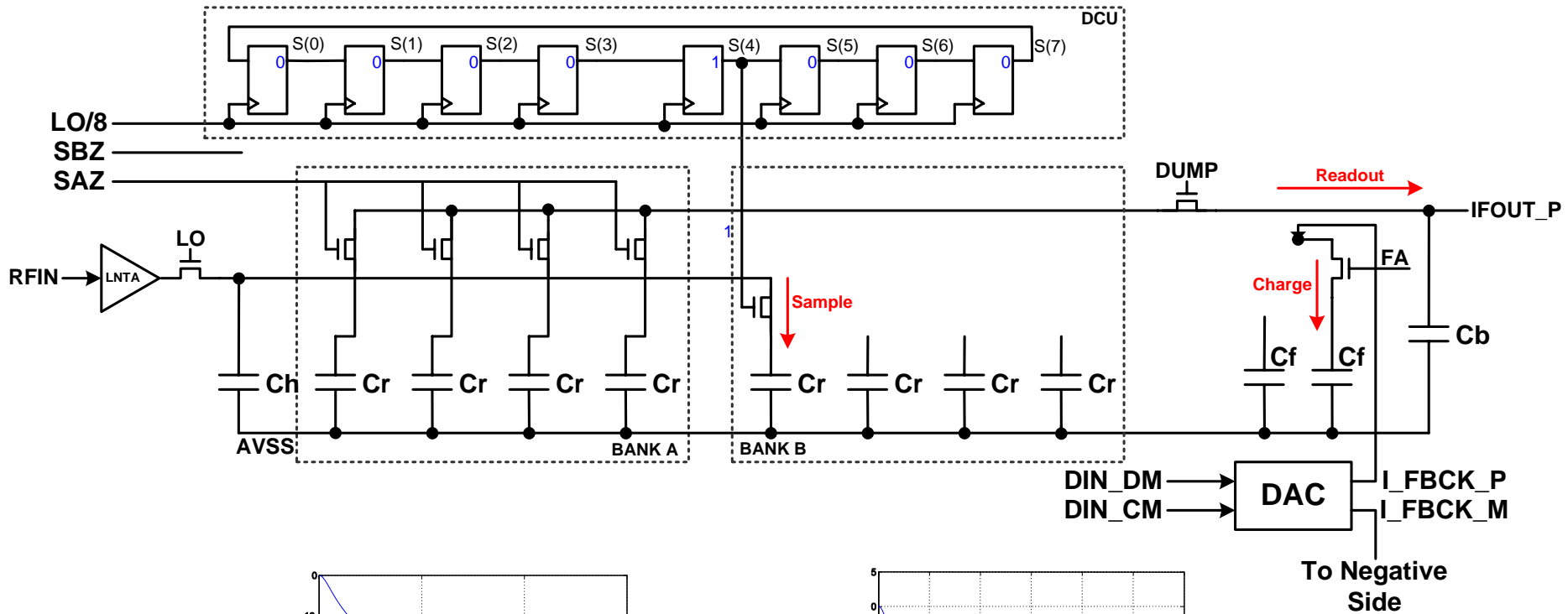



Phase 6

  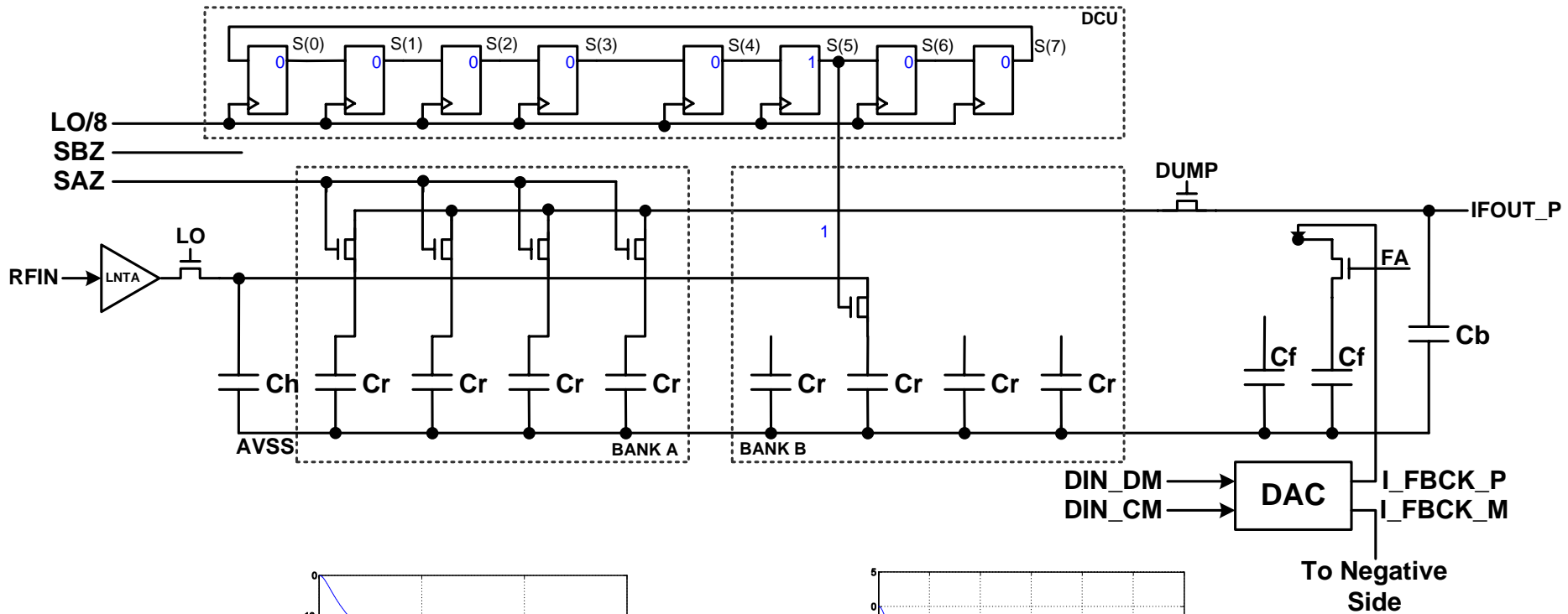


Phase 7

 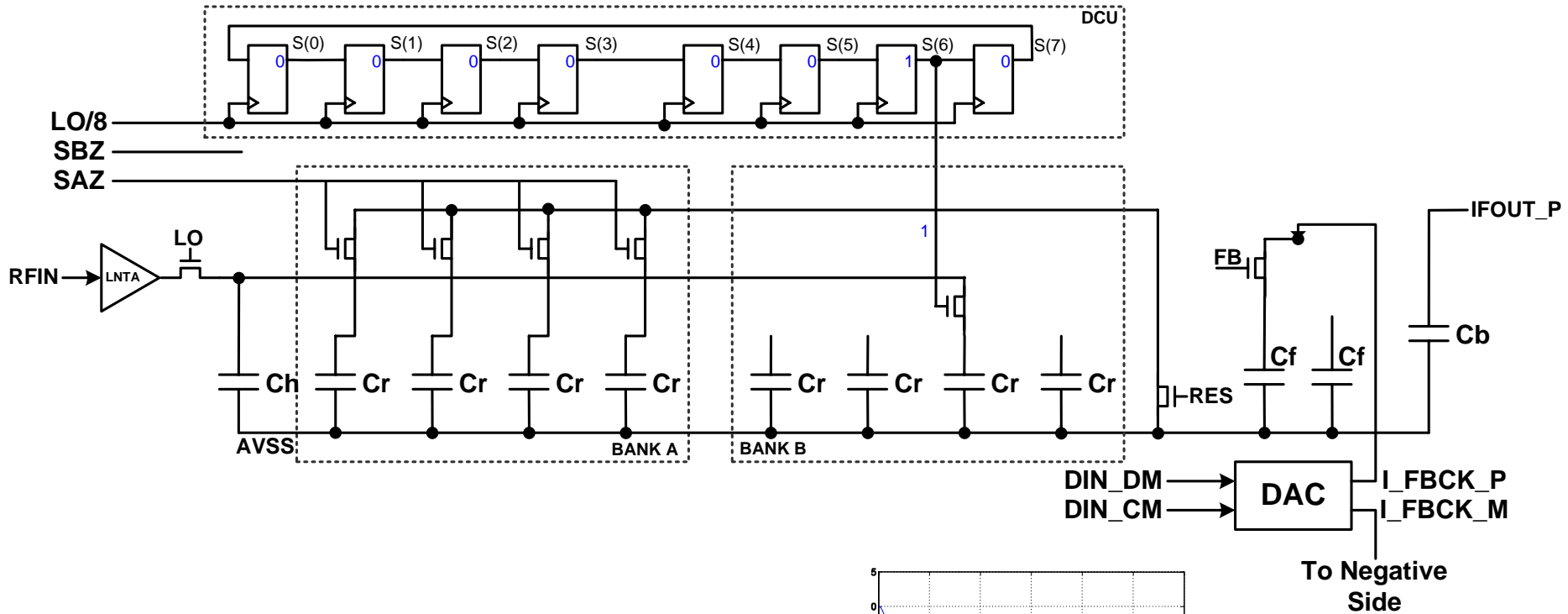


Phase 8

 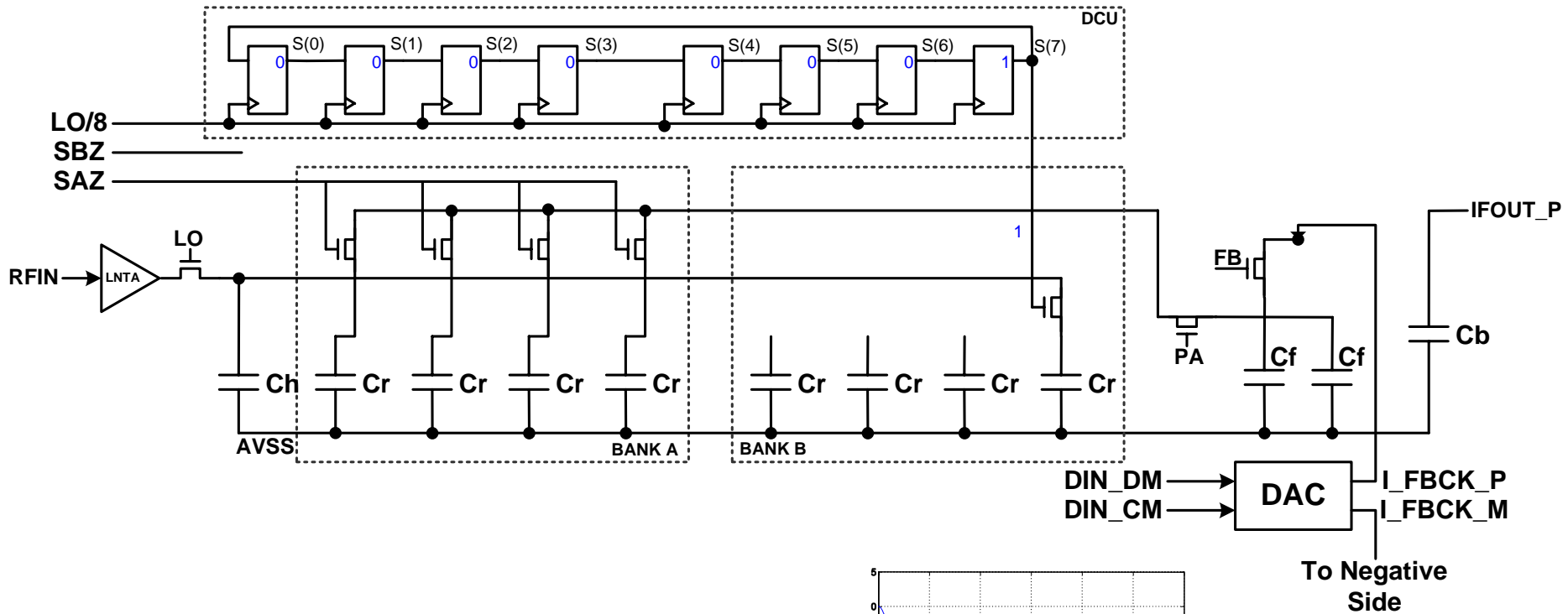


MTDSM Sinc Response

 


Digital Receiver Backend

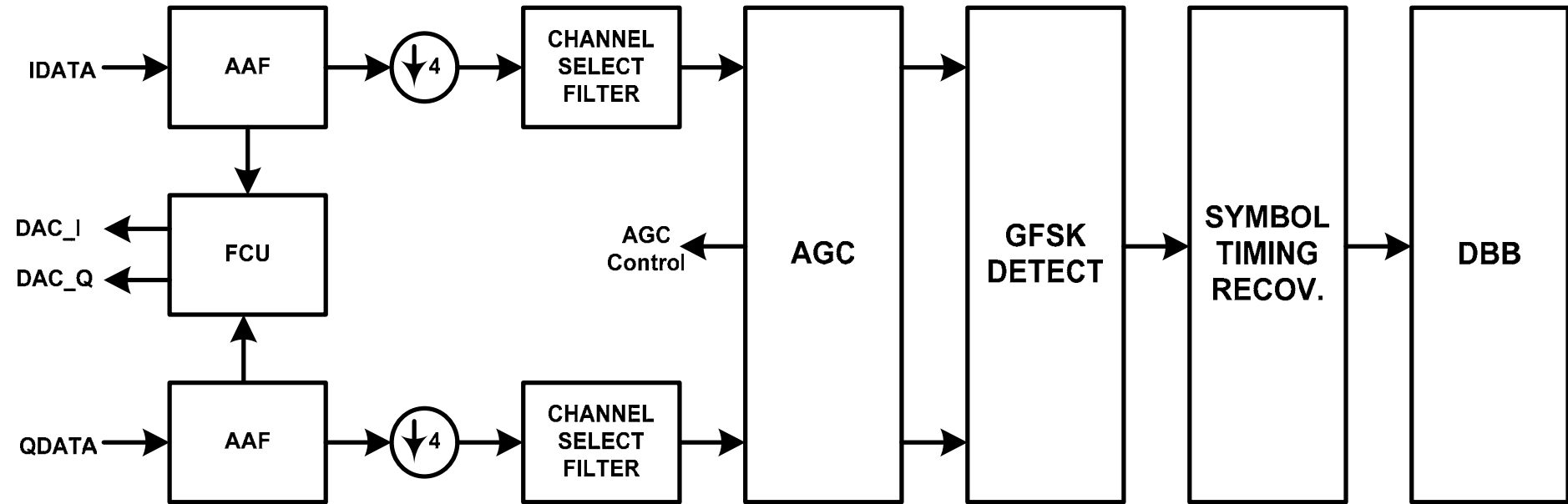

Calibration

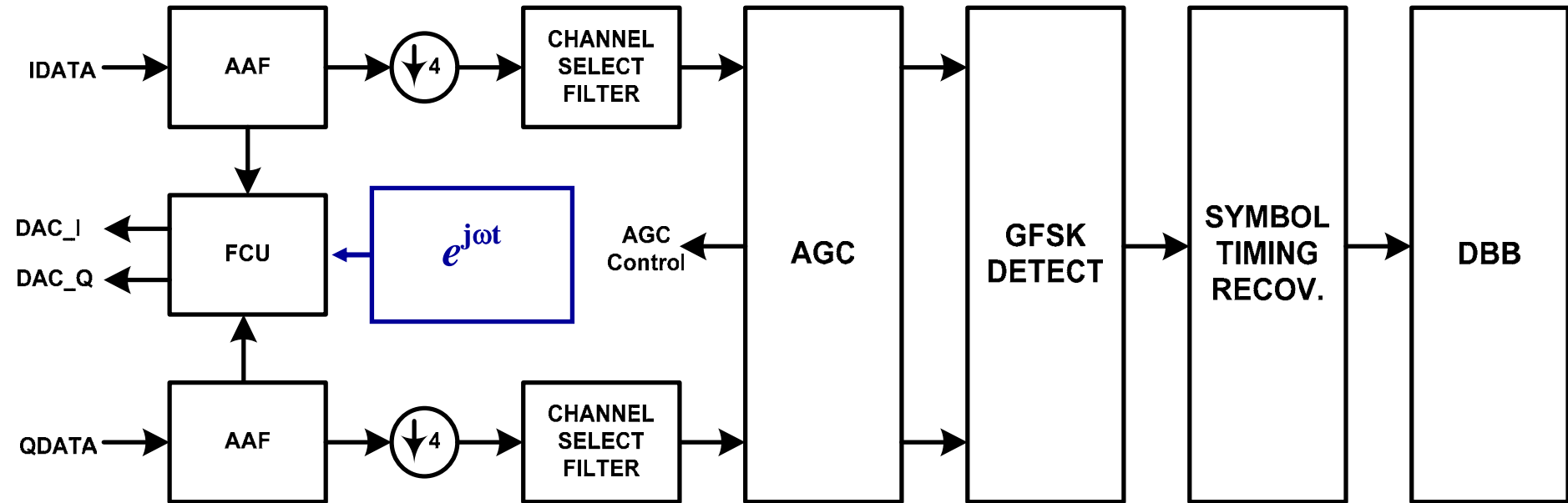

Higher Rate Sampling: 2-pole system

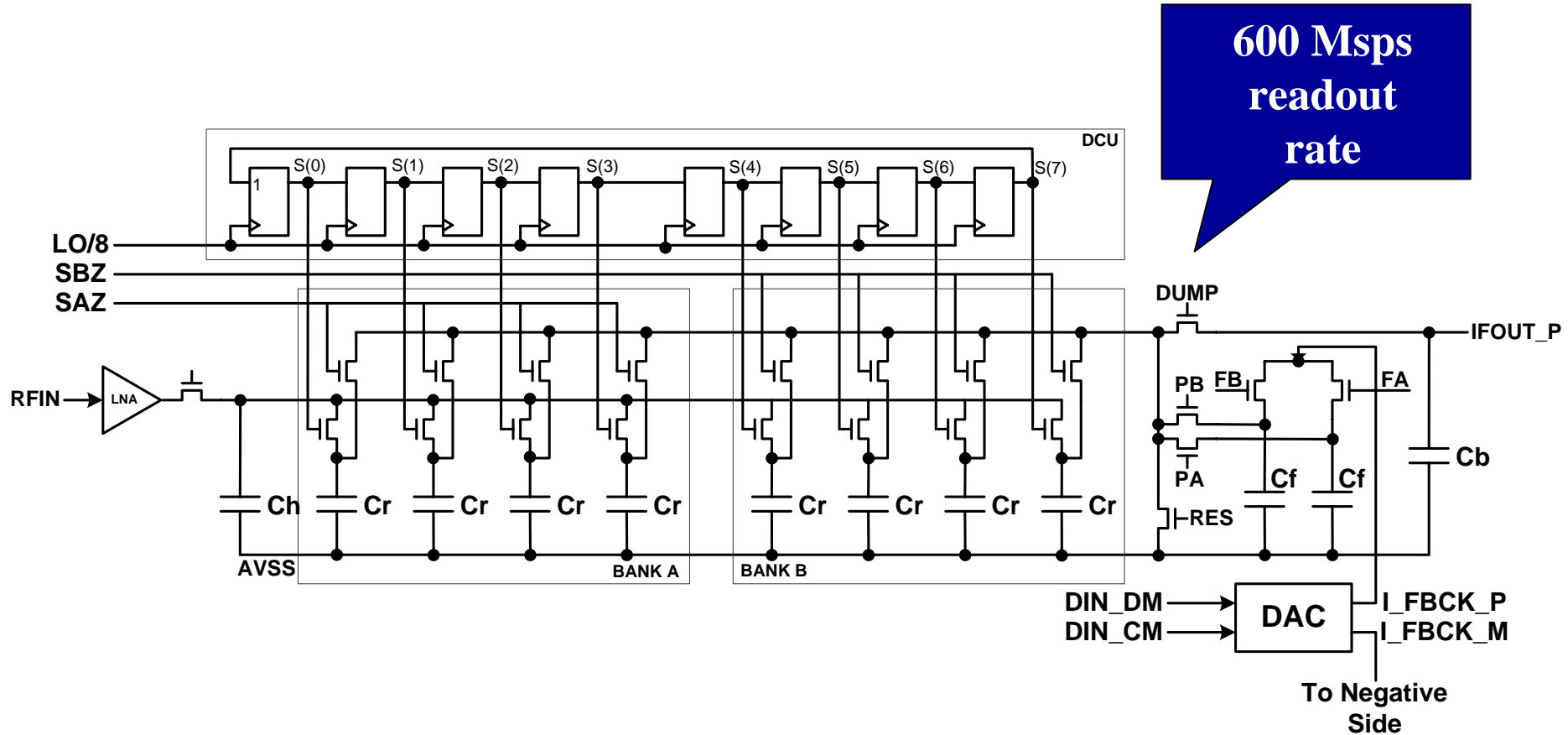

600 Mps
readout
rate

Bank A



Bank B



MTDSM Advantages

- Mixer embedding a filter
 - Anti-aliasing
 - Adjacent channel interferer rejection
 - Reduces linearity requirements of ABE
 - Reduces dynamic range requirements of ABE
 - No further filtering required
 - Modular and scalable
 - Programmable
 - Filtering performance
 - Noise performance
 - Feedback configuration

IV. Results

Implementation

- Digital deep-submicron 0.13 μm CMOS process with no analog extensions
- RF and analog integrated with digital

Interconnect material	copper
Minimum metal pitch	0.35 μm
Transistor nom. voltage	1.5 V
L drawn	0.11 μm
L effective	0.08 μm
Gate oxide	29 \AA

Measurement Results

- Passed the official Bluetooth qualification
- C/I = 10.5 dB, Max. Input = -5dBm, DBB = 4 mA

Work	Technology	TX Current (mA)	RX Current (mA)	Sensitivity dBm
This one	0.13u,1.575V	25	37	-83
[1]	0.18u 2.5-3.0V	35.5	30.5	-78
[2]	0.18u 2.7V	37	39	-83
[3]	0.25u ?V	36	45	≤ -70
[4]	0.25u 2.5V	<70	<50	-80

Chip Micrograph - Bluetooth

130nm Digital
CMOS Process

Digital Baseband

BB
LDO

Logic

BGAP

ADPLL+TX Mod

DAC

DCO

ADC


MTDSM

LNTA
+PA

- Single-chip Bluetooth radio
- RX path
 - Direct RF Sampling
 - Discrete time RX path with $\Sigma\Delta$ ADC
- 1.575V / 37mA current consumption in continuous RX mode

Chip Micrograph – GSM/GPRS

90nm Digital
CMOS Process

 

RX path

- Direct RF Sampling
- Discrete time RX, $\Sigma\Delta$ ADC@500Msps
- 1.4V design
- Scalable architecture

Conclusions

- The first commercial discrete time wireless RX at par with continuous time architectures
 - Bluetooth
 - GSM/GPRS
 - ...
- Direct rf sampling followed by discrete-time signal processing
- Performance demonstrated in single-chip fully-compliant radios

References

- [1] P. T. M. van Zeijl et al., “A Bluetooth Radio in 0.18um CMOS,” *ISSCC Dig. Tech. Papers*, pp. 86–87, Feb. 2002.
- [2] G. Chang et al., “A Direct-Conversion Single-Chip Radio-Modem for Bluetooth,” *ISSCC Dig. Tech. Papers*, pp. 88–89, Feb. 2002.
- [3] J. Cheah et al., “Design of a Low-Cost Integrated 0.25um CMOS Bluetooth SOC in 16.5mm² Silicon Area,” *ISSCC Dig. Tech. Papers*, pp. 90–91, Feb. 2001.
- [4] Eynde et al., “A Fully-Integrated Single-Chip SoC for Bluetooth,” *ISSCC Dig. Tech. Papers*, pp. 196–197, Feb. 2001.