

Sigma-Delta ADC Tutorial and Latest Development in 90 nm CMOS for SoC

Jinseok Koh

Wireless Analog Technology Center


Texas Instruments Inc.

Dallas, TX

Outline


- **Fundamentals for ADCs**
- **Over-sampling and Noise shaping**
- **Sigma-Delta ADC**
- **Double Sampling Technique**
- **2nd Order Single Amplifier Sigma-Delta ADC**
- **Implementation in 90nm CMOS for SoC**
- **Conclusions**

Modeling of Quantizer

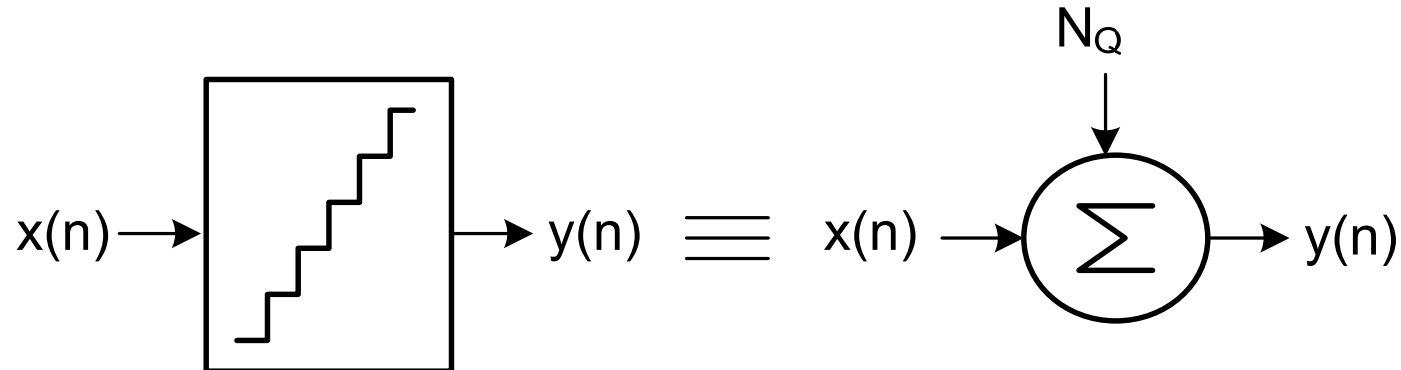

- **Quantizer is non-linear building block**
 - Need modeling for simplifying the analysis
- **White additive noise assumptions**
 - It is not fulfilled in many applications, However
 - It makes analysis easy and makes possible the use of z-transformation




Quantization Noise

 


- **Quantity of in-band noise depends on the over-sampling ratio**
 - $SNR = 10\log(\sigma_x^2) - 10\log(\sigma_n^2) + 3.01r(\text{dB})$, where
 - σ_x^2 and σ_n^2 are input signal power and in-band noise power respectively, and
 - r is defined by over-sampling ratio, $f_s/2f_b = 2^r$

Pervez M. Aziz, "An overview of sigma-delta converters," IEEE Signal processing Magazine, pp 61-84, Jan. 1996


Nyquist Rate vs. Oversampled

 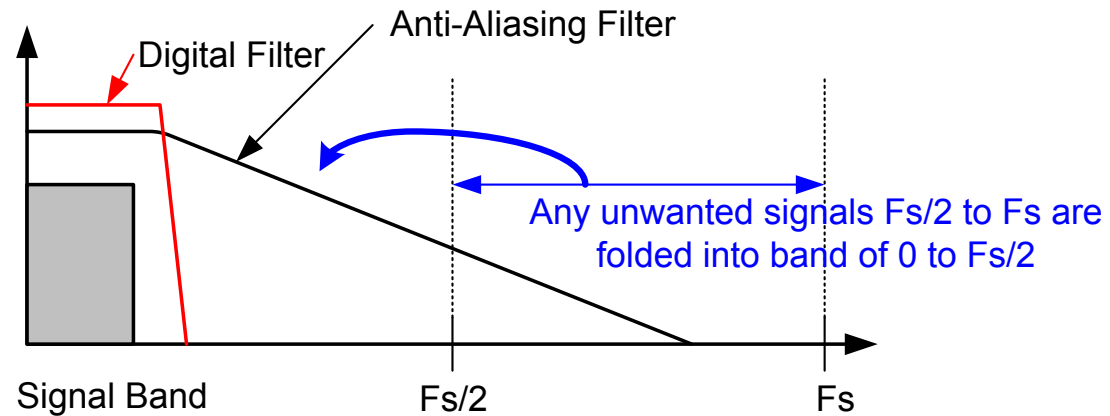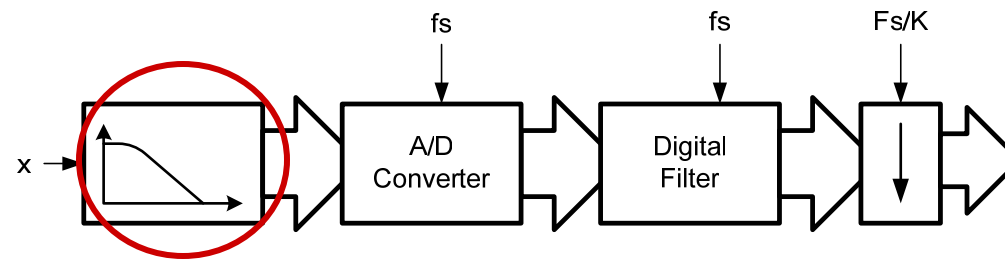

Over-sampling and Noise Shaping

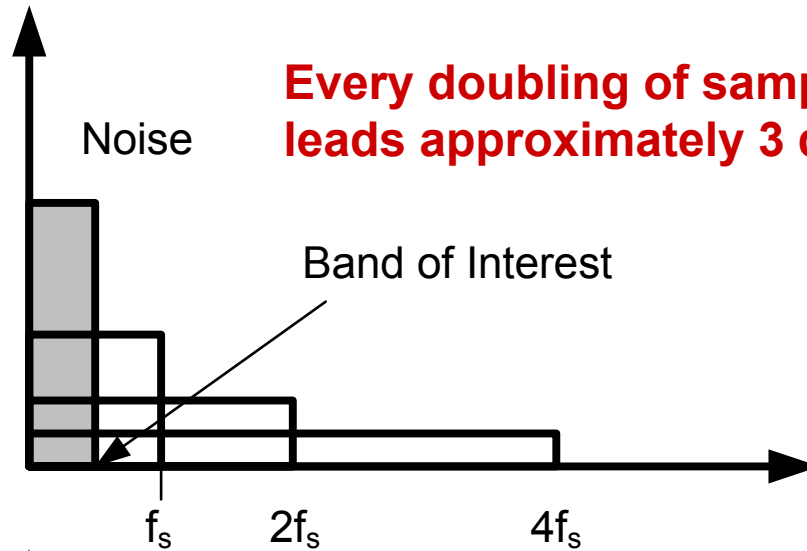


 Every doubling of sampling frequency leads approximately 3 dB enhancement in SNR



Noise shaping pushes quantization noise to higher frequency resulting in suppressing Q. noise in the band of interest

How to Shape the noise?

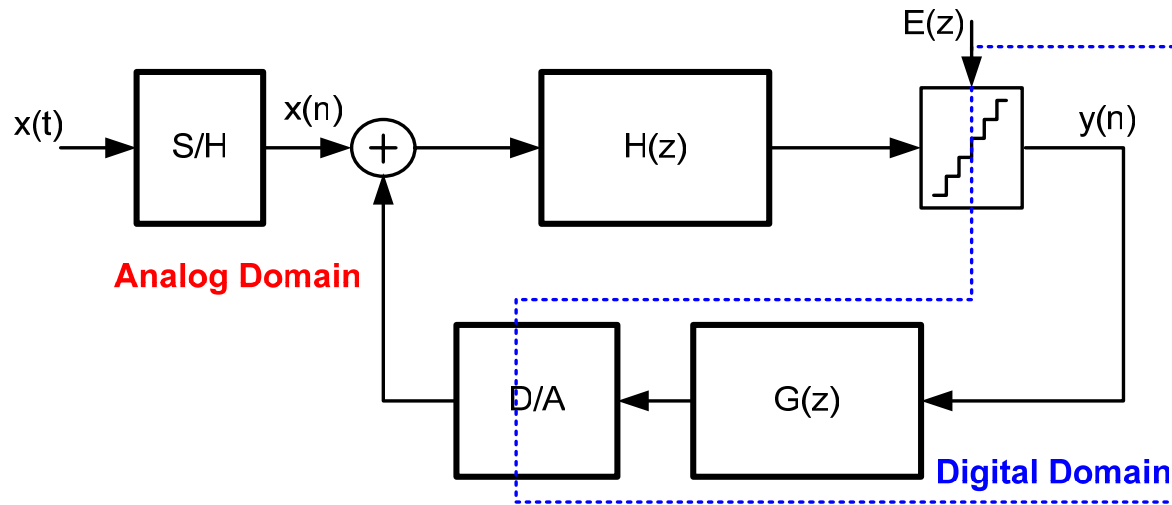


$$Y(z) = \underbrace{\frac{H(z)}{1+H(z)G(z)}}_{\text{STF}} \cdot X(z) + \underbrace{\frac{1}{1+H(z)G(z)}}_{\text{NTF}} \cdot E(z)$$

If $H(z) = z^{-1}/1-z^{-1}$ and $G(z)=1$, NTF and STF will be:

$$\text{NTF} = \frac{Y(z)}{E(z)} = 1 - Z^{-1} \qquad \text{STF} = \frac{Y(z)}{X(z)} = Z^{-1}$$


Example, 2_{nd} order Sigma-Delta ADC

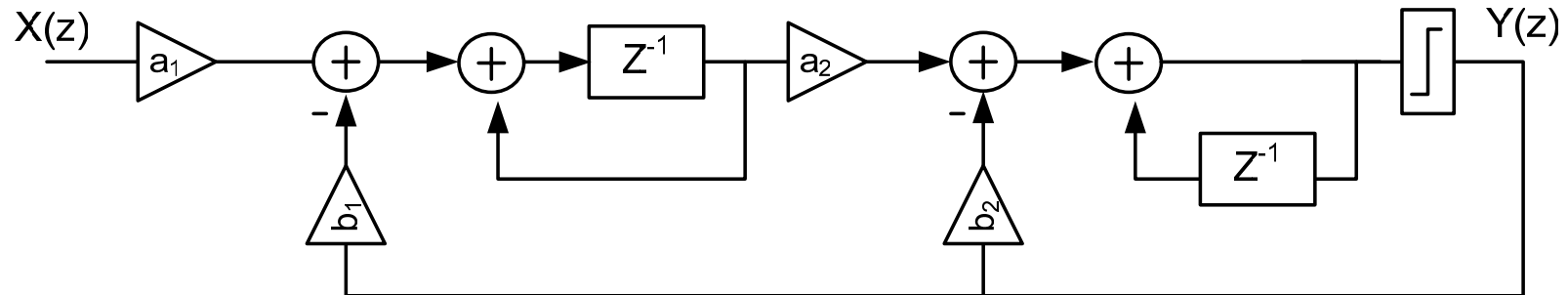

Summary

- **Sigma-delta ADC provide trade-offs between:**
 - Power consumption,
 - Over-sampling ratio (*OSR*)
 - System performance (*SNR*)
- **High OSR implies:**
 - Lower number of quantization levels
 - Lower modulator order, but
 - More demanding settling requirements for the analog building blocks



Objectives

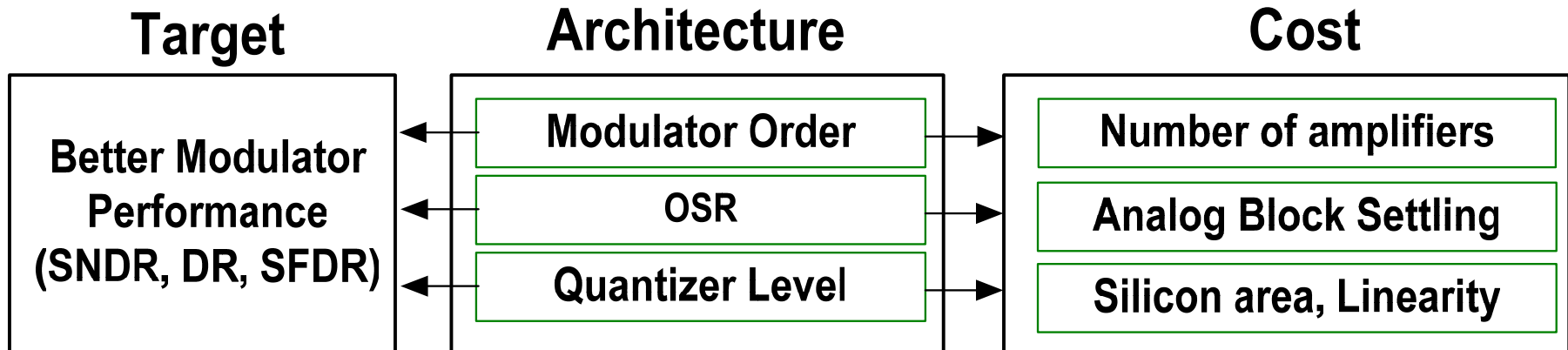

- **For a given performance requirement, power consumption and area are optimized by:**
 - Increasing sampling frequency → Double sampling technique
 - Increasing modulator order → Single Amplifier topology
 - Higher number of levels in Quantizer → 5-level quantizer with ILA

Double sampling

 
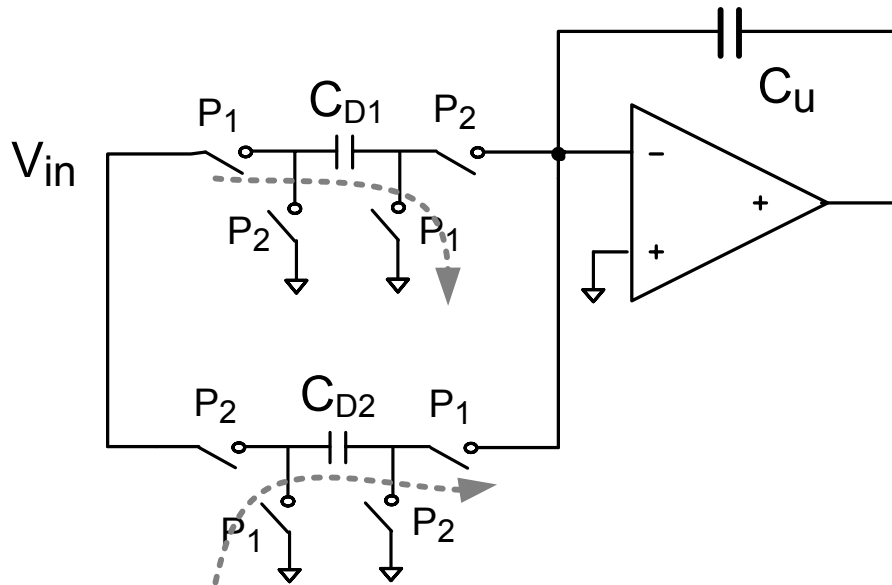
- **Advantages:**
 - Efficient technique to double the OSR
 - Doesn't need faster op-amp settling
 - Provides improvement of SQNR by $6n+3$ dB (n =order)
- **Disadvantage:**
 - Mismatch between capacitors creates noise folding




Noise Folding In Double Sampling

- Alternating gain effect

→ Noise at $F_s/2$ is folded into Signal bandwidth

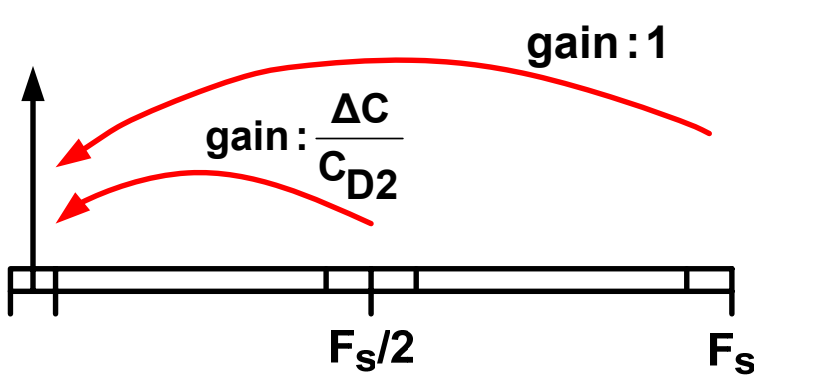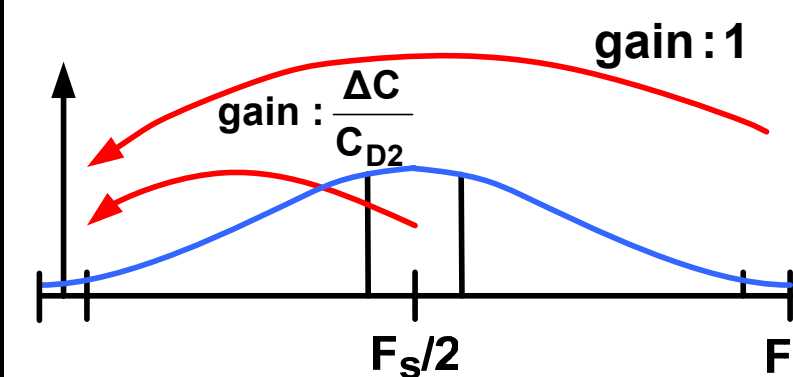
Noise folding (Input sampling circuit)	Noise folding (DAC in feedback path)
 <ul style="list-style-type: none"> • Noise at $F_s/2$ is suppressed by <ul style="list-style-type: none"> - Anti-aliasing filter - Pre-filtering 	 <ul style="list-style-type: none"> • No filtering on quantization noise

Conventional Double Sampling DAC

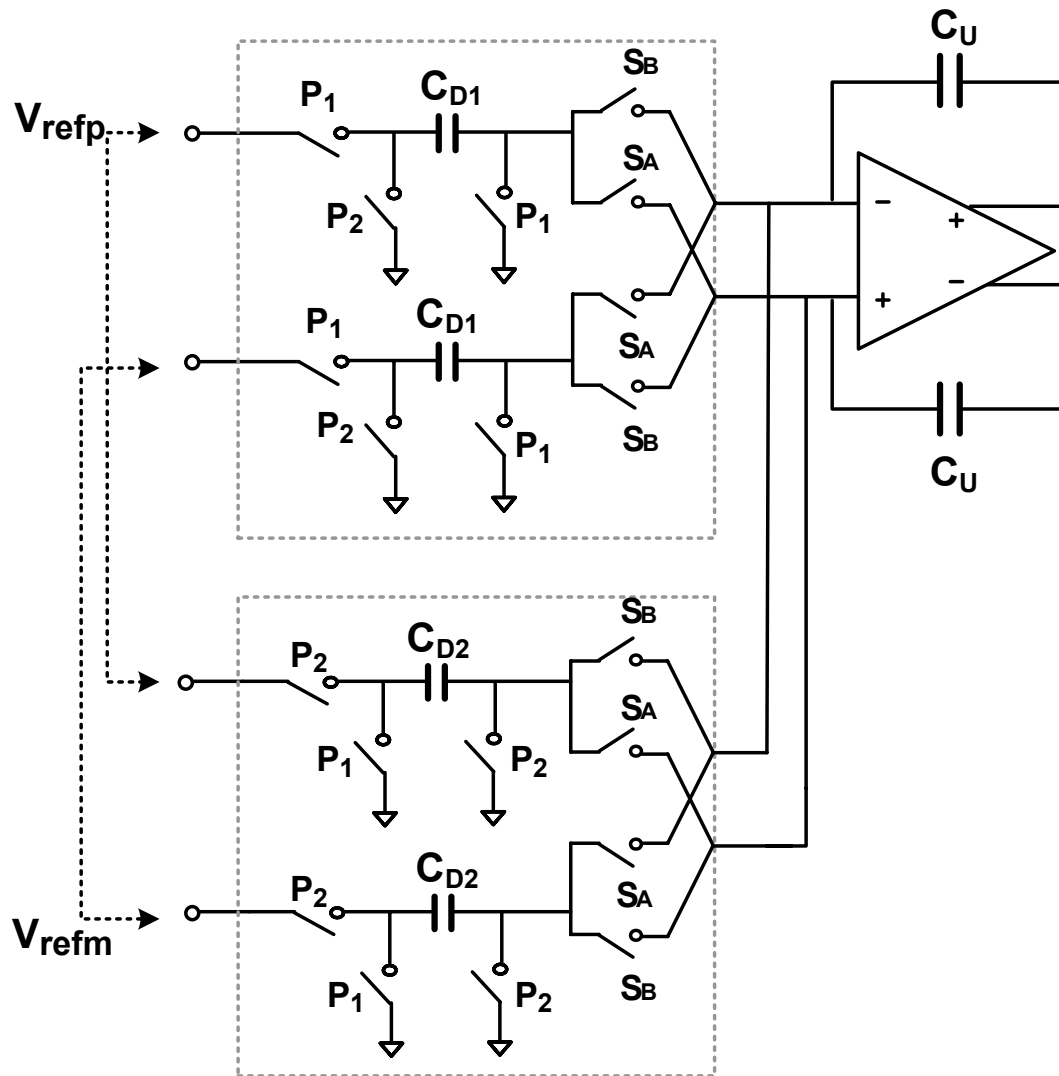


- On P1 phase,
Stored charge in C_{D1} :
 $C_{D1}(V_{refp}-V_{refm})$
- On P2 phase,
Stored charge in C_{D2} :
 $C_{D2}(V_{refp}-V_{refm})$
- Requires two sets of
switched capacitor DACs
- Mismatch on stored
charge causes alternating
gain effect

 Proposed SC DAC element for double sampling




- **Advantages of this approach vs. conventional approach:**
 - Only one pair of capacitors needed
 - No “alternating-gain” effect
 - No additional circuitry needed for matching purposes

Operation of Proposed SC DAC element

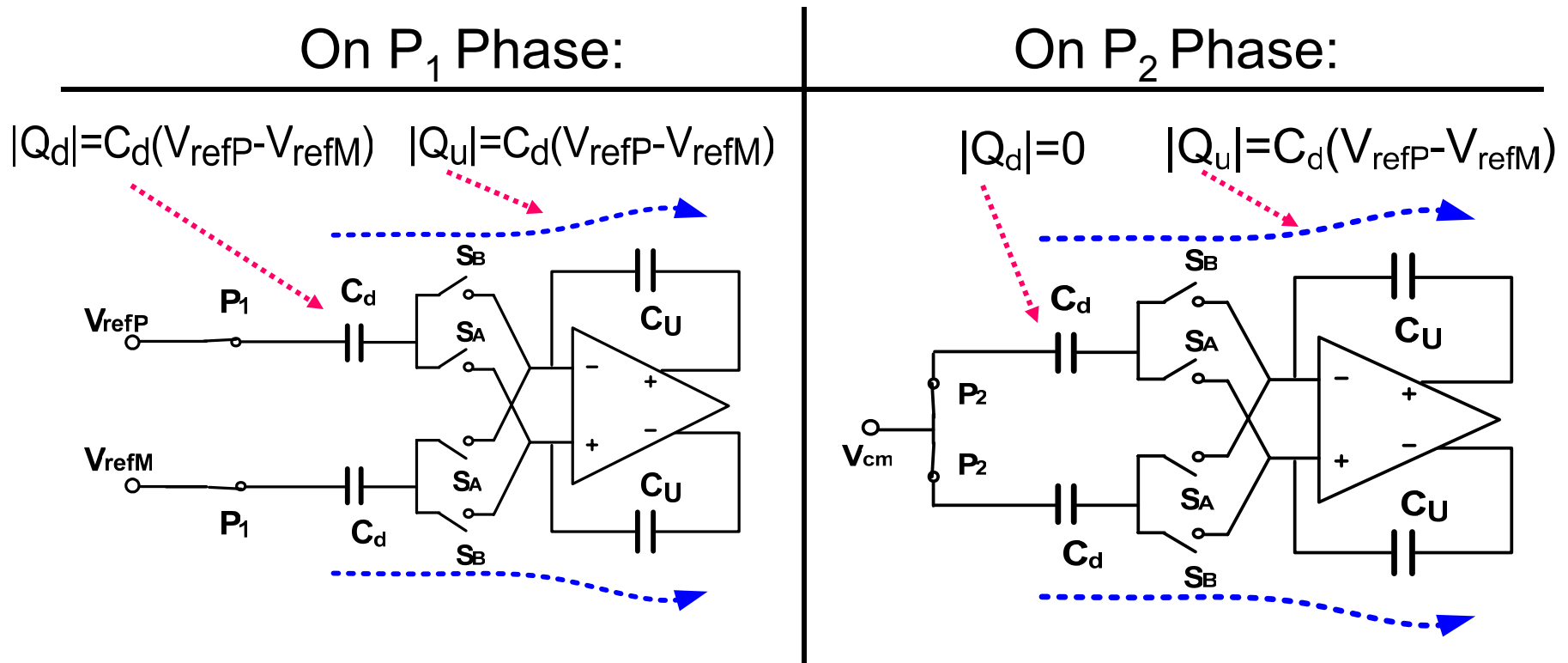

- On phase P_1 the charge transferred to Integrating Capacitor is:
 - $Q_u = C_d(V_{refp} - V_{refm})$
 - Q_u is equal to the charge stored into C_d
 - This charge will be used during next integration phase


Conventional 2nd Order Sigma-Delta ADC

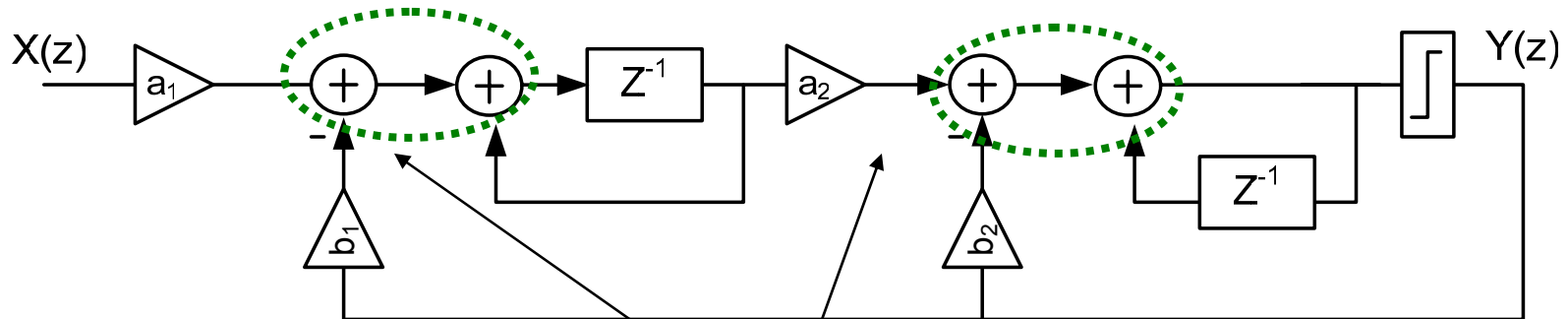

Each Summing Node requires an Amplifier


- **Conventional Sigma-delta ADC:**
 - Needs an amplifier per summing node
 - Poles and zeros are chosen by a_i and b_i , where $i=1,2$

Q-path Operation


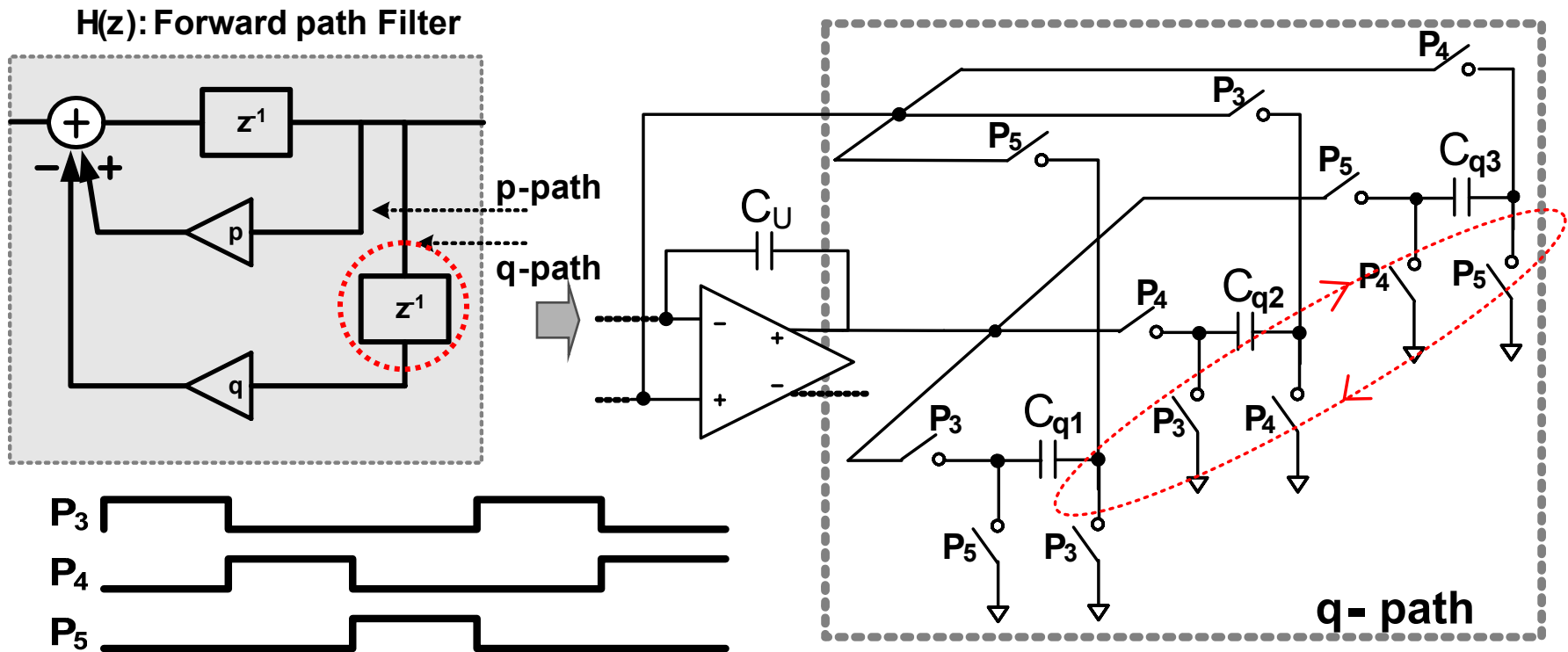


- Rotating to do sampling, holding and integrating functions
 - The first SC circuit **samples** the output $v_o(n)$
 - while the second one **holds** the previous output $v_o(n-1)$
 - and the third one **transfers** $v_o(n-2)$ to the integrating capacitor, C_U

Full Filter implementation

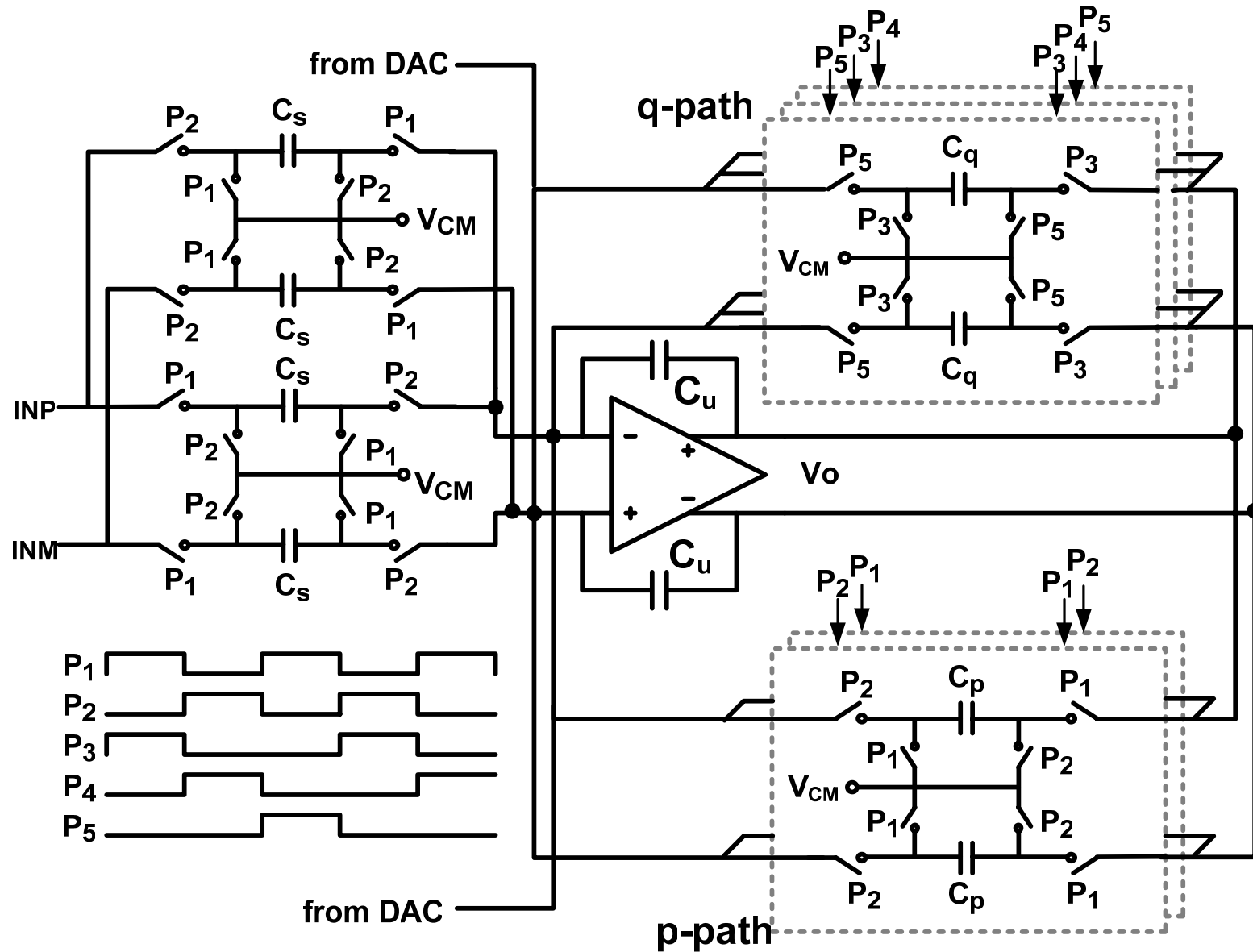


Amplifier design (SR, GBW)

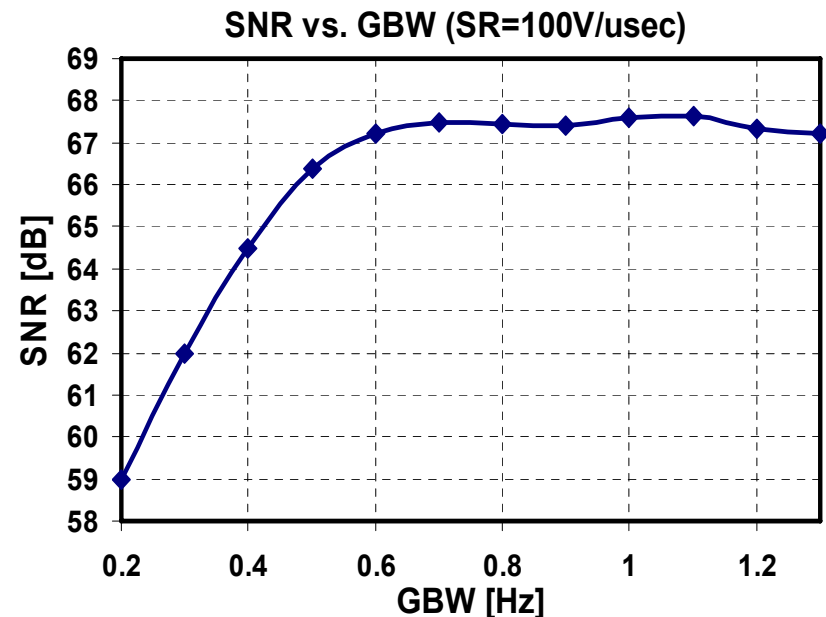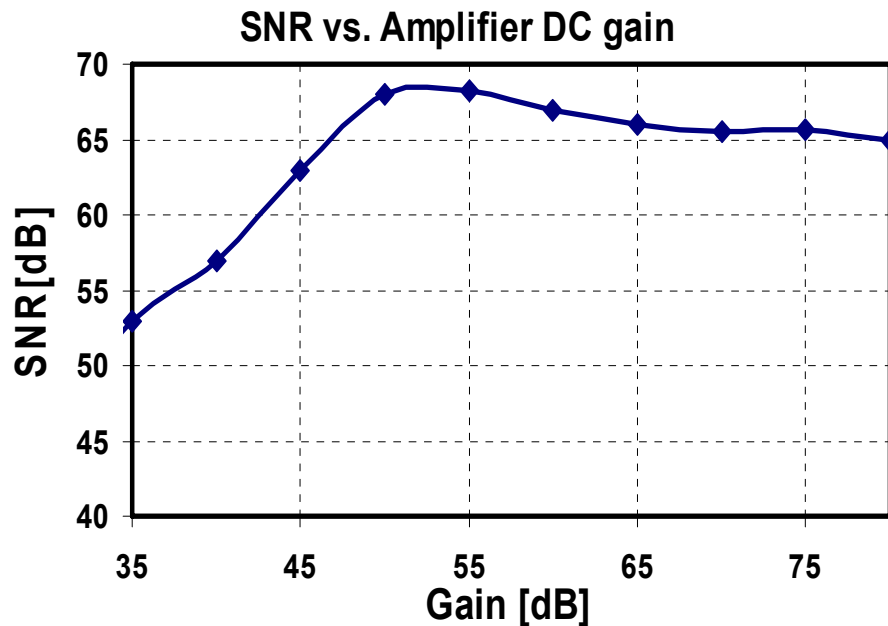


- GBW and SR were simulated in Matlab behavioral model
- Amplifier was designed to have:
 - DC Gain > 60dB, SR > 100V/ μ sec and GBW > 50MHz
- Single amplifier topology has a benefit since settling requirement is lower than conventional one

Amplifier implementation

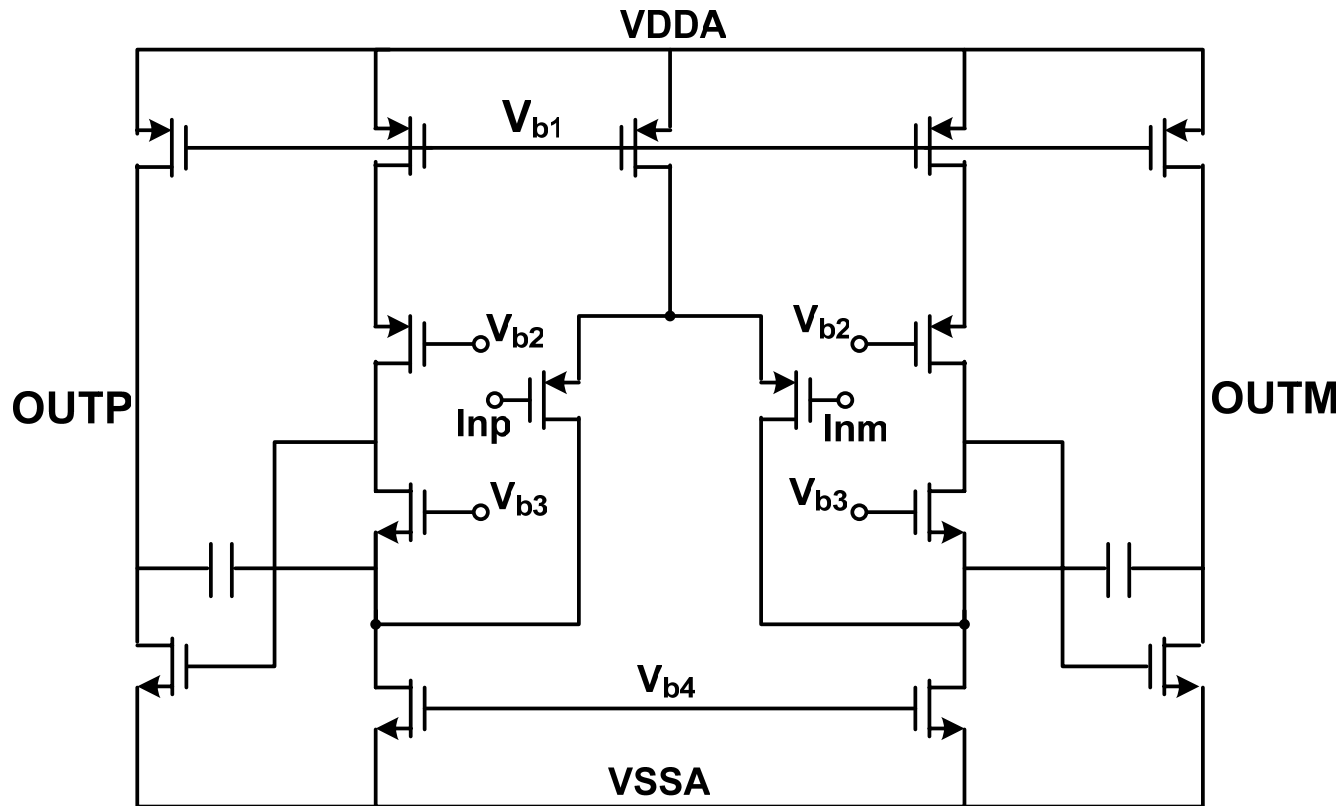


Load Capacitance	1.6 pF
GBW	100 MHz
Input referred Noise*	70 μ Vrms
Slew Rate	200 V/usec
Current Consumption	700 μ A

Measured Power Spectral Density

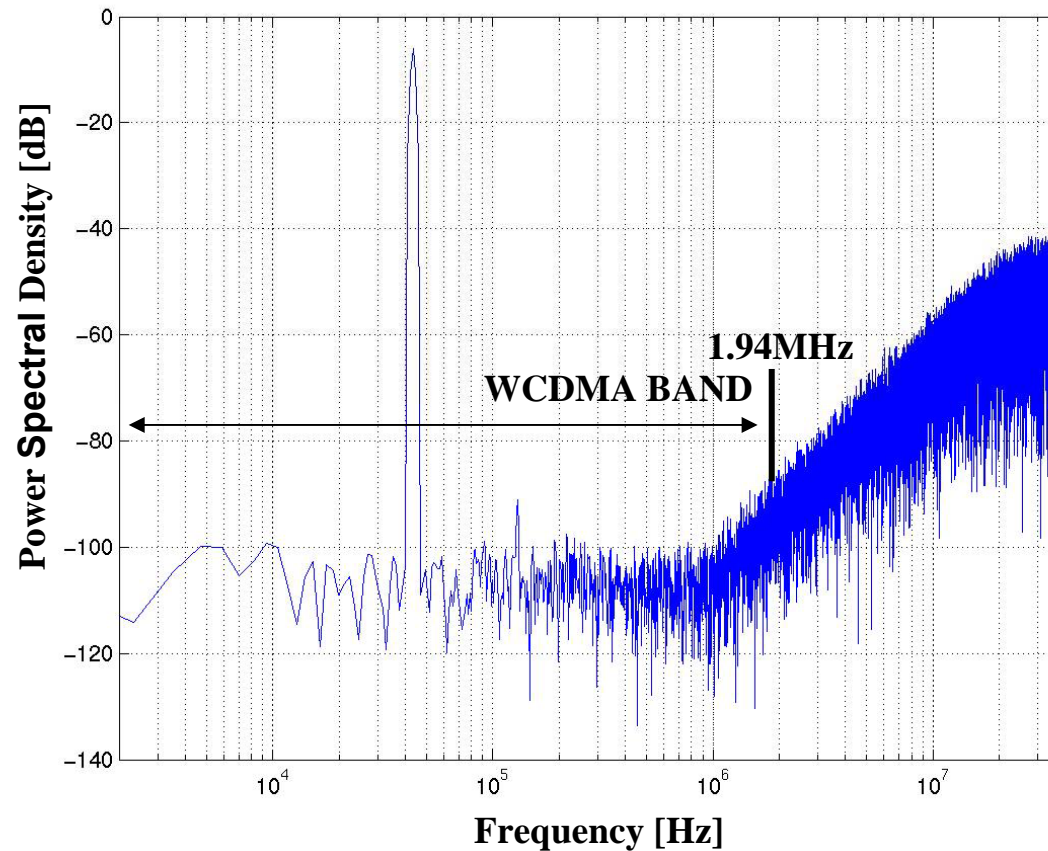


- **Input signal: -6 dBFS sine at 448 kHz**
- **3rd harmonic shows up at -91 dBV**
- **Noise floor shows no noticeable noise folding**

SNDR vs. Input power

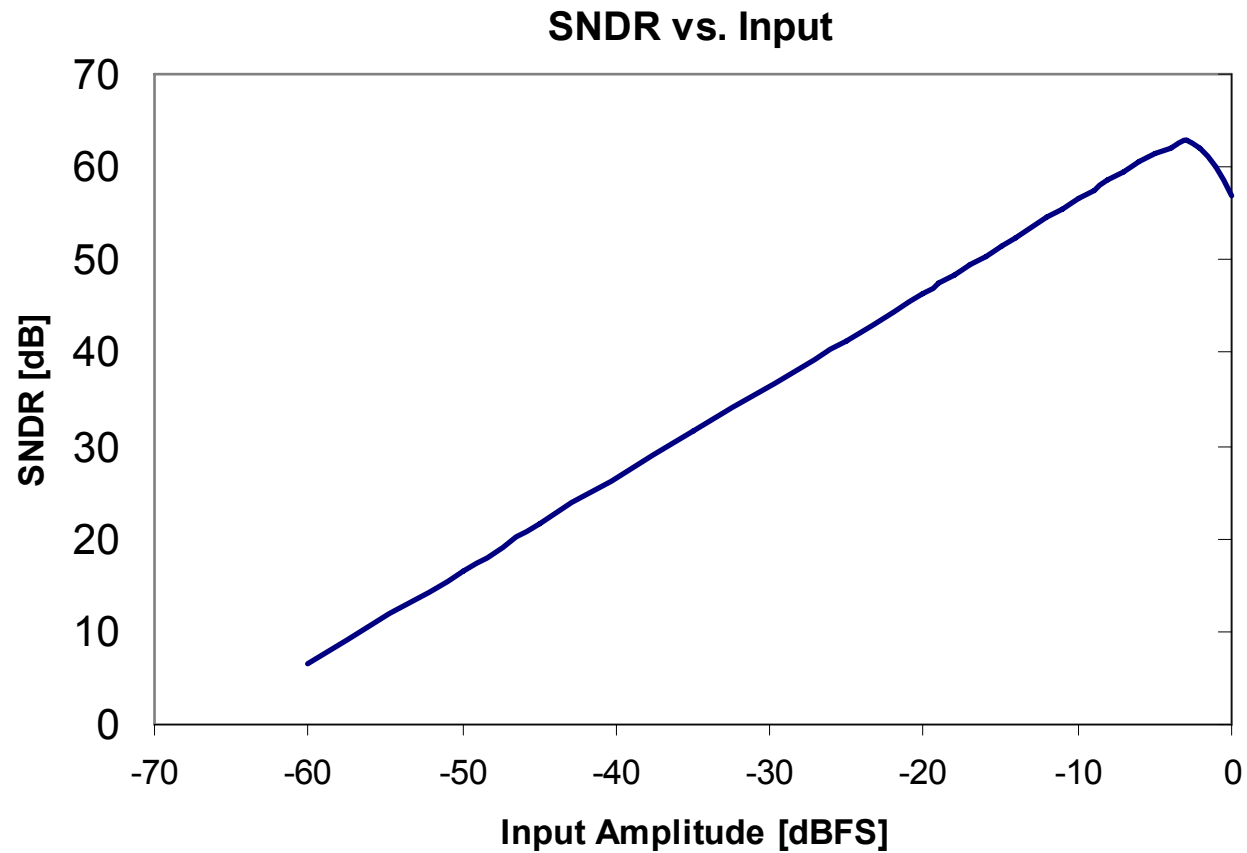

- **63dB peak SNDR happens at -3dBFS input sinusoidal**

Die Photography for dual channel ADCs

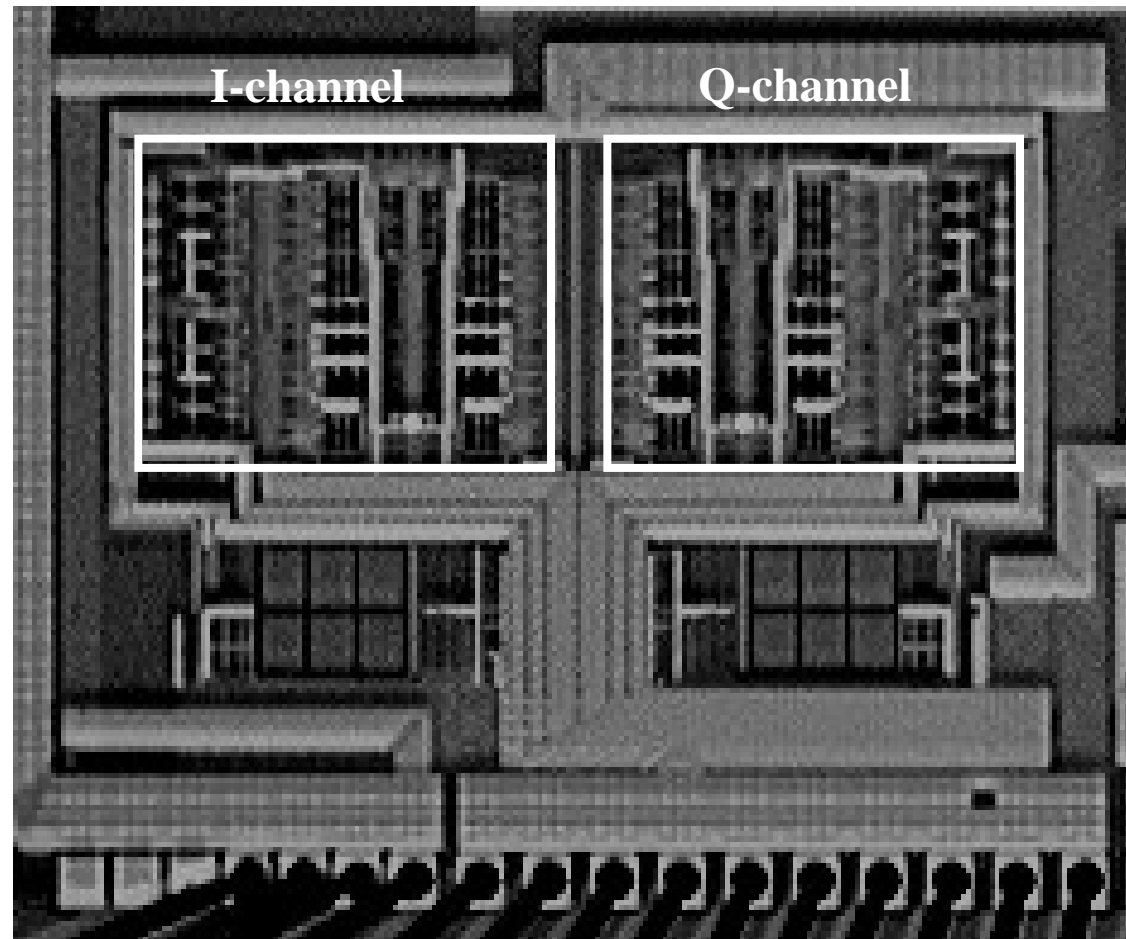

- Implemented in 90nm 5 metal digital CMOS process

Performance Summary

Technology	90 nm Digital CMOS
Signal Bandwidth	1.94 MHz
Clock Frequency	38.4 MHz
Sampling Frequency	76.8 MHz
Peak SNDR	63 dB
Dynamic Range	66 dB
Input Range	1.5 V_{pp} (differential)
Voltage Supply	1.2 V
Power Consumption	1.2 mW per ADC
Core Area	0.2 mm² per ADC

Conclusions

- **Second order 5 level Single Amplifier Sigma-Delta ADC with double sampling technique was realized in 90 nm CMOS.**
- **By using double sampling technique, OSR is doubled with no increase of power consumption and silicon area.**
- **Single-capacitor double-sampling DAC solved “alternating-gain” error effect.**
- **2nd order modulator is implemented using a Single-amplifier architecture. Higher order modulator is feasible.**
- **Low power consumption: 1.2mW for WCDMA, measured with a 1.2V power supply.**
- **66dB dynamic range was achieved in 1.94MHz bandwidth.**