

Design Trends in deep-submicron CMOS with example of GPS-Receiver

Dr. Srinivasan Venkatraman
Texas Instruments Inc., Dallas, Tx.

- **In the late 1950s, a new aircraft carrier had 350,000 electronic components, requiring millions of hand-soldered connections – "tyranny of numbers" (Jack Kilby)**

- **Transforming Nature**

- **Michael E. Gorman, University of Virginia**

Today...

- Shrinking geometries enable more than 10-Million devices per die.
 - **New problems and issues.**
 - **New Opportunities for innovation**

Deep-Submicron CMOS- Opportunities

- Shrinking geometries → **more transistors.**
- Smaller devices → **Higher ft & faster transistors.**
- More transistors → **Complex digital processing and more digital content.**
- More integration → **The economic drive of lowering the cost of electronics.**

Deep-Submicron CMOS - Issues

- Smaller geometry → Lower supply voltage.
- Smaller devices → More 1/f noise.
- Smaller devices → More leakage.
- Higher digital gate density → Larger portion of silicon is taken by analog circuits (Need to shrink, to gain economic edge).
- More integration → Isolation issues between various sub-modules of the system.


System-on-chip - Examples

- **Network processors**
- **Graphics Processors**
- **Bluetooth transceivers**
- **WLAN transceivers**
- **GPS receivers**
- **GSM transceivers**


System design – Changing paradigms

- What works in regular system design may-not work for SoC.
- The building blocks available are slightly different –
 - **Eg: Transmission lines & stubs are not available easily on an IC.**
 - **Using SAW filters is an expensive option, mainly due to off-chip interface, pins & board space.**

GPS Receiver architecture


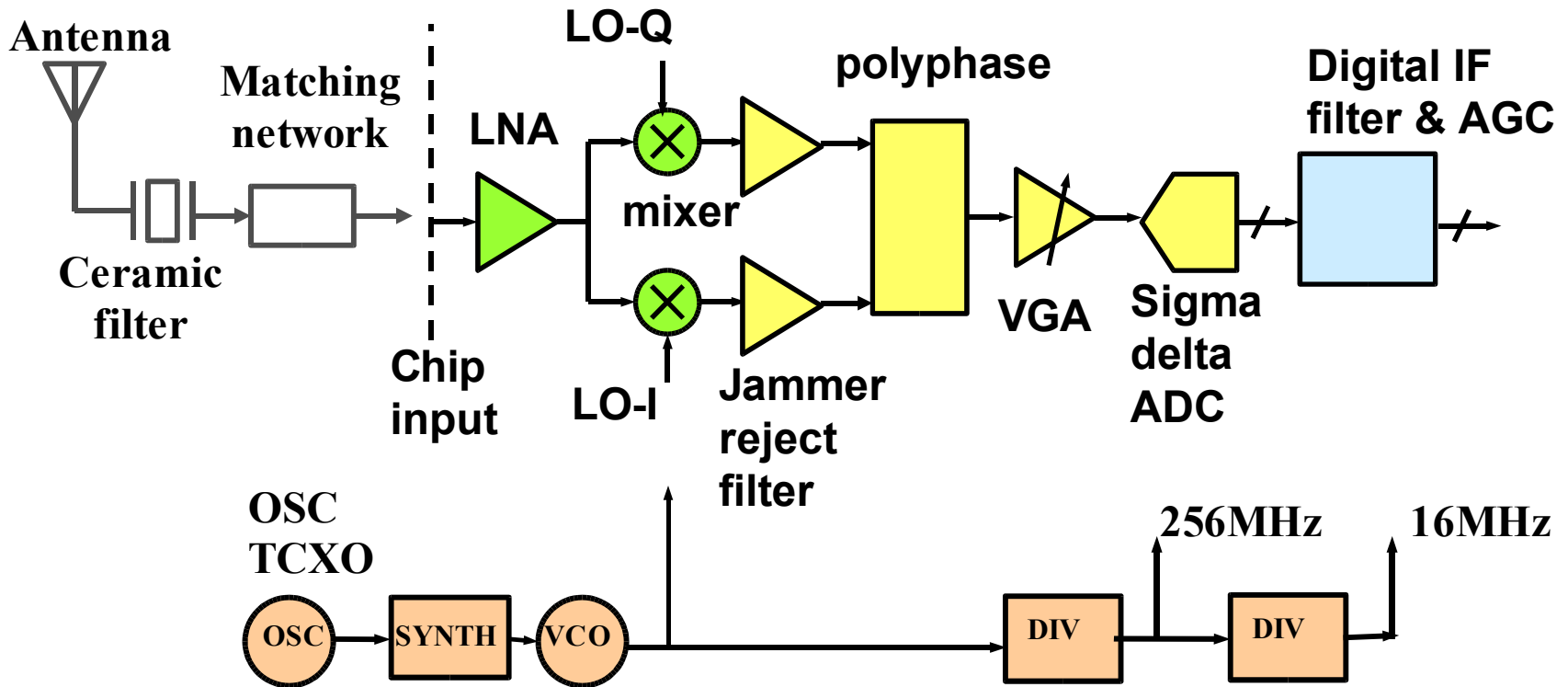


Front-end

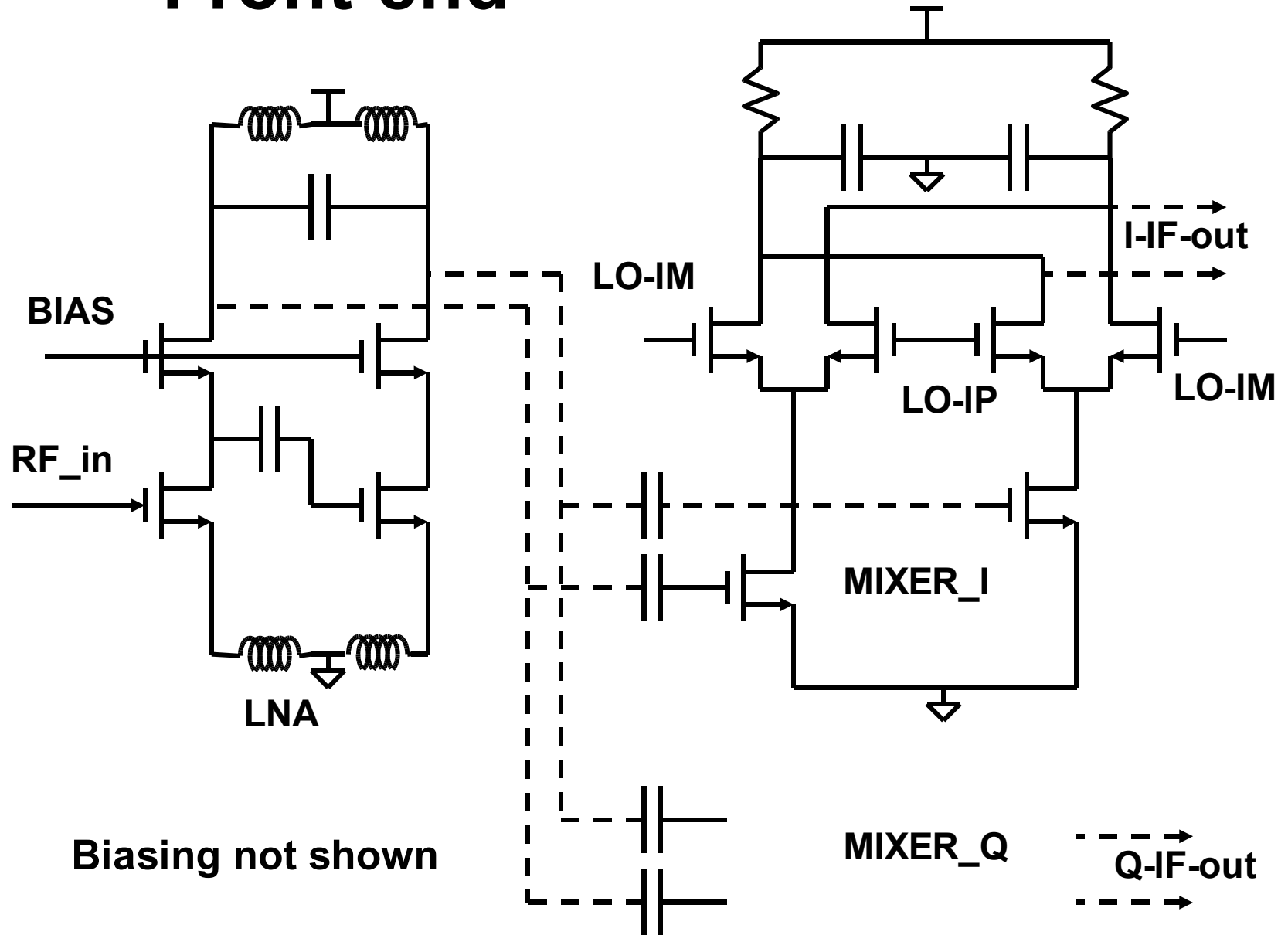


IF chain signal processing

  
- **Deep-submicron process not suitable for accurate analog filtering**




Jammer reject filter

 



PolyPhase Filter

 


Passive continuous time delta-sigma ADC

 

Digital filter architecture

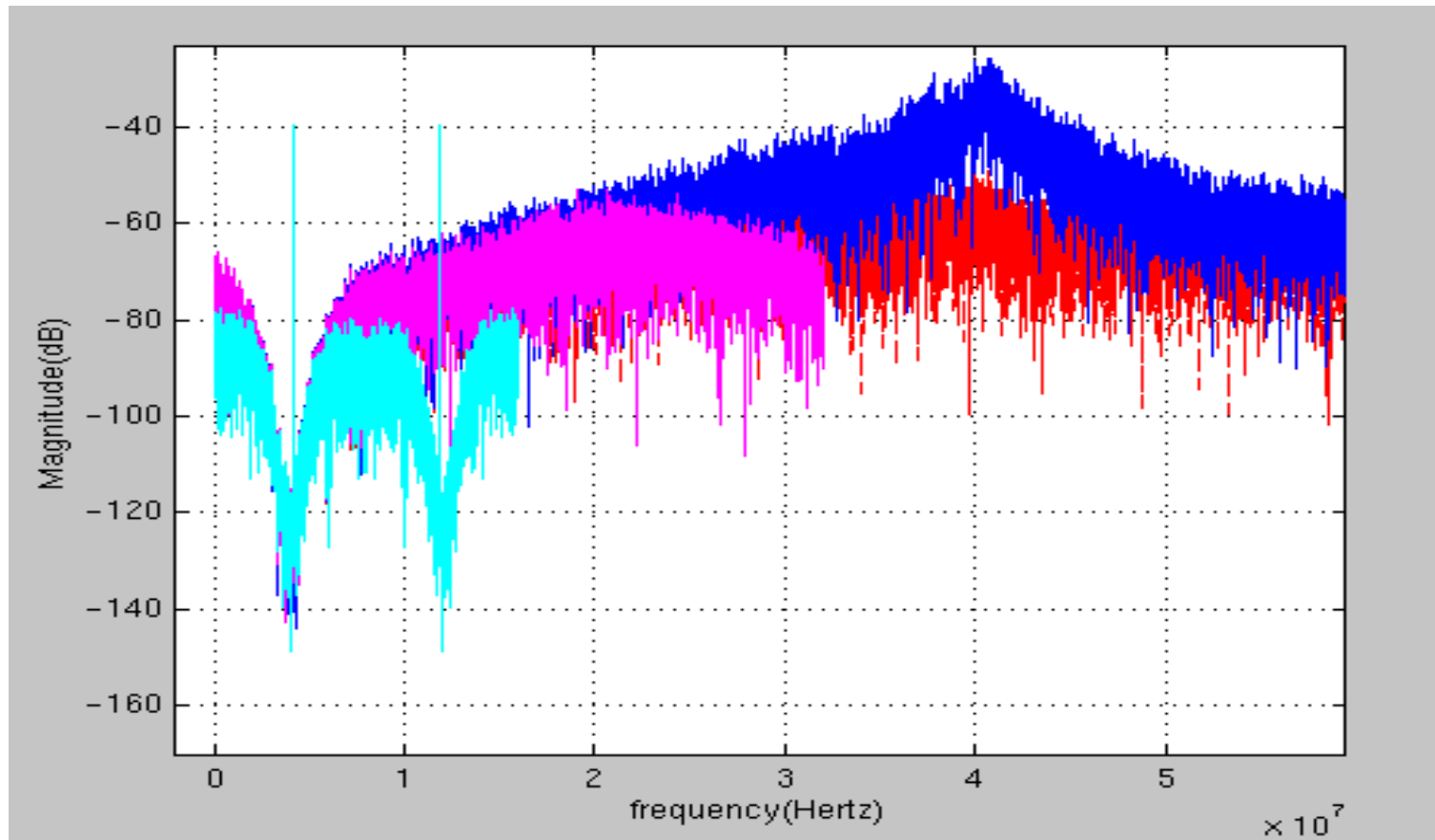 


Synthesizer architecture

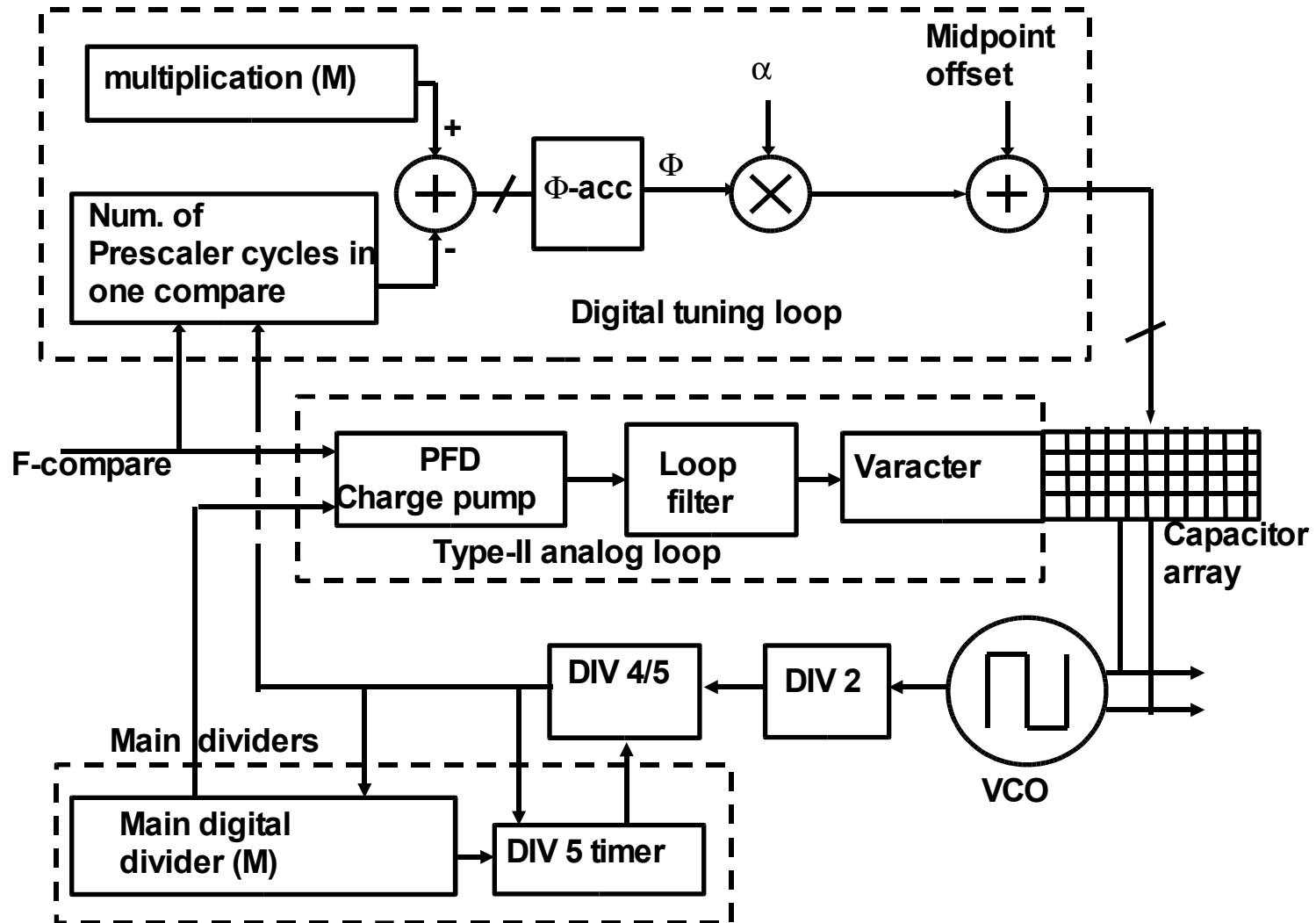

- Type-II analog integer-N PLL
- Type-I digital tuning loop for PVT calibration of VCO Freq.

VCO

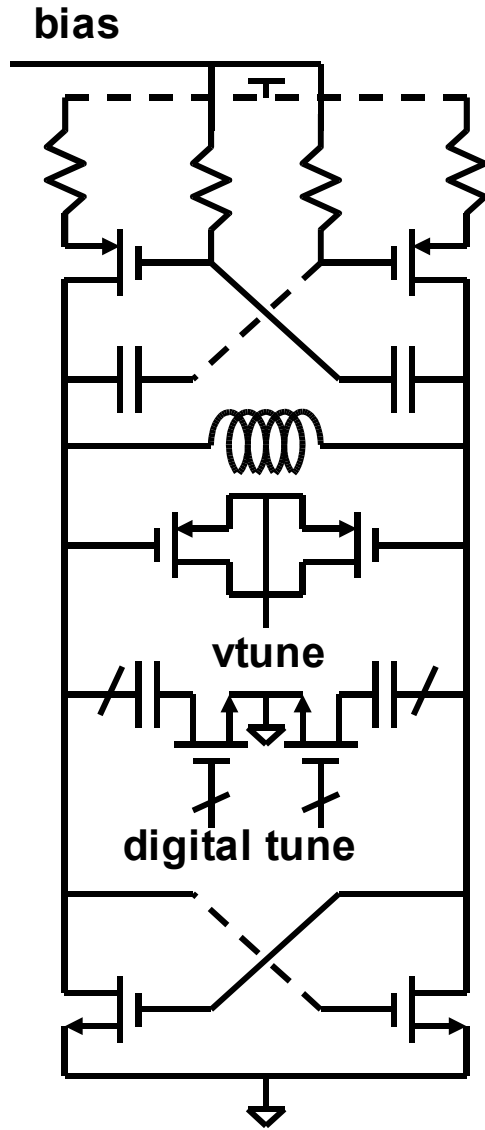


- **LC tank with metal-spiral and MOS varactor**
- **Switched capacitor (MIM) array to augment the tuning range**
- **Cross-coupled MOS gain stage for negative resistance**
- **Self-tracking bias to minimize supply pull on VCO frequency**


Challenges

- **Low Supply Voltage (1.4 volts).**
- **SoC integration of RF + Base-band.**
- **Achieve high-linearity of RF front-end.**
- **Choice of pin-out to minimize package coupling.**
- **Floor-plan to minimize influence of digital noise on RF circuits.**
- **Isolation of supplies and grounds (power supply coupling).**
- **IR drop analysis and isolation of high-activity regions.**
- **Minimize power-supply spikes and use de-coupling capacitors to provide switching current.**
- **Judicious use of guard rings to isolate noise.**

Receiver response

 


De-sense with out-of-band jammers

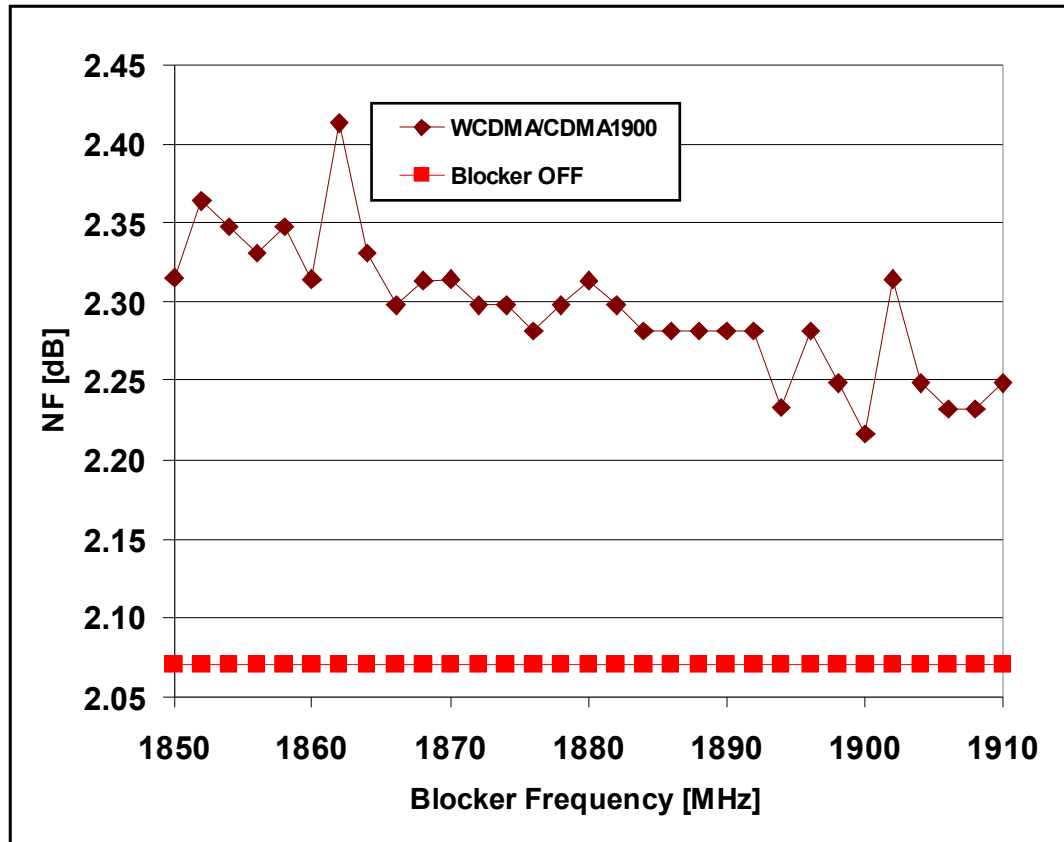

- Noise figure without any jammer is 2.05 dB
- With -31dBm jammer at 1850MHz the Noise figure goes up to 2.3 dB
- With stronger LO drive (elevated supply) the desense is < 0.1dB

Phase noise at LO/4

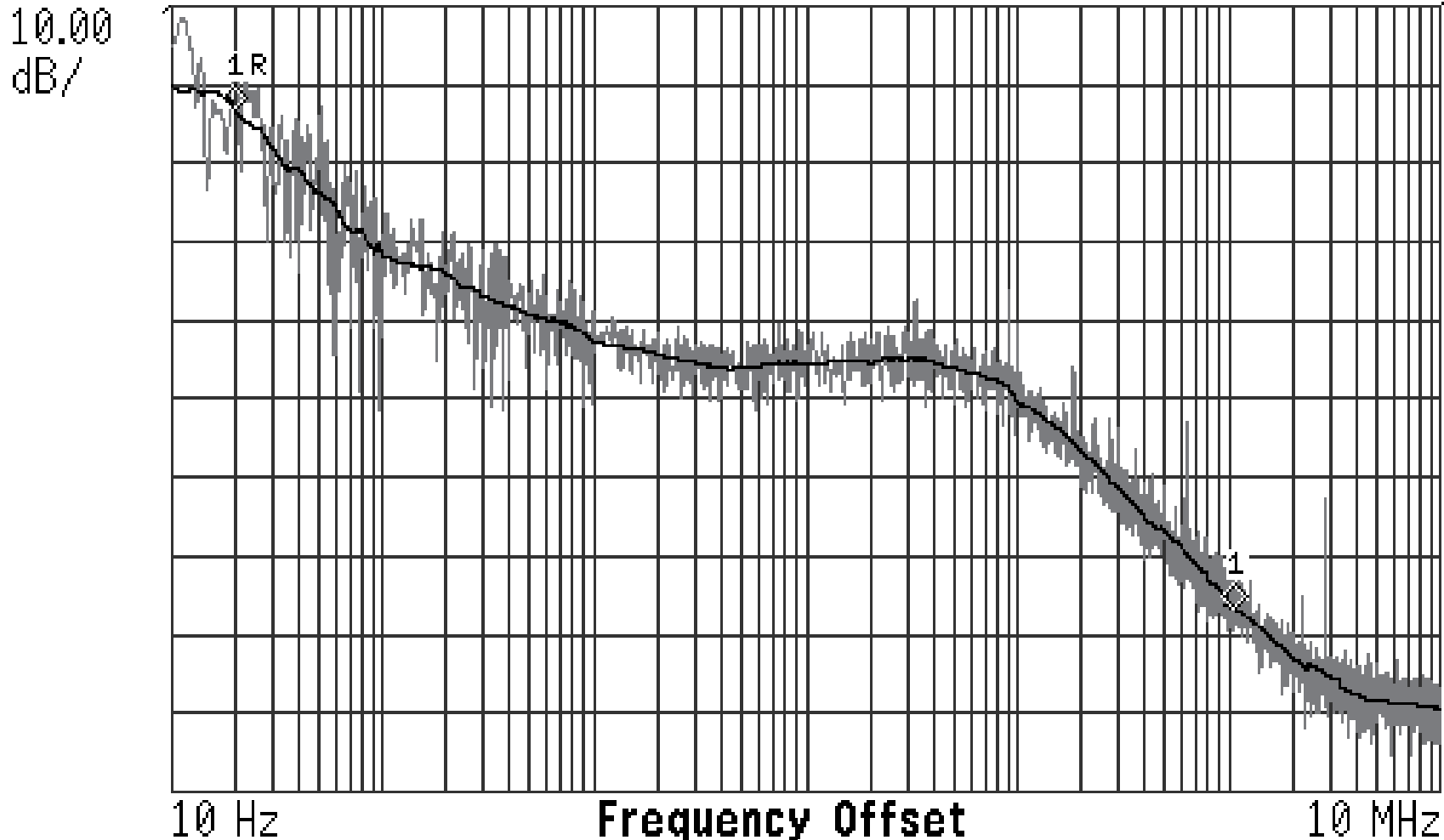Carrier Power -13.60 dBm Atten 0.00 dB Mkr1 1.05421 MHz
Ref -50.40dBc/Hz 467.5m Deg




Measured Performance

LNA + IRM	
Gain	38 dB
Noise Figure	1.8 dB
S11	-11 dB
IIP3 (@ 1576MHz and 1576.5MHz)	5dBm
PCS band jammer desense	0.1dB
ADC	
Dynamic Range	38dB

Performance Continued...

SYNTHESIZER	
Phase noise at 100KHz	-88dBc/Hz
Phase noise at 1MHz	-113dBc/Hz
Integrated rms Phase error	2 deg
Lock Time	100ms
Reference Spur	-60dBc
FULL RECEIVER	
Die Area	12.8 mm²
Image rejection	18dB
Power	60mA @ 1.4V


Single-Tone Response of Receiver

 


Spot Noise-Figure of Receiver

Baseband freq.(kHz)	-500	-250	0	250	500
NF (dB) at Baseband	8.43	2.49	2.59	2.63	8.87
NF at ADC output (dB)	2.26	3.06	3.54	3.68	2.82
Front-end NF (dB)	1.51	1.51	1.51	1.51	1.51

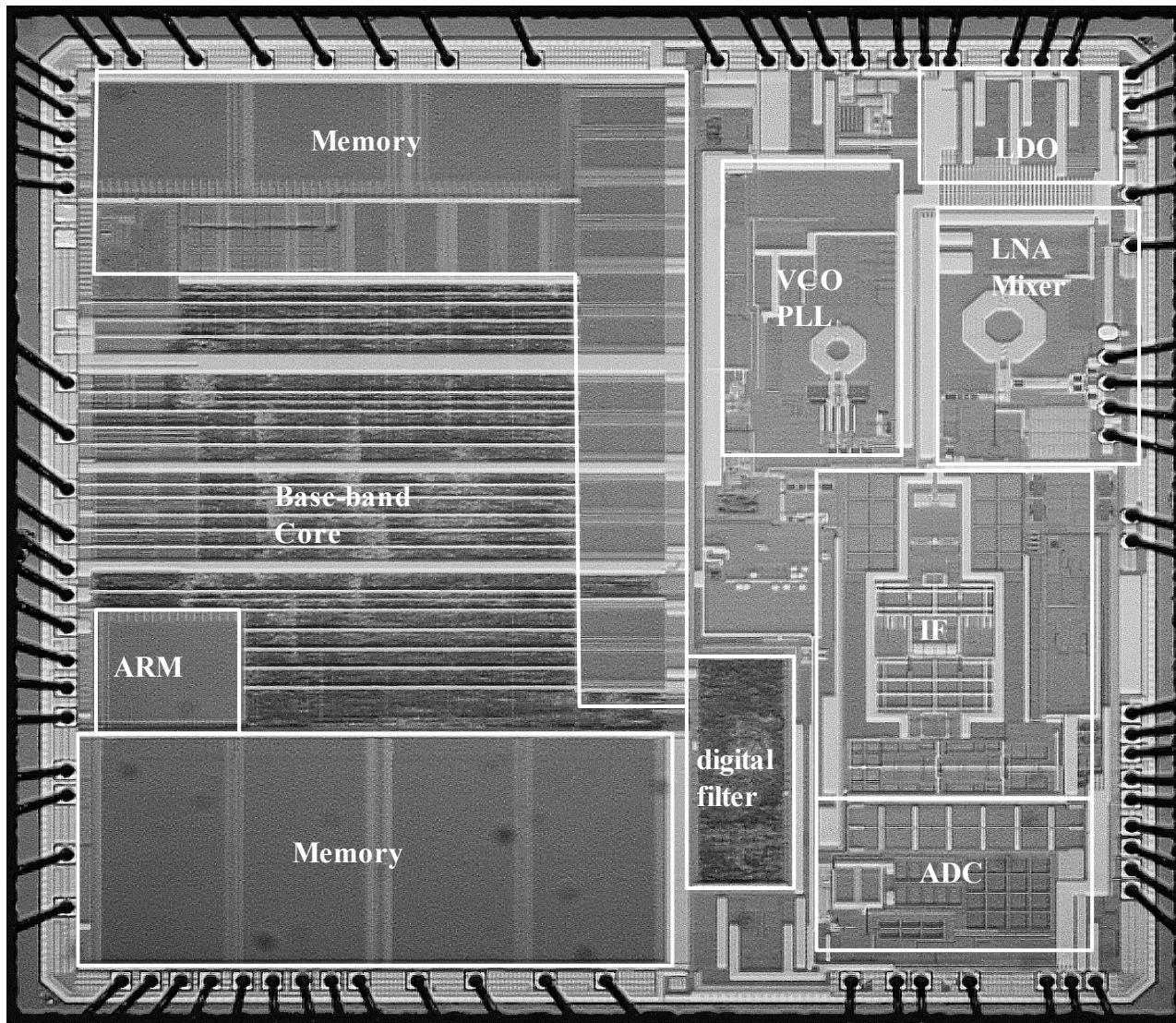
- NF at ADC output is degraded due to high speed digital output
- NF from base-band is better as digital test buffers are off
- NF within the narrow bandwidth of base-band filter is good
- Indicates substrate coupling does not degrade the RF performance



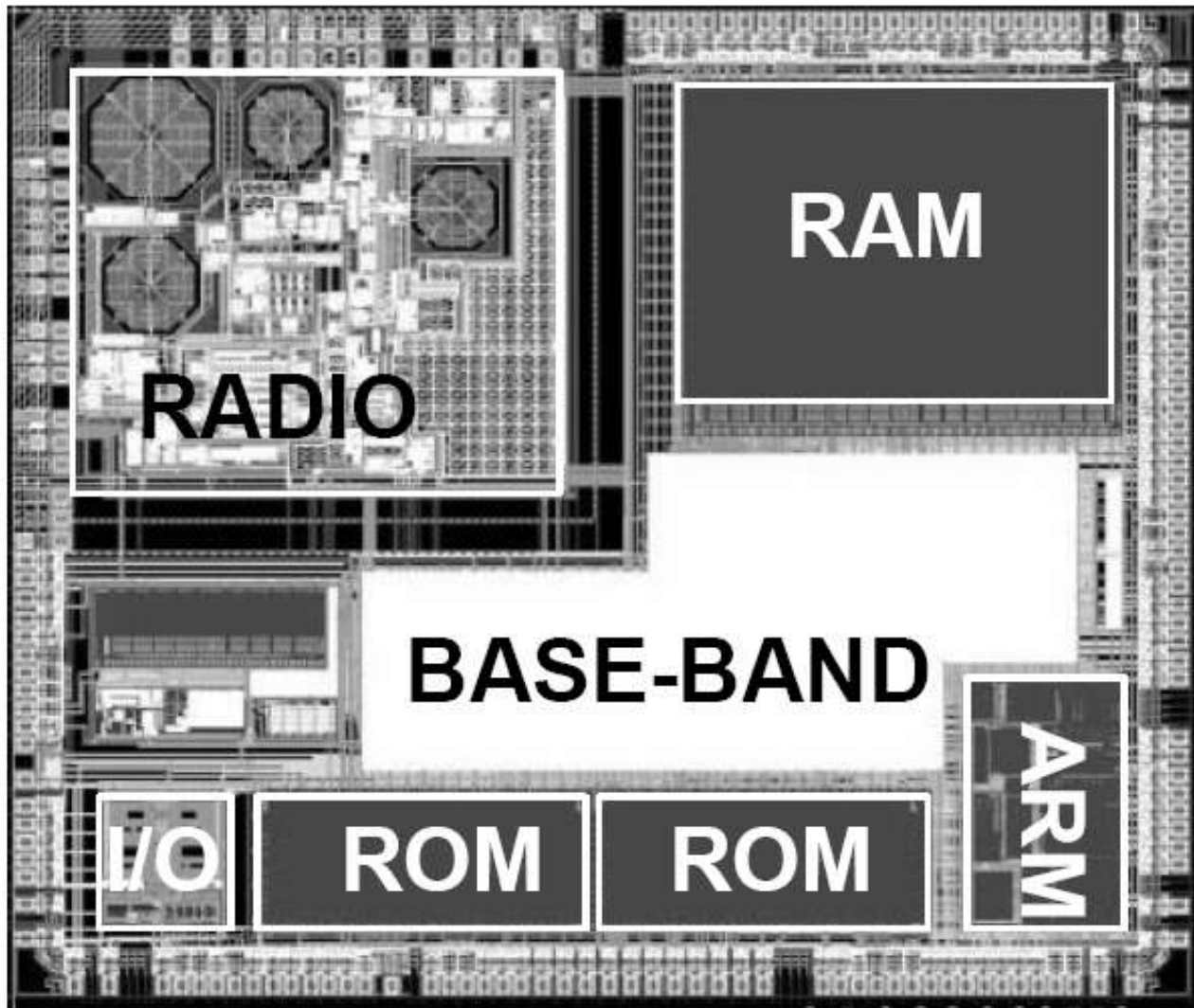GPS Receiver – Texas Instruments
13 mm² – 0.09 μM CMOS (2005)



 **Single-chip GPS receiver ST-Microelectronics
23 mm² – 0.18 μ M CMOS (2004)**



Single-chip GPS Receiver - Sony Corporation
40 mm² - 0.18 μM CMOS (2004)

Conclusion

- **It is possible to get high-performance SoC for complex functions.**
- **Effective isolation methods are necessary before such SoC products can be widely used.**
- **Shifting analog gain and processing into digital domain is still necessary for SoCs.**
- **Regular 90nm CMOS process can still be used, provided design innovations address the shortcomings.**

Open Problems

- **Power dissipation** and power-density is high.
- **Thermal issues** – too much heat generation.
- **Isolation issues** – Getting enough isolation is still a black-magic art. Modeling & design methods need to improve, so that it can be routinely achieved.
- **New architectures** that use wider bandwidth (faster transistors, but lower capacitance and area are needed).
- **Driving interfaces takes power** – be it air-interface or off-chip interfaces. RF power amplification needs to be effectively addressed.

References

- **A 23mm² Single-Chip 0.180μm CMOS GPS Receiver with 28mW- 4.1 mm² Radio and CPU/DSP/RAM/ROM**
- G.Gramegna, M.Losi, P.Mattos, S.Das, M.Franciotta, N.G.Bellantone, M.Vaiana, V.Mandara, M.Paparo.
IEEE CICC 2004,
- **A Complete Single-Chip GPS Receiver With 1.6-V 24-mW Radio in 0.18-μm CMOS**
- Takahide Kadoyama, Norihito Suzuki, *Member, IEEE*, Noboru Sasho, Hiroshi Iizuka, Ikuho Nagase, Hideaki Usukubo, and Masayuki Katakura, *Member, IEEE*
- IEEE JSSC, VOL. 39, NO. 4, APRIL 2004

References

- **A Fully-Integrated GPS Receiver Front-End with 40mW Power Consumption**
- Michiel Steyaert, Philippe Coppejans, Wouter De Cock, Paul Leroux, Peter Vancorenland
- ISSCC 2002 / SESSION 24 / RF SYSTEMS / 24.1