

Two Zero Two Pole Active Compensation Replaces a Charge Pump and Regulator in PLLs 6-25-08

Stanley J. Goldman
Texas Instruments




Agenda

- PLL Review
- Various Loop Filters
- 2 Zero 2 Pole Plots and Equations
- 2 Zero 2 Pole Results



PLL Basic Block Diagram

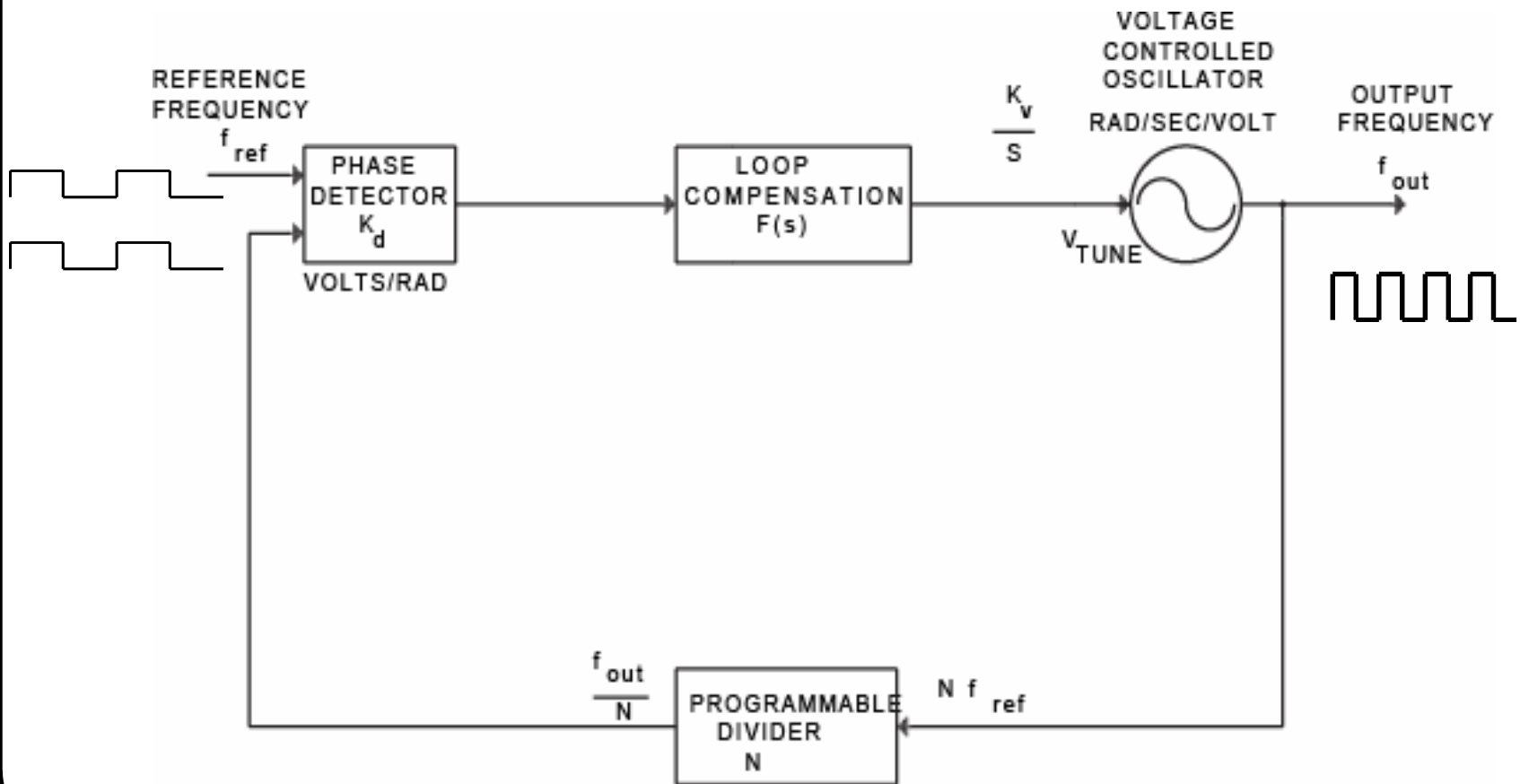
Input Phase Transduced to Voltage and
Voltage Transduced to Output Phase



Ideal VCO Transfer Function, Transduces Voltage to Frequency (Edges)

$$\omega_{out} = \omega_{off} + K_v V_{tune}$$
 
$$\omega_{out} = \Delta\theta_{out} / \Delta t$$





Tune Voltage (V)

Wireless




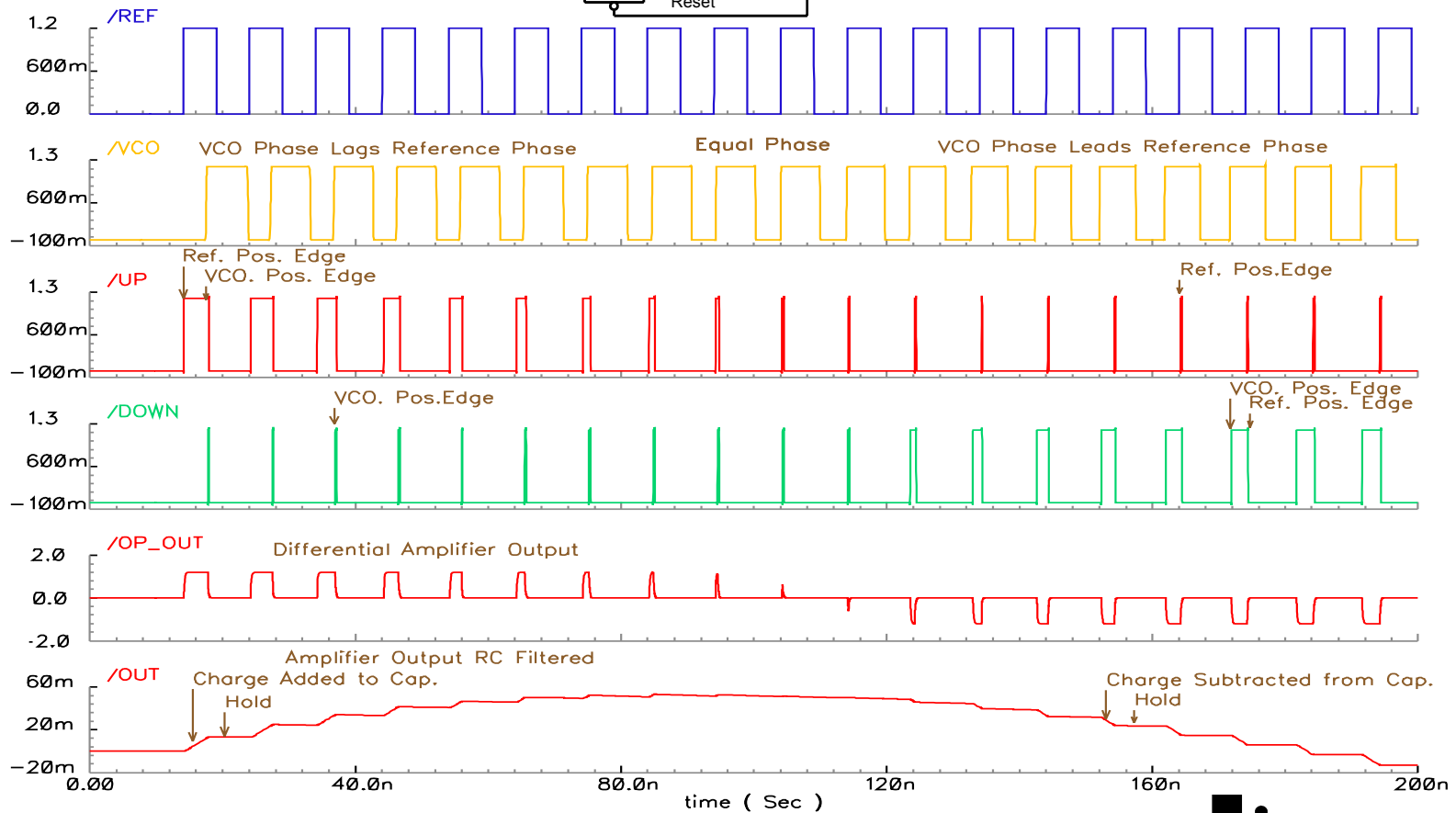 Digital Phase Detector Timing and Response to Ramped VCO Phase




Ideal Phase Detector Transfer Function, Transduces Frequency (Edge) Differences to Voltage

 
$$V_{pd_avg} = K_d \theta_e \text{ (5MHz Ref. Freq.)}$$






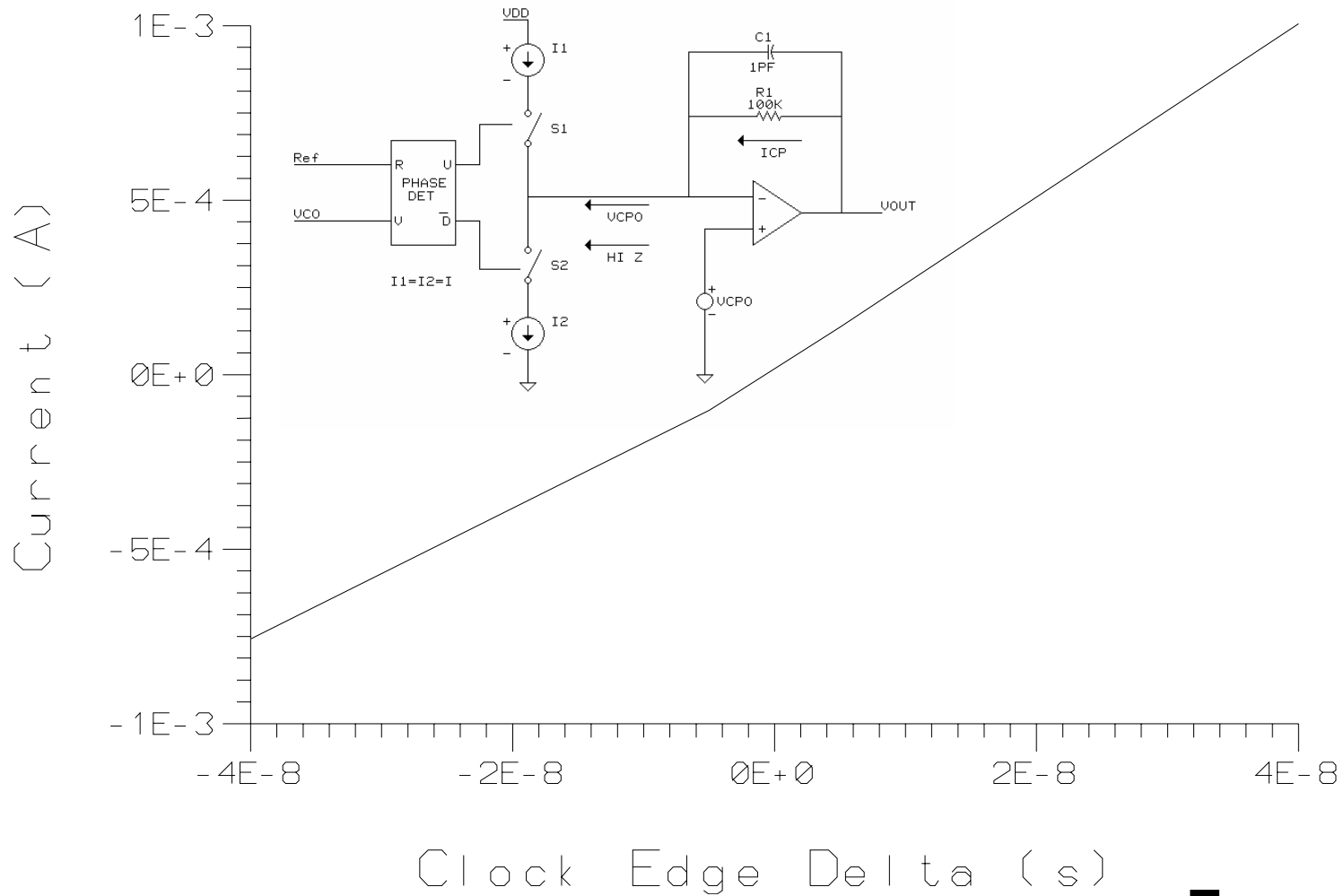
Charge Pump Output Transduces Frequency (Edge) Differences to Current, $K_p = I / (2 \pi)$



Example of Lock, Digital Loop (In Phase)

 

Loop Classifications

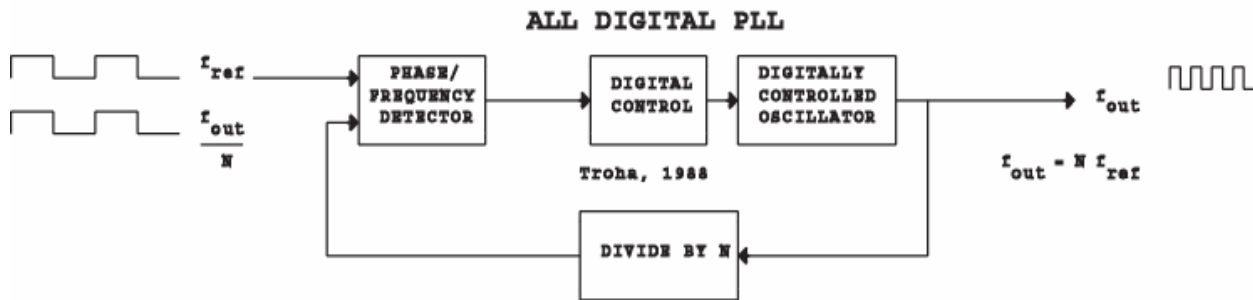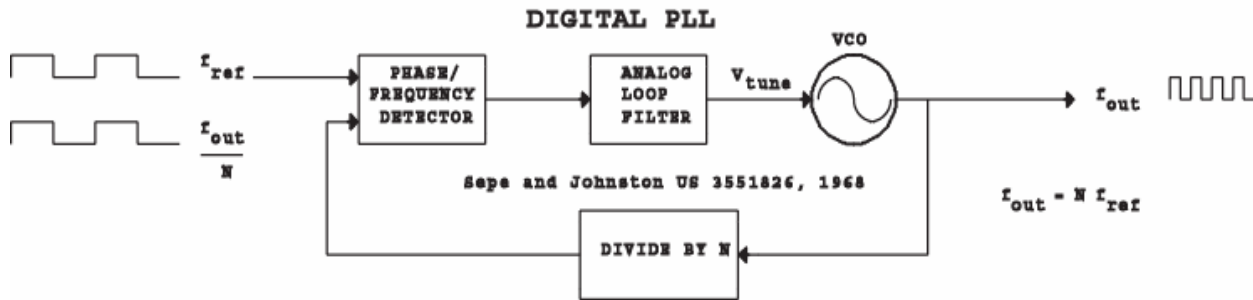 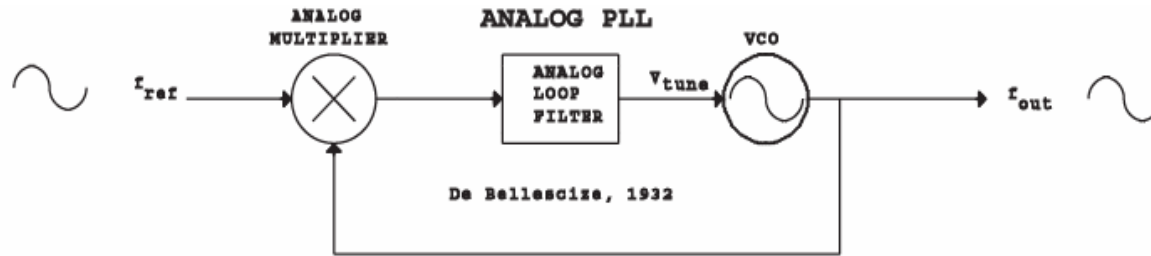


Comparison of PLL Loop Filters with Regulators driving VCO

- Charge pump PLL
- Replica Bias PLL
- Digital PLL
- 1 Zero Active PLL




Charge Pump PLL with Regulator

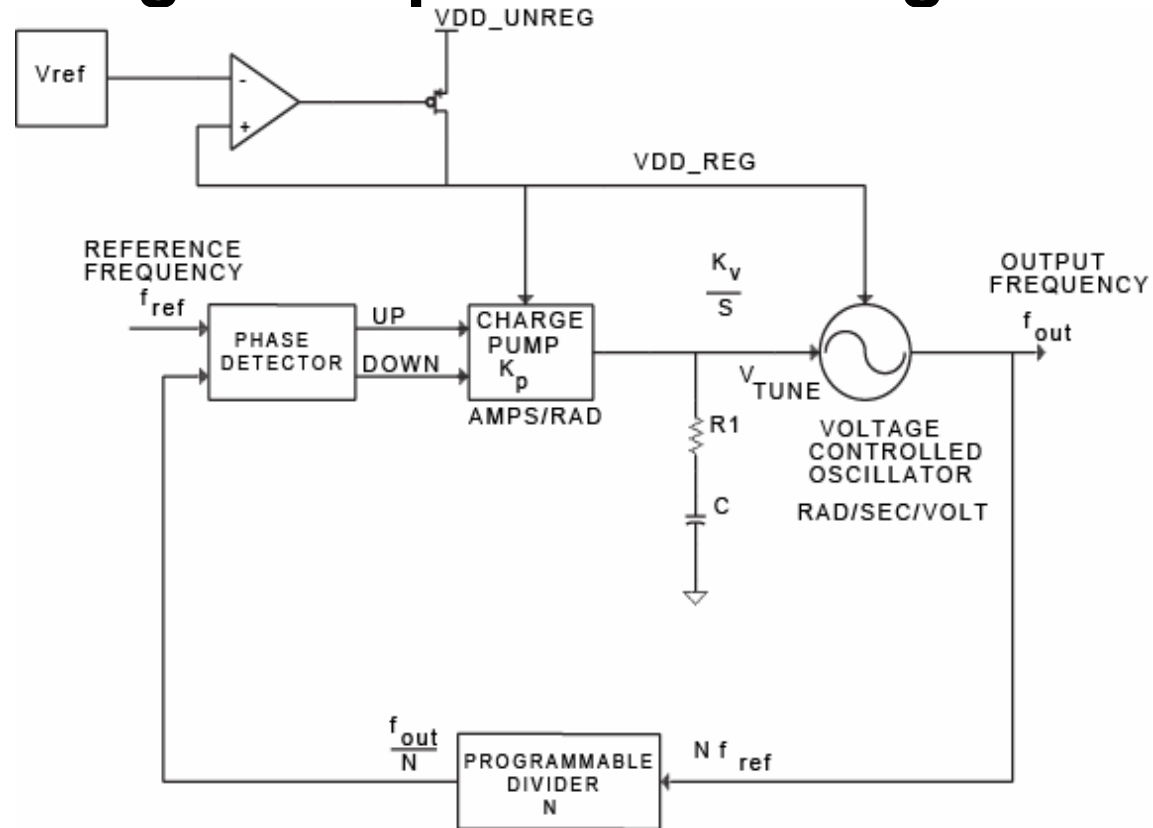

- Charge pump can not drive high current load
- 1 pin for external components

Replica Biased Charge Pump PLL

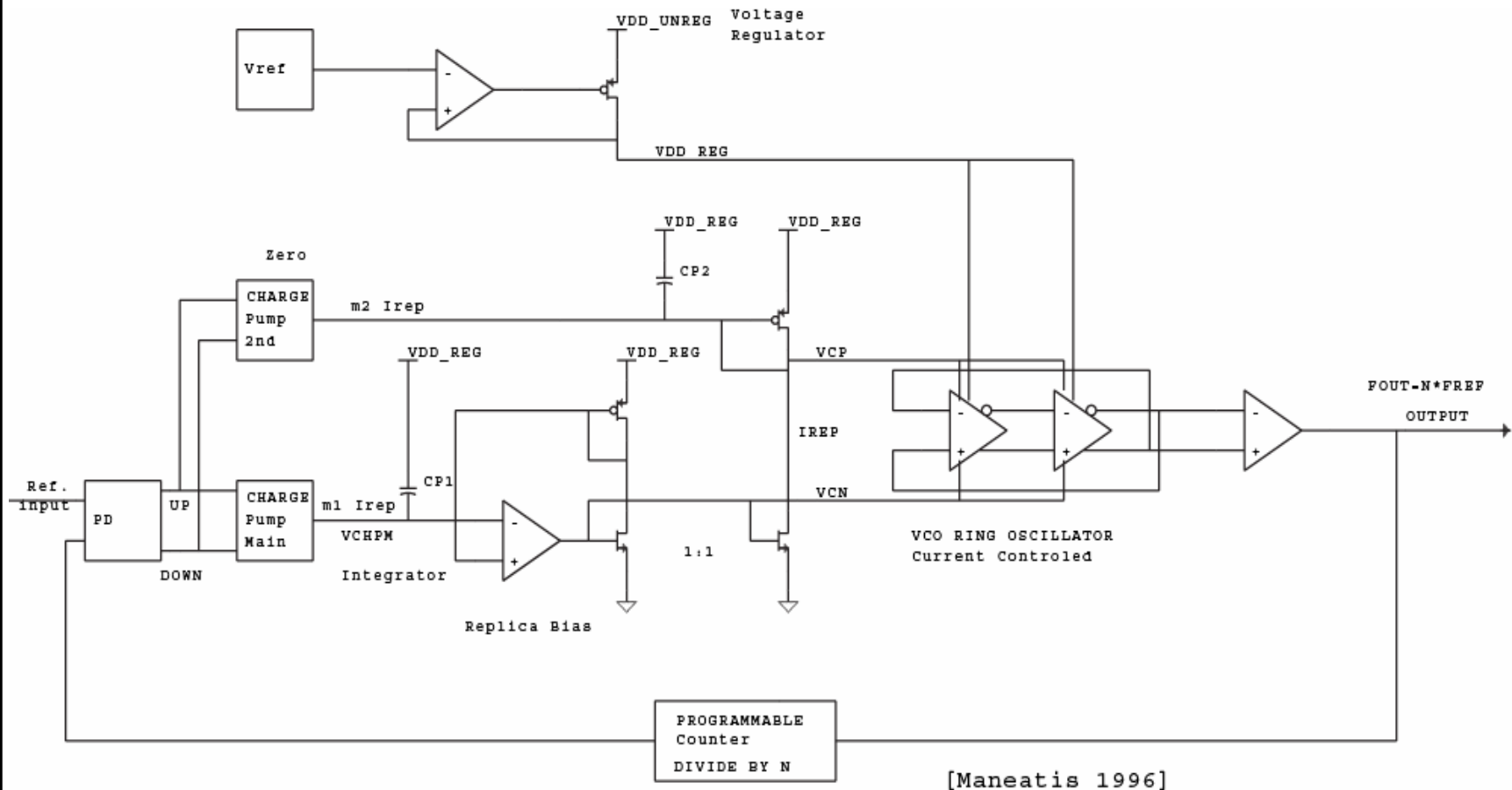


Advantages/Disadvantages

- Widely used for many years and many designs
- High sensitivity to power supply at regulator output
- Narrow frequency tuning range (~200mV for nano scaled devices)
- Low output voltage swing to differential to single ended converter (50mVpp)
- Narrow output voltage range for charge pump (~200mV for nano scaled devices)
- Differential ring stops oscillating

Wireless




All Digital PLL with Regulator

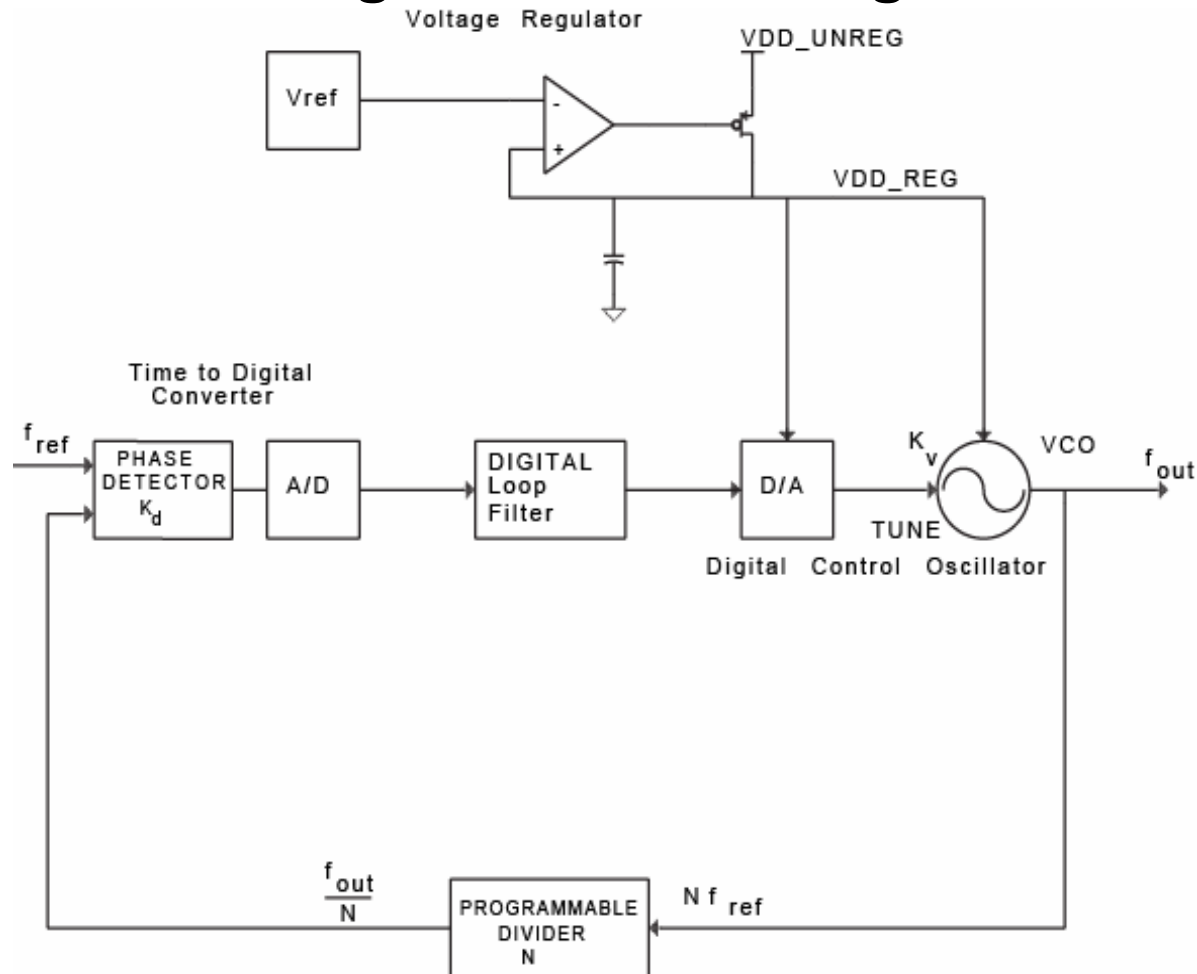

- Sensitivity to power supply
- Not state of the art performance in power, area, and noise? trade offs
- Leakage does not change frequency

1 Zero Active Compensation

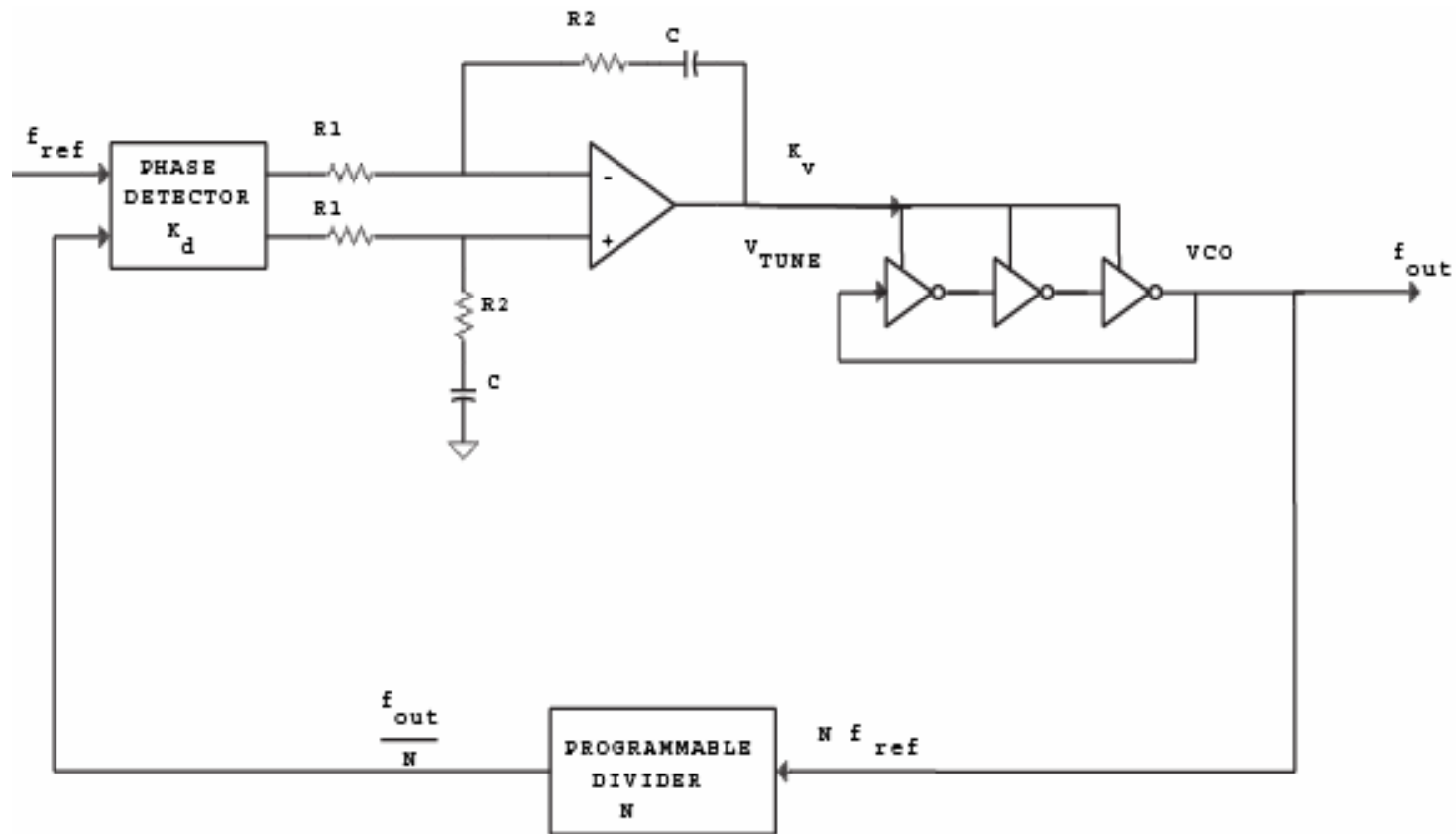

1 Zero, Type 2 Second Order Open Loop Gain Function (Active Filter)

Cascade of Transfer functions for Open Loop Gain

$$G(s)H(s) = (\text{Phase Detector Gain})(\text{Filter Transfer Function})(\text{VCO Transfer Function})(\text{Divider Transfer Function})$$

Substitute and Rearrange for Open Loop Gain Expression

$$G(s) \cdot H(s) = \frac{K_d \cdot K_v}{n_{mf} \cdot C \cdot R_1} \cdot \left(\frac{1}{s^2} \right) \cdot (s \cdot C \cdot R_2 + 1)$$


Substitute and Rearrange for Closed Loop Gain Expression

$$\frac{G(s)}{1 + G(s) \cdot H(s)} = \frac{\frac{K_d \cdot K_v}{C \cdot R_1} \cdot \left[\frac{s}{\left(\frac{1}{C \cdot R_2} \right)} + 1 \right]}{s^2 + s \cdot \left(\frac{K_d \cdot K_v \cdot R_2}{n_{mf} \cdot R_1} \right) + \frac{K_d \cdot K_v}{n_{mf} \cdot C \cdot R_1}}$$

K_d = Phase detector gain (volts/radian),
 = VCO transfer function gain constant (radians/second/volt),
 n_{mf} = Integer divider value,
 = Loop Frequency Multiplication Factor,
 = Output frequency/ input frequency,

C = Capacitor in the operational amplifier's feedback path (F),
 R_1 = Resistor in operational amplifier's feedback path (ohms) and,
 R_2 = Resistor at the negative input terminal of the operational amplifier (ohms).

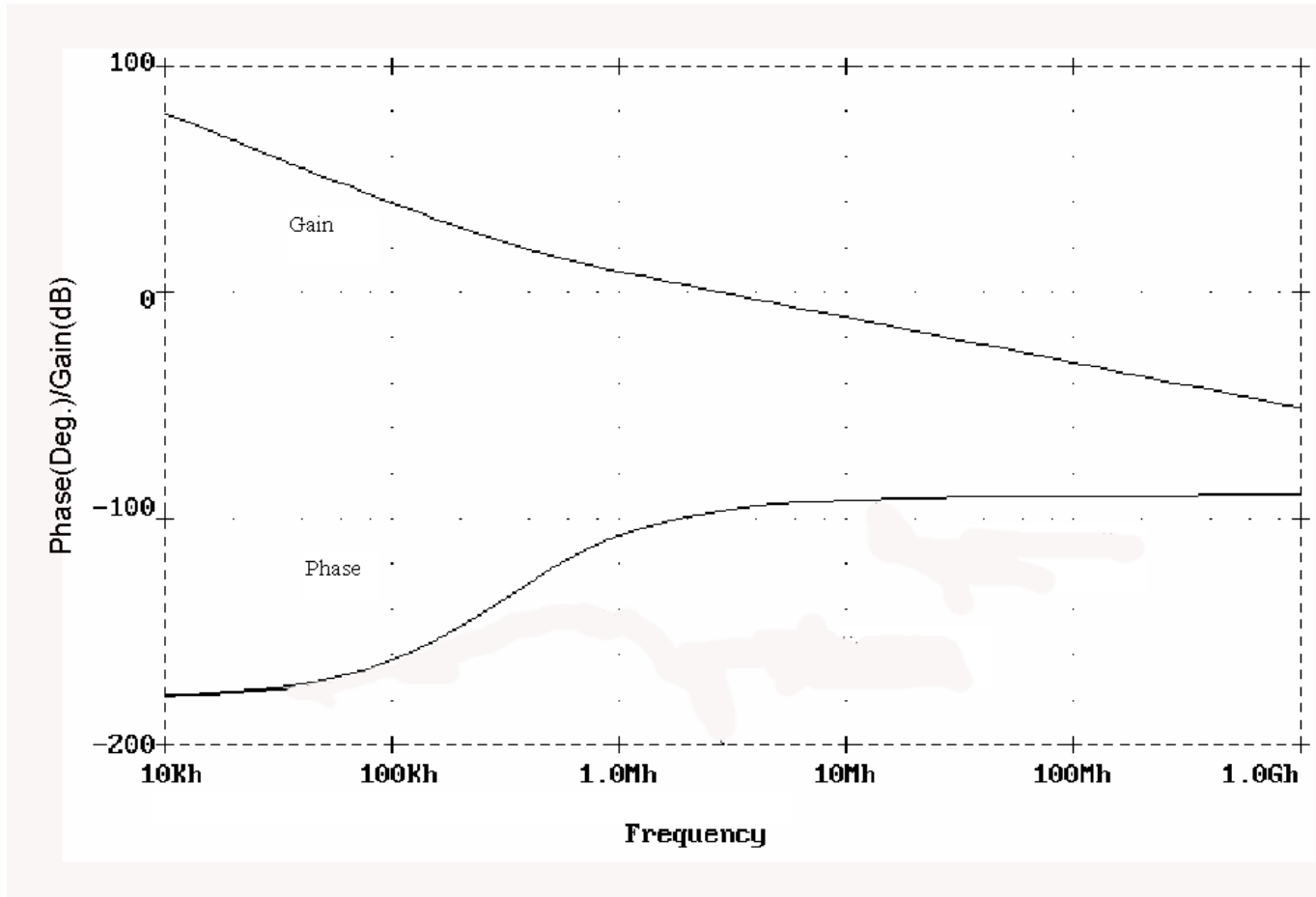
Uncentered Type 2 1 Zero Open Loop Magnitude and Phase, 1MHz Bandwidth example




Advantages of 2 Zero 2 Pole Compensation

- OPAMP Replacing a Charge Pump
 - Wider Supply Operating Range, Rail to Rail
 - Lower Voltage drop out
 - Linear Differential to Single Ended Conversion
 - Sources VCOs that draw current
 - No power down resets
 - Acts as voltage regulator to minimize sensitivity to power supply
 - Flexibility in Compensation Polynomials
- 2 Zero 2 Pole Compensation
 - >90 deg. Added to Phase Margin
 - Wider Bandwidth
 - Wider and Optimum Stable Region for less process sensitivity

 
Desired high phase boost example of 2 zero 2 Pole magnitude response for compensation only and phase margin greater than 90 degrees, 10kHz BW Example



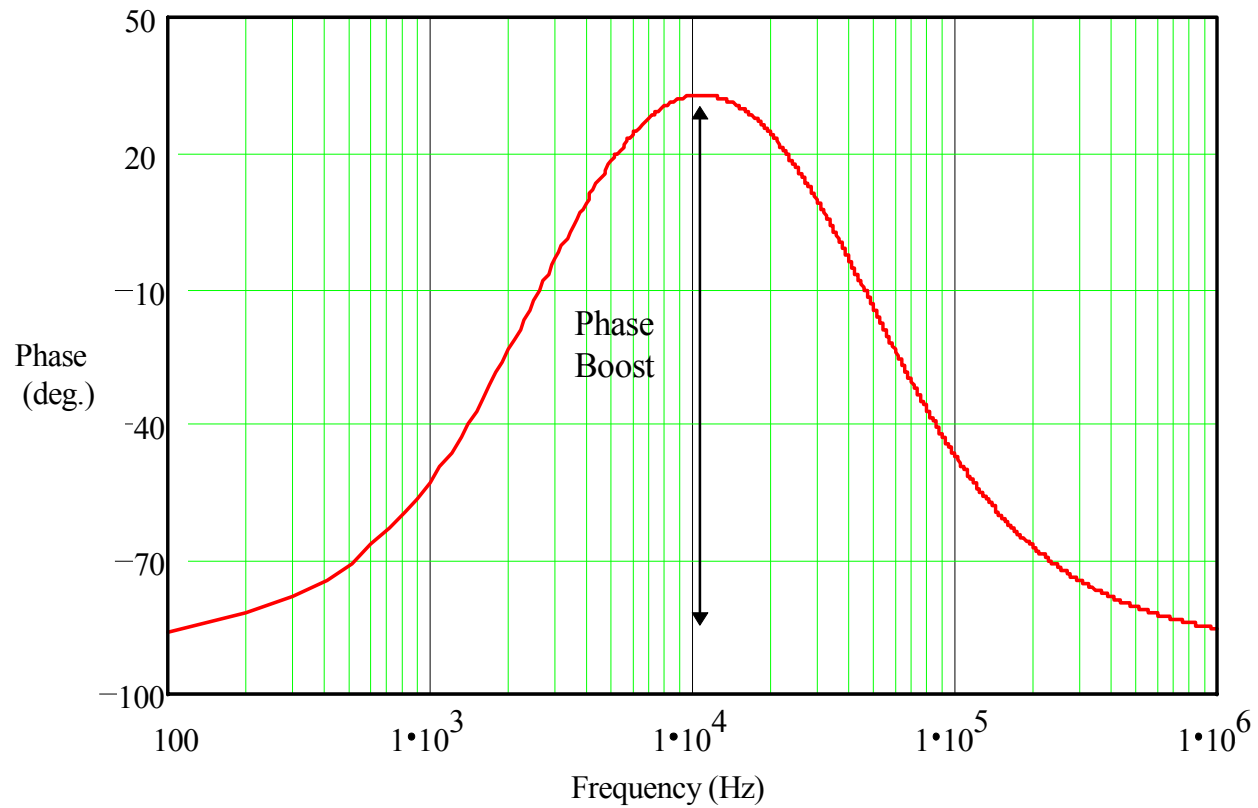
Desired 2 Zero Phase Response for Compensation Only for Phase Margin Greater Than 90 degrees (120 deg), 10kHz BW Example



 
RC +90% and -50% process variation, shows PLL bandwidth insensitivity with 0.7 Damping factor and Symmetric centering of the poles and zeroes



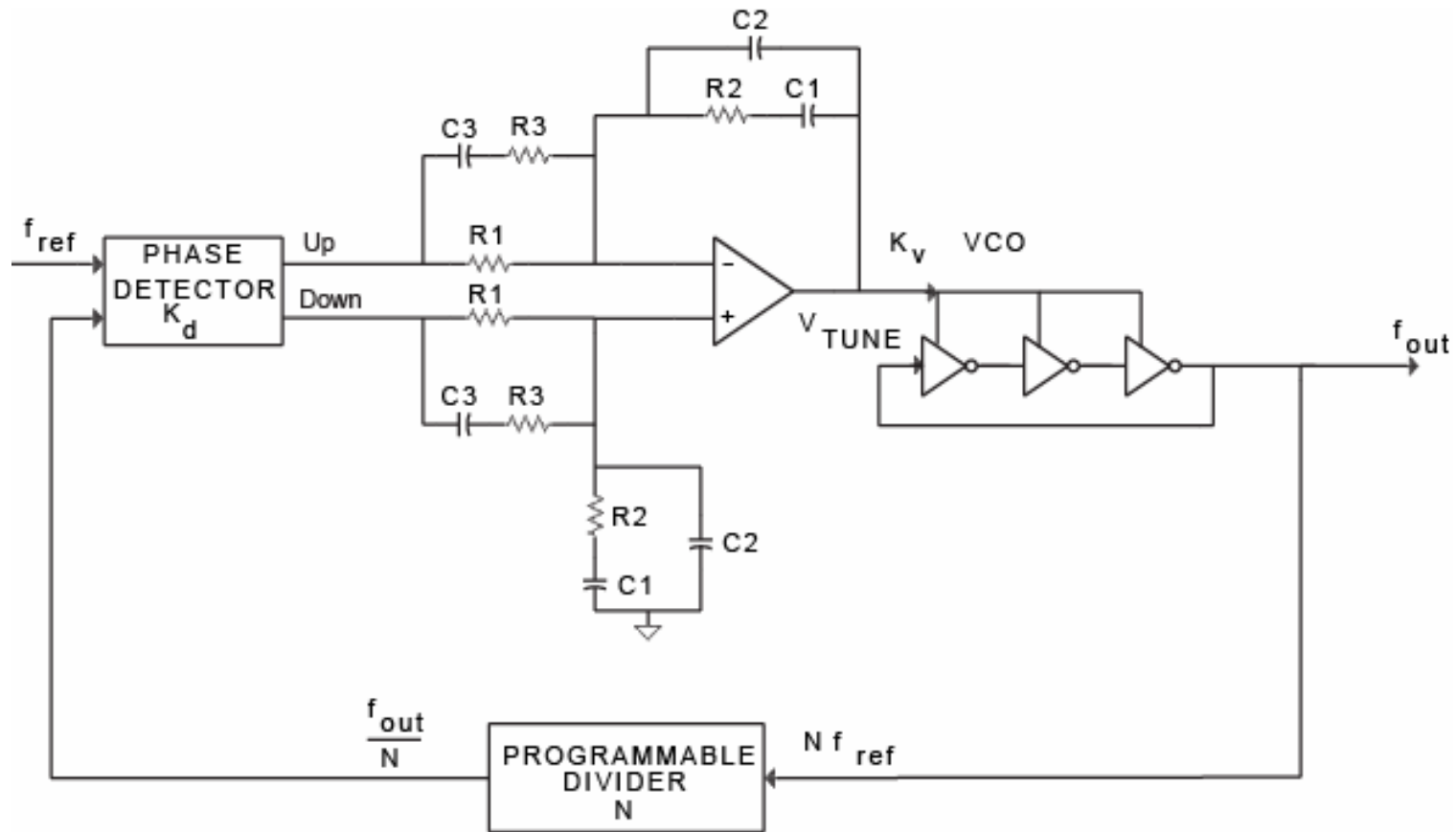PLL connection for a type 2 and 2 zero loop compensation.



VCO Description

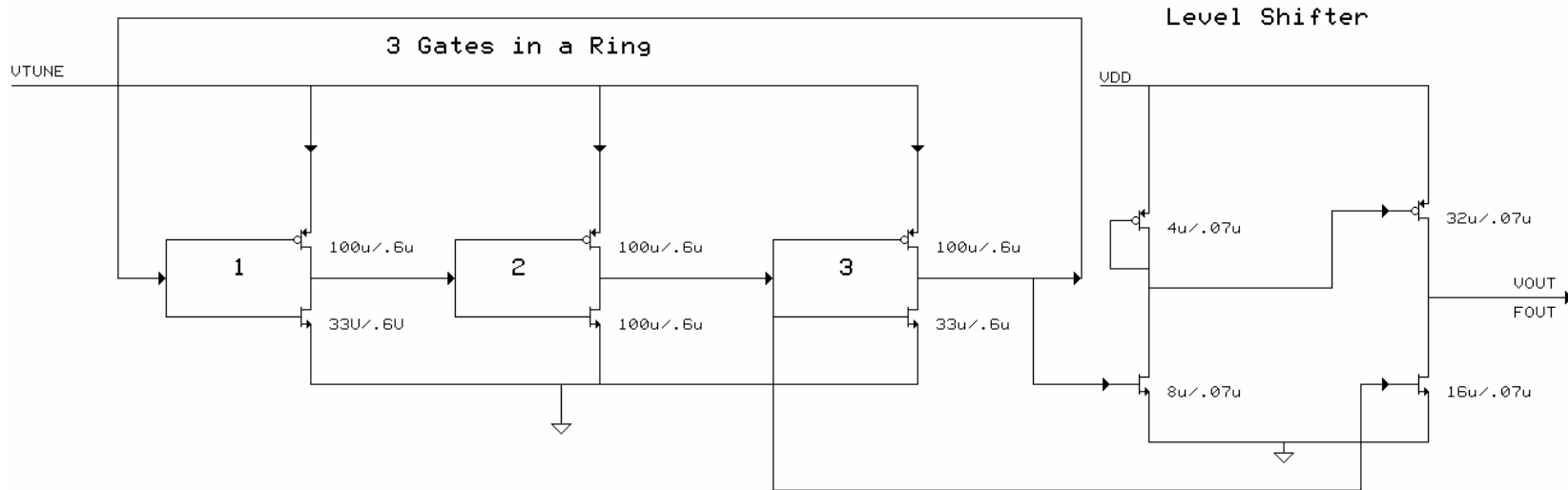

2 Zero 2 Pole Open Loop Transfer Function Equations


$$\frac{V_o}{V_i} = \frac{1}{s \cdot (C_1 + C_2) \cdot R_1} \cdot \frac{s \cdot C_1 \cdot R_2 + 1}{1 + s \cdot R_2 \cdot C_2} \cdot \frac{s \cdot (R_1 + R_3) \cdot C_3 + 1}{s \cdot R_3 \cdot C_3 + 1}$$

$$k = \tan \left(\frac{\phi_{\text{boost}}}{4} + 45 \right)^2$$


$$\frac{V_o}{V_i} = \frac{1}{\left(\frac{s}{\omega_x \cdot \frac{G_x}{k}} \right)} \cdot \frac{\left[1 + \frac{s}{\omega_x} \right] \cdot \left[1 + \frac{s}{\omega_x} \right]}{\left(1 + \frac{s}{\omega_x \cdot \sqrt{k}} \right) \cdot \left(1 + \frac{s}{\omega_x \cdot \sqrt{k}} \right)}$$

$$G_x = \frac{1}{\left(\frac{K_d \cdot K_v}{N \cdot \omega_x} \right)}$$

 
Magnitude response of 2 zero compensation solution to the design



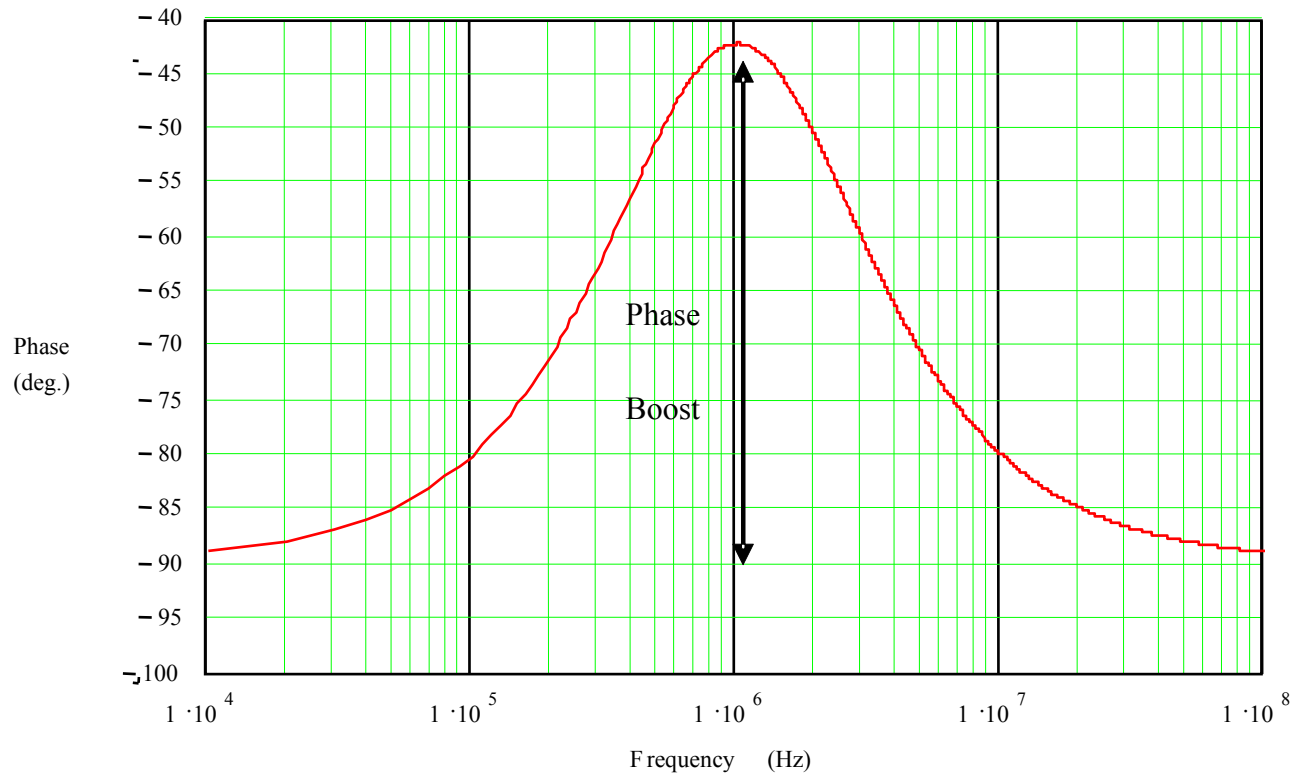
Open loop phase response with type 2 and 2 zero compensation.



 
Open loop magnitude response with type 2 and 2 zero compensation



 
C021 Die photo of the PLL circuit, $300 \times 200 \mu\text{m} = 0.06 \text{mm}^2$



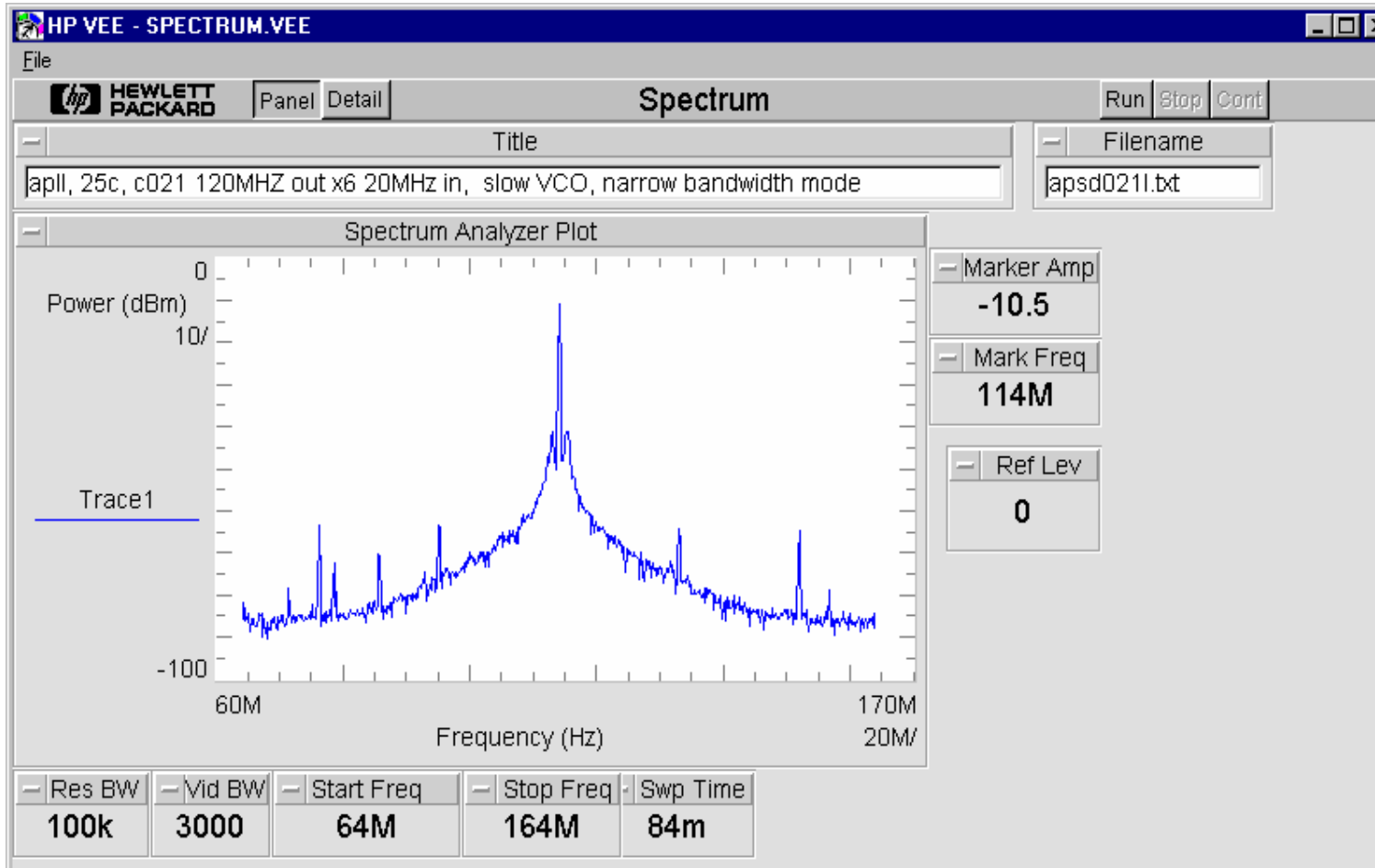
Measured Data Spectrum, Reference Sidebands <-60dBc



Measured Data Jitter <80ps peak to peak

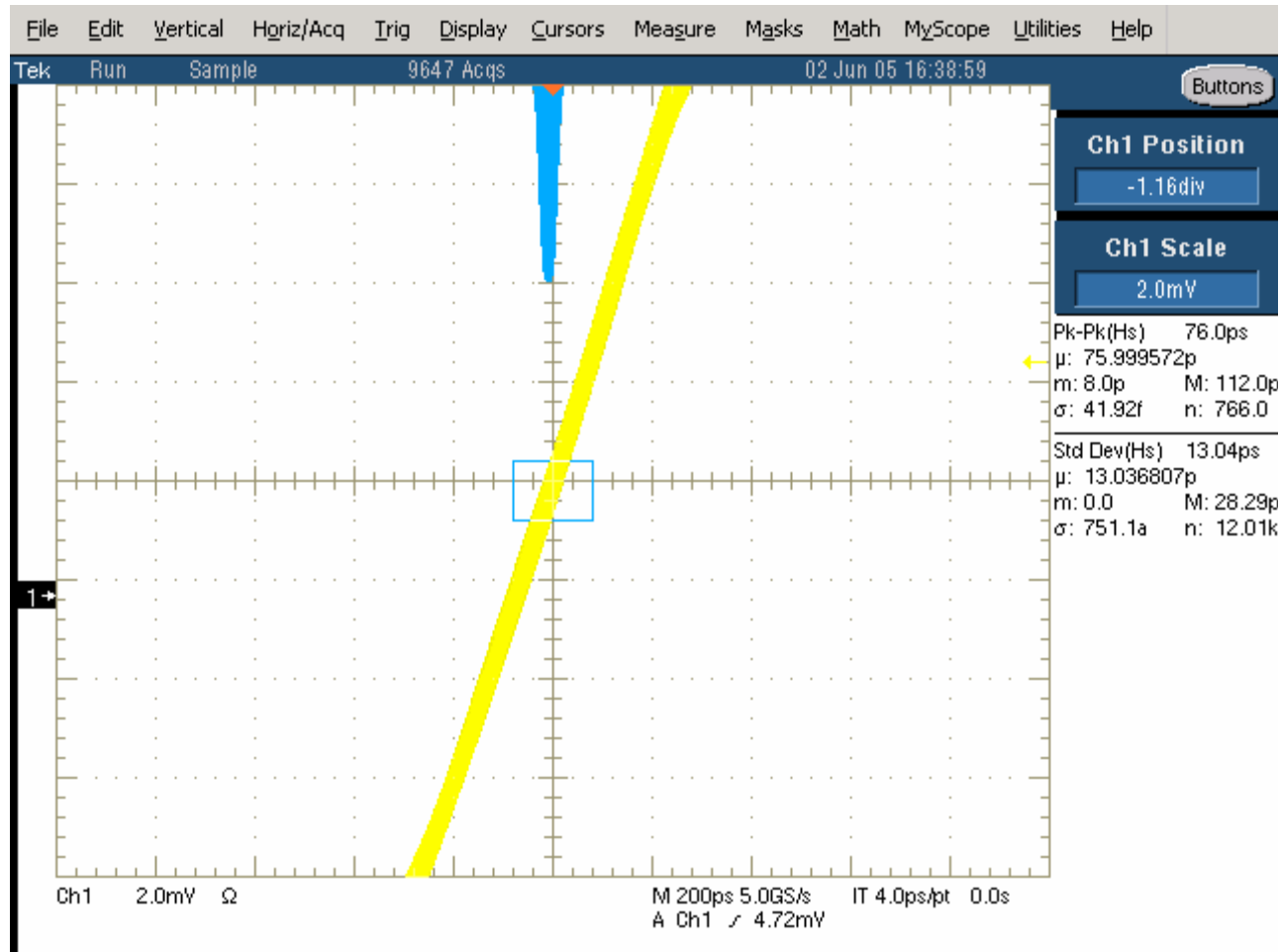

 Measured Phase Noise, 1MHz Bandwidth, -92dBc/Hz Phase Noise at 1MHz, High Phase Margin, Low additive Noise



Wireless



Comparison Table of Measured Data with Comparable PLL References

Description	Processes	Power	Area (mm ²)	VCO Output Frequency (MHz)	Jitter	power supply sensitivity, %-fvco/%-Vdd	Comments
S. Sidropoulos VLSI '00	.35um 3.3V	21.5mW@500MHz	0.047	30-650		.06%/1%	Simulated, Supply Controlled Ring VCO, wide BW
J.M. Ingino ISSCC '01	.15um 3.3V	132mW@4GHz	1.48	600- 4000	44ps p-p at 700MHz	.007%/1%	Regulator included, single ended ring CCO
H. Ahn JSSC '00	.25um 1.9V	25mW@320MHz	0.087	17-1320		.32%/1%	Supply Controlled Ring VCO, wide BW, 2.5MHz BW
K. Minami CICC '01	.1um 1.2V	30mW at 2000MHz	0.15	500-2350	21ps p-p		Single ended ring CCO
Maneatis ISSCC '03	.13um 1.5V	7mW at 240MHz	0.18	30-650	48ps p-p		Differential ring VCO, self biased
Hozer ISSCC '02	.13um 1.5V	7mW at 200MHz	0.16	10-350	155ps p-p 360MHz		Differential ring VCO, VCR
Fahim TCAS '03	.25um 1.9V	3.12mW at 160MHz		30-160	130ps p-p		All Digital PLL, diff. ring VCO
This work APLL	.065um 1.2V	1mW at 240MHz	0.06	12-600	80ps p-p	.02%/1%	

References,

1. Stanley Goldman, *Phase Locked Loop Engineering Handbook*, Artech House, Boston, 2007.
2. Roland Best, *Phase Locked Loops Design Simulation, & Applications*, McGraw Hill, New York, 1997.
3. Behzad Razavi, *Monolithic Phase-Locked Loops and Clock Recovery Circuits*, IEEE Press, New York 1996.
4. William Egan, *Frequency Synthesis by Phase-Lock*, Wiley Interscience, New York, 1981.
5. Floyd Martin Gardner, *Phaselock Techniques*, Wiley Interscience, New York, 1979.

Key Points

- Voltage Regulator can be incorporated into loop compensation (Dual Use)
- Geometrically Centered Zeroes and Poles Reduces sensitivity to R C process variations
- Increasing Resistance can be used to reduce capacitor size and overall loop size.
- Wider loop bandwidths can be achieved with 2 zeros because of the increase in phase margin.
- Widest loops give lowest phase noise for references with lower noise than the VCO
- Further future improvements can be made to reduce power, size, and area.
- Active Compensation gives flexibility in compensation