

A 410-GHz CMOS Push-push Oscillator with a Patch Antenna

Eunyoung Seok¹, Changhua Cao^{1,2}, Dongha Shim¹,
Daniel J. Arenas¹, David B. Tanner¹,
Chih-Ming Hung³, and Kenneth K. O¹

¹University of Florida, Gainesville, FL

²NXP Semiconductors, Austin, TX




³Texas Instruments Inc., Dallas, TX

Outline

- ❑ Introduction
- ❑ Push-push oscillator design
- ❑ On-chip patch antenna design
- ❑ Measurements of submillimeter-wave/THz
- ❑ Conclusions

Submillimeter-wave/THz

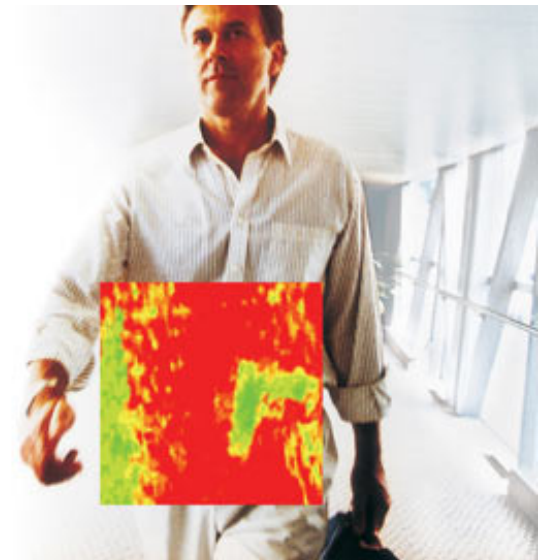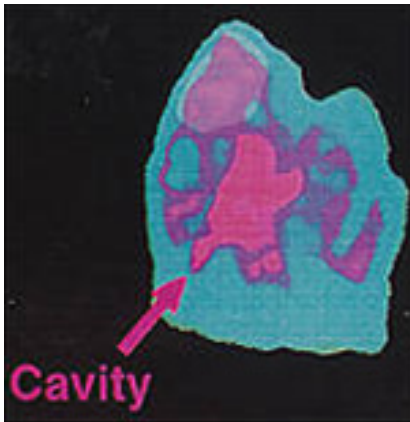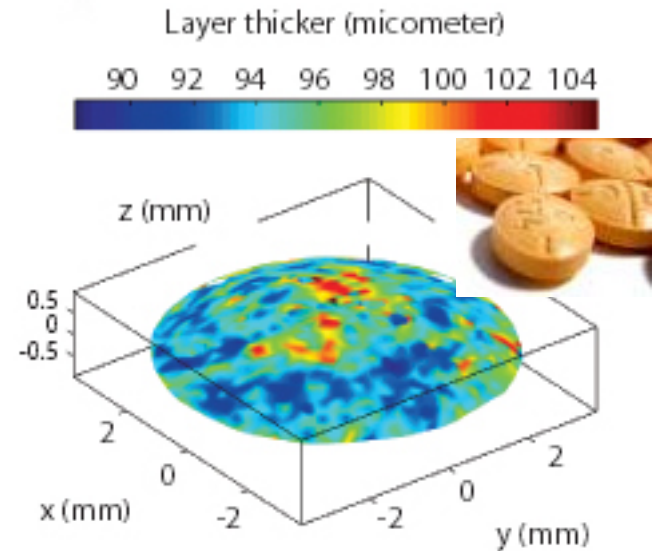- ❑ 300GHz-3THz
- ❑ The radio astronomy
- ❑ Advanced imaging, detection of concealed weapons, chemicals, bio-agents and cancers
- ❑ Non-ionizing radiation: less risk for human body




Submillimeter-wave/THz

- ❑ Compound semiconductor devices are employed.
- ❑ Industrial and commercial applications of submillimeter-wave require low cost, compact and portable systems.
 - ✓ Higher levels of integration
 - ✓ Higher yield
 - ✓ Lower manufacturing cost
 - ✓ Larger die size
- ❑ Correct imperfections of submillimeter-wave circuits using digital CMOS circuits


Push-push VCO

- ❑ Fundamental oscillator: limited by f_{\max}
- ❑ Oscillator-doubler: larger and more complex
- ❑ Push-push oscillator: compact and overcome f_{\max}


Fundamental
Oscillator

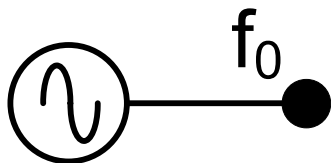

Oscillator-doubler

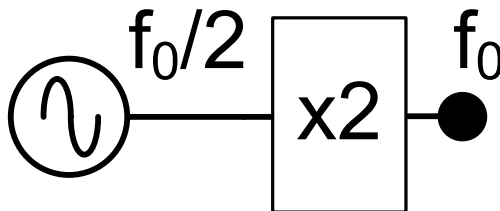


Push-push
Oscillator

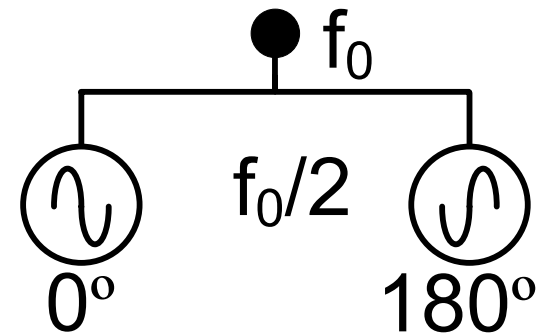


Push-push Oscillator

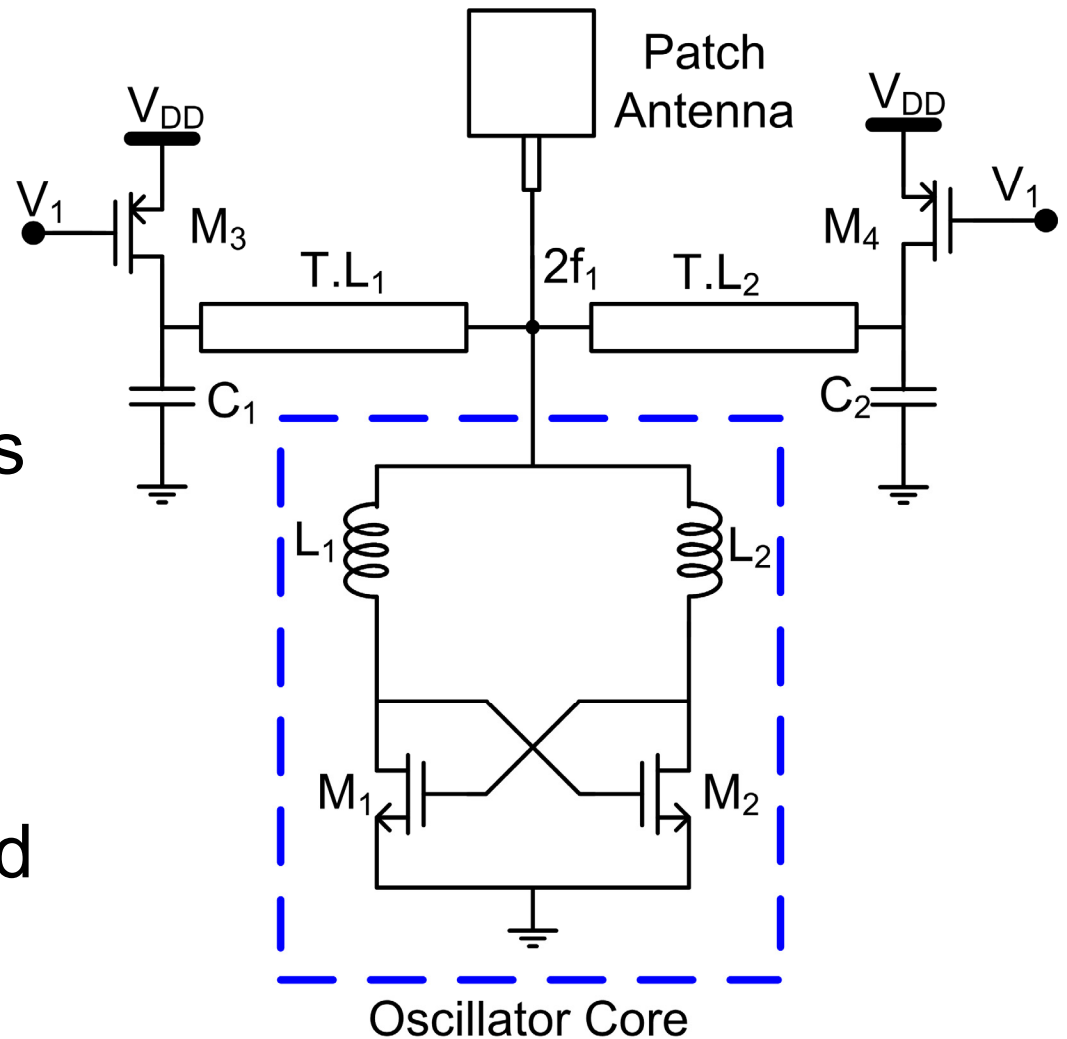- Generate differential signals and eliminates the concern for even-mode oscillation.
- 2nd harmonic is extracted and radiated through the on-chip patch antenna.




Push-push Oscillator

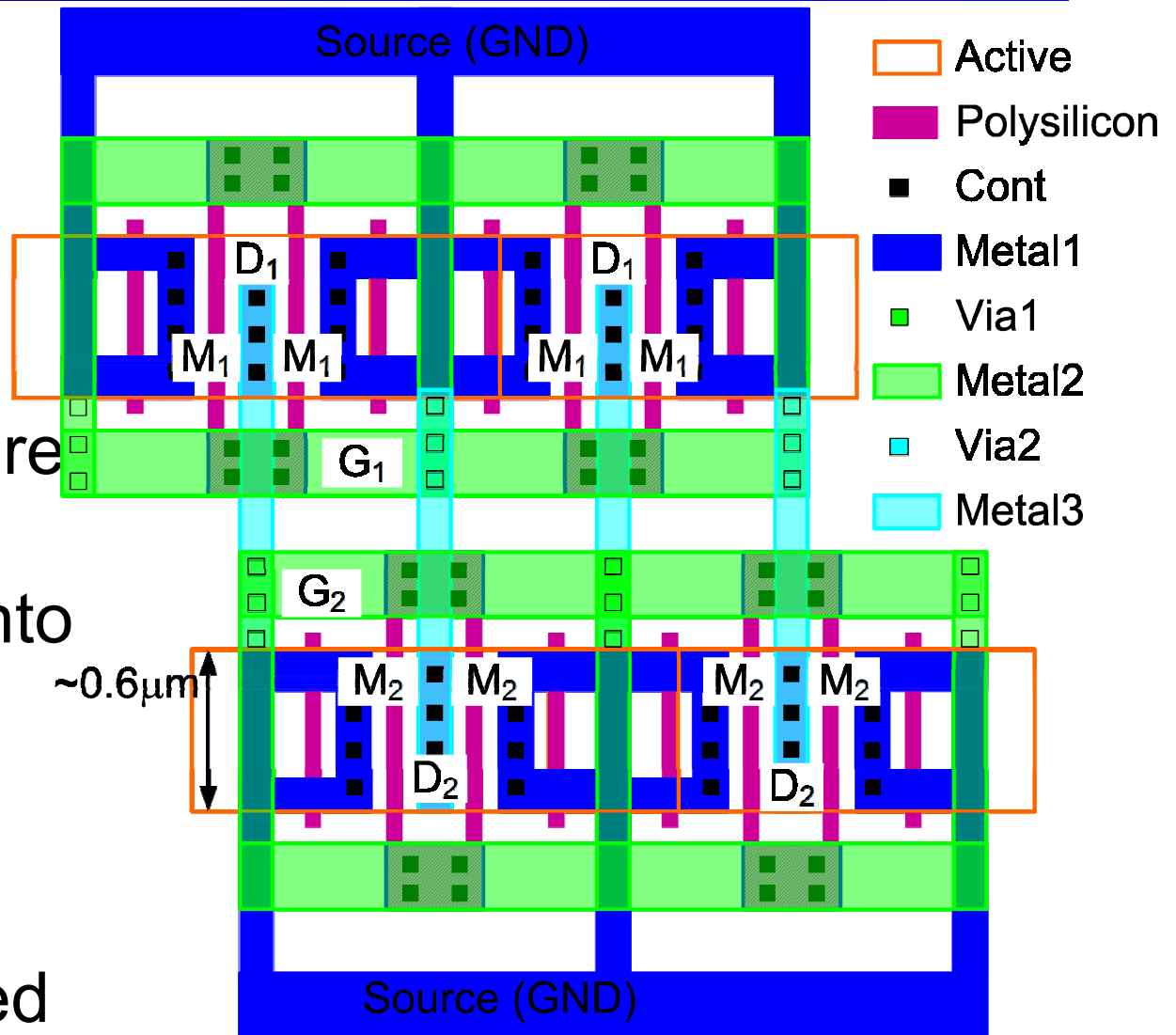- ❑ The width of the cross-coupled transistor is about $10\mu\text{m}$.
- ❑ Transistor gates are contacted on both ends and folded into multiple fingers.
- ❑ Each finger has 2 contacts on each side and connected using metal2.



Passive Device Modeling

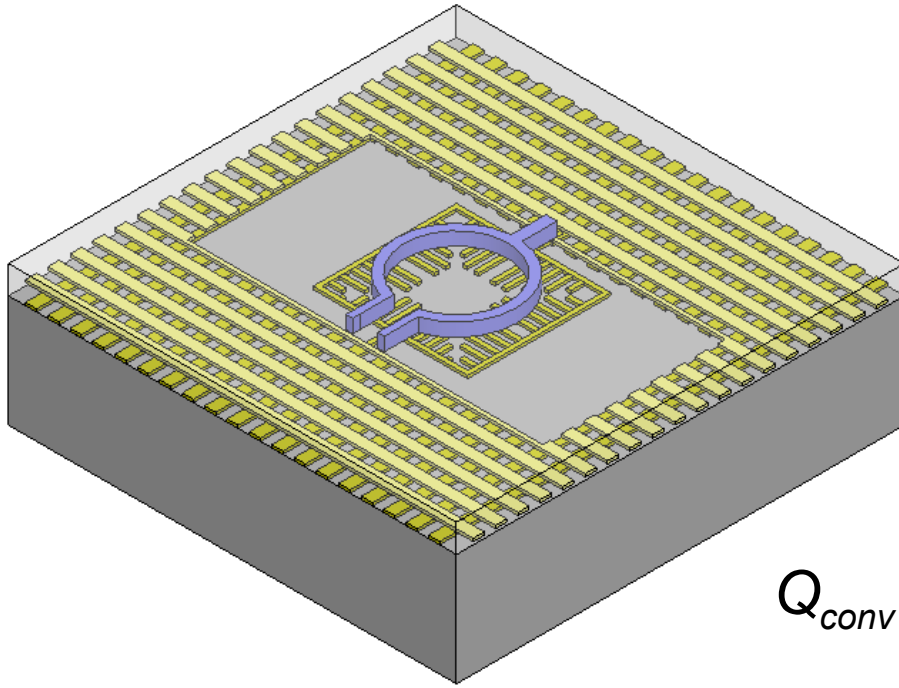


$$L_{eff} = \frac{\text{Im}(Z_{11})}{\omega} \approx 40pH$$

$$Q_{conv} = -\frac{\text{Im}(Y_{11})}{\text{Re}(Y_{11})} \approx 8 \text{ @ } 200\text{GHz}$$


- ❑ Design and optimization of inductors solely rely on the 3D EM simulator (Ansoft HFSS).
- ❑ Diameter $\sim 20\mu\text{m}$, Width $\sim 1.6\mu\text{m}$
- ❑ Inductors are 3-port devices in the simulation.

Passive Device Modeling

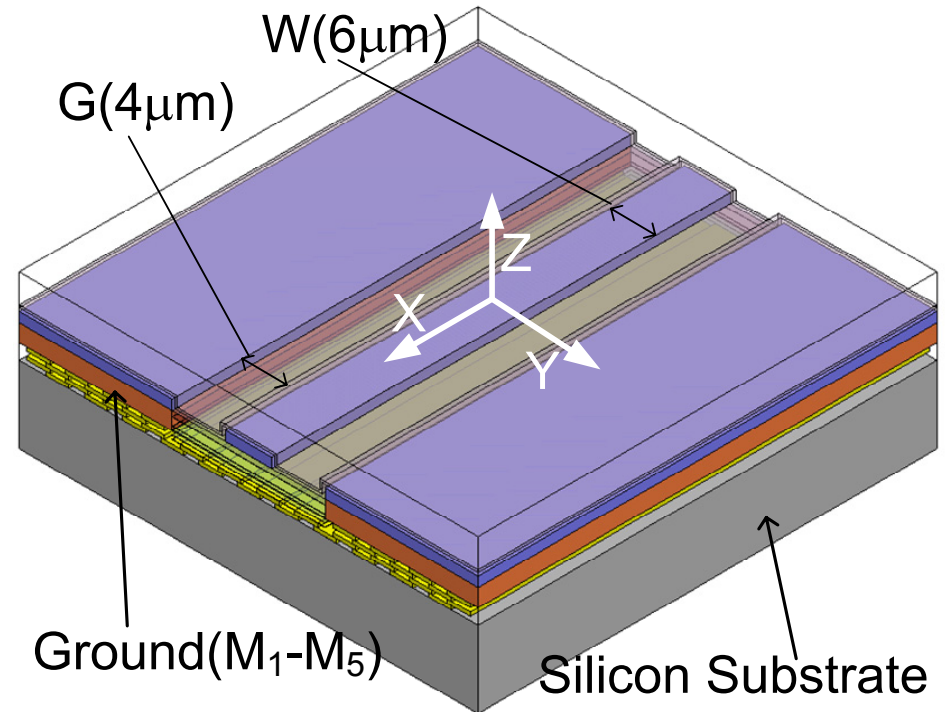- ❑ Grounded Coplanar Wave guide (GCPW)
- ❑ Confine fields relatively small area
- ❑ Reduce loss caused by substrate & interference with nearby circuits
- ❑ Loss ~ 2.5 dB/mm @400GHz
- ❑ $W=6\mu\text{m}$, $G=4\mu\text{m}$
for $Z_0 = 50\Omega$




On-chip Antenna

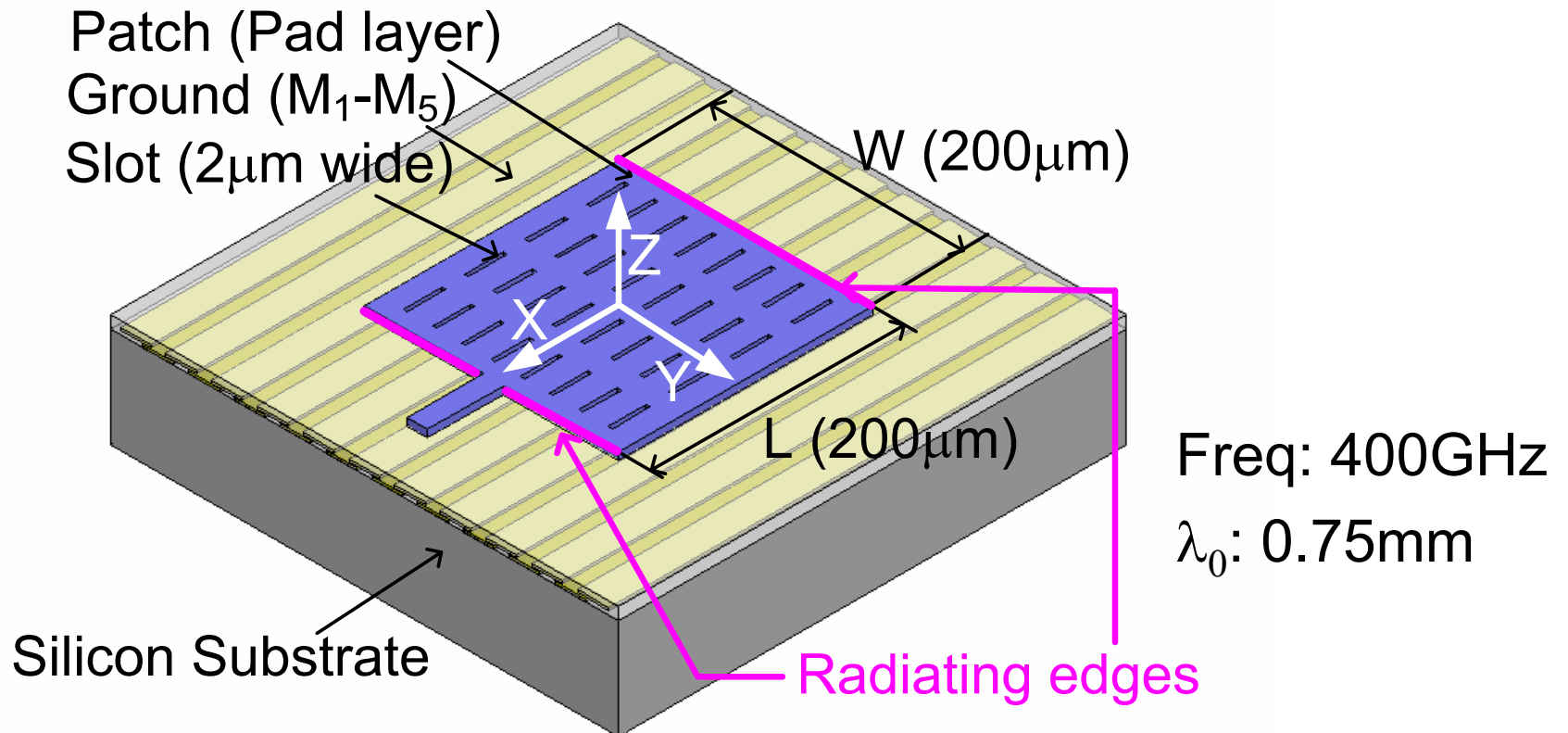


- ❑ The fringing fields at the edges are responsible for the radiation.
- ❑ The dielectric thickness between the patch and ground plane is ~4μm.

Antenna Size

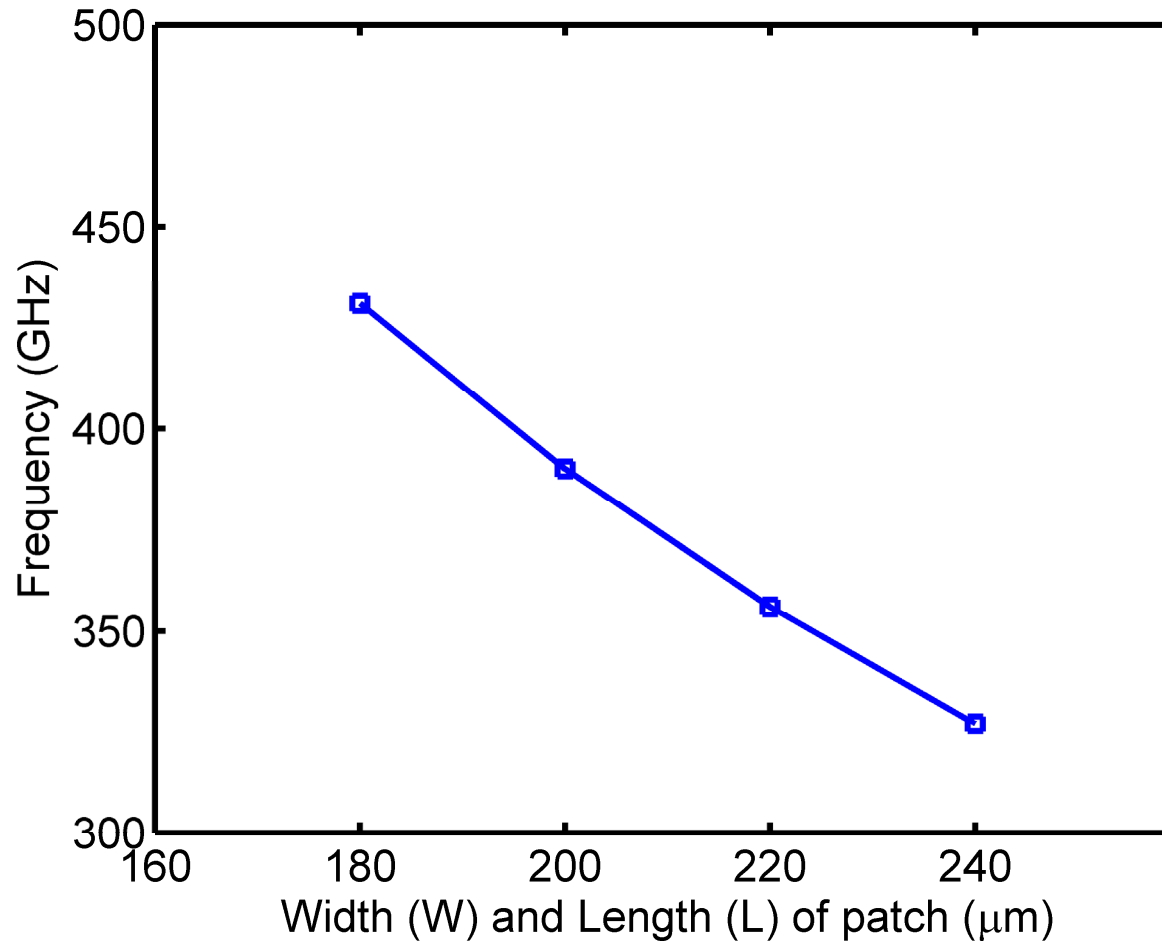

- ❑ The patch length (L) is about half wavelength.
- ❑ L is a dominant factor for the resonant frequency.

Antenna Efficiency

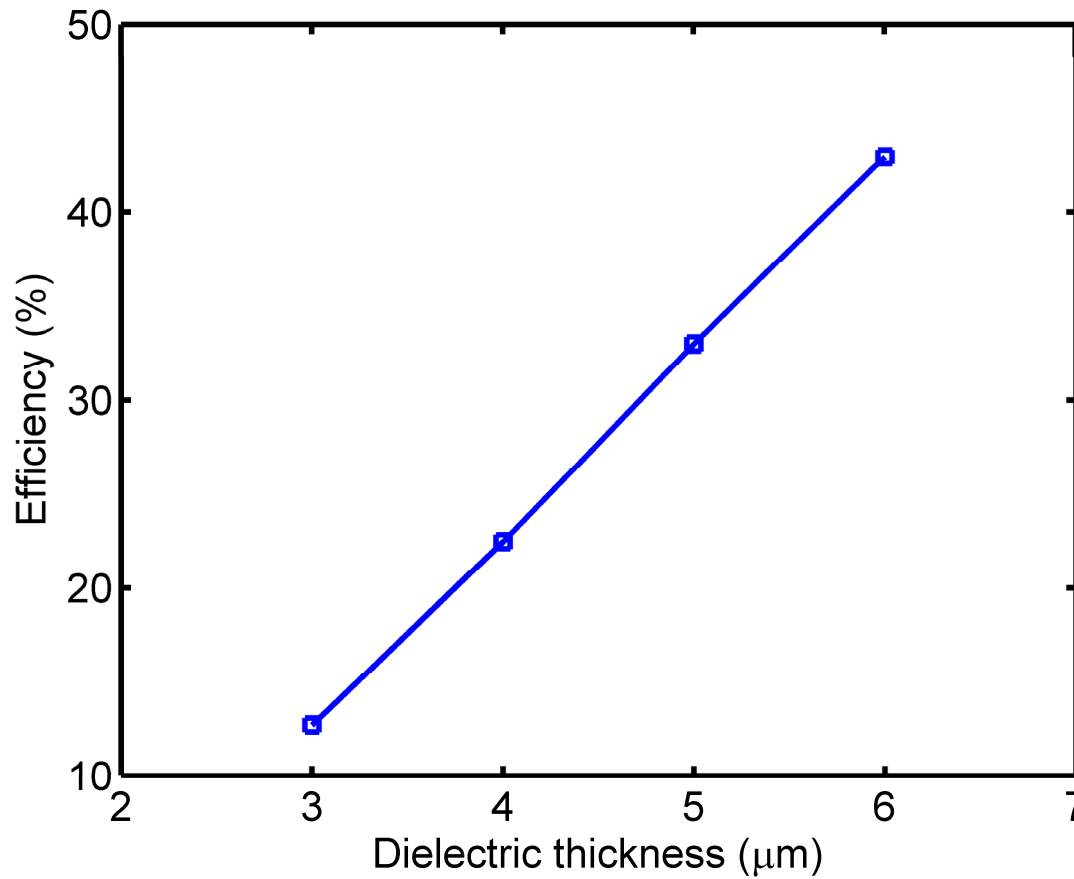


Efficiency (ε)

$$= \frac{\text{Radiated Power}}{\text{Total Applied Power}}$$

Frequency ~ 390GHz

- The thickness of the dielectric layer between the patch and ground is a dominant factor for the radiation efficiency.


Radiation Pattern

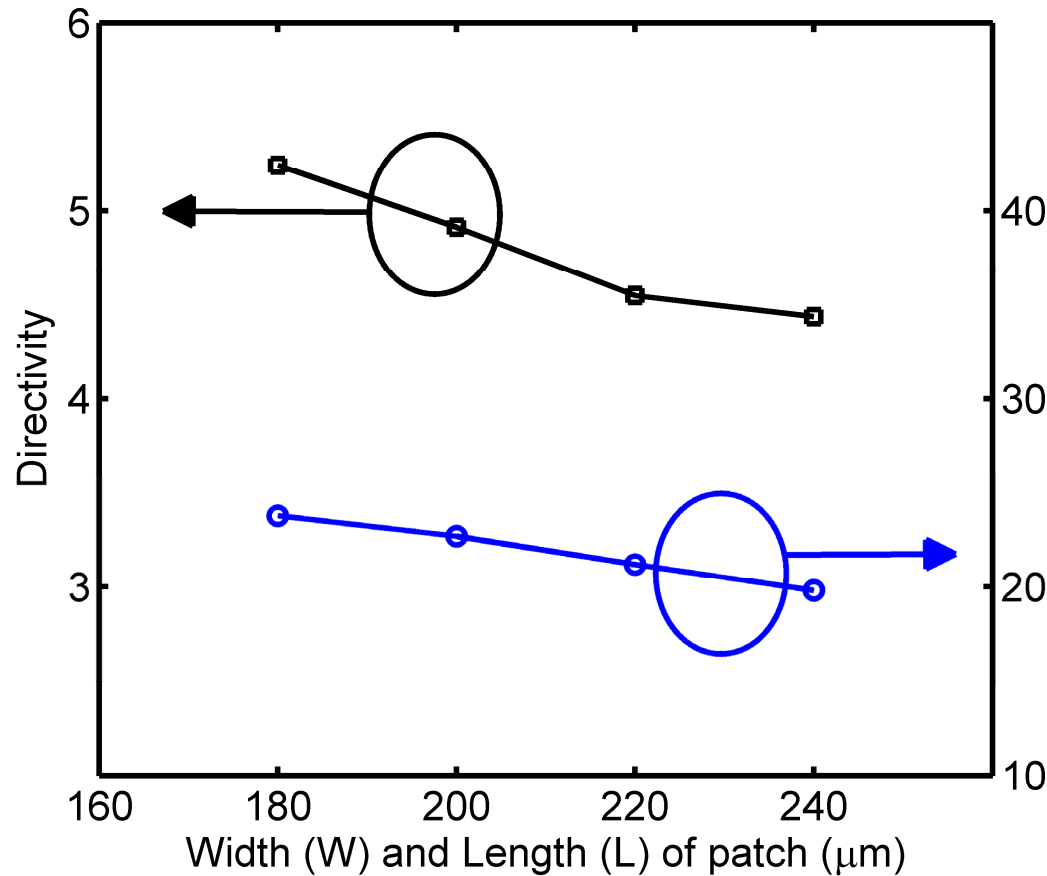


Directivity(D)

$$= \frac{\text{Power Density}(\theta, \phi)}{\text{Average Power Density}}$$

Efficiency (%)


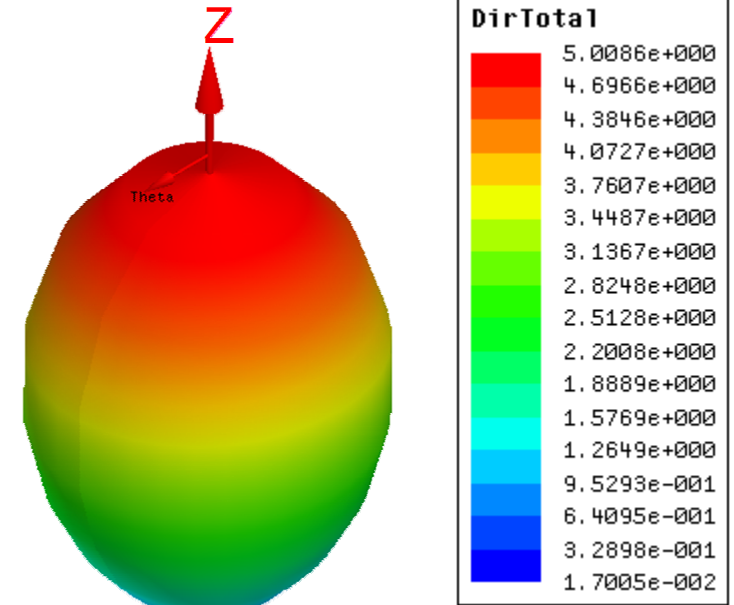


Dielectric thickness
~4μm

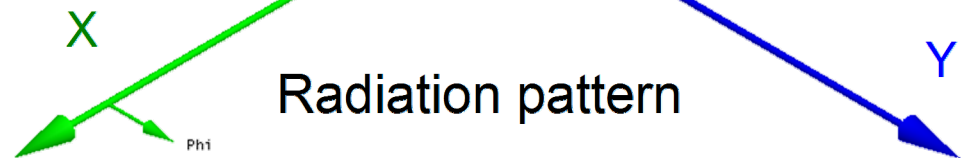


FTIR

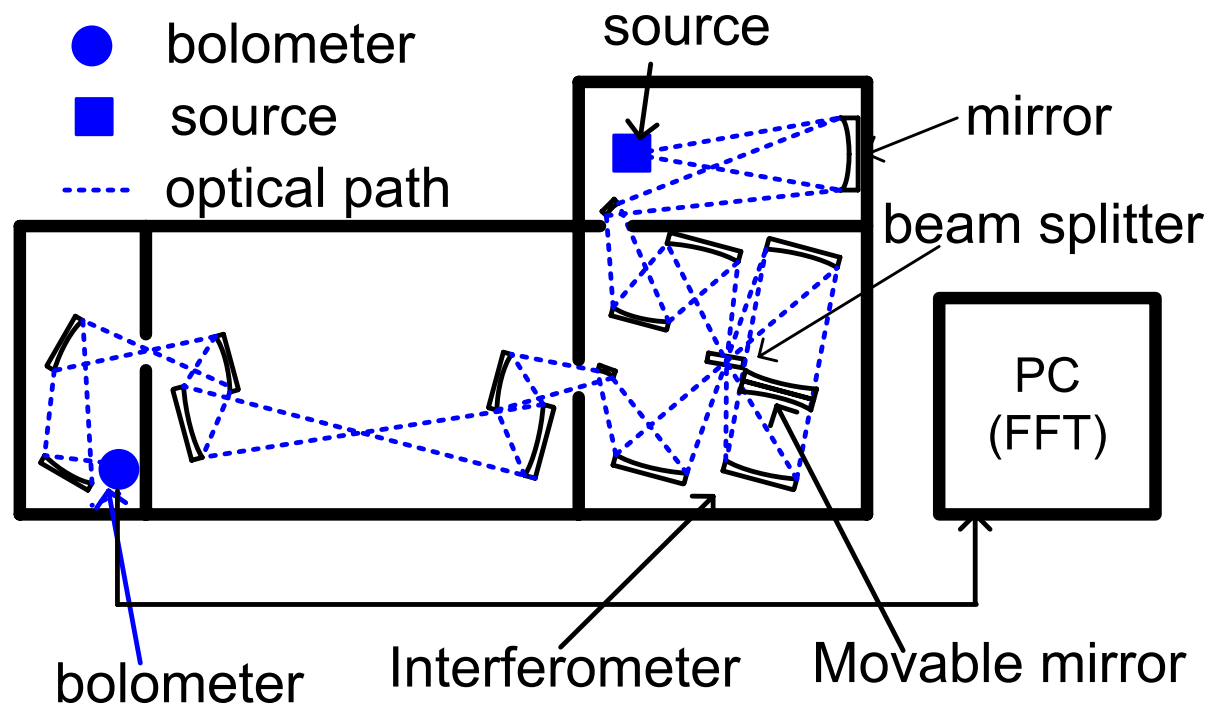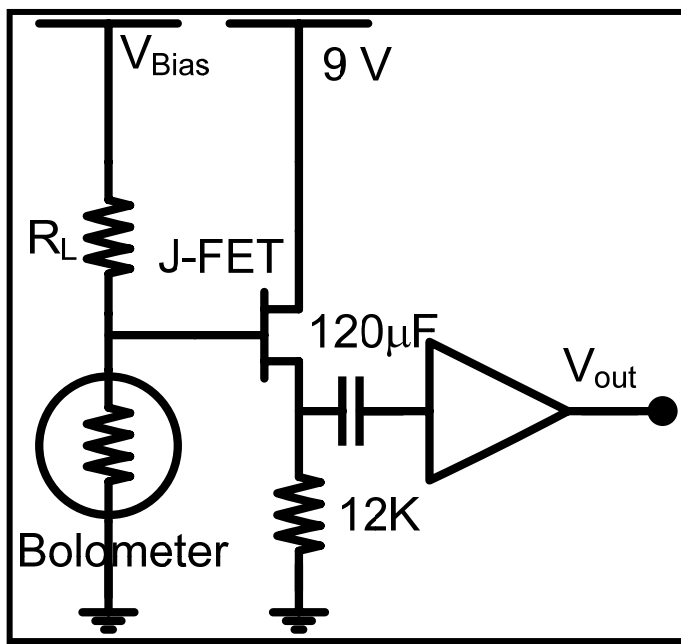- ❑ Off the shelf electrical probes go up to 325GHz.
- ❑ Fourier transform infrared spectroscopy (FTIR) consists of a bolometer, an interferometer and sources.
- ❑ Silicon bolometer (HD-3, IR Lab), 5-mil beam splitter




Interferometer

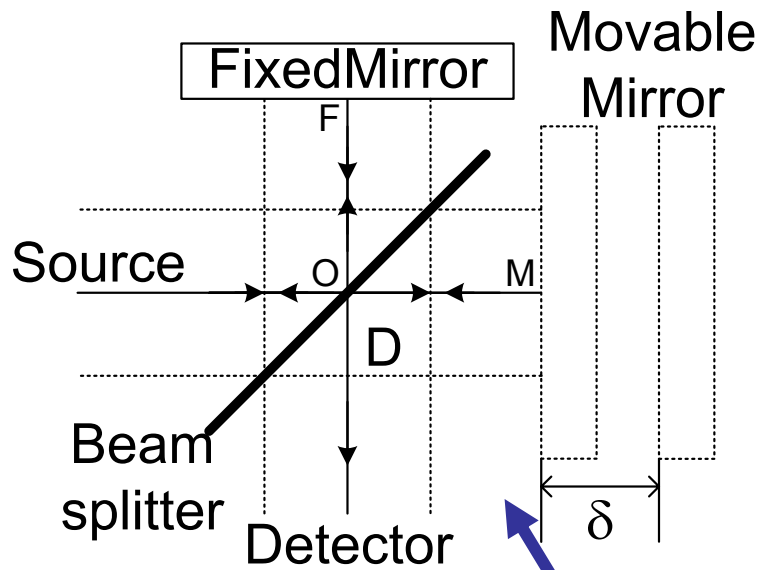


Freq: 400GHz
 Period: 2.5p sec
 λ_0 : 0.75mm


Reflected wave form

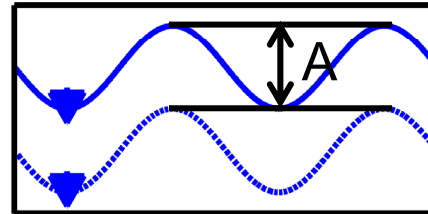

time ($\delta = 0$)

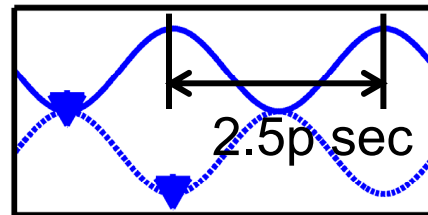


time ($\delta = \lambda/4$)

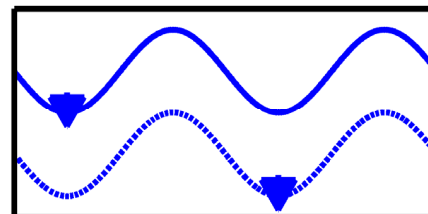


time ($\delta = \lambda/2$)


Wave form at D

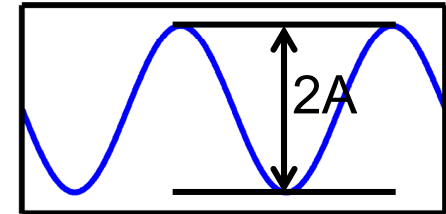


time ($\delta = 0$)

 

time ($\delta = \lambda/4$)

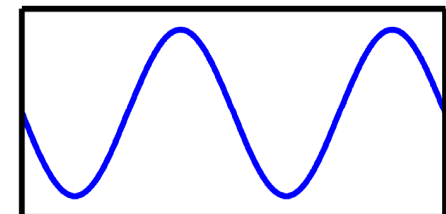

time ($\delta = \lambda/2$)

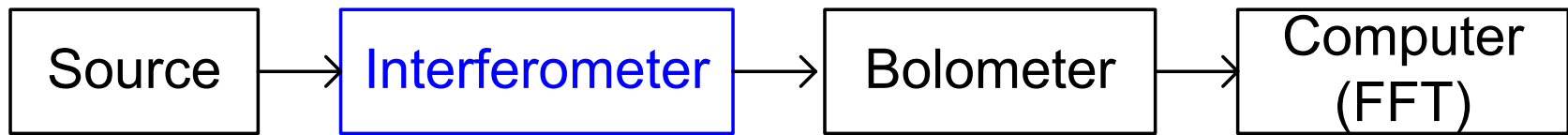

Interferogram

Interferogram

$$= (1 + \cos 2\pi \frac{2\delta}{\lambda_0})$$



$$= (1 + \cos 2\pi \frac{2V_M}{\lambda_0} \times t)$$

□ $\delta = V_M \times t$


(V_M : mirror velocity)

□ $\text{Freq} = c / (2V_M \times t_1)$

($c = 3 \times 10^8$ m/sec)


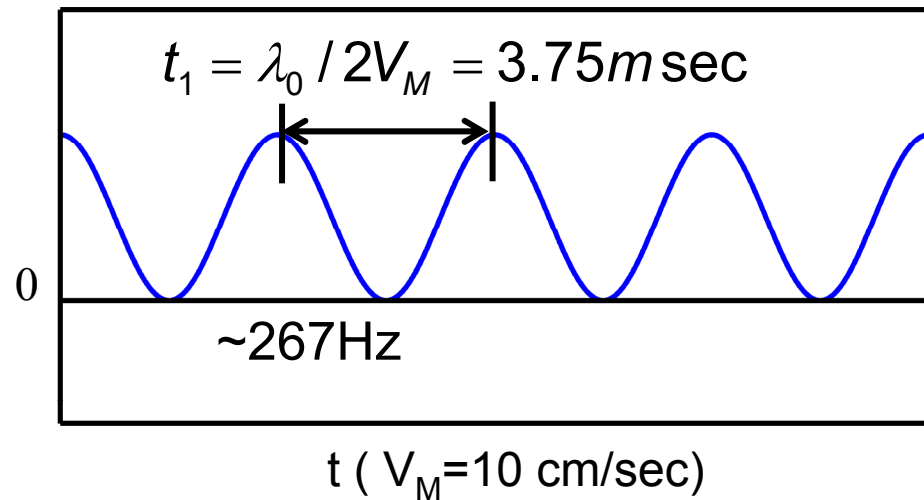
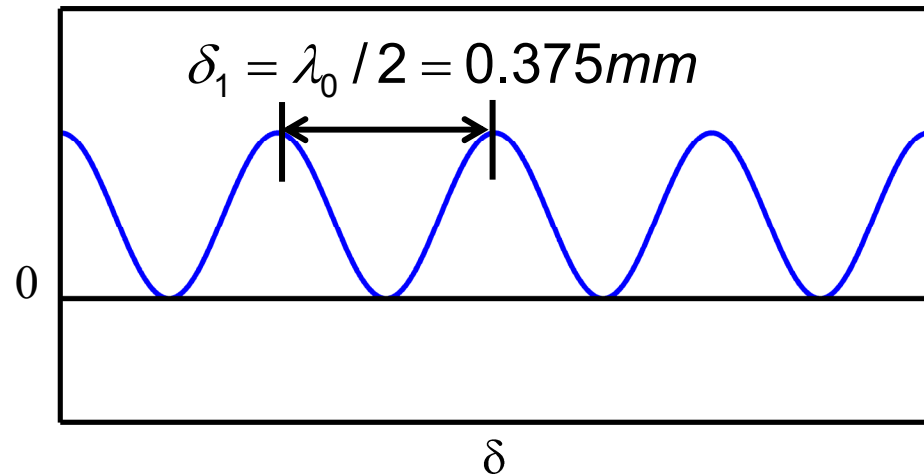


Interferometer

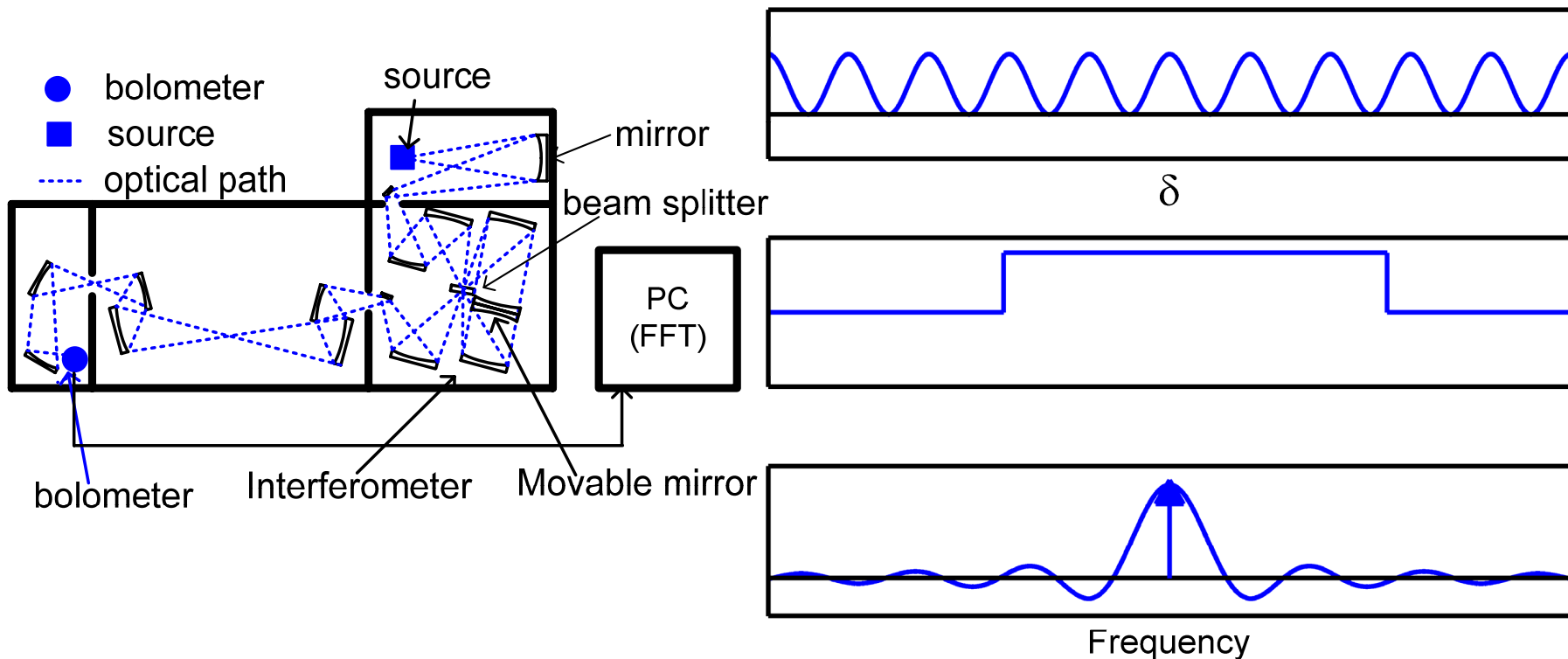


- ❑ The mirror movement is limited and the recovered spectrum is convolved with a sinc function in the frequency domain.


THz Measurements

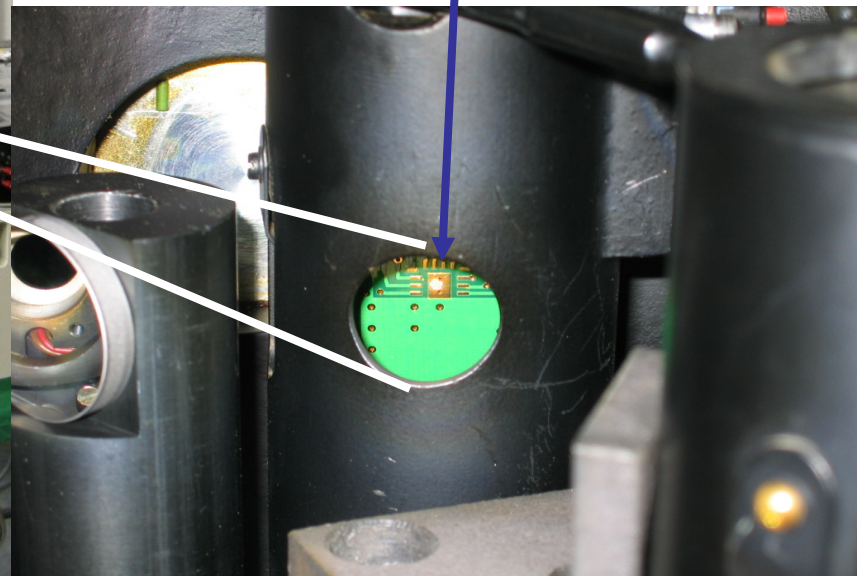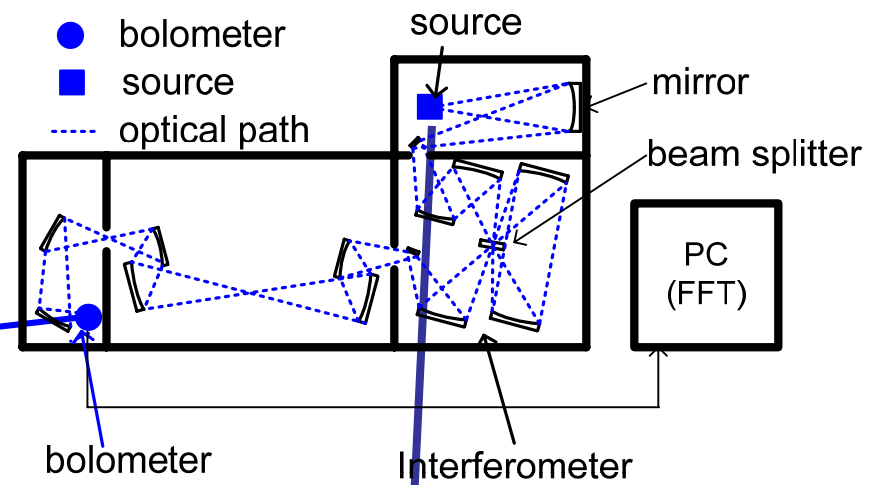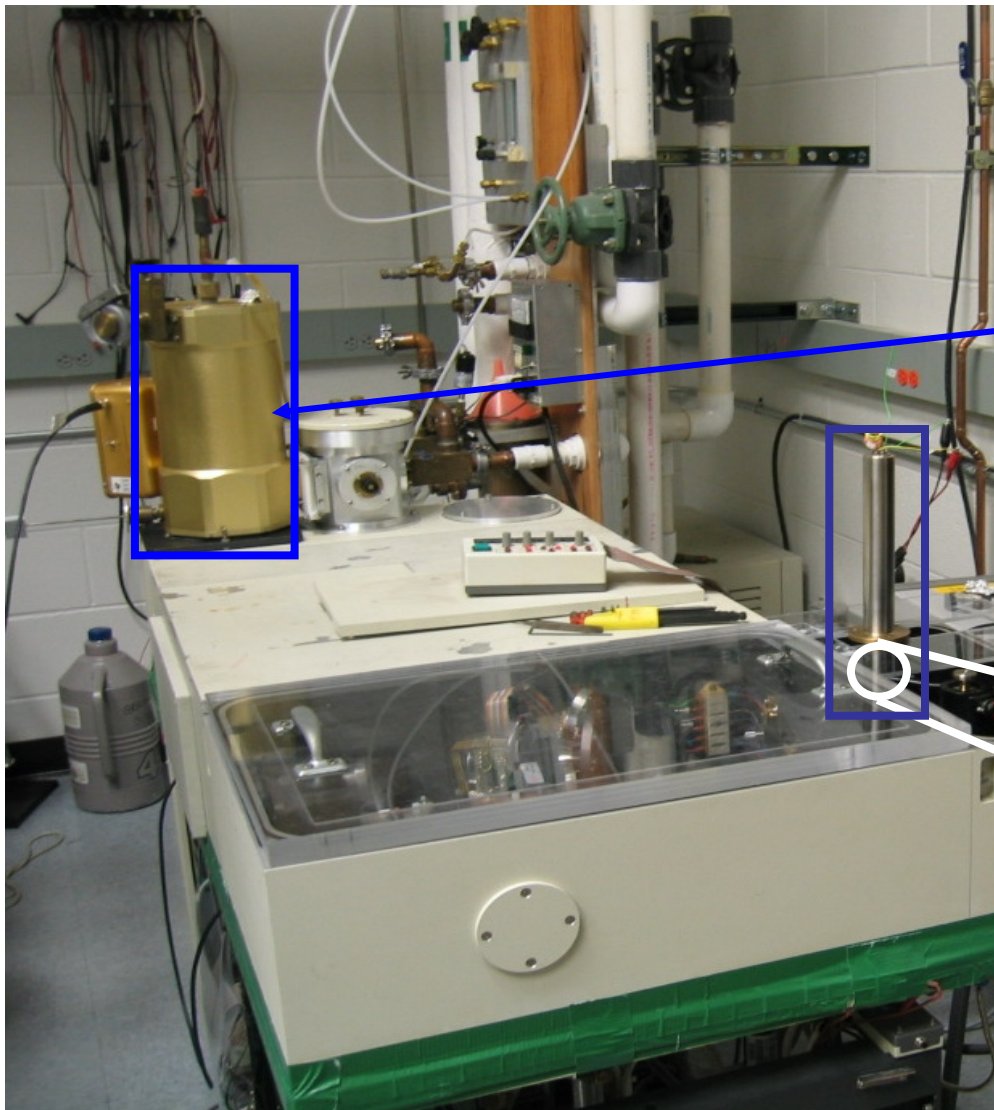



Power Measurement

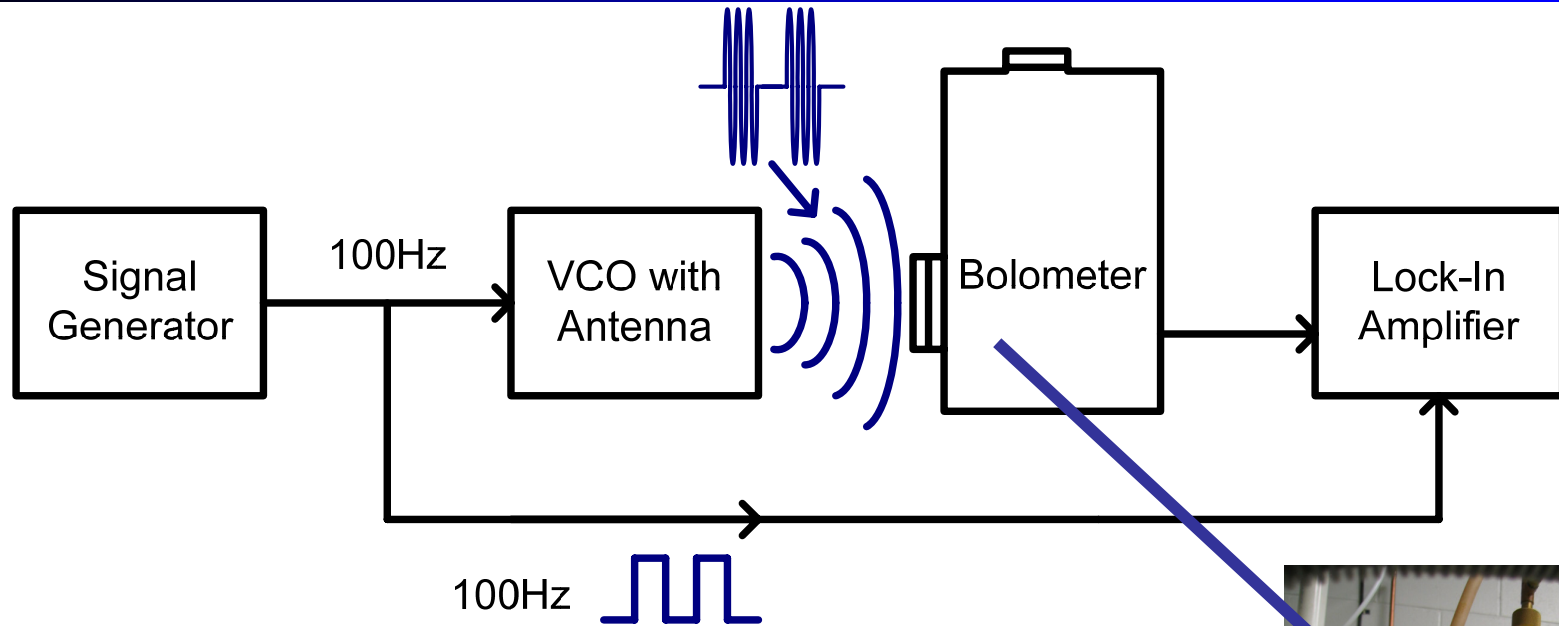

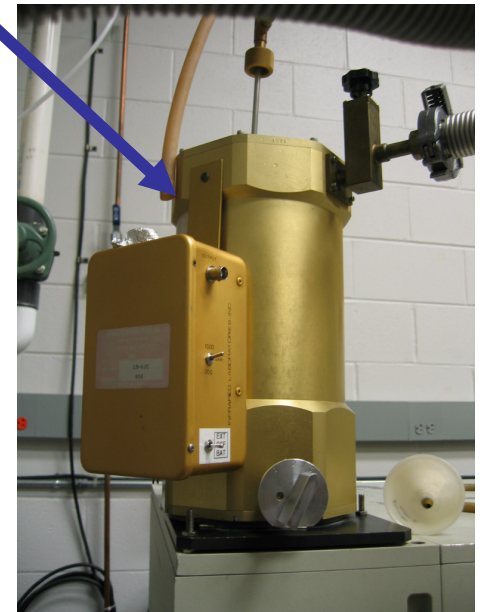- ❑ 100Hz modulation on V_{DD} of Oscillator
- ❑ A lock-in amplifier detects signals in noisy environments.
- ❑ Measures power radiated through the on-chip patch antenna




Fundamental Oscillator Measurement

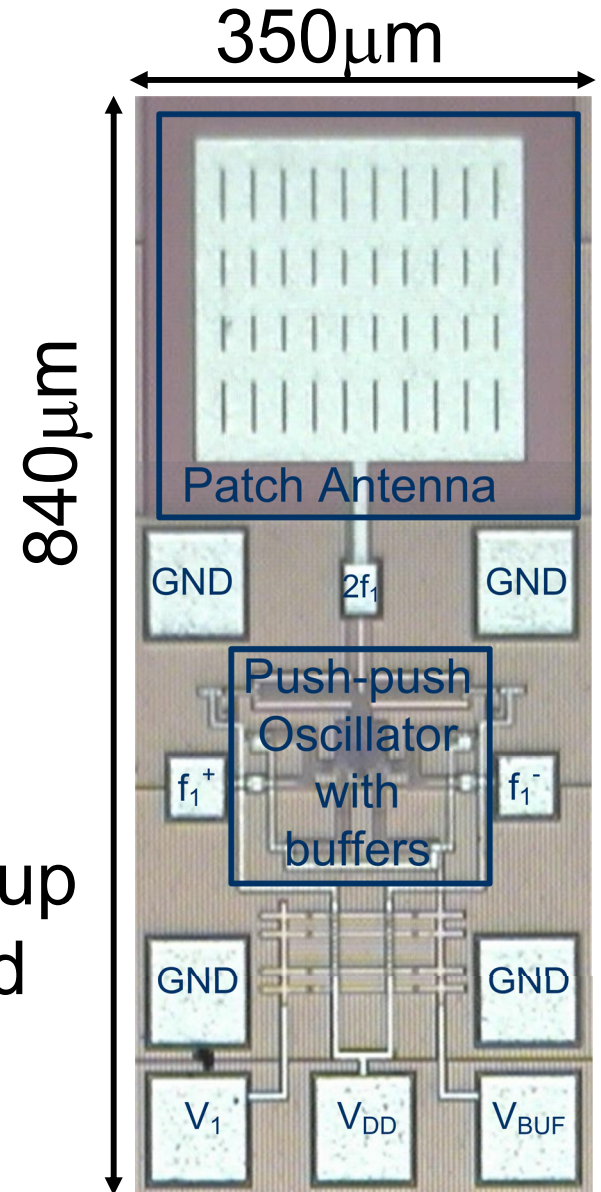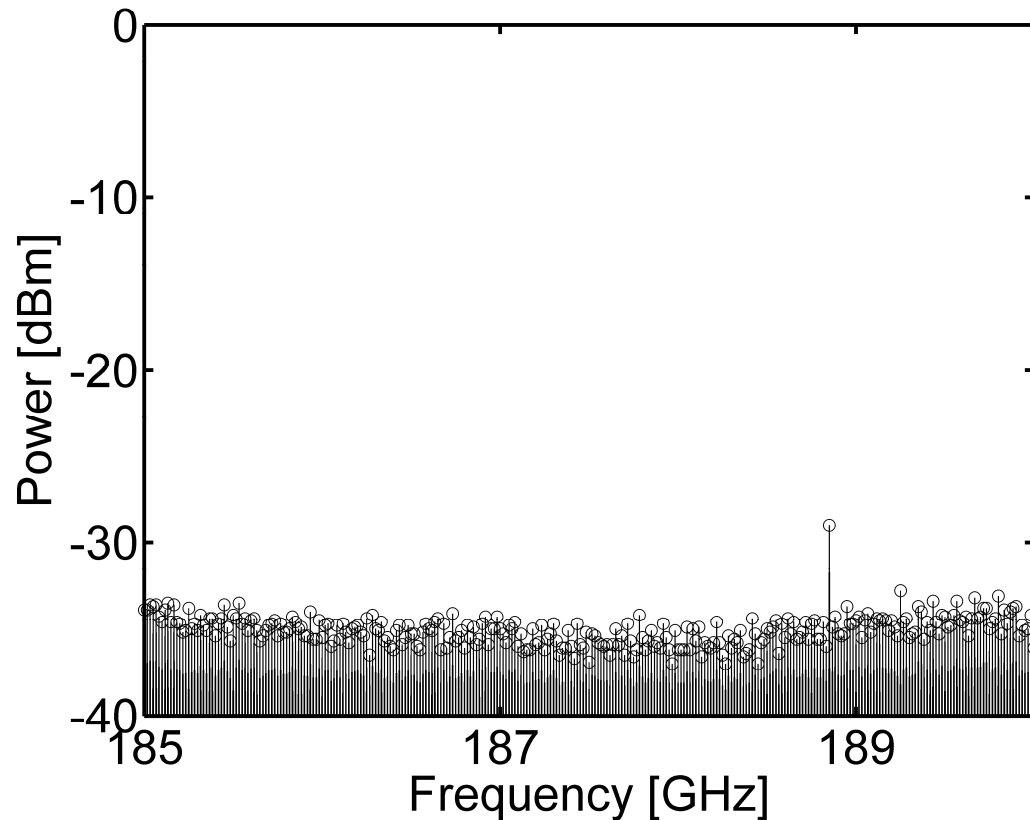


- A fundamental oscillator operating up to 189 GHz has been demonstrated using low leakage transistors in 45nm CMOS.

THz VCO

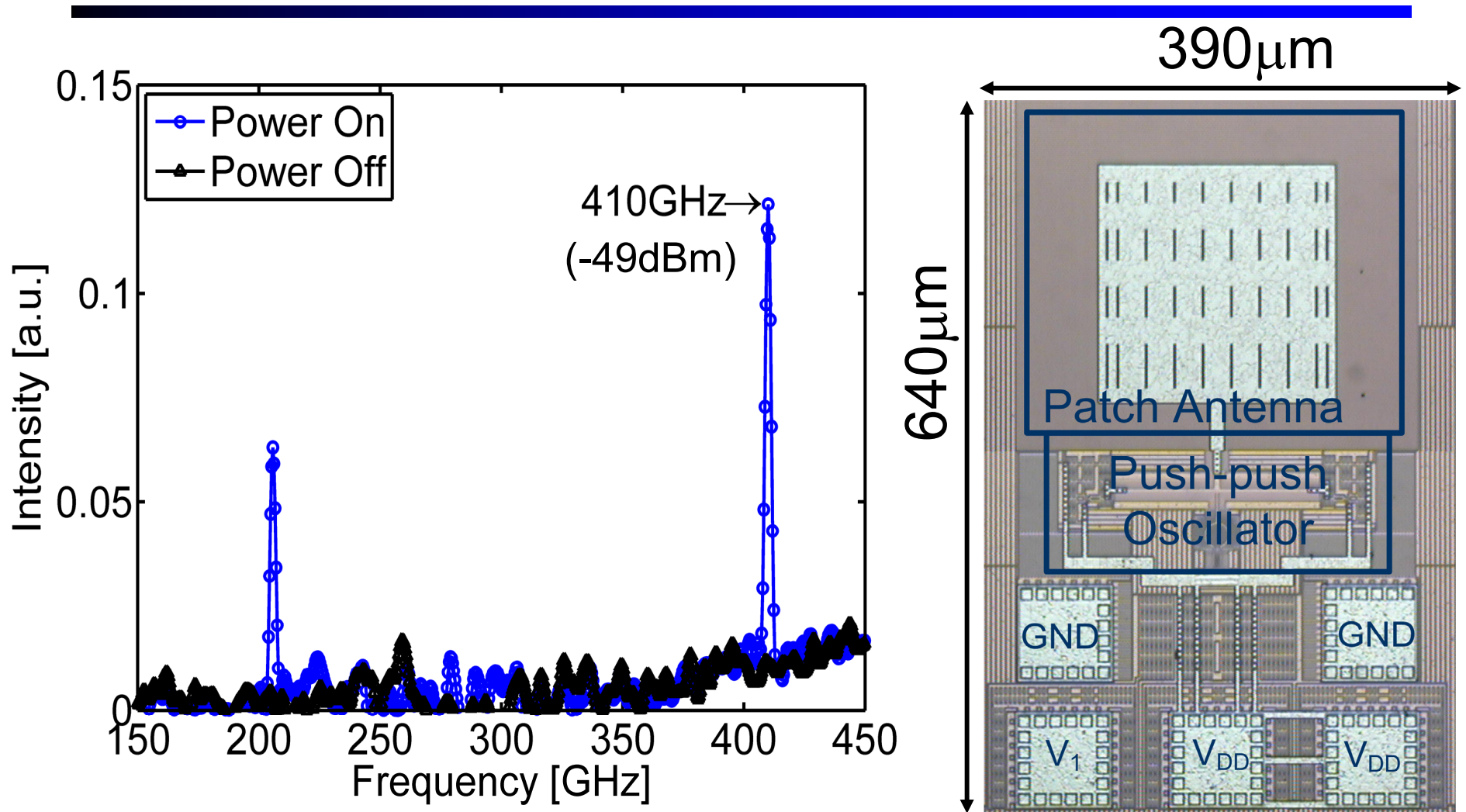


THz Measurements

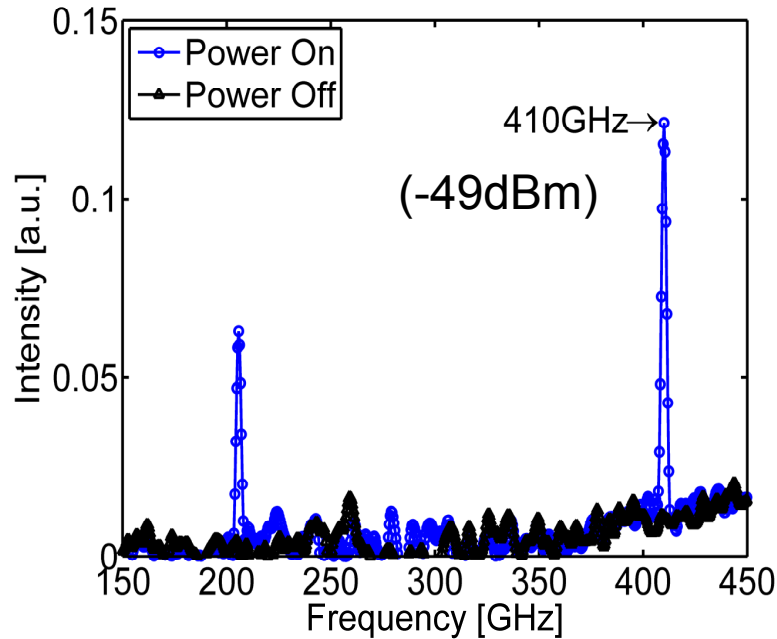


□ When the inductor Q increased to 8 and bypass cap Q increased to 5 and $R_{sub} = 1k\Omega$ then P_{out} is -18 dBm.

| | |
|--|---------|
| Measured Power | -47 dBm |
| 2 nd Harmonic Power | -49 dBm |
| Antenna loss | 7 dB |
| Mismatch loss | 2 dB |
| Calculated Push-push P_{out} | -40 dBm |
| Simulated P_{out} with inductor Q of 6 @200GHz, bypass cap Q of 1 @400GHz and R_{sub} of 200Ω | -39dBm |

THz Measurements

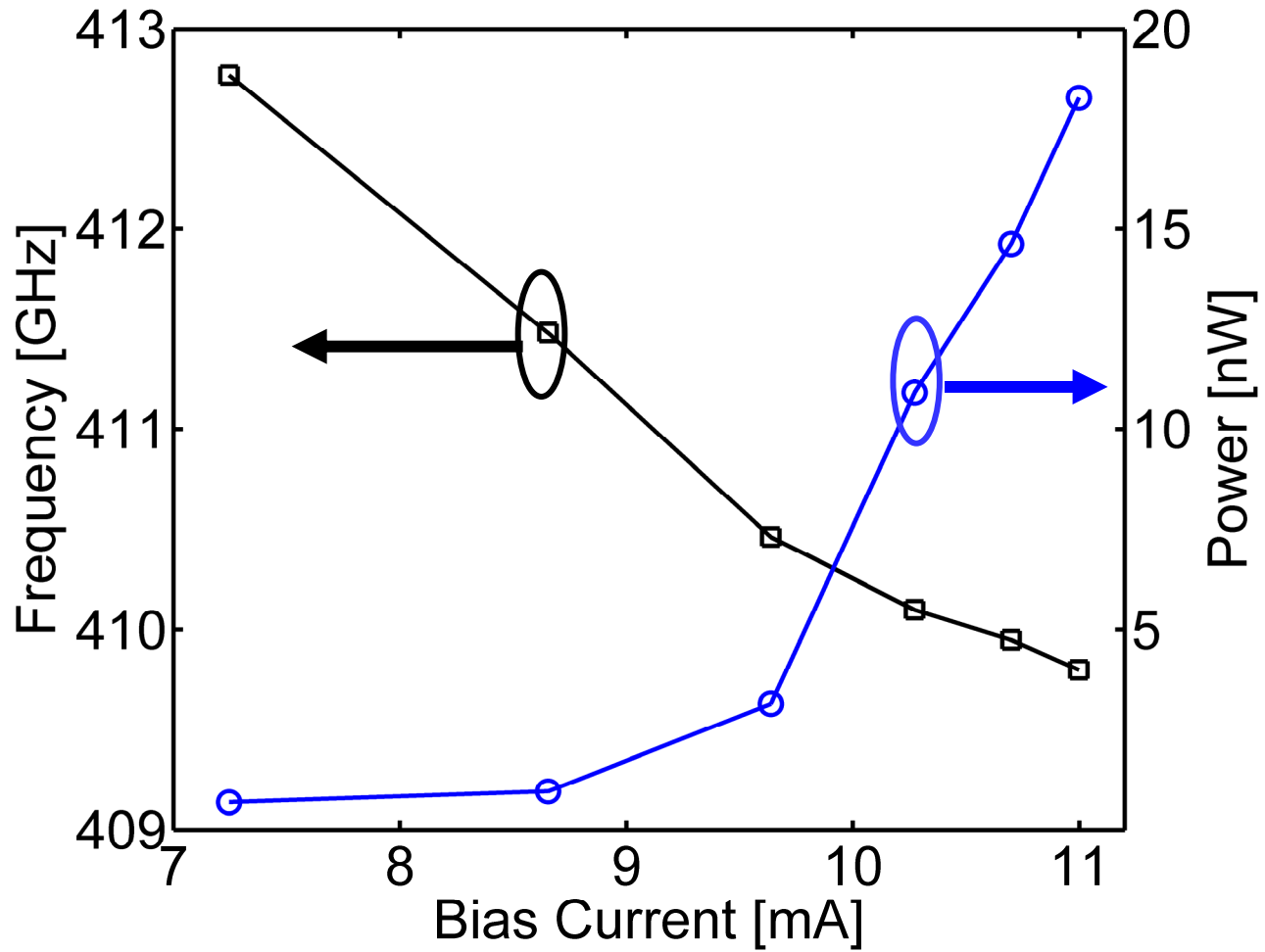


Summary

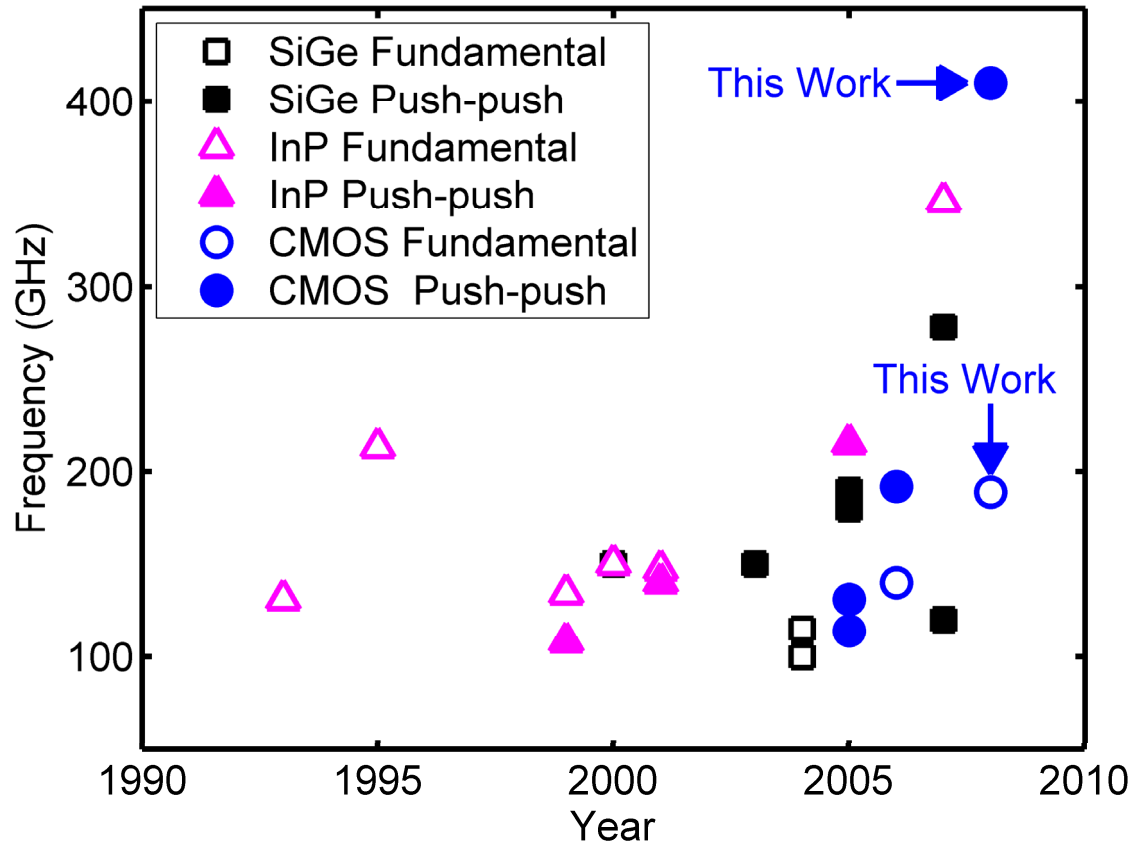

| Process | Freq (GHz) | P_{out} (dBm) | VCO | Ref |
|-------------------|------------|-----------------|------------------|------------------|
| SiGe HBT | 278 | -20 | Push-push | IMS 2007 |
| 35-nm InP HEMT | 346 | -16 | Fundamental | MWC 2007 |
| 45-nm CMOS | 410 | -49 | Push-push | This Work |

Summary

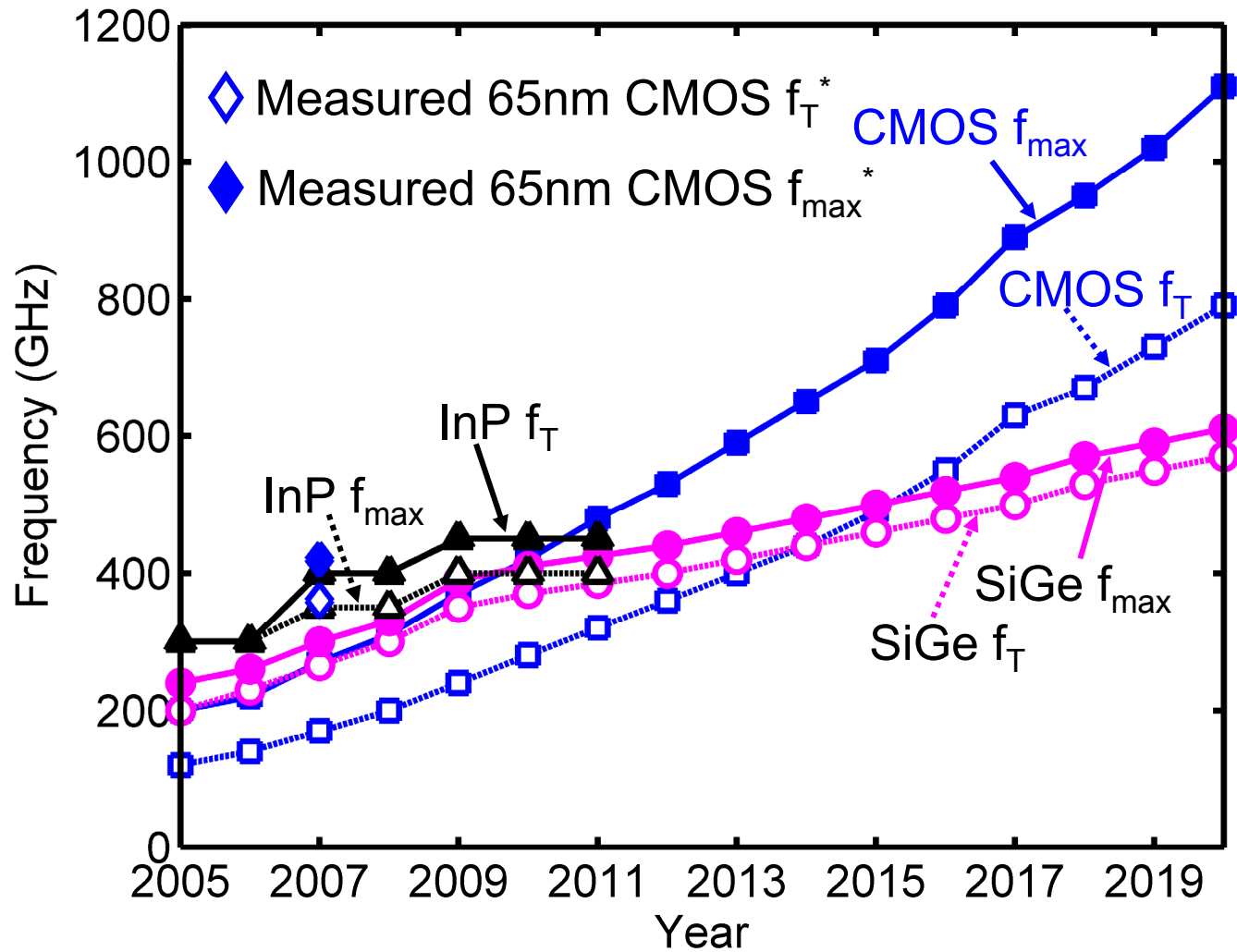

2006 ITRS roadmap & IEDM 2006*

Conclusions

- ❑ A 410-GHz push–push oscillator with an on-chip patch antenna fabricated using low leakage transistors of a 45-nm CMOS process with 6 metal layers is demonstrated.
- ❑ Using an FTIR system, the spectrum and power of the 410-GHz signals are measured.
- ❑ Presently output power is low.
- ❑ This work suggests the possibility of CMOS THz circuits.