

**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS**

**Denis DUFOURNET**

**Head of CERDA High Power and High Voltage  
Laboratories in Villeurbanne, France.**

**Georges MONTILLET**

**Dead Tank Circuit Breakers Product Manager  
Development, Charleroi, PA USA.**

## THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS

### WHY THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE CIRCUIT-BREAKERS ?

- *Both IEC and ANSI/IEEE define 3-phase faults as the basis for rated short-circuit current.*
- *Reason : 3-phase faults produce the highest stress on circuit-breakers during interruption*
  - *higher short-circuit current*
  - *higher peak of Transient Recovery Voltage*


## THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS

### WHY SYNTHETIC TESTING ?

- HV circuit-breakers have very high short-circuit interrupting capabilities :
  - 245 kV 50/63kA 1 break (21200 / 26700 MVA 3-phase or 10600 / 13350 MVA 1-phase)
  - They cannot be tested with one source of current and voltage (max. short-circuit power = 8000 MVA)
- Solution : synthetic tests with separate sources of current and voltage

**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS**

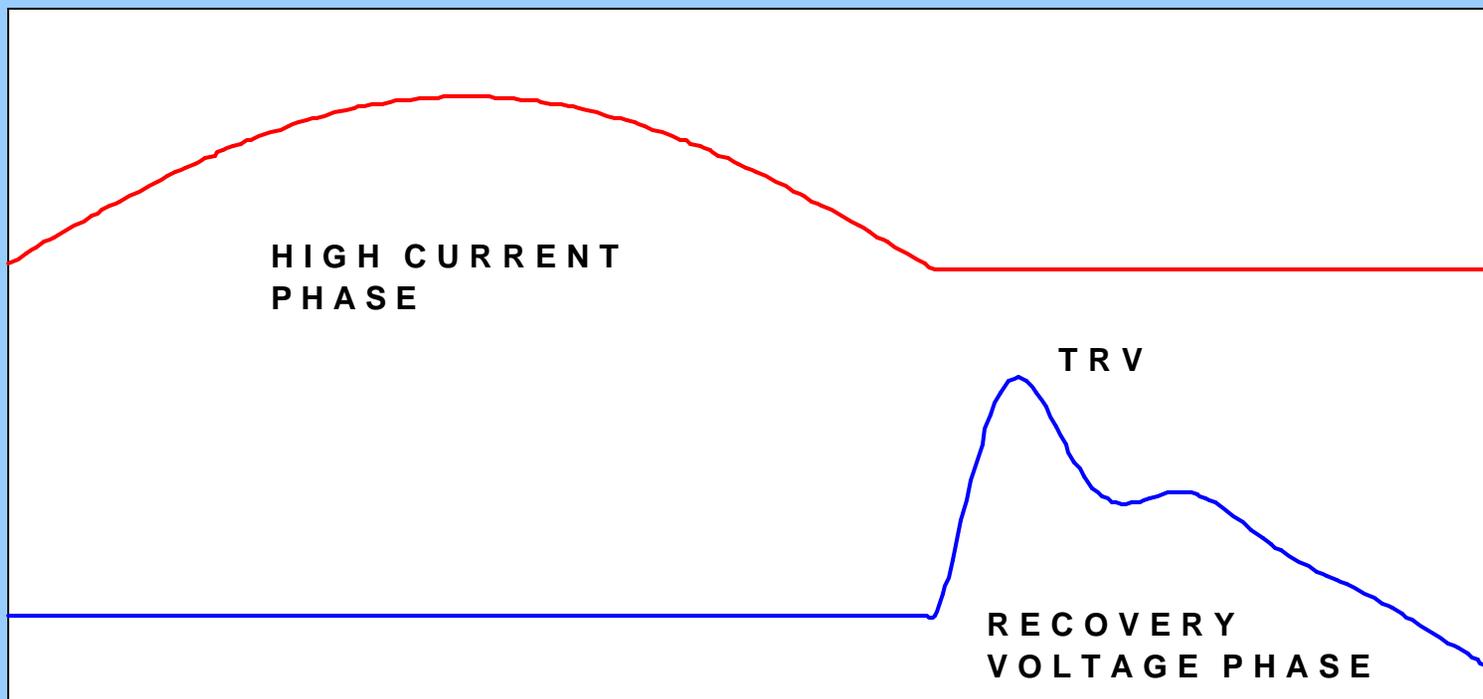
**PHASES DURING SHORT-CIRCUIT INTERRUPTION**



## **THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS**

### **SYNTHETIC TESTING PRINCIPLE**

- High current period : current delivered by generator(s) or power network,
- TRV and Recovery voltage period : voltage delivered by a high-voltage source (capacitor bank),
- 2 schemes used :
  - current injection,
  - voltage injection.

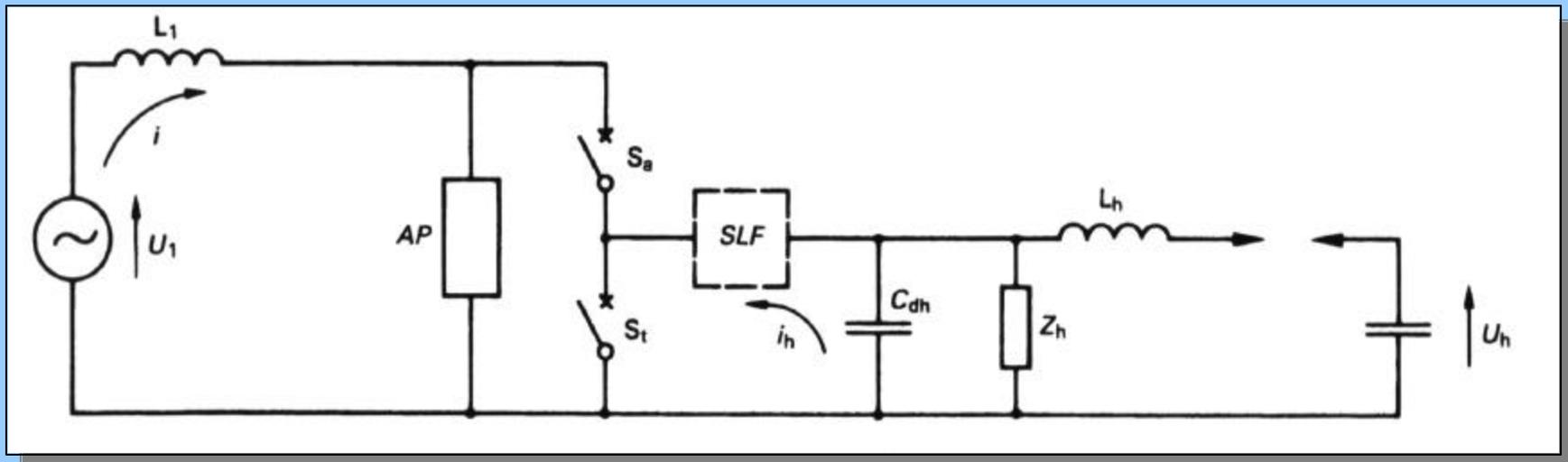**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS****SYNTHETIC TESTS WITH CURRENT INJECTION**

## IEEE SWITCHGEAR COMMITTEE

---




Example of synthetic test laboratories to illustrate the testing discussed in this paper.

TRANSMISSION & DISTRIBUTION  
High Voltage Switchgear

IEEE Switchgear Meeting  
Charleston, May 1999 Slide # 7

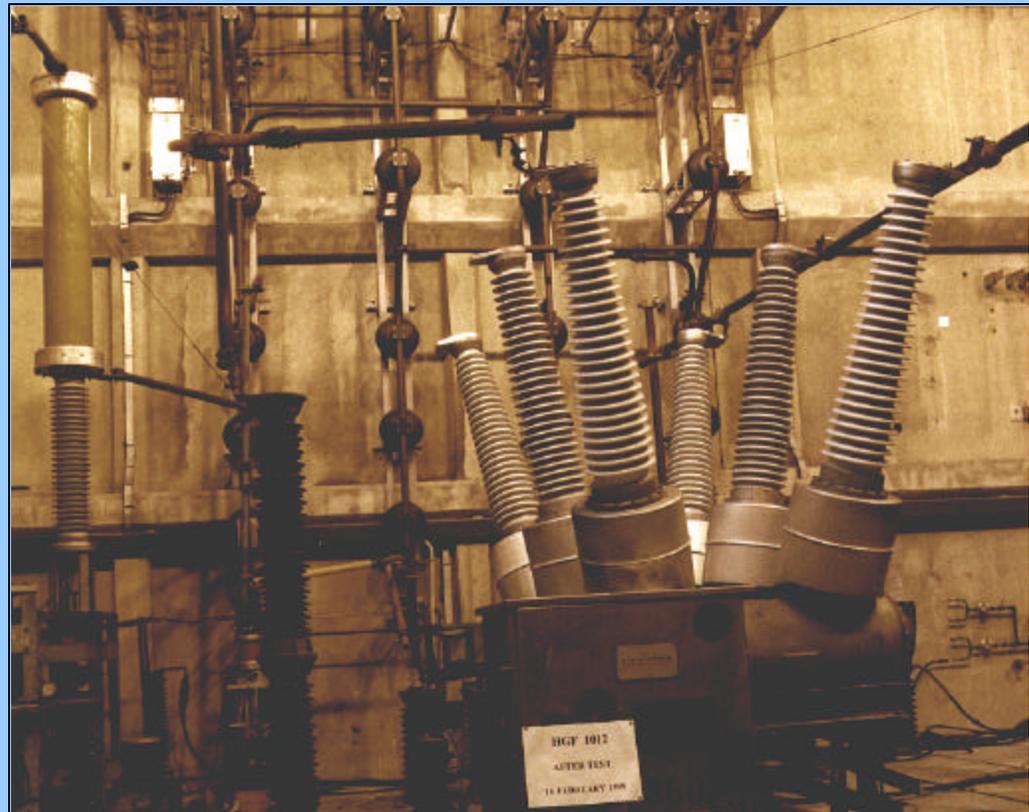**THREE-PHASE  
SHORT-CIRCUIT  
TESTING OF HIGH-  
VOLTAGE CIRCUIT-  
BREAKERS USING  
SYNTHETIC  
CIRCUITS**



**SYNTHETIC TESTS : Example of circuit-breaker under tests**


**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS****THREE-PHASE SYNTHETIC TESTS PRINCIPLE**

2 voltage circuits :

- one to apply the TRV on the first pole to clear.
- one to apply the TRV on second and third pole to clear.


**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS**

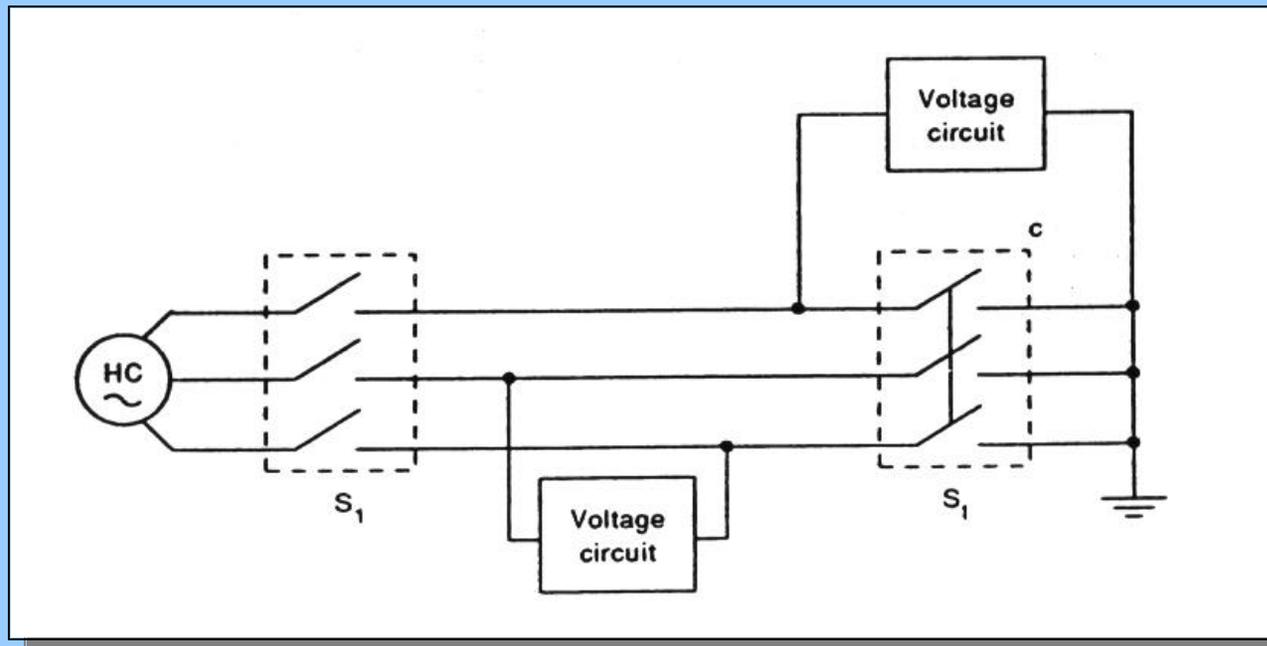**THREE-PHASE SYNTHETIC TESTS : SCHEME USED**




**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS**

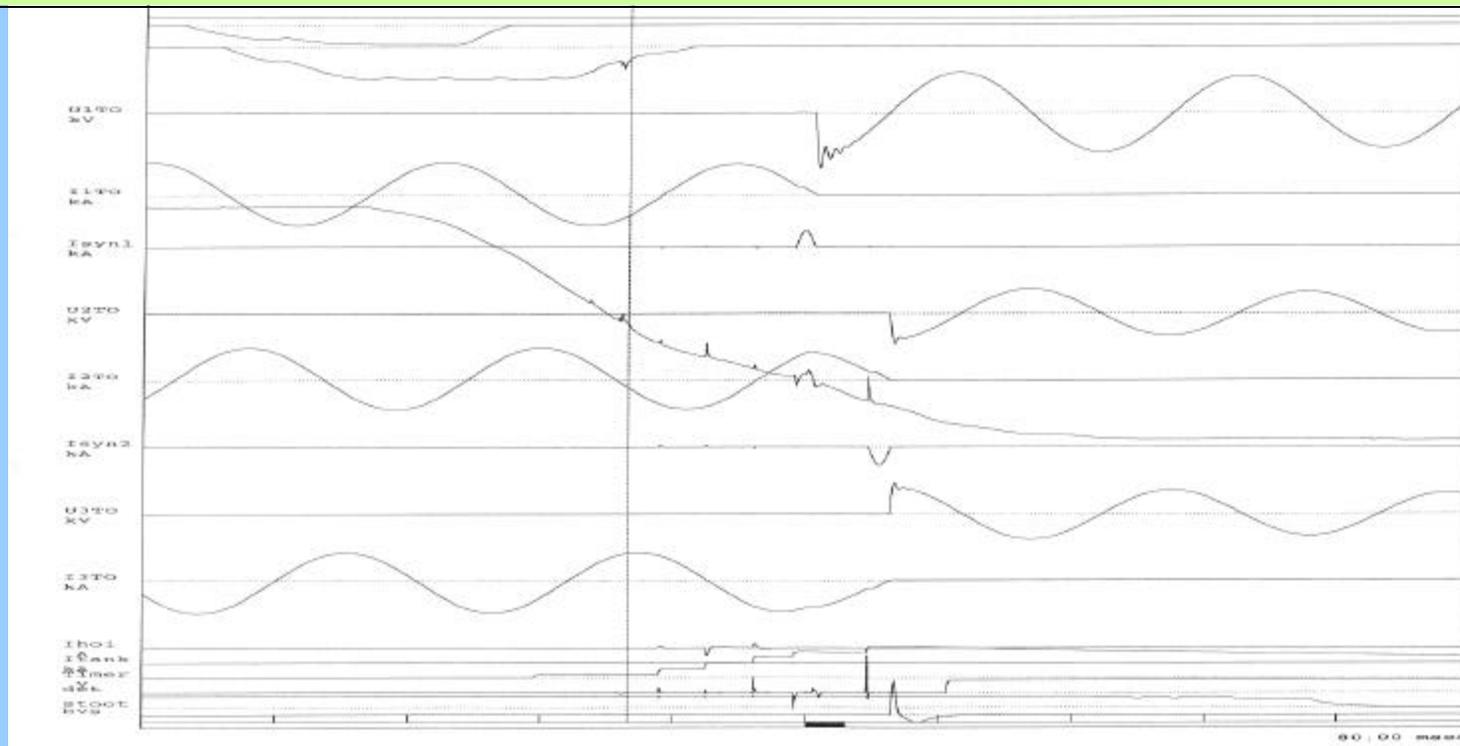SYNTHETIC TESTS : example of oscillograph from KEMA



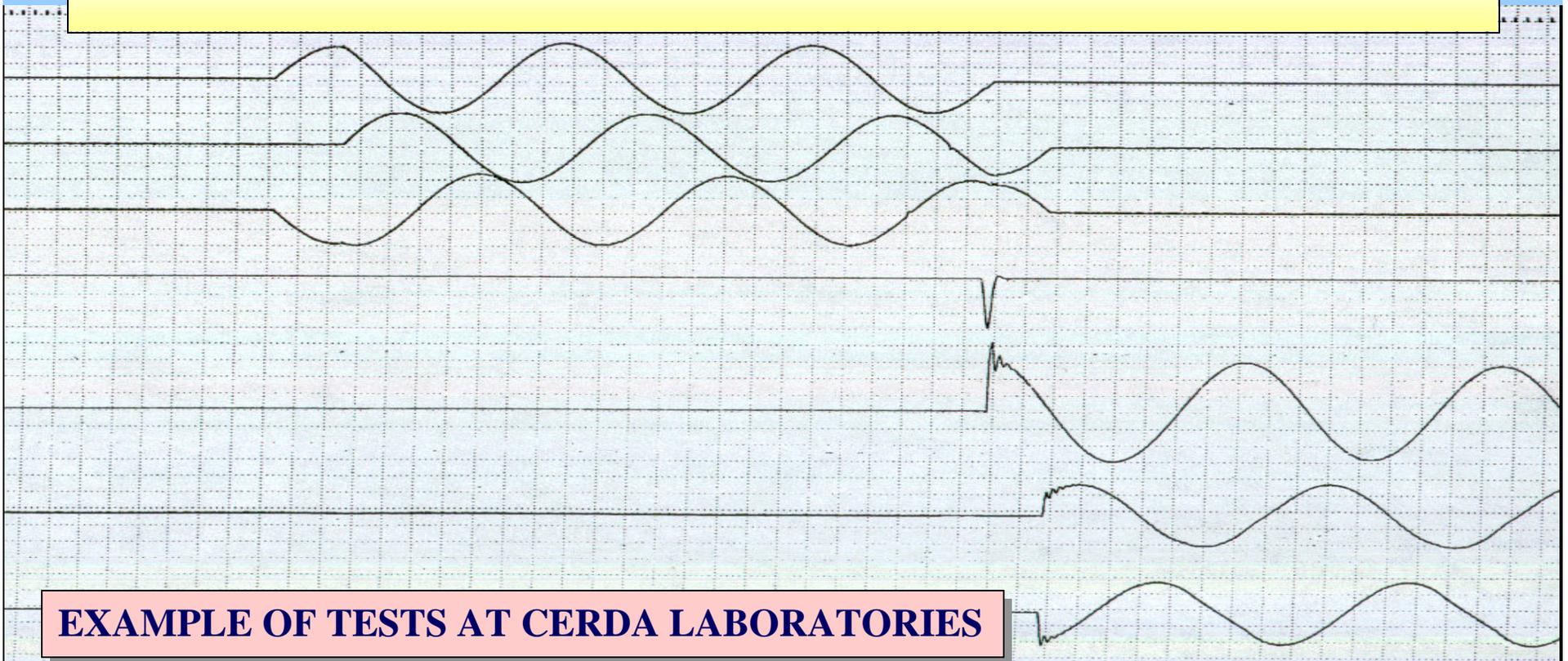**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS**



**EXAMPLE OF TESTS AT CERDA LABORATORIES**

## THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS

### 3-PHASE SYNTHETIC TESTS WITH SYMMETRICAL CURRENTS


- current zeros occur in any phase every  $60^\circ$  el.
- range of arcing times for the 1st pole to clear =  $60^\circ - E = 42^\circ$  el.
- 3 interruptions are required with arcing times (1st pole) :

To (minimum arcing time)

To +  $42^\circ$  el. (maximum arcing time)

To +  $21^\circ$  el. (medium arcing time)

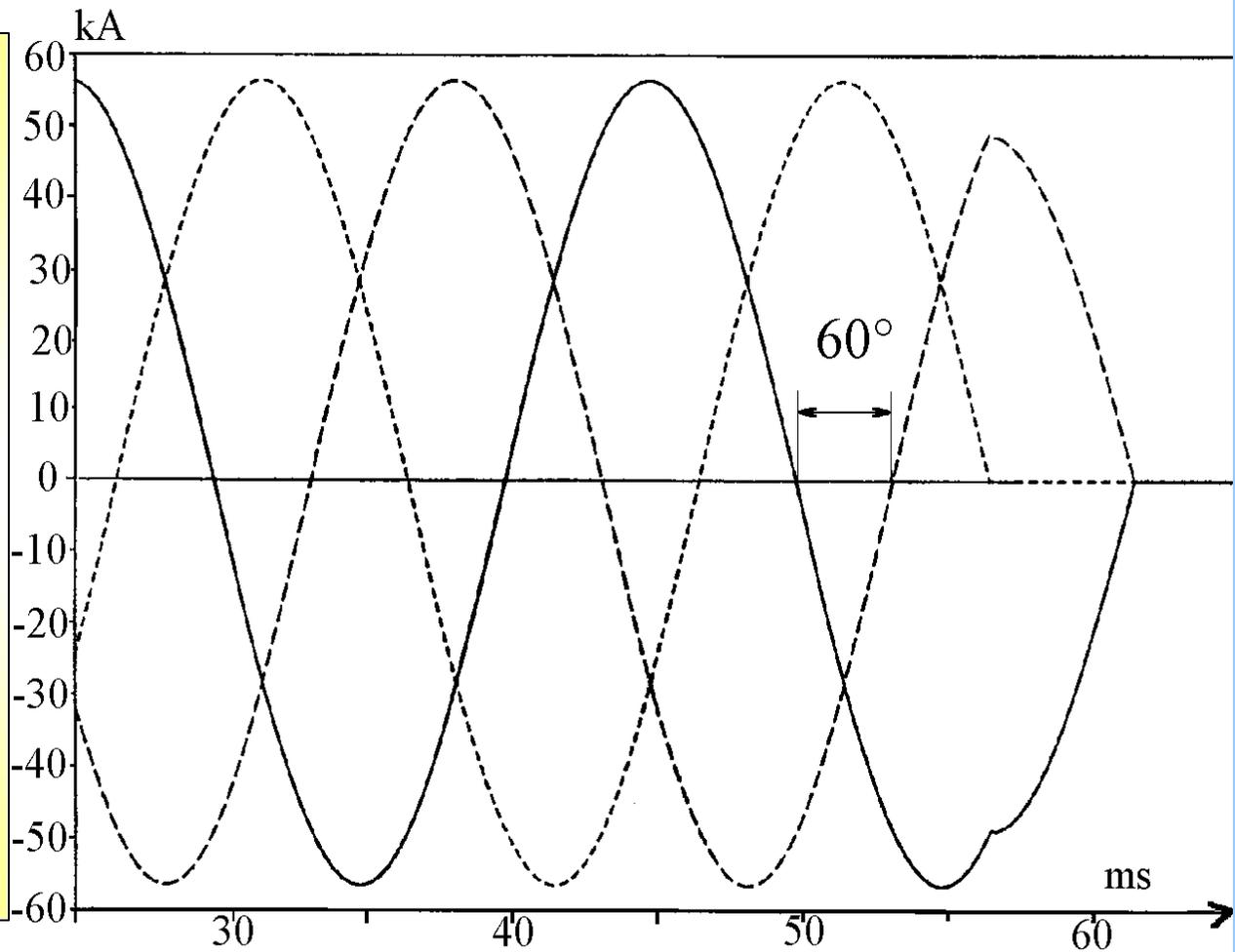**THREE-PHASE  
SHORT-CIRCUIT  
TESTING OF  
HIGH-VOLTAGE  
CIRCUIT-  
BREAKERS  
USING  
SYNTHETIC  
CIRCUITS**  
Three-phase  
symmetrical  
current  
interruption



## THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS

### 3-PHASE SYNTHETIC TESTS WITH SYMMETRICAL CURRENTS

Arcing times for the 2nd and 3rd pole to clear will be

- 90° el. longer (ungrounded system)
- 77° el. and 120°el. longer (grounded system)

## **THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS**

### **3-PHASE SYNTHETIC TESTS WITH ASYMMETRICAL CURRENTS**

- No standardized method today in IEC and ANSI/IEEE.
- Our proposal in IEEE Paper accepted for publication in Transactions on Power Delivery.

To define a procedure which:

- test the 2 most severe cases required in standards, and
- require a maximum of 3 tests with asymmetrical currents.

**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS****WHAT ARE THE 2 MOST SEVERE CASES ?**

as defined in future ANSI C37-09 & IEC 60056 :

- Case 1 : interruption by the 1st pole to clear after a major loop of current with the required asymmetry,
- Case 2 : interruption by one of the last pole after a major extended loop of current with the required asymmetry.

**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS****PROPOSED METHOD**

- defined for grounded neutral networks and ungrounded neutral networks
- covers the most general possible cases
- special cases should be treated separately : a standard is not a catalogue of all possible cases

**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS****NETWORKS WITH GROUNDED NEUTRAL**


Case 1: interruption by the 1st pole to clear after a major loop  
of current with the required asymmetry

- maximum arcing time for 1st pole to clear :

$$t1 = t0 \text{ (minimum symmetrical) } + 60^\circ \text{ el. (2 cycle c.b.)}$$

$$t1 = t0 \text{ (minimum symmetrical) } + 54^\circ \text{ el. (3 cycle c.b.)}$$

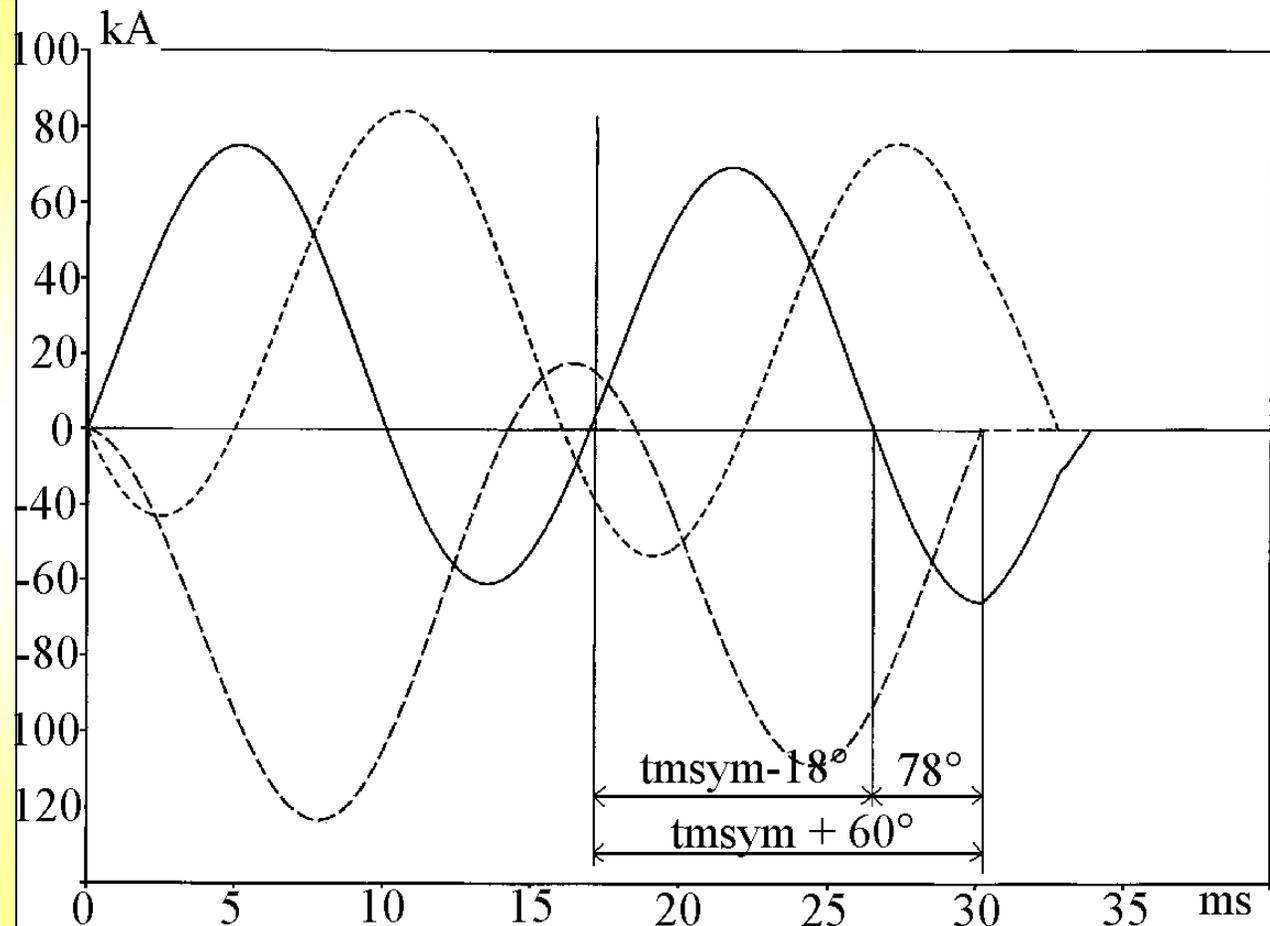**Asymmetrical currents during 3-phase short circuit interruption of 40 kA-60 Hz by 2-cycle circuit breaker with  $k_{pp}=1.3$ . Interruption of the first pole to clear after a major loop.**



**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS****NETWORKS WITH GROUNDED NEUTRAL**


Case 1: interruption by the 1st pole to clear after a major loop of current with the required asymmetry

if the 1st pole cannot interrupt with arcing time  $t_1$ , another phase must be interrupted with the same conditions ( $I$ , TRV) and a longer arcing time :


$$t_1 = t_0 \text{ (minimum symmetrical) } + 142^\circ \text{ el.} \quad \text{(2 cycle c.b.)}$$

$$t_1 = t_0 \text{ (minimum symmetrical) } + 129^\circ \text{ el.} \quad \text{(3 cycle c.b.)}$$

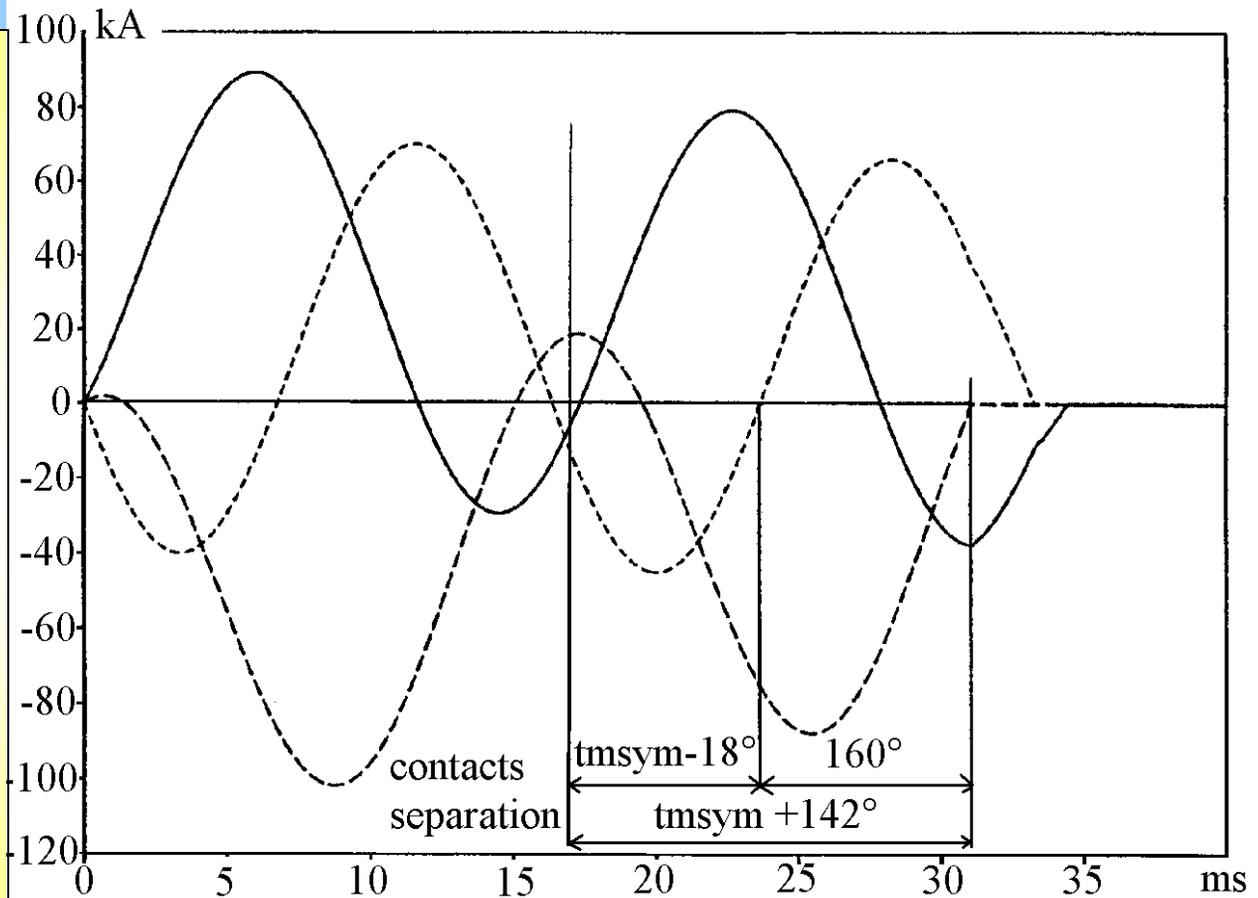
**Asymmetrical currents during 3-phase short-circuit interruption of 40 kA-60Hz by 2-cycle circuit breaker with  $k_{pp}=1.3$ . Interruption of the first pole to clear after a major loop.**



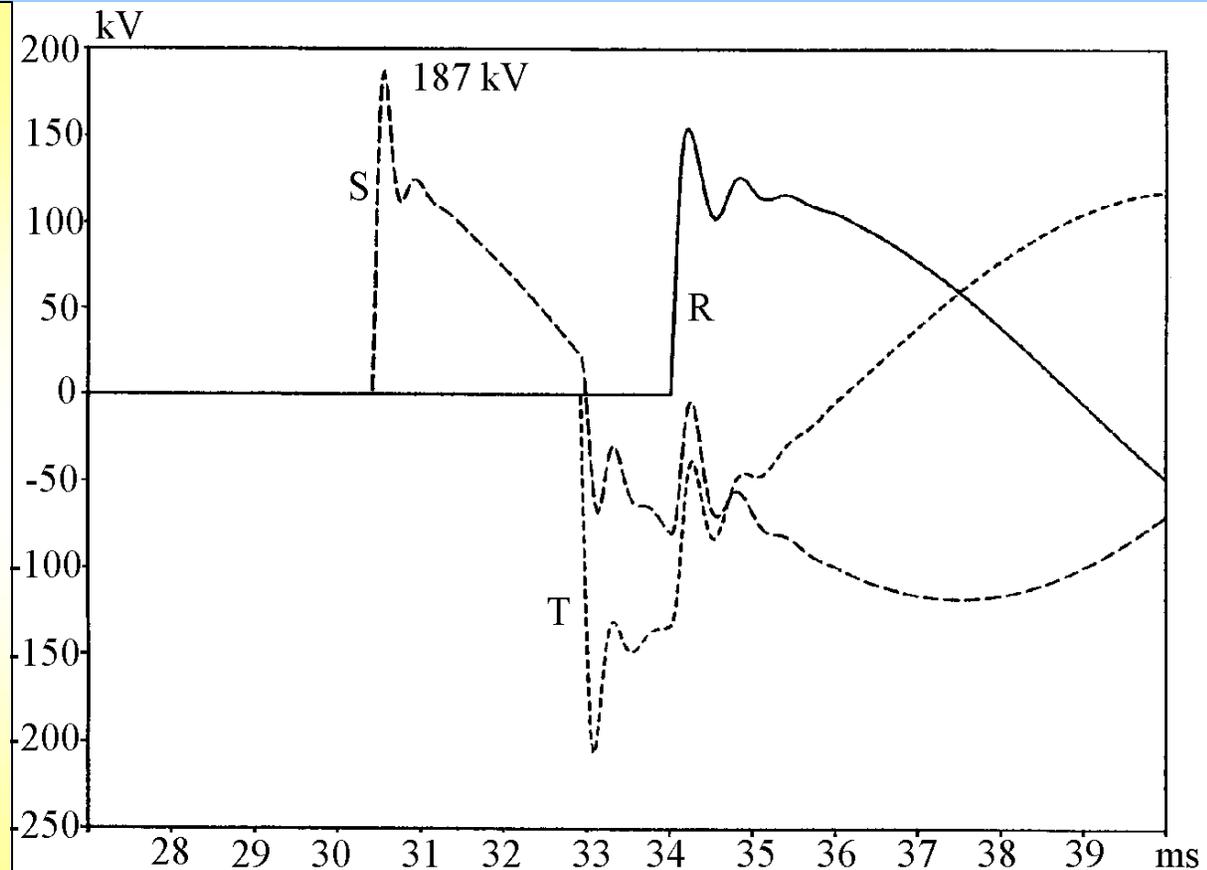**Transient  
Recovery  
Voltage during  
3-phase short  
circuit  
interruption of  
40 kA-60 Hz by  
2-cycle circuit  
breaker with  
 $k_{pp}=1.3$ .  
Interruption of  
the first pole to  
clear after a  
major loop.**



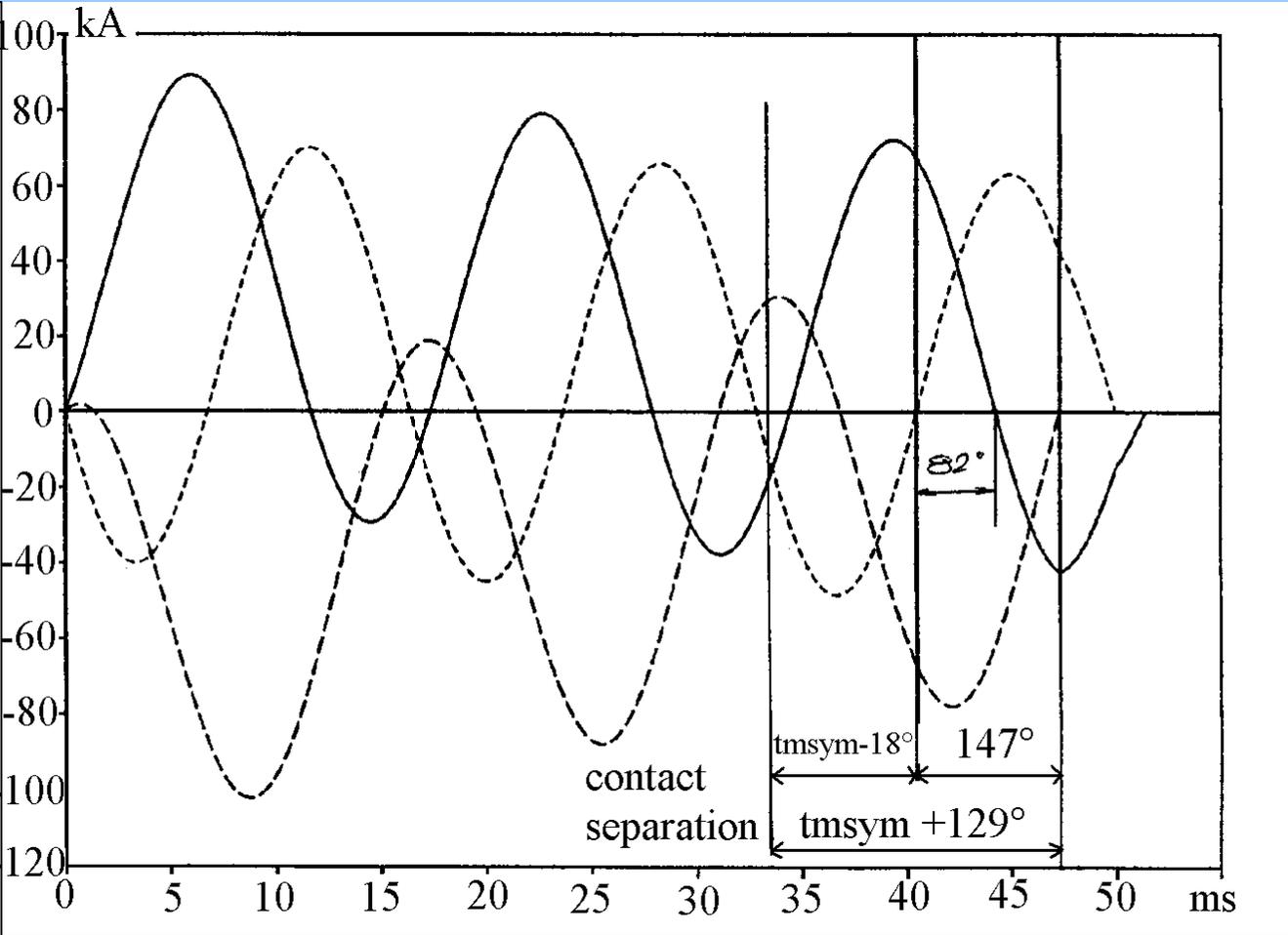**Asymmetrical currents during 3-phase short-circuit interruption of 40 kA-60 Hz by 3-cycle circuit breaker with  $k_{pp}=1.3$ . Interruption of the first pole to clear factor after a major loop.**



**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS****NETWORKS WITH GROUNDED NEUTRAL**


Case 2 : interruption by the 2nd pole to clear after a major loop of current with the required asymmetry.

The second pole must interrupt with arcing time :


$$t_1 = t_0 \text{ (minimum symmetrical) } + 155^\circ \text{ el.} \quad \text{(2 cycle c.b.)}$$

$$t_1 = t_0 \text{ (minimum symmetrical) } + 143^\circ \text{ el.} \quad \text{(3 cycle c.b.)}$$

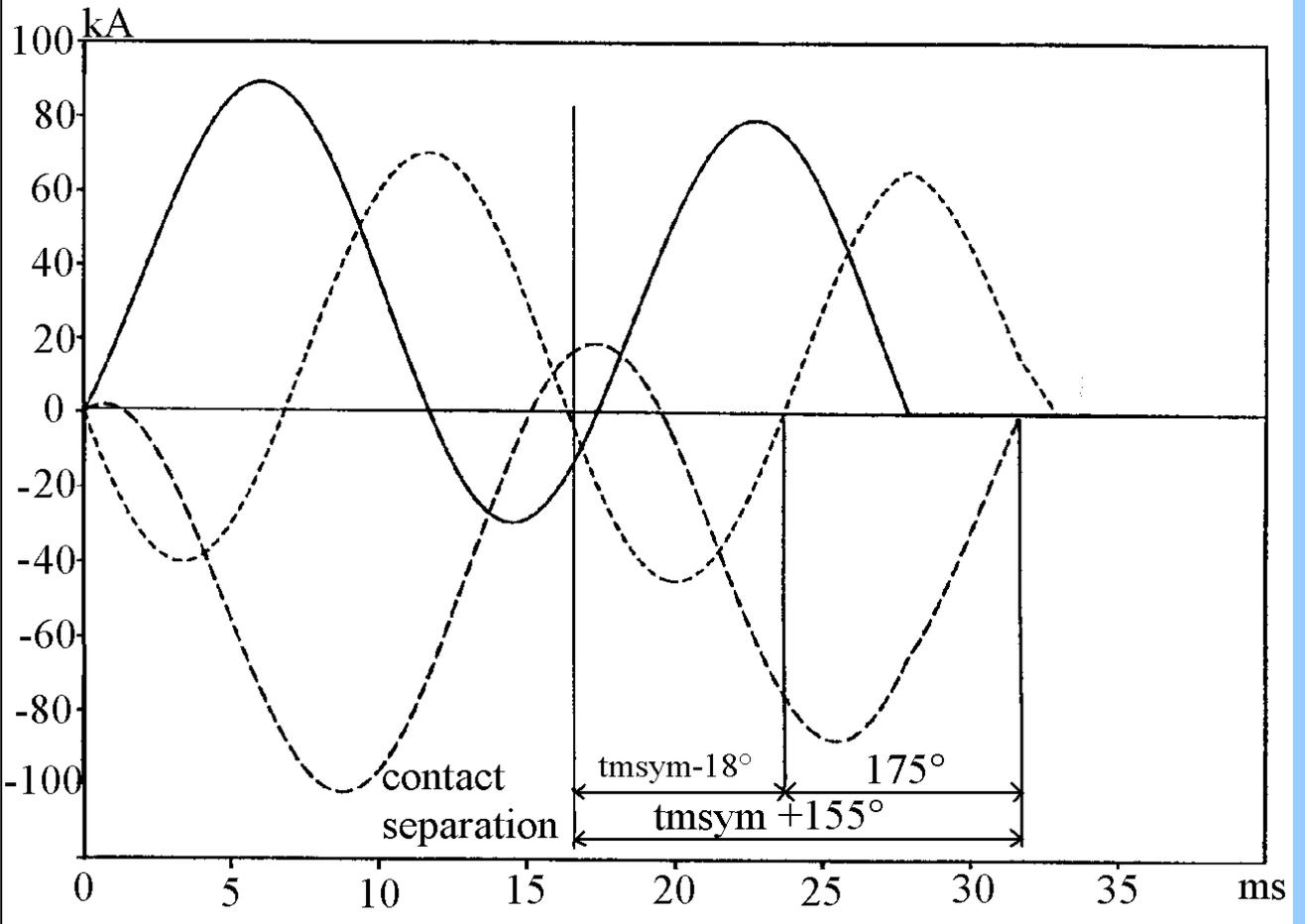**Asymmetrical currents during 3-phase short-circuit interruption of 40 kA-60Hz by 2-cycle circuit breaker with  $k_{pp}=1.3$ . Interruption after a major extended loop by the second pole to clear.**



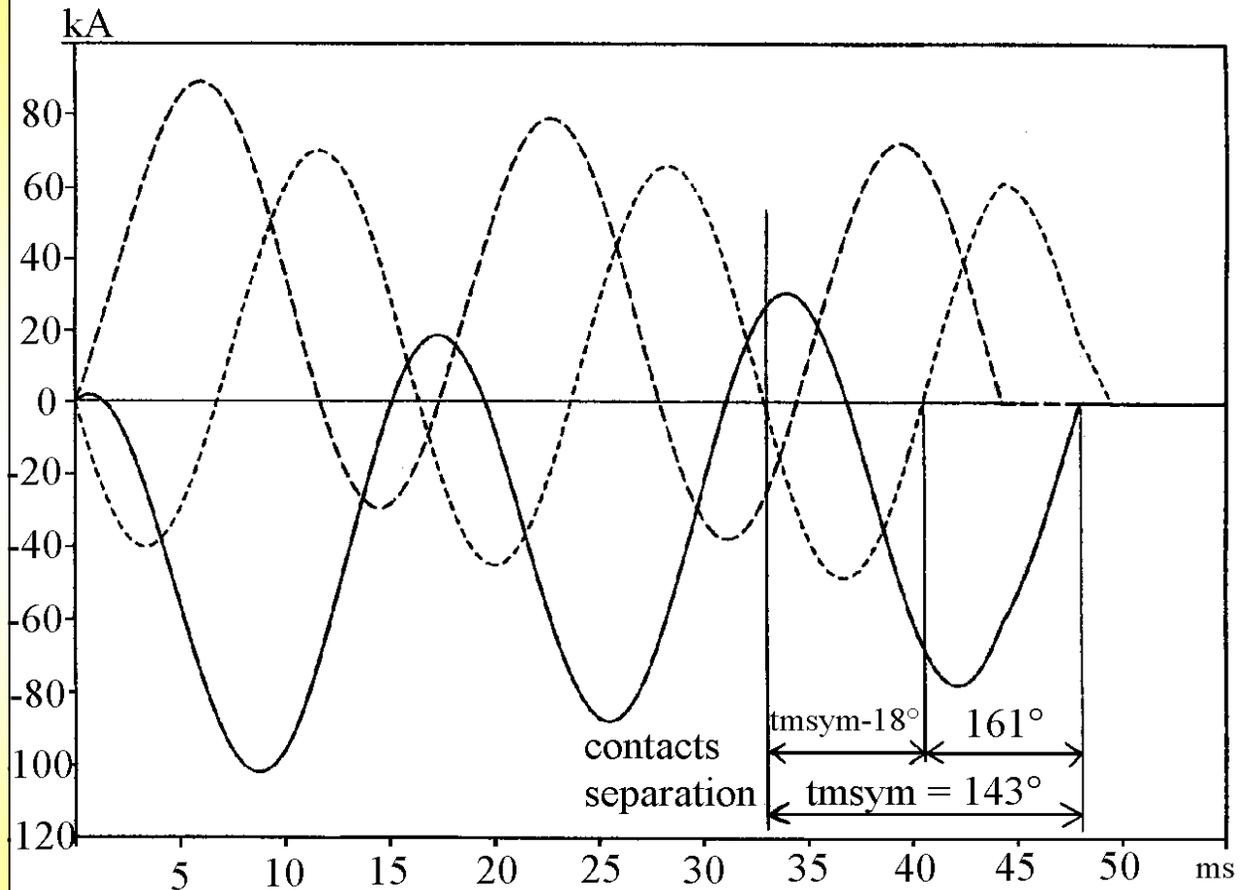**Asymmetrical currents during 3-phase short-circuit interruption of 40 kA-60Hz by 3-cycle circuit breaker with  $k_{pp}=1.3$ . Interruption after a major extended loop by the second pole to clear.**




**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS****NETWORKS WITH UNGROUNDED NEUTRAL**

- testing of 1st pole to clear after a major loop of current : same as with grounded networks
- testing of 2nd pole to clear after a major extended loop of current with the same method:


maximum arcing time =  $t_0 + 163^\circ$  el. (2 cycle c.b.)

$t_0 + 153^\circ$  el. (3 cycle c.b.)

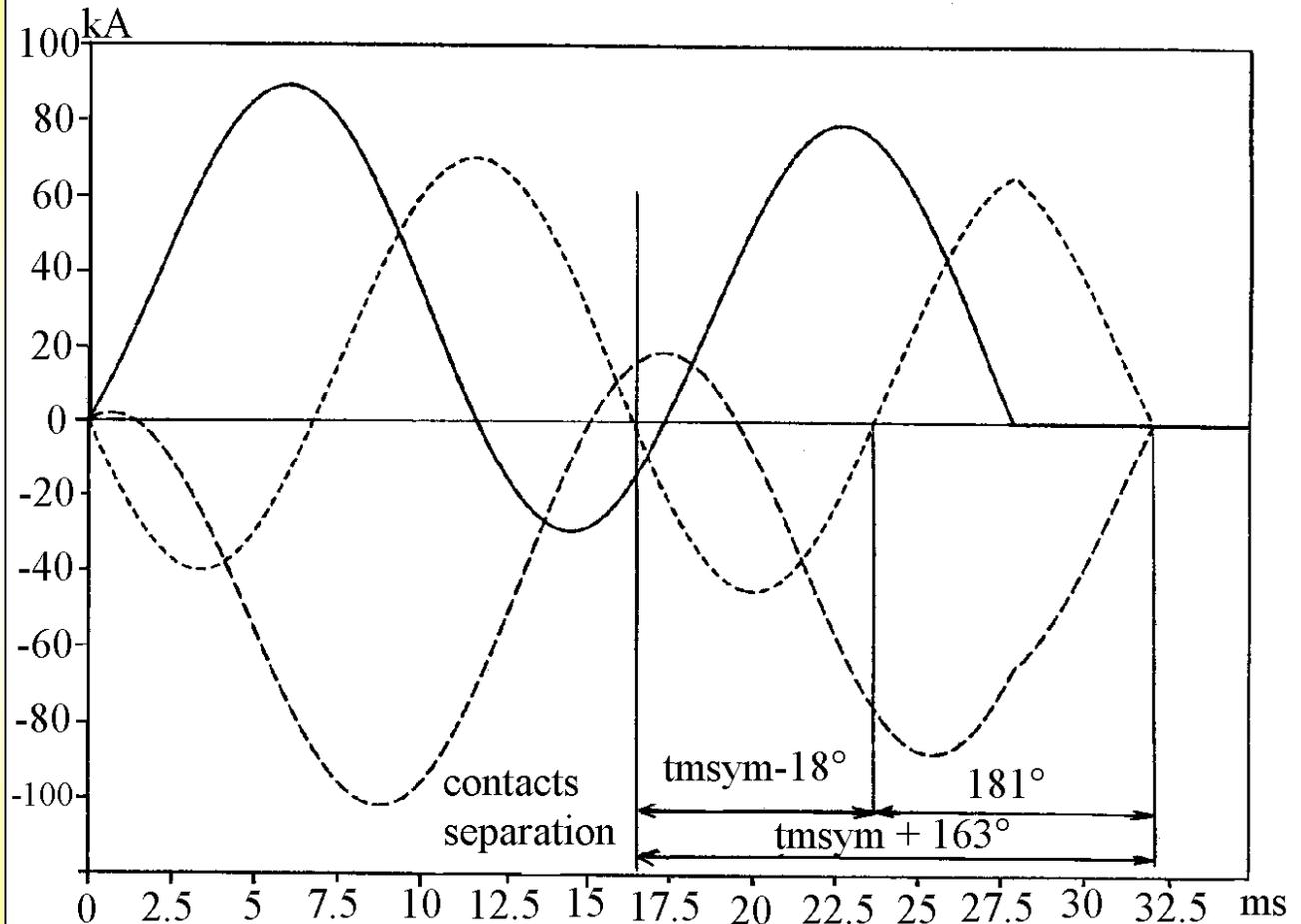**Asymmetrical currents during 3-phase short-circuit interruption of 40 kA-60Hz by 2-cycle circuit breaker with  $k_{pp}=1.5$ . Interruption after a major extended loop by the second pole to clear.**



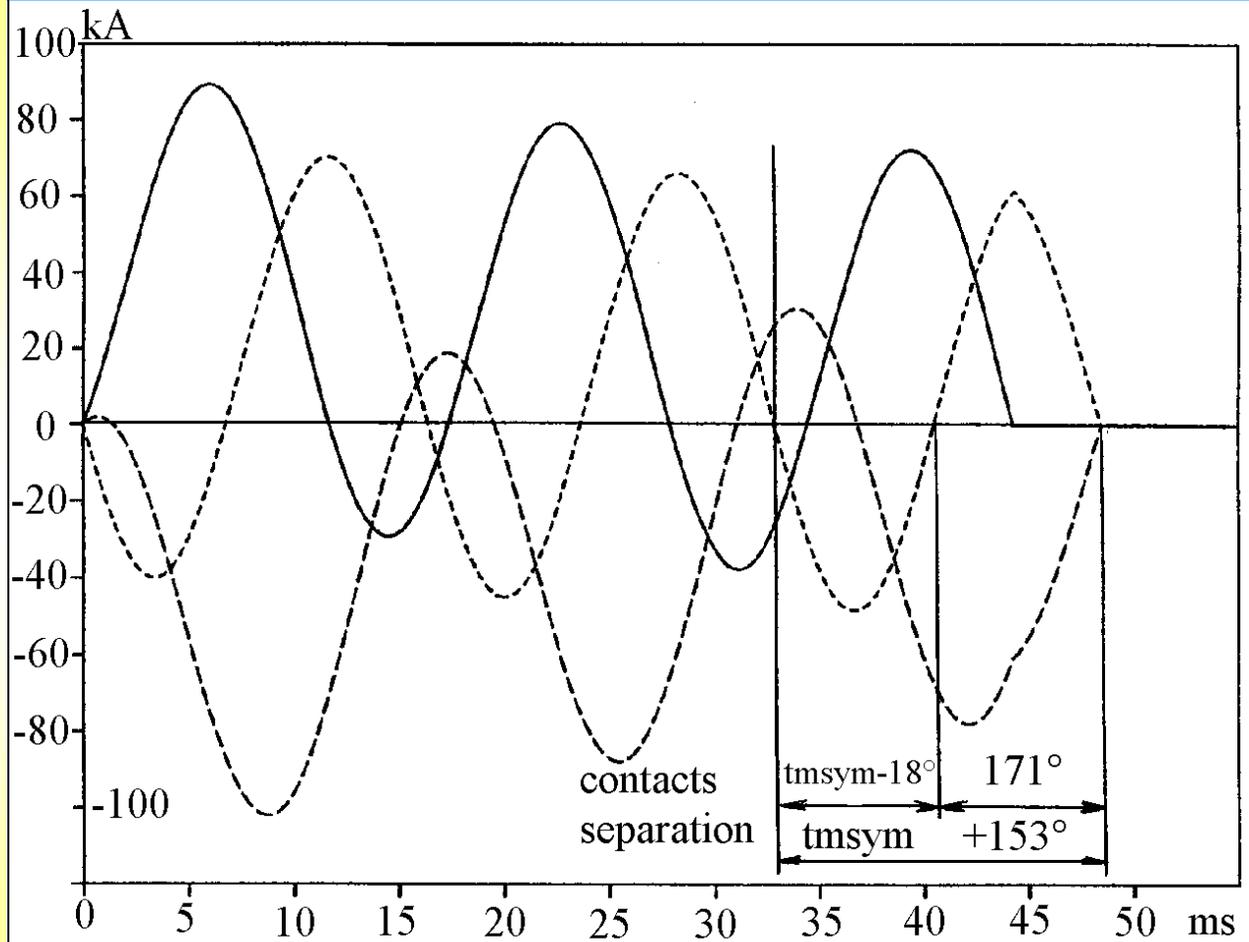**Asymmetrical currents during 3-phase short-circuit interruption of 40 kA-60Hz by 3-cycle circuit breaker with  $k_{pp}=1.5$ . Interruption after a major extended loop by the second pole to clear.**



**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS****APPLICATION TO STANDARDS**

a) 1 test with interruption of 1st pole to clear after a major loop of current and required asymmetry:

arcing time =  $t_{\min \text{ sym.}} + 60^\circ \text{ el.}$

if the circuit-breaker fails to interrupt do (b) and (c)

if the circuit-breaker interrupts do (c) and (d)

b) repeat (a) with arcing time =  $t_{\min \text{ sym.}} + 135^\circ \text{ el.}$

the circuit-breaker must interrupt after the major loop or the subsequent minor loop.

**THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE  
CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS**

c) 1 test with interruption of the 2nd pole to clear after a major extended loop and required asymmetry:

arcing time =  $t_{msym} + 150^\circ$  el. (grounded neutral)

arcing time =  $t_{msym} + 160^\circ$  el. (ungrounded neutral)

d) when (a) and (c) are both successful, a 3rd test is done to verify that (c) is the condition with the longest arcing time contact separation is advanced by  $30^\circ$  el.

1st pole must interrupt at a previous current zero (after a symmetrical or minor loop).


## THREE-PHASE SHORT-CIRCUIT TESTING OF HIGH-VOLTAGE CIRCUIT-BREAKERS USING SYNTHETIC CIRCUITS

### CONCLUSION :

- a standard method is needed for 3-phase synthetic testing of HV circuit-breakers : no IEC or IEEE/ANSI procedure today.
- a method is proposed to demonstrate interruption in the most severe cases.
  - It is strongly encouraged that the IEEE Switchgear Committee should take the lead in standardizing a test procedure.

**THREE-PHASE SHORT-  
CIRCUIT TESTING OF  
HIGH-VOLTAGE  
CIRCUIT-BREAKERS  
USING SYNTHETIC  
CIRCUITS**

**IEEE #  
PE-052-PWRD-0-03-  
1999**

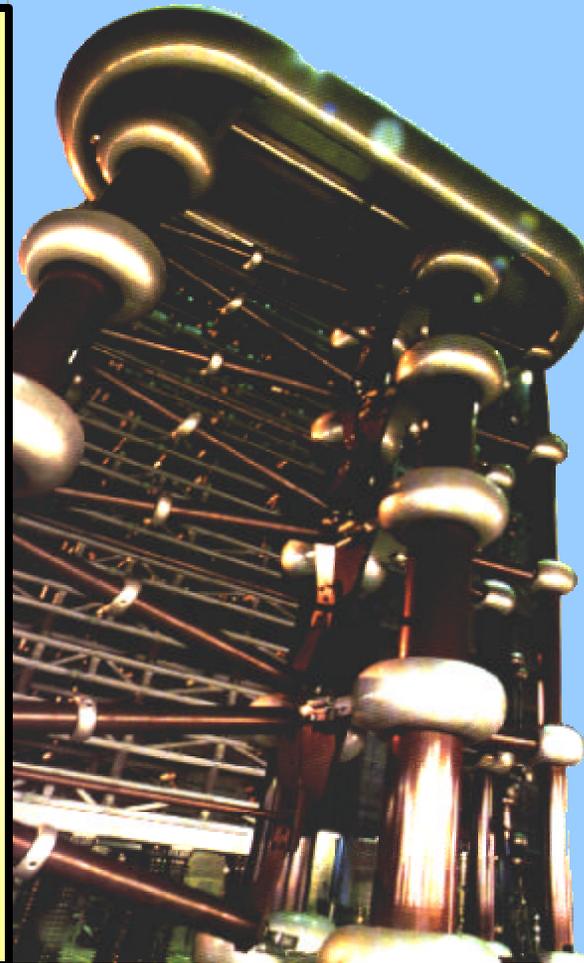

TRANSMISSION & DISTRIBUTION  
High Voltage Switchgear

IEEE Switchgear Meeting  
Charleston, May 1999 Slide # 34